
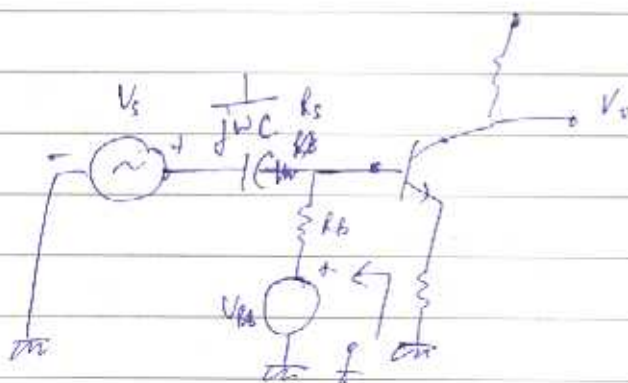


$$\begin{aligned} \text{Max } I_E &= 100 \times 7.5 \text{ mA} \\ &= 0.75 \text{ Amp.} \end{aligned}$$

$$\text{Min } R_L = \frac{7.5 - 0.7}{0.75 \text{ Amp.}} = 9.07 \Omega$$

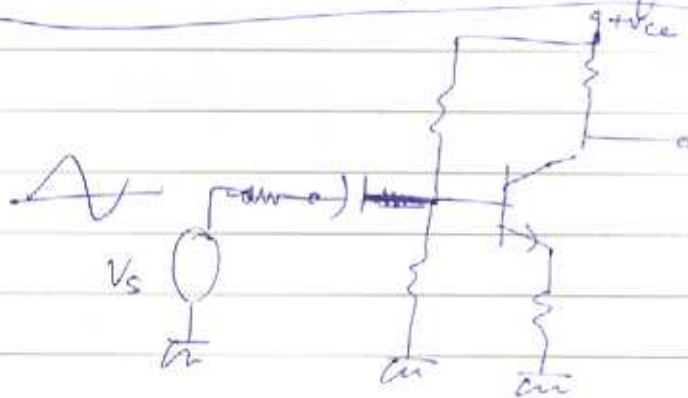Constant voltage source for $R_L > 9.07 \Omega$



Around operating point
if I_B is varied
this will cause
variation in I_C
hence in V_{CE}

$$\frac{V_s - V_{BE}}{R_s + R_B + \frac{1}{j\omega C}} \times R_L + V_{BB} = V_o + V_s'$$



$$\frac{(V_s - V_{BE}) j\omega C R_L}{j\omega C (R_s + R_B) + 1} + V_{BB} = V_o + V_s'$$

$$V_{BB} \left(\frac{-j\omega C R_L + 1 + j\omega C R_s + j\omega C R_B}{1 + j\omega C (R_s + R_B)} \right) = V_o + V_s'$$

$$V_o = \frac{V_{in} \left(\frac{1 + j\omega C R_s}{1 + j\omega C (R_s + R_o)} \right)}$$

$R_s \gg R_o$ then $V_o = V_{in}$
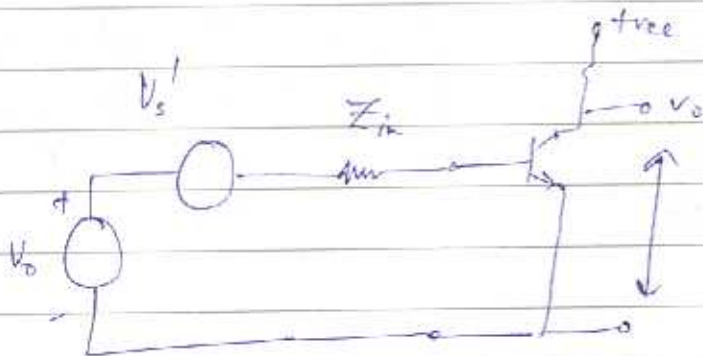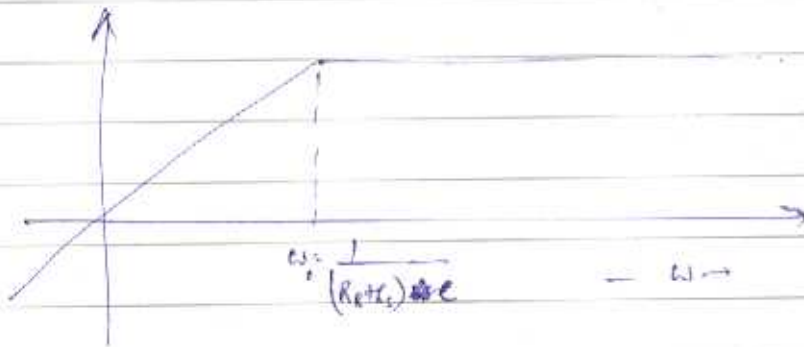
$$V_s' = \frac{V_s \cdot j\omega C R_o}{1 + j\omega C (R_o + R_s)} \quad \left. \vphantom{V_s'} \right\} \text{high pass function}$$







Operational amplifier -

Commonly Versatile Integrated device.

One get it in ± 74 packaged IC form


Example IC 741.

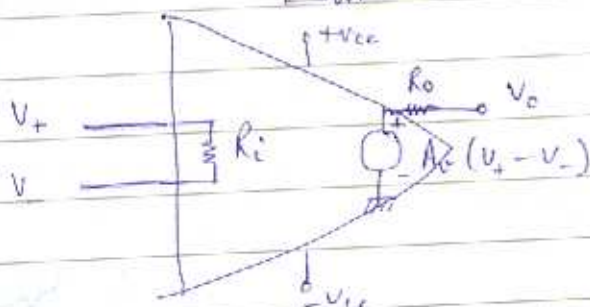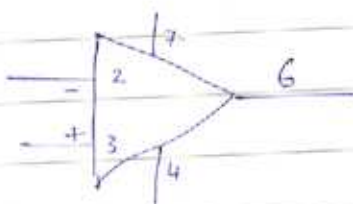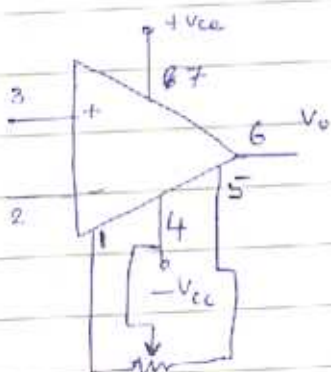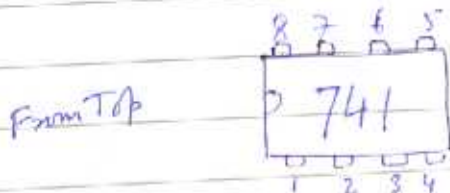


R_i is very large

A_v is very large

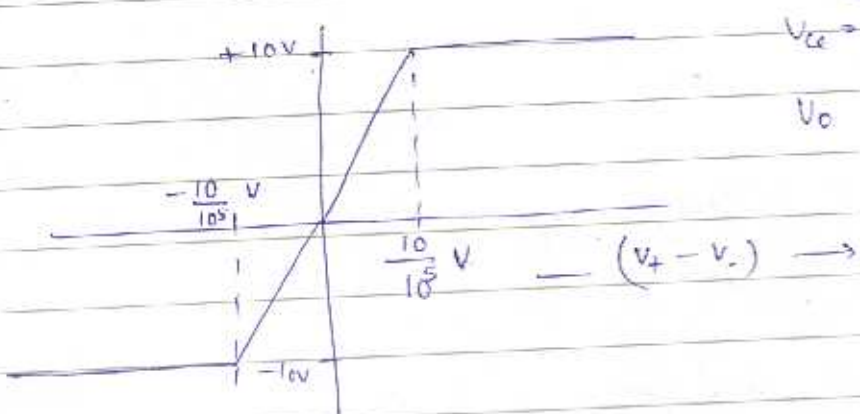for ideal op-amp
 Can be assumed $\infty \Omega$.
 R_o is very small $\sim 0 \Omega$.
 100,000 (10^5 for 741).
 $R_i = 2 M\Omega$, $R_o = 75 \Omega$



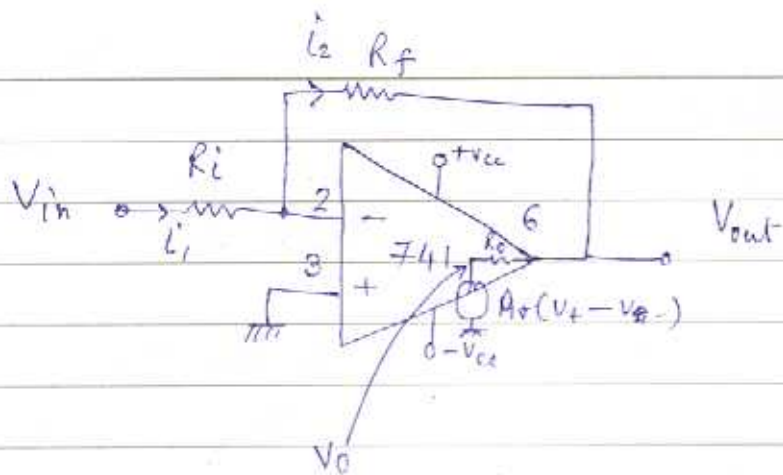

$$\frac{V_{in} - V_-}{R_i} = i_1 \quad \text{--- (1)}$$

$$i_2 = \frac{V_- - V_{out}}{R_f} \quad \text{--- (2)}$$

$$i_1, V_-, i_2, V_{out}$$

$$R_f' = R_f + R_o$$

$$(0 - V_-) A_v = V_{out} \quad \text{--- (3)}$$

$$i_1 - i_2 = \frac{V_-}{R_i} \quad \text{--- (4)}$$

As R_i is very large.

$$i_1 - i_2 \approx 0$$

$$i_1 = i_2$$

Assuming op-amp
operating in linear
region

The above equations
not valid in saturation
and linear region.

$$-V_- A_v = V_{out} \quad \text{--- (1)}$$

$$\frac{V_{in} - V_-}{R_i} = \frac{V_- - V_{out}}{R_f} \quad \text{--- (2)}$$

$$\frac{V_{in} - V_-}{R_i} = i_1 \quad \text{--- (3)}$$

Using (1) and (2)

$$\left(V_{in} + \frac{V_{out}}{A_v} \right) \frac{1}{R_i} = \left(-\frac{V_{out}}{A_v} - V_{out} \right) \frac{1}{R_f}$$

$$\frac{V_{in}}{R_i} = -\frac{1}{R_f} \left(\frac{1}{A_v} + \frac{R_f}{R_i A_v} + 1 \right) V_{out}$$

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= -\frac{R_f}{R_i} \left(\frac{A_v + 1}{A_v} \right) \left(\frac{A_v}{1 + A_v} \right) \left(\frac{A_v}{A_v + 1 + \frac{R_f}{R_i}} \right) \\ &= -\frac{R_f}{R_i} \left(\frac{1}{1 + \frac{1 + \frac{R_f}{R_i}}{A_v}} \right) \end{aligned}$$

$A_v \sim \text{large} \cdot (10^5)$


$A_v \gg \frac{1 + \frac{R_f}{R_i}}{A_v}$ Then \Rightarrow $\frac{V_{out}}{V_{in}} \sim -\frac{R_f}{R_i}$

$$V_- = V_{in} \left(-\frac{R_f}{R_i} \right) \frac{1}{A_v}$$

as A_v is very large $V_- \sim 0$.

In the above circuit

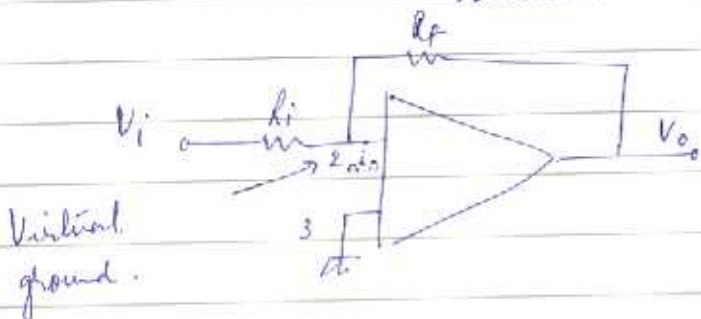
Potential at V_- and V_+ are almost same.



For most of the circuits this is true.

- $R_i \gg R_i, R_f$
- $A_v \gg 2$
- $A_v \gg R_f/R_i$
- $R_f \gg R_o$

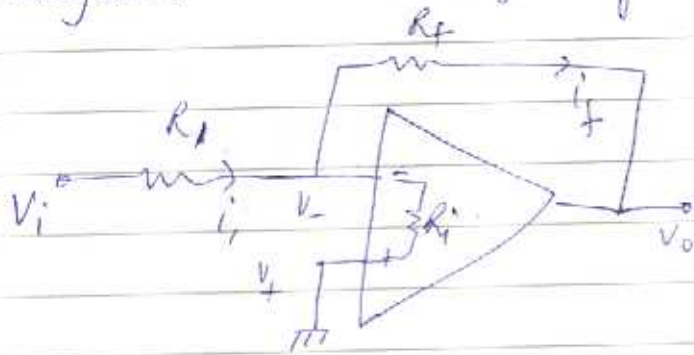Subjective Understanding why this happens.



because $V_o = -A_o V_-$



$$\begin{aligned}
 I_f \uparrow & \quad \text{because} \quad \frac{V_- - V_o}{R_f} \\
 & = \frac{V_- + A_o V_-}{R_f} \\
 & = (1 + A_o) \frac{V_-}{R_f}
 \end{aligned}$$

Current through $R_i \approx 0$ as R_i is very large.




Change in V_i , i_1 is fixed increases ~~change~~ V_- leading to
~~change~~ I_f change in I_f


This increase I_1 reducing V_-

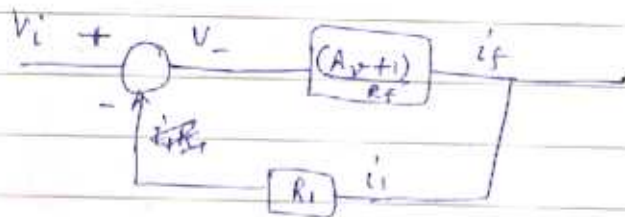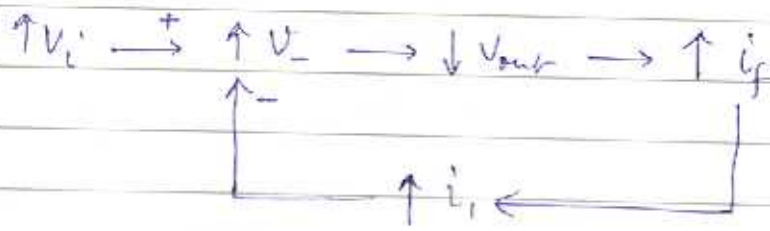

-ve feedback

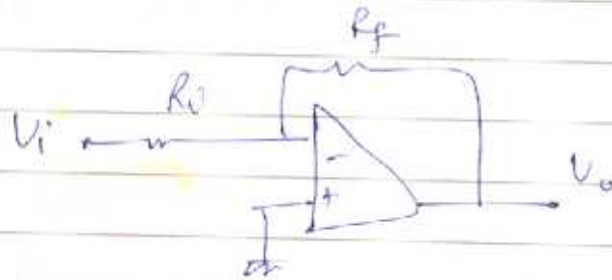


$$\frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

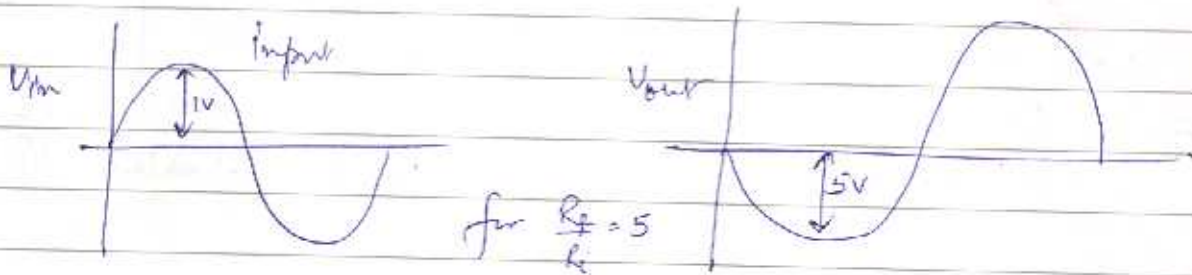


Always $V_{out} \leq V_{cc}$

for $\frac{R_f}{R_i} = 12$


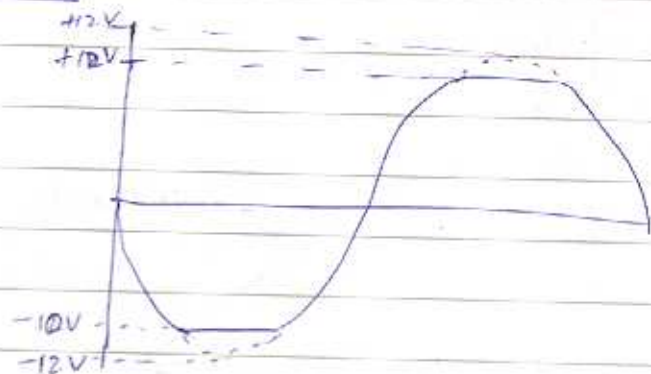


CARR

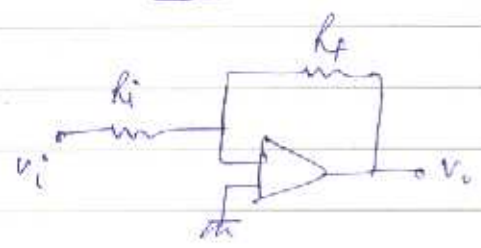




$$V_i = V_p \sin(\omega t)$$
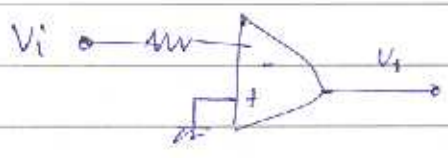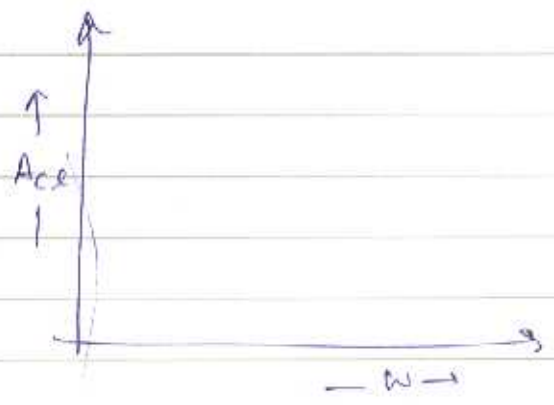
$$V_o = V_p [A_{ce}] \sin(\omega t + \phi)$$



open loop
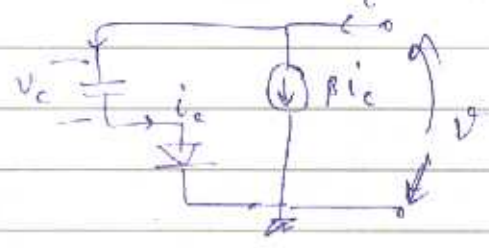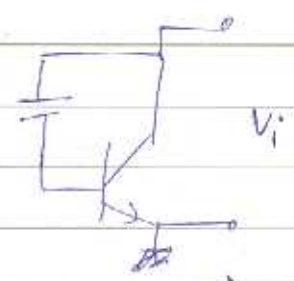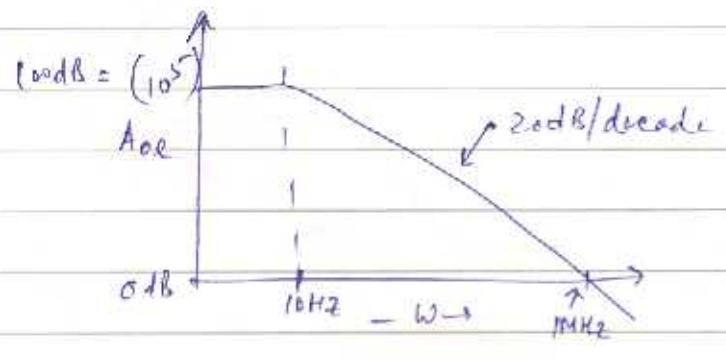
$$\frac{V_o(\omega)}{V_i(\omega)} = A_d$$



$$C \frac{dV_c}{dt} = i_c$$

$$i = i_c + \beta i_c = (1 + \beta) i_c$$

$$V_c + V_b = 0$$


$$C \frac{d(V_c + V_b)}{dt} = i_c$$

$$i = (\beta + 1) C \frac{dV}{dt}$$

Effective capacitance $(\beta + 1) C$

show -ve feedback work.


DATE.....

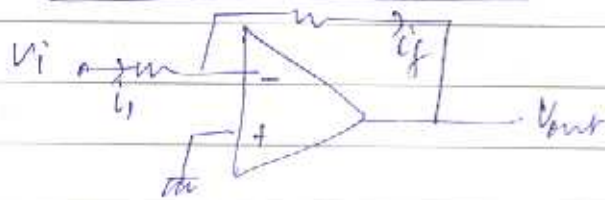

V_i is at $\omega \gg 10 \text{ Hz}$

Req. 100 Hz

A_{ol} is small.

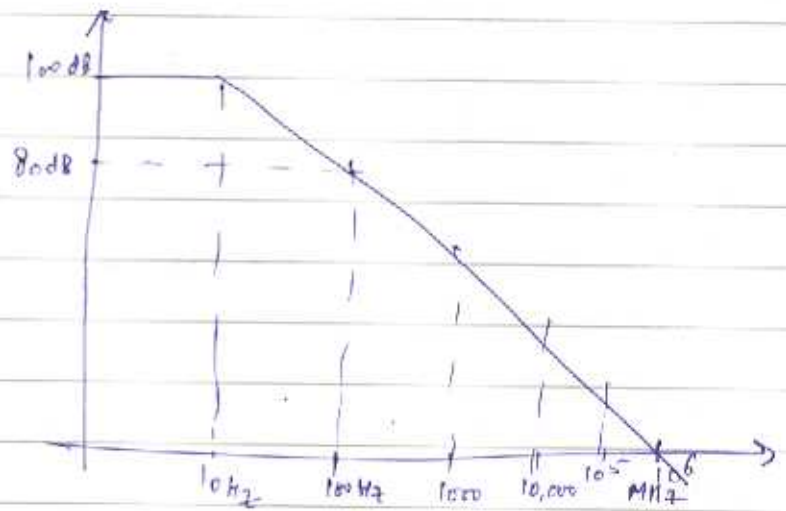

$$A_{ol} = 10^4$$

$$= 10^{(80/20)}$$

due to smaller A_{ol} , $|V_{out}|$ is smaller hence it is high (less -ve)

but

This causes drop in f_c and thus drop in i_i

and hence increase in V_- , this leading to increase in V_{out} .

-ve feedback Compensates for reduction of A_{ol} .

$$\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_i} \left(\frac{A_{ol}}{1 + A_{ol}} \right) \left(\frac{1}{1 + \frac{(1+R_f/R_i)}{A_{ol}}} \right)$$


A_{ol} is still ^{much} larger than $\frac{(1+R_f/R_i)}{A_{ol}}$

$$\frac{V_{out}}{V_{in}} \approx -\frac{R_f}{R_i}$$

When $A_{vo} = 1 + \frac{R_f}{R_{in}}$, then cut off for

A_{cl} happens

At $f_{ce} \neq$, $A_{cl} = 1 + A_{ce}$

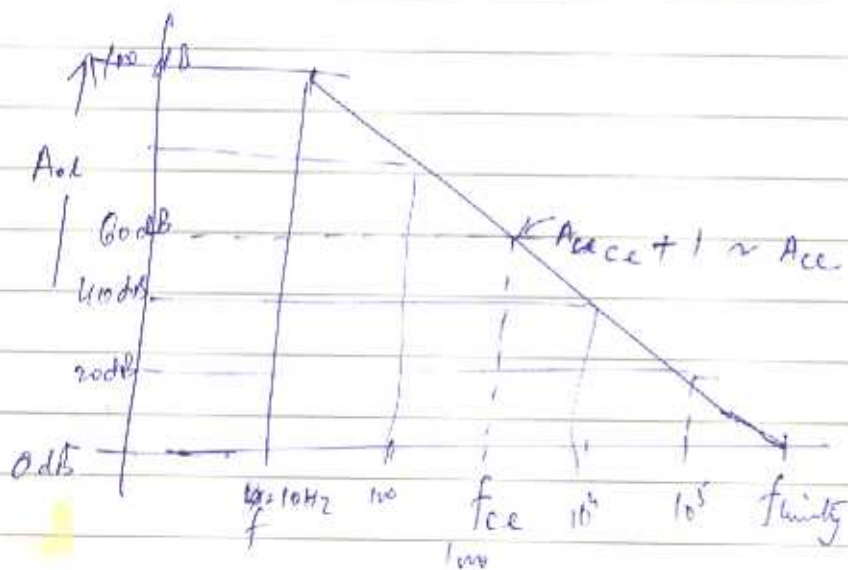

20dB/decade

$$20 \log \frac{A_{ce} + 1}{1} = 20 \left(\log \left(\frac{f_{unity}}{f_{ce}} \right) \right)$$


$$\frac{f_{unity}}{A_{ce} + 1} = f_{ce}$$

As usually $A_{ce} > 10$ in practical cases.

$$f_{unity} = 10 \text{ MHz}$$

with gain of 1000 $f_{ce} = \frac{10^6}{10^3} = 10^3 \text{ Hz}$

Non inverting amplifiers.

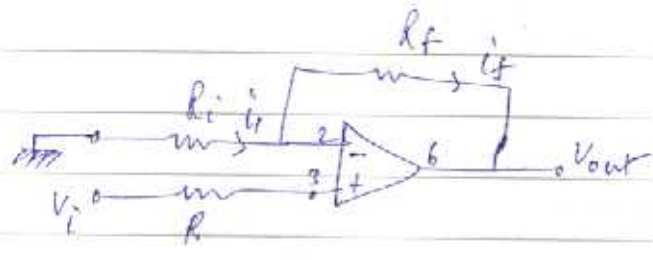

Since no current is flowing into ^{pin} 3,
 R is immaterial for in the circuit.

$$V_+ = V_i$$

$$-(V_- - V_+) \approx (V_- - V_i) A_v = V_{out}$$

$$\Rightarrow V_- = \frac{-V_{out} + A_v V_i}{A_v} = -\frac{V_{out}}{A_v} + V_i$$

$$i_1 \approx i_f$$

$$V_o = V_- - R_f i_f$$

$$0 - i_f R_i = V_-$$

$$V_{out} = -i_f R_i - R_f i_f$$

$$V_{out} = -(R_i + R_f) i_f$$

$$V_{out} = + (R_i + R_f) \frac{V_-}{R_i}$$

Thus ~~$V_- = \frac{(R_i + R_f) V_-}{R_i} + V_i$~~

$$\frac{V_{out} R_i}{R_i + R_f} = -\frac{V_{out}}{A_v} + V_i$$

~~$$V_- \left(1 - \frac{R_i + R_f}{R_i} \times \frac{1}{A_v} \right) = V_i$$~~

$$V_{out} \left(\frac{R_i}{R_i + R_f} + \frac{1}{A_v} \right) = V_i$$

$$\frac{V_{out}}{V_{in}} = \frac{R_i + R_f}{R_i \left(1 + \frac{R_i + R_f}{R_i A_v} \right)}$$

When $A_v \gg \frac{R_i + R_f}{R_i}$

Then $\frac{V_{out}}{V_{in}} \approx \frac{R_i + R_f}{R_i}$

When $A_{ol} = \frac{R_i + R_f}{A_{cl} R_i}$, thereafter the A_{cl} drops.

$$f_{cl} \approx \frac{f_{unity}}{A_{cl}}$$

$$f_{cl} \times A_{cl} = f_{unity}$$

$$\frac{-V_{out}}{(R_f + R_i)} = I_f$$


$$V_- = -I_f R_i = + \frac{V_{out} R_i}{R_f + R_i}$$

$$V_- = V_{in}$$

Both - and + terminals will have same voltage due to feedback.

Differential amplifier
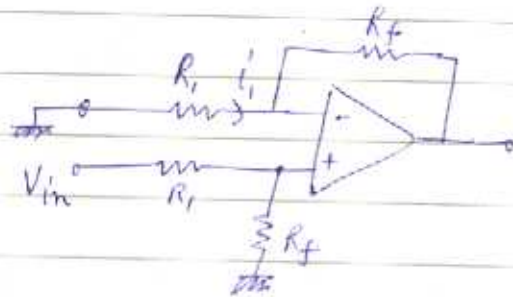
$$(V_{in1} - V_{in2}) G = V_{out} \quad \Rightarrow$$



$$V_+ = \frac{V_{in} R_f}{R_i + R_f}$$

Due to -ve feedback


V_- and V_+ will be same.

$$i_i = - \frac{V_{in} R_f}{R_i + R_f} \times \frac{1}{R_i}$$

$$V_{out} = 0 - \frac{V_{in} R_f}{R_i + R_f} \times \frac{R_f}{R_i} - \frac{V_{in} R_f}{R_i + R_f} \times \frac{1}{R_i} \times R_f$$

$$= - \frac{V_{in} R_f}{R_i + R_f} \left(1 + \frac{R_f}{R_i} \right)$$

$$V_{out} = - V_{in} \frac{R_f}{R_i}$$

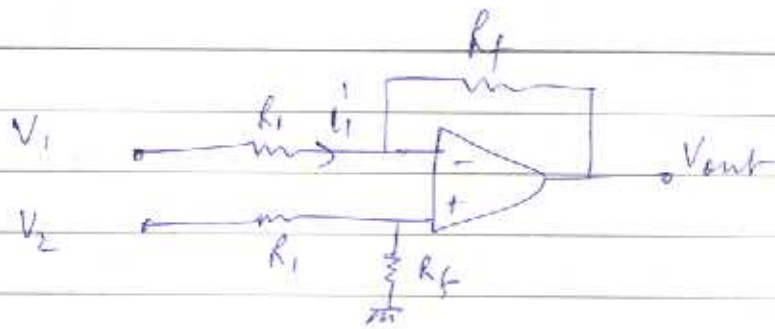

$$V_+ = \frac{V_2 R_f}{R_1 + R_f}$$

$$V_- = \frac{V_2 R_f}{R_1 + R_f} \Rightarrow i_1 = \left(V_1 - \frac{V_2 R_f}{R_1 + R_f} \right) \frac{1}{R_1}$$

$$V_{out} = V_1 - i_1 R_1 - i_1 R_f$$


$$= V_1 - i_1 (R_1 + R_f)$$

$$= V_1 - \left(V_1 - \frac{V_2 R_f}{R_1 + R_f} \right) \frac{(R_1 + R_f)}{R_1}$$


$$= V_1 - V_1 \left(\frac{R_1 + R_f}{R_1} \right) + \frac{V_2 R_f}{R_1}$$

$$= -V_1 \frac{R_f}{R_1} + V_2 \frac{R_f}{R_1}$$



$$= (V_2 - V_1) \frac{R_f}{R_1}$$

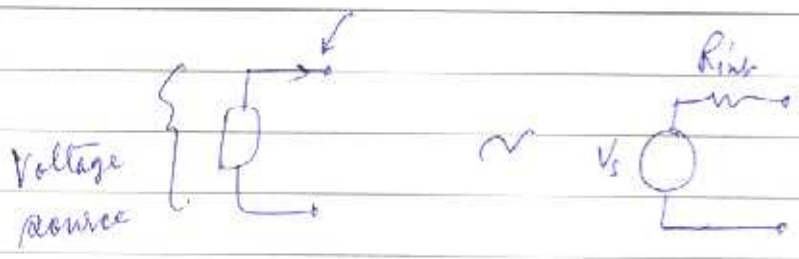

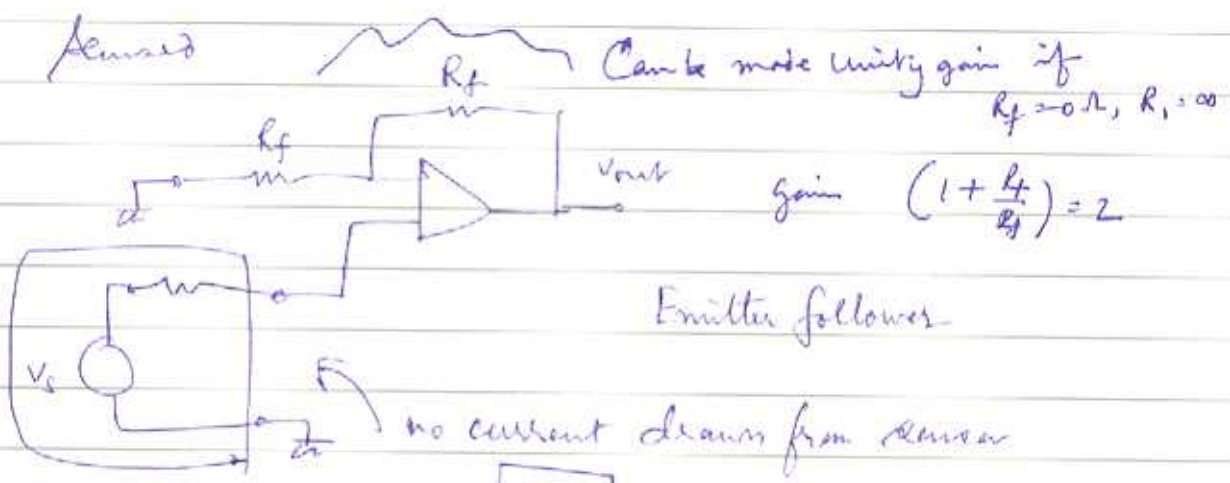Without drawing any current voltage need to be sensed




Emitter follower

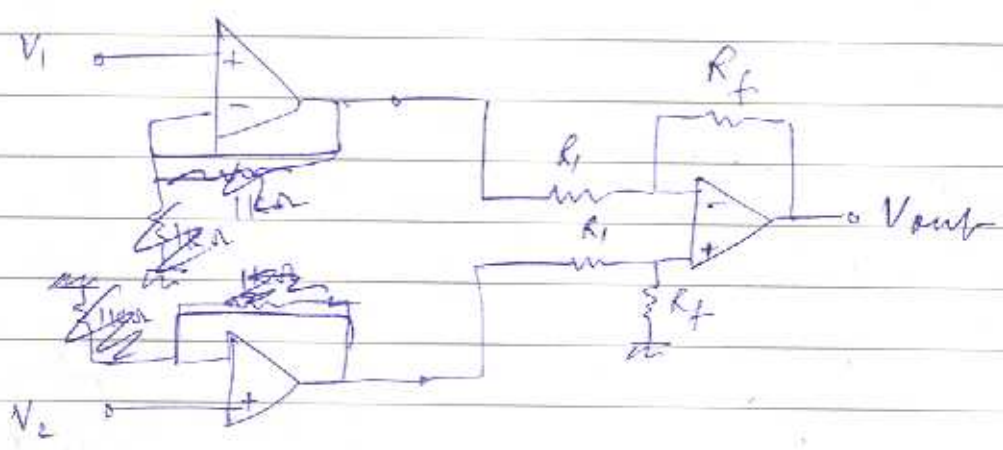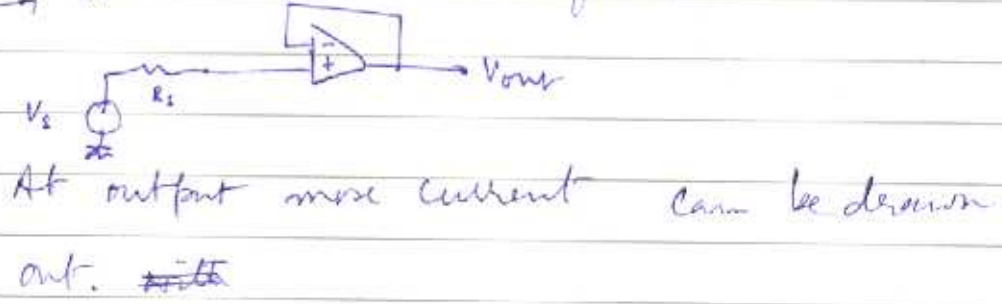

$$V_{out} = (V_2 - V_1) \frac{R_f}{R_1}$$

Instrumentation amplifier.

Integrator

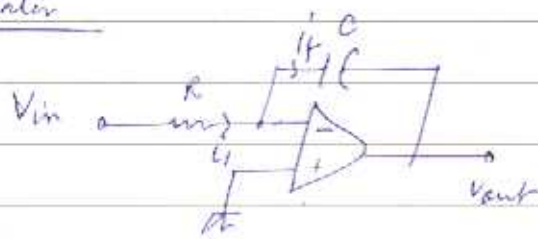

V_- is virtually grounded.


$$i_f = \frac{V_{in}}{R} = i_f$$

$$-C \frac{dV_{out}}{dt} = -i_f = \frac{V_{in}}{R}$$

$$V_{out} = -\int_0^t \frac{V_{in}}{RC} dt$$

$$\text{gain} = \frac{1}{RC}$$

Differentiator

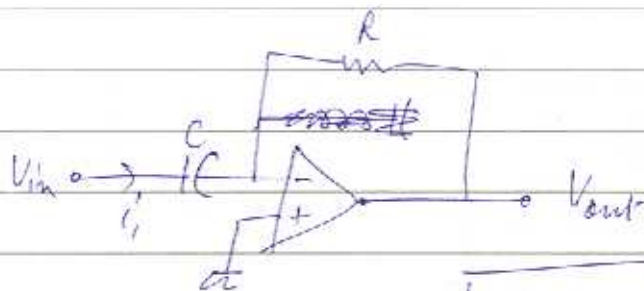


$$i_f = C \frac{dV_{in}}{dt}$$

$$V_{out} = -i_f R$$

$$V_{out} = -RC \frac{dV_{in}}{dt}$$



Adder
Subtractor

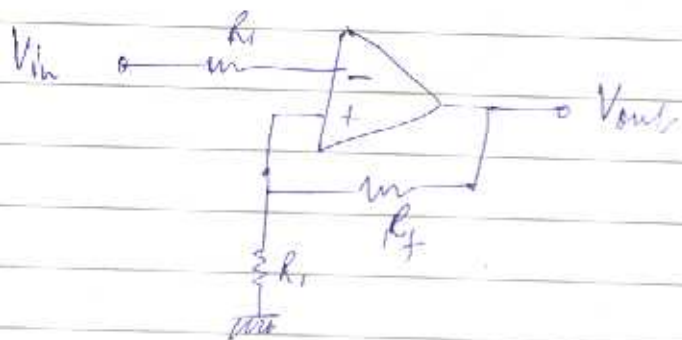


$$V_+ = \frac{V_{out} \times R_1}{R_1 + R_f}$$

When $V_{in} < V_+$, $V_{out} = +V_{cc}$ and $V_+ = \frac{V_{cc} R_1}{R_1 + R_f}$

When $V_{in} > \frac{V_{cc} R_1}{R_1 + R_f}$, then $V_{out} = -V_{cc}$


and V_+ changes to $-\frac{V_{cc} R_1}{R_1 + R_f}$

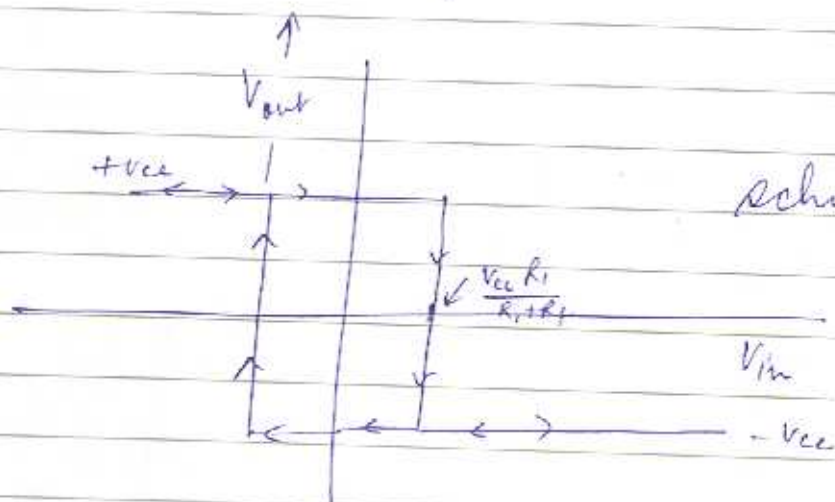Now any further decrease of V_{in} will not change the V_{out} till $V_{in} < -\frac{V_{cc} R_1}{R_1 + R_f}$



Schmitt trigger.

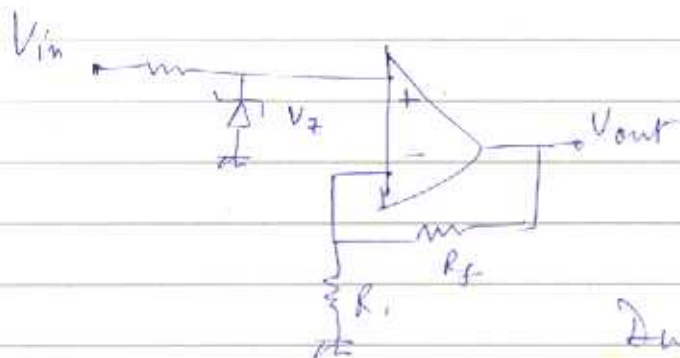Voltage Reference (typical for large voltage)




Due to negative feedback

$$V_- = V_+$$


$$\frac{V_{out}}{R_i + R_f} \times R_i = V_- = V_+$$

$$V_{out} = \left(\frac{R_i + R_f}{R_i} \right) V_z$$
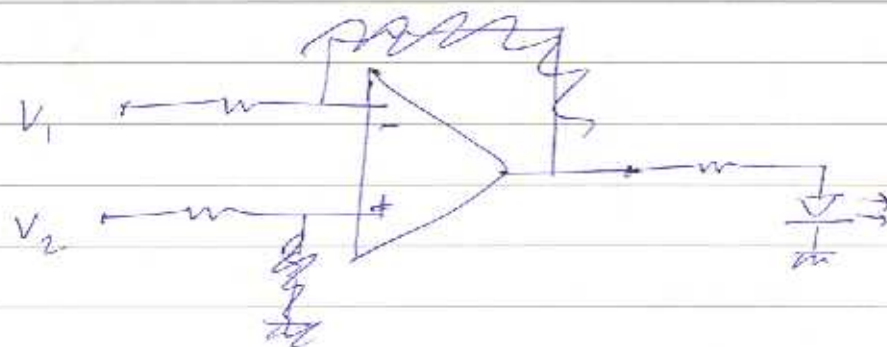
$$V_{out} = \left(1 + \frac{R_f}{R_i} \right) V_z$$



V_1 is reference, when V_2 crosses V_1 , ^{LED} light should glow.

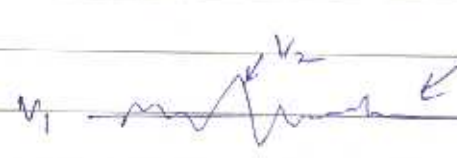v_1  v_2 This will cause flickering of LED.

If instead of LED a relay is used it will chatter.

To reduce this effect.

hysteresis is introduced (using +ve feedback).



This is schmitt trigger.



Closed loop gain unity
phase shift = 2π

Barkhausen
Criterion

Then oscillations will happen.

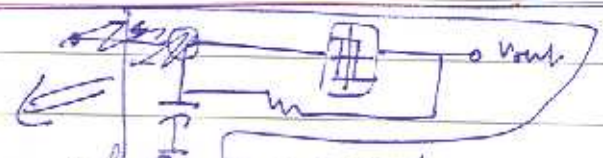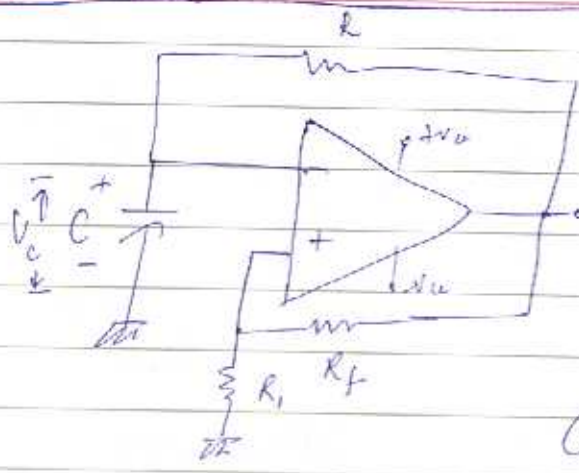

When Capacitor has no charge $v_c = 0$
 $v_{out} = +V_{cc}$
Capacitor will start charging.

When it is charged upto $\frac{V_{cc} R_1}{R_1 + R_f}$, then


$$V_{out} = -\frac{V_{cc} R_1}{R_1 + R_2} - V_{cc}, \quad V_2 = -\frac{V_{cc} R_1}{R_1 + R_2}$$

now Capacitor will start discharging till

it gets charged in reverse direction

$$t_0 = \frac{-V_{cc} R_1}{R_1 + R_2}$$

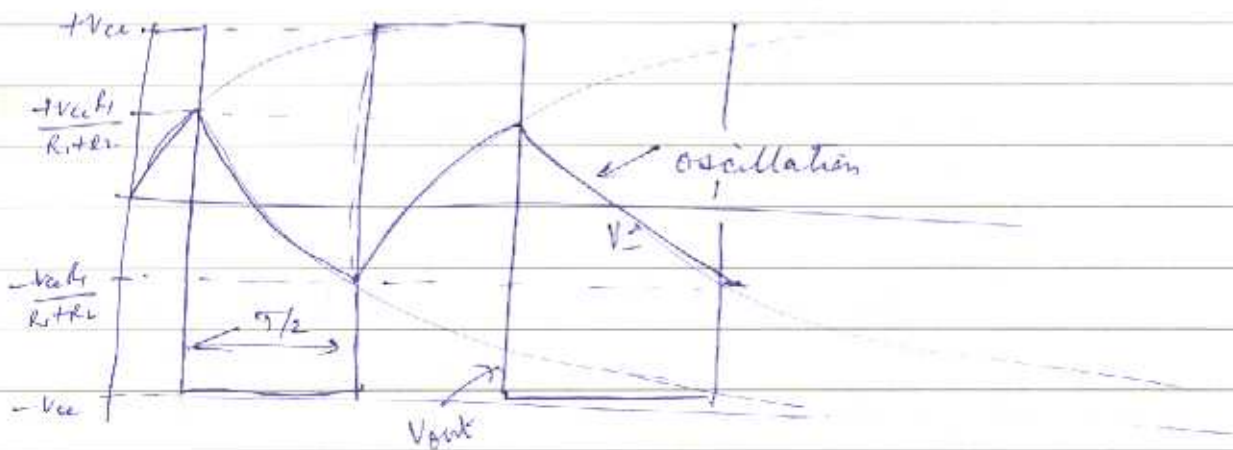At that again V_{out} will change to $+V_{cc}$.



⇒ astable multivibrator

⇒ Monostable multivibrator

⇒ Bistable multivibrator

$$-\frac{V_{cc} R_1}{R_1 + R_2} = -V_{cc} + \left(\frac{V_{cc} R_1}{R_1 + R_2} + V_{cc} \right) e^{-t/\tau}$$

$$\frac{\left(V_{cc} - \frac{V_{cc} R_1}{R_1 + R_2} \right)}{\left(V_{cc} + \frac{V_{cc} R_1}{R_1 + R_2} \right)} = e^{-t/\tau}$$


$$\frac{V_{ce} R_2}{2V_{ce} R_1 + V_{ce} R_2} = \frac{R_2}{2R_1 + R_2} = e^{-t/RC}$$

$$T_{1/2} = RC \ln \left(\frac{2R_1 + R_2}{R_2} \right)$$

$$T = 2RC \ln \left(1 + \frac{2R_1}{R_2} \right)$$



CMRR ⇒

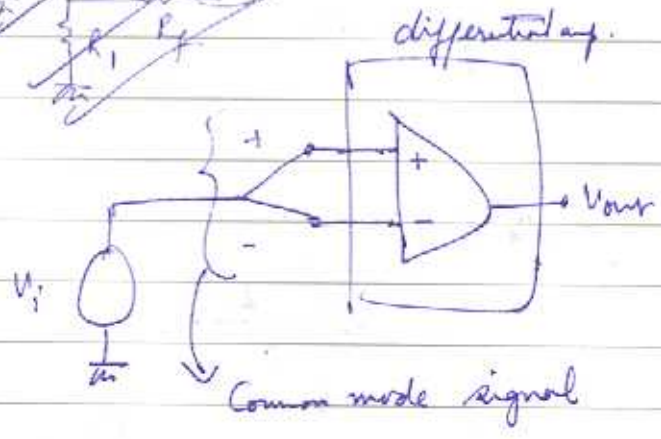


$$\frac{V_{out}}{V_{in}} = A_{cm} \leftarrow \text{Common mode gain}$$


$$\underline{CMRR} = \frac{A_{dm}}{A_{cm}} \leftarrow \text{differential mode gain}$$

Common mode rejection ratio.


(Specified in dB).

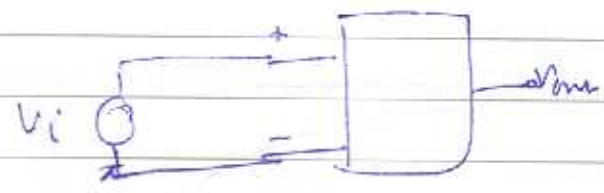

$$\frac{V_{out}}{V_{in}} = A_{dm}$$

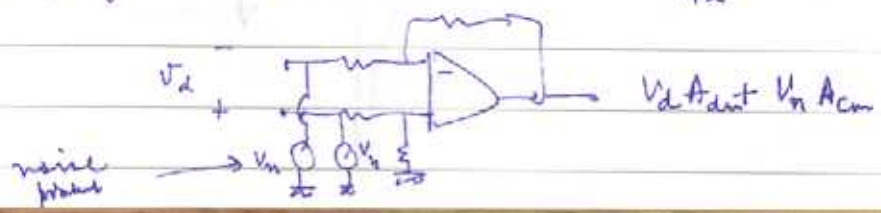

Oscillator

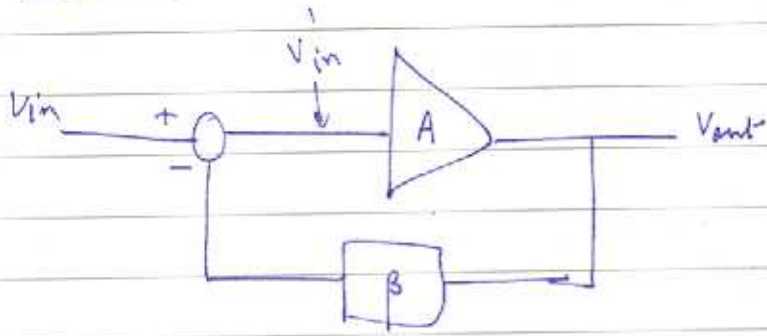

$$(V_{in} - V_{out} \beta) A = V_{out}$$

$$V_{in} A = V_{out} (1 + \beta A)$$

$$G = \frac{V_{out}}{V_{in}} = \frac{1}{A} \cdot A \cdot \frac{A}{1 + \beta A}$$

$$\left. \begin{array}{l} \text{if } \beta > 0 \\ \infty > \beta > 0 \end{array} \right\} \text{-ve feedback} \quad \begin{array}{l} 0 < G < A \\ \infty > \beta > 0 \end{array}$$


$$\left. \begin{array}{l} \text{for } \frac{-1}{A} < \beta < 0 \end{array} \right\} \text{+ve feedback}$$

$\beta A \gg 1$


$$\infty > G > A$$

$$-\infty < \beta < -\frac{1}{A}$$

$$0 > G > -\infty$$

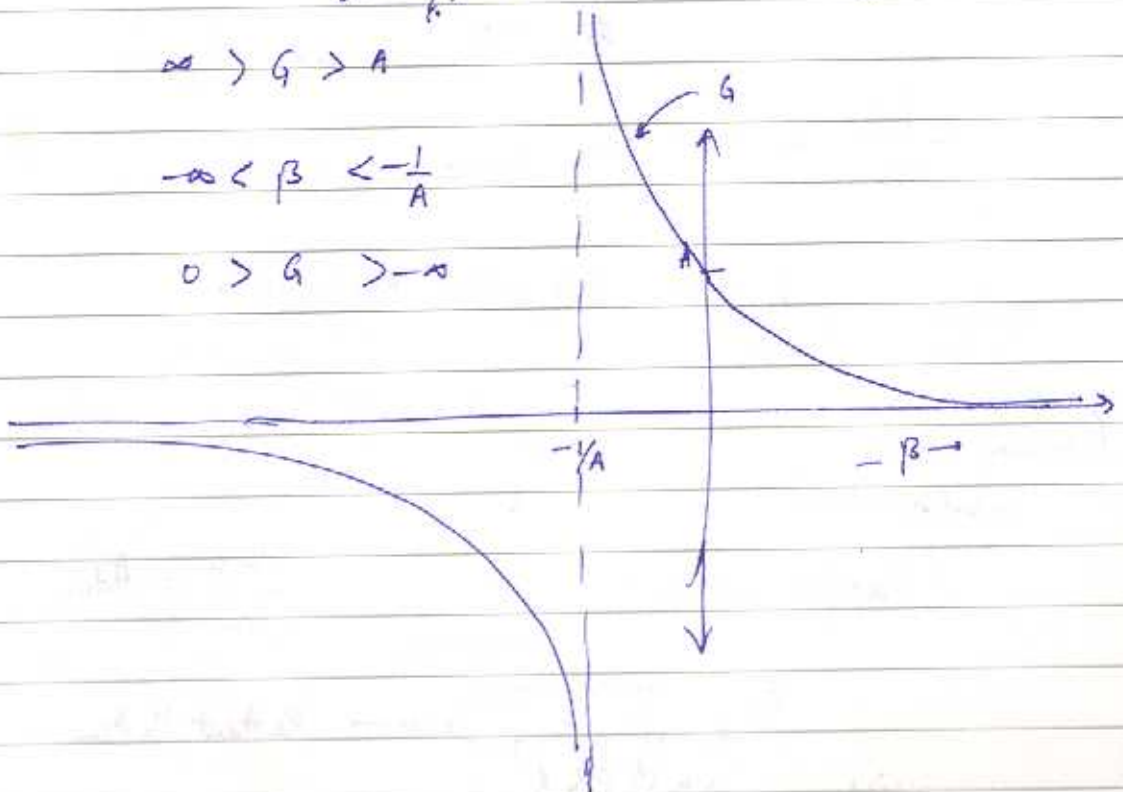



A is Constant with V_{in}'

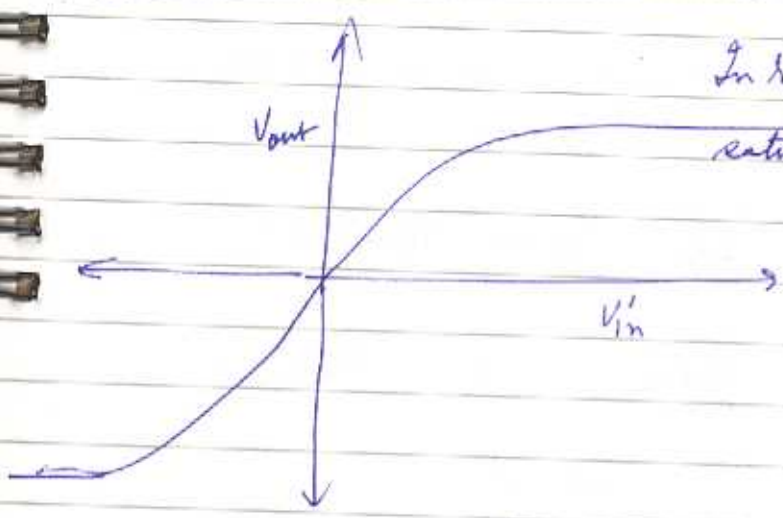

In real life. $\beta = \text{Constant}$, A is variable with V_{in}'
saturation

~~when β is constant.~~

and A is large in mag

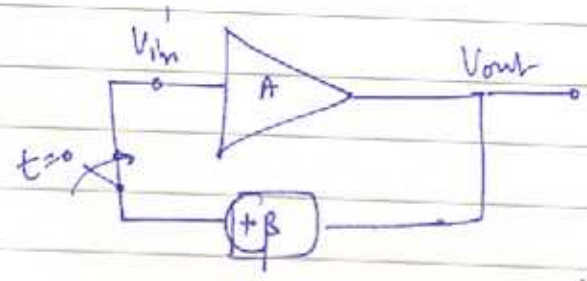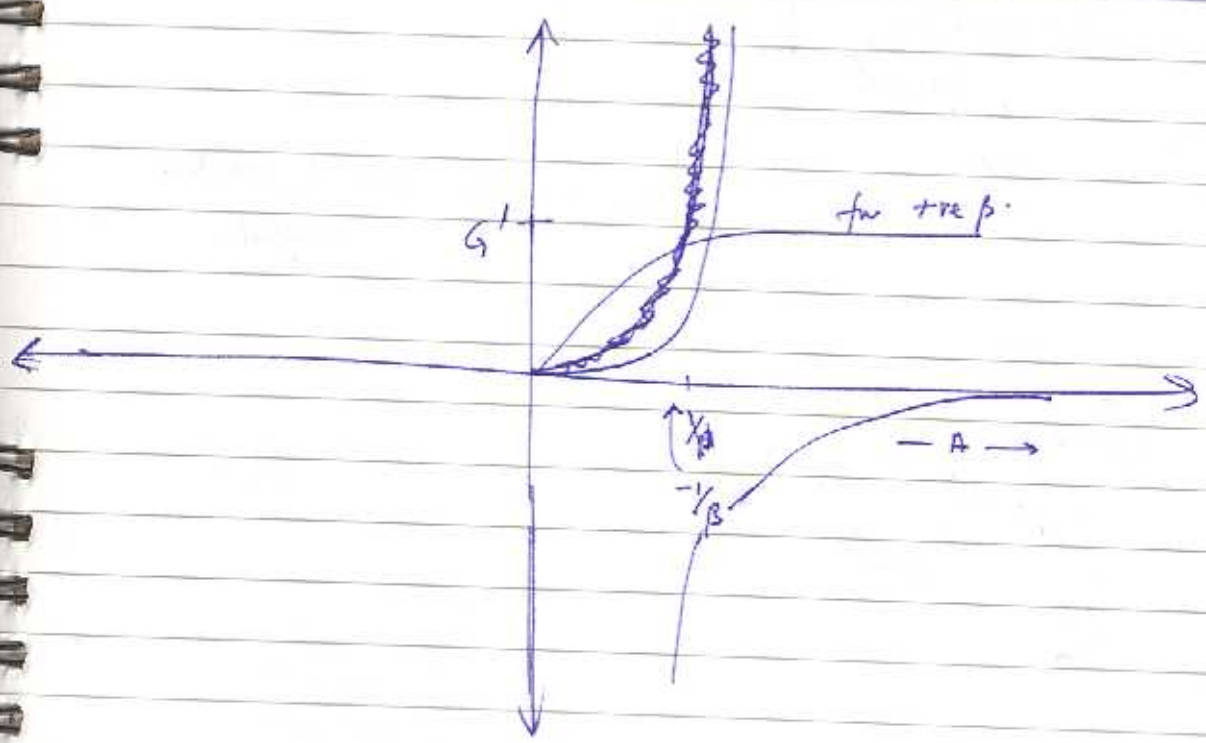

for when $A > \frac{1}{\beta}$ at $t < 0$

after $t \geq 0$

V_{out} will increase

and A will reduce till


$$A = \frac{1}{\beta}$$

Then ~~more~~ more increase is feasible.

~~A~~ and β is ~~also~~ frequency dependent.

$A(\omega) = \frac{1}{\beta(\omega)}$ // ω 's satisfying these can oscillate

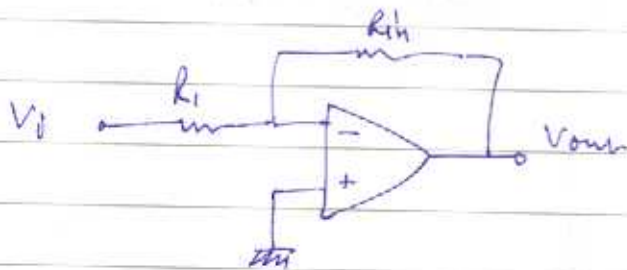phase shift in the loop should be $2\pi n$



V_{out} and V_{in} are π radians shifted.

