

Unit 3 - Week 2

Course outline

How does an NPTEL online course work?

Week 1

Week 2

- Third harmonic addition in Sine PWM
- Introduction to Space Vectors
- Space Vector PWM- Timing Calculation
- Space Vector PWM- Switching Sequence
- Space Vector PWM- Using Carriers

Quiz : Assignment 2

- Lecture slides Week 2
- Week 2 Feedback Form

Week 3

Week 4

Week 5

Week 6

Week 7

Week 8

week 9

Week 10

Week 11

Week 12

Download Videos

Assignment Solutions

Text Transcripts

Assignment 2

The due date for submitting this assignment has passed. **Due on 2020-02-12, 23:59 IST.**
 As per our records you have not submitted this assignment.

1) The main purpose of adding a third harmonic component in the reference waveform is to _____ **1 point**

- Improve harmonic profile of load voltage
- Increase the DC bus voltage utilization
- Improve harmonic profile of load current
- Reduce switching frequency of the converter

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 Increase the DC bus voltage utilization

2) A Voltage Source Converter (VSC) (shown in Fig. 1) with $V_D = 600V$ feeds a series R-L load of value $(5+j3)$ ohm/phase. What is the fundamental maximum rms load phase voltage possible if third harmonic component of magnitude $1/6^{th}$ of fundamental, is added to the reference waveform? **2 points**

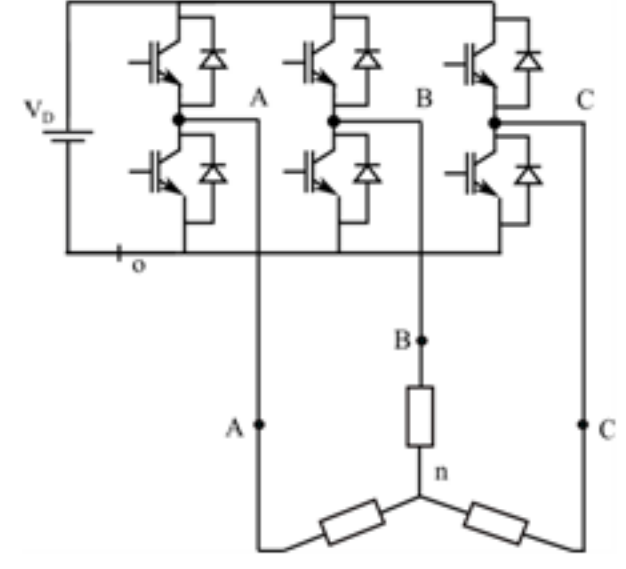


Figure 1

- 244V
- 210V
- 300V
- 600V

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 244V

3) For the condition given in question 2, what is the three phase active and reactive powers consumed by the load? **2 points**

- 100 KW and 50 KVAR
- 20 KW and 10 KVAR
- 26.25 KW and 15.75 KVAR
- 20.23 KW and 12.45 KVAR

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 26.25 KW and 15.75 KVAR

4) In question 2, the magnitude of third harmonic component present in the line voltage is _____ V.

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 (Type: String) 0

5) The magnitude and phase angle of the space vector for 011 switching combination with $V_D=700$ V DC bus is, **1 point**

- 700,180°
- 467,120°
- 467,180°
- 700,120°

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 467,180°

6) To realize the reference vector (V_R) shown in Fig. 2. The correct switching sequence for realizing space vector PWM is, **1 point**

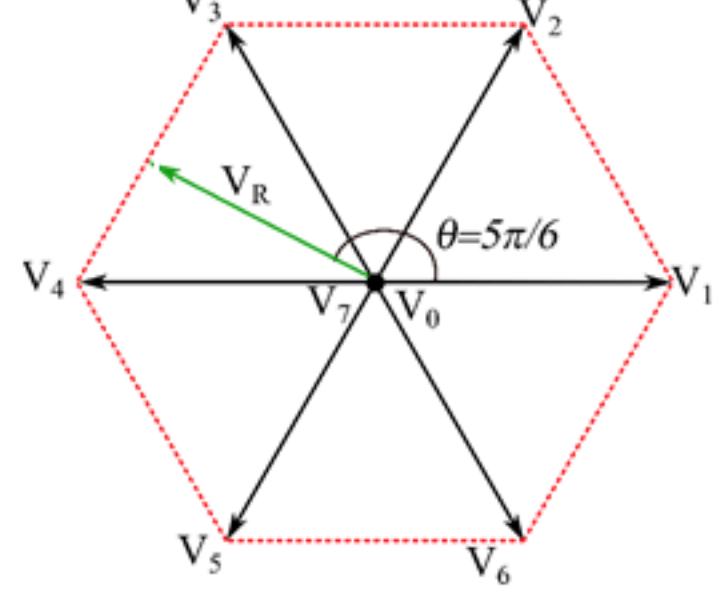


Figure 2

- 010-000-011-111-011-000-010
- 000-011-010-111-011-010-000
- 000-010-011-111-011-010-000
- 000-100-110-111-110-100-000

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 000-010-011-111-011-010-000

7) For condition given in question 6, for realizing the reference vector V_R , the timing durations of switching vectors V_3 , V_4 and zero vector are..... respectively. (Sampling time period, $T_s=200 \mu s$, $V_D=700$ V and magnitude of $V_R = 400$ V). **2 points**

- $T_1=96.7 \mu s$, $T_2=96.7 \mu s$, $T_0= 2.6 \mu s$
- $T_1=98.97 \mu s$, $T_2=98.97 \mu s$, $T_0= 2.06 \mu s$
- $T_1=99.7 \mu s$, $T_2=98.7 \mu s$, $T_0= 1.6 \mu s$
- $T_1=98.7 \mu s$, $T_2=97.7 \mu s$, $T_0= 3.6 \mu s$

No, the answer is incorrect.
 Score: 0
 Accepted Answers:
 $T_1=98.97 \mu s$, $T_2=98.97 \mu s$, $T_0= 2.06 \mu s$