

X

NPTEL

▼

Courses » Industrial Instrumentation

Announcements

Course

Forum

Progress

Mentor

## Unit 7 - Week 6

### Course outline

How to access the portal

Week 1

Week 2

Week 3

Week 4

Week 5

Week 6

● Lecture 15: LVDT

● Lecture 16: Capacitance Transducers

○ Quiz : Week 6 assignment on LVDT and Capacitance transducers

○ Week 6: Assignment Solution

Week 7

Week 8

Week 9

Week 10

Week 11

Week 12

### Week 6 assignment on LVDT and Capacitance transducers

1)

2 points

A differential parallel plate capacitive arrangement, where distance between the plates varies, is arranged in a Wheatstone bridge configuration as shown in Fig. 1(a) and 1(b).  $C_1$  is the capacitance between plates P and M and  $C_2$  is the capacitance between plate Q and M. The relative permittivity of the medium is 2.5. Common area between the plates is  $1 \text{ cm}^2$ . Nominal distance between the plates is  $d = 1 \text{ cm}$ . If  $x = 0.1 \text{ cm}$ , Find output voltage  $e_o$  if  $2 \text{ V}$  peak-to-peak sinusoidal signal ( $e_{ex}$ ) of  $2.5 \text{ kHz}$  excitation is used


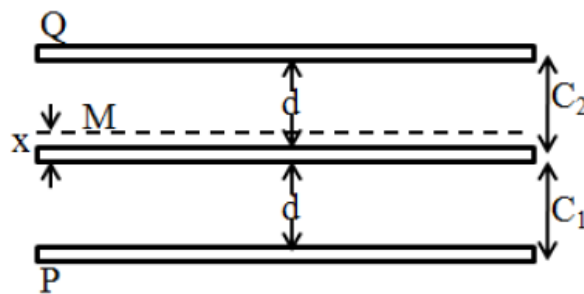


Figure 1: (a) differential capacitive sensor

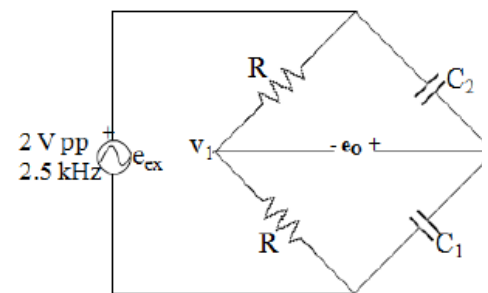

(b) Bridge circuit for differential capacitance arrangement

- a) 1 V peak-to-peak
- b) 0.1 V peak-to-peak
- c) 0.05 V peak-to-peak
- d) 2 V peak-to-peak

**Accepted Answers:**

b) 0.1 V peak-to-peak

2)

2 points

A differential capacitive arrangement, as in Figure 1(a), is used with the signal conditioning circuit, in Figure 2, to obtain output voltage  $V_O$ . If maximum non-linearity of 1% can be tolerated in output  $V_O$ , then find the largest ratio of  $\frac{x}{d}$ .

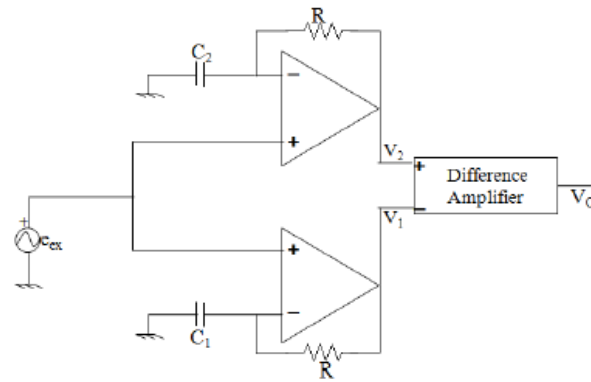


Figure 2

- a) 0.01
- b) 0.05
- c) 0.1
- d) None of these

**Accepted Answers:**

c) 0.1

3)

2 points

Find the sensitivity (assuming linear input-output relationship) of  $V_O$  with-respect-to  $x$  from the circuit in Figure 2; given  $V_{ex} = 2V$  rms at 10 kHz,  $R = 10\text{ k}\Omega$ ,  $d = 1\text{ cm}$ . (Vacuum permittivity =  $8.85 \times 10^{-12}\text{ F/m}$ )

- a) 0.056 V/m
- b) 0.112 V/m
- c) 5.6 V/m
- d) 11.2 V/m

**Accepted Answers:**

a) 0.056 V/m

4)

4 points

The following circuit, in Figure 3(b), is used with the capacitive level measurement system shown in Figure 3(a). Capacitance ( $C_h$ ) between the probe and tank well, in Figure 3(a), is given by,  $C_h = a + b \times h$ ; where, 'a' and 'b' are constants for a particular measuring liquid medium. If a 10V peak-to-peak, 10 kHz sinusoidal excitation signal is used as  $e_{ex}$ , then which of the following options is the best choice for  $R_f$ ,  $C_f$  (assuming  $C_h$  varies in the range 200 pf to 800 pf).

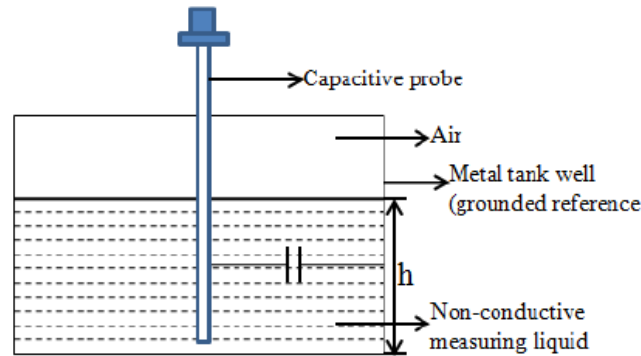


Figure 3(a)

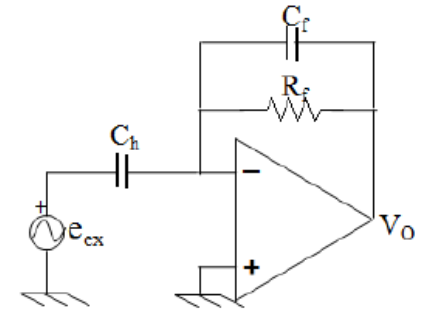


Figure 3(b)

**(Hint:** Obtain the expression for  $V_o$  in Laplace domain. Then find which of the following options is the most suitable for expressing  $V_o/e_{ex}$  as only a function of capacitances.

- a)  $R_f = 10 \text{ k}\Omega$ ,  $C_f = 1 \text{ nF}$
- b)  $R_f = 100 \text{ k}\Omega$ ,  $C_f = 10 \text{ nF}$
- c)  $R_f = 100 \text{ k}\Omega$ ,  $C_f = 470 \text{ pF}$
- d)  $R_f = 220 \text{ k}\Omega$ ,  $C_f = 100 \text{ pF}$

**Accepted Answers:**

b)  $R_f = 100 \text{ k}\Omega$ ,  $C_f = 10 \text{ nF}$

5)

2 points

**Answer questions 5 to 9 based on Figure 4**

A LVDT is to be designed with the following specifications (Refer to Figure 4):

Range of operation:  $\pm 10 \text{ mm}$ ; Maximum frequency of displacement: 1 kHz; Supply voltage: 5 rms; maximum non-linearity: 1 %; wire used for windings: 19 SWG (wire diameter: 1.016 mm)

There are 1 primary and 2 secondary windings of inner diameter  $d_i$  and outer diameter

$$d_o. \text{ Output voltage is given by, } e_o = e_1 - e_2 = \omega I_p \left[ \frac{4\pi N_p N_s \mu_o L_p \times x \left( 1 - \frac{x^2}{2L_p^2} \right)}{3 \sin\left(\frac{d_o}{d_i}\right)} \right].$$

Where,  $x$  – displacement of the core from null position;  $\omega$  – frequency of excitatic signal;  $L_p$  – current in primary winding;  $N_p$ ,  $N_s$  – number of turns in primary and seconda windings;  $\mu_o$  – permeability of free space ( $4\pi \times 10^{-7} \text{ H/m}$ ).

It is also given,  $\frac{d_i}{L_a} \cong 0.1$ ;  $\frac{d_o}{d_i} = 4$ ;  $L_a = 3L_p$ ;  $L_g \ll L_p$ .

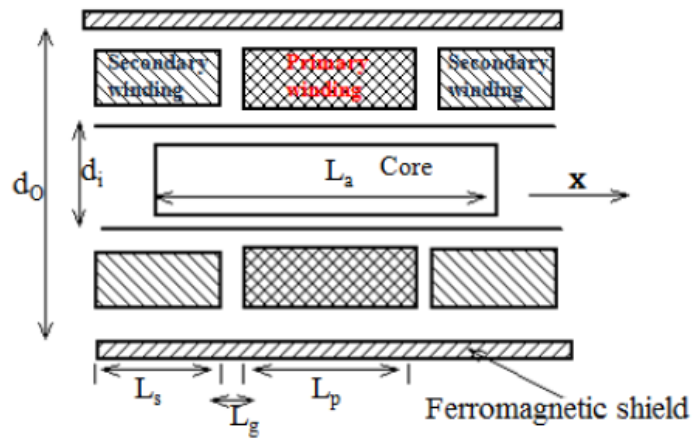


Figure 4

Find the following parameters:-

5. Length ( $L_p$ ) of the primary

(Hint: Observe the expression of  $e_o$  above and given maximum non-linearity)

- a) 500 mm
- b) 22.36 mm
- c) 44.72 mm
- d) 70.7 mm

**Accepted Answers:**

d) 70.7 mm

6)

2 points

Length ( $L_s$ ) of each of the secondary

(Hint: Find expression for  $L_s$  from different length parameters (i.e.,  $L_a$ ,  $L_p$  and  $x$ ) given in Figure 4)

- a) 8 mm
- b) 70.7 mm
- c) 80.7 mm
- d) 212.1 mm

**Accepted Answers:**

c) 80.7 mm

7) Length ( $L_a$ ) of the core.

2 points

- a) 67.08 mm
- b) 134.16
- c) 212.1 mm
- d) 500 mm

**Accepted Answers:**

c) 212.1 mm

8) Inner and outer diameter ( $d_i$  and  $d_o$ ) of the secondary.

2 points

- a) 21.21 mm, 84.84 mm
- b) 13.42 mm, 53.68 mm
- c) 26.84 mm, 107.36
- d) None of these

**Accepted Answers:**

a) 21.21 mm, 84.84 mm

9)

4 points

Number of turns ( $N_p$  and  $N_s$ ) of primary and secondary respectively.

(Hint:  $N_p = (\text{number of layers of winding in primary}) \times (\text{number of turns in each layer})$ . No. of layers depend on  $d_o$ ,  $d_i$  and wire diameter. No. of turns in each layer depends on length of primary/secondary.)

- a) 2449, 2139
- b) 2139, 2449
- c) 2319, 2944
- d) 2449, 2449

**Accepted Answers:**

b) 2139, 2449

10)

3 points

Assume the following parameter-values for an LVDT (Refer to Figure 4):

$L_p = 80$  mm,  $L_s = 100$  mm,  $\frac{d_o}{d_i} = 4$ ,  $N_p = 2000$  and  $N_s = 2500$  (meanings of the notations are same as in the previous problem)

Using the values these parameters, find out  $e_o$  for displacement of core  $x = 5$  mm, given  $I_p = 1$  mA peak current at 10 kHz frequency.

Permeability of free space ( $\mu_0$ ) =  $4\pi \times 10^{-7}$  H/m  
(Ignore sign of output, if any)

- a) 4.36 V peak
- b) 54.64 V peak
- c) 5.46 V peak
- d) 43.6 V peak

**Accepted Answers:**

a) 4.36 V peak

[Previous Page](#)
[End](#)

