

X

NPTEL

Courses » Industrial Instrumentation

Announcements

**Course**

Forum

Progress

Mentor

## Unit 4 - Week 3

### Course outline

How to access the portal

Week 1

Week 2

Week 3

- Lecture 7: Thermistor
- Lecture 8: Thermocouples
- Lecture 9: Resistance Temperature Detector
- Quiz : Week 3 Assignment on Temperature Measurements
- Week 3: Assignment Solution
- Feedback for Week 3

Week 4

Week 5

Week 6

Week 7

Week 8

Week 9

Week 10

Week 11

Week 12

### Week 3 Assignment on Temperature Measurements

1) 2 points

For a K-type thermocouple, thermoelectric voltage at 50 °C and 500 °C are 2.023 mV and 20.644 mV, respectively when the reference junction is kept at 0 °C. Thermoelectric voltage versus temperature relation is approximated as,  $e_{0-t} = a \times t + b \times t^2$ . For a certain temperature ( $t_1$ ) of the hot junction, the thermocouple shows 10 mV, with the reference junction at 25 °C. Find, the unknown temperature ' $t_1$ ' of the hot junction.

- a) 269.4 °C
- b) 278.5 °C
- c) 298.7 °C
- d) None of these

**Accepted Answers:**

a) 269.4 °C

2) 2 points

Resistance-temperature relation for a thermistor is given by,  $R = R_0 \exp \left[ \beta \left( \frac{1}{T} - \frac{1}{T_0} \right) \right]$

where 'R' is resistance of thermistor at temperature T,  $R_0$  is resistance of thermistor at temperature  $T_0$ .  $\beta = 3800$  K, is a constant for a particular thermistor. It is known that for  $T_0 = 25$  °C,  $R_0 = 1250 \Omega \pm 5\%$ . Calculate the maximum error in measurement of temperature T =  $T_1$ , if resistance R at temperature  $T_1$  is measured to be 2000  $\Omega$ .

- a) 0.98 K
- b) 1.64 K
- c) 1.11 K
- d) 1.06 K

**Accepted Answers:**

c) 1.11 K

3) Based on Figure 1., answer question (3) and (4)

2 points

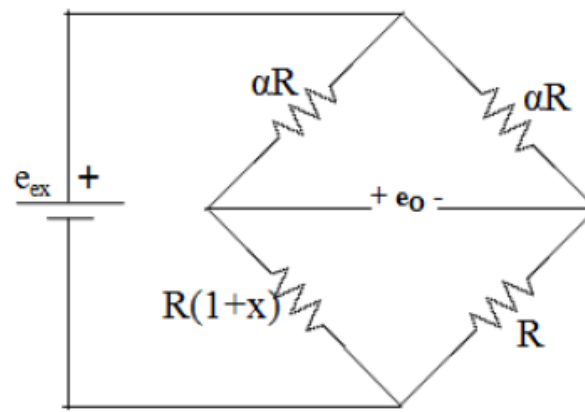


Figure 1

3)

Assume  $\alpha = 1$ , find the normalised sensitivity (of  $e_o/e_{ex}$ ) of the circuit for very small  $x$ .

- a) 0.25
- b) 0.5
- c) 0.75
- d) 1.0

**Accepted Answers:**

a) 0.25

4)

3 points

If it is required to keep the maximum non-linearity within 5 % over the range of  $x$  between 0 and 0.5, then evaluate the minimum value  $\alpha$ .

- a) 7
- b) 8
- c) 9
- d) 10

**Accepted Answers:**

c) 9

5)

2 points

If the circuit in Figure 2 is used in place of Figure 1, for RTD signal conditioning, then find out (i) the normalised sensitivity (of  $e_o/e_{ex}$ ) of the circuit with-respect-to  $x$  and (ii) maximum non-linearity of the output voltage  $V_o$ .

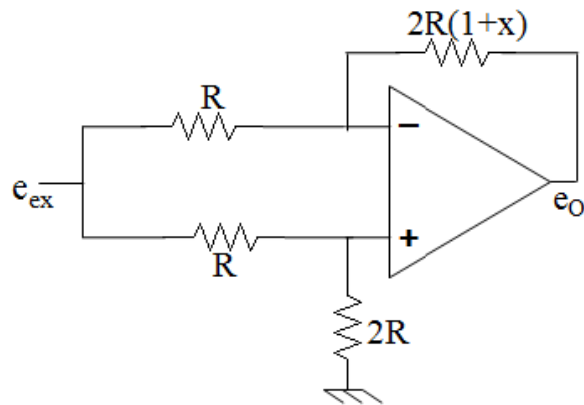


Figure 2

- a) (i) 0.25; (ii) 0 %
- b) (i) 0.67; (ii) 0 %
- c) (i) 0.5; (ii) 0.25 %
- d) (i) 0.5; (ii) 0 %

**Accepted Answers:**

b) (i) 0.67; (ii) 0 %

6)

2 points

Figure 3 shows two circuits for improving the linearity of thermistor response. If maximum allowable non-linearity is 2 %, then which of the two circuits can be used for larger input range? (Assume,  $R_1 = R_2 = R$  and  $R_T = RX(1+x)$ )

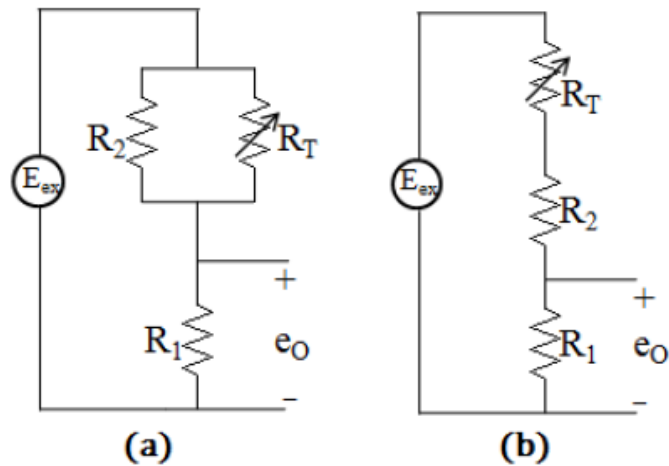


Figure 3

- a) circuit (a)
- b) circuit (b)
- c) Both have same input range
- d) Insufficient data

**Accepted Answers:**

b) circuit (b)

7)

2 points

The following circuit, in Figure 4, is used to measure temperature using a Pt-100 RTD ( $R_t$ ) (assume, 1<sup>st</sup> order resistance-temperature relation for the RTD). The constant current source provides 1 mA current. Resistances of the lead wires are,  $R_{L1} = R_{L2} = 0.6 \Omega$  and  $R_{L3} = R_{L4} = 0.7 \Omega$ . If the voltmeter shows 138.5 mV, what is the measuring temperature (Temperature coefficient of resistance  $\alpha = 0.00392 \Omega/\Omega\text{-}^\circ\text{C}$ )

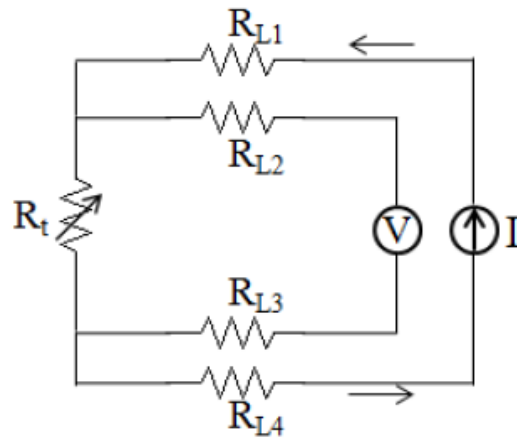


Figure 4

- a) 138.5 °C
- b) 100 °C
- c) 39.2 °C
- d) 98.2 °C

Accepted Answers:

d) 98.2 °C

8)

2 points

Figure 5 shows a parallel combination of thermocouples.  $e_1$ ,  $e_2$  and  $e_3$  are the generate thermoelectric voltages at the output of the individual thermocouples as shown in the figure. Determine the expression for voltage  $e_0$  as shown in the figure.

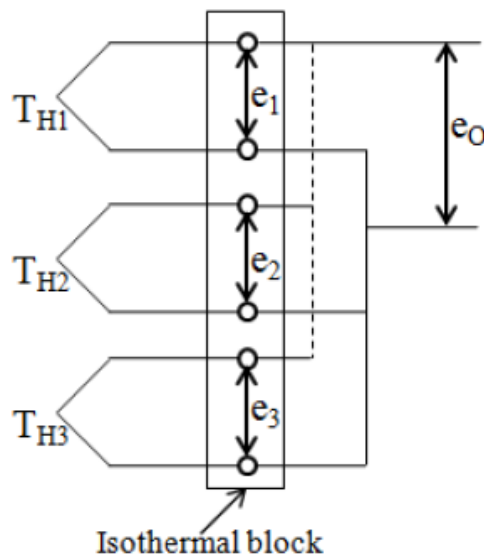


Figure 5

- a)  $e_0 = (e_1 + e_2 + e_3)/3$
- b)  $e_0 = (e_1 + e_2 + e_3)$
- c)  $e_0 = (e_1 \times e_2 \times e_3)$
- d) None of these

Accepted Answers:

a)  $e_0 = (e_1 + e_2 + e_3) / 3$

Previous Page

End

© 2014 NPTEL - Privacy & Terms - Honor Code - FAQs -



A project of



In association with



Funded by

Government of India  
Ministry of Human Resource Development

Powered by

