

# Introduction to Time-Varying Electrical Networks : Week 11

## Problem 1

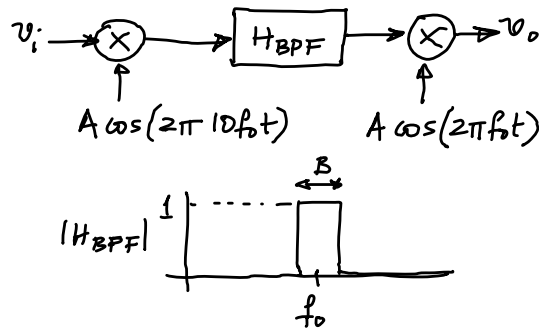


Figure 1: LPTV system for problem 1.

In the figure above, the bandpass filter is ideal; it is centered at  $f_0$  and has a narrow bandwidth, denoted by  $B$ . Determine all the frequencies in the input  $v_i$  that can result in a non-zero output at  $v_o$ .

## Problem 2

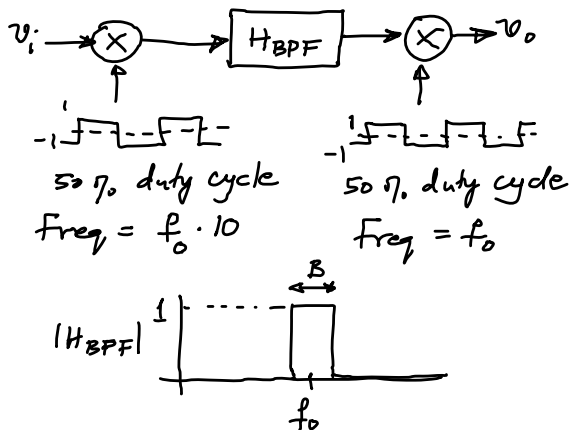


Figure 2: LPTV system for problem 2.

Repeat problem 1 for the system of Fig. 2.

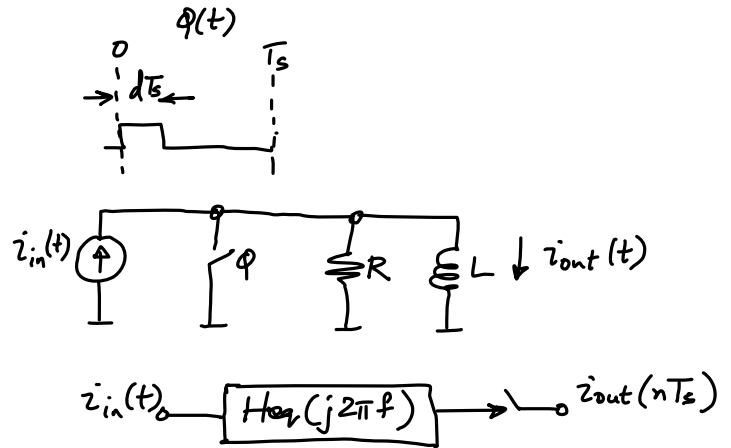


Figure 3: LPTV system for problem 3.

## Problem 3

A switched RL network is shown in Fig. 3. Determine the transfer function of the equivalent LTI filter that relates the input  $i_{in}(t)$  to the sampled output  $i_{out}(nT_s)$ . The switch is ideal, and is controlled by a periodically operated switch with period  $T_s$  and duty cycle  $d$ .