

# Introduction to Time-Varying Electrical Networks : Week 6

## Problem 1

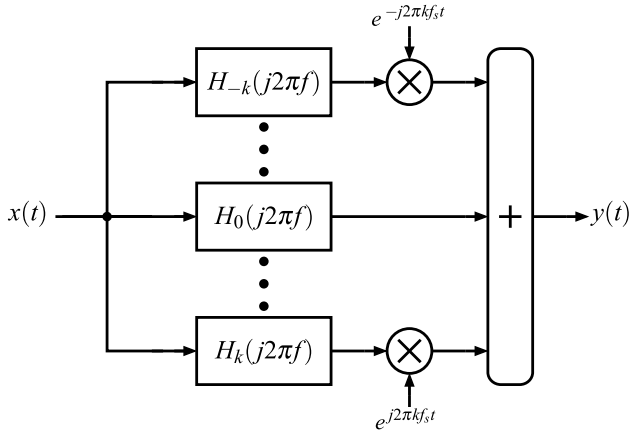


Figure 1: Zadeh expansion of an LPTV system.

The figure above shows the Zadeh expansion of an LPTV network, where  $k$  ranges from  $-\infty$  to  $\infty$ .

- Are the impulse responses corresponding to  $H_k(j2\pi f)$  real or complex?
- What is the relationship between the impulse responses of the filters  $H_k(j2\pi f)$  and  $H_{-k}(j2\pi f)$  for a given  $k$ ?
- Suppose that  $x(t) = \cos(2\pi f t)$ . Determine the output of the branches containing  $H_k(j2\pi f)$  and  $H_{-k}(j2\pi f)$ . Also determine their sum. Repeat the exercise above for  $x(t) = \sin(2\pi f t)$ . What do you conclude?

## Problem 2

Fig. 2 shows an alternative representation of an LPTV system. How are the  $F_k(j2\pi f)$  related to the  $H_k(j2\pi f)$  of Fig. 1?

## Problem 3

Fig. 3 shows an LPTV system. Determine its Zadeh expansion.

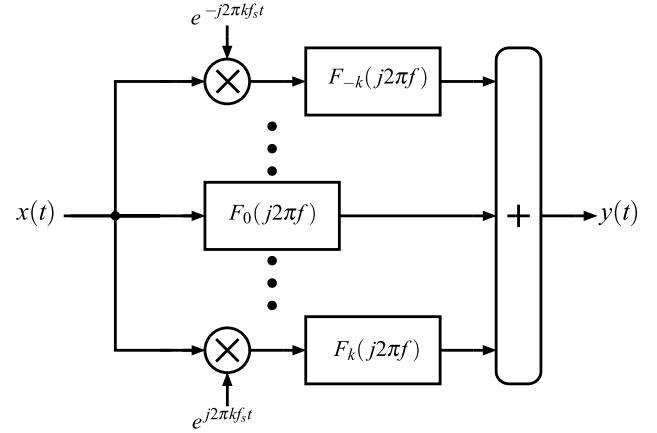


Figure 2: Alternative representation of an LPTV system.

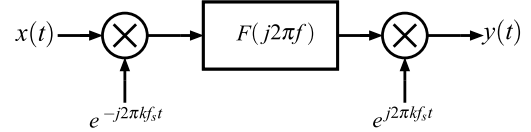


Figure 3: LPTV system for problem 3.

## Problem 4

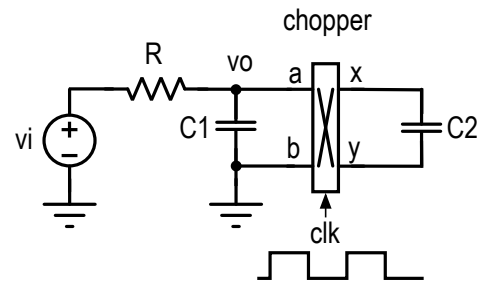


Figure 4: LPTV system for problem 4.

The circuit shown above is an LPTV network. The chopper is a network of ideal switches that works as follows. When  $\text{clk}$  is high, nodes  $a$  and  $b$  are connected to nodes  $x$  and  $y$  respectively. When  $\text{clk}$  is low, nodes  $a$  and  $b$  are connected to nodes  $y$  and  $x$  respectively. The  $\text{clk}$  signal has a 50% duty cycle and frequency  $f_s$ . Denote the zeroth order harmonic transfer function from  $v_i$  to  $v_o$  by  $H_0(j2\pi f)$ . Determine  $H_0(0)$ .