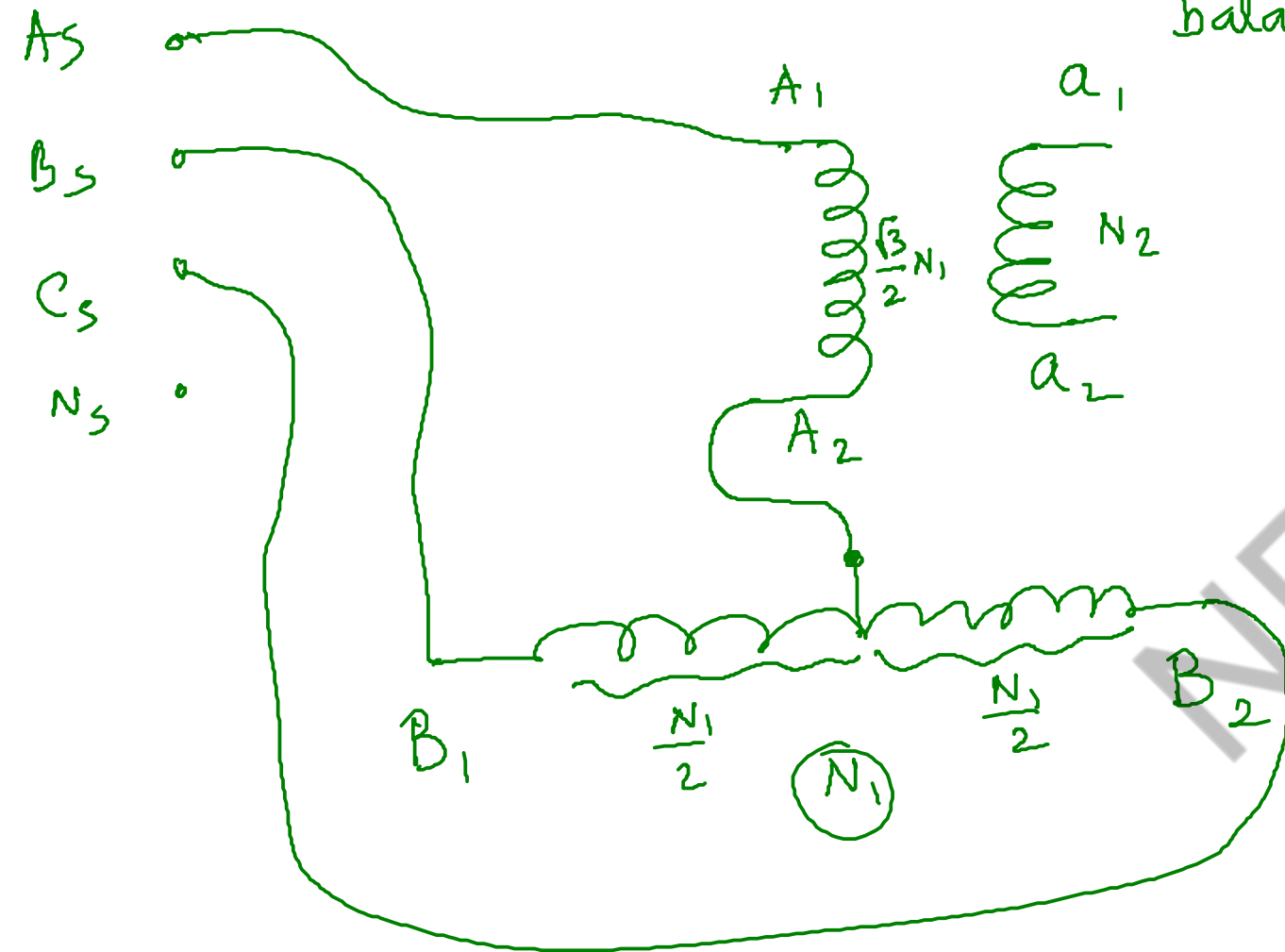


Phase conversion:

Scott connection: uses ^{Two nos} of 1-ph. tfo dec 45

3 ph voltage $\rightarrow$ 2 ph. balanced voltage.




primary turns
of tfo B = N_1
Then primary turns
of tfo A = $\frac{\sqrt{3}}{2} N_1$

Volt per turn
of tfo B = $\frac{V_{LL}}{N_1}$

$$|V_{b_1 b_2}| = \frac{V_{LL}}{N_1} \times N_2$$

$$= \frac{N_2}{N_1} V_{LL}$$

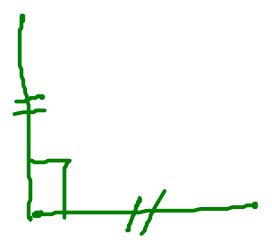

$$a_A = \frac{\sqrt{3} N_1}{2 N_2}$$


$$A_1 O \equiv V_{LL} \frac{\sqrt{3}}{2}$$

$$\therefore \text{voltage/turn } \delta B = \frac{V_{LL} \sqrt{3}/2}{\sqrt{3}/2 N_1} = \frac{V_{LL}}{N_1}$$

voltage/turn must be same for tfo A and tfo B

$$I_{AS} = \frac{2 N_2 I_a}{\sqrt{3} N_1}$$

$$= \frac{V_{LL}}{N_1}$$

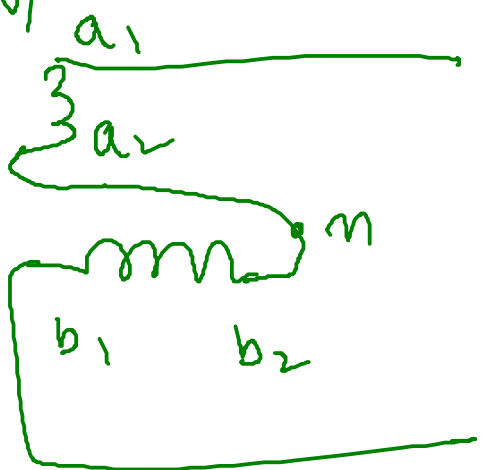


$$I_{AS} + I_{BS} + I_{CS} = 0$$

$$\text{or } I_{BS} + I_{CS} = -I_{AS}$$

$$I_a' = \frac{I_a}{a_A}$$



$$= I_{AS}$$
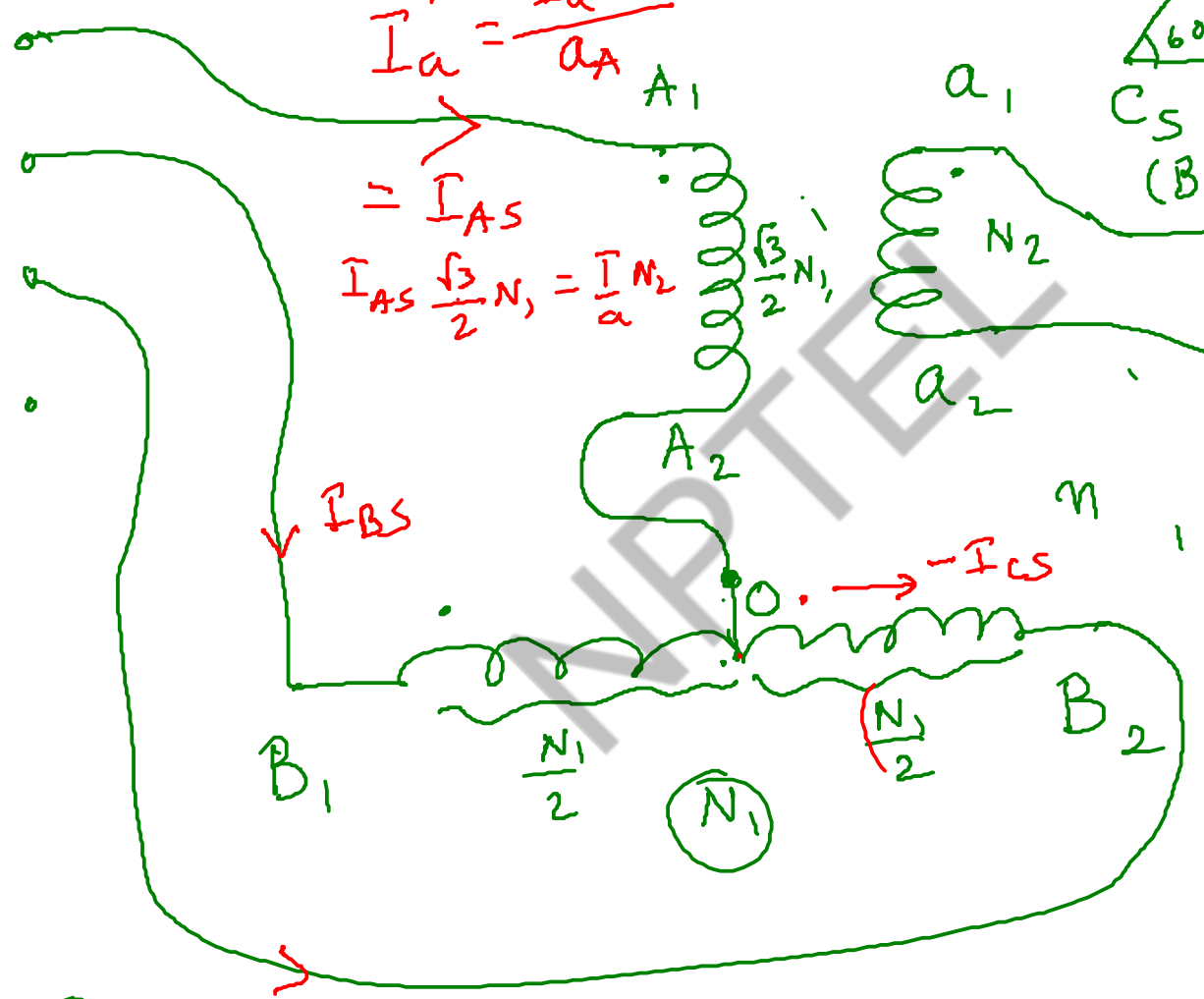
$$I_{AS} \frac{\sqrt{3} N_1}{2} = \frac{I_a N_2}{a}$$




$$I_{BS} \frac{N_1}{2} + (-I_{CS}) \frac{N_1}{2} = I_b \frac{N_2}{2}$$
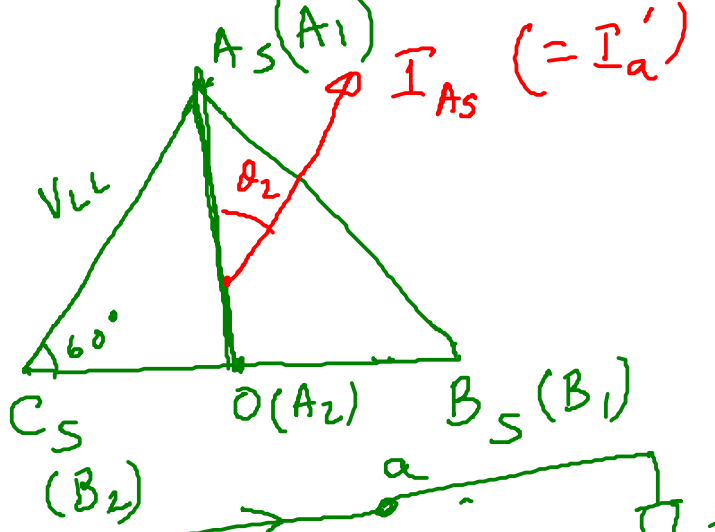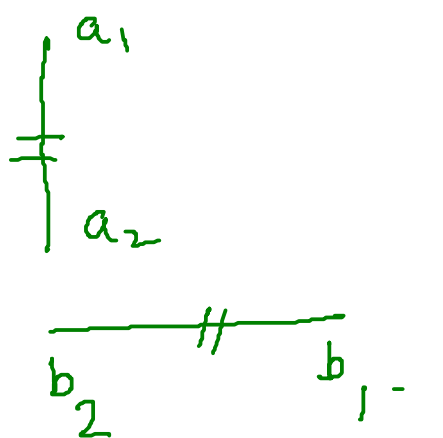
$$I_{BS} - I_{CS} = I_b \frac{N_2}{N_1}$$



length δB $a_1 a_2$ & $b_1 b_2$

$$= \frac{V_{LL}}{N_1} N_2$$

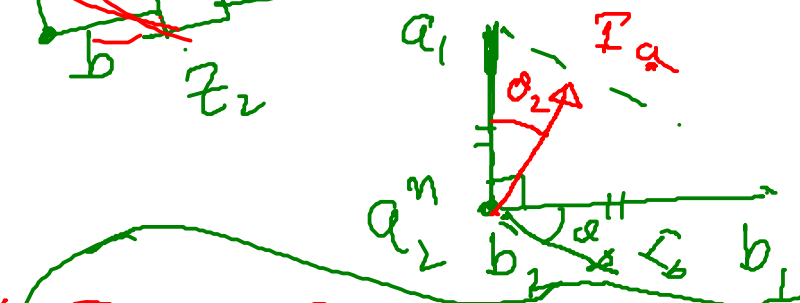


(1)

Scott connection

lec 46

$$I_{As} + I_{Bs} + I_{Cs} = 0$$



N_s

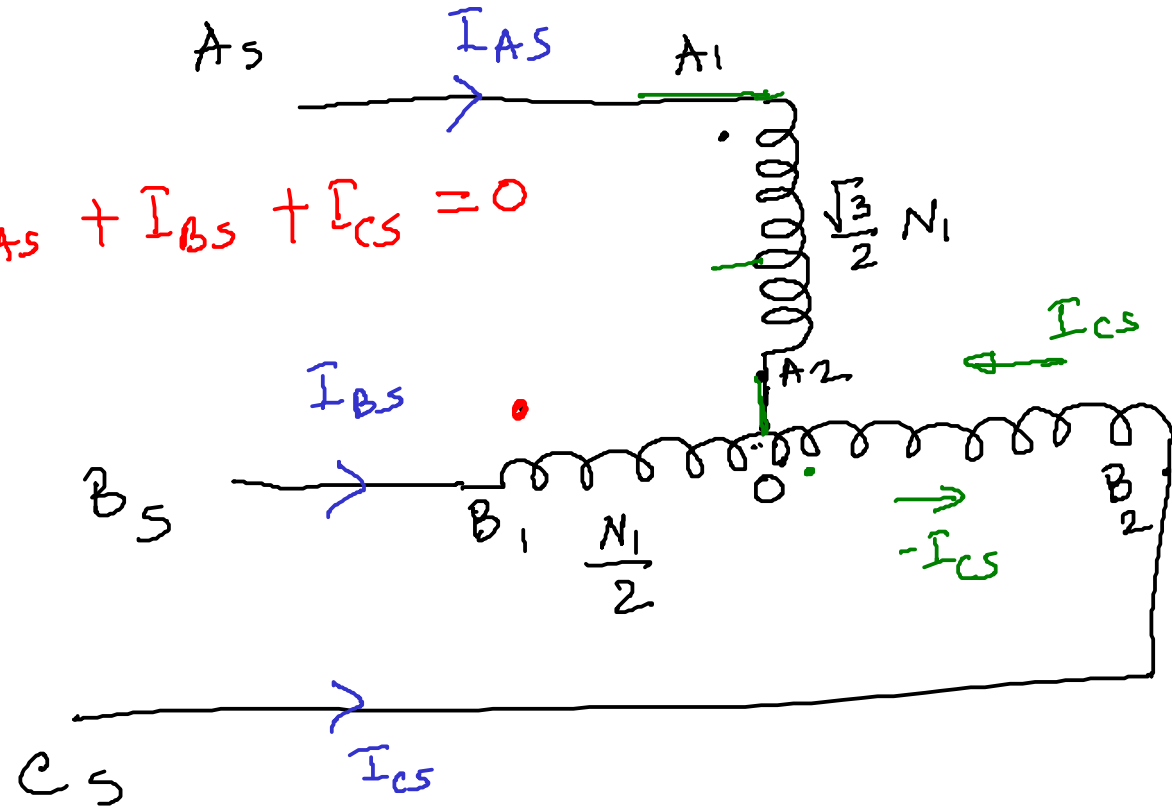

$$I_{As} \frac{\sqrt{3}}{2} N_1 = N_2 I_a$$

$$\therefore I_{As} = \frac{2 N_2 I_a}{\sqrt{3} N_1}$$
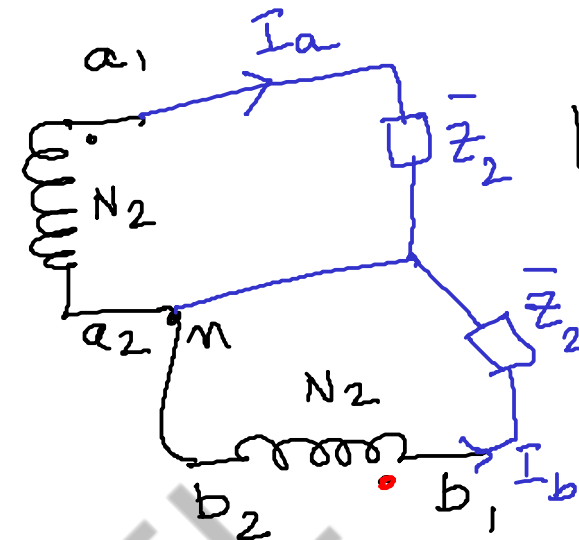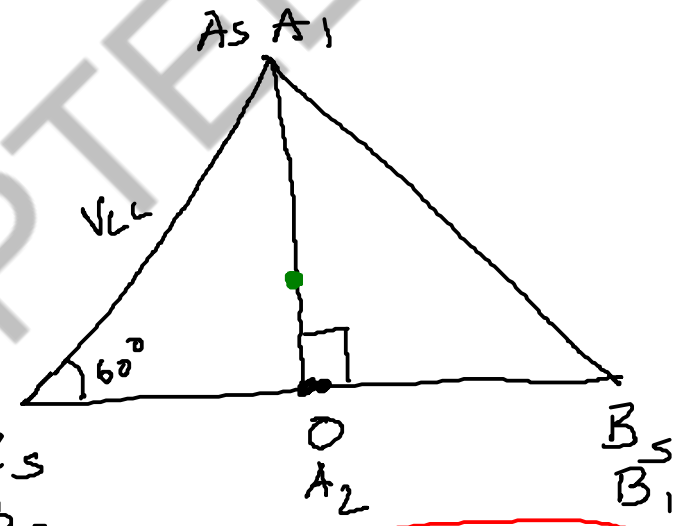
$$I_{Bs} \frac{N_1}{2} + (-I_{Cs}) \frac{N_1}{2} = N_2 I_b$$



$$\therefore I_{Bs} - I_{Cs} = \frac{2 N_2 I_b}{N_1}$$

$$I_{Bs} + I_{Cs} = -I_{As}$$


$$|V_{b_1 b_2}| = \frac{V_{LL} N_2}{N_1}$$

$$|V_{a_1 a_2}| = \frac{V_{LL} \frac{\sqrt{3}}{2} N_2}{\frac{\sqrt{3}}{2} N_1} = \frac{V_{LL} N_2}{N_1}$$

$$N_{B, B_2} = N_1$$

$$N_{A, A_2} = \frac{\sqrt{3}}{2} N_1$$

$$N_{B, O} = N_{B_2 O} = \frac{N_1}{2}$$

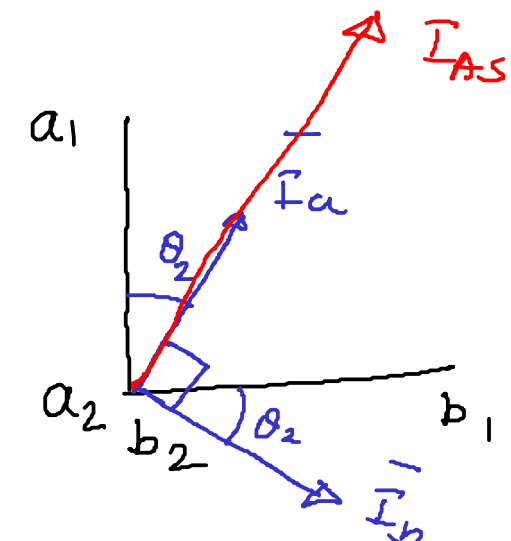

$$I_{Bs} = -\frac{I_{As}}{2} + \frac{2 N_2 I_b}{\sqrt{3} N_1}$$

$$I_{Cs} = -\frac{I_{As}}{2} - \frac{2 N_2 I_b}{\sqrt{3} N_1}$$



$$I_{BS} = -\frac{I_{AS}}{2} + \frac{N_2}{N_1} I_b$$

$$I_{CS} = -\frac{I_{AS}}{2} - \frac{N_2}{N_1} I_b$$



$$\therefore I_{AS} = \frac{2 N_2 I_a}{\sqrt{3} N_1}$$



$$\tan \alpha = \frac{\frac{1}{2} \frac{2 N_2}{\sqrt{3} N_1} |I_a|}{\frac{N_2}{N_1} |I_b|} = \frac{1}{\sqrt{3}} \quad \therefore \alpha = 30^\circ$$

With unbalanced load on 2ndary side:

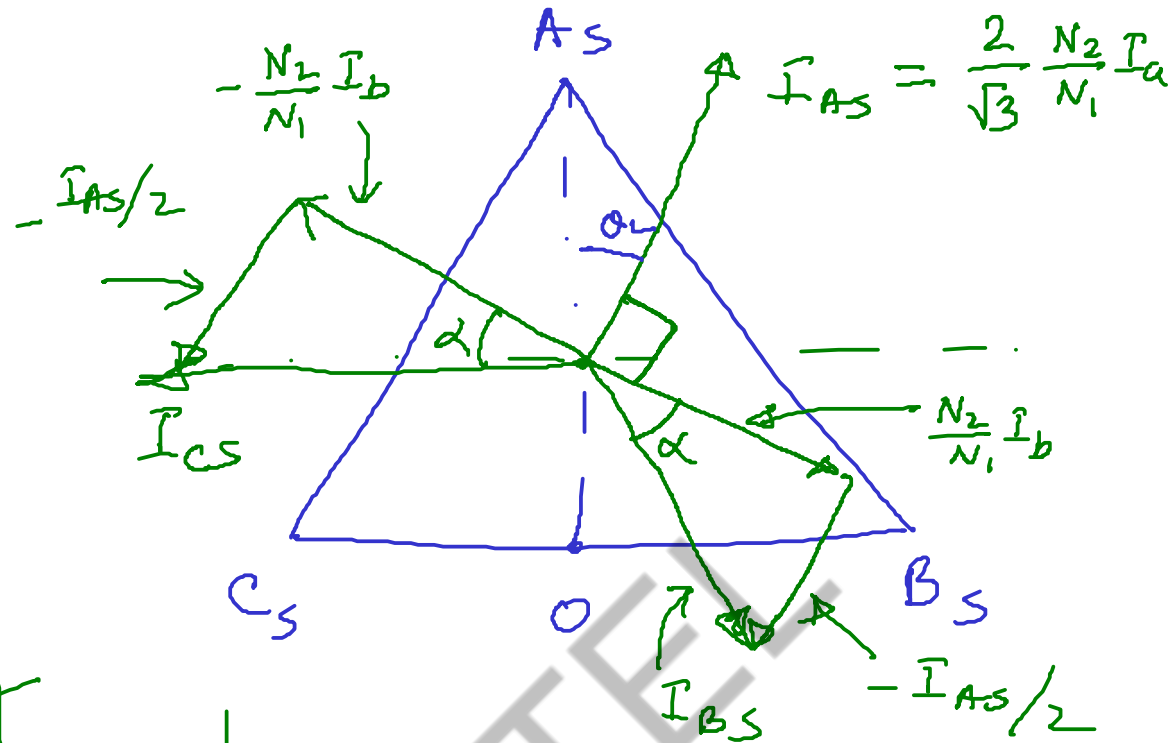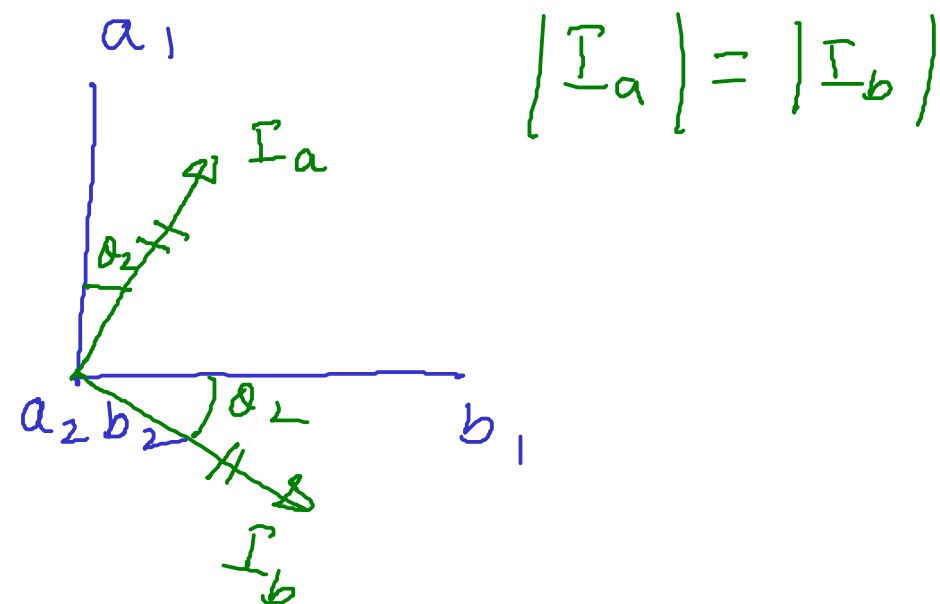

$$|I_a| = |I_b|$$






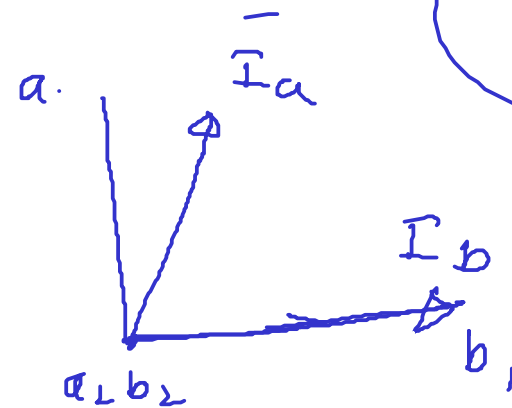
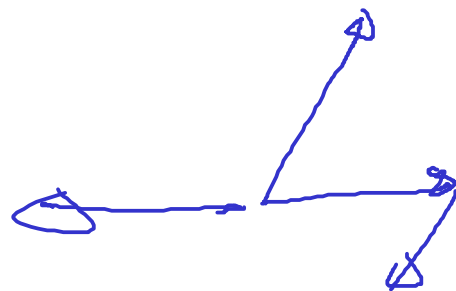


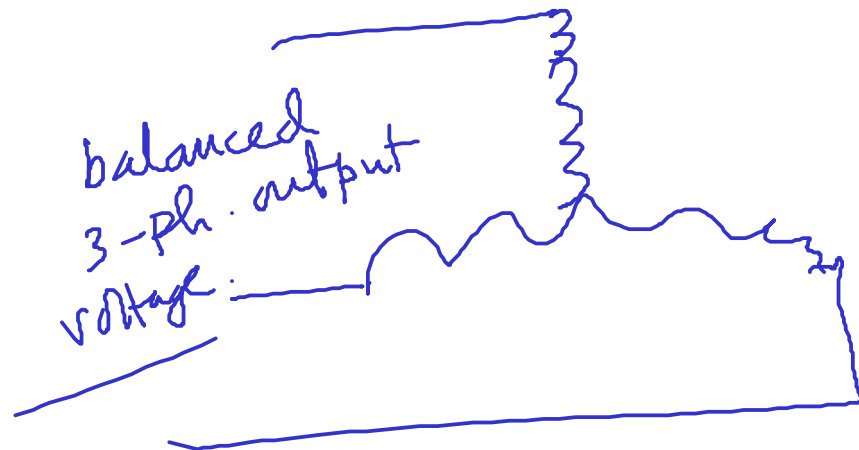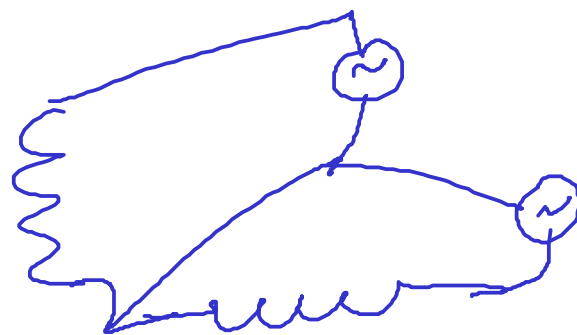

NPTTEL

Phase conversion

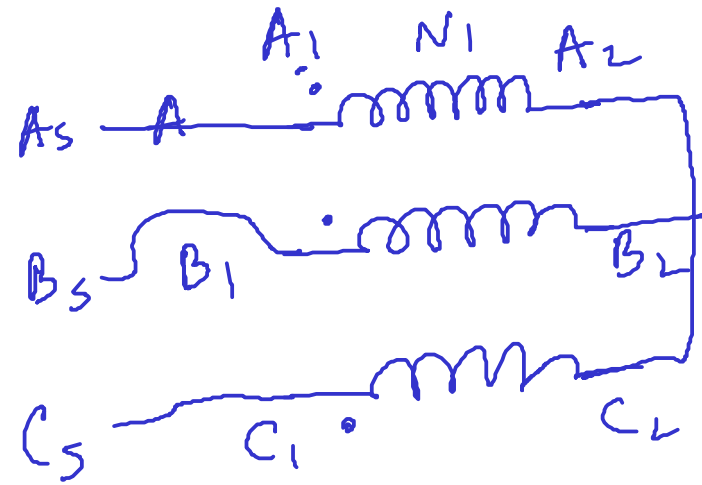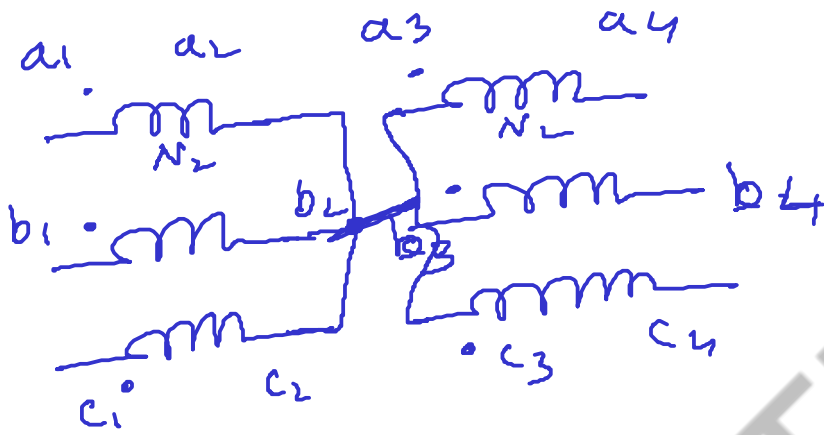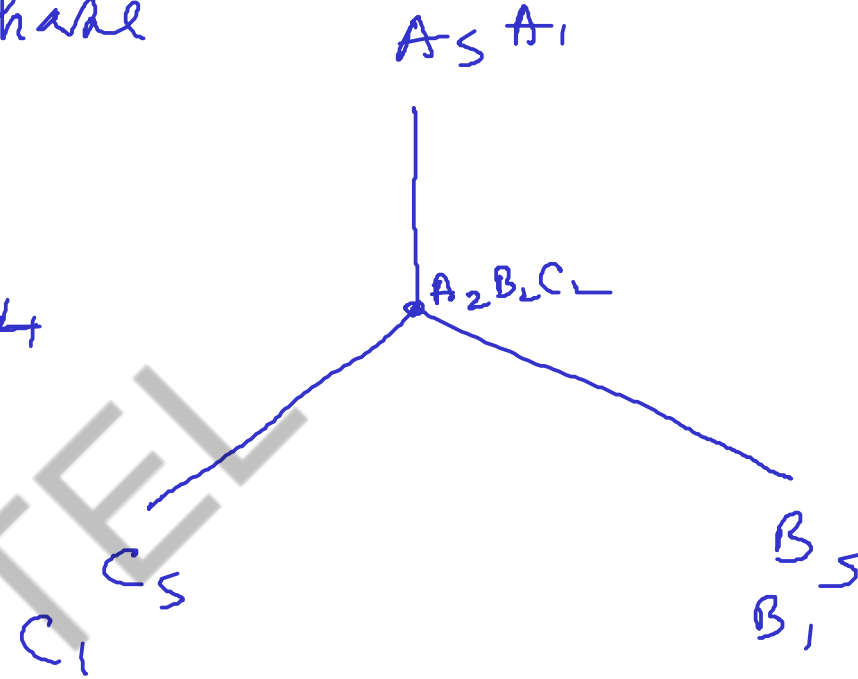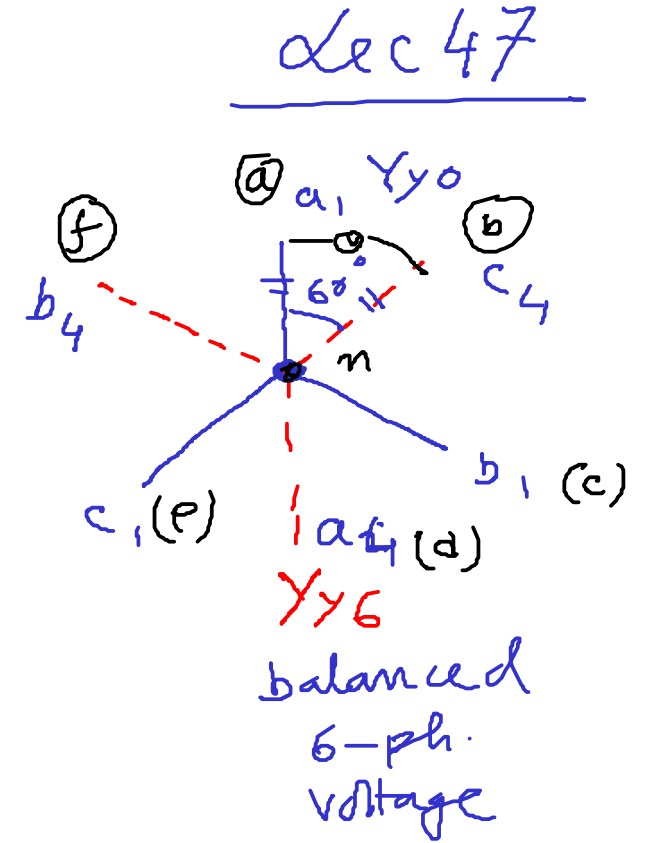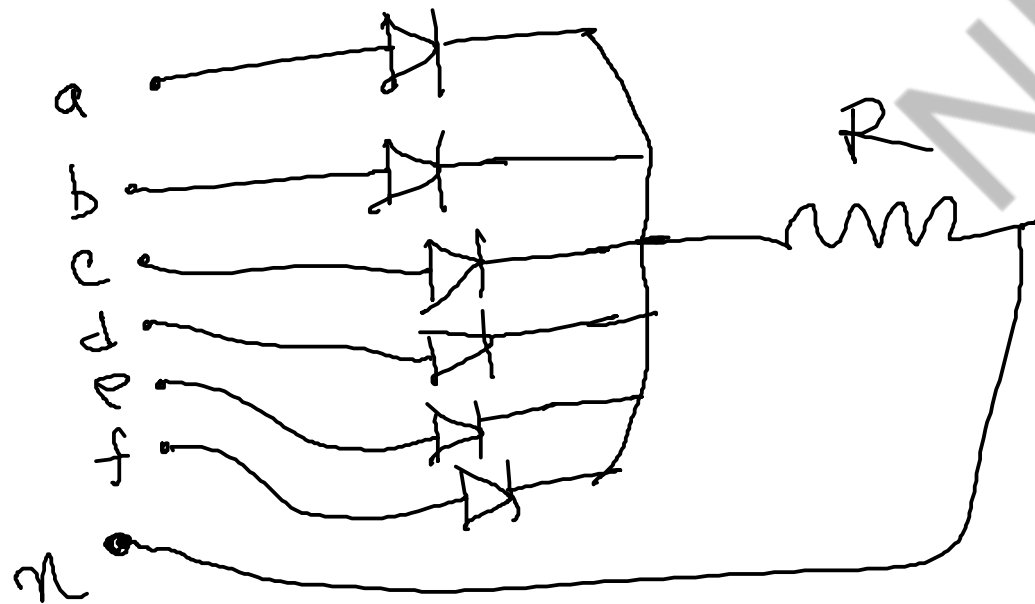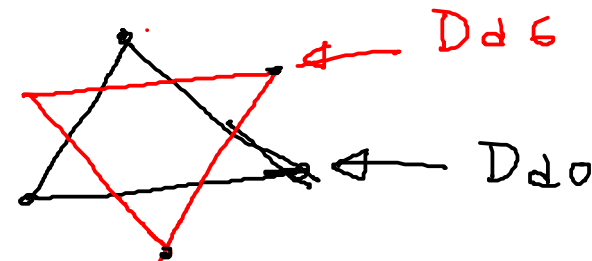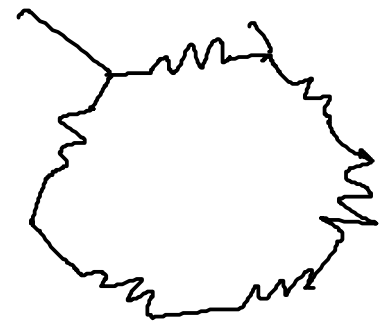3 Phase to 2 Phase (Scott connection)
3 phase to 6 phase





30 KVA,

400V/200V,

3 ϕ , 50Hz, +fo

per Phase
Equivalent
Ckt,

O.C

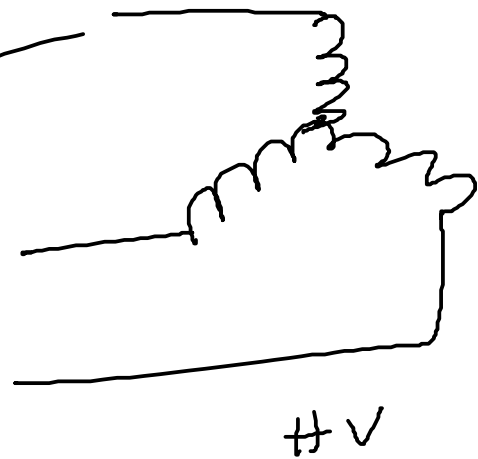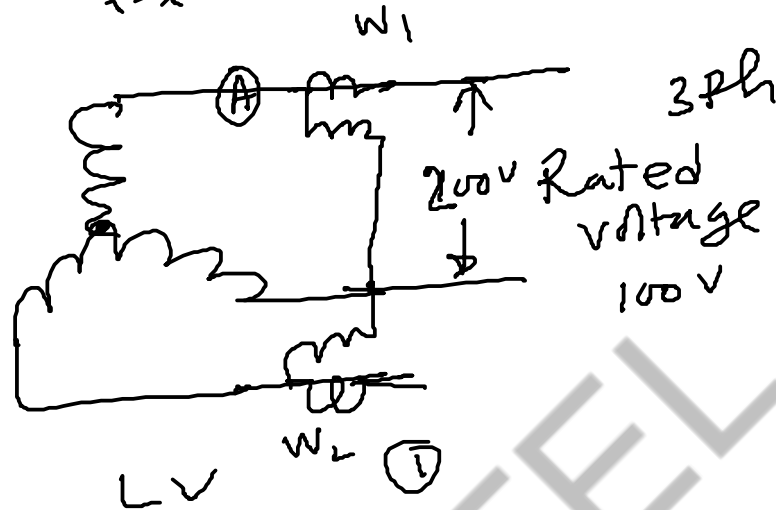

$$W_1 + W_2 = \text{Cu-loss} = I_{sc}^2 r_{e2} = W_{sc}$$

$$Z_{e2} = \frac{V_{sc}}{\sqrt{3} I_{sc}}$$


$$r_{e2} = \sqrt{Z_{e2}^2 - x_{e2}^2}$$

$$I_o, W_o, V = W_1 + W_2$$

$$\sqrt{3} \times 200 I_o \cos \theta_o = W_o$$

$$\cos \theta_o \checkmark$$

$$\sin \theta_o \checkmark$$

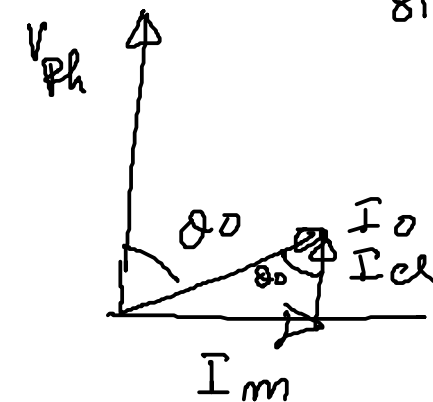

$$I_{ci} = I_o \cos \theta_o$$


$$I_m = I_o \sin \theta_o$$

$$R_{cl} = \frac{V}{I_{ci}}$$

$$X_{m1} = \frac{V}{I_m}$$

$$I_{HV \text{ rated}} = \frac{30000}{\sqrt{3} \times 400} \approx 43 \text{ A}$$

30 KVA, 400V/200V,
 Δ Δ

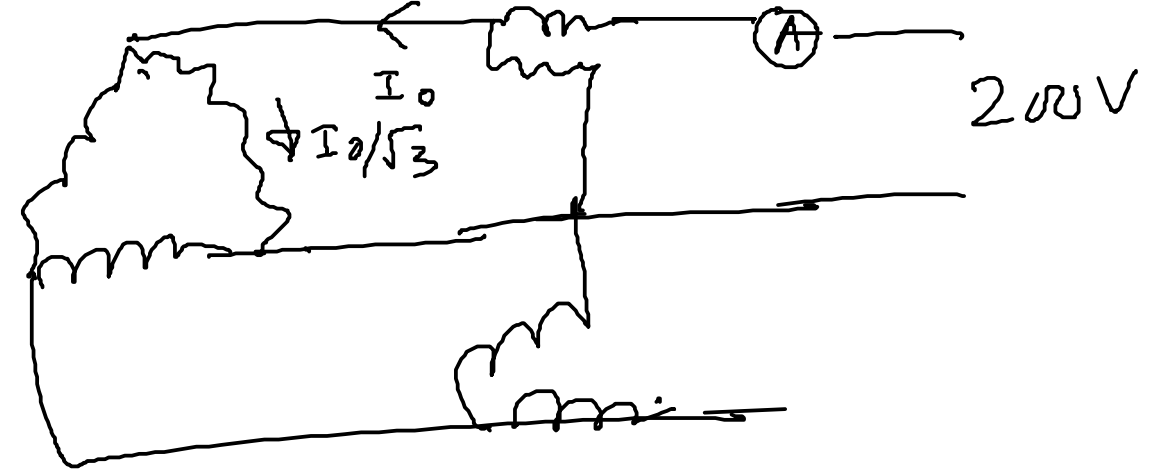


$$\therefore \frac{(W_1 + W_2)}{3} = \overset{0-C}{\bullet} 200 \left(\frac{I_0}{\sqrt{3}} \right) \cos \theta_0$$

Parallel operation of transformers

400V/200V, 400V/200V,



1st ph tfo 50Hz 100KVA
50KVA


trf A
trf B

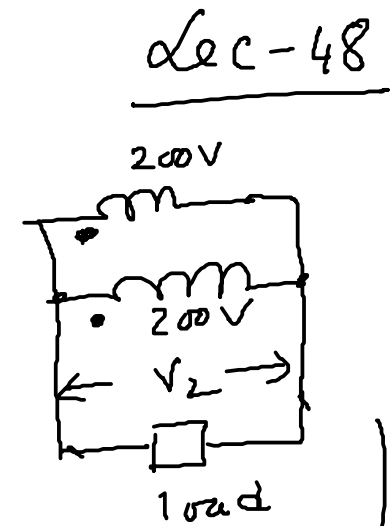


3rd, 6.6 KV/440V, 50Hz, 150KVA
✓ Polarity must be same while connecting in parallel

Equivalent circuit ref. to load side

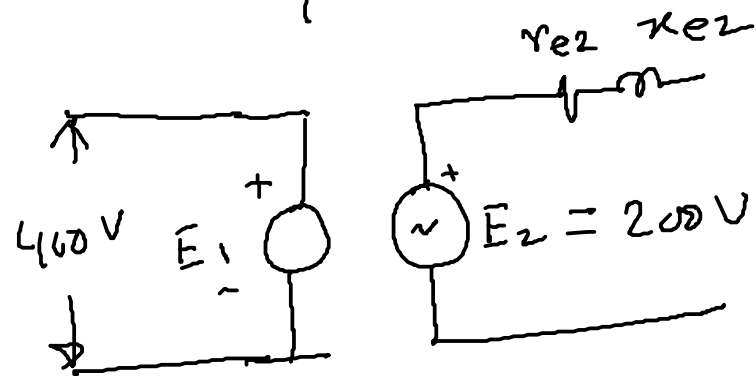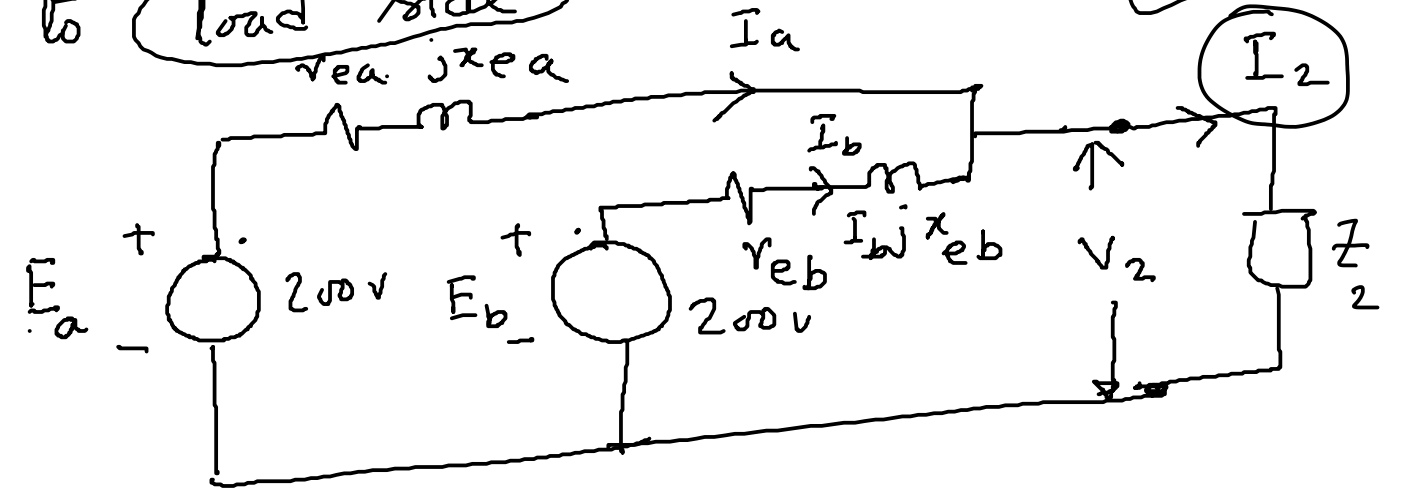

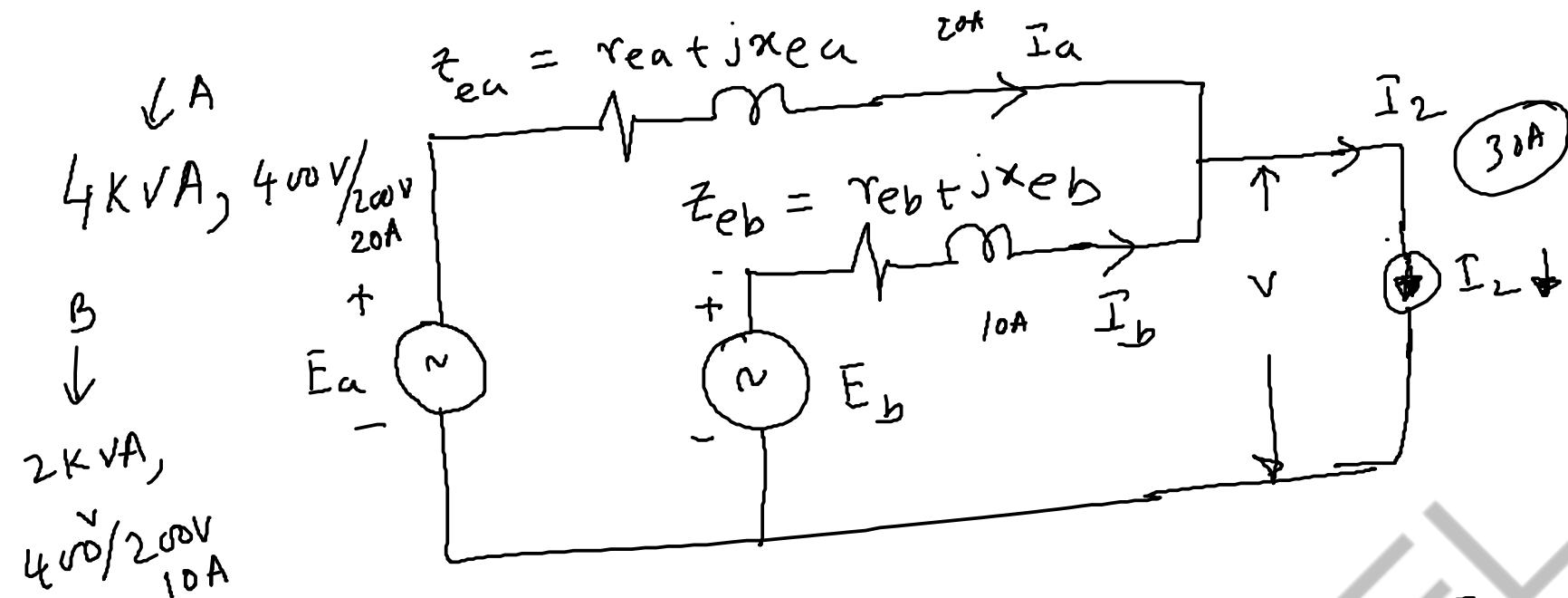

Suppose load current I_2 is known

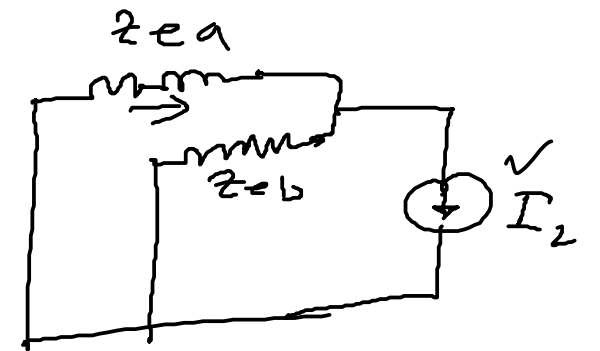

$$I_a = \frac{E_a - E_b}{z_{ea} + z_{eb}} + I_2 \frac{z_{eb}}{z_{ea} + z_{eb}}$$

$$I_b = \frac{E_b - E_a}{z_{ea} + z_{eb}} + I_2 \frac{z_{ea}}{z_{ea} + z_{eb}}$$

$$\frac{I_a}{I_b} = \frac{z_{eb}}{z_{ea}}$$

In case

$$E_a = E_b$$

$$I_a = \frac{z_{eb}}{z_{ea} + z_{eb}} I_2$$

$$I_b = \frac{z_{ea}}{z_{ea} + z_{eb}} I_2$$

$$\frac{I_a}{I_b} = \frac{Z_{eb}}{Z_{ea}} \Rightarrow \frac{|I_a|}{|I_b|} = \frac{|Z_{eb}|}{|Z_{ea}|} = \frac{2}{1}$$

transformer A

|| B

$$E_a = E_b = 200 \text{ V}$$

current shared by transformer $\propto \frac{1}{\text{leakage impedance}}$


$$\therefore |Z_{eb}| = 2|Z_{ea}|$$

$$I_2 : I_a : I_b = 3 : 2 : 1$$

Transformer leakage impedance $\propto \frac{1}{\text{KVA}}$

$$\overset{10A}{400V} / \overset{(20A)}{200V}, 50 \text{ Hz}, \text{ (4 KVA)}$$
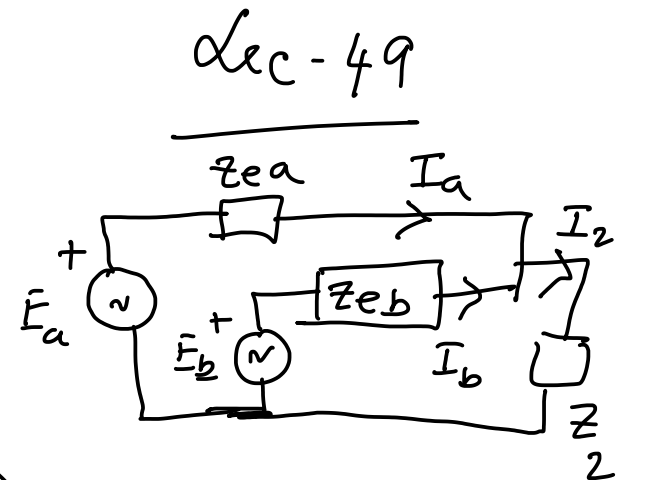
$$\overset{5A}{400V} / \overset{(10A)}{200V}, 50 \text{ Hz}, \text{ (2 KVA)}$$



$$\begin{aligned} I_2 &= 30 \text{ A} \\ I_a &= 20 \text{ A} \\ I_b &= 10 \text{ A} \end{aligned}$$

$$\frac{I_a}{I_b} = \frac{2}{1}$$

$$\frac{|Z_{eb}|}{|Z_{ea}|} = \frac{1}{2}$$

$$Z_{ea} = r_{ea} + jx_{ea} \quad | \quad Z_{eb} = r_{eb} + jx_{eb}$$

$$|Z_{ea}| = \sqrt{r_{ea}^2 + x_{ea}^2} \quad |Z_{eb}| = \sqrt{r_{eb}^2 + x_{eb}^2}$$

$$Z_e \propto \frac{1}{S}$$

$$|Z_{ea}| = k \frac{1}{S_a}$$

$$|Z_{eb}| = k \frac{1}{S_b}$$

Equality of the leakage impedances.


$$\frac{x_{ea}}{r_{ea}} = \frac{x_{eb}}{r_{eb}}$$

$$\tan^{-1} \frac{x_{ea}}{r_{ea}} = \tan^{-1} \frac{x_{eb}}{r_{eb}} = \theta$$

Voltage across

$$Z_{ea} = E_a - E_2$$
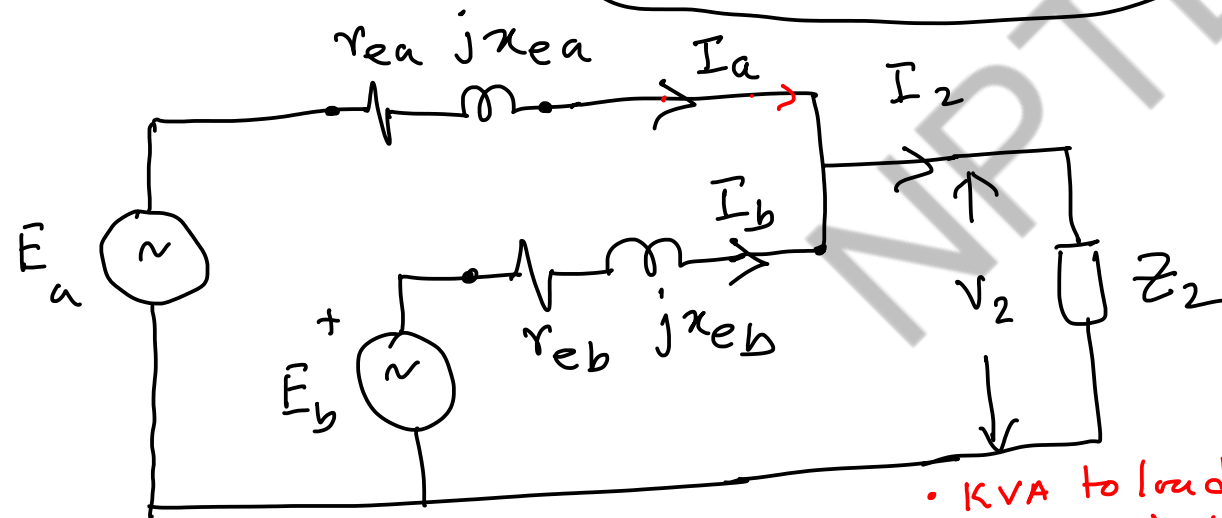
$$= \text{Voltage across } Z_{eb} = \bar{V}_{ab}$$




$$\underline{E_a = E_b}$$

$$\bullet \text{ KVA to load} = V_2 I_2$$

$$\bullet \text{ KVA supp. by trf A} = V_2 I_a$$

$$\bullet \text{ KVA supp. by trf B} = V_2 I_b$$
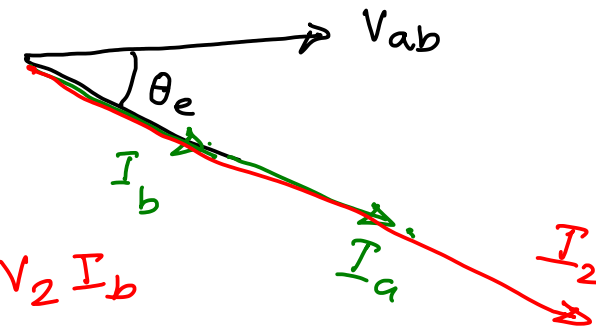
$$V_2 I_a + V_2 I_b = V_2 I \leftarrow \text{algebraic sum.}$$






Suppose

$$\tan^{-1} \frac{x_{ea}}{r_{ea}} \neq \tan^{-1} \frac{x_{eb}}{r_{eb}} = \theta_{eb}$$

but $z_e \propto \frac{1}{s}$

$$\frac{|I_{ea}|}{|I_{eb}|} = \frac{|z_{eb}|}{|z_{ea}|} \quad \checkmark \quad \underline{\alpha \approx 50}$$

$$I_2 = I_{ea} + I_{eb}$$

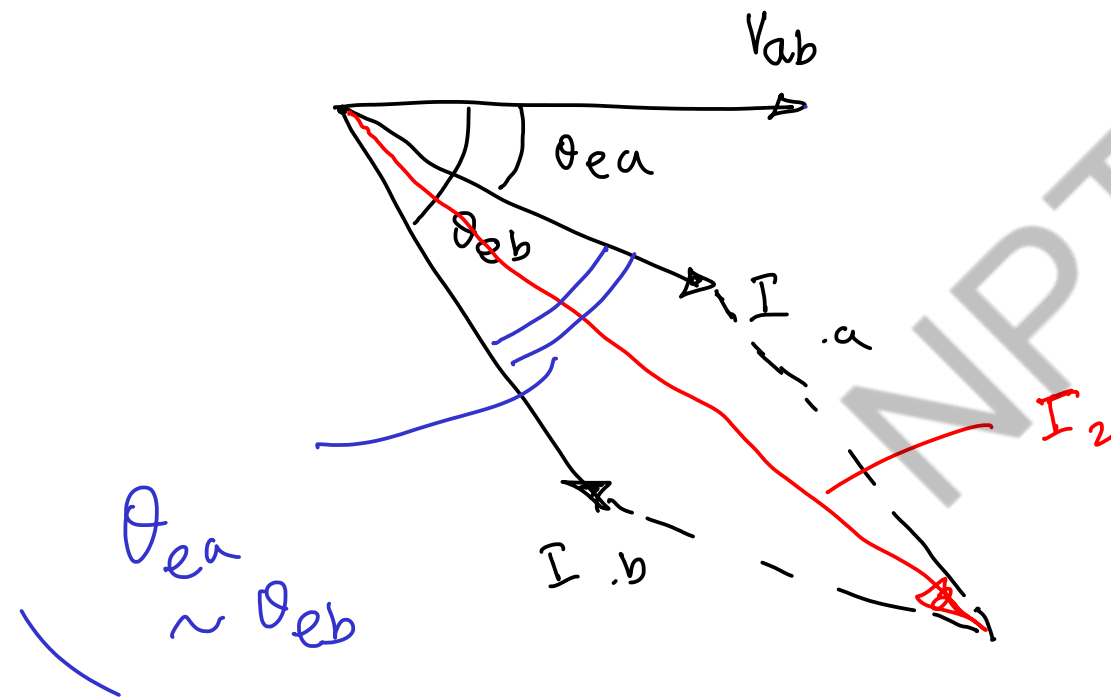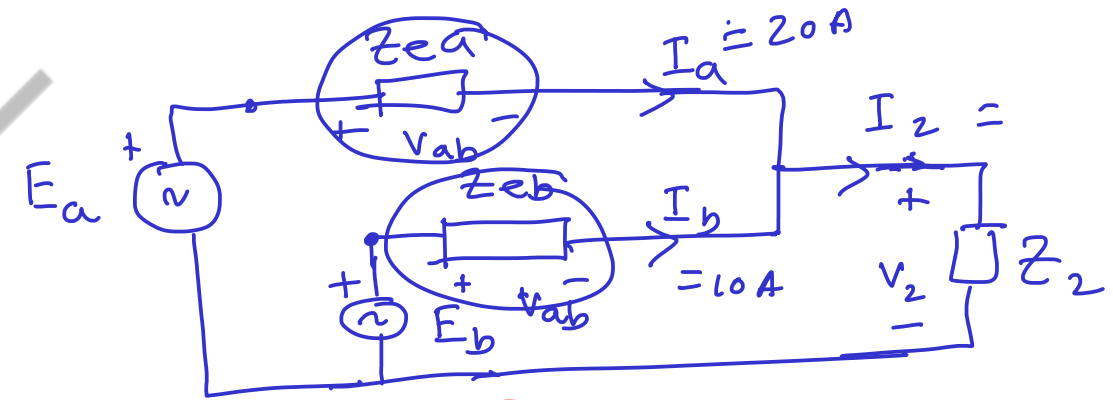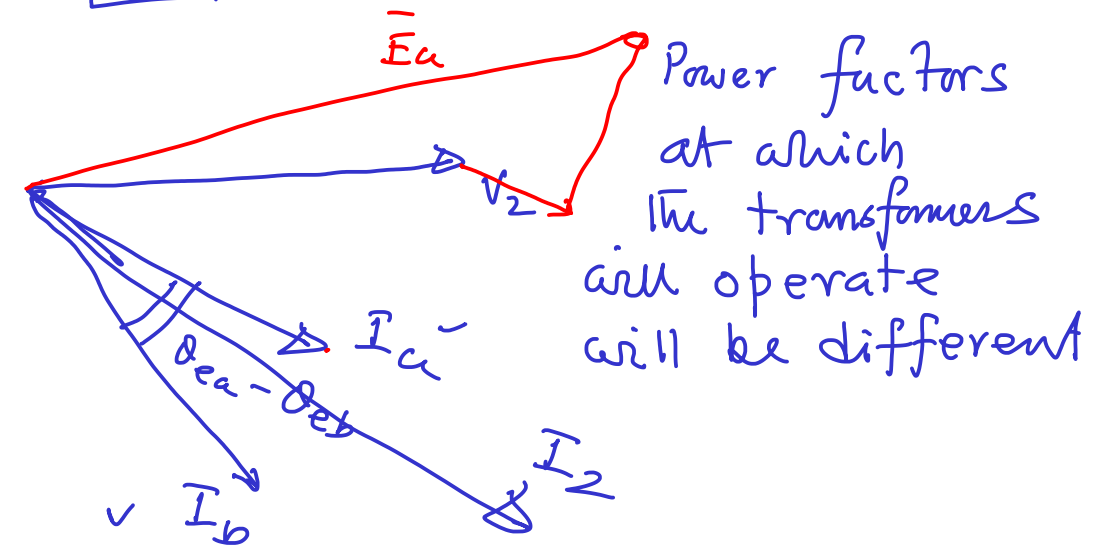

leakage impedance of tfo $\propto \frac{1}{s}$

→ p.u values of the leakage impedance should be same

p.u value of leakage imp. of tfo A

$$\frac{|I_a| |Z_{ea}|}{V_2} = Z_{pu(a)}$$

p.u value of leakage impedance of tr B.

$$\frac{|I_b| |Z_{eb}|}{V_2} = Z_{pu(b)}$$

for successful & effective parallel operation of transformers

- ① Voltages of HV & LV side should be same. (for 3 ph l-l voltage ratings should be same)
- ② $Z_e \propto \frac{1}{S}$ or $Z_{p.u}$ of the tfo should be same

($\rightarrow$)

- ③ The qualities of the leakage impedances should be same $\Rightarrow$ tfo. will operate at same p.f.

3-ph. $\rightarrow$ tfo

④

The transformers must belong to same vector group.

$Dy1$

$Yd1$
 $Yz1$

Small transformers few KVAs
 200V/100V, 50Hz

1-ph. tfo

$$V_1 \approx E_1 = 4.44 f \Phi_{\max} N_1$$




- specific magnetic loading ($B_{\max}$)
Tesla
- specific electric loading

δ = current density
 of Cu (or Al) 2.5 to 3 A/mm²

LV side a_1 = cross section of wire
 HV side a_2 = " " of wire

δ = same both for LV
 & HV side.

Let I_1 be the current rating
 side 1, (LV side) $I_1 = \delta a_1$
 HV side (rated) $I_2 = \delta a_2$

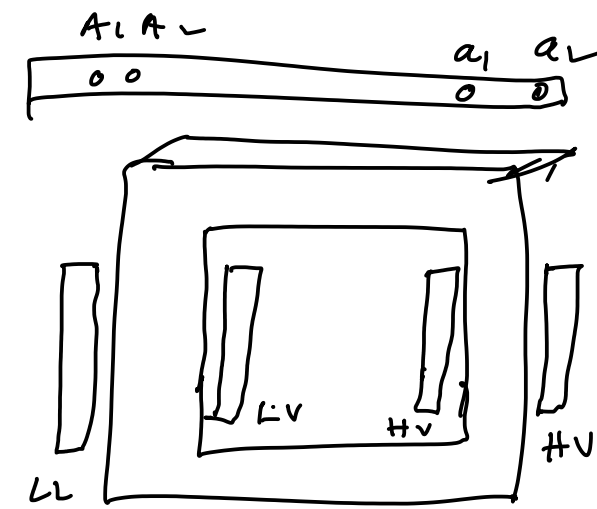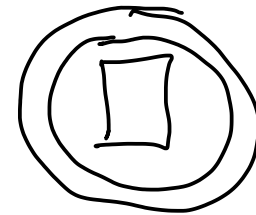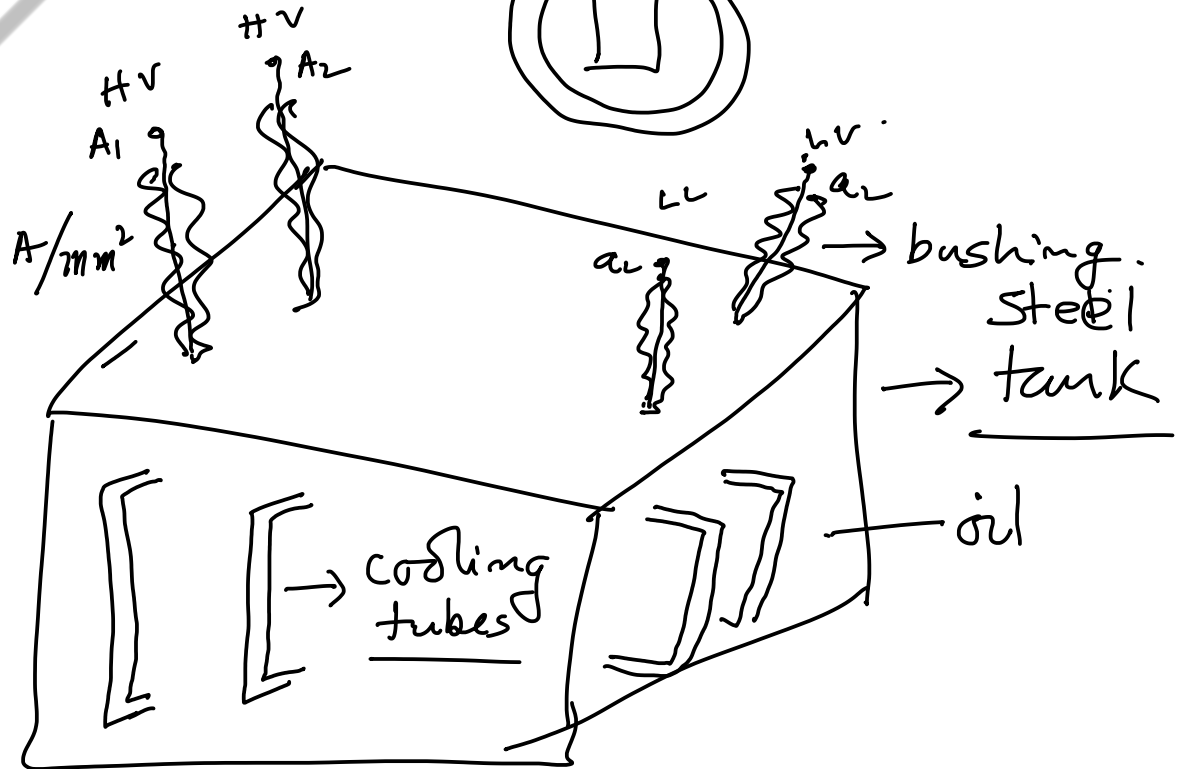


Dec 51

1 ph. tfo

$$S \approx 4.44 f \phi_{\max} N_1 I_1 \times 10^{-3} \quad B_{\max} \approx 1 \text{ T} \quad \delta = 2.5 \text{ to } 3 \text{ A/mm}^2$$

$$= 4.44 f B_{\max} A_{i(\text{net})} N_1 \delta a_1 \times 10^{-3}$$
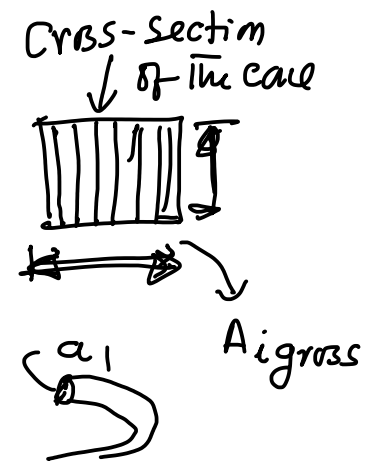
$$S = 4.44 f B_{\max} \delta_f A_{i(\text{gross})} N_1 a_1 \delta \times 10^{-3}$$



$$A_{i(\text{net})} = \delta_f A_{i(\text{gross})}$$

$\delta_f = \text{stack factor}$
(0.95)

$A_w = \text{window area}$


Window space factor:-

$$k_w = \frac{\text{Area used by Cu}}{A_w} = \frac{(N_1 a_1 + N_2 a_2)}{A_w} \approx \underline{\underline{0.35}}$$

$$N_1 I_1 = N_2 I_2$$

$$\therefore N_1 a_1 \delta = N_2 a_2 \delta \quad \therefore N_1 a_1 = N_2 a_2$$

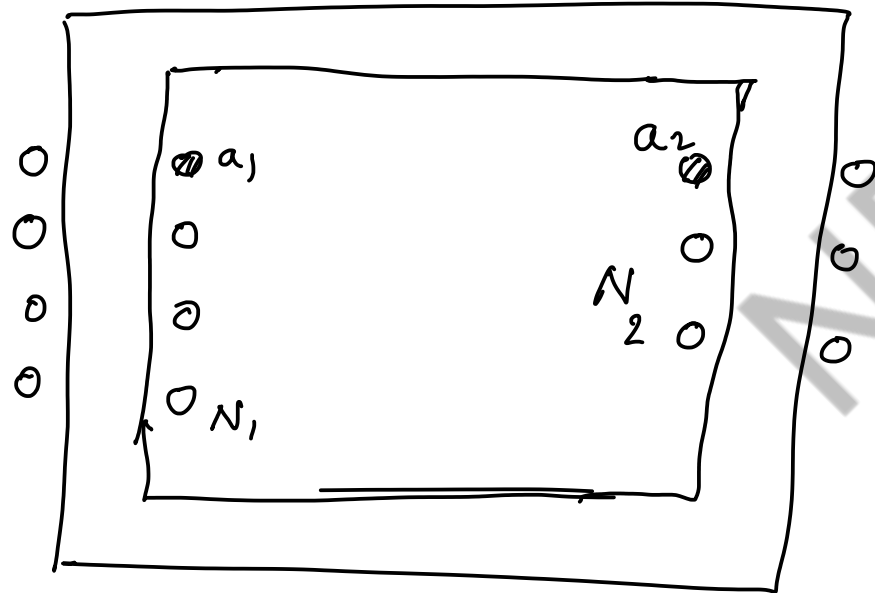
$$k_w = \frac{2 N_1 a_1}{A_w} \quad \therefore N_1 a_1 = \frac{k_w A_w}{2}$$



$$S = 4.44 f B_{\max} \delta_f A_{i \text{ gross}} \delta \frac{k_w A_w}{2} \times 10^{-3}$$

$$S = 2.22 f \delta_f k_w \underbrace{A_{i \text{ gross}} A_w}_{\text{decides the physical dimension}} B_{\max} \delta \times 10^{-3}$$

output Eqⁿ

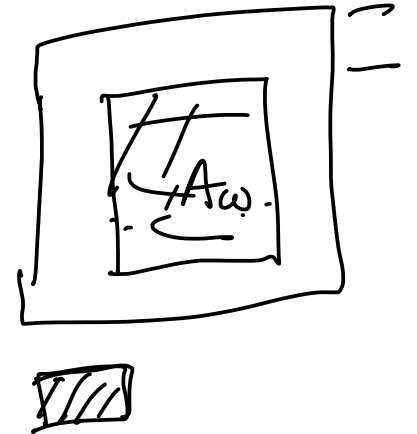



Let all the linear dimensions of the transformer is increased by a factor of 'x'
 Keeping $B_{\max}$ & δ constant

$\therefore$ kVA of the tfo will increase by a factor of $(?)$ x^4 ✓

Area will be increased by a factor of x^2
 To show That Losses will increase by a factor of x^3 ✓

dec 52
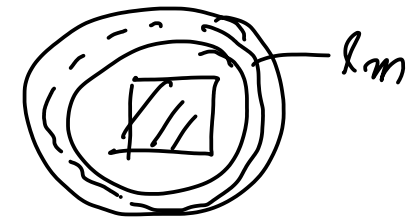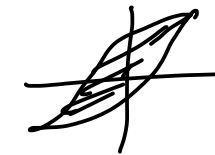
$$\begin{aligned} \text{Cu-loss} &:- I_1^2 r_1 + I_2^2 r_2 \\ &= \delta^2 a_1 \frac{P_{N_1} l_{m1}}{a_1} + \delta^2 a_2 \frac{P_{N_2} l_{m2}}{a_2} \end{aligned}$$



Cu loss $\propto$ vol. of Cu.

$\therefore$ Cu loss increases by a factor $\frac{x^3}{x^3}$


Core loss :-

$$\frac{P_{\text{total loss}}}{S_{\text{surface}}}$$

✓ S


✓ $P_{\text{total loss}}$

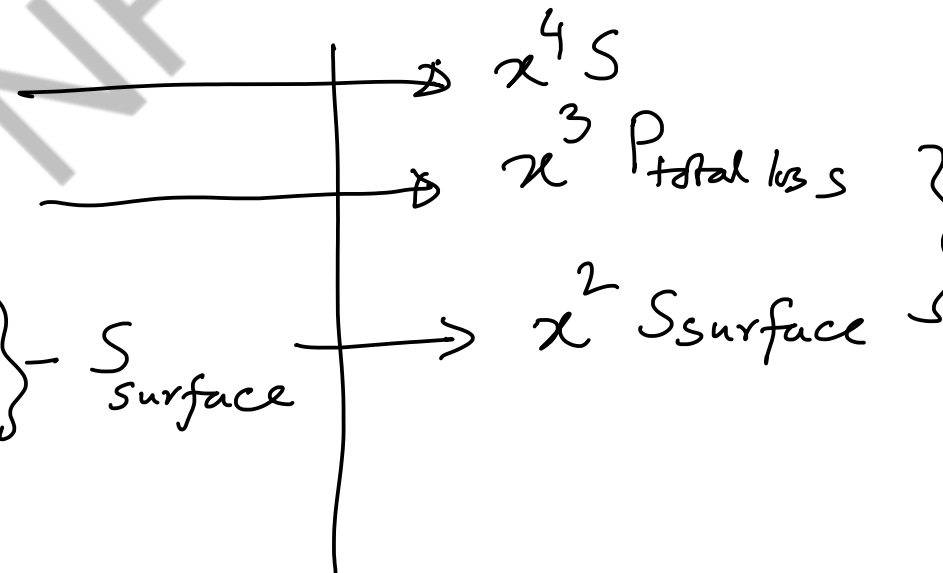surface area
through which
heat is dissipated } S_{surface}




$$\frac{x^3 P_{\text{total loss}}}{x^2 S_{\text{surface}}}$$

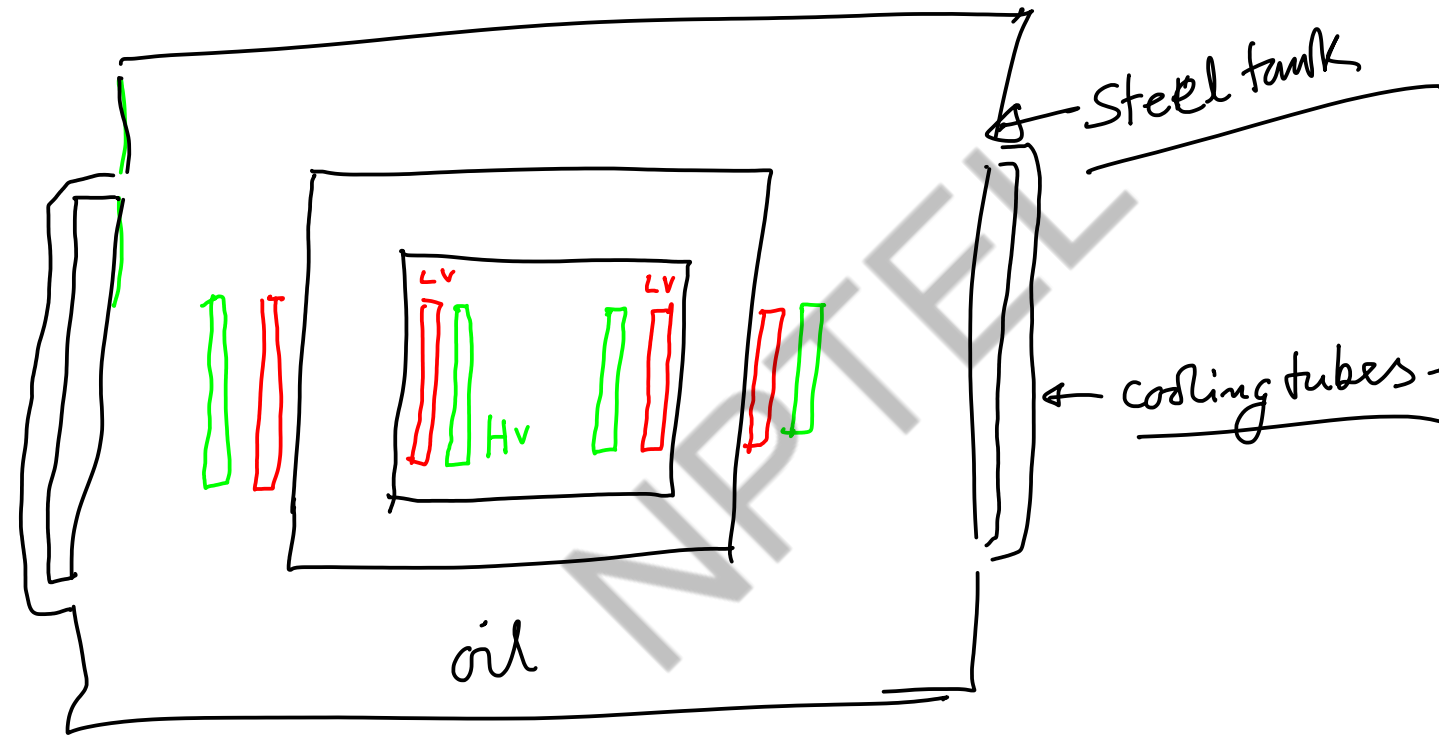Area available to dissipate the losses in a large transformer will be less.
Hence temp. rise will be more.



$$P_{\text{loss}} = \int_{\text{surface}} \lambda \theta_{\text{temp}} \quad \downarrow \text{emissivity } \tilde{\epsilon}$$
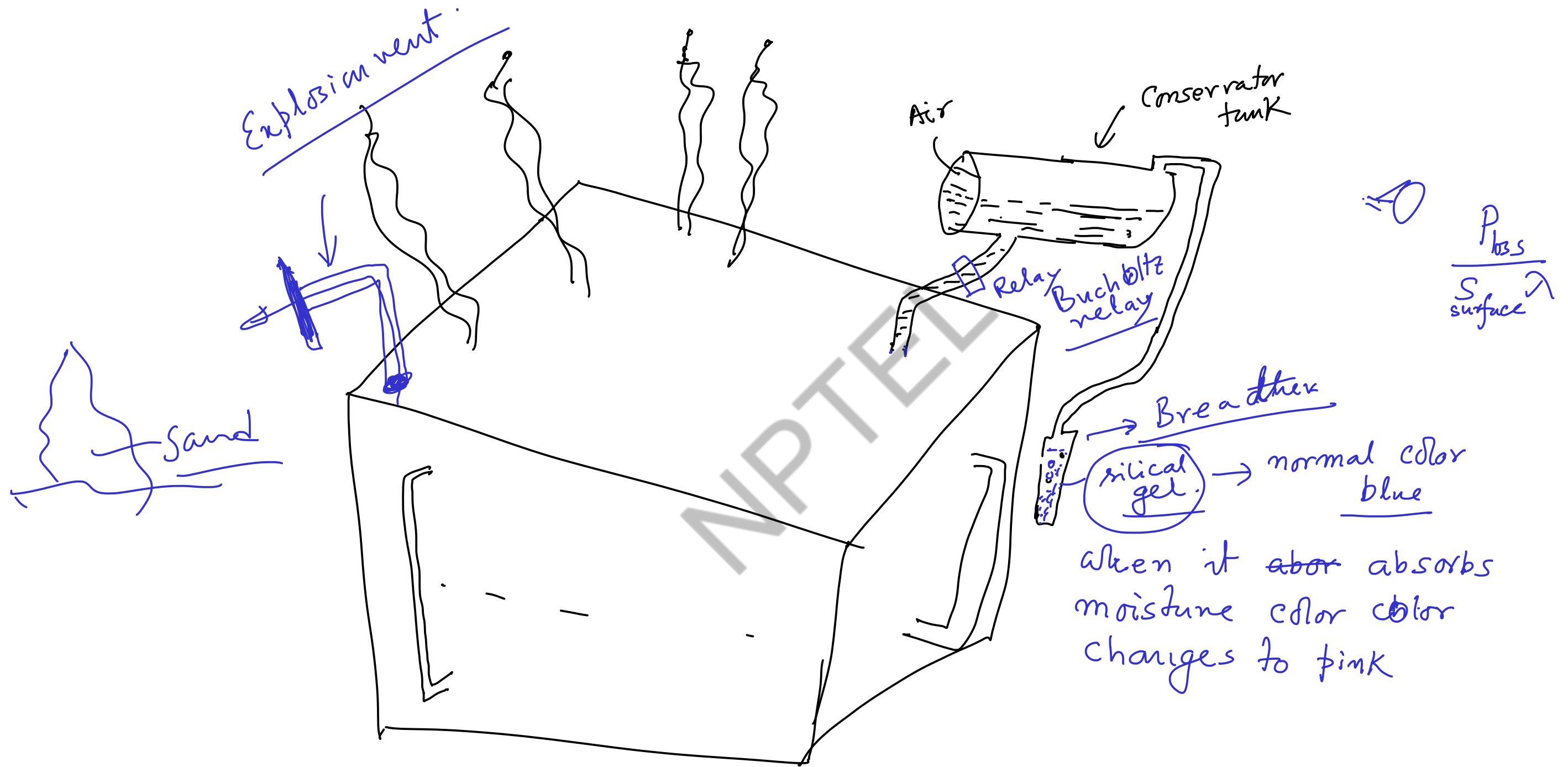
$$\theta_{\text{temp rise}} = \frac{P_{\text{loss}}}{\text{Surface}}$$




dec-53.

AN $\rightarrow$ air natural

ANOL $\rightarrow$ air natural & oil natural

Radiators

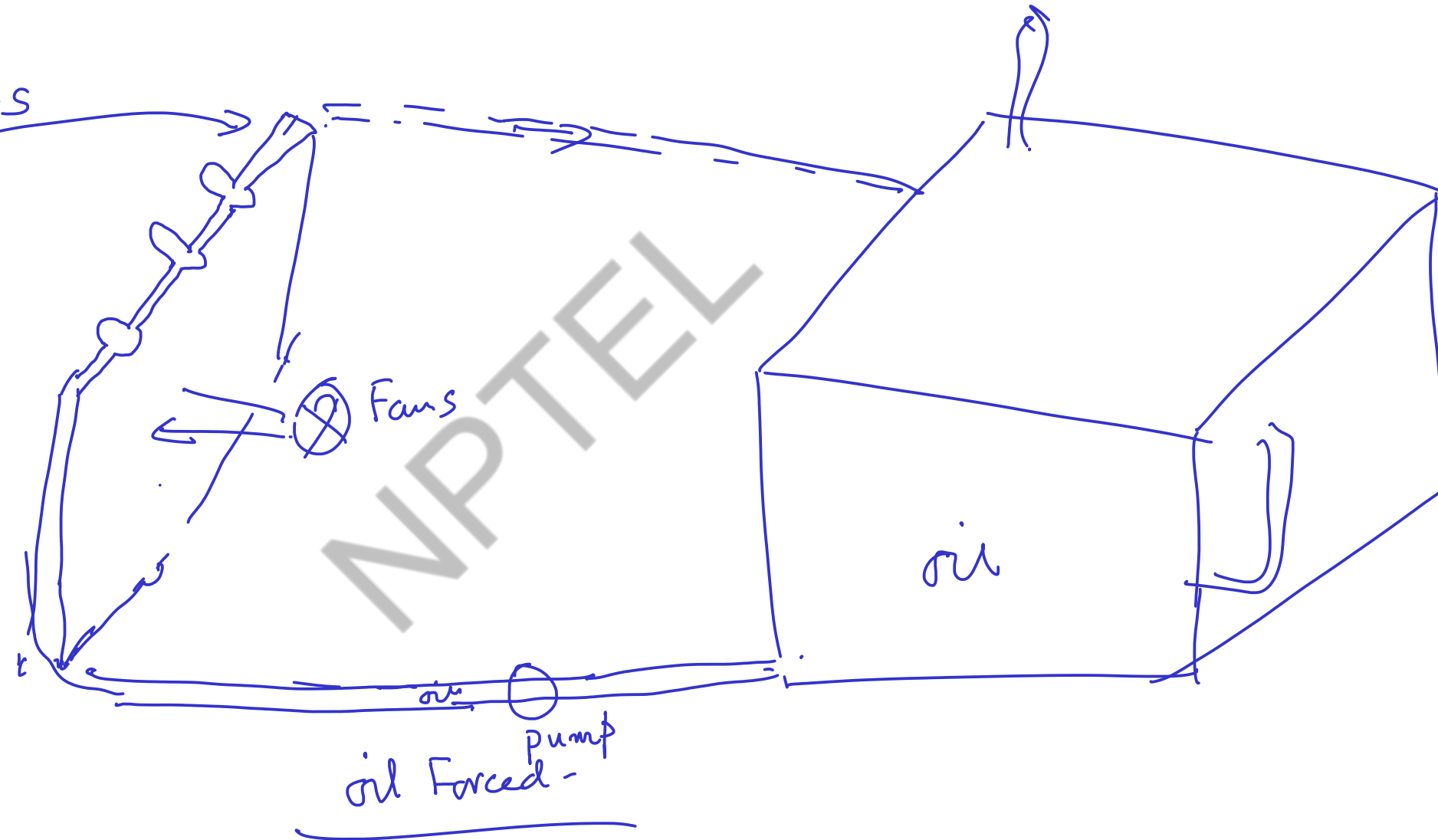

output equⁿ of 3-phase core type tr.


$$S = 3 V_{ph1} I_{ph1} \times 10^{-3}$$

$$\approx 3 \times 4.44 f B_{\max} \left(\delta_f A_{i \text{ gross}} \right) N_1 \delta a_1$$


$$N_1 I_1 = N_2 I_2$$

Show that




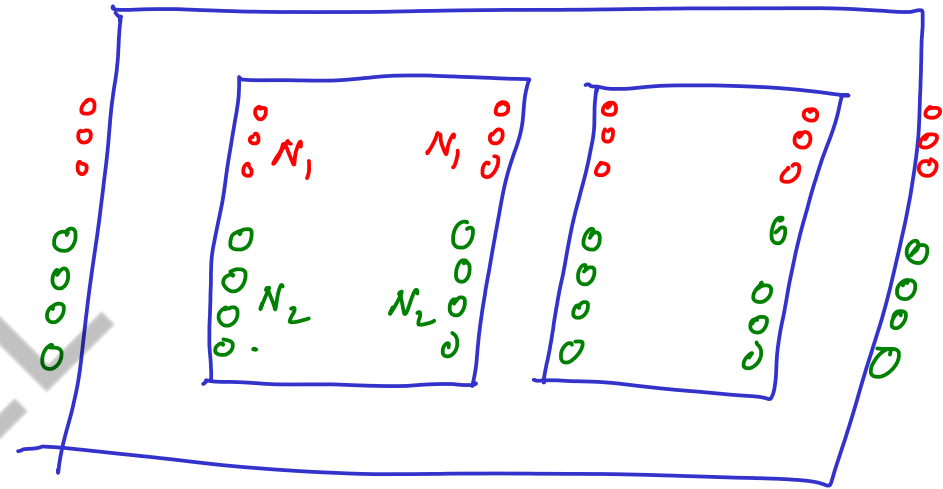
$$\rightarrow S = 3.33 f B_{\max} \delta \delta_f k_w A_{i \text{ gross}} A_w$$


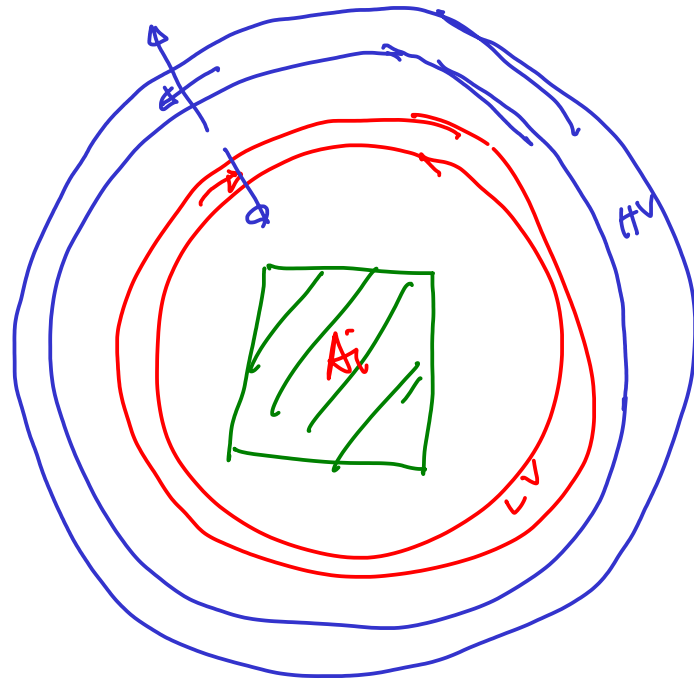
$$k_w = \frac{2 N_1 a_1 + 2 N_2 a_2}{A_w}$$



tap changers

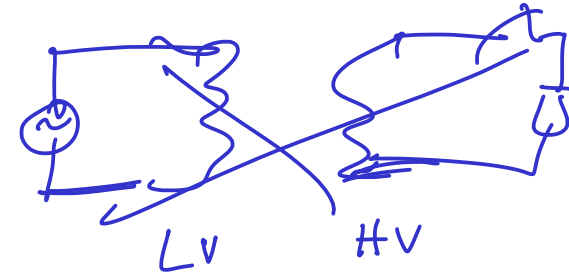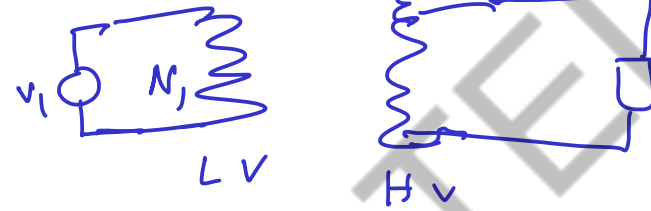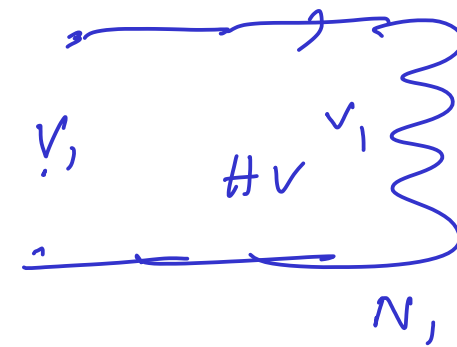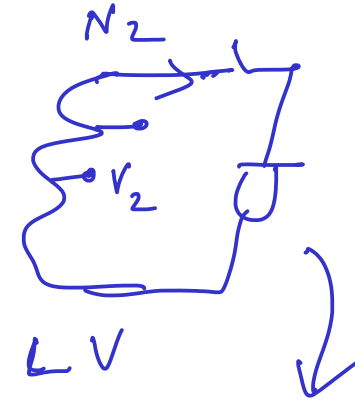

ON Load tap changers
should be on which side?

Ans:- on HV side?

