



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Semiconductor Memory

Santanu Chattopadhyay

Electronics and Electrical Communication Engineering

Introduction


- There are two types of memories that are used in digital systems:

Random-access memory(RAM): perform both the write and read operations.

Read-only memory(ROM): perform only the read operation.
- The read-only memory is a programmable logic device. Other such units are the programmable logic array(PLA), the programmable array logic(PAL), and the field-programmable gate array(FPGA).

Random-Access Memory

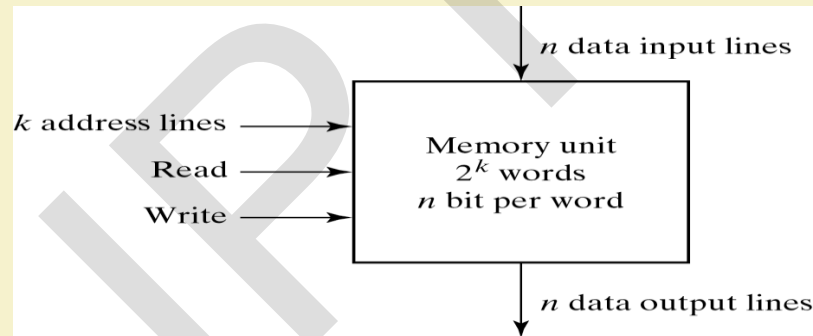- A memory unit stores **binary information in groups of bits** called **words**.
 - 1 byte = 8 bits
 - 1 word = 2 bytes (or more)
- The communication between a memory and its **environment is achieved** through **data input and output lines**, **address selection lines**, and **control lines** that specify the direction of transfer.



Block Diagram of a Memory Unit

Content of a memory

- Each **word in memory** is assigned an **identification number**, called an **address**, starting from 0 up to 2^k-1 , where k is the **number of address lines**.
- The number of words in a memory with one of the letters $K=2^{10}$, $M=2^{20}$, or $G=2^{30}$.

$$64K = 2^{16} \quad 2M = 2^{21} \quad 4G = 2^{32}$$

Memory address		Memory content
Binary	decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

Content of a 1024×16 Memory

Write and Read operations

- Transferring a new word to be stored into memory:
 1. Apply the **binary address** of the desired word to the **address lines**.
 2. Apply the **data bits** that must be stored in memory to the **data input lines**.
 3. **Activate the write input.**

Write and Read operations


- Transferring a stored word out of memory:
 1. Apply the **binary address** of the desired word to the **address lines**.
 2. **Activate the read input.**
- Commercial memory sometimes provide the **two control inputs** for **reading and writing** in a somewhat different configuration.

Control Inputs to Memory Chip

Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word


Timing Waveforms (write)

 - The **access time** and **cycle time** of the memory must be within a time equal to a **fixed number of CPU clock cycles**.
- The memory enable and the read/write signals must be activated after the signals in the address lines are stable to avoid destroying data in other memory words.
- Enable and read/write signals must stay active for at least 50ns.



Timing Waveforms (read)

 - The CPU can transfer the data into one of its internal registers during the **negative transition of T3**.



Types of memories

- In **random-access memory**, the word locations may be thought of as **being separated in space**, with each word occupying one particular location.
- In **sequential-access memory**, the information **stored in some medium is not immediately accessible**, but is **available only certain intervals of time**. A **magnetic disk or tape** unit is of this type.

Types of memories

- In a **random-access memory**, the **access time is always the same** regardless of the particular location of the word.
- In a **sequential-access memory**, the time it takes to access a word depends on the position of the word with respect to the reading head position; therefore, the **access time is variable**.

Static RAM

- SRAM consists essentially of **internal latches** that store the binary information.
- The stored information remains valid as long as power is applied to the unit.
- SRAM is easier to use and has **shorter read and write cycles**.
- **Low density, low capacity, high cost, high speed, high power consumption.**

Dynamic RAM

- DRAM stores the binary information in the **form of electric charges on capacitors**.
- The **capacitors** are provided inside the chip by **MOS transistors**.
- The capacitors tends to discharge with time and must be periodically recharged by **refreshing the dynamic memory**.

Dynamic RAM

- DRAM offers reduced power consumption and larger storage capacity in a single memory chip.
- High density, high capacity, low cost, low speed, low power consumption.

Types of memories


- Memory units that **lose stored information** when power is turned off are said to be **volatile**.
- Both static and dynamic, are of this category since the binary cells need external power to maintain the stored information.
- Nonvolatile memory, such as magnetic disk, ROM, retains its stored information after removal of power.

Memory decoding

- The equivalent logic of a binary cell that stores one bit of information is shown below.

Read/Write = 0, select = 1, input data to S-R latch

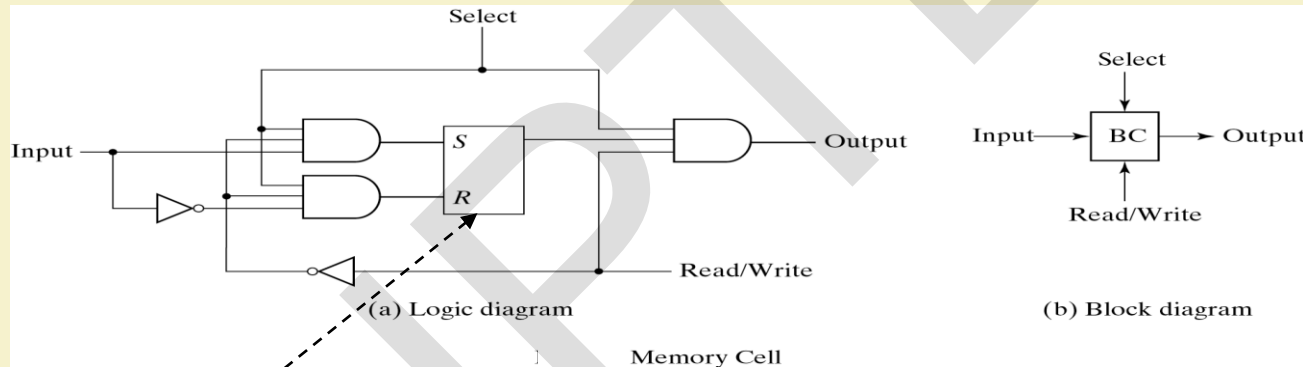
Read/Write = 1, select = 1, output data from S-R latch



SR latch with NOR gates


4X4 RAM

- There is a need for **decoding circuits** to select the memory word specified by the input address.
- During the **read operation**, the four bits of the selected **word go through OR gates** to the output terminals.
- During the **write operation**, the data available in the input lines are transferred into the four binary cells of the selected word.
- A memory with 2^k words of n bits per word requires k address lines that go into $k \times 2^k$ decoder.

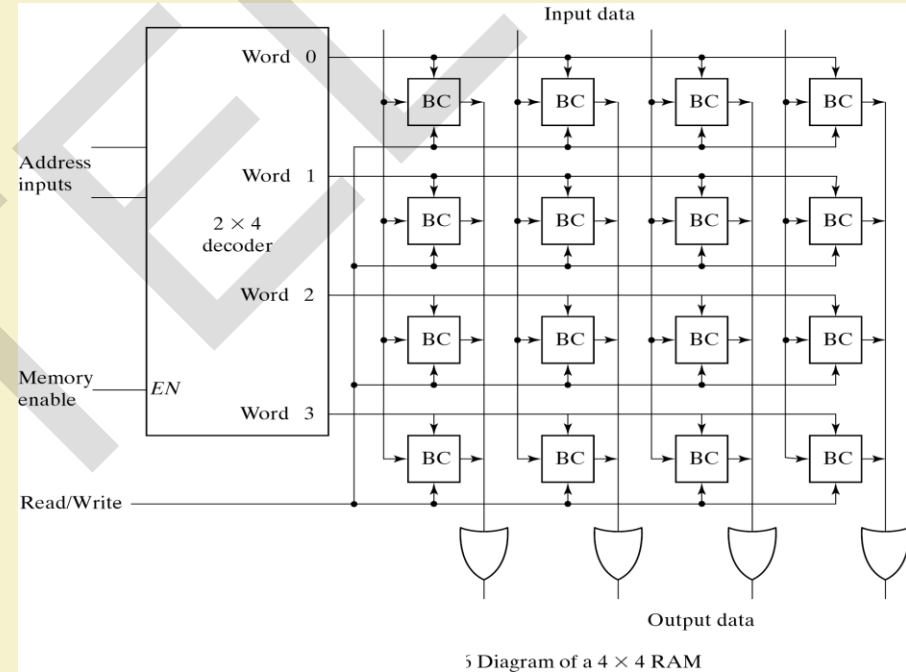

Coincident decoding

 - A decoder with k inputs and 2^k outputs requires 2^k AND gates with k inputs per gate.
- Two decoding in a two-dimensional selection scheme can reduce the number of inputs per gate.
- 1K-word memory, instead of using a single 10X1024 decoder, we use two 5X32 decoders.



Address multiplexing


- DRAMs typically have **four times the density** of SRAM.
- The **cost per bit of DRAM** storage is **three to four times less than SRAM**. Another factor is lower power requirement.

Address multiplexing

- Address multiplexing will reduce the number of pins in the IC package.
- In a two-dimensional array, the address is applied in two parts at different times, with the row address first and the column address second. Since the same set of pins is used for both parts of the address, so can decrease the size of package significantly.

Address multiplexing for 64K DRAM

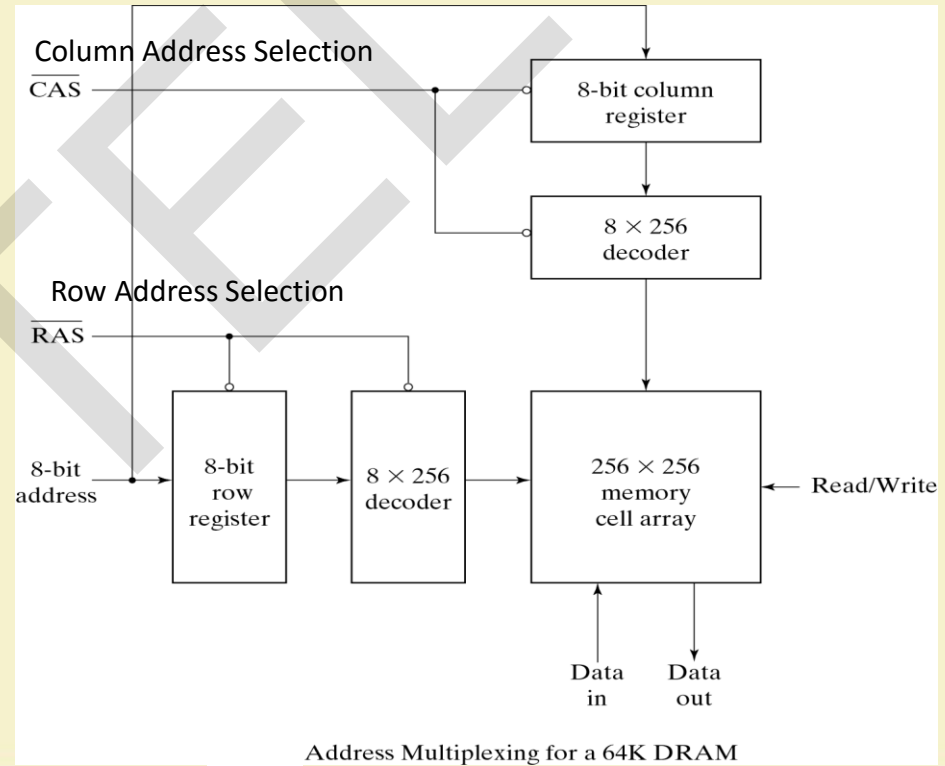- After a time equivalent to the settling time of the row selection, RAS goes back to the 1 level.
- Registers are used to store the addresses of the row and column.
- CAS must go back to the 1 level before initializing another memory operation.



Error detection and correction

- It is protecting the occasional errors in storing and retrieving the binary information.
- Parity can be used to check the error, but it can't be corrected.
- An error-correcting code generates multiple parity check bits that are stored with the data word in memory.

Hamming Code

- One of the most **commonly used** in RAM was devised by R. W. Hamming (called Hamming code).

- In Hamming code:

k = parity bits in n -bit data word,

forming a new word of $n + k$ bits. Those positions numbered as a power of 2 are reserved for the parity bits.

the remaining bits are the data bits.

Hamming Code

Ex. Consider the 8-bit data word 11000100. we include four parity bits with it and arrange the 12 bits as follows:

Bit position:	1	2	3	4	5	6	7	8	9	10	11	12
	P_1	P_2	1	P_4	1	0	0	P_8	0	1	0	0

$$P_1 = \text{XOR of bits}(3,5,7,9,11) = 1 \oplus 1 \oplus 0 \oplus 0 \oplus 0 = 0$$

$$P_2 = \text{XOR of bits}(3,6,7,10,11) = 1 \oplus 0 \oplus 0 \oplus 1 \oplus 0 = 0$$

$$P_4 = \text{XOR of bits}(5,6,7,12) = 1 \oplus 0 \oplus 0 \oplus 0 = 1$$

$$P_8 = \text{XOR of bits}(9,10,11,12) = 0 \oplus 1 \oplus 0 \oplus 0 = 1$$

Hamming Code

- The data is stored in memory together with the parity bit as 12-bit composite word.

Bit position: 1 2 3 4 5 6 7 8 9 10 11 12
 0 0 1 1 1 0 0 1 0 1 0 0

- When read from memory, the parity is checked over the same combination of bits including the parity bit.

$$C_1 = \text{XOR of bits}(3,5,7,9,11)$$

$$C_2 = \text{XOR of bits}(3,6,7,10,11)$$

$$C_4 = \text{XOR of bits}(5,6,7,12)$$

$$C_8 = \text{XOR of bits}(9,10,11,12)$$

Error-Detection

- A 0 check bit designates an even parity over the checked bits and a 1 designates an odd parity.
- Since the bits were stored with even parity, the result,
 $C = C_8C_4C_2C_1 = 0000$, indicates that no error has occurred.
- If $C \neq 0$, then the 4-bit binary number formed by the check bits gives the position of the erroneous bit.

Example

Bit position:	1	2	3	4	5	6	7	8	9	10	11	12	
	0	0	1	1	1	0	0	1	0	1	0	0	No error
	1	0	1	1	1	0	0	1	0	1	0	0	Error in bit 1
	0	0	1	1	0	0	0	1	0	1	0	0	Error in bit 5

- Evaluating the XOR of the corresponding bits, get the four check bits

	C_8	C_4	C_2	C_1
For no error:	0	0	0	0
with error in bit 1:	0	0	0	1
with error in bit 5:	0	1	0	1

Hamming Code

- The **Hamming Code** can be used for data words of any length.
- Total bit in Hamming Code is $n + k$ bits, the syndrome value C consists of k bits and has a range of 2^k value between 0 and $2^k - 1$. The range of k must be equal to or greater than $n + k$, giving the relationship

$$2^k - 1 \geq n + k$$

Range of Data Bits for k Check Bits

Number of Check Bits, k	Range of Data Bits, n
3	2-4
4	5-11
5	12-26
6	27-57
7	58-120

Single-Error correction, Double-Error detection

- The Hamming Code can detect and correct only a single error.
- By adding another parity bit to the coded word, the Hamming Code can be used to correct a single error and detect double errors. Becomes 001110010100P₁₃.

001110010100 P₁₃ → 001110010100 1

P = XOR(001110010100 1)

if P = 0, the parity is correct (even parity), but if P = 1, then the parity over the 13 bits is incorrect (odd parity).


the following four cases can occur:

Single-Error correction, Double-Error detection

 1. If $C = 0$ and $P = 0$, no error occurred
2. If $C \neq 0$ and $P = 1$, a single error occurred that can be corrected
3. If $C \neq 0$ and $P = 0$, a double error occurred that is detected but that cannot be corrected
4. If $C = 0$ and $P = 1$, an error occurred in the P_{13} bit

Read-Only Memory


- A block diagram of a ROM is shown below. It consists of k address inputs and n data outputs.
- The number of words in a ROM is determined from the fact that k address input lines are needed to specify 2^k words.



ROM Block Diagram

Construction of ROM

 - Each output of the decoder represents a memory address.
- Each OR gate must be considered as having 32 inputs.
- A $2^k \times n$ ROM will have an internal $k \times 2^k$ decoder and n OR gates.



Truth table of ROM

- A programmable connection between two lines is logically equivalent to a switch that can be altered to either be close or open.
- Intersection between two lines is sometimes called a cross-point.


ROM Truth Table (Partial)

Inputs					Outputs							
I4	I3	I2	I1	I0	A7	A6	A5	A4	A3	A2	A1	A0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		⋮					⋮					
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

Programming the ROM

In Table, 0 → no connection
 1 → connection

 Address 3 = 10110010 is permanent storage using fuse link



X : means connection

1 Programming the ROM According to Table 3

Combinational circuit implementation

- The **internal operation** of a ROM can be interpreted in two way: **First**, a memory unit that contains a fixed pattern of stored words. **Second**, implements a combinational circuit.
- Previous figure may be considered as a combinational circuit with eight outputs, each being a function of the five input variables.

$$A_7(I_4, I_3, I_2, I_1, I_0) = \Sigma(0, 2, 3, \dots, 29)$$

Sum of minterms

In Table, output A_7

Example


- Design a combinational circuit using a ROM. The circuit accepts a 3-bit number and generates an output binary number equal to the square of the input number.

Derive truth table first

Truth Table for Circuit

Inputs			Outputs						Decimal
A ₂	A ₁	A ₀	B ₅	B ₄	B ₃	B ₂	B ₁	B ₀	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

Example

 

(a) Block diagram

A_2	A_1	A_0	B_5	B_4	B_3	B_2
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table

ROM Implementation

Types of ROMs

- The required paths in a ROM may be programmed in four different ways.
 1. **Mask programming**: fabrication process
 2. **Read-only memory or PROM**: blown fuse /fuse intact
 3. **Erasable PROM or EPROM**: placed under a special ultraviolet light for a given period of time will erase the pattern in ROM.
 4. **Electrically-erasable PROM(EEPROM)**: erased with an electrical signal instead of ultraviolet light.

Combinational PLDs

- A **combinational PLD** is an integrated circuit with **programmable** gates divided into an **AND array** and an **OR array** to provide an **AND-OR** sum of product implementation.
- **PROM**: fixed **AND** array constructed as a decoder and **programmable OR** array.
- **PAL**: **programmable AND** array and **fixed OR** array.
- **PLA**: both the **AND** and **OR** arrays can be programmed.


Combinational PLDs



(a) Programmable read-only memory (PROM)



(b) Programmable array logic (PAL)

 

(c) Programmable logic array (PLA)

Basic Configuration of Three PLDs


Programmable Logic Array

- The decoder in PROM example can be replaced by an array of AND gates that can be programmed to generate any product term of the input variables.
- The product terms are then connected to OR gates to provide the sum of products for the required Boolean functions.
- The output is inverted when the XOR input is connected to 1 (since $x \oplus 1 = x'$). The output doesn't change and connect to 0 (since $x \oplus 0 = x$).

PLA

$$F1 = AB' + AC + A'BC'$$

$$F2 = (AC + BC)'$$

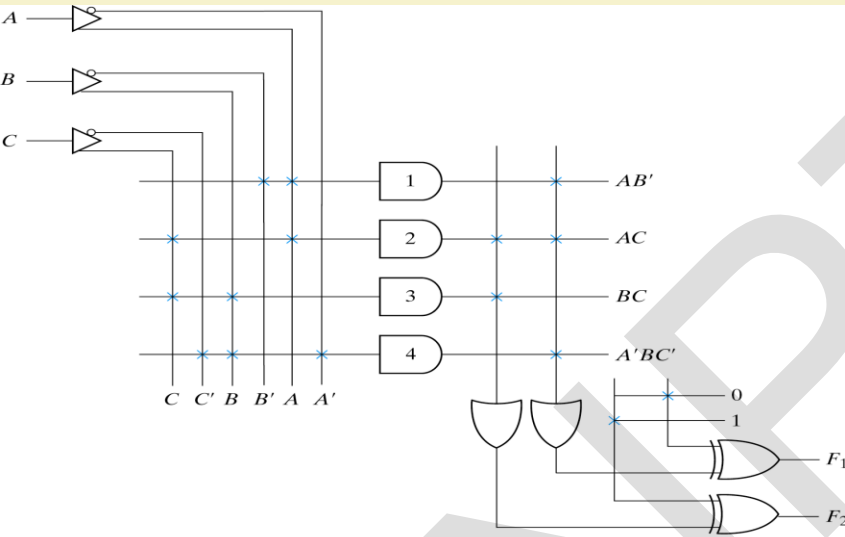

PLA with 3 Inputs, 4 Product Terms, and 2 Outputs

PLA Programming Table

		Inputs			Outputs	
					(T)	(C)
		A	B	C	F ₁	F ₂
AB'	1	1	0	-	1	-
AC	2	1	-	1	1	1
BC	3	-	1	1	-	1
A'BC'	4	0	1	0	1	-

Programming Table

1. First: list the product terms numerically
2. Second: specify the required paths between inputs and AND gates
3. Third: specify the paths between the AND and OR gates
4. For each output variable, we may have a T(ure) or C(complement) for programming the XOR gate

Simplification of PLA

- Careful investigation must be undertaken in order to **reduce the number of distinct product terms**, PLA has a **finite number of AND gates**.
- Both the **true and complement of each function** should be simplified to see which one can be **expressed with fewer product terms** and which one provides product terms that are common to other functions.

Example

Implement the following two Boolean functions with a PLA:

$$F_1(A, B, C) = \sum(0, 1, 2, 4)$$

$$F_2(A, B, C) = \sum(0, 5, 6, 7)$$

The two functions are simplified in the maps shown.

		BC			
		00	01	11	10
A	0	1	1	0	1
	1	1	0	0	0

1 elements

$$F_1 = A'B' + A'C' + B'C'$$

0 elements

$$F_1 = (AB + AC + BC)'$$

		BC			
		00	01	11	10
A	0	1	0	0	0
	1	0	1	1	1

$$F_2 = AB + AC + A'B'C'$$

$$F_2 = (A'C + A'B + AB'C)'$$

PLA table by simplifying the function


- Both the **true** and **complement** of the functions are simplified in **sum of products**.
- We can find the same terms from the group terms of the functions of F_1 , F_1' , F_2 and F_2' which will make the minimum terms.

$$F_1 = (AB + AC + BC)'$$

$$F_2 = AB + AC + A'B'C'$$


PLA programming table						
	Product term	Inputs			Outputs	
		A	B	C	(C) F_1	(T) F_2
AB	1	1	1	–	1	1
AC	2	1	–	1	1	1
BC	3	–	1	1	1	–
$A'B'C'$	4	0	0	0	–	1

PLA implementation

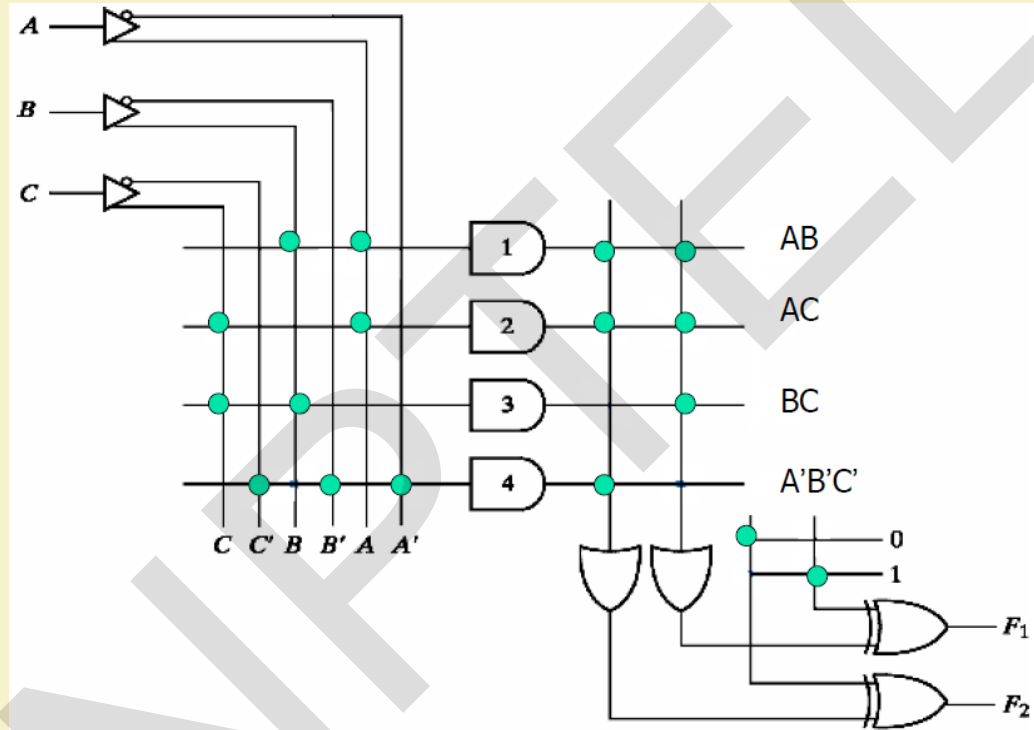

Programmable Array Logic

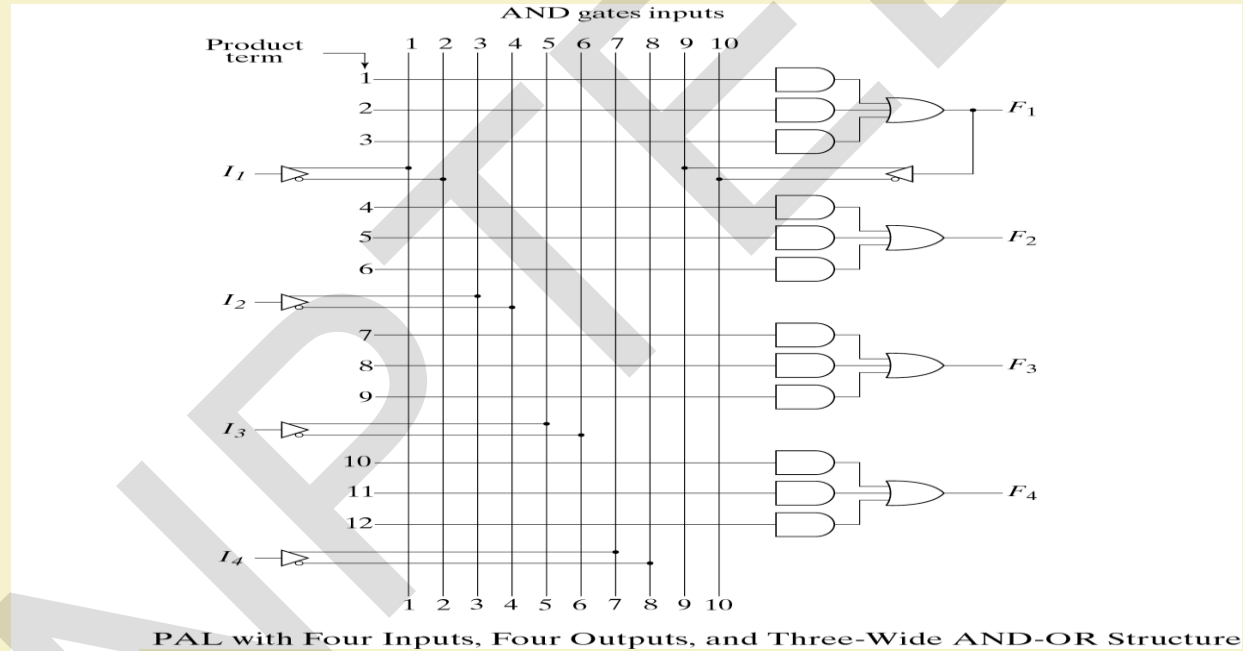- The PAL is a programmable logic device with a fixed OR array and a programmable AND array.



PAL

- When designing with a PAL, the Boolean functions must be simplified to fit into each section.
- Unlike the PLA, a product term cannot be shared among two or more OR gates. Therefore, each function can be simplified by itself without regard to common product terms.
- The output terminals are sometimes driven by three-state buffers or inverters.

Example

$$w(A, B, C, D) = \sum(2, 12, 13)$$

$$x(A, B, C, D) = \sum(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \sum(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A, B, C, D) = \sum(1, 2, 8, 12, 13)$$

Simplifying the four functions as following Boolean functions:

$$w = ABC' + A'B'CD'$$

$$x = A + BCD$$

$$y = A'B + CD + B'D'$$

$$z = ABC' + A'B'CD' + AC'D' + A'B'C'D = w + AC'D' + A'B'C'D$$

PAL Table


- z has four product terms, and we can replace by w with two product terms, this will reduce the number of terms for z from four to three.

PAL Programming Table


Product Term	AND Inputs					Outputs
	A	B	C	D	W	
1	1	1	0	—	—	$w = ABC' + A'B'CD'$
2	0	0	1	0	—	
3	—	—	—	—	—	
4	1	—	—	—	—	$x = A + BCD$
5	—	1	1	1	—	
6	—	—	—	—	—	
7	0	1	—	—	—	$y = A'B + CD + B'D'$
8	—	—	1	1	—	
9	—	0	—	0	—	
10	—	—	—	—	1	$z = w + AC'D' + A'B'C'D$
11	1	—	0	0	—	
12	0	0	0	1	—	



PAL implementation

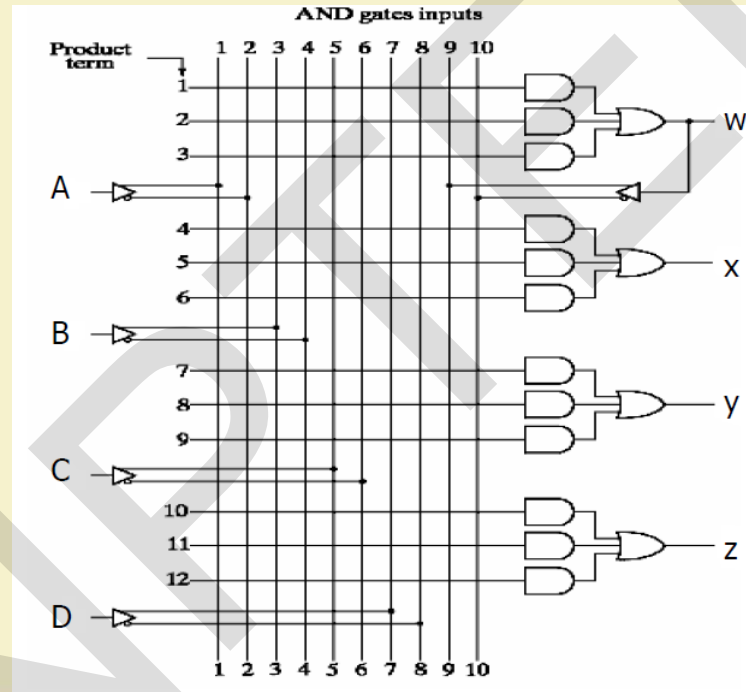

Fuse map for example

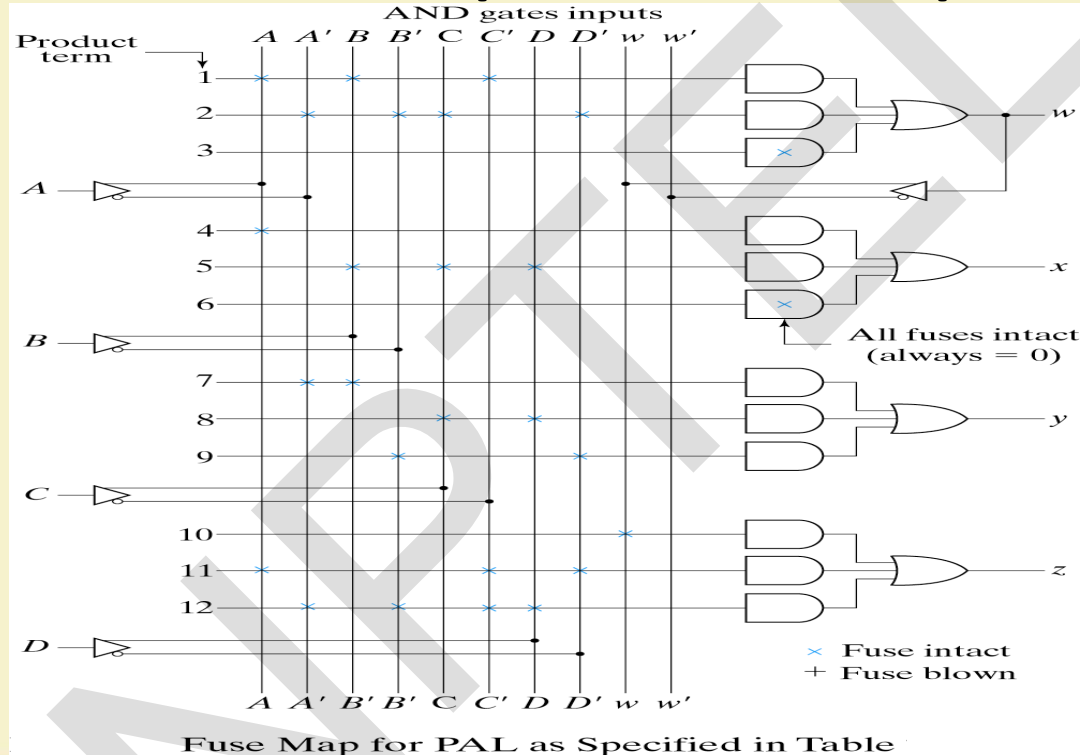

Field Programmable Gate Array (FPGA)

Santanu Chattopadhyay

Electronics and Electrical Communication Engineering



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Evolution of implementation technologies


- Logic gates (1950s-60s)
- Regular structures for two-level logic (1960s-70s)
 - muxes and decoders, PLAs
- Programmable sum-of-products arrays (1970s-80s)
 - PLDs, complex PLDs
- Programmable gate arrays (1980s-90s)
 - densities high enough to permit entirely new class of application, e.g., prototyping, emulation, acceleration

**trend toward
higher levels
of integration**




Gate Array Technology (IBM - 1970s)

 - Simple logic gates
 - combine transistors to implement combinational and sequential logic
- Interconnect
 - wires to connect inputs and outputs to logic blocks
- I/O blocks
 - special blocks at periphery for external connections
- Add wires to make connections
 - done when chip is fabbed
 - “mask-programmable”
 - construct any circuit



Field-Programmable Gate Arrays

 - Logic blocks
 - to implement combinational and sequential logic
- Interconnect
 - wires to connect inputs and outputs to logic blocks
- I/O blocks
 - special logic blocks at periphery of device for external connections
- Key questions:
 - how to make logic blocks programmable?
 - how to connect the wires?
 - *after the chip has been fabbed*



CPLD vs. FPGA


- CPLD has a somewhat restrictive structure consisting of one or more programmable sum-of-products logic arrays feeding a relatively small number of clocked registers.
- Results in less flexibility, with the advantage of more predictable timing delays and a higher logic-to-interconnect ratio.
- The FPGA architectures are dominated by interconnect. This makes them far more flexible (in terms of the range of designs that are practical for implementation within them) but also far more complex to design for.
- In practice, the distinction between FPGAs and CPLDs is often one of size as FPGAs are usually much larger in terms of resources than CPLDs.
- Typically only FPGA's contain more advanced embedded functions such as adders, multipliers, memory and other hardened functions.
- Another common distinction is that CPLDs contain embedded flash to store their configuration while FPGAs usually, but not always, require an external flash

Programmability of FPGAs

- *User programmability* of CPLDs and FPGAs is achieved via user-programmable switch technologies.
- For CPLDs, floating-gate transistors are used like EPROM or EEPROM. On the otherhand, FPGAs normally use SRAM (static RAM) or antifuse technology.
- Properties of the switches, such as, *size*, *on-resistance*, and *capacitance* dictate trade-offs in architecture.
- In SRAM based FPGAs, there is an SRAM bit corresponding to each of the programmable points within the device.

- When the device is powered-on or reset, it reads a configuration program from an off-chip memory and loads it into on-chip SRAM.
- The configuration program defines the logic function realized by individual logic blocks and interconnections.
- Devices using SRAM based switching can be reprogrammed easily by just changing the configuration program.
- FPGAs belonging to *Xilinx, Plassey, Algotronix, Concurrent Logic, Toshiba*, etc. are SRAM based.
- SRAM provides fast reprogrammability at the cost of large area (at least five transistors for cell and one for switch).


SRAM controlled switching

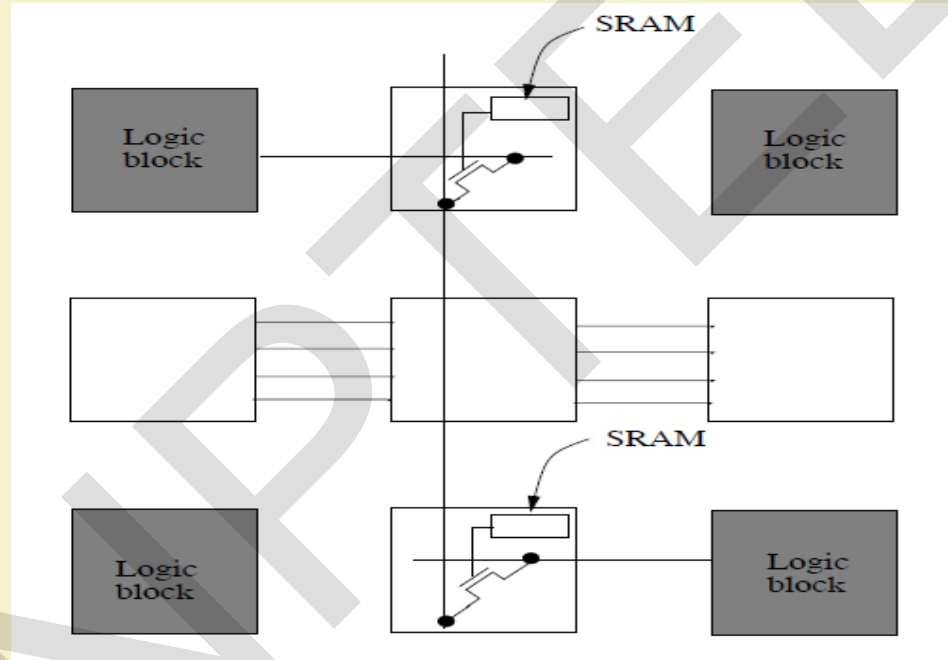

Antifuse based programming

- Antifuses are originally open-circuit, offering very high resistance. However, on programming (applying a 11-20V across terminals), the resistance becomes very low, thus, establishing electric connections.
- Antifuses can be made very small using modified CMOS technology, thus offering very high device density, compared to SRAM.
- However, once programmed, they cannot be reused. Thus, the device is one-time programmable.
- The structure is commonly known as PLICE (Programmable Low-Impedence Circuit Element).
- PLICE uses Poly-Si and n⁺ diffusion as conductors and ONO (silicon diOxide - silicon Nitride- silicon diOxide) as an insulator.
- The advantages include small size (little more than the cross-section of two metal wires) and low series resistance.
- It has disadvantages, such as, large size of programming transistors, need of isolation transistors, and one-time programmability.
- FPGAs from *Actel*, *Quicklogic*, *Crosspoint*, etc. support antifuses.


Antifuse structure

 

Floating gate

- FPGA devices from *Altera, Plus Logic, AMD, etc.* use floating gate programming technology.
- While *Altera and Plus Logic* use ultraviolet erasable EPROM, *AMD* uses electrically
- erasable EEPROM.
- It contains a control gate and a floating gate. The transistor can be disabled by applying a high voltage between control gate and drain. This injects charge on the floating gate, increasing the threshold voltage of the transistor – disabling it.
- Charge can be removed by exposing floating gate to ultraviolet light or by erasing electrically. It provides reprogrammability and unlike SRAM, no external memory is needed to program the chip on power-up.
- However, EPROM technology requires additional processing steps, high ON resistance and high static power consumption due to pull-up resistor.

Floating gate programming

 

Comparison between programming techniques



Name	Whether reprogrammable	Whether volatile	Technology
Fuse	no	no	Bipolar
EPROM	yes, out of circuit	no	UVC MOS
EEPROM	yes, in circuit	no	EECMOS
SRAM	yes, in circuit	yes	CMOS
Antifuse	no	no	CMOS+

FPGA Logic Blocks

- There are wide variations in the logic block structure of FPGAs available from different vendors.
- They vary in number of inputs and outputs, amount of area consumed, complexity of logic functions that they can realize, total number of transistors needed, and so on.
- The logic blocks can broadly be classified into the following two categories – Fine Grain, Coarse Grain


Fine Grain Logic Block

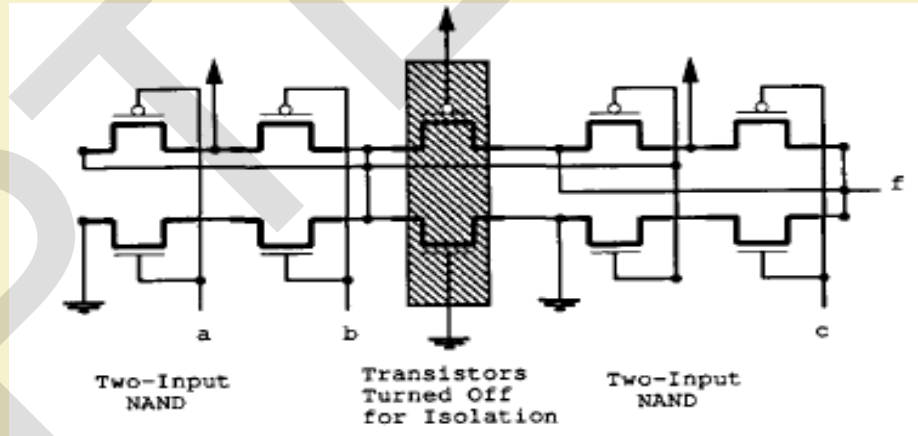 - The block contains a few transistors that can be interconnected via programming.
- *Crosspoint* FPGA uses a single transistor pair for each Boolean variable in the logic block.




$$f = ab + c'$$

Coarse Grain Block – XC4000 from Xilinx

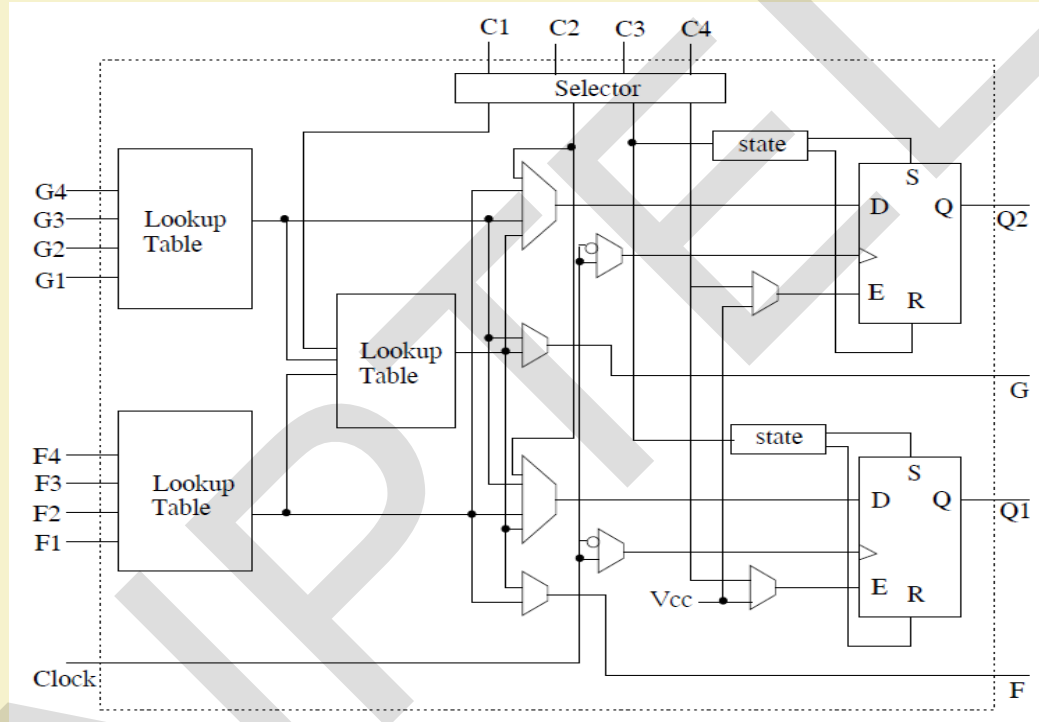


Coarse Grain Block – ACT1 from Actel

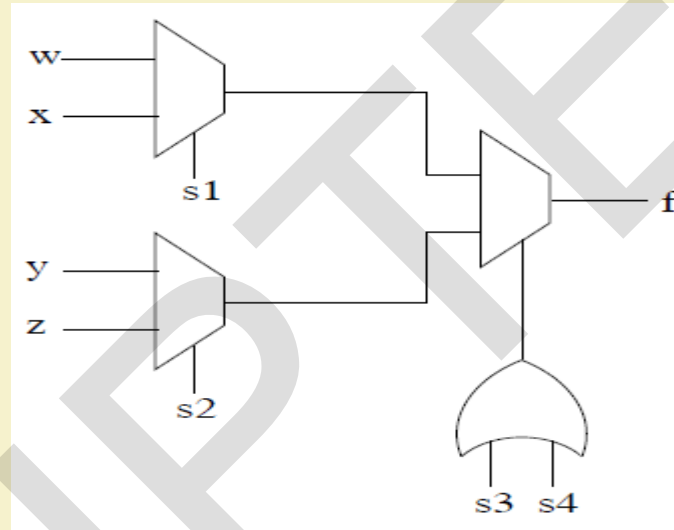

Trade-offs

- A large logic block can implement more logic within a single block, requires lesser number of logic blocks to realize a given functionality on the FPGA.
- On the other hand, a large logic block consumes more space of FPGA.
- 4-input look-up table gives best result in terms of logic synthesized and area consumed.
- A higher granularity level results in lesser delay between system input and output.
- With the increase of granularity level, average fanout increases, number of switches also increases as each block has more pins.
- Also, the length of wires increases with increase in size of logic block.

FPGA Design Flow

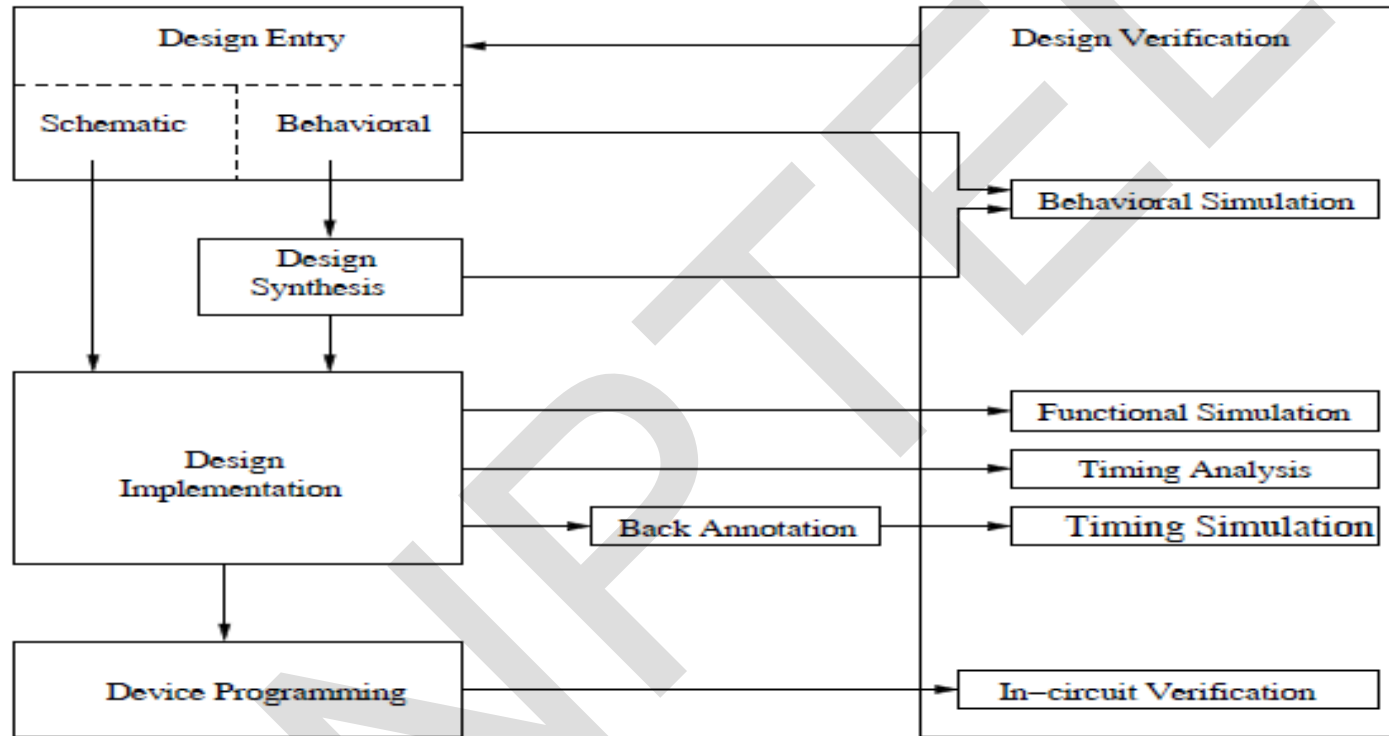

Modern FPGAs

- In addition to the basic blocks (such as, logic blocks, I/O blocks and interconnects), modern FPGAs have additional units that make the design process simpler and more efficient.
- The two major system components, difficult to implement in FPGAs are embedded memories and blocks for arithmetic calculations.
- Amongst the various calculations, multiplication is the most widely used one. Most of the modern FPGAs contain embedded logic blocks for multiplication and memories to hold data. DSP functionalities are highly facilitated by the availability of these.
- In many applications, FPGAs need to communicate with microprocessors. This has motivated many FPGA vendors to embed soft processor cores within FPGAs. This reduces the latency of communication between the microprocessor and the FPGA.

Xilinx Virtex-6 and Virtex-7 FPGA

- Each CLB of a *Virtex-6 FPGA* can be configured as one 6-input LUT or two 5-input LUTs.
- The LUT can also be used as a 64-bit RAM or two 32-bit RAMs.
- Apart from this, every *Virtex-6 FPGA* has 156-1064 (depending upon the subfamily) dual port block RAMs, each storing 36 Kbits.
- They also possess many dedicated, full-custom, low-power DSP slices. Each slice contains 25, 18-bit, 2's complement multiplier and a 48-bit accumulator.
- Each *Virtex-6* device has a 17-channel, 10-bit ADC and 8-72 Gbps transceiver.
- The next advanced version, *Virtex-7* is a 3D IC with many improved features.
- The peak transceiver speed varies between 12.5-28.05 Gbps with 36-96 transceivers.
- It can perform 2756-5314 giga multiply accumulates (GMACS) and contains 46.5-85 Mb block RAM, PCI express bus interface, and upto 1200 I/O pins.