

 


# Conversion to NAND

 

# Conversion to NOR

 

# Exclusive-OR (XOR) Function

- XOR (also  $\oplus$ ) : the “not-equal” function
- $\text{XOR}(X,Y) = X \oplus Y = X'Y + XY'$
- Identities:
  - $X \oplus 0 = X$
  - $X \oplus 1 = X'$
  - $X \oplus X = 0$
  - $X \oplus X' = 1$
- Properties:
  - $X \oplus Y = Y \oplus X$
  - $(X \oplus Y) \oplus W = X \oplus (Y \oplus W)$




# XOR function implementation

- $\text{XOR}(a,b) = ab' + a'b$
- Straightforward: 5 gates
  - 2 inverters, two 2-input ANDs, one 2-input OR
  - 2 inverters & 3 2-input NANDs
- Nonstraightforward:
  - 4 NAND gates



# XOR circuit with 4 NANDs

 

# Exclusive-NOR (XNOR) Function

- XNOR: the “equality” function
- $\text{XNOR}(a,b) = ab + a'b'$
- Observe that  $\text{XNOR}(a,b) = (\text{XOR}(a,b))'$ 
  - $(a \oplus b)' = (a'b + ab')'$   
 $= (a'b)'(ab')'$   
 $= (a + b')(a' + b)$   
 $= ab + a'b'$
- $a \oplus b' = (a \oplus b)' = a' \oplus b$



# Odd Function

- $x \oplus y = x'y + xy'$
- $x \oplus y \oplus z = xy'z' + x'yz' + x'y'z + xyz$
- $x \oplus y \oplus z \oplus w = x'yzw + xy'zw + xyz'w + xyzw' + x'y'z'w + x'yz'w' + x'y'zw' + xy'z'w'$
- ... Observe a pattern here?
- An n-input XOR function is implied (=1) by all the minterms that have an odd # of 1s
- Thus, XOR is also known as the ***odd function***



# Odd Function (cont.)

		Y			
		00	01	11	10
X	0		1		1
	1	1		1	

(a)  $X \oplus Y \oplus Z$

		C			
		00	01	11	10
A	00		1		1
	01	1		1	
	11		1		1
	10	1		1	

(b)  $A \oplus B \oplus C \oplus D$

Minterms are ALWAYS ***distance two*** from each other





IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES



## Odd Function (cont.)

  

# Even Function

- How would you implement an even *function*?

The complement of XOR  $\rightarrow$  XNOR



# Parity Generation and Checking

- Odd and even functions can be used to implement parity checking circuits used for error detection and correction.
- Use even parity as example.
- *Parity generator*: the circuit that generates the parity bit before transmitting.
- *Parity checker*: the circuit that checks the parity in the receiver.



# Even Parity Generation

Three-Bit Message			Parity Bit
X	Y	Z	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

- $P(X,Y,Z)$  must produce a 1 for all the input combinations that contain an odd number of 1s
- Thus, it is a 3-input odd function  $P = X \oplus Y \oplus Z$



# Even Parity Checking

How would you implement a parity checker for the previous example?

Use a 4-input XOR circuit (odd function)

$$C = X \oplus Y \oplus Z \oplus P \rightarrow 1 \text{ indicates an error}$$

OR

A 4-input XNOR circuit (even function)

$$C = (X \oplus Y \oplus Z \oplus P)' \rightarrow 1 \text{ indicates a pass}$$



IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES

# Logic Families

- DTL
- TTL
- ECL
- NMOS
- PMOS
- CMOS
- Etc.



# Static CMOS Logic Family




IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES
 
# Dopants


- Silicon is a semiconductor
- Pure silicon has no free carriers and conducts poorly
- Adding dopants increases the conductivity
- Group V: extra electron (n-type)
- Group III: missing electron, called hole (p-type)





 
# nMOS Operation

- Body is commonly tied to ground (0 V)
- When the gate is at a low voltage:
  - P-type body is at low voltage
  - Source-body and drain-body diodes are OFF
  - No current flows, transistor is OFF




 
# Transistors as Switches

- We can view MOS transistors as electrically controlled switches
- Voltage at gate controls path from source to drain



# CMOS Inverter

A	Y
0	
1	

  


IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES
 
# Inverter Cross-section

- Typically use p-type substrate for nMOS transistors
- Requires n-well for body of pMOS transistors




IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES

# Static CMOS

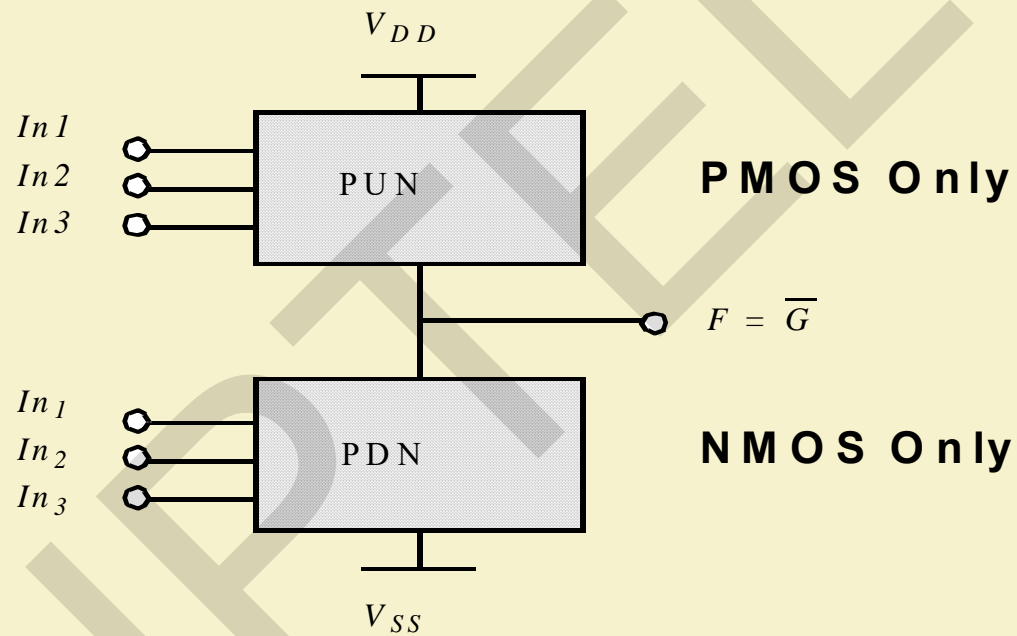

**PUN and PDN are Dual Networks**



IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES


## Complementary CMOS Logic Style Construction

- **PUP is the DUAL of PDN**  
(can be shown using DeMorgan's Theorem's)

$$\overline{A + B} = \bar{A}\bar{B}$$

$$\overline{AB} = \bar{A} + \bar{B}$$

 - **The complementary gate is inverting**




**AND = NAND + INV**



# Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 

PDN:  $G = A B \Rightarrow$  Conduction to GND

PUN:  $F = \overline{A + B} = \overline{AB} \Rightarrow$  Conduction to  $V_{DD}$


$$\overline{G(In_1, In_2, In_3, \dots)} \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$$



# Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Truth Table of a 2 input NOR gate

 


$$\text{OUT} = \overline{A + B}$$





## Example Gate: COMPLEX CMOS GATE

 

## Properties of Complementary CMOS Gates

- High noise margin.  $V_{OH}$  and  $V_{OL}$  are at  $V_{DD}$  and GND respectively
- No static power consumption
- Comparable rise and fall times
- Highly compact structure



# Timing diagrams and Hazards




IIT KHARAGPUR




NPTEL ONLINE  
CERTIFICATION COURSES

# Noise Margins

 

 
# Logic Level Matching

- Levels at output of one gate must be sufficient to drive another gate


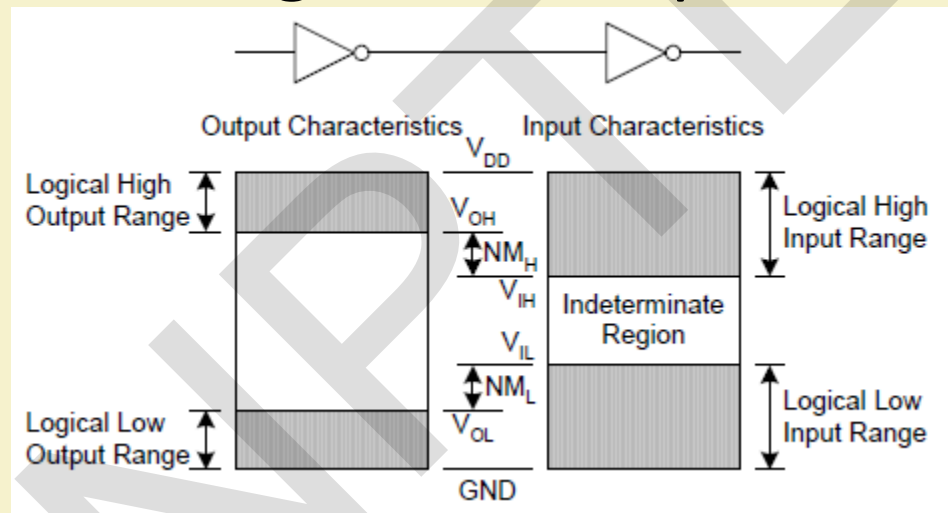
# Noise Margins

- How much noise a gate input see before it does not recognize the input?




# Noise Margin

- Noise Margin = Voltage difference between the output of one gate and input of next. Noise must exceed noise margin to make the second gate produce wrong output.


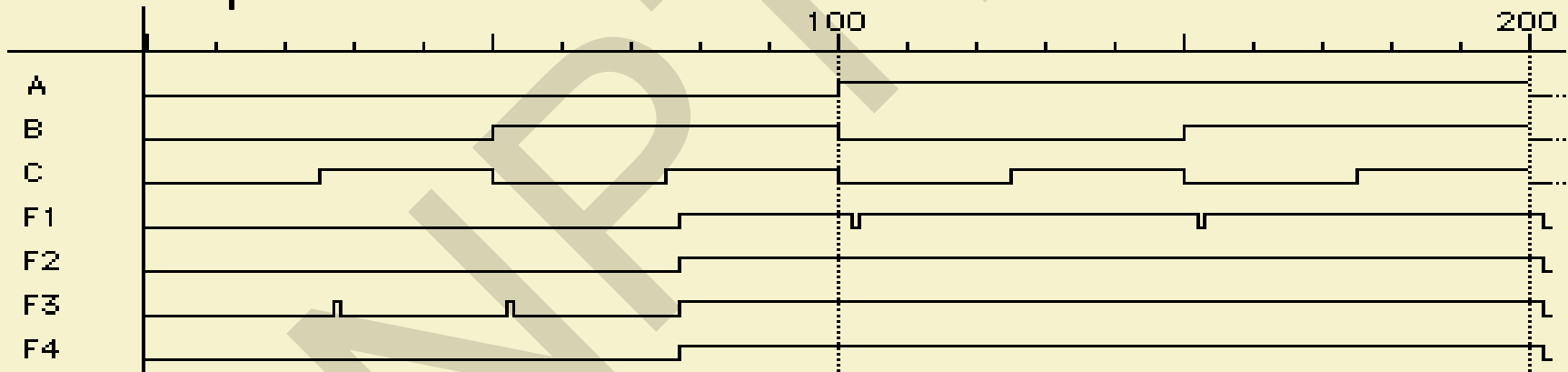
# Timing diagrams (waveforms)



- Shows time-response of circuits
- Like a sideways truth table
- Example:  $F = A + BC$




  
# Timing diagrams


- Real gates have real delays
- Example:  $A' \cdot A = 0$ ?



- Delays cause transient  $F=1$



# $F = A + BC$ in 2-level logic

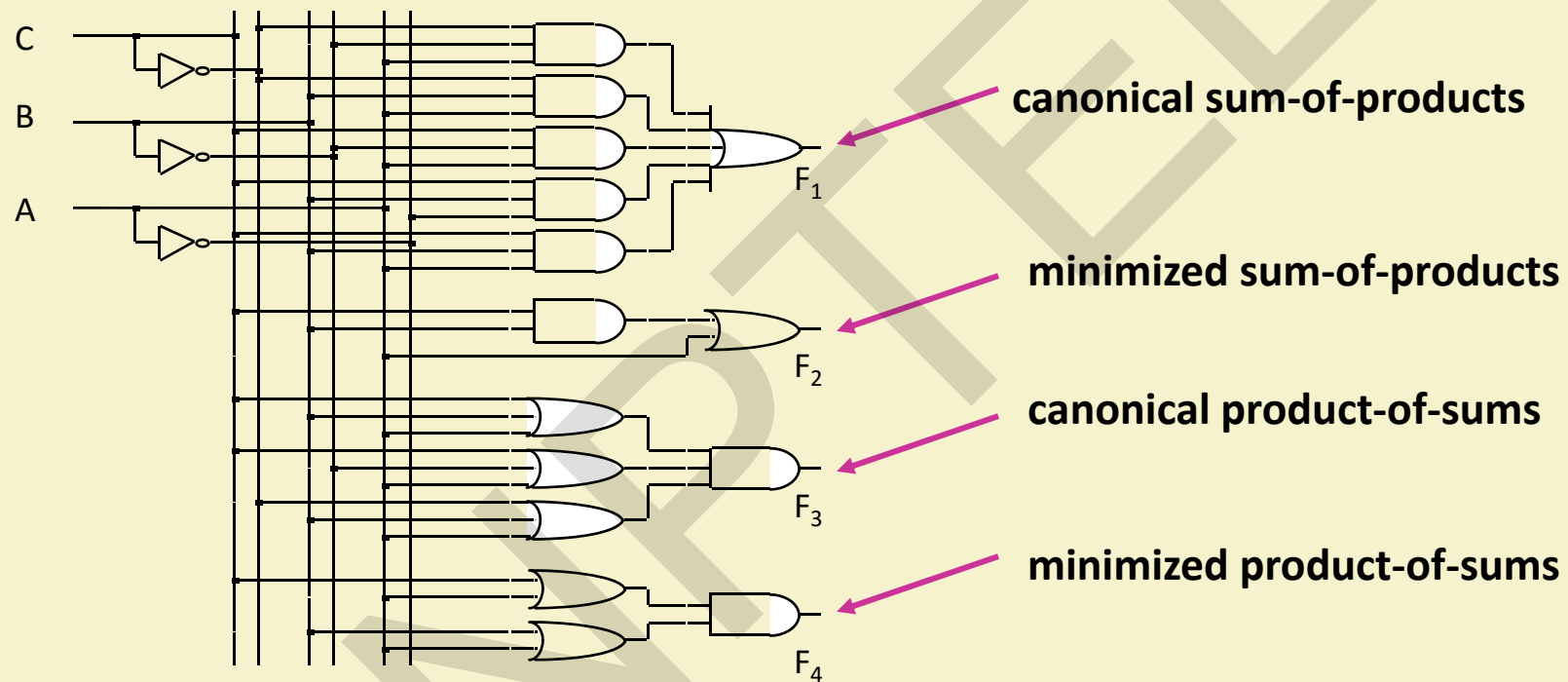


IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES
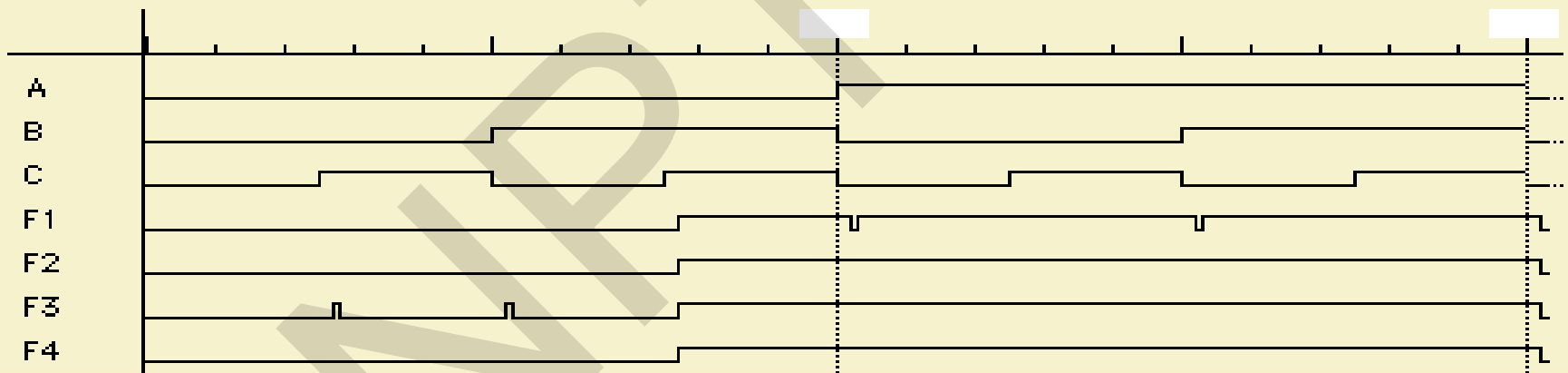
# Timing diagram for $F = A + BC$

- Time waveforms for  $F_1 - F_4$  are identical except for glitches



# Hazards and glitches

- **glitch**: unwanted output
- A circuit with the potential for a glitch has a **hazard**.
- Glitches occur when different pathways have different delays
  - Causes circuit noise
  - Dangerous if logic makes a decision while output is unstable






# Hazards and glitches

- Solutions
  - Design hazard-free circuits
    - Difficult when logic is multilevel
  - Wait until signals are stable


   
# Types of hazards

- Static 1-hazard
  - Output should stay logic 1
  - Gate delays cause brief glitch to logic 0
- Static 0-hazard
  - Output should stay logic 0
  - Gate delays cause brief glitch to logic 1
- Dynamic hazards
  - Output should toggle cleanly
  - Gate delays cause multiple transitions




# Static hazards

- Often occurs when a literal and its complement momentarily assume the same value
  - Through different paths with different delays
  - Causes an (ideally) static output to *glitch*




# Static hazards

 





# Timing diagram for $F = A + BC$

 

# $F = A + BC$ in 2-level logic

 

# Timing diagram for $F = A + BC$

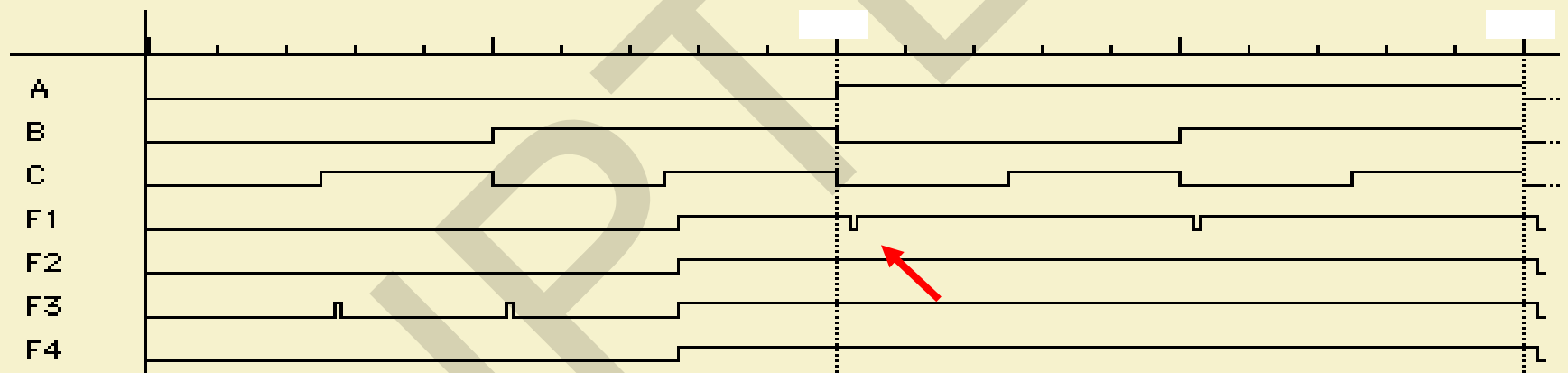


IIT KHARAGPUR




NPTEL ONLINE  
CERTIFICATION COURSES

# $F = A + BC$ in 2-level logic

 
 
# Dynamic hazards



- Often occurs when a literal assumes multiple values
  - Through different paths with different delays
  - Causes an output to toggle multiple times



Dynamic hazards



# Dynamic hazards

  

Dynamic hazard



IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES

## Eliminating static hazards

- Key idea: Glitches happen when a changing input spans separate K-map encirclements
  - Example: 1101 to 0101 change can cause a static-1 glitch

AB		A			
		00	01	11	10
CD	00	0	0	1	1
	01	1	1	1	1
	11	1	1	0	0
	10	0	0	0	0

**C**

**B**


**D**



# Eliminating static hazards

- ABCD: 1101  $\rightarrow$  0101

$$F = AC' + A'D$$

 

AB		A	
		11	10
CD	00	0	0
	01	1	1
	11	1	1
	10	0	0

Diagram illustrating the Karnaugh map for the function  $F = AC' + A'D$ . The map shows the output F for all combinations of inputs A, B, C, and D. The map is a 4x4 grid with columns labeled AB (00, 01, 11, 10) and rows labeled CD (00, 01, 11, 10). The output F is 1 for the combinations (A,B,C,D) = (1,0,0,0), (1,0,1,0), (1,1,0,0), and (1,1,1,0). The map is partitioned into two groups of four cells each, labeled A and B, indicating the prime implicants  $AC'$  and  $A'D$ .






# Eliminating static hazards

- Solution: Add redundant K-map encirclements
  - Ensure that all single-bit changes are covered by same block
  - First eliminate static-1 hazards: Use SOP form
  - If need to eliminate static-0 hazards, use POS form
- Technique only works for 2-level logic



# Eliminating static hazards

$$F = AC' + A'D + \textcolor{red}{C'D}$$

 

AB		A			
		11	10		
CD	00	0	0	1	1
	01	1	1	1	1
	11	1	1	0	0
	10	0	0	0	0
		B		D	



# Summary of hazards

- We can eliminate static hazards in 2-level logic for **single-bit changes**
  - Eliminating static hazards also eliminates dynamic hazards
- Hazards are a difficult problem
  - Multiple-bit changes in 2-level logic are hard
  - Static hazards in multilevel logic are harder
  - Dynamic hazards in multilevel logic are harder yet




# Example: Calendar System

- Determine number of days in a month (to control watch display)
  - Used in controlling the display of a wrist-watch LCD screen
  - Inputs: month, leap year flag
  - Outputs: number of days


 
# Formalize the Problem

- Encoding:
  - Binary number for month: 4 bits
  - 4 wires for 28, 29, 30, and 31 one-hot – only one true at any time
- Block diagram



month	leap	28	29	30	31
0000	–	–	–	–	–
0001	–	0	0	0	1
0010	0	1	0	0	0
0011	1	0	1	0	0
0100	–	0	0	1	0
0101	–	0	0	0	1
0110	–	0	0	1	0
0111	–	0	0	0	1
1000	–	0	0	0	1
1001	–	0	0	1	0
1010	–	0	0	0	1
1011	–	0	0	1	0
1100	–	0	0	0	1
1101	–	–	–	–	–
111–	–	–	–	–	–



# Implementation

$$28 = m8' m4' m2 m1' \text{ leap'}$$

$$29 = m8' m4' m2 m1' \text{ leap}$$


$$30 = m8' m4 m1' + m8 m1$$

$$31 = m8' m1 + m8 m1'$$



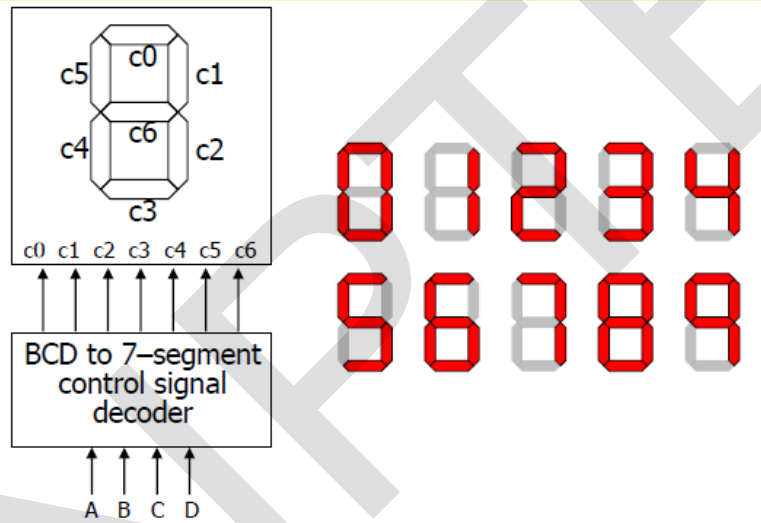
## BCD to 7-Segment Display Controller

- Input: 4-bit BCD digit (A, B, C, D)
- Output: 7 control signals for the display (C0 to C6)



# Truth Table

A	B	C	D	C0	C1	C2	C3	C4	C5	C6
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	-	-	-	-	-	-	-	-
1	1	-	-	-	-	-	-	-	-	-

 



# Implementation

- 15 unique product terms when minimized individually

$C0 = A + B D + C + B' D'$   
 $C1 = C' D' + C D + B'$   
 $C2 = B + C' + D$   
 $C3 = B' D' + C D' + B C' D + B' C$   
 $C4 = B' D' + C D'$   
 $C5 = A + C' D' + B D' + B C'$   
 $C6 = A + C D' + B C' + B' C$



## Better Implementation

- 9 unique product terms
- Share terms among outputs
- Each output not necessarily in minimized form

				A
C2	1	1	X	1
	1	1	X	1
C	1	1	X	X
	0	1	X	X
				B

$$\begin{aligned}
 C0 &= A + B D + C + B' D' \\
 C1 &= C' D' + C D + B' \\
 C2 &= B + C' + D \\
 C3 &= B' D' + C D' + B C' D + B' C \\
 C4 &= B' D' + C D' \\
 C5 &= A + C' D' + B D' + B C' \\
 C6 &= A + C D' + B C' + B' C
 \end{aligned}$$

				A
C2	1	1	X	1
	1	1	X	1
C	1	1	X	X
	0	1	X	X
				B

$$\begin{aligned}
 C0 &= B C' D + C D + B' D' + B C D' + A \\
 C1 &= B' D + C' D' + C D + B' D' \\
 C2 &= B' D + B C' D + C' D' + C D + B C D' \\
 C3 &= B C' D + B' D + B' D' + B C D' \\
 C4 &= B' D' + B C D' \\
 C5 &= B C' D + C' D' + A + B C D' \\
 C6 &= B' C + B C' + B C D' + A
 \end{aligned}$$




# Production Line Control

- Rods of varying length ( $\pm 10\%$ ) travel on conveyor belt
  - Mechanical arm pushes rods within spec ( $\pm 5\%$ ) to one side
  - Second arm pushes rods too long to other side
  - Rods that are too short stay on belt
  - 3 light barriers (light source + photocell) as sensors
  - Design combinational logic to activate the arms
- Understanding the problem
  - Inputs are three sensors
  - Outputs are two arm control signals
  - Assume sensor reads "1" when tripped, "0" otherwise
  - Call sensors A, B, C


 
# Sketch of the problem

- Position of Sensors
  - A to B distance = specification – 5%
  - A to C distance = specification + 5%



# Problem formulation

- Truth Table
  - Show don't cares

A	B	C	Function
0	0	0	do nothing
0	0	1	do nothing
0	1	0	do nothing
0	1	1	do nothing
1	0	0	too short
1	0	1	don't care
1	1	0	in spec
1	1	1	too long

logic implementation now straightforward  
just use three 3-input AND gates

"too short" =  $AB'C'$   
(only first sensor tripped)

"in spec" =  $A B C'$   
(first two sensors tripped)

"too long" =  $A B C$   
(all three sensors tripped)



# Logical Function Unit

- Multi-purpose Function Block
  - 3 control inputs to specify operation to perform on operands
  - 2 data inputs for operands
  - 1 output of the same bit-width as operands

C0	C1	C2	Function	Comments
0	0	0	1	always 1
0	0	1	$A + B$	logical OR
0	1	0	$(A \bullet B)'$	logical NAND
0	1	1	$A \text{ xor } B$	logical xor
1	0	0	$A \text{ xnor } B$	logical xnor
1	0	1	$A \bullet B$	logical AND
1	1	0	$(A + B)'$	logical NOR
1	1	1	0	always 0



# Truth Table

C0	C1	C2	A	B	F
0	0	0	0	0	1
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0



# Arithmetic Circuits

Santanu Chattopadhyay

Electronics and Electrical Communication Engineering



IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES




# Adder

- Great example of Iterative design
- Design a 1-bit adder circuit, then expand to n-bit adder
- Look at
  - Half adder – which is a 2-bit adder
  - Inputs are bits to be added
    - Outputs: result and possible carry
  - Full adder – includes carry in, really a 3-bit adder



# Half Adder

- $S = X \oplus Y$
- $C = XY$

 

**Truth Table of Half Adder**

Inputs		Outputs	
X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



# Full Adder

- Three inputs. Two are operand bits, third is  $C_{in}$
- Two outputs: sum and carry

Truth Table of Full Adder

Inputs			Outputs	
X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



# K Map for S

		Y			
		00	01	11	10
X	YZ				
	0		1		1
1	1	1		1	

- What is this?

$$S = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$

$$= X \oplus Y \oplus Z$$

In a half adder the sum bit:

$$S = X \oplus Y$$

Truth Table of Full Adder

Inputs			Outputs	
X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1




IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES

# K Map for C

 

In a half adder the carry bit:

$$C = XY$$

**Truth Table of Full Adder**

Inputs			Outputs	
X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



# Using two half Adders to Build a Full Adder

- Full adder functions

$$S = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ \\ = X \oplus Y \oplus Z$$

$$C = XY + XZ + YZ \\ = XY + Z(X\bar{Y} + \bar{X}Y) \\ = XY + Z(X \oplus Y)$$


- Half adder functions

$$S = X \oplus Y$$

$$C = XY$$



## Two Half Adders (and an OR)

 


IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES

# Ripple-Carry Adder

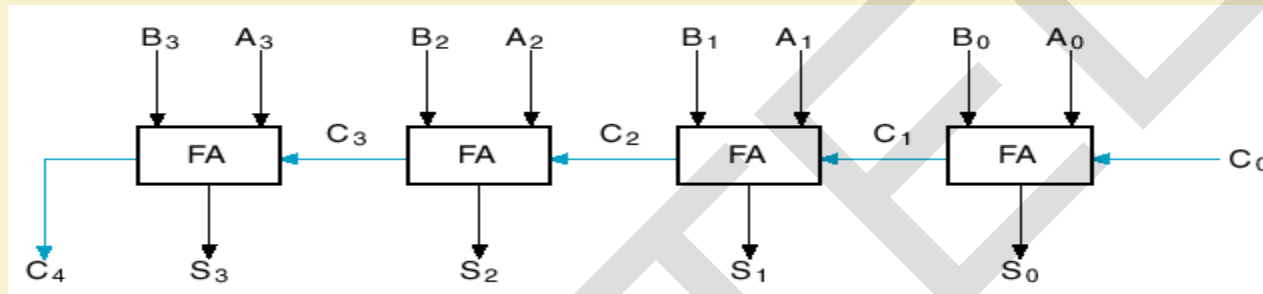

- Straightforward – connect full adders
- C<sub>4</sub> : Chain carry-out to carry-in of FA of bits A<sub>4</sub> & B<sub>4</sub>
  - C<sub>0</sub> in case this is part of larger chain
  - otherwise just set to zero





# Hierarchical 4-Bit Adder

- We can easily use hierarchy here
- Design half adder
- Use in full adder
- Use full adder in 4-bit adder




# Subtractor

- Compute M-N
  - Add 2's complement of N to M:  
 $M + (2^n - N)$ 
    - If  $M \geq N$ , need only “one adder” and a “complementer of N” to do the subtraction.
    - If  $M < N$ , we also need to take 2's complement of adder's output to produce magnitude of result  
 $2^n - \{ M + (2^n - N) \} = N - M$


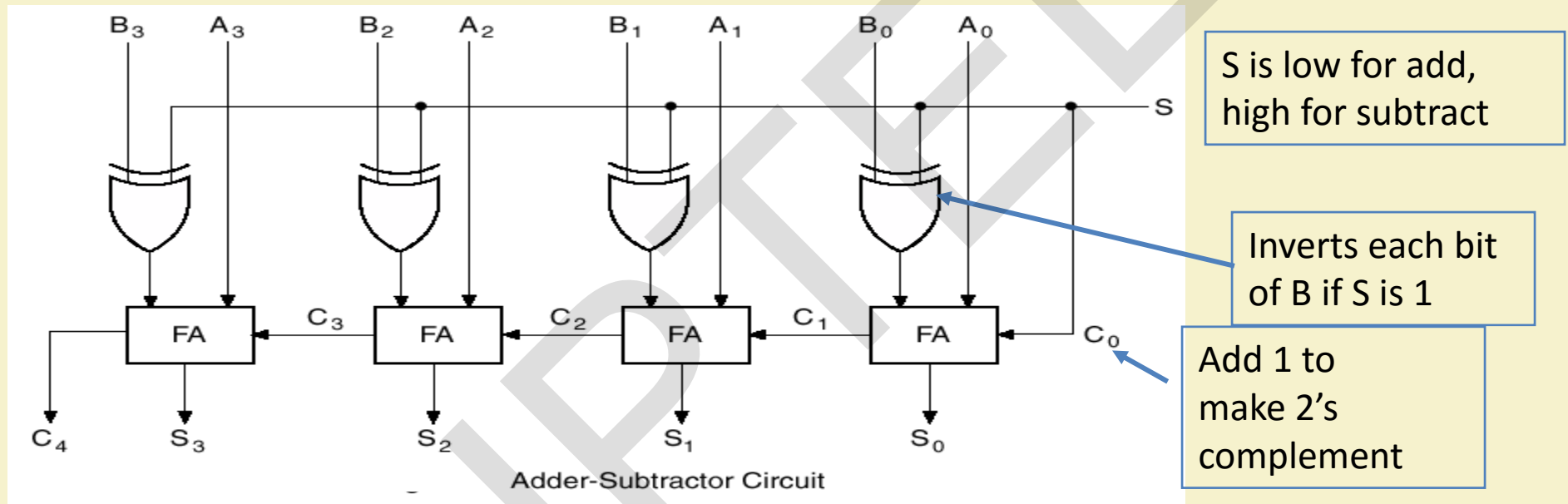
## Adder-Subtractor Design: $(A+B)$ OR $(A-B)$



- Output is result if  $A \geq B$ ; Discard carry
- Output is 2's complement of result if  $B > A$



IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES

# Overflow

- Overflow means that **result cannot be represented with the number of bits used**
- Two cases of overflow for addition of signed numbers
  - Two large positive numbers overflow into sign bit
    - Not enough bits for result
  - Two large negative numbers added
    - Same – Not enough bits for result



- Consider  $7 + 7$
- Overflow: cannot represent 14 using only 4 bits
- Generates NO CARRY,  $C_4 = 0$



## Example 2

- Consider  $-7 - 7$
- **Overflow: cannot represent -14 using only 4 bits**
- Generates CARRY,  $C_4 = 1$



- Consider  $4 + 4$
- **Overflow: cannot represent 8 using only 4 bits**
- Generates NO CARRY,  $C_4 = 0$




- Consider  $7 - 7$
- **NO Overflow**
- Generates CARRY,  $C_4 = 1$




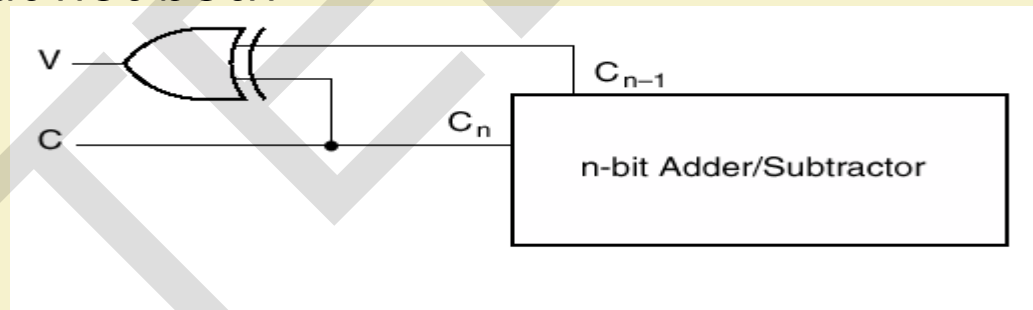
# Overflow Detection

- Condition for overflow:
  - either  $C_{n-1}$  or  $C_n$  is high, but not both



- $7 + 7$ ; only  $C_{n-1}$  ( $C_3$ ) is high ; **overflow**
- $-7 - 7$ ; only  $C_n$  ( $C_4$ ) is high ; **overflow**
- $4 + 4$ ; only  $C_{n-1}$  ( $C_3$ ) is high ; **overflow**
- $7 - 7$ ; BOTH  $C_{n-1}$  &  $C_n$  ( $C_4$  &  $C_3$ ) are high; **no overflow**



# Carry-Lookahead Adders



IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES

## Possible solutions to the carry propagate problem

1. Detect the end of propagation rather than wait for the worst-case time
- 2. Speed-up propagation via**
  - **look-ahead**
  - **carry select, etc.**
3. Limit carry propagation to within a small number of bits
4. Eliminate carry propagation through the redundant number representation



# Basic Signals

**Generate signal:**

$$g_i = x_i y_i$$

**Propagate signal:**

$$p_i = x_i \oplus y_i$$

**Anihilate (absorb) signal:**

$$a_i = \overline{x_i} \overline{y_i} = \overline{x_i + y_i}$$

**Transfer signal:**

$$t_i = g_i + p_i = \overline{a_i} = x_i + y_i$$

$c_{\text{out}} = 1$  given  $c_{\text{in}} = 1$

**Carry recurrence**

$$c_{i+1} = g_i + c_i p_i = g_i + c_i t_i$$



# Unrolling Carry Recurrence

$$\begin{aligned}
 c_i &= g_{i-1} + c_{i-1}p_{i-1} = \\
 &= g_{i-1} + (g_{i-2} + c_{i-2}p_{i-2})p_{i-1} = g_{i-1} + g_{i-2}p_{i-1} + c_{i-2}p_{i-2}p_{i-1} = \\
 &= g_{i-1} + g_{i-2}p_{i-1} + (g_{i-3} + c_{i-3}p_{i-3})p_{i-2}p_{i-1} = \\
 &= g_{i-1} + g_{i-2}p_{i-1} + g_{i-3}p_{i-2}p_{i-1} + c_{i-3}p_{i-3}p_{i-2}p_{i-1} = \\
 &= \dots = \\
 &= g_{i-1} + g_{i-2}p_{i-1} + g_{i-3}p_{i-2}p_{i-1} + g_{i-4}p_{i-3}p_{i-2}p_{i-1} + \dots + \\
 &\quad + g_0p_1p_2\dots p_{i-2}p_{i-1} + c_0p_0p_1p_2\dots p_{i-2}p_{i-1} = \\
 &= \boxed{g_{i-1} + \sum_{k=0}^{i-2} g_k \prod_{j=k+1}^{i-1} p_j + c_0 \prod_{j=0}^{i-1} p_j}
 \end{aligned}$$



## 4-bit Carry-Lookahead Adder

$$c_4 = g_3 + g_2 p_3 + g_1 p_2 p_3 + g_0 p_1 p_2 p_3 + c_0 p_0 p_1 p_2 p_3$$

$$c_3 = g_2 + g_1 p_2 + g_0 p_1 p_2 + c_0 p_0 p_1 p_2$$

$$c_2 = g_1 + g_0 p_1 + c_0 p_0 p_1$$

$$c_1 = g_0 + c_0 p_0$$

---

$$s_0 = x_0 \oplus y_0 \oplus c_0 = p_0 \oplus c_0$$

$$s_2 = p_2 \oplus c_2$$

$$s_1 = p_1 \oplus c_1$$

$$s_3 = p_3 \oplus c_3$$



## 4-bit Carry-Lookahead Adder (2)

$$c_4 = g_3 + c_3 p_3$$

3 gates less

$$c_3 = g_2 + g_1 p_2 + g_0 p_1 p_2 + c_0 p_0 p_1 p_2$$

$$c_2 = g_1 + g_0 p_1 + c_0 p_0 p_1$$

$$c_1 = g_0 + c_0 p_0$$

---

$$s_0 = x_0 \oplus y_0 \oplus c_0 = p_0 \oplus c_0$$


$$s_1 = p_1 \oplus c_1$$

$$s_2 = p_2 \oplus c_2$$

$$s_3 = p_3 \oplus c_3$$


 
# 4-bit Carry Network with Full Lookahead



IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES



# Equations for 4-bit Lookahead Carry Generation

$$c_{i+3} = g_{i+2} + g_{i+1} p_{i+2} + g_i p_{i+1} p_{i+2} + c_i p_i p_{i+1} p_{i+2}$$

$$c_{i+2} = g_{i+1} + g_i p_{i+1} + c_i p_i p_{i+1}$$

$$c_{i+1} = g_i + c_i p_i$$

---

$$g_{[i..i+3]} = g_{i+3} + g_{i+2} p_{i+3} + g_{i+1} p_{i+2} p_{i+3} + g_i p_{i+1} p_{i+2} p_{i+3}$$

$$p_{[i..i+3]} = p_i p_{i+1} p_{i+2} p_{i+3}$$



# 4-bit Lookahead Carry Generator Schematic

