
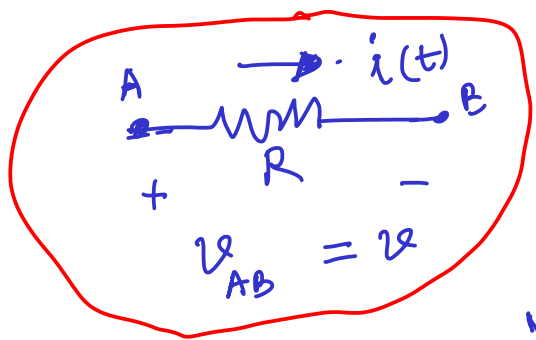


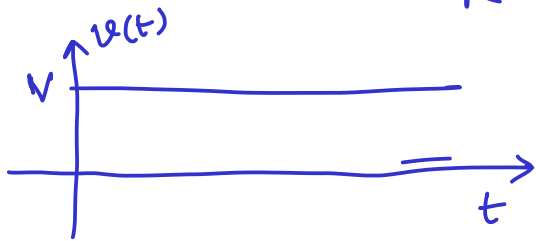


$$i(t) = \frac{v_{AB}(t)}{R} = \frac{v(t)}{R}$$

→ Terminal v - i relation Sec - 9




$$\begin{aligned} \text{Power} &= vi \\ &= Ri^2 \end{aligned}$$

→ will be lost


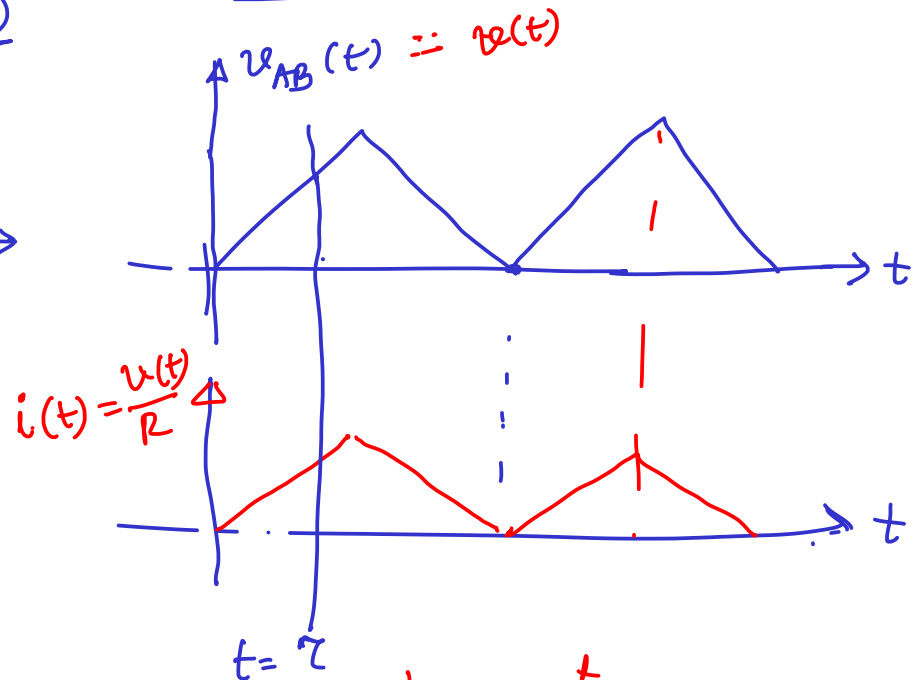


Resistance → is memory less element

Inductor (L)

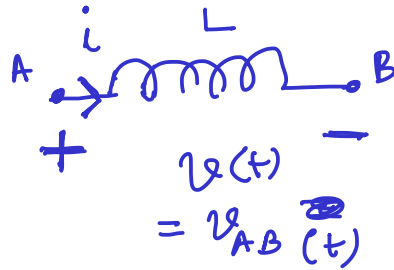

$$v = v_{AB}(t) = L \frac{di}{dt}$$

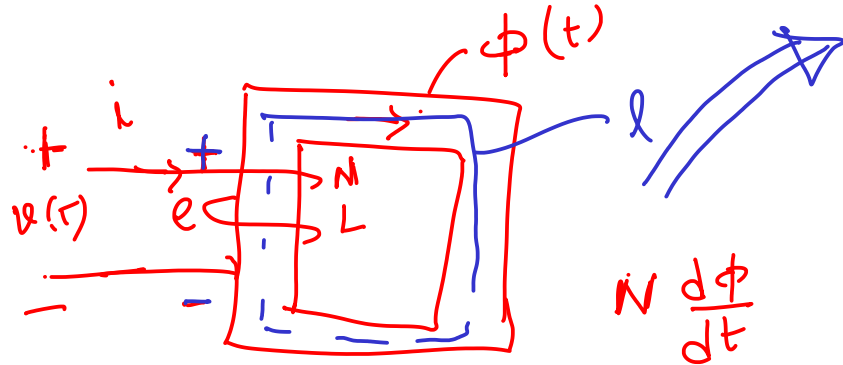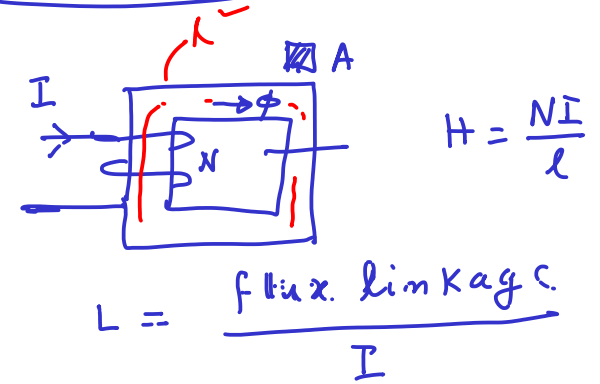

$$L = \mu_0 \mu_r \frac{N^2 A}{l}$$

$$e = \frac{N^2 \mu_0 \mu_r A}{l} \frac{di}{dt} = L \frac{di}{dt}$$


$$e = \frac{d}{dt} (N\phi) = N \frac{d\phi}{dt} = N \frac{d}{dt} (B(t) A) = N \frac{d}{dt} \left[\mu_0 \mu_r \frac{NI}{l} A \right]$$

$R = \frac{l}{\mu_0 \mu_r A}$
 $Li =$ instantaneous flux linkage with the coil

$$L = \frac{N}{I} \cdot \frac{BA}{\mu_0 \mu_r} = \frac{N}{I} A \mu_0 \mu_r H = \frac{NA}{\frac{l}{\mu_0 \mu_r}} \mu_0 \mu_r \frac{NI}{l}$$

$$= \frac{N\phi}{I} \rightarrow \frac{\text{Wb-turns}}{A} \quad (H)$$

$$\& B = \mu_0 \mu_r H$$

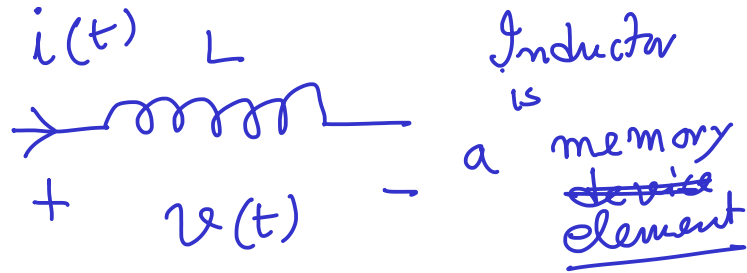

$$L \frac{di}{dt} = v$$

$$\frac{di}{dt} = \frac{1}{L} v(t)$$


$$di = \frac{1}{L} v(t) dt$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

$$\frac{di}{dt} = \frac{1}{L} v(t)$$

$$\int di = \frac{1}{L} \int_{-\infty}^t v(t) dt$$
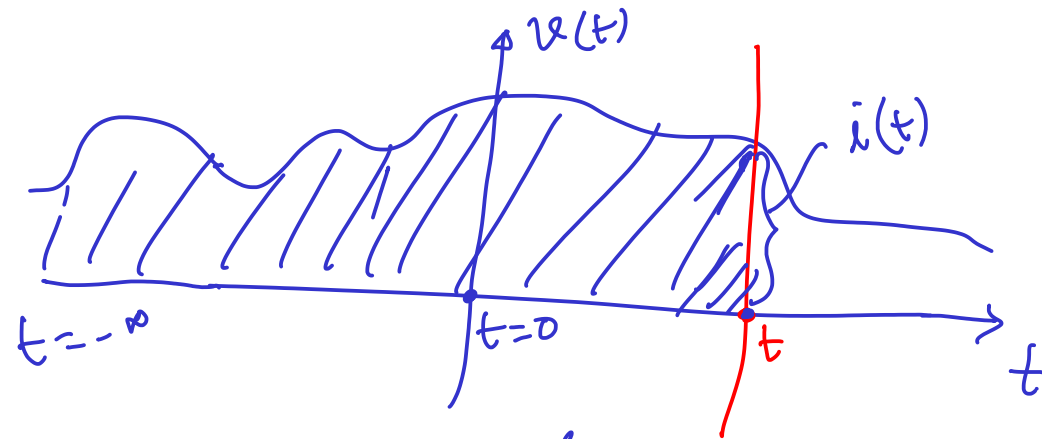
$$i(t) = \frac{1}{L} \int_{-\infty}^t v(t) dt$$




If an inductor

carries a fixed current

I (which is constant) The voltage across the inductor will be $L \frac{d}{dt} (I) = 0$

Inductor :
memory

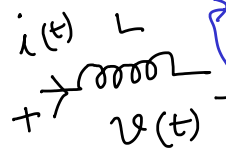

$$i(0^-) = \frac{1}{L} \int_{t=-\infty}^{0^-} v(t) dt$$


$$v(t) = L \frac{di}{dt}$$



Lec-10



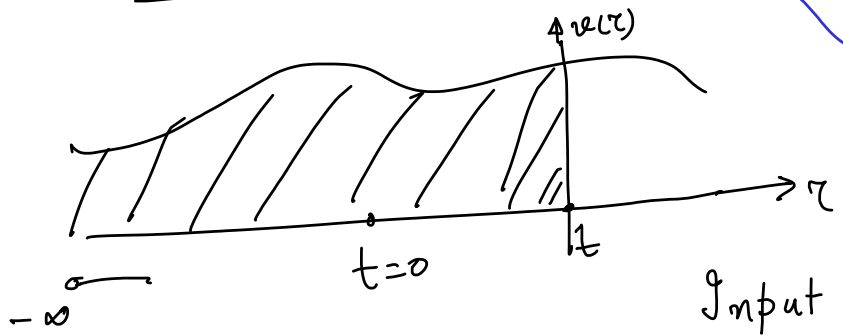
$$i(t) = \frac{1}{L} \int_{t=-\infty}^t v dt = \frac{1}{L} \int_{t=-\infty}^t v(\tau) d\tau$$



Input voltage $v(t)$ is a reasonable signal.
[$v(t)$ excludes an impulse $\delta(t)$]

$$i(0^+) = \frac{1}{L} \int_{t=-\infty}^{t=0^+} v(t) dt$$
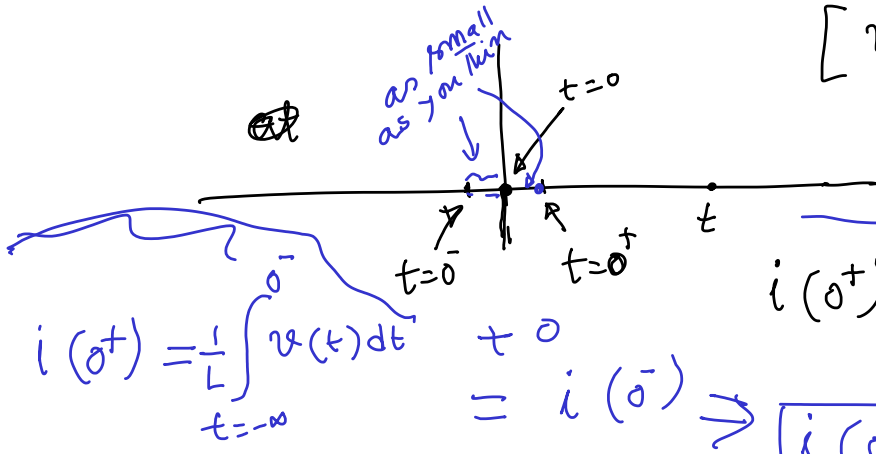
$$i(0^+) = \frac{1}{L} \int_{t=-\infty}^{t=0^-} v(t) dt + \left(\frac{1}{L} \int_{t=0^-}^{0^+} v(t) dt \right) = 0$$



$$i(0^+) = \frac{1}{L} \int_{t=-\infty}^{0^-} v(t) dt = i(0^-) \Rightarrow$$

$$\boxed{i(0^+) = i(0^-)}$$

$$i(0^-) = \frac{1}{L} \int_{t=-\infty}^{0^-} v(t) dt$$

$$t=0^- \text{ or } 0 \text{ or } 0^+ \equiv 0$$


$$t > 0$$

$$i(t) = \frac{1}{L} \int_{t=-\infty}^t v(t) dt = \frac{1}{L} \int_{t=-\infty}^{0^-} v(t) dt + \frac{1}{L} \int_{t=0^-}^{0^+} v(t) dt + \frac{1}{L} \int_{t=0^+}^t v(t) dt$$

$$i(t) = i(0^-) + \frac{1}{L} \int_{t=0^+}^t v(t) dt$$

$$i(0^+) = i(0^-)$$


Inductor can store energy

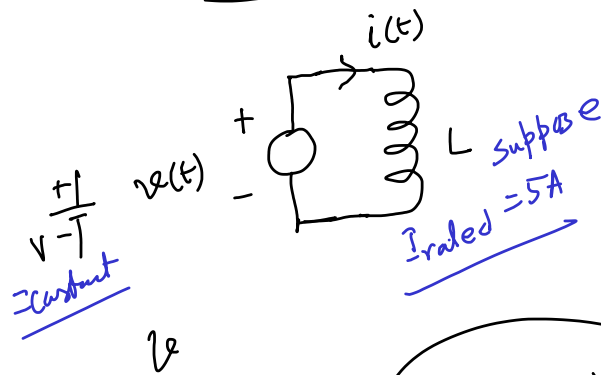

$$v(t) \text{ for } t \geq 0$$

$$v(t) = V$$

$$i(t) = \frac{V}{L} t$$

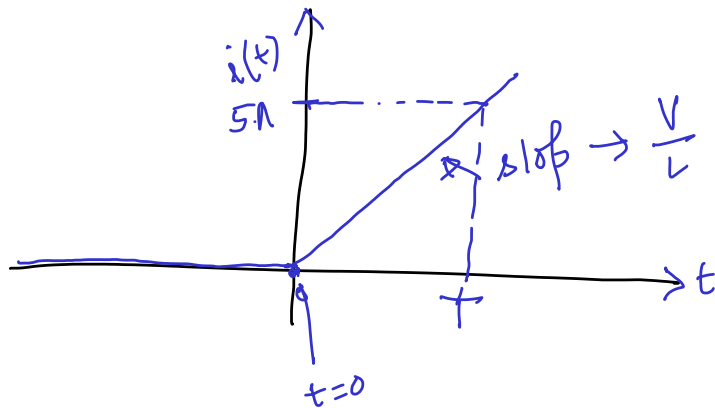

for $t < 0$ $v(t) = 0$

$i(0^-) = 0 \rightarrow$ initial current
 $\Rightarrow i(0^+) = 0$


$$i(t) = i(0^-) + \frac{1}{L} \int_{0^+}^t v(t) dt$$

$$i(t) = \frac{1}{L} \int_{0^+}^t v(t) dt = \frac{1}{L} \int_0^t v(t) dt$$

$$= \frac{1}{L} \int_0^t V dt = \left(\frac{V}{L} \right) t$$

Inductor can store energy

lec - 11

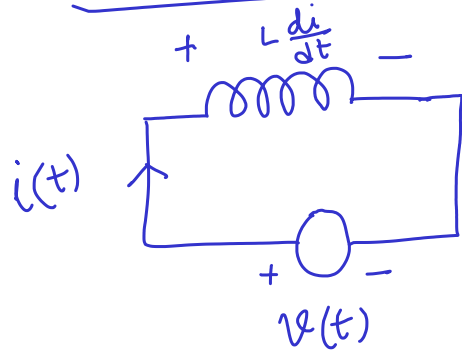

$$p(t) = L \frac{di}{dt} i$$

energy supplied to L over a time " dt " ($dt \rightarrow 0$)

$$dW = L \frac{di}{dt} i dt$$

$$dW = L i di$$


total Energy
supplied

5 A $L = 2 \text{ H}$

A diagram showing a horizontal wire with an inductor (represented by a series of loops) in the middle. An arrow points to the left from the start of the wire, with "5 A" written above it. The inductor is labeled with $L = 2 \text{ H}$ above it.



$$\rightarrow \frac{1}{2} \times 2 \times 5^2 = 25 \text{ J}$$
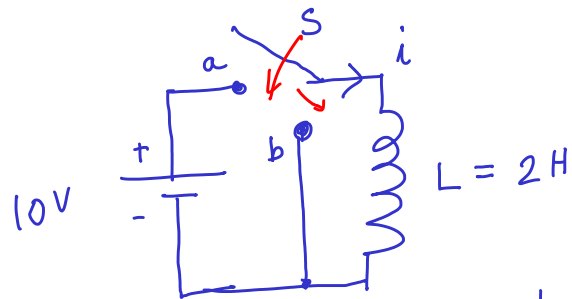
$$W = L \int_0^i i(di) = \frac{1}{2} L i^2$$



at $t=0$ move the switch to position "a"
 at $t=2$ move the switch from "a" to position "b" ✓
 $i(0^-) = 0 = i(0^+) = i(0)$

for $t \geq 0$

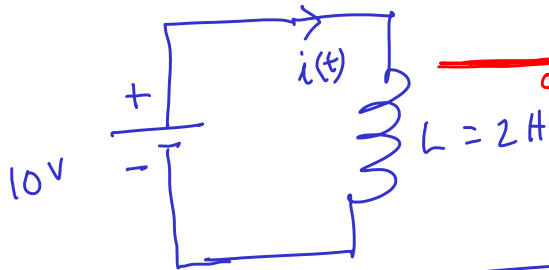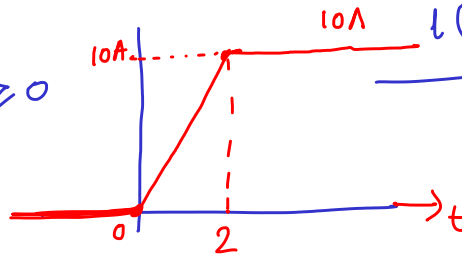

$$V = L \frac{di}{dt} = 10$$

$$\text{or } 2 \frac{di}{dt} = 10$$


for $t > 2$

$$\frac{di}{dt} = 0$$

$$\text{or } i = 5t + A$$

$$i(0) = 0 \therefore A = 0$$

for $t \geq 2$

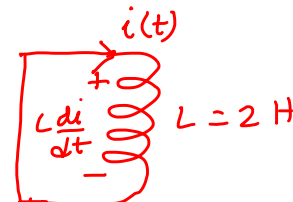


$$i(t=2^-) = 10A$$

$$i(t=2^+)$$


slope
 $i = 5t$

Energy stored
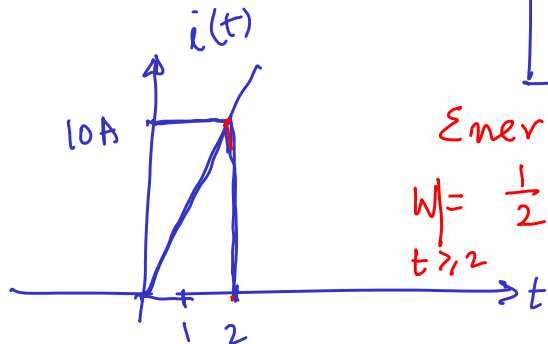
$$W = \frac{1}{2} \times 2 \times 100 = 100 \text{ J}$$




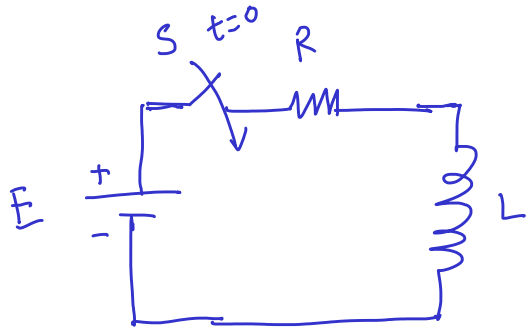$2 \frac{di}{dt} = 0 \Rightarrow i$ must be a constant for $t > 2$




for $t < 0$ $S \rightarrow$ opened.
 $i(0^-) = 0$

at $t = 0$ S is closed.

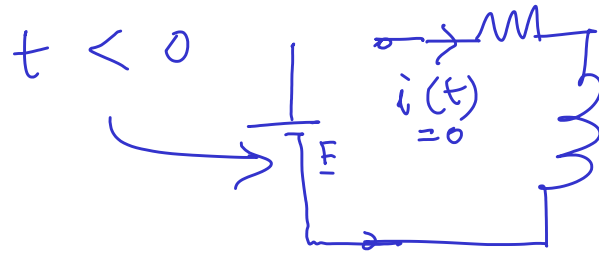

ckt for $t \geq 0$

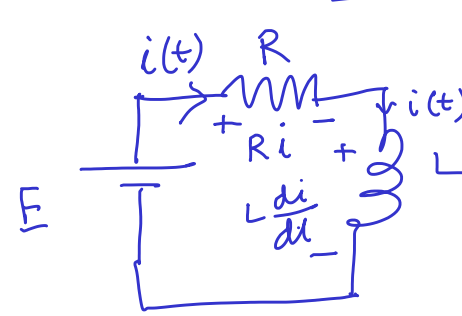


at $t = 0^+$
 $i(0^+) = i(0^-) = 0$
 $= i(0)$

$$E - Ri - L \frac{di}{dt} = 0$$

$$\boxed{L \frac{di}{dt} + Ri = E}$$

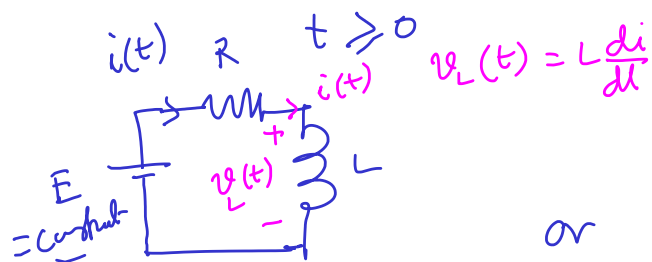✓ 1st order
 linear differential
 Equation.



$$L \frac{di}{dt} + R i = E$$

$$\text{or } \frac{di}{dt} + \left(\frac{R}{L}\right) i = \frac{E}{L}$$

Integrating factor

$$\left\{ e^{\frac{R}{L}t} \frac{di}{dt} + \frac{R}{L} e^{\frac{R}{L}t} i \right\} = \frac{E}{L} e^{\frac{R}{L}t}$$


$$\int d \left(e^{\frac{R}{L}t} i \right) = \int \frac{E}{L} e^{\frac{R}{L}t} dt + A$$

$$e^{\frac{R}{L}t} i = \frac{E}{L} \frac{e^{\frac{R}{L}t}}{\frac{R}{L}} + A = \frac{E}{R} e^{\frac{R}{L}t} + A$$

$$i(t) = \frac{E}{R} - \frac{E}{R} e^{-\frac{R}{L}t}$$

$$= \frac{E}{R} (1 - e^{-\frac{R}{L}t})$$
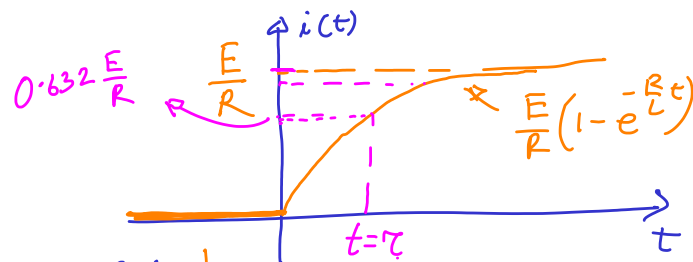
$$i(t) = \frac{E}{R} + A e^{-\frac{R}{L}t}$$



$$\frac{L}{R} = \tau = \text{time constant}$$

$$i(t) = \frac{E}{R} (1 - e^{-t/\tau})$$

↓ constant


$$i(0) = 0$$

$$0 = \frac{E}{R} + A \quad \text{or} \quad A = -\frac{E}{R}$$

Dec 12

$$i(t) = \frac{E}{R} \left(1 - e^{-t/\tau} \right)$$

$$\tau = \frac{L}{R}$$

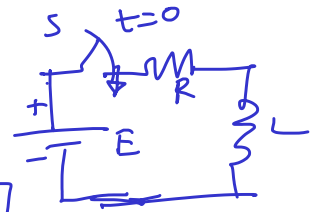


voltage across the inductor.

$$v_L(t) = L \frac{di}{dt} = L \frac{d}{dt} \left[\frac{E}{R} \left(1 - e^{-t/\tau} \right) \right]$$

$$= L \frac{d}{dt} \left(-e^{-t/\tau} \frac{E}{R} \right) = \frac{EL}{R} \frac{d}{dt} \left(-e^{-t/\tau} \right)$$
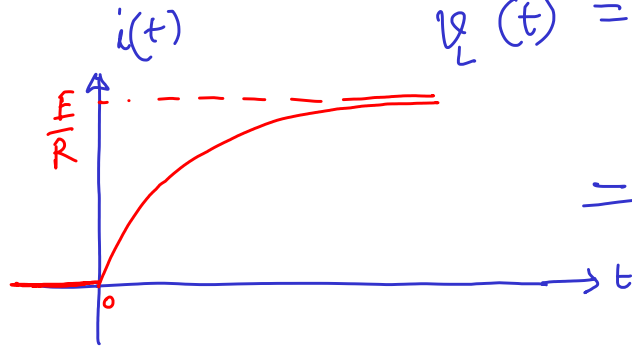
$$= \frac{EL}{R} \frac{1}{\frac{L}{R}} e^{-t/\tau} = E e^{-t/\tau} = v_L(t)$$




Current through an inductor can not have a step jump!

$$v_L(0^-) = 0$$



$$v_L(0^+) = E e^{-0/\tau} = E$$

voltage of course can have a step jump.

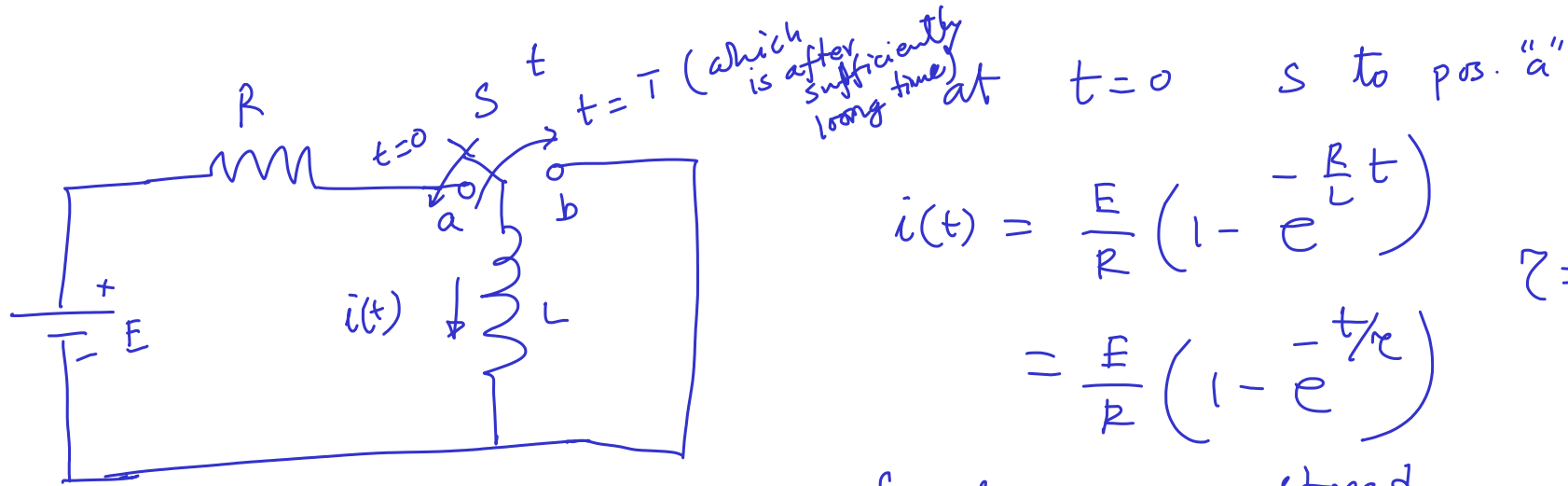


$$i(t) = \frac{E}{R} \left(1 - e^{-\frac{R}{L}t} \right)$$
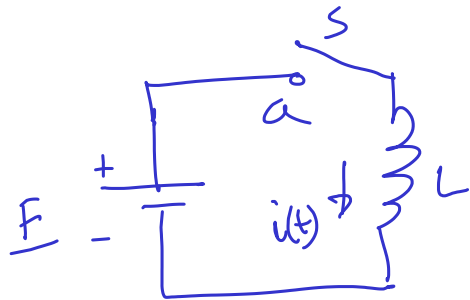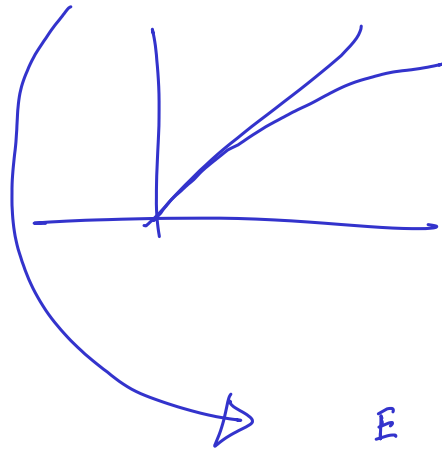
$$= \frac{E}{R} \left(1 - e^{-t/\tau} \right) \quad \tau = \frac{L}{R}$$




final energy stored in the inductor
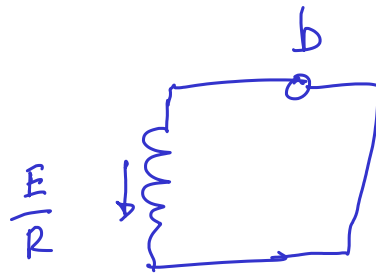
$$= \frac{1}{2} L \left(\frac{E}{R} \right)^2$$



S is moved to pos. "b".

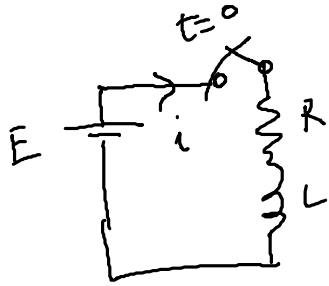


$$i(t) = \frac{E}{R} (1 - e^{-t/\tau}) \quad \tau = \left(\frac{L}{R} \right)$$

$$\downarrow$$

$$i(t_1) = \frac{E}{R} (1 - e^{-t_1/\tau})$$

$$i(t'=0) = i(t_1)$$

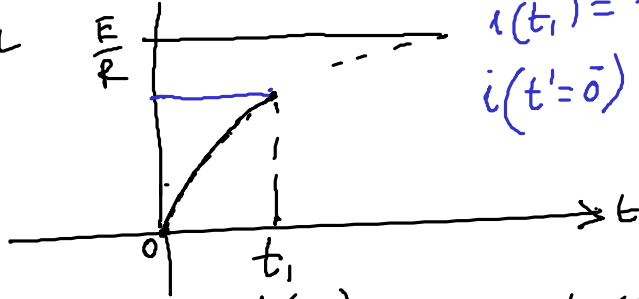

$$\frac{di(t')}{dt'} + \frac{R_L}{L} i(t') = 0$$

$$e^{\frac{R_L}{L}t'} \frac{di}{dt'} + \frac{R_L}{L} e^{\frac{R_L}{L}t'} i = 0$$

$$i(t) = \frac{E}{R} (1 - e^{-t/\tau}) \quad 0 \leq t \leq t_1$$

$\frac{d}{dt'} (e^{\frac{R_L}{L}t'} i) = 0$ at $t = t_1$ s is moved from pos. a to pos. b very quickly (practically in no time)




$$e^{\frac{R_L}{L}t'} i = A$$

or

$$i(t') = A e^{-\frac{R_L}{L}t'}$$

$$L \frac{di(t')}{dt'} + R_L i(t') = 0$$

$$i(0) = i(t'=0)$$

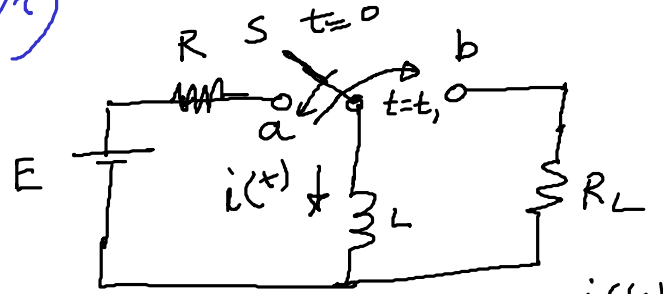


$$0 < t < t_1$$

$$i(t_1) =$$




for $t > t_1$
or $t' > 0$

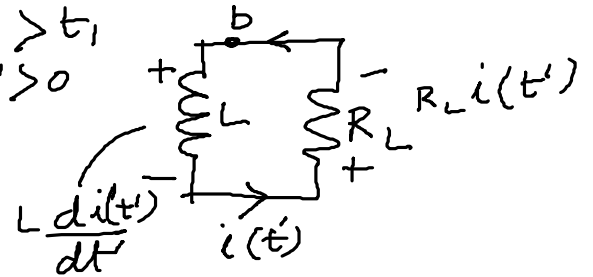


$$\therefore i(0) = \underline{A} = i(t_1)$$

$$i(t') = i(t=t_1) e^{-\frac{R}{L}t'}$$
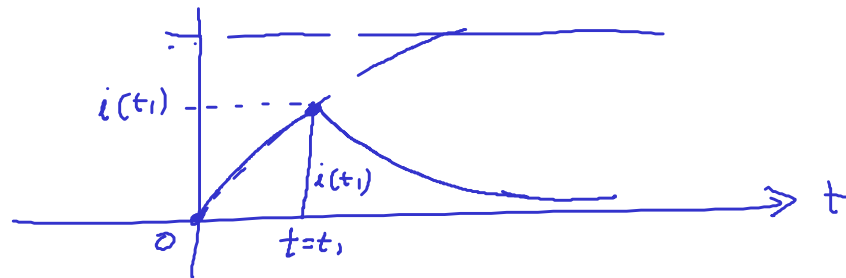
$$= i(t_1) e^{-\frac{R}{L}(t-t_1)} \quad t \geq t_1$$



$$\frac{1}{2} L i(\bar{o})^2$$

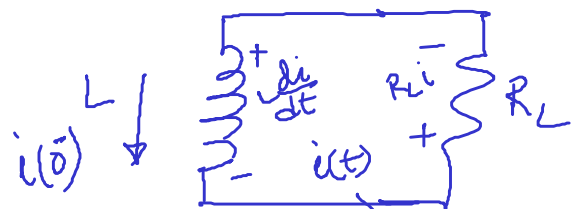

$$L \frac{di}{dt} + R_L i = 0$$

$$\frac{di}{dt} + \frac{R_L}{L} i = 0 \Rightarrow$$



$$i_L(t) = i(\bar{o}) e^{-\frac{R_L}{L}t}$$

Energy dissipated in R_L


at $t=0$, R_L is connected across the inductor with initial current $i(\bar{o})$

$i(\bar{o})$ inherited by other ckt)

$$W = \int_0^{\infty} i^2 R_L dt$$

$$= \int_0^{\infty} i(\bar{o})^2 e^{-\frac{2R_L}{L}t} dt$$

$$= \frac{1}{2} L i(\bar{o})^2$$

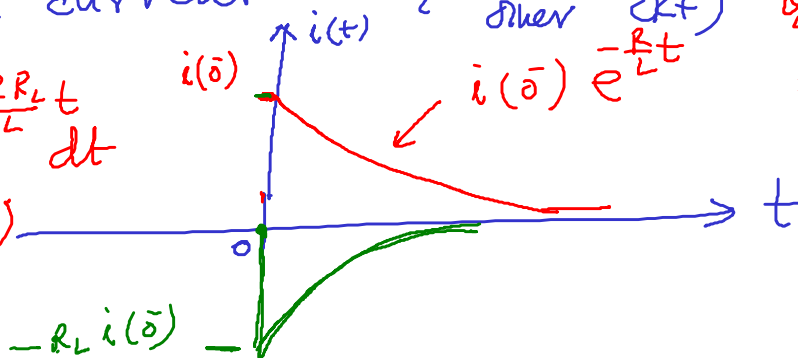


$$P_L(t) = L \frac{di}{dt}$$

$$= L \left(-\frac{R_L}{L} \right) i(\bar{o}) e^{-\frac{R_L}{L}t}$$

$$= -R_L i(\bar{o}) e^{-\frac{R_L}{L}t}$$

$$= -R_L i(t)$$

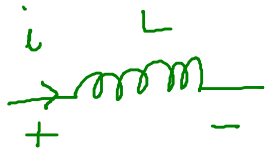


$$V_L = L \frac{di}{dt}$$

To store energy in an inductor
we have to pump current into
it

$$i(t) = \frac{1}{L} \int_{-\infty}^t V_L dt \rightarrow \text{Volt-sec}$$

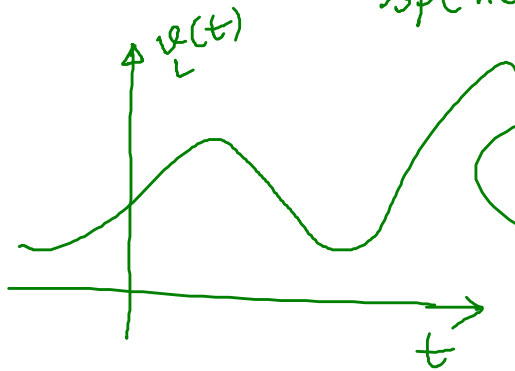To establish current
in an inductor we have
spend Volt-sec.



$$L \frac{di}{dt} = V_L$$

$$\frac{di}{dt} = \frac{V_L}{L}$$

$$m \frac{dv}{dt} = F$$



$$v(t) = \frac{1}{m} \int_{-\infty}^t F dt$$

$m \xrightarrow{0} v$

if $V_L = +ve \therefore \frac{di}{dt} > 0$ & current has to rise
if $V_L = -ve \therefore \frac{di}{dt} < 0$

Lec-14

$$L = 2H$$

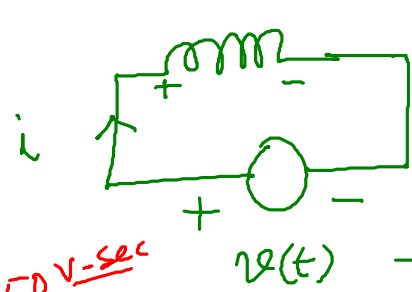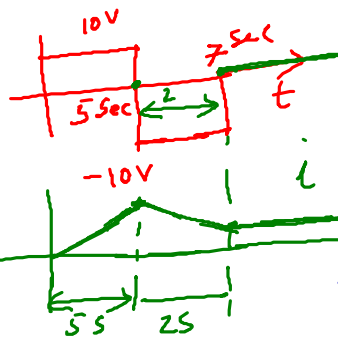



$$L \frac{di}{dt} = v(t)$$

$$i(0^-) = 0$$


$$\frac{di}{dt} = \frac{v(t)}{L}$$

$$\frac{1}{L} \int v dt$$

50 V-sec

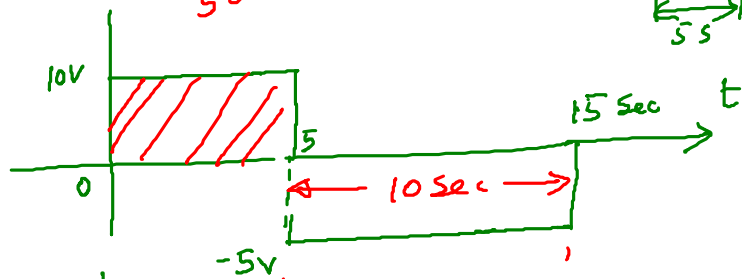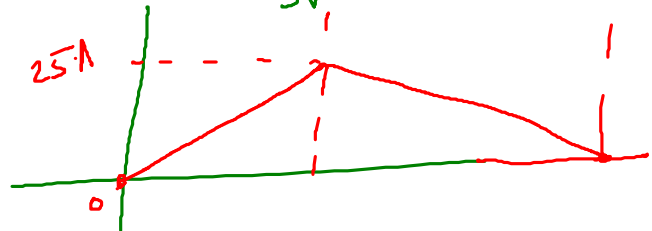

$$\frac{V}{L} \frac{T}{2}$$

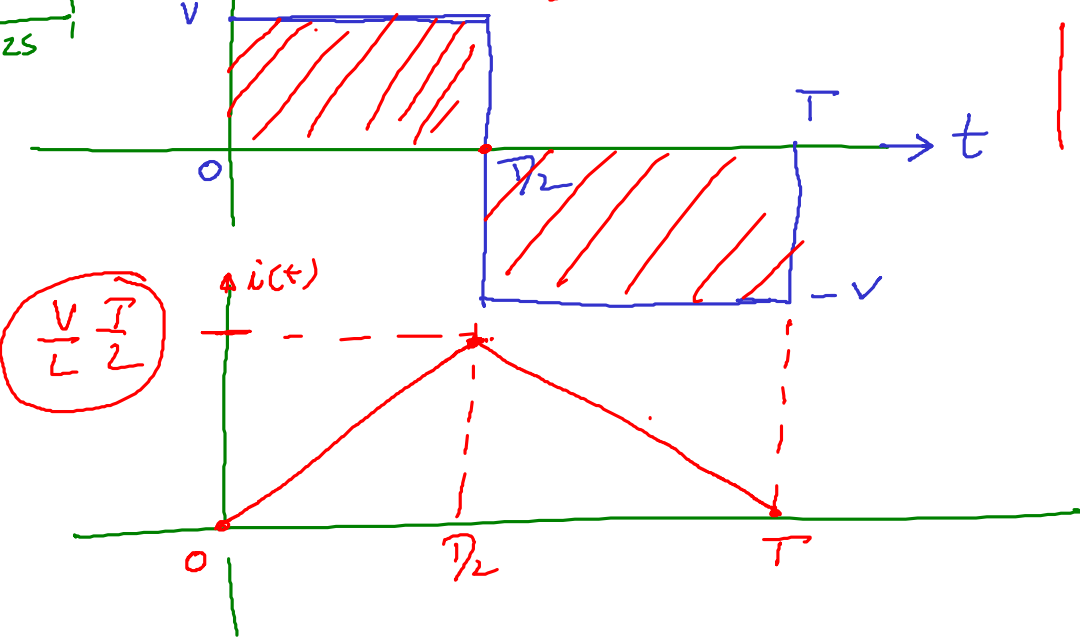

Capacitor

voltage across the capacitor can not change instantaneously

C

$$i(t) = C \frac{dv}{dt}$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v dt$$

$$v = \frac{q}{C}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i dt$$

→ element with capacitor

$$v(t) = \frac{1}{C} \int_{-\infty}^{0^-} i dt + \frac{1}{C} \int_{0^-}^{0^+} i dt + \frac{1}{C} \int_{0^+}^t i dt$$

$$v(0^+) = \frac{1}{C} \int_{-\infty}^{0^-} i dt + \frac{1}{C} \int_{0^-}^{0^+} i dt = 0$$

$$v(0^+) = v(0^-)$$

$$v = \frac{q}{C}$$

$$i \equiv \frac{\text{Amp} \cdot \text{Coulomb}}{s}$$

$$q = \int_{-\infty}^t i dt$$

= present charge on the plates of the capacitor


current source

$i(t)$ is not

an impulse source

$$v(0^+) = v(0^-)$$

Capacitor stores energy:

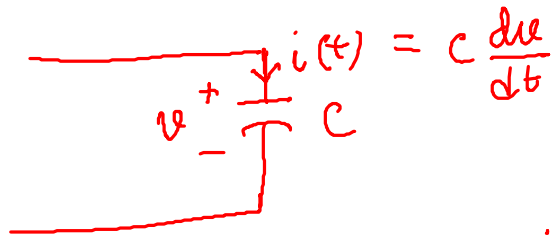

$$i(t) = C \frac{dv}{dt}$$

Let at $t=0$ $v(0^-) = 0 = v(0^+) = v(0)$


instantaneous power absorbed

$$p(t) = v C \frac{dv}{dt} = C v \frac{dv}{dt}$$

$\therefore$ energy absorbed by the capacitor
in time dt

$$dW = p(t) dt = C v \frac{dv}{dt} dt = C v dv$$
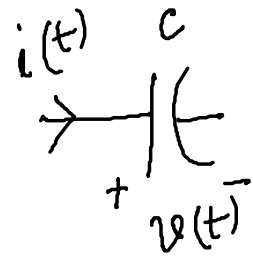
$$W = C \int_{v=0}^{v=v} v dv = \frac{1}{2} C v^2$$



$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i dt = \frac{1}{C} \int_{-\infty}^{0^-} i dt + \int_{0^-}^{0^+} i dt + \int_{0^+}^t i dt$$

$$v(t) = v(0^-) + \int_{0^+}^t i dt$$

$$v(0^+) = v(0^-) + \int_{0^+}^{0^+} i dt = v(0^-)$$

Lec-15

$$\frac{1}{2} C v^2 \text{ Joules}$$


$C \rightarrow F$

$v \rightarrow \text{volts}$

$$\tau = \frac{L}{R}$$

$$i(0^+) = i(0) = \frac{E}{R}$$

Charging a capacitor

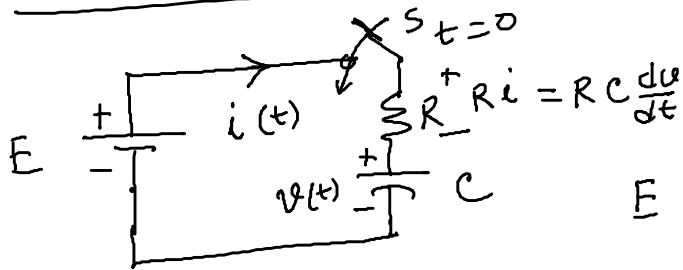

$$\frac{1}{2} C E^2$$

$$v(0^-) = 0 = v(0^+) = v(0)$$

$$i = C \frac{dv}{dt}$$


$$E - RC \frac{dv}{dt} - v = 0$$

or

$$RC \frac{dv}{dt} + v = E$$

or
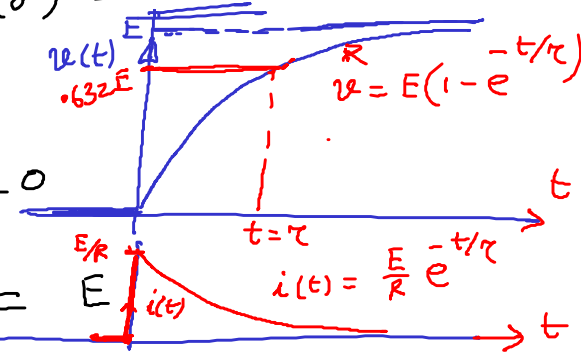
$$\frac{dv}{dt} + \frac{1}{RC} v = \frac{E}{RC}$$



$$e^{\frac{t}{RC}} v = \frac{E}{RC} \frac{1}{e} + A e^{\frac{t}{RC}}$$

$$v = E + A e^{-t/RC}$$

$\tau = RC$
= time constant

$$v(0) = 0 \Rightarrow 0 = E + A$$

$$A = -E$$

$$v(t) = E - E e^{-t/RC} = E (1 - e^{-t/RC})$$

$$v(t \rightarrow \infty) = E = E (1 - e^{-t/RC})$$


$$e^{\frac{1}{RC}t} \frac{dv}{dt} + \frac{1}{RC} e^{\frac{1}{RC}t} v = \frac{E}{RC} e^{\frac{1}{RC}t}$$

$$\int d \left(e^{\frac{t}{RC}} v \right) = \int \frac{E}{RC} e^{\frac{t}{RC}} dt$$

$$i(t) = C \frac{dv}{dt}$$

$$i(t) = \frac{E}{R} e^{-t/RC}$$

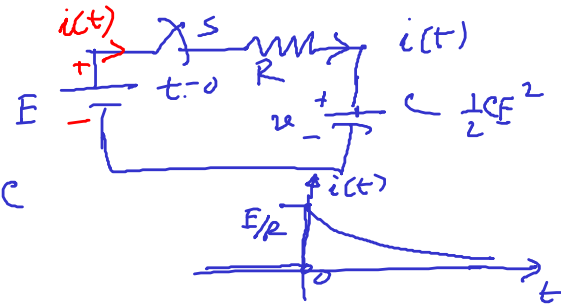Energy dissipated in R while charging the capacitor to the supply voltage (E)



Energy diss. in R $\rightarrow$ is independent of the value of R
 $\frac{1}{2}CE^2 = \text{energy stored in cap.}$

$$v(t) = E(1 - e^{-t/\tau}) \quad \tau = RC$$

$$i(t) = \frac{E}{R} e^{-t/RC}$$

instantaneous power loss in the ckt $\hookrightarrow i^2 R$

Energy dissipated in R in time dt

$$dw = p dt = i^2 R dt = \frac{E^2}{R^2} e^{-\frac{2t}{RC}} R dt$$

~~Total~~ Amount of power delivered by the source

Energy delivered $\odot W = \int_0^\infty E i(t) dt$
 $= E \int_0^\infty \frac{E}{R} e^{-t/RC} dt$

$\therefore$ total energy dissipated in R

$$W = R \frac{E^2}{R^2} \int_0^\infty e^{-\frac{2t}{RC}} dt = \frac{E^2}{R} \left[\frac{e^{-\frac{2t}{RC}}}{-\frac{2}{RC}} \right]_{t=0}^\infty$$

$$= \frac{E^2}{R} \frac{RC}{2} \left[\frac{e^{-\frac{2t}{RC}}}{1} \right]_{t=0}^\infty = \frac{1}{2} C E^2 [1 - 0] = \frac{1}{2} C E^2$$


$$= \frac{E^2}{R} \left[\frac{e^{-t/RC}}{-1/RC} \right]_0^\infty = \frac{CE^2}{2} \left[e^{-t/RC} \right]_0^\infty = \frac{CE^2}{2}$$

Dec 16

$$i(t) = C \frac{dv(t)}{dt}$$

$$i(t) = C \frac{dv}{dt} \quad \left| \quad v(t) = \frac{1}{C} \int_{-\infty}^t i dt \right.$$

$$v(0^+) = v(0^-) = v(0)$$

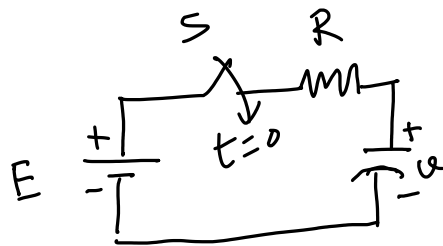



$$v(0^-) = 0$$

$$v(t) = E(1 - e^{-t/\tau})$$

$$\tau = RC$$


$$i(t) = \frac{E}{R} e^{-t/\tau}$$

$$W_{\theta}(t) = \frac{1}{2} C v^2$$

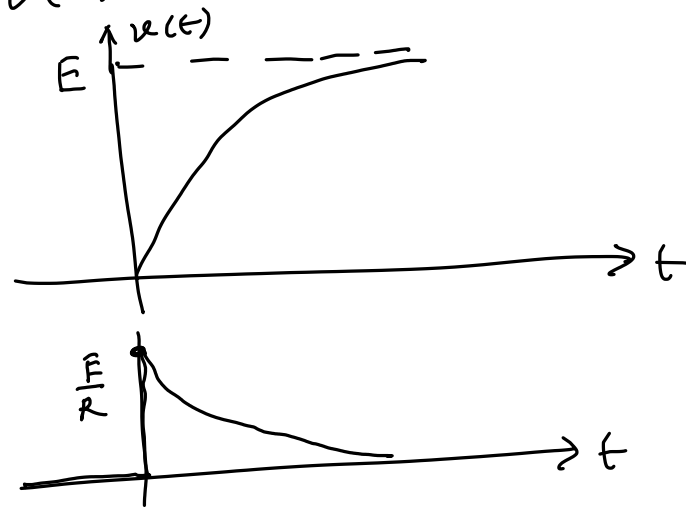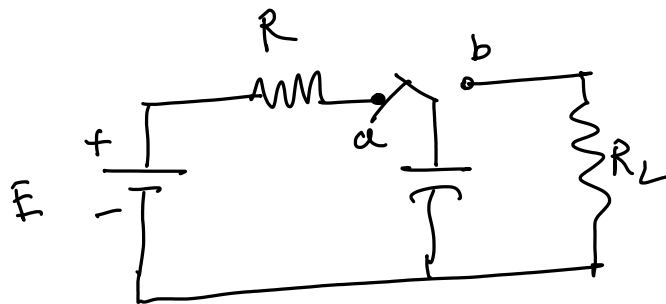

$$v(0^-) = 0$$


$$i = C \frac{dv}{dt}$$

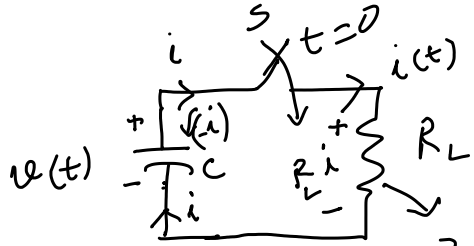

$$i(t) = \frac{v(t)}{R_L}$$

$$v(0^-) = V_0$$

$$\frac{1}{2} C V_0^2$$

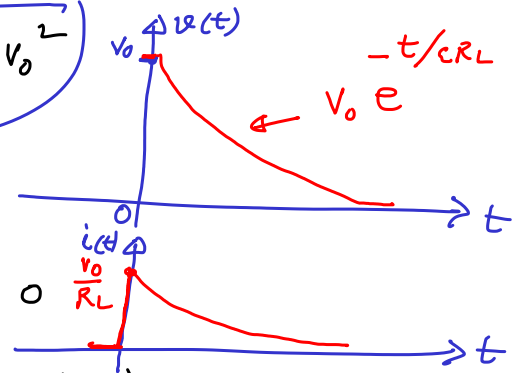

$$v(0^-) = V_0$$

$$-i = C \frac{dv}{dt}$$

$$R_L i = -C \frac{dv}{dt}$$

KVL :-

$$v - R_L i = 0$$

$$v - R_L \left(-C \frac{dv}{dt} \right) = 0$$


$$C R_L \frac{dv}{dt} + v = 0$$

$$\frac{dv}{dt} + \frac{v}{C R_L} = 0$$

$$e^{\frac{t}{C R_L}} \frac{dv}{dt} + \frac{1}{C R_L} e^{\frac{t}{C R_L}} v = 0 \quad \int_{t=0}^{\infty} i^2 R_L dt = \text{Total Energy dissipated in } R_L = \frac{1}{2} C V_0^2$$

$$\frac{d}{dt} \left(e^{\frac{t}{C R_L}} v \right) = 0$$

$$i(t) = \frac{V_0}{R_L} e^{-t/CR_L}$$

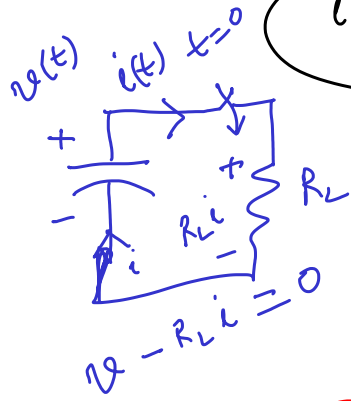

$$e^{t/CR_L} v = A$$


$$v = A e^{-t/CR_L}$$

$$v(0^-) = v(0^+) = v(0) = V_0$$

$$\text{Get } A = V_0$$

$$-i = C \frac{dv}{dt}$$

$$v(t) = V_0 e^{-t/CR_L}$$

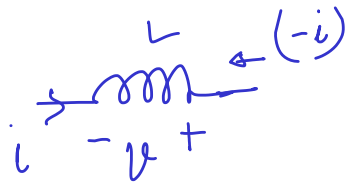


$$v = L \frac{d}{dt} (-i)$$


Inductor (L) 5mH



Capacitor

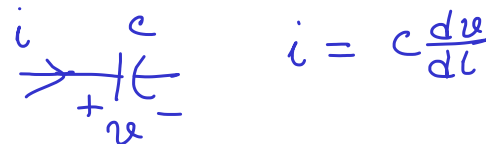

Resistance

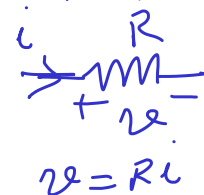

Are these element linear or not?


v is input signal
 i is the output response

$v = 0 \quad i = 0$

Homogeneity cond.

$i_1(t) = \frac{1}{L} \int_0^t v_1(t) dt$

$i_2(t) = \frac{1}{L} \int_0^t v_2 dt$

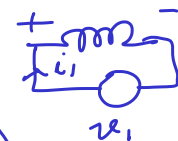

Principle Superposition:-

$v_1 \rightarrow i_1$
 $v_2 \rightarrow i_2$

$v_1 + v_2 \rightarrow i_1 + i_2$

$i_3(t) = \frac{1}{L} \int_0^t (v_1 + v_2) dt$
 $= i_1 + i_2$




Add $i_1 + i_2 = \frac{1}{L} \int_0^t (v_1 + v_2) dt$

Dec 17


$i = \frac{1}{L} \int_0^t v dt$
 $i(0^-) = 0$

What happens when inductor has finite initial current $i(0^-) \neq 0$

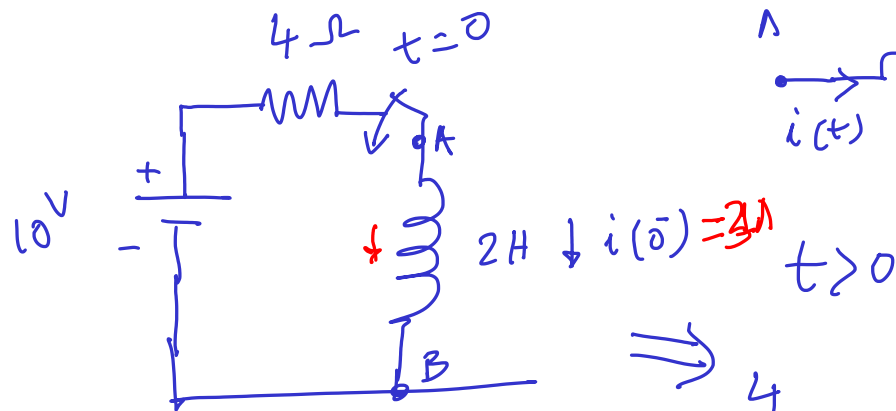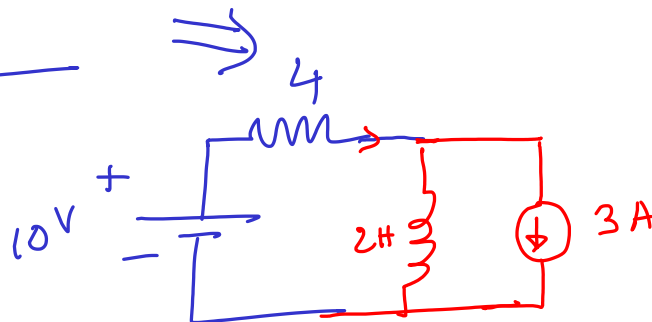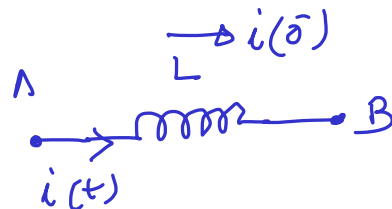
$$i(t) = i(0^-) + \frac{1}{L} \int_0^t v(t) dt$$



we link

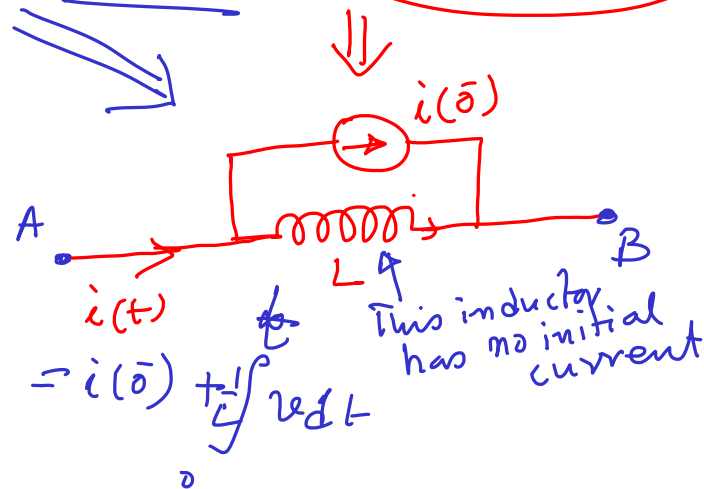

Is capacitor a linear element

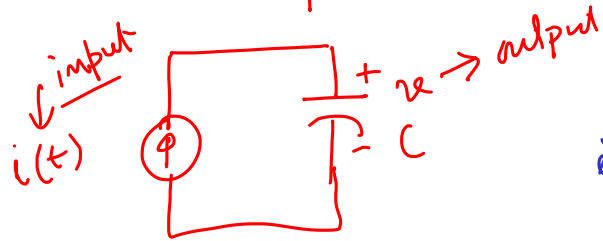

0 input $\rightarrow$ 0 output

$$i_1 + i_2 \rightarrow v_3 = 2 + \frac{1}{C} \int_0^t (i_1 + i_2) dt$$

$$v(t) = \frac{1}{C} \int_0^t i dt = \left(\frac{1}{C} \int_{-\infty}^0 i dt \right) + \frac{1}{C} \int_0^t i dt$$

$$\frac{V-s}{A-s} \rightarrow Cn$$

$i \rightarrow$ not an impulse

$$v(t) = v(0^-) + \frac{1}{C} \int_0^t i dt$$


Let $v(0^-) = 0$

input $i_1 \rightarrow$ output v_1

$i_2 \rightarrow v_2$

$i_1 + i_2 \rightarrow v_3$
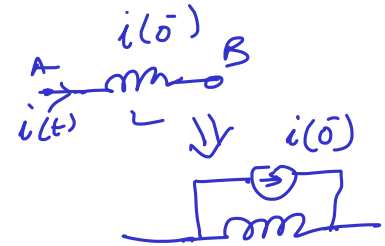
$$v_3(t) = \frac{1}{C} \int_0^t (i_1 + i_2) dt = \frac{1}{C} \int_0^t i_1 dt + \frac{1}{C} \int_0^t i_2 dt = v_1 + v_2$$




$$v_0 + \frac{1}{C} \int_0^t i dt \quad \text{Let } v(0^-) = 2V$$

$$v_1 = 2 + \frac{1}{C} \int_0^t i_1 dt$$

$$v_2 = 2 + \frac{1}{C} \int_0^t i_2 dt$$
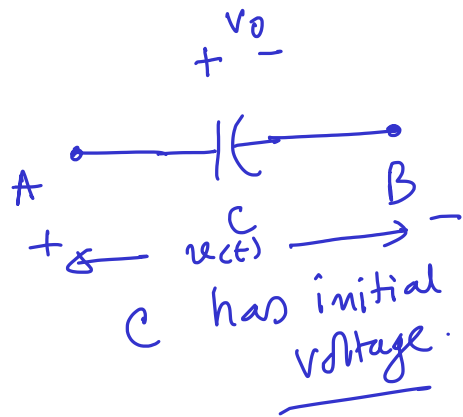
$$v_1 + v_2 = 4 + \frac{1}{C} \int_0^t (i_1 + i_2) dt$$



$$v(t) = V_0 + \frac{1}{C} \int_0^t i \, dt$$

constant 0

