
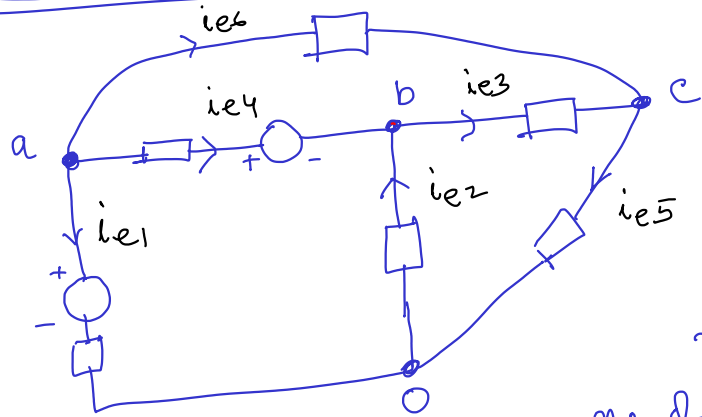


Graph Theory applied to network Problem :-

Lec 59

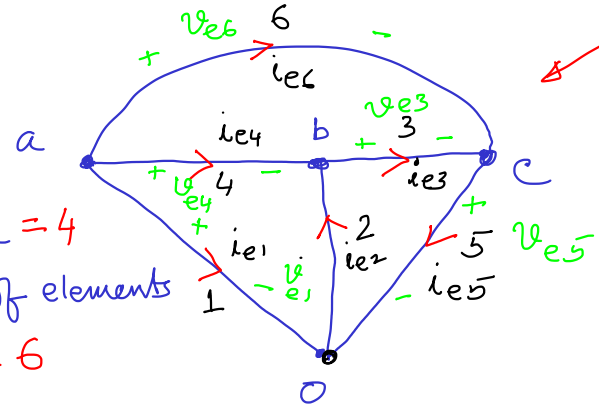

Graph of the
Network



Directed
Graph.

no. of nodes = $n = 4$

no. of branches = no. of elements
= $e = 6$

Incidence Matrix $[A]$

write KCL equations at nodes a, b, c and o


at node a: $i_{e1} + i_{e4} + i_{e6} = 0$ — (1)

--- b: $i_{e3} - i_{e4} - i_{e2} = 0$ — (2)

at node c: $i_{e5} - i_{e3} - i_{e6} = 0$ — (3)

--- at node o: $i_{e2} - i_{e4} - i_{e5} = 0 \rightarrow$ no new equation

Independent Eqⁿ

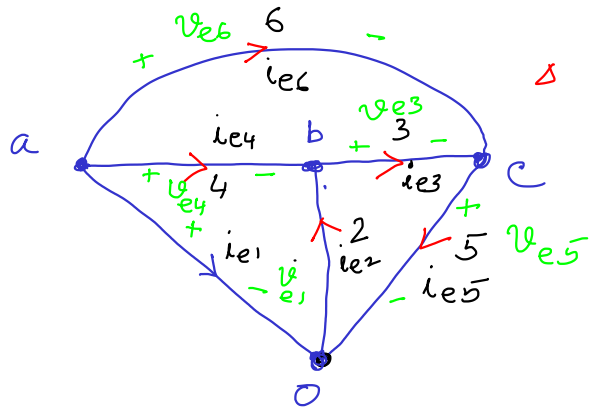

KCL at - node a:

$$i_{e1} + i_{e4} + i_{e6} = 0 \quad \text{--- (1)} \quad \checkmark$$

--- b:

$$i_{e3} - i_{e4} - i_{e2} = 0 \quad \text{--- (2)}$$

at node c:

$$i_{e5} - i_{e3} - i_{e6} = 0 \quad \text{--- (3)}$$

at node o:

$$i_{e2} - i_{e1} - i_{e5} = 0 \quad \text{--- (4)} \rightarrow \text{not new eq.}$$

[A]

$$\begin{array}{c} a \\ \rightarrow b \\ c \\ \rightarrow \end{array} \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 0 & 1 & -1 \\ \hline \vdots & \vdots & \vdots & \vdots & \vdots & \vdots \end{bmatrix} \begin{bmatrix} i_{e1} \\ i_{e2} \\ i_{e3} \\ i_{e4} \\ i_{e5} \\ i_{e6} \end{bmatrix}$$


$$= \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$\Rightarrow$

reduced incidence Matrix

$$[A][i_e] = [0]$$

--- (1)

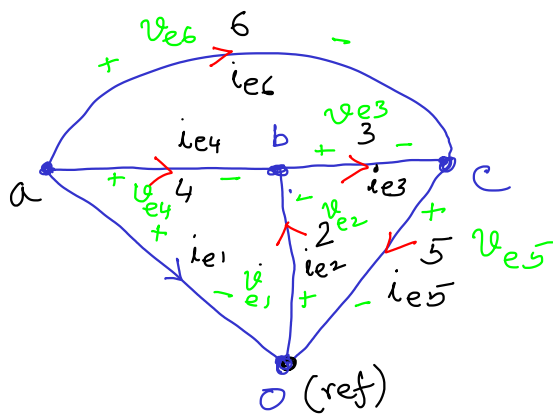

$$[A] [i_e] = [0]$$

$(n-1) \times e$ $\downarrow$ (ex1)

$$\begin{matrix} a \\ b \\ c \end{matrix}
 \begin{bmatrix}
 1 & 2 & 3 & 4 & 5 & 6 \\
 1 & 0 & 0 & 1 & 0 & 1 \\
 0 & -1 & 1 & -1 & 0 & 0 \\
 0 & 0 & -1 & 0 & 1 & -1
 \end{bmatrix}
 \begin{bmatrix} i_{e1} \\ i_{e2} \\ i_{e3} \\ i_{e4} \\ i_{e5} \\ i_{e6} \end{bmatrix}
 =
 \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$\downarrow$ ex1

If $n = \text{total nodes} = 4$
 $e = \text{no. of edges} = 6$

Try to express the element voltages
 in terms of node voltages (v_{ao}, v_{bo}, v_{co})

$$v_{e1} = v_{ao}$$

$$v_{e2} = v_{ob} = -v_{bo}$$

$$v_{e3} = v_{bo} - v_{co}$$

$$v_{e4} = v_{ao} - v_{bo}$$

$$v_{e5} = v_{co}$$

$$v_{e6} = v_{ao} - v_{co}$$

$$\begin{bmatrix} v_{e1} \\ v_{e2} \\ v_{e3} \\ v_{e4} \\ v_{e5} \\ v_{e6} \end{bmatrix}
 =
 \begin{bmatrix}
 v_{ao} & v_{bo} & v_{co} \\
 1 & 0 & 0 \\
 0 & -1 & 0 \\
 0 & 1 & -1 \\
 1 & -1 & 0 \\
 0 & 0 & 1 \\
 1 & 0 & -1
 \end{bmatrix}
 \begin{bmatrix} v_{ao} \\ v_{bo} \\ v_{co} \end{bmatrix}$$

$\downarrow$ ex1 $\downarrow$ ex (n-1)

(column vector)

$\rightarrow [A]^T$

or $[v_e] = [A]^T [v_N]$
 $\uparrow$ (ex1) $\downarrow$ ex(n-1)


$(n-1) \times 1$

(Reduced order) $[A]$ matrix



$$\begin{aligned} [A] [ie] &= [0] \\ [A]^T [v_N] &= [v_e] \end{aligned}$$

Solving ckt
by modal analysis
method these eqn^s
to be used.


Tie set Matrix $[B]$

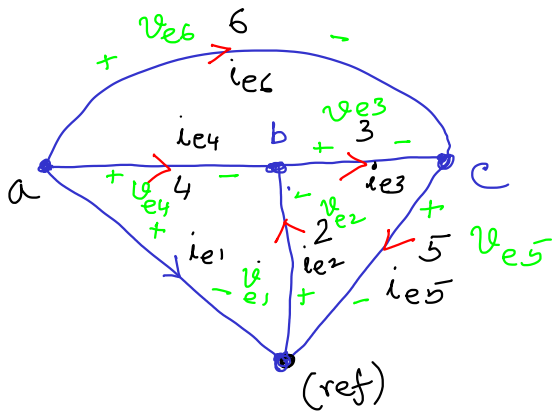


Tree of a graph.

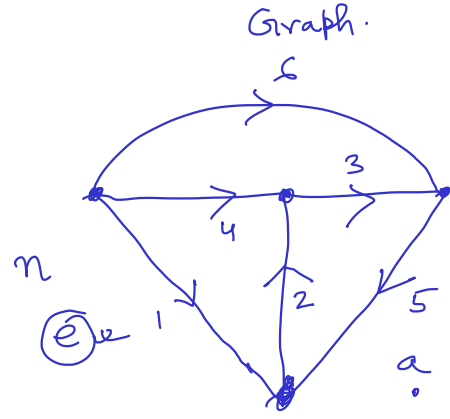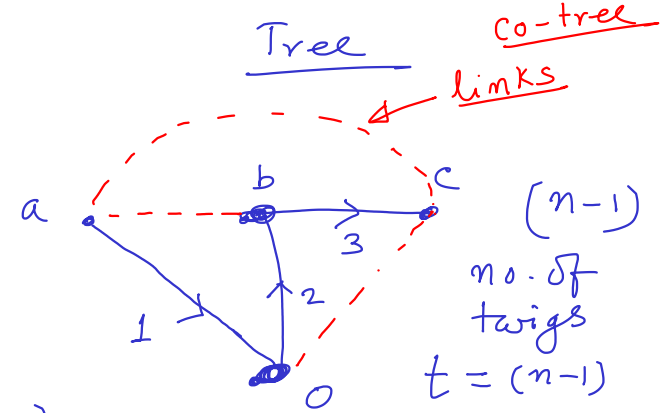

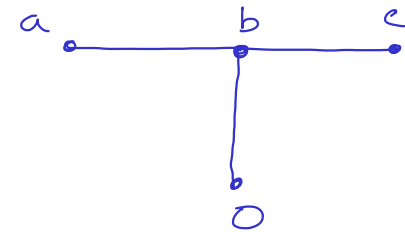branches of a co-tree = links
branches of a tree = twigs.
(n-1)




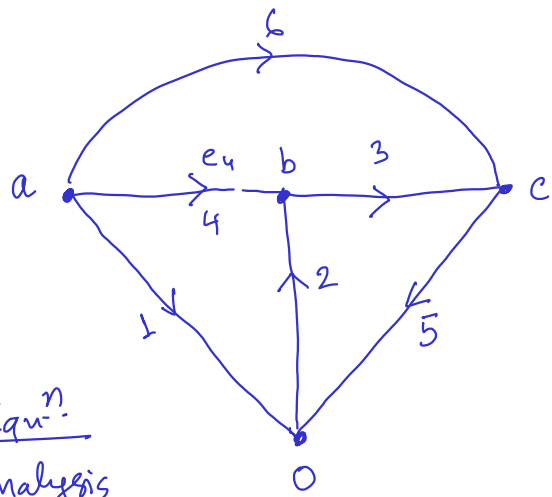Lec-61
 — Tree ^{twigs}
 - - - Co-tree
 ↓
links



KVL Equⁿ
Loop analysis

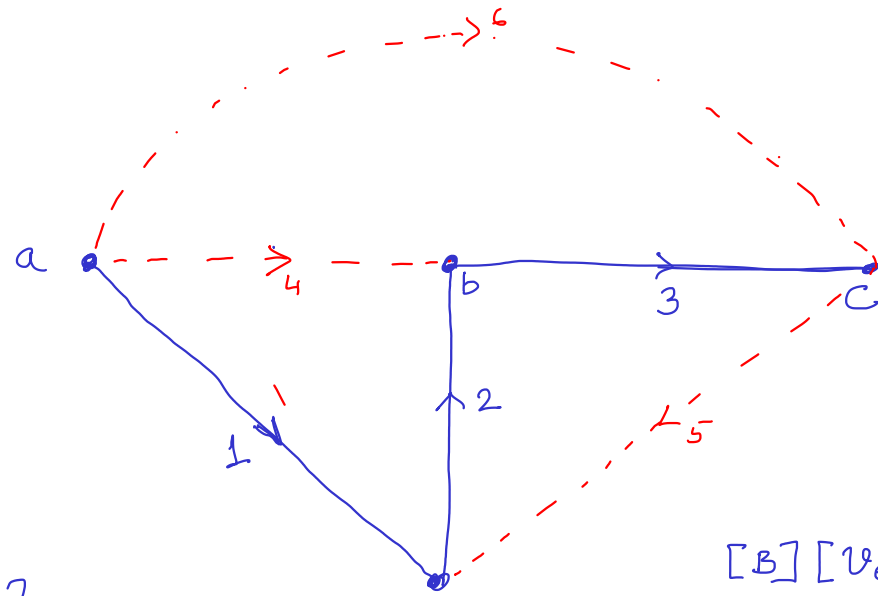
$$\left. \begin{array}{l} L4: e_4 - e_2 - e_1 = 0 \\ L5: e_5 + e_2 + e_3 = 0 \\ L6: e_6 - e_3 - e_2 - e_1 = 0 \end{array} \right\}$$



In matrix form

$[B][v_e] = [0]$ $\leftarrow$ KVL
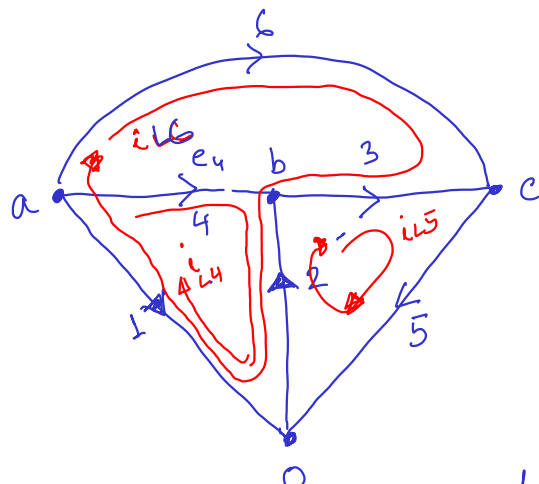
$$\begin{array}{l} L4 \\ L5 \\ L6 \end{array} \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ -1 & -1 & 0 & 1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 1 & 0 \\ -1 & -1 & -1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_{e1} \\ v_{e2} \\ v_{e3} \\ v_{e4} \\ v_{e5} \\ v_{e6} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$



$$\begin{cases} [B][v_e] = [v] \\ [B]^T[i_L] = [v_e] \end{cases} \rightarrow \text{KVL eqn. in fund loops}$$


$$l = e - (n - 1)$$

Expressing element currents in terms of loop currents.


$$\begin{cases} i_{e1} = -i_{L4} - i_{L6} \\ i_{e2} = i_{L5} - i_{L4} - i_{L6} \\ i_{e3} = i_{L5} - i_{L6} \\ i_{e4} = i_{L4} \\ i_{e5} = i_{L5} \\ i_{e6} = i_{L6} \end{cases}$$

$$[i_e] = [B]^T[i_L]$$
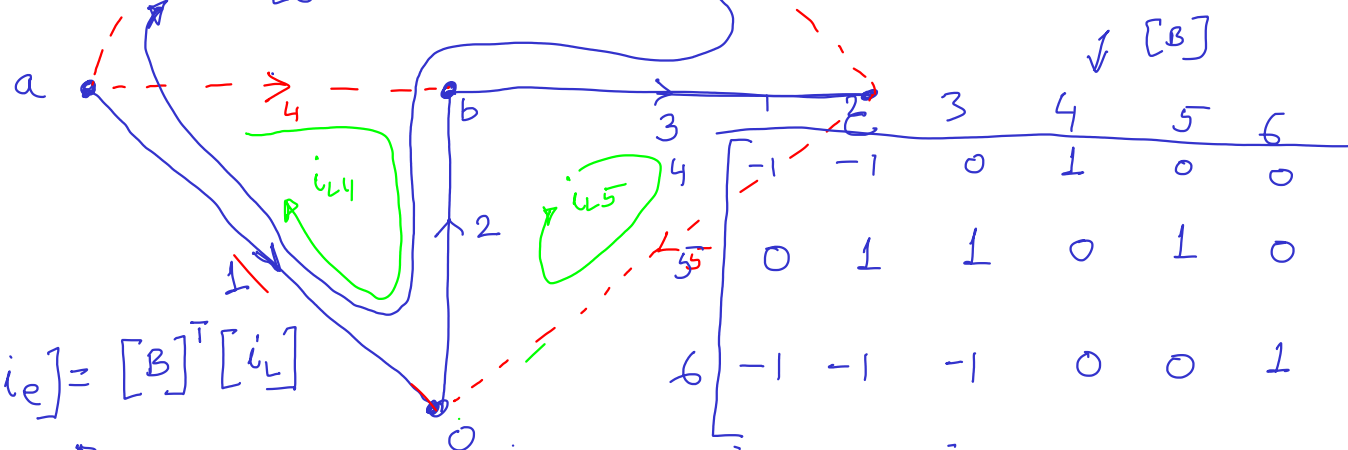
$$\begin{matrix} \text{ex 6} & \begin{bmatrix} i_{e1} \\ i_{e2} \\ i_{e3} \\ i_{e4} \\ i_{e5} \\ i_{e6} \end{bmatrix} & = & \begin{bmatrix} -1 & 0 & -1 \\ -1 & 1 & -1 \\ 0 & 1 & -1 \\ 0 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_{L4} \\ i_{L5} \\ i_{L6} \end{bmatrix} \end{matrix}$$


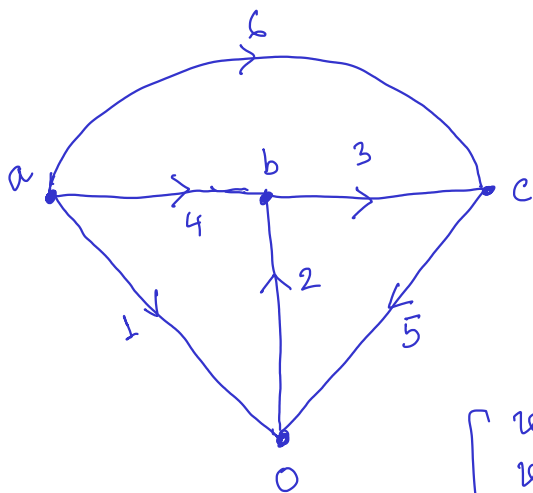
$$[B] = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \\ 6 \end{matrix} & \begin{bmatrix} -1 & -1 & 0 & 1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 1 & 0 \\ -1 & -1 & -1 & 0 & 0 & 1 \end{bmatrix} \end{matrix}$$



Incidence Matrix

$$[A] = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\ \begin{matrix} a \\ b \\ c \end{matrix} & \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 0 & 1 & -1 \end{bmatrix} \end{matrix}$$

$$[A][i_e] = 0$$

$$[v_e] = [A]^T [v_N]$$


$$v_N = \begin{bmatrix} v_{ao} \\ v_{bo} \\ v_{co} \end{bmatrix}$$

$$\rightarrow [v_e] = \begin{bmatrix} v_{e1} \\ v_{e2} \\ v_{e3} \\ v_{e4} \\ v_{e5} \\ v_{e6} \end{bmatrix}$$

Tie Set Matrix [B]:

$$[B][v_e] = [0] \rightarrow \text{KVL eqns in fundamental loops}$$

$$[B]^T [i_l] = [i_e]$$


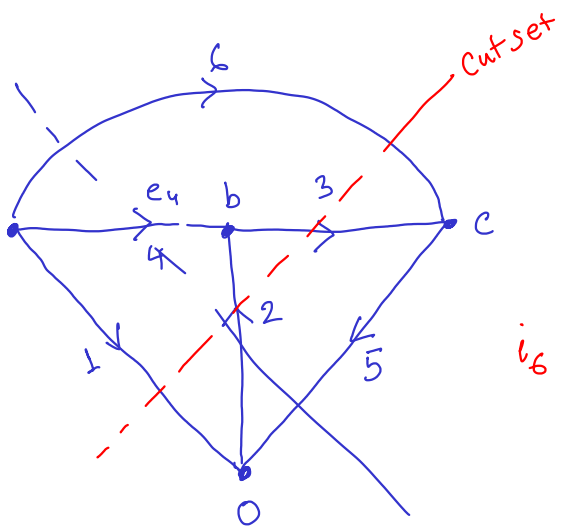


Cut set Matrix $[Q]$


KCL nst at nodes
but at some line (cut set)

$$i_1 - i_2 + i_3 - i_4 = 0$$


$$i_6 + i_3 - i_2 + i_1 = 0$$

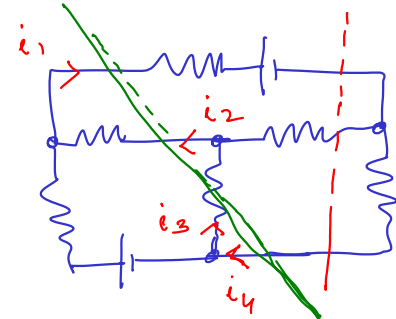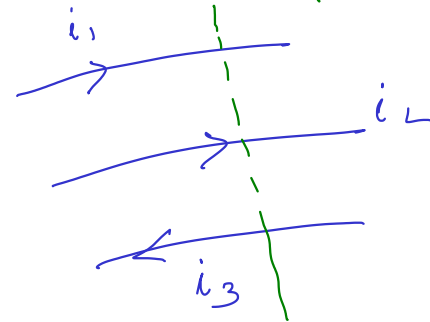

$$i_1 + i_2 - i_3 = 0$$

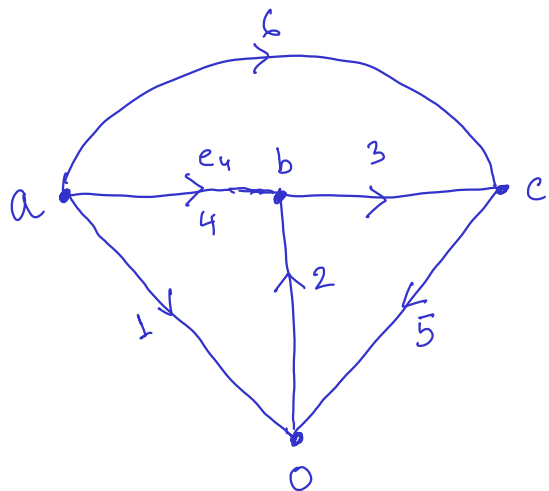

$\Rightarrow$

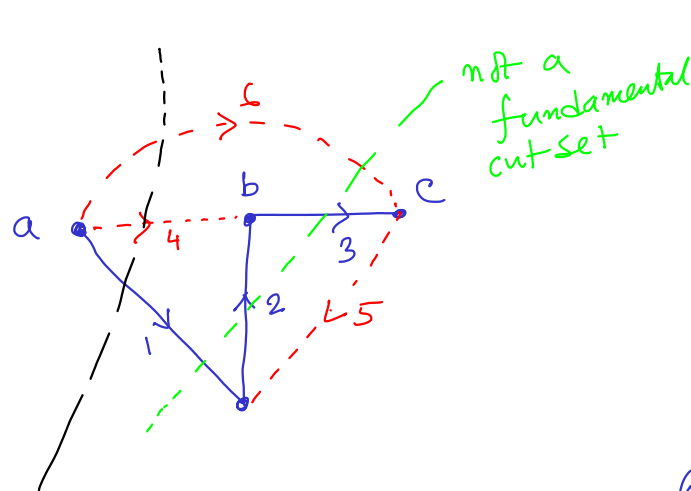

— (1) 2, 3 are twigs.
 - - - 4, 5, 6 are links.

Fundamental cut-set
 is one which will involve one and only one twig.

Write down KCL at the cut-set lines


KCL at cutsets:

$$CS-1: i_{e1} + i_{e4} + i_{e6} = 0$$

$$CS-2: i_{e2} + i_{e4} + i_{e6} - i_{e5} = 0$$

$$CS-3: i_{e3} + i_{e6} - i_{e5} = 0$$


connection

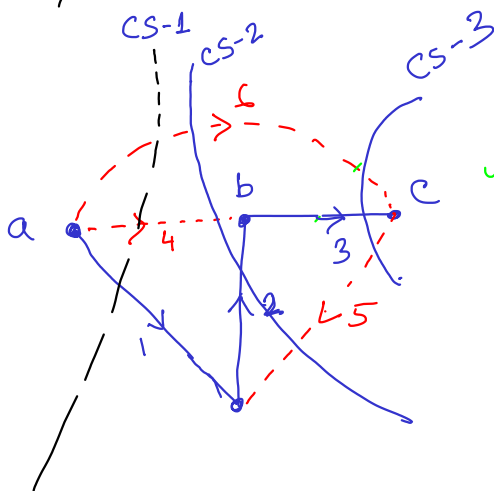

$$t = n - 1$$

[Q]

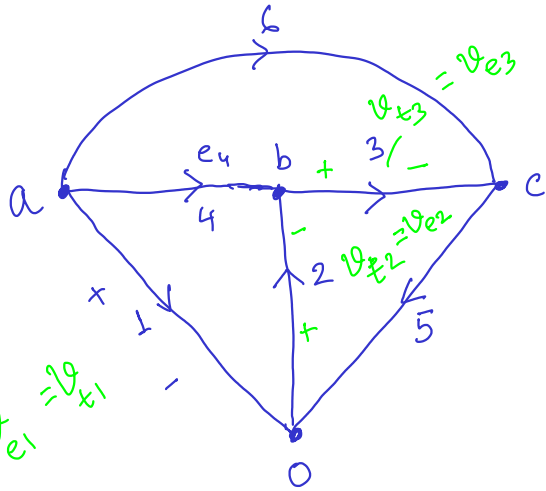Suppose v_{t1}, v_{t2} & v_{t3} are known




KCL at cutsets:

$$CS-1: i_{e1} + i_{e4} + i_{e6} = 0$$

$$CS-2: i_{e2} + i_{e4} + i_{e6} - i_{e5} = 0$$

$$CS-3: i_{e3} + i_{e6} - i_{e5} = 0$$

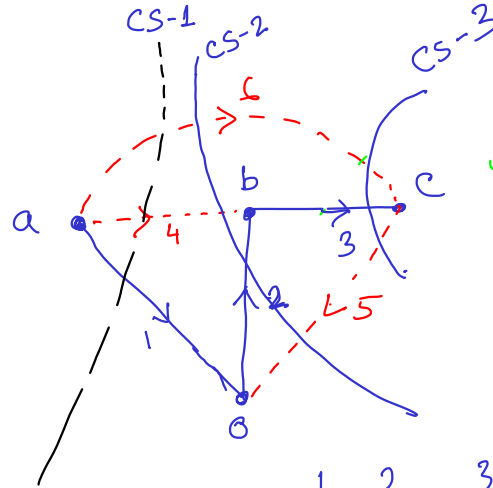

	1	2	3	4	5	6
CS-1	1	0	0	1	0	1
CS-2	0	1	0	1	-1	1
CS-3	0	0	1	0	-1	1

$$\begin{bmatrix} i_{e1} \\ i_{e2} \\ i_{e3} \\ i_{e4} \\ i_{e5} \\ i_{e6} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$[Q] [i_e] = [0]$$

$t \times e \quad e \times 1 \quad t \times 1$


① 2, 3 are twigs.

4, 5, 6 are links.

Fundamental cut-set is one which will involve one and only one twig.

[Q]

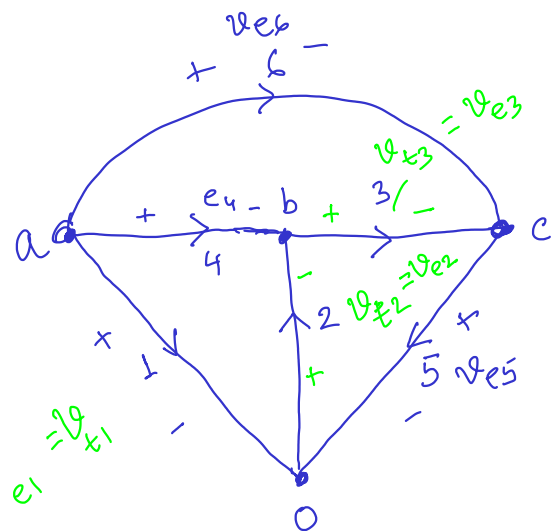Suppose v_{t1}, v_{t2} & v_{t3} are known



KCL at cutsets:


CS-1: $i_{e1} + i_{e4} + i_{e6} = 0$

CS-2: $i_{e2} + i_{e4} + i_{e6} - i_{e5} = 0$

CS-3: $i_{e3} + i_{e6} - i_{e5} = 0$

correction

$[Q][i_e] = 0$
 $[Q]^T[v_t] = [v_e]$

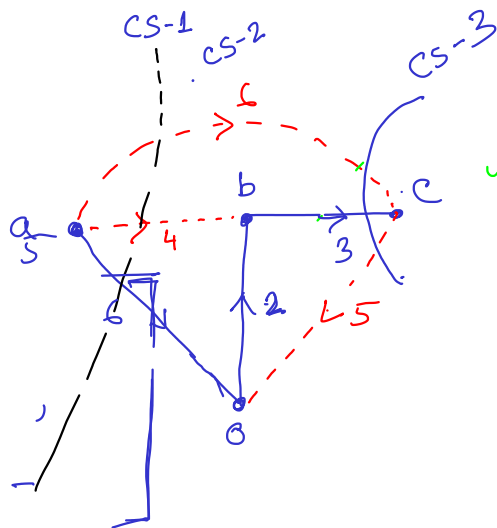

Relate element voltages with twig voltages

$v_{e1} = v_{t1}$

$v_{e2} = v_{t2}$

$v_{e3} = v_{t3}$

$v_{e4} = v_{t1} + v_{t2}$

$v_{e5} = -v_{t2} - v_{t3}$


$v_{e6} = v_{t1} + v_{t2} + v_{t3}$

$[A][i_e] = [0]$
 $[A]^T[v_t] = [v_e]$

$\begin{bmatrix} v_{e1} \\ v_{e2} \\ v_{e3} \\ v_{e4} \\ v_{e5} \\ v_{e6} \end{bmatrix} =$

$\begin{bmatrix} - & t_1 & - & t_2 & - & t_3 & - \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 1 & 0 \\ 0 & -1 & -1 \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} v_{t1} \\ v_{t2} \\ v_{t3} \end{bmatrix}$

$[Q]^T[v_t]$

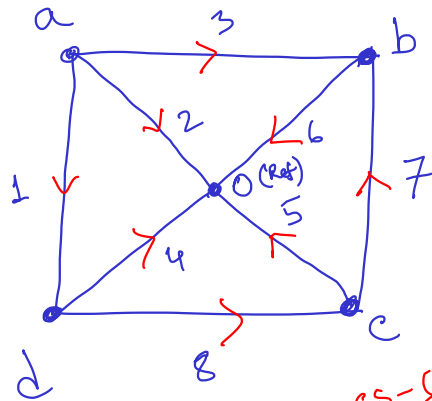


$$n = 5$$

$$e = 8$$

$$[B][v_e] = 0$$

Take This Tree

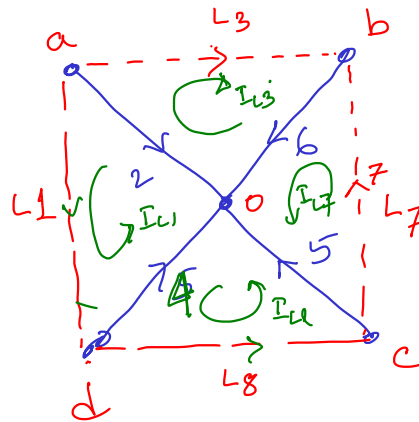

write $[Q]$ matrix $L8$

$$[A] = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \end{matrix} \\ \begin{matrix} a \\ b \\ c \\ d \end{matrix} & \begin{bmatrix} 1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & -1 & 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 1 & -1 \\ -1 & 0 & 0 & 1 & 0 & 0 & 0 & 1 \end{bmatrix} \end{matrix}$$

KCL


$$[B] =$$



$$L3:$$

$$L1:$$

$$L7:$$
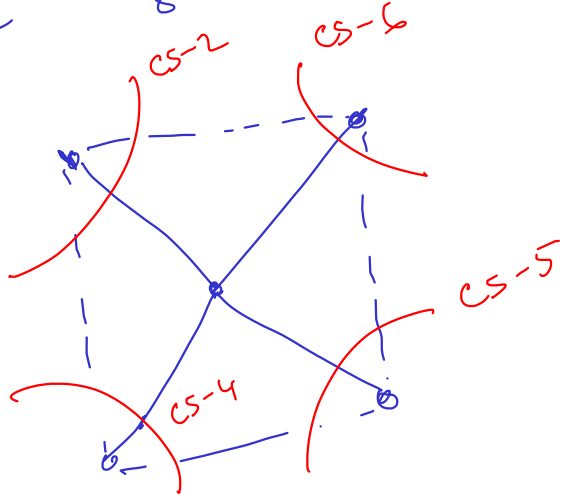
$$\begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \\ 0 & -1 & 1 & 0 & 0 & 1 & 0 & 0 \\ 1 & -1 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & -1 & 1 & 0 & 0 & 1 \end{bmatrix}$$



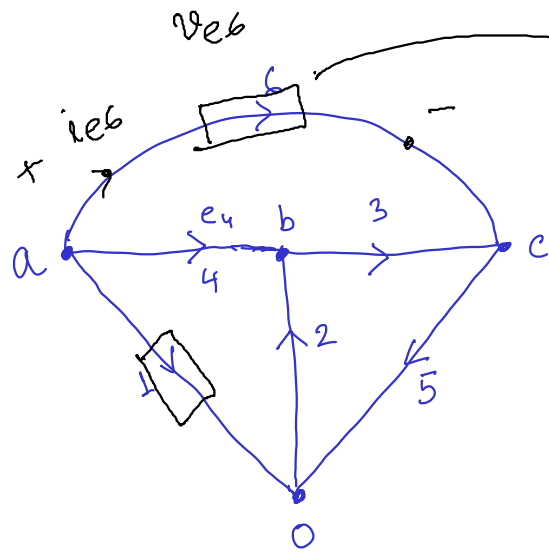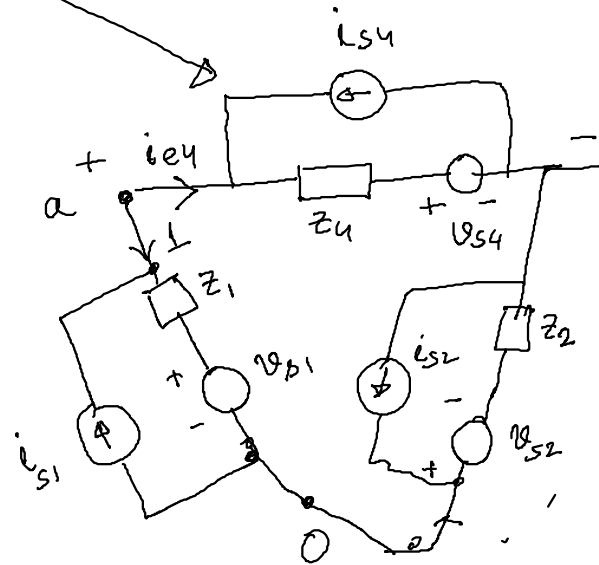

incidence matrix

$$\rightarrow [A][i_e] = [0] \quad \text{KCL}$$

$$[A]^T [v_N] = [v_e] \quad \text{Nodal}$$

etc

$$\text{Tie-set} \quad [B][v_e] = [0] \quad \text{KVL}$$

$$[B]^T [i_L] = [i_e] \quad \text{Loop analysis}$$



etc

$$\text{Cut-set} \quad [Q][i_e] = [0] \quad \text{KCL at fund. cutsets}$$

$$[Q]^T [v_t] = [v_e]$$

Want to solve a network problem by for loop analysis

k^{th} element looks like:

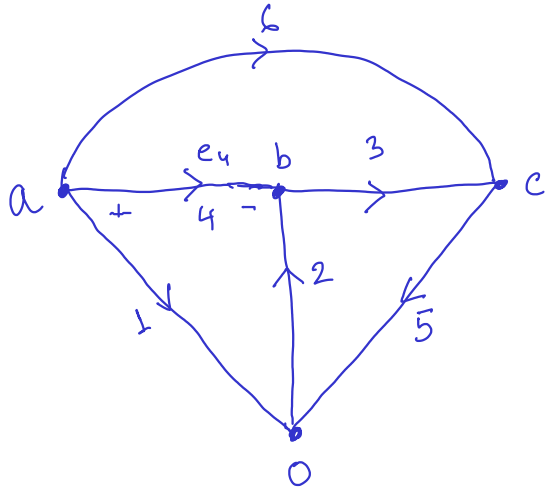
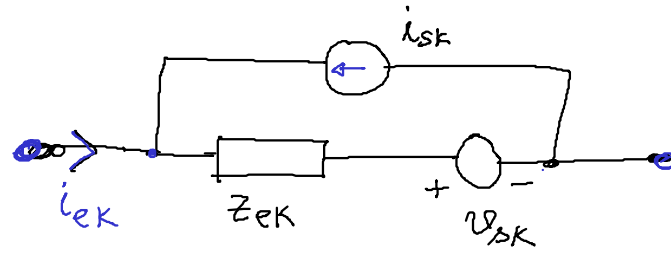


$i_{sk} \rightarrow$ source current
in the k^{th}
element

$v_{sk} \rightarrow$ source voltage
in k^{th} element

Want to solve a network problem by loop analysis

k^{th} element looks like:

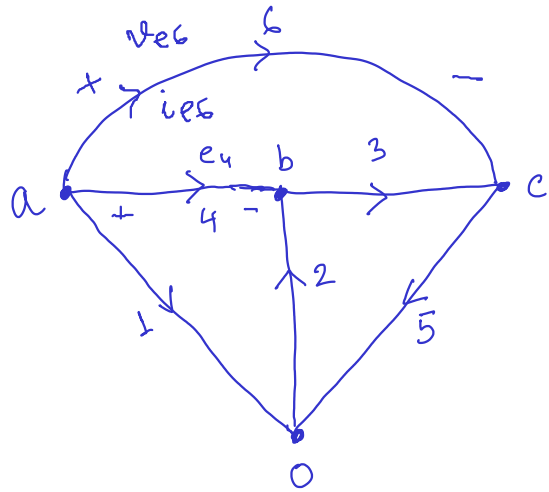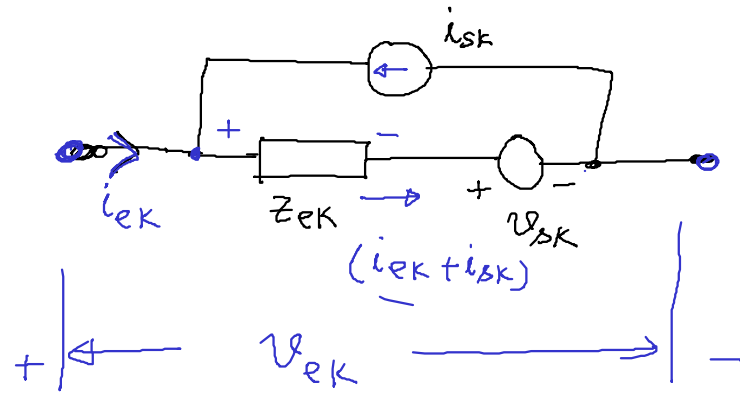

$i_{sk} \rightarrow$ source current
in the k^{th}
element

$v_{sk} \rightarrow$ source voltage
in k^{th} element

$$v_{ek} = Z_{ek}(i_{ek} + i_{sk}) + v_{sk} = Z_{ek} i_{ek} + Z_{ek} i_{sk} + v_{sk}$$

$$\begin{array}{l} v_{e1} = Z_{e1} i_{e1} + Z_{e1} i_{s1} + v_{s1} \\ v_{e2} = Z_{e2} i_{e2} + Z_{e2} i_{s2} + v_{s2} \\ v_{e3} = Z_{e3} i_{e3} + Z_{e3} i_{s3} + v_{s3} \end{array} \quad \left| \quad \begin{array}{l} v_{e4} = Z_{e4} i_{e4} + Z_{e4} i_{s4} + v_{s4} \\ v_{e5} = Z_{e5} i_{e5} + Z_{e5} i_{s5} + v_{s5} \\ v_{e6} = Z_{e6} i_{e6} + Z_{e6} i_{s6} + v_{s6} \end{array} \right.$$

$$v_{ek} = z_{ek}(i_{ek} + i_{sk}) + v_{sk} = z_{ek} i_{ek} + z_{ek} i_{sk} + v_{sk}$$

$$\begin{array}{l} v_{e1} = z_{e1} i_{e1} + z_{e1} i_{s1} + v_{s1} \\ v_{e2} = z_{e2} i_{e2} + z_{e2} i_{s2} + v_{s2} \\ v_{e3} = z_{e3} i_{e3} + z_{e3} i_{s3} + v_{s3} \end{array} \quad \left| \quad \begin{array}{l} v_{e4} = z_{e4} i_{e4} + z_{e4} i_{s4} + v_{s4} \\ v_{e5} = z_{e5} i_{e5} + z_{e5} i_{s5} + v_{s5} \\ v_{e6} = z_{e6} i_{e6} + z_{e6} i_{s6} + v_{s6} \end{array} \right.$$

$$\begin{aligned} [v_e] &= [z_e][i_e] \\ &\quad + [z_e][i_s] \\ &\quad + [v_s] \end{aligned}$$

$$\begin{bmatrix} v_{e1} \\ v_{e2} \\ v_{e3} \\ v_{e4} \\ v_{e5} \\ v_{e6} \end{bmatrix} = \begin{bmatrix} z_{e1} & & & & & \\ & z_{e2} & & & & \\ & & z_{e3} & & & \\ & & & z_{e4} & & \\ & & & & z_{e5} & \\ & & & & & z_{e6} \end{bmatrix} \begin{bmatrix} i_{e1} \\ i_{e2} \\ i_{e3} \\ i_{e4} \\ i_{e5} \\ i_{e6} \end{bmatrix} + \begin{bmatrix} z_{e1} & & & & & \\ & z_{e2} & & & & \\ & & & & & \\ & & & & & \\ & & & & & \\ & & & & & z_{e6} \end{bmatrix} \begin{bmatrix} i_{s1} \\ i_{s2} \\ i_{s3} \\ i_{s4} \\ i_{s5} \\ i_{s6} \end{bmatrix} + \begin{bmatrix} v_{s1} \\ v_{s2} \\ v_{s3} \\ v_{s4} \\ v_{s5} \\ v_{s6} \end{bmatrix}$$

$$[v_e] = [z_e][i_e] + [z_e][i_s] + [v_s]$$

$$[B][v_e] = 0$$

$$\frac{\text{KVL}}{[B]^T [i_L]} \quad \swarrow \text{loop current}$$

Premultiply by $[B]$

$$[B][v_e] = [B][z_e][i_e] + [B][z_e][i_s] + [B][v_s] = 0 \quad = [i_e]$$

$$\text{or} \quad [B][z_e][i_e] = -[B][z_e][i_s] - [B][v_s]$$

$$\text{or} \quad \underline{[B][z_e][B]^T [i_L]} = -[B][z_e][i_s] - [B][v_s]$$

$\nwarrow [Z] = \text{loop imp. matrix} -$

$$\nwarrow [i_L] = -[Z]^{-1} [B][z_e][i_s] - [Z]^{-1} [B][v_s]$$

$$[i_e] = [B]^T [i_L]$$

$$\text{Then } i_{z_1} = i_{e1} + i_{s1} \quad \left| \begin{array}{l} [i_{zk}] = [i_e] \\ \quad \quad \quad + [i_s] \end{array} \right.$$



Want to solve a network problem by Nodal analysis

lec 65

k^{th} element looks like:

$$[A][i_e] = [0]$$

$$[A]^T [v_N] = [v_e]$$

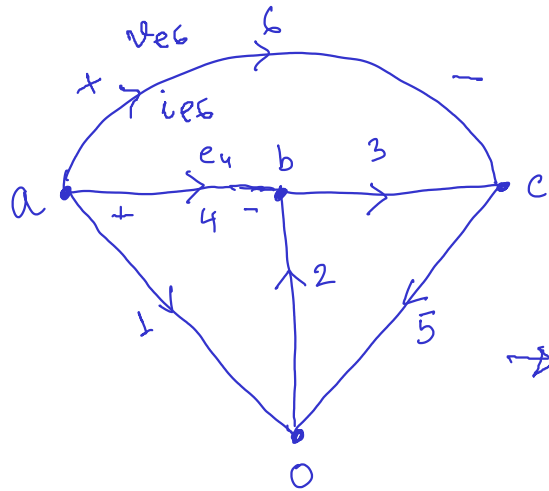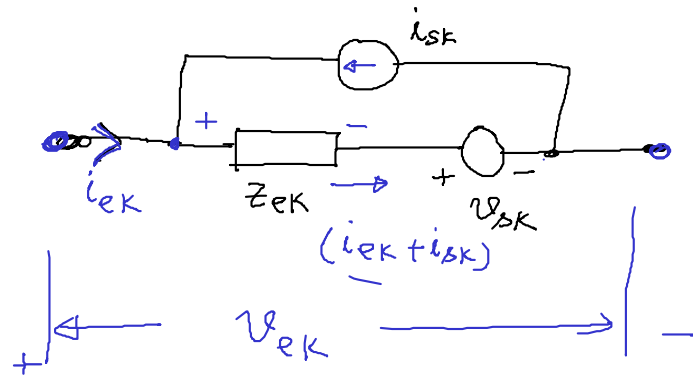

$i_{sk} \rightarrow$ source current in the k^{th} element

$v_{sk} \rightarrow$ source voltage in k^{th} element

$$i_{ee} = [i_e] + [i_s]$$

$$v_{ek} = Z_{ek} i_{ek} + Z_{ek} i_{sk} + v_{sk}$$

$$Z_{ek} i_{ek} = v_{ek} - Z_{ek} i_{sk} - v_{sk}$$

$$i_{ek} = \frac{1}{Z_{ek}} v_{ek} - i_{sk} - \frac{v_{sk}}{Z_{ek}} = Y_{ek} v_{ek} - i_{sk} - Y_{ek} v_{sk}$$

$$v_{ek} = z_{ek} (\underline{i_{ek} + i_{sk}}) + v_{sk} = z_{ek} i_{ek} + z_{ek} i_{sk} + v_{sk} \quad \left\{ \begin{array}{l} [A][i_e] = [0] \\ [A]^T [v_N] = [v_e] \end{array} \right.$$

After getting $[v_N]$

$$i_{ek} = \frac{1}{z_{ek}} v_{ek} - i_{sk} - \frac{v_{sk}}{z_{ek}} = y_{ek} v_{ek} - i_{sk} - y_{ek} v_{sk}$$

or, $i_{ek} = y_{ek} v_{ek} - i_{sk} - y_{ek} v_{sk}$

$[Y] = \begin{bmatrix} y_{e1} & y_{e2} & \dots & y_{en} \\ \vdots & \vdots & \ddots & \vdots \\ y_{n1} & y_{n2} & \dots & y_{nn} \end{bmatrix}$ $[v_e] = [A]^T [v_N]$

$$[i_e] = [Y][v_e] - [i_s] - [Y][v_s]$$


$$[A][i_e] = [A][Y][v_e] - A[i_s] - [A][Y][v_s] = [0]$$

$$= [0] \quad \therefore [A][Y][v_e] = [A][i_s] + [A][Y][v_s]$$


Node Admittance
matrix $[Y]$

$$\underline{[A][Y][A]^T} [v_N] = [A][i_s] + [A][Y][v_s]$$

Example

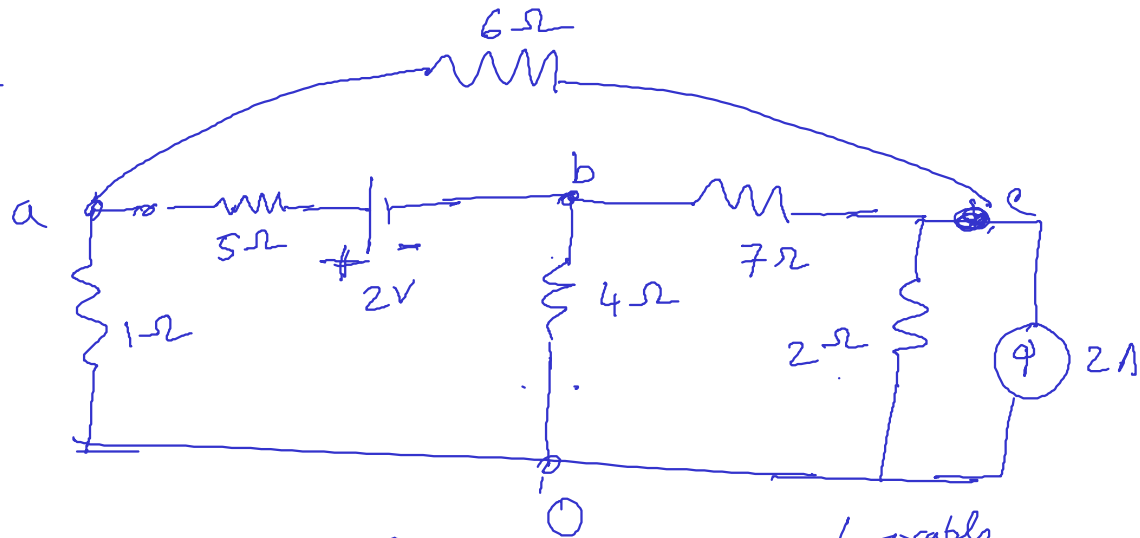

↓ graph

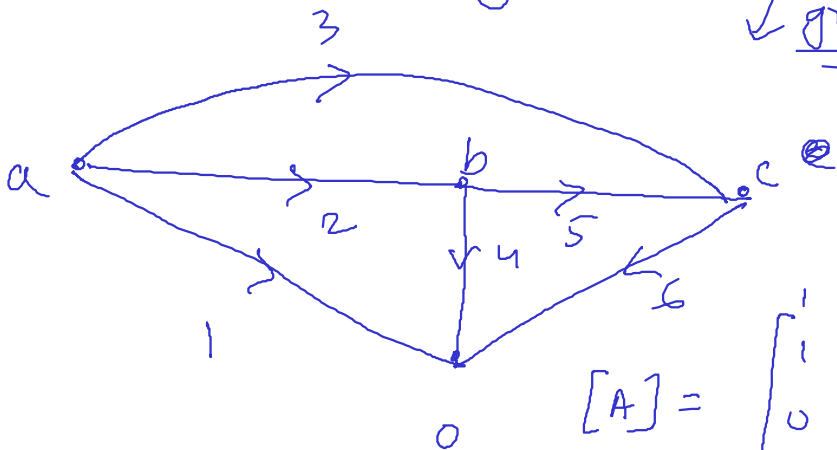

$$[A] =$$

$$\begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 1 & 1 & 0 \\ 0 & 0 & -1 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_{e1} \\ i_{e2} \\ i_{e3} \\ i_{e4} \\ i_{e5} \\ i_{e6} \end{bmatrix}$$

$$[Y] = \begin{bmatrix} 1 & 1/5 & 1/6 & 1/4 & 1/7 & 1/2 \\ 1 & 5 & 6 & 4 & 7 & 2 \end{bmatrix}$$

$$[V_s] = \begin{bmatrix} 0 \\ 2 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$[I_s] = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 2 \end{bmatrix}$$