

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

$z_{12} = z_{21}$
for Reciprocity

lec: 76

if $z_{11} = z_{22} \rightarrow$ symmetric

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$\left. \frac{V_1}{I_1} \right|_{I_2=0} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$\left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$\left. \begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned} \right\} \Rightarrow \left. \frac{V_1}{I_1} \right|_{I_2=0} \Rightarrow$$

$$0 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

$$V_2 = -\frac{y_{21}}{y_{22}} V_1$$

$$0 = y_{21} V_1 + y_{22} V_2$$

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$\Rightarrow I_1 = y_{11} V_1 - \frac{y_{21} y_{12}}{y_{22}} V_1$$

$$= \frac{(y_{11} y_{22} - y_{21} y_{12}) V_1}{y_{22}}$$


$$\therefore \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{y_{22}}{y_{11} y_{22} - y_{21} y_{12}}$$

$$\therefore \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{y_{11}}{y_{11} y_{22} - y_{21} y_{12}}$$

$$y_{11} = y_{22}$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

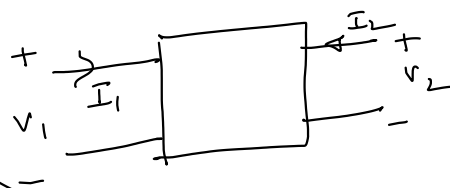

$$\left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \& \quad \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$\left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$0 = h_{21} I_1 + h_{22} V_2 \quad \therefore V_2 = -\frac{h_{21}}{h_{22}} I_1$$

$$\rightarrow V_1 = h_{11} I_1 - \frac{h_{12} h_{21}}{h_{22}} I_1$$

$$\left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} \quad \dots \textcircled{1}$$

$$\left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$V_1 = h_{11} \times 0 + h_{12} V_2 = h_{12} V_2$$


$$I_2 = h_{21} \times 0 + h_{22} V_2 = h_{22} V_2$$

$$\left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{1}{h_{22}}$$

$$\therefore \frac{1}{h_{22}} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}}$$

$$\text{or } h_{11} h_{22} - h_{12} h_{21} = 1$$
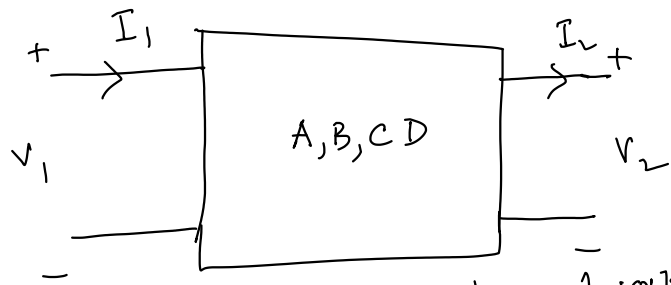
$$\text{or } \det \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = 1$$



$$\begin{aligned} V_1 &= AV_2 + BI_2 \\ I_1 &= CV_2 + DI_2 \end{aligned}$$

If this Two-port network is to be symmetric

$$\left. \frac{V_1}{I_1} \right|_{I_2=0} = \left. \frac{V_2}{-I_2} \right|_{I_1=0}$$

$$\left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$\begin{aligned} V_1 &= AV_2 \\ I_1 &= CV_2 \end{aligned}$$

$$\therefore \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{A}{C} \quad \dots \textcircled{1}$$

$$\left. \frac{V_2}{-I_2} \right|_{I_1=0}$$

$$V_1 = AV_2 + BI_2$$

$$\rightarrow 0 = CV_2 + DI_2$$


$$\therefore CV_2 = -DI_2$$

$$\text{or } \left. \frac{V_2}{-I_2} \right|_{I_1=0} = \frac{D}{C}$$

$$\therefore \frac{A}{C} = \frac{D}{C}$$

$$\text{or } \boxed{A = D}$$

Series Connection of Two port Networks

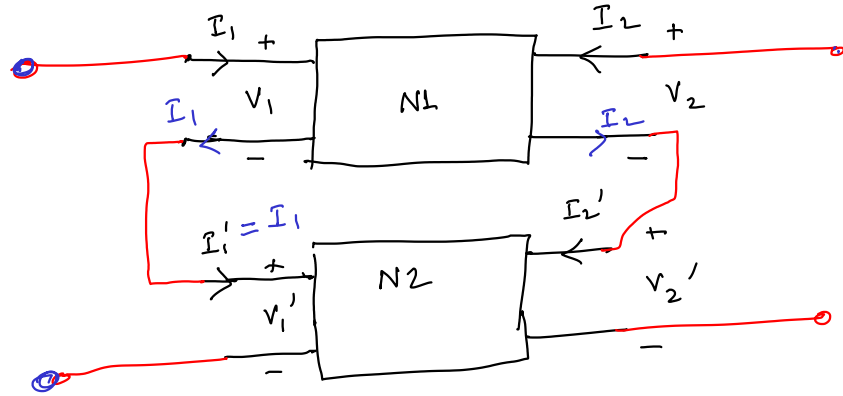

$$I_1' = I_1$$

$$\text{and } I_2' = I_2$$

Add (1) + (5)

$$V_1 + V_1' = (z_{11} + z_{11}') I_1 + (z_{12} + z_{12}') I_2$$

Add (2) + (6) $V_2 + V_2' = (z_{21} + z_{21}') I_1 + (z_{22} + z_{22}') I_2$

Overall imp. matrix is

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} + \begin{bmatrix} z_{11}' & z_{12}' \\ z_{21}' & z_{22}' \end{bmatrix} = \begin{bmatrix} z_{11} + z_{11}' & z_{12} + z_{12}' \\ z_{21} + z_{21}' & z_{22} + z_{22}' \end{bmatrix}$$

for N1 :-

$$V_1 = z_{11} I_1 + z_{12} I_2 \quad \text{--- (1) } \checkmark$$

$$V_2 = z_{21} I_1 + z_{22} I_2 \quad \text{--- (2) } *$$

for N2 :-


$$V_1' = z_{11}' I_1' + z_{12}' I_2' \quad \text{--- (3) }$$

$$V_2' = z_{21}' I_1' + z_{22}' I_2' \quad \text{--- (4) }$$

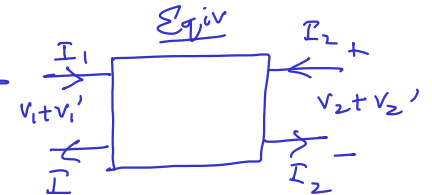
(3) & (4)

$$V_1' = z_{11}' I_1 + z_{12}' I_2 \quad \text{--- (5) } \checkmark$$

$$V_2' = z_{21}' I_1 + z_{22}' I_2 \quad \text{--- (6) } *$$



dec-77

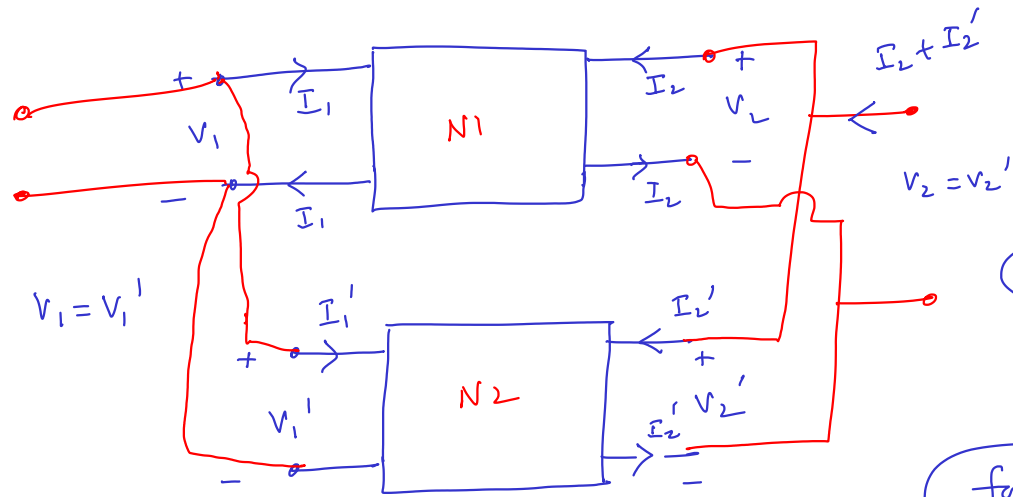

Connect input ports
in parallel & output ports in parallel

$$V_1' = V_1$$

for $N1$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (1)}$$


$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (2)}$$

for $N2$

$$I_1' = Y_{11}' V_1 + Y_{12}' V_2 \quad \text{--- (3)}$$

$$I_2' = Y_{21}' V_1 + Y_{22}' V_2 \quad \text{--- (4)}$$

/// Equiv

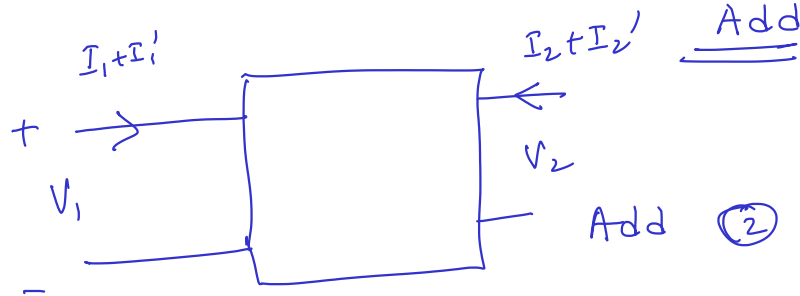


① + ③

$$I_1 + I_1' = (Y_{11} + Y_{11}') V_1 + (Y_{12} + Y_{12}') V_2$$

$$\text{Add } ② + ④ \quad I_2 + I_2' = (Y_{21} + Y_{21}') V_1 + (Y_{22} + Y_{22}') V_2$$

$$\therefore [Y_{eq}] = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} + \begin{bmatrix} Y_{11}' & Y_{12}' \\ Y_{21}' & Y_{22}' \end{bmatrix}$$

Two Port Network in Cascade

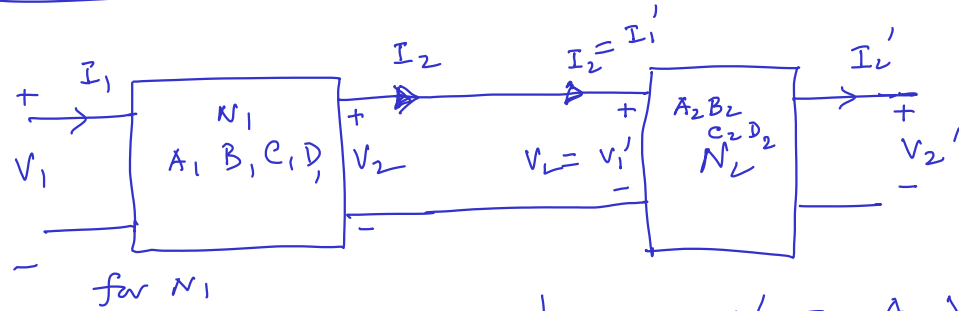

$$V_1 = A_1 V_2 + B_1 I_2$$

$$I_1 = C_1 V_2 + D_1 I_2$$

$$\text{or } \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$\text{or } \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_2' \\ I_2' \end{bmatrix}$$

$$= \begin{bmatrix} A_{eq} & B_{eq} \\ C_{eq} & D_{eq} \end{bmatrix}$$


$$V_2 = V_1' = A_2 V_2' + B_2 I_2'$$

$$I_2 = I_1' = C_2 V_2' + D_2 I_2'$$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_2' \\ I_2' \end{bmatrix}$$

Represent Each
two-Network in terms of
A-B-C-D parameters


Equiv.

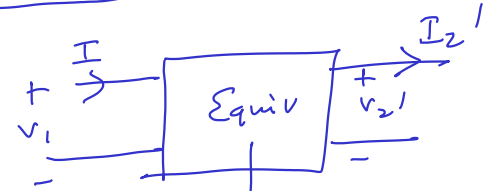

ABC D parameters
of this equiv
Two port network

$$= \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \times \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

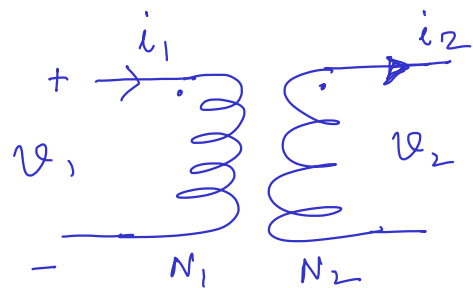How to represent an ^{ideal} Transformer as a two port network



$$\frac{v_2}{v_1} = \frac{N_2}{N_1}$$

$$N_2 i_2 = N_1 i_1$$

$$i_2 = \frac{N_1}{N_2} i_1$$

$$\therefore v_2 = \frac{N_2}{N_1} v_1 = \frac{v_1}{a}$$

$$\therefore \begin{aligned} v_2 &= \frac{1}{a} v_1 \\ i_2 &= a i_1 \end{aligned}$$

$$\text{Let } \frac{N_1}{N_2} = a$$

$$\left. \begin{aligned} v_1 &= a v_2 \\ i_1 &= \frac{i_2}{a} \end{aligned} \right|$$

$$[h] = \begin{bmatrix} 0 & a \\ a & 0 \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \underbrace{\begin{bmatrix} a & 0 \\ 0 & \frac{1}{a} \end{bmatrix}}_{\substack{\uparrow \\ \begin{bmatrix} A & B \\ C & D \end{bmatrix}}} \begin{bmatrix} v_2 \\ i_2 \end{bmatrix}$$

$$v_1 = h_{11} i_1 + h_{12} v_2 = a v_2$$


$$i_1 = h_{21} i_1 + h_{22} v_2 = a i_1$$

$$\left\{ \begin{aligned} v_1 &= z_{11} i_1 + z_{12} i_2 \\ v_2 &= z_{21} i_1 + z_{22} i_2 \end{aligned} \right.$$

$$i_1 = y_{11} v_1 + y_{12} v_2$$

$$i_2 = y_{21} v_1 + y_{22} v_2$$

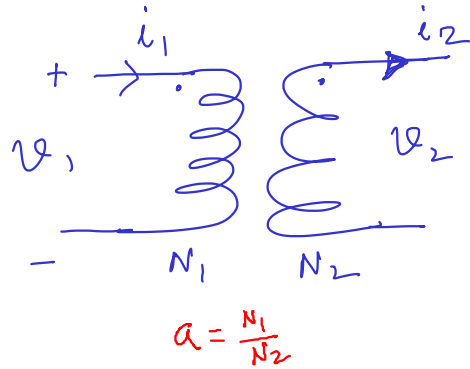How to represent an ^{ideal} Transformer as a two port network



$$\frac{v_2}{v_1} = \frac{N_2}{N_1}$$

$$\therefore v_2 = \frac{N_2}{N_1} v_1 = \frac{v_1}{a}$$

$$\text{def } \frac{N_1}{N_2} = a$$

$$N_2 i_2 = N_1 i_1$$

$$i_2 = \frac{N_1}{N_2} i_1$$

$$\therefore \begin{cases} v_2 = \frac{1}{a} v_1 \\ i_2 = a i_1 \end{cases}$$

$$\begin{cases} v_1 = a v_2 \\ i_1 = \frac{i_2}{a} \end{cases}$$

$$[h] = \begin{bmatrix} 0 & a \\ a & 0 \end{bmatrix}$$


$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \underbrace{\begin{bmatrix} a & 0 \\ 0 & \frac{1}{a} \end{bmatrix}}_A \begin{bmatrix} v_2 \\ i_2 \end{bmatrix}$$

$$\begin{aligned} v_1 &= h_{11} i_1 + h_{12} v_2 = a v_2 \\ i_2 &= h_{21} i_1 + h_{22} v_2 = a i_1 \end{aligned}$$

$$\begin{cases} v_1 = z_{11} i_1 + z_{12} i_2 \\ v_2 = z_{21} i_1 + z_{22} i_2 \end{cases}$$

$$\begin{cases} i_1 = y_{11} v_1 + y_{12} v_2 \\ i_2 = y_{21} v_1 + y_{22} v_2 \end{cases}$$

In terms of ABCD (or T parameters)

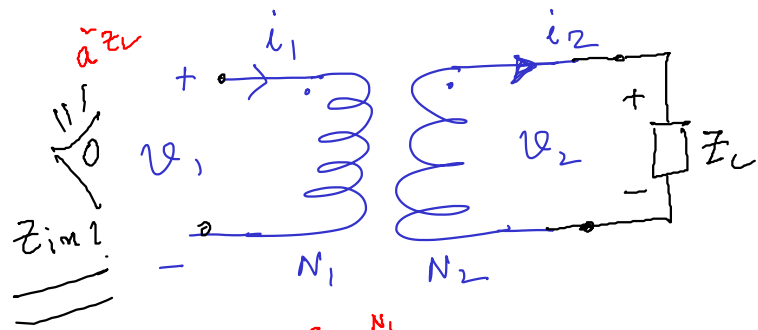


$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} a & 0 \\ 0 & 1/a \end{bmatrix} \begin{bmatrix} v_2 \\ i_2 \end{bmatrix} \quad (\text{ABCD})$$

$$v_1 = a v_2 \quad a = \frac{N_1}{N_2}$$


$$i_1 = i_2 / a$$

$$\therefore \frac{v_1}{i_1} = \frac{a v_2}{i_2 / a} = a^2 \frac{v_2}{i_2}$$

$$a = \frac{N_1}{N_2}$$

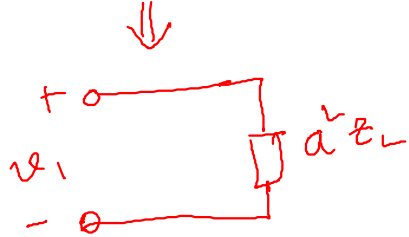

Cascade

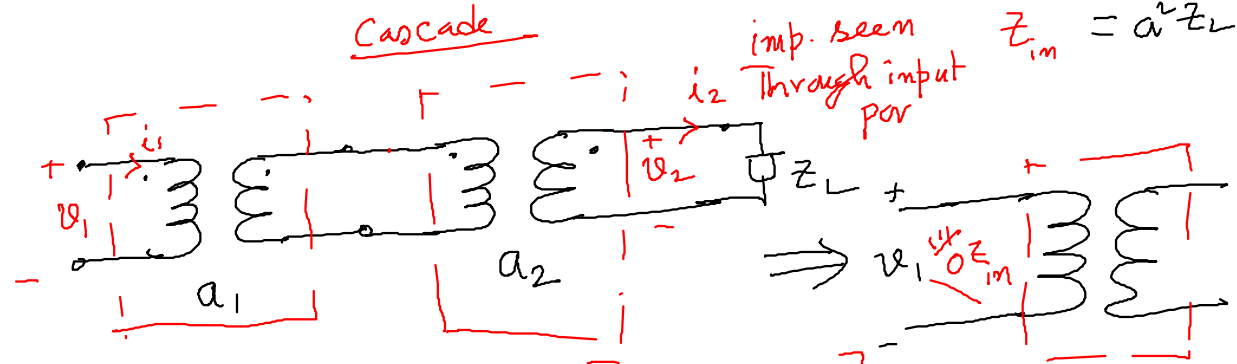


$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} a_1 & 0 \\ 0 & 1/a_1 \end{bmatrix} \begin{bmatrix} a_2 & 0 \\ 0 & 1/a_2 \end{bmatrix} \begin{bmatrix} v_2 \\ i_2 \end{bmatrix} = \begin{bmatrix} a_1 a_2 & 0 \\ 0 & 1/(a_1 a_2) \end{bmatrix} \begin{bmatrix} v_2 \\ i_2 \end{bmatrix}$$

$$a_{eq} = a_1 a_2$$

$$Z_{eq} = (a_1 a_2)^2 Z_L$$

Gyrator :-

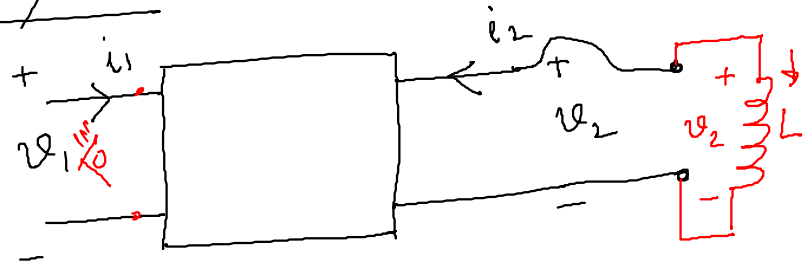

Suppose :-

$$v_1 = -k i_2$$

$$v_2 = k i_1$$

k = Gyrator constant
or Gyrator resistance

$$v = \frac{1}{C} \int i dt$$

$$-i_2 = \frac{1}{L} \int v_2 dt \quad \text{or} \quad i_2 = -\frac{1}{L} \int v_2 dt$$

$$v_1 = -k i_2$$

$$= (-k) \left(-\frac{1}{L}\right) \int v_2 dt = \frac{k}{L} \int v_2 dt$$

but $v_2 = k i_1$

$$v_1 = \frac{k}{L} \int k i_1 dt = \frac{k^2}{L} \int i_1 dt$$


$$v_1 = \frac{k^2}{L} \int i_1 dt = \left(\frac{1}{L/k^2}\right) \int i_1 dt$$



$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & -k \\ k & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$


4 Z parameters

A, B, C, D parameters

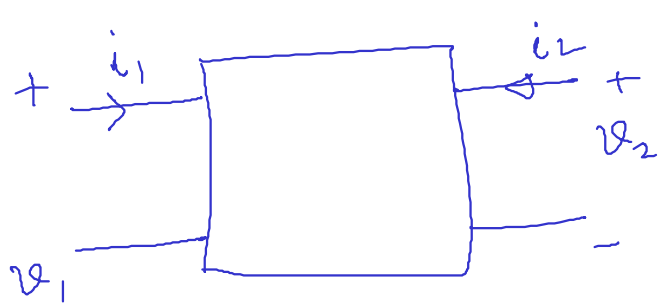

$$\begin{cases} V_1 = -K i_2 \\ V_2 = K i_1 \end{cases}$$

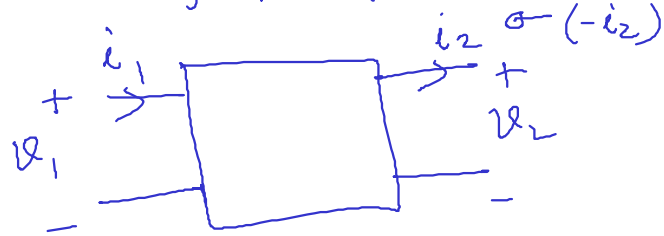representation of a two port gyrator:
for ABCD parameters




$$V_1 = K(-i_2) = K i_2$$

$$V_2 = K i_1 \Rightarrow i_1 = \frac{1}{K} V_2$$

$$\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} 0 & K \\ \frac{1}{K} & 0 \end{bmatrix} \begin{bmatrix} V_2 \\ i_2 \end{bmatrix}$$
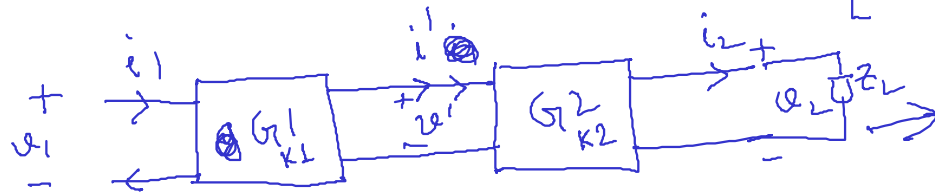
$$\begin{aligned} \begin{bmatrix} V_1 \\ i_1 \end{bmatrix} &= \begin{bmatrix} \frac{K_1}{K_2} & 0 \\ 0 & \frac{K_2}{K_1} \end{bmatrix} \begin{bmatrix} V_2 \\ i_2 \end{bmatrix} \\ &= \begin{bmatrix} a & 0 \\ 0 & \frac{1}{a} \end{bmatrix} \begin{bmatrix} V_2 \\ i_2 \end{bmatrix} \\ \text{where } a &= \frac{K_1}{K_2} \end{aligned}$$



$$Z_{eq} = \left(\frac{K_1}{K_2} \right)^2 Z_L$$

$$\begin{bmatrix} V' \\ i' \end{bmatrix} = \begin{bmatrix} 0 & K_2 \\ \frac{1}{K_2} & 0 \end{bmatrix} \begin{bmatrix} V_2 \\ i_2 \end{bmatrix} \quad \text{for } G_2$$

$$\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} 0 & K_1 \\ \frac{1}{K_1} & 0 \end{bmatrix} \begin{bmatrix} V' \\ i' \end{bmatrix} = \begin{bmatrix} 0 & K_1 \\ \frac{1}{K_1} & 0 \end{bmatrix} \begin{bmatrix} 0 & K_2 \\ \frac{1}{K_2} & 0 \end{bmatrix} \begin{bmatrix} V_2 \\ i_2 \end{bmatrix}$$