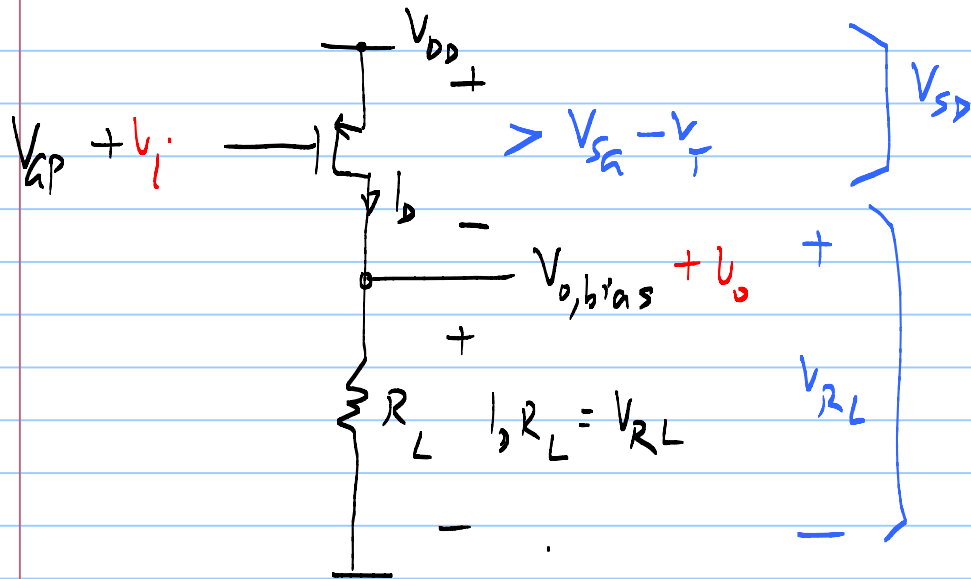


$$V_{DD} = V_{SD} + V_{RL} \geq \underbrace{V_{SG} - V_T}_{\geq 200mV} + V_{RL}$$

pMOS Common source amplifier



$$\text{Gain magnitude} = g_m R_L = \frac{2 \cdot I_D}{V_{SG} - V_T}$$

Increase g_m : Increasing I_D , W/L

Increase R_L :

$$g_m = \frac{2 I_D}{\underbrace{V_{SG} - V_T}_{\text{overdrive voltage}}}$$

Operating point

$$V_{SG} = V_{DD} - V_{Gp}$$

$$V_{o,bias} = I_D \cdot R_L$$

$$I_D = \frac{\mu_p C_{ox}}{2} \frac{W}{L} \cdot (V_{SG} - V_T)^2$$

Signal:

$$\underline{v_o = -g_m R_L \cdot v_i}$$

Gain magnitude :

$$\frac{2 \cdot V_{aL}}{V_{SA} - V_T}$$

$$\frac{2 \cdot 1V}{200mV}$$

$$I_D = \frac{\mu_{p6x}}{2} \cdot \frac{W}{L} (V_{SA} - V_T)^2$$

Decreasing $V_{SA} - V_T$:

Square law model valid only if

$$\underbrace{V_{SA} - V_T}_{\sim 200mV \text{ or more}} \gg \frac{kT}{q} \sim 25mV @ 300K$$

$\sim 200mV$ or more

$V_{SA} - V_T \geq 200mV$, for operation in saturation region


Increase V_{aL} : \Rightarrow We have to increase V_{DD}

$$V_{DD} > 10.2V$$


$I_{D0} =$

$$\frac{2 \cdot 10V}{200mV}$$

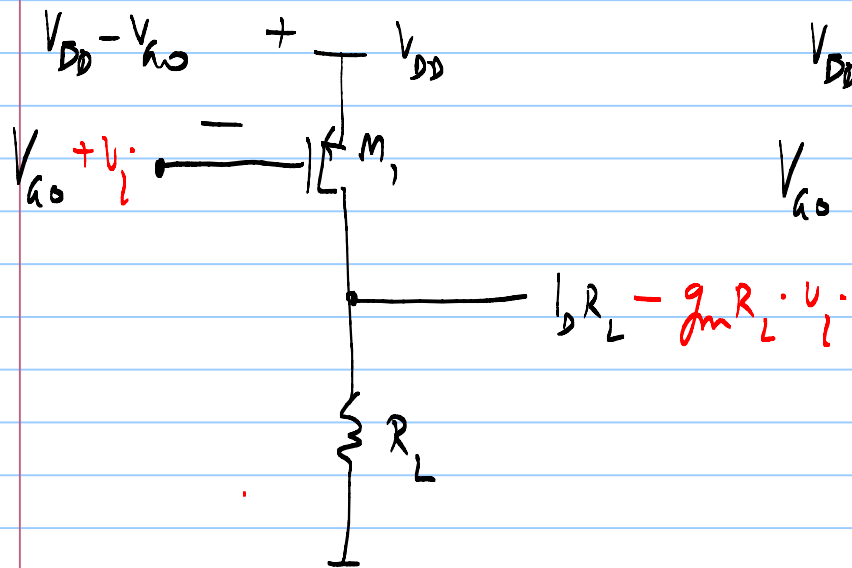
Common source amplifier with a large gain




Total picture





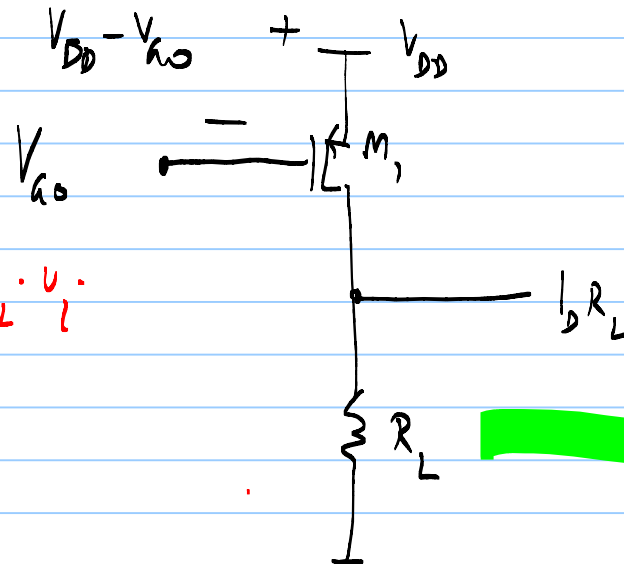


operating point

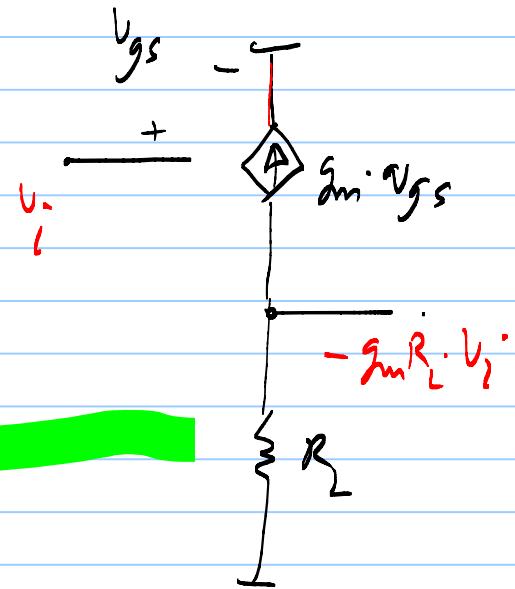


Incremental
signal picture

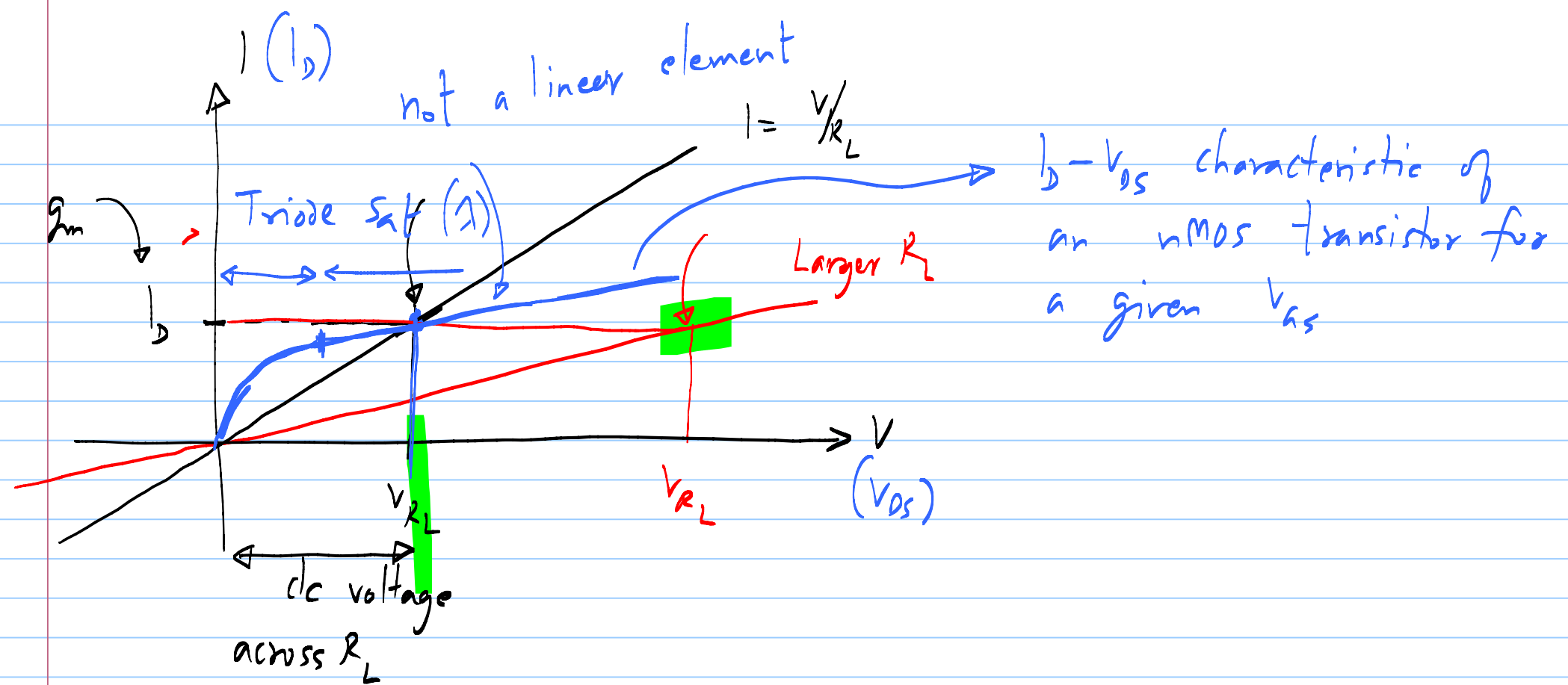

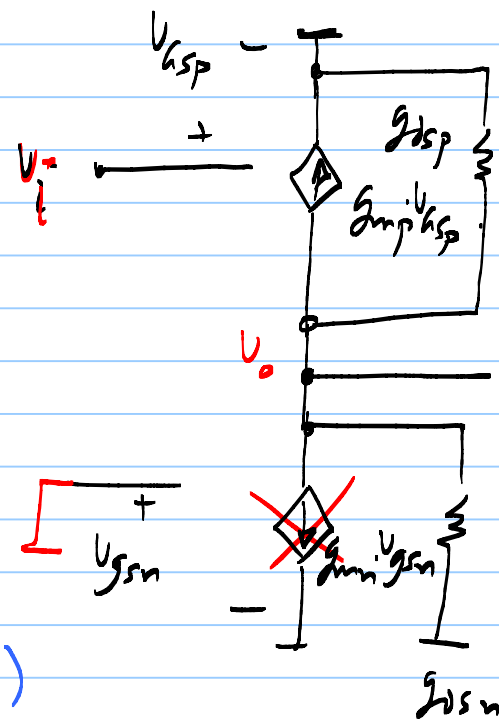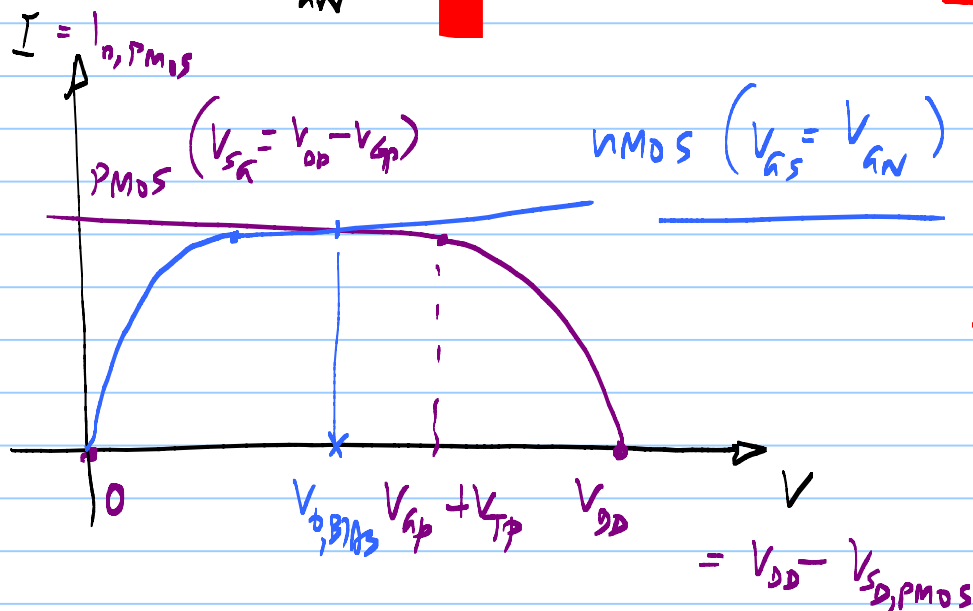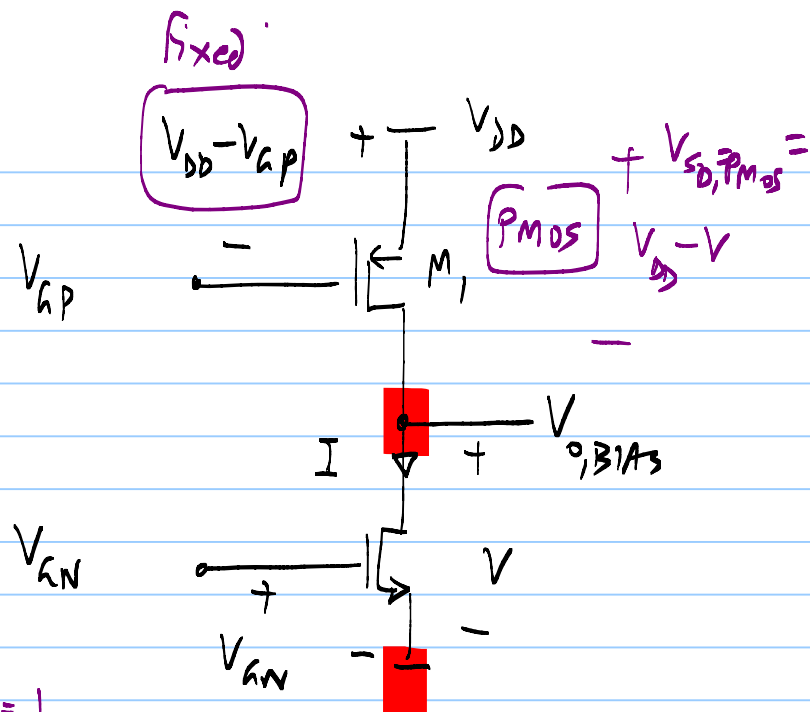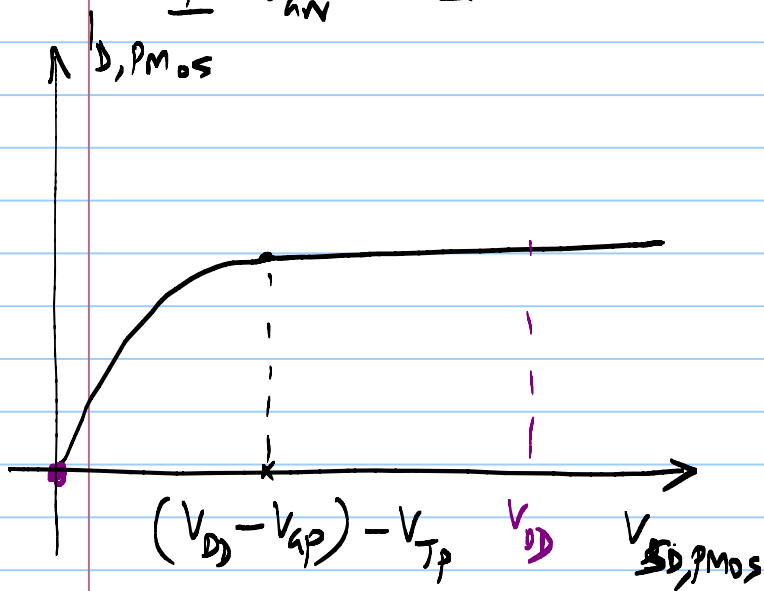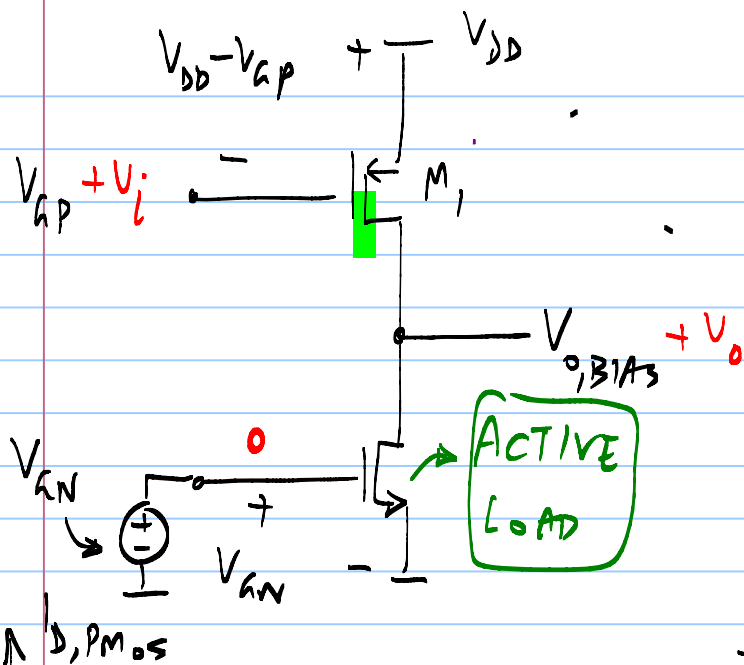




$$\frac{V_O}{V_i} = - \frac{g_{mp}}{g_{sp} + g_{sn}}$$

PMOS CS amplifier with nMOS active Load

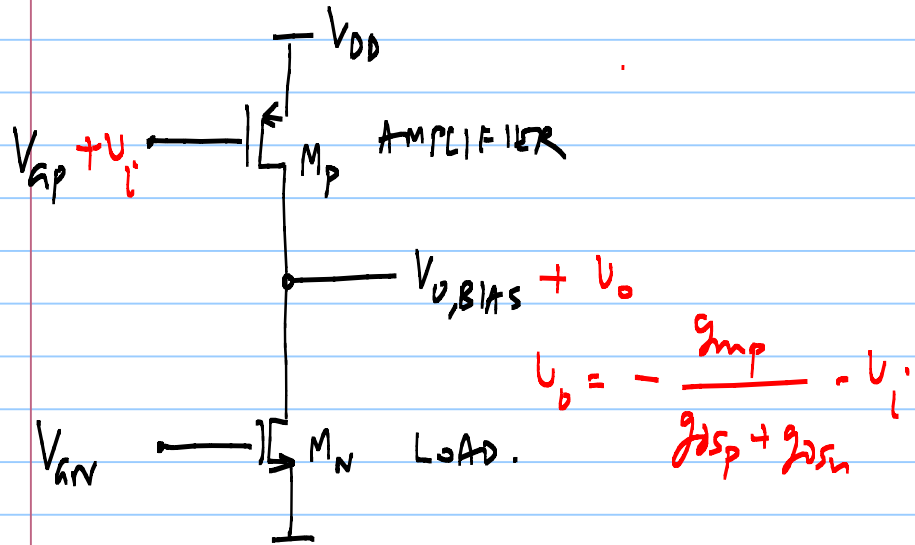


nMOS CS amplifier with PMOS active load

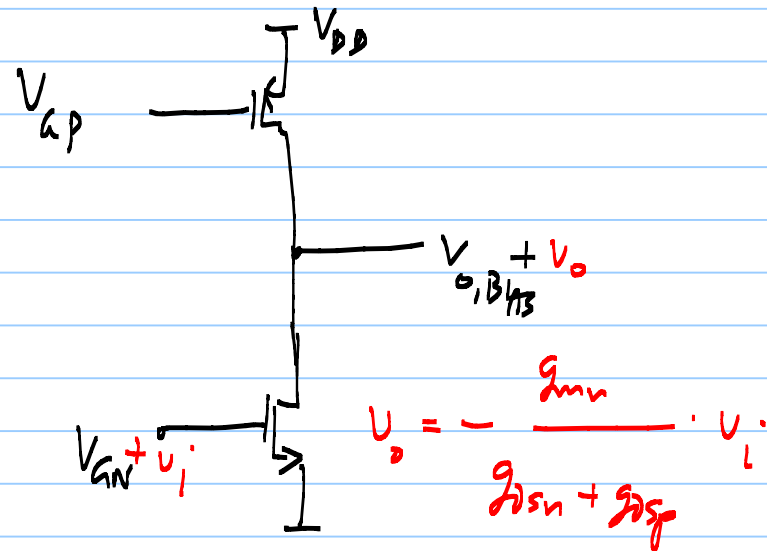

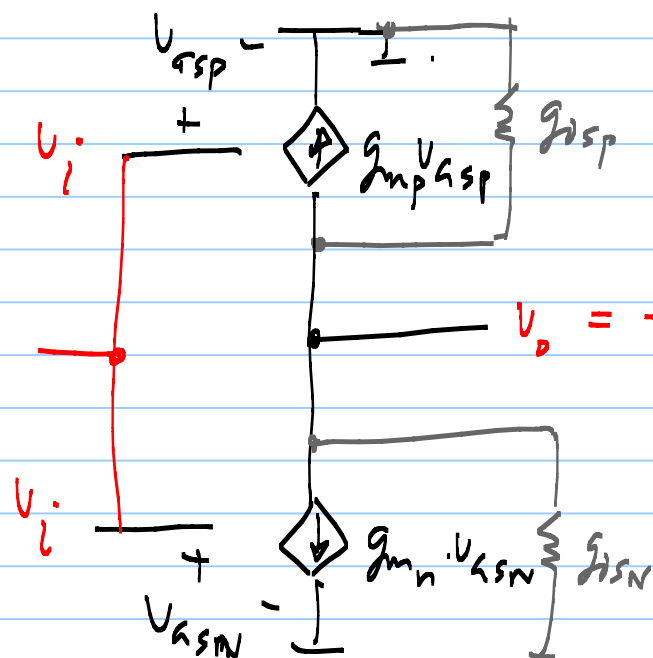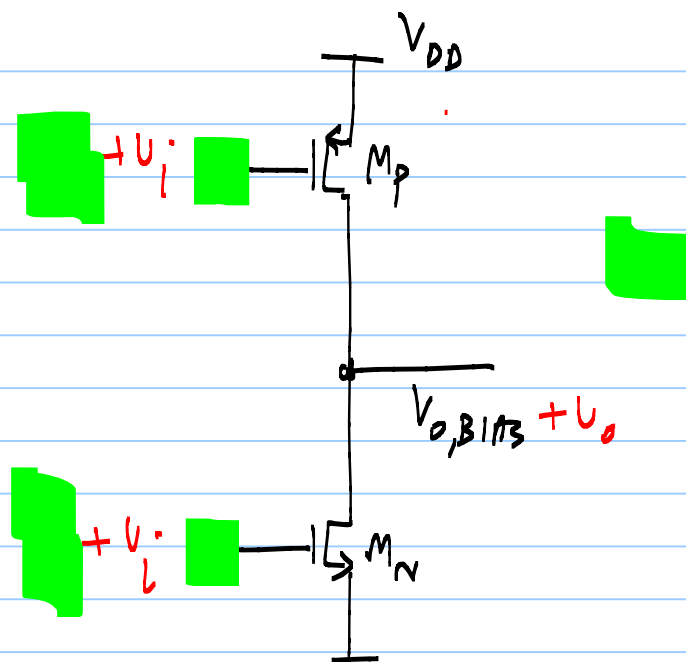
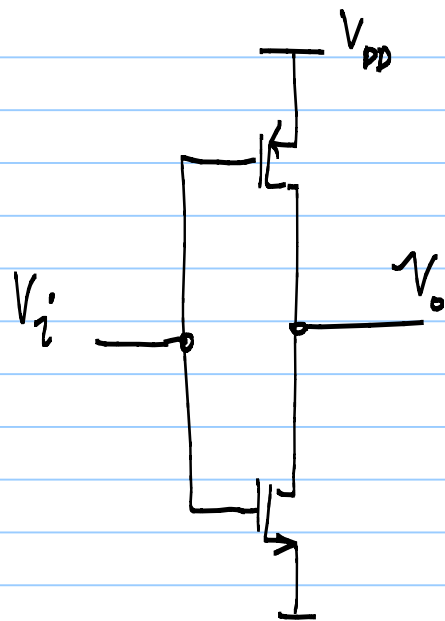
$$V_o = - \frac{g_{m_n} + g_{m_p}}{g_{sn} + g_{osp}} \cdot V_i$$




CMOS inverter

$V_{thp} = V_{thn}$.

PMOS CS amplifier

w/ nmos active load

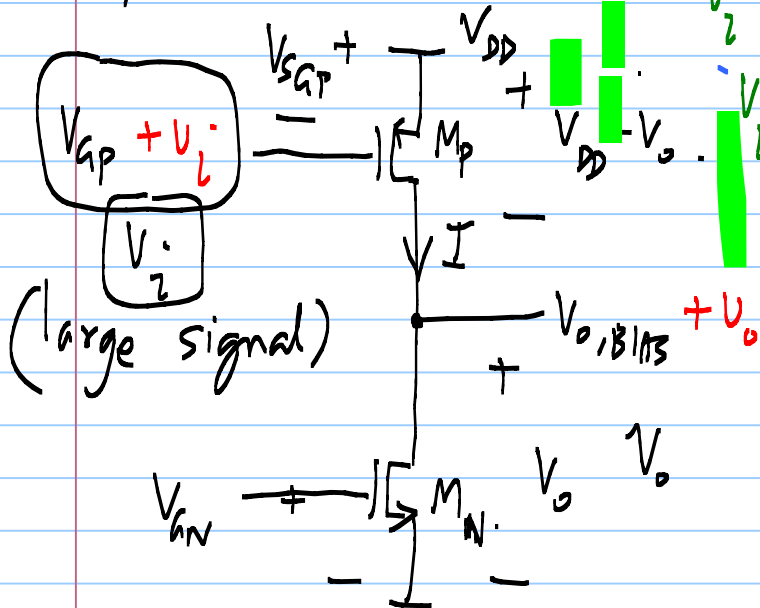

V_D vs. V_L

PMDs:


$$V_{SGP} = V_{DD} - V_i$$

$$V_{SDP} = V_{DD} - V_D$$


nMOS:

$$V_{GSN} = V_{GN}$$

$$V_{DSN} = V_o$$

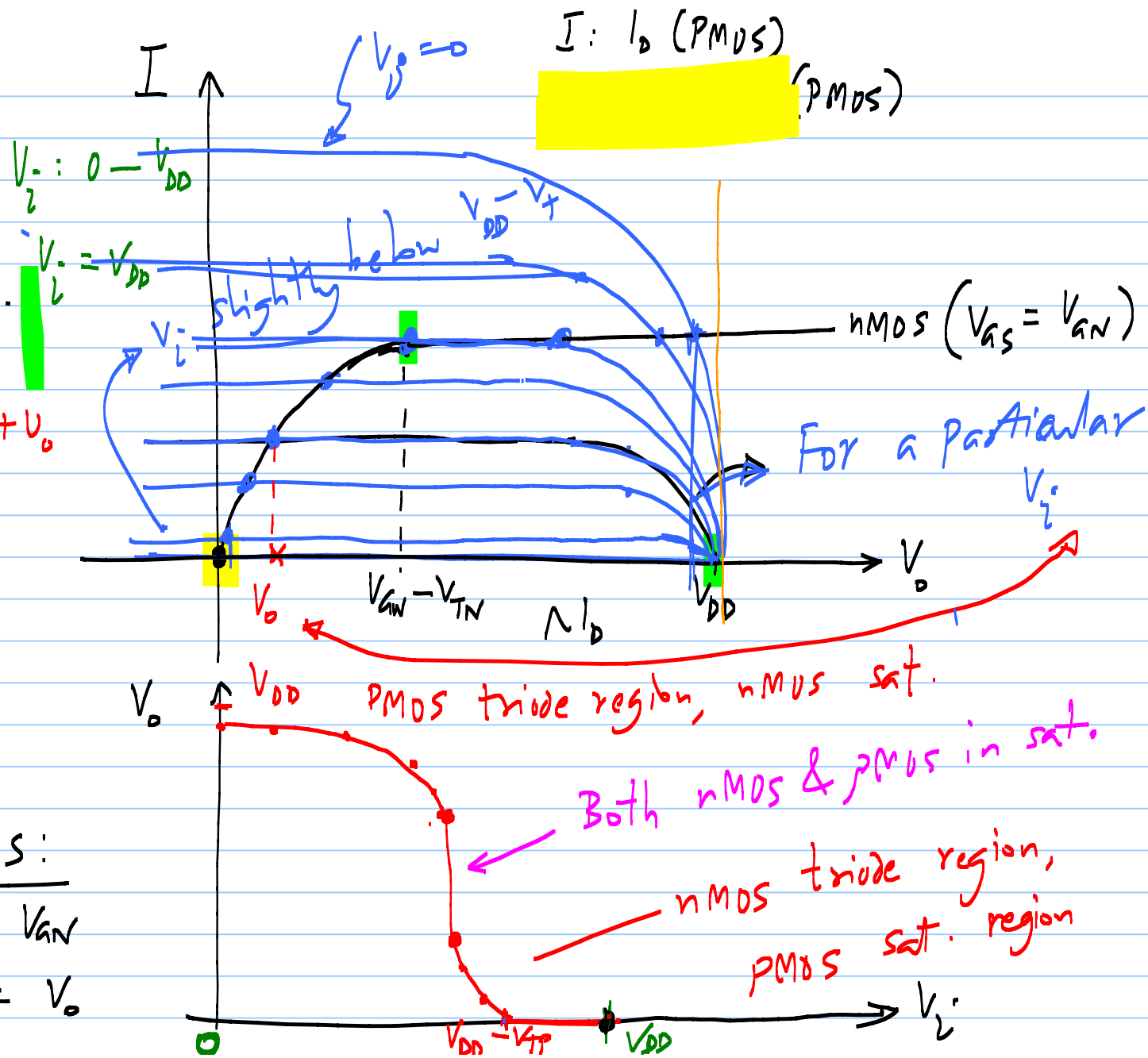

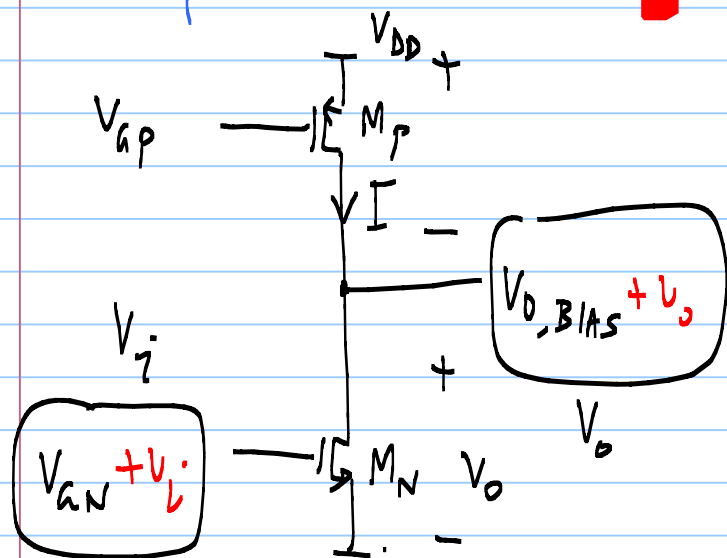
nMOS CS amplifier loaded by a pMOS active load




V_O vs. V_{G_i}

pMOS: $V_{S_Gp} = V_{DD} - V_{Gp}$; $V_{D_Gp} = V_O$

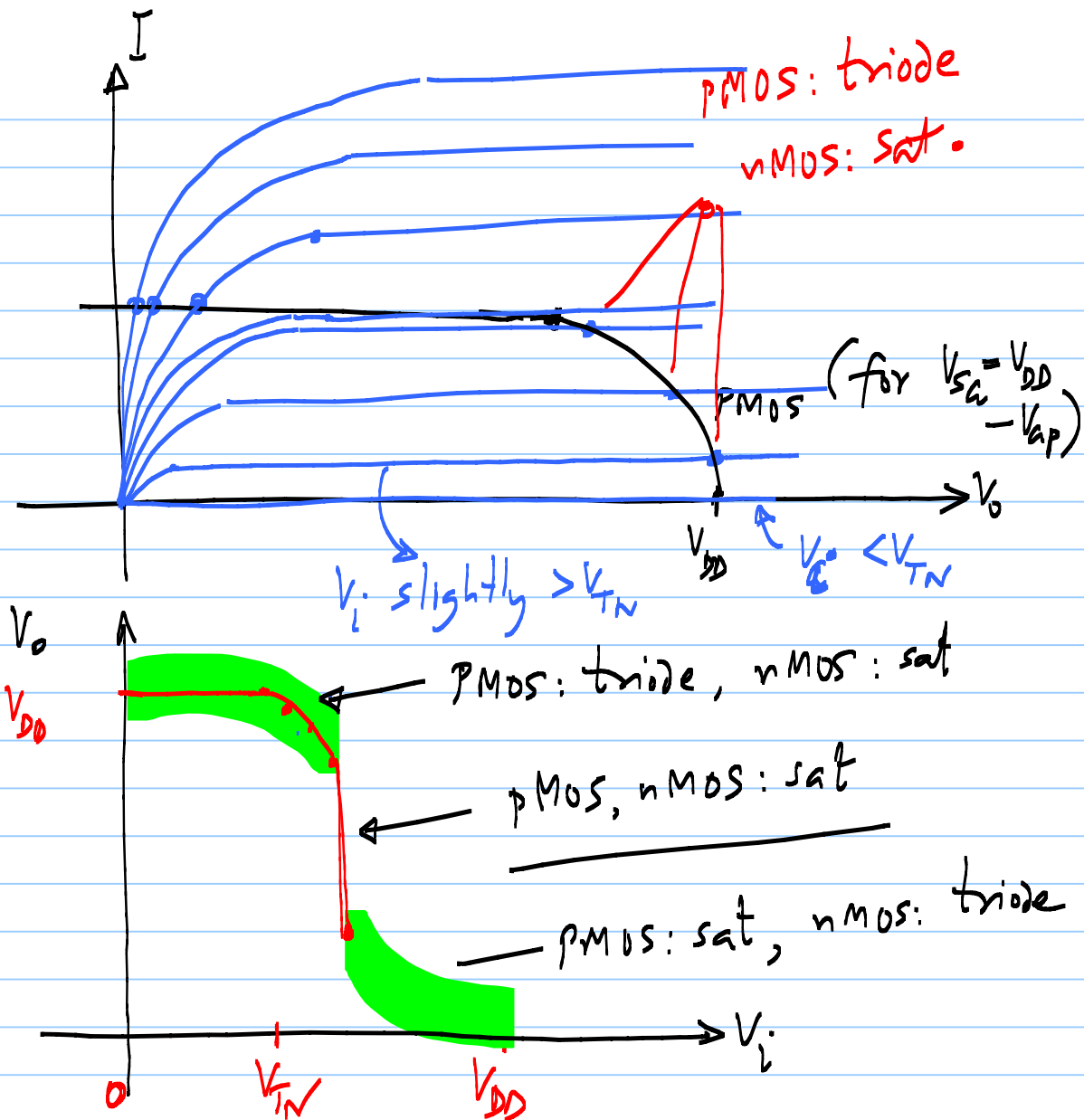nMOS: $V_{G_SN} = V_{G_i}$; $V_{D_SN} = V_O$



CMOS inverter

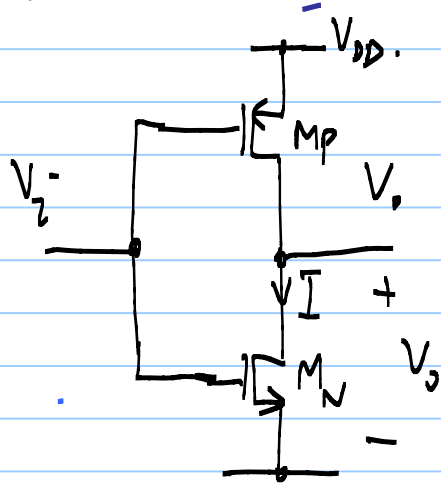



$$V_{DD} - V_{TP} \leq V_i \leq V_{DD}$$

PMOS: $V_{SG} = V_{DD} - V_i$

$V_{SD} = V_{DD} - V_o$


nMOS: $V_{GS} = V_i$

$V_{DS} = V_o$

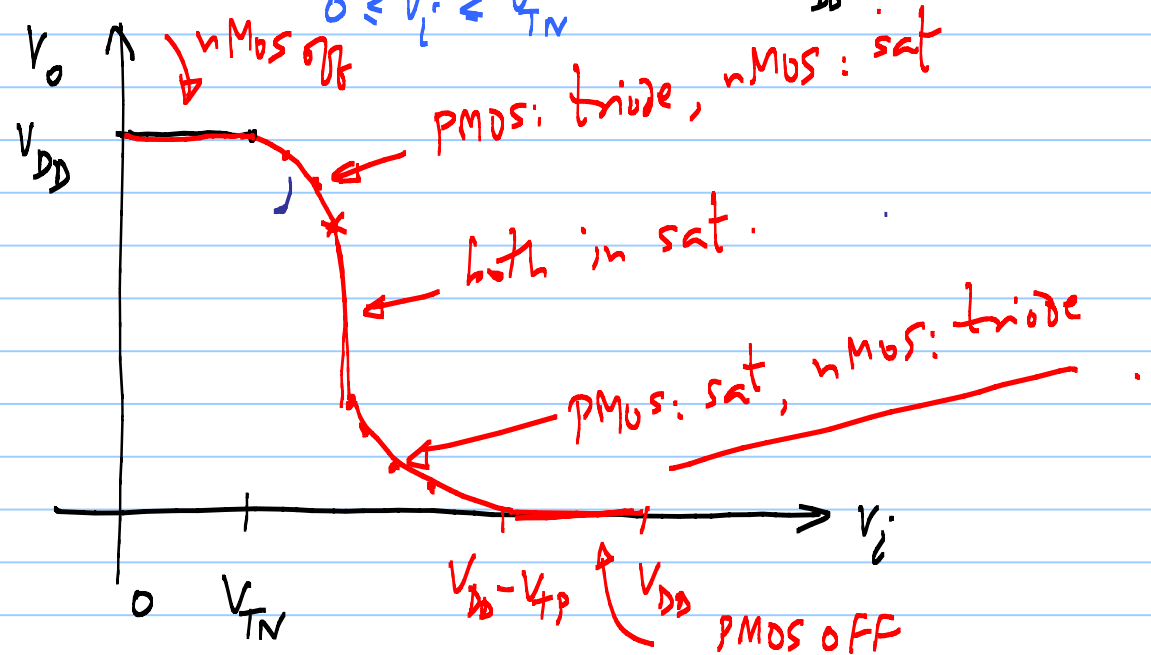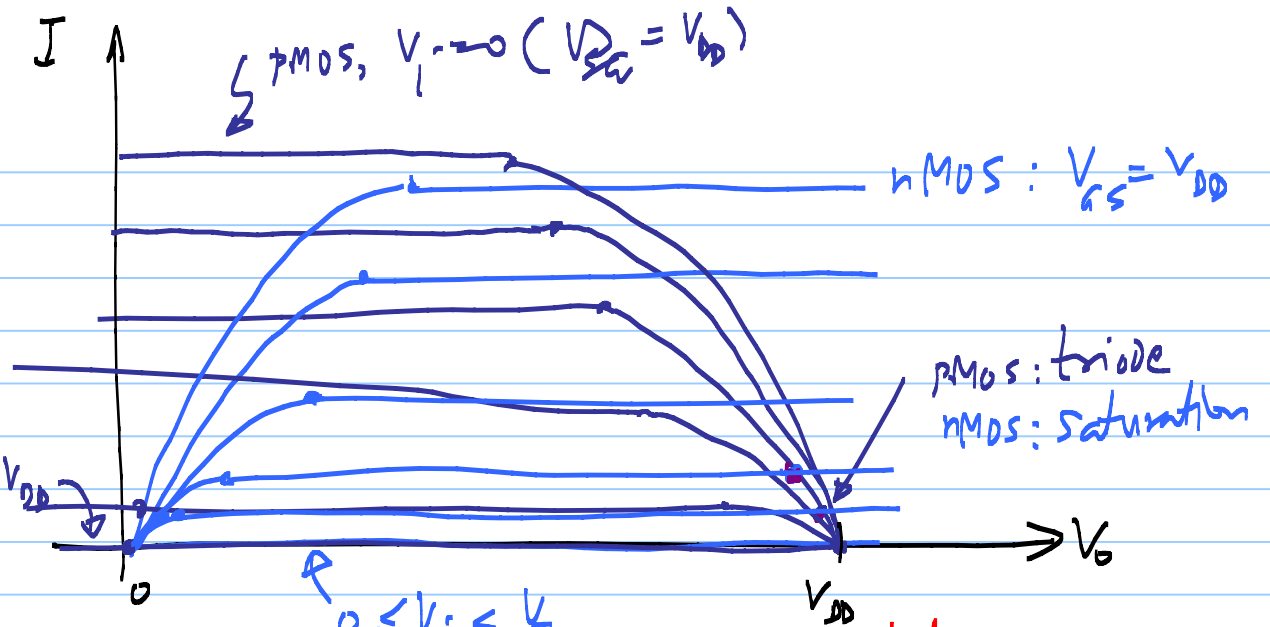

CS amplifiers with active loads: Digital inverters


PMOS CS w/ nMOS Load

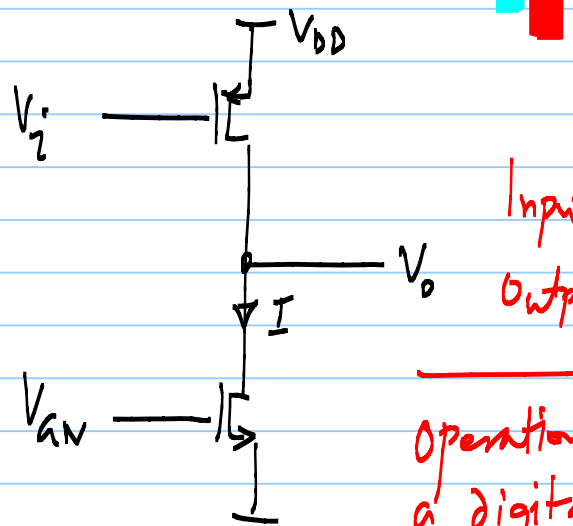



Input: $L_0 (0)$
Output: HI (1)

Operation as
a digital
inverter
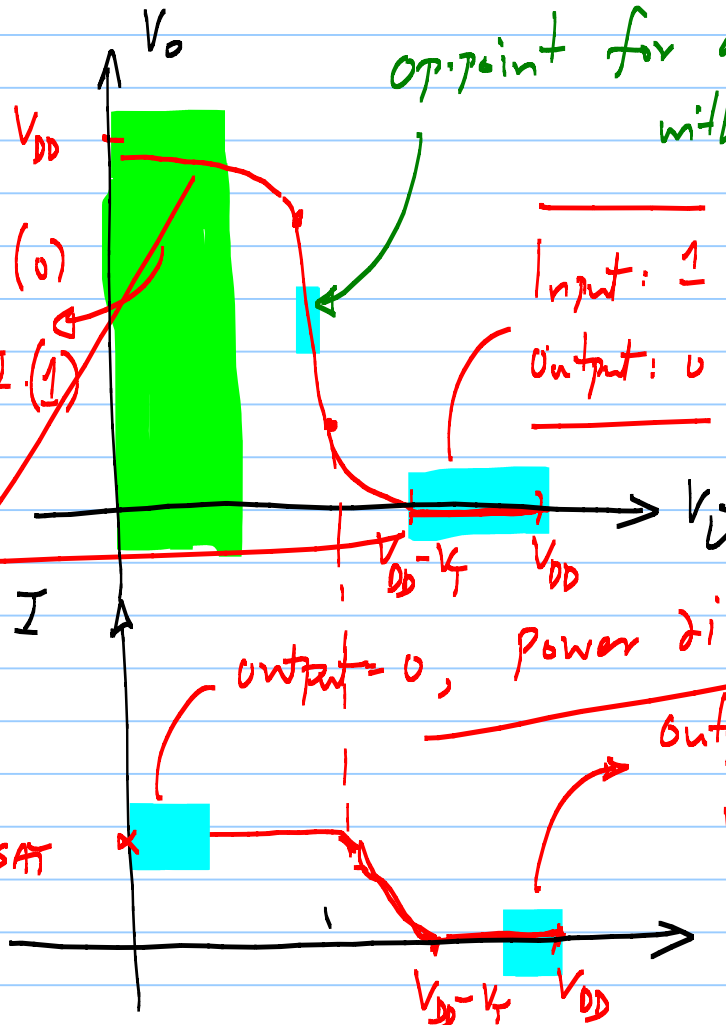
$$\frac{\mu_n C_{ox}}{2} \frac{W_N}{L_N} (V_{GN} - V_{TN})^2 = I_{SAT}$$




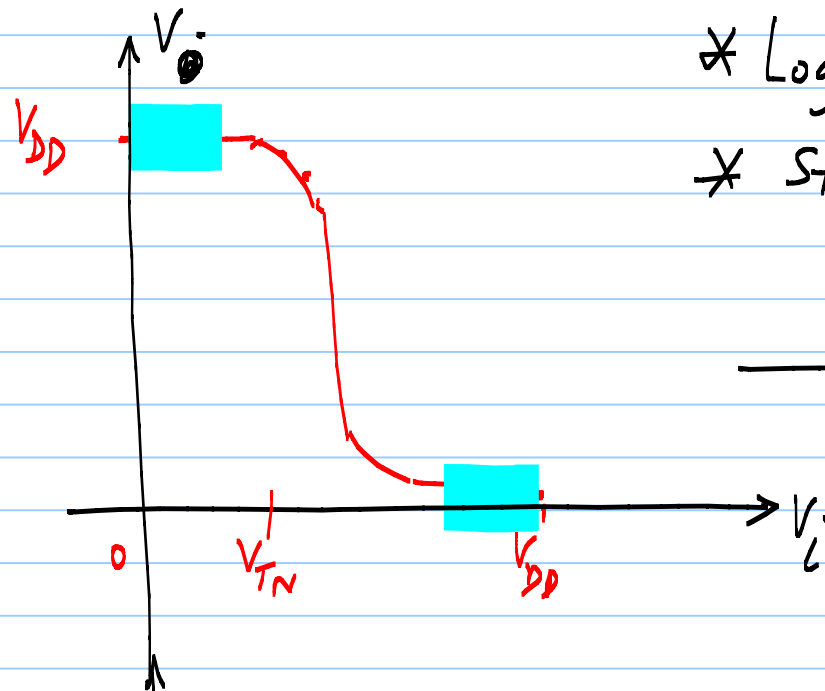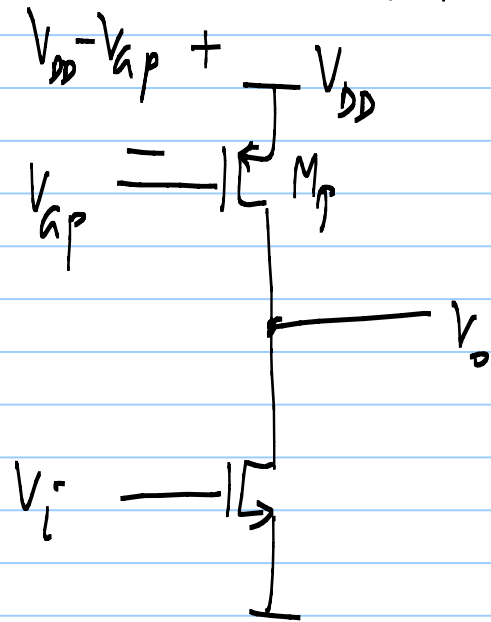\rightarrow faster than pMOS ($\mu_n > \mu_p$) nMOS logic
nMOS CS amplifier w/ pMOS load





* Logical inverter
 * Static power dissipation
 (output: LO(0))

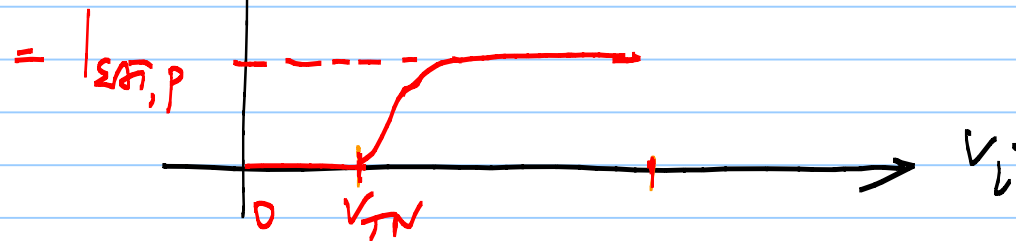
$$\frac{\mu_p C_{ox}}{2} \frac{W_p}{L_p} (V_{DD} - V_{GP} - V_{TP})^2 = I_{SAT,p}$$



CMOS inverter

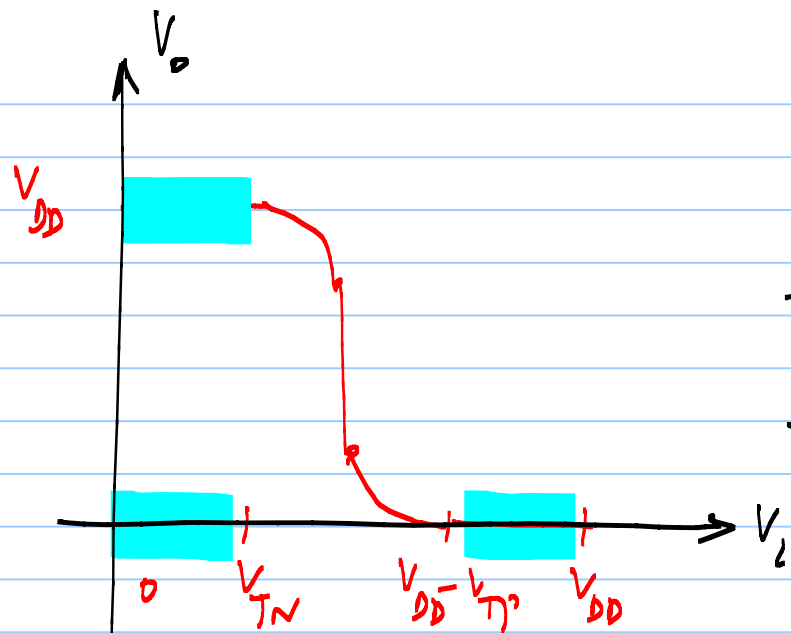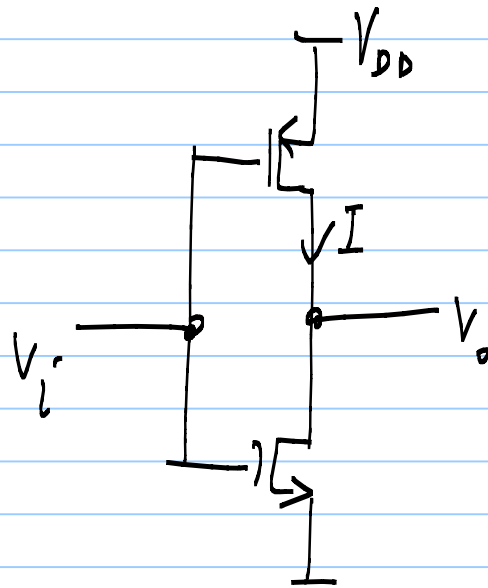


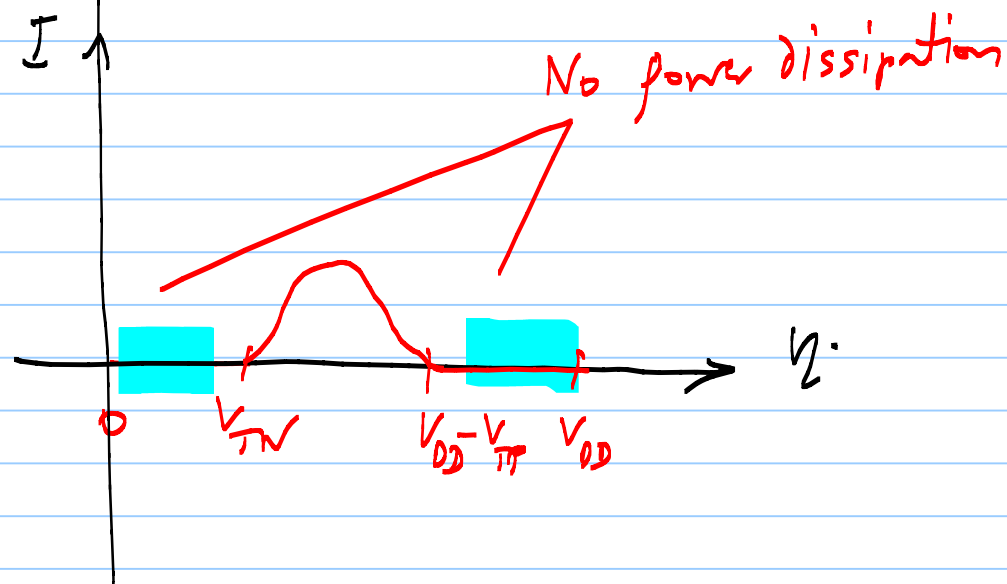- * Logical inverter
- * No static power dissipation




Biasing a CMOS inverter in the high gain region

9/24/2018

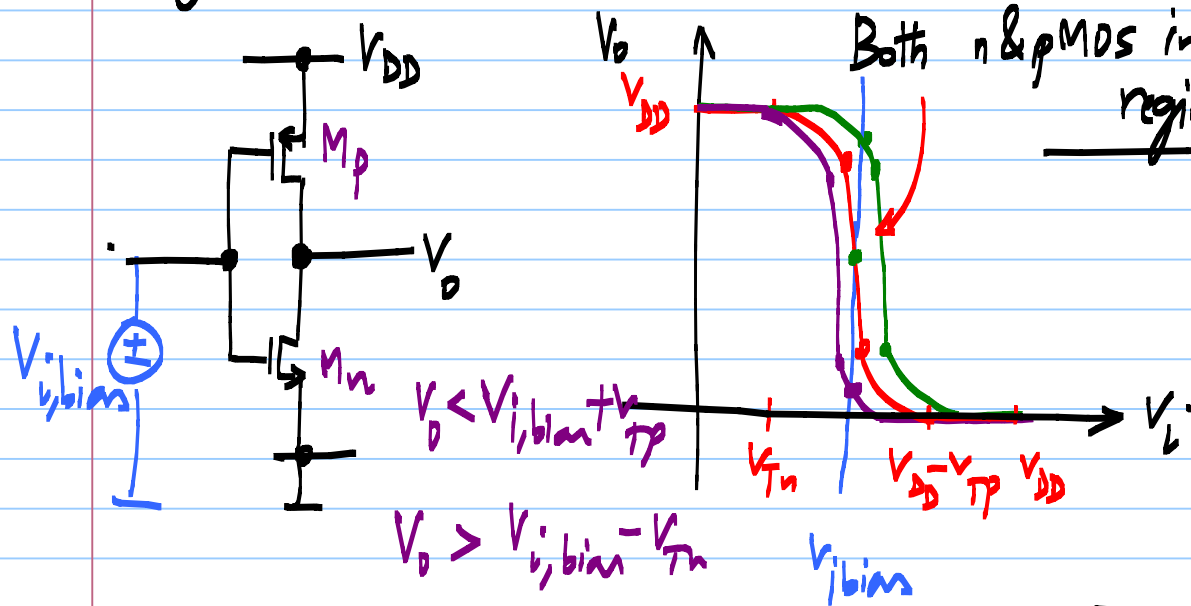


Both n & pMOS in saturation region
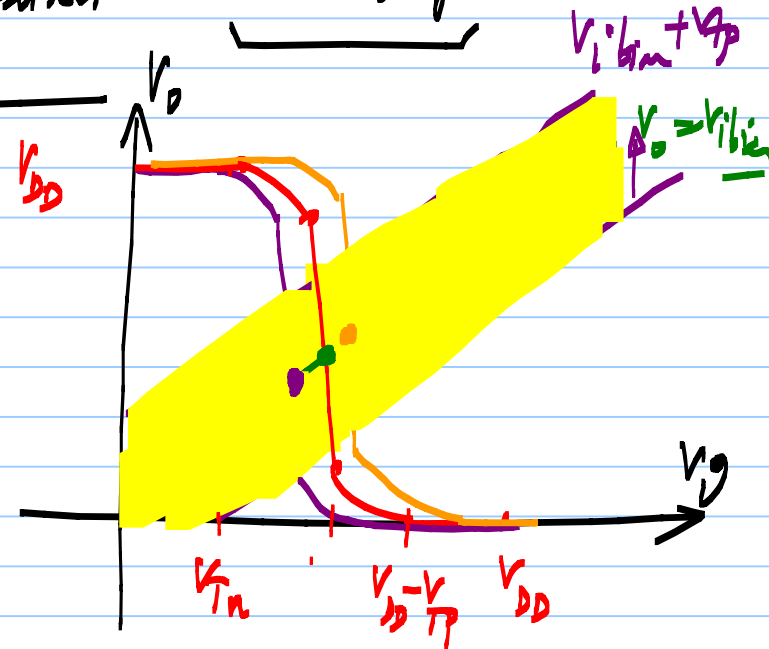
$$\frac{I_{n,sat} + I_{p,sat}}{I_{n,sat} + I_{p,sat}}$$



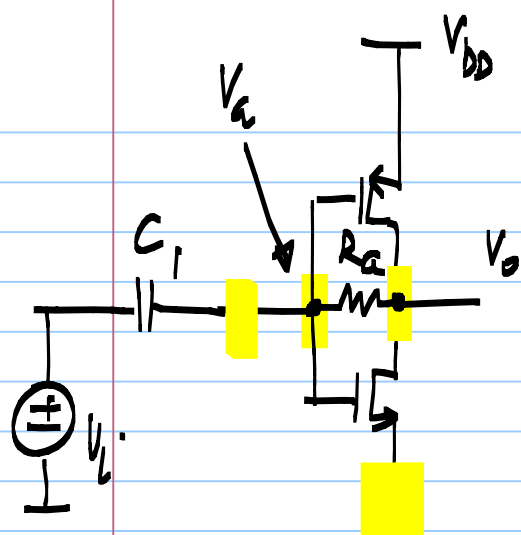
$$\begin{aligned} M_n \text{ saturation: } & V_{i,bias} - V_o < V_{TN} \quad [V_{TN} > 0] \\ M_p \text{ saturation: } & V_o - V_{i,bias} < V_{TP} \quad [V_{TP} > 0] \end{aligned}$$



R_D must be large
 C_1 must be large

@ dc, $V_G = V_o$

@ ac, $V_G = v_i$

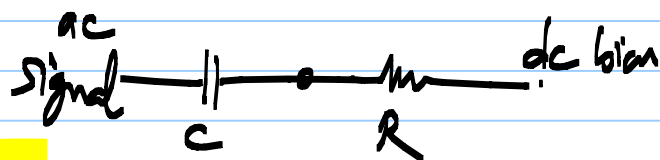


For dc bias : $V_{i,bias}$

Incremental signals, v_i , the input voltage



R_D is large enough to be treated as an open circuit

Incremental picture

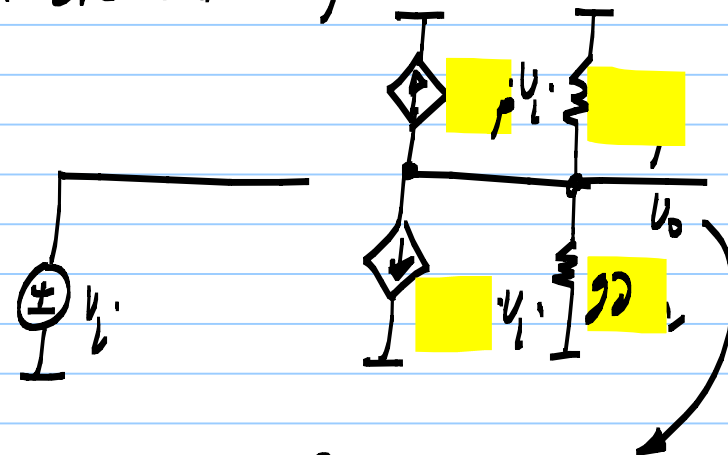

$$\frac{v_o}{v_i} = - \frac{g_{mn} + g_{mp}}{g_{kn} + g_{kp}}$$

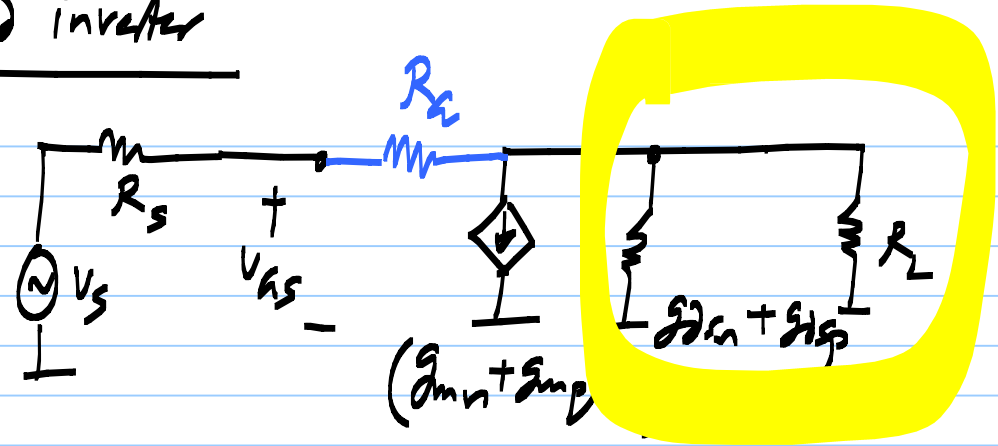
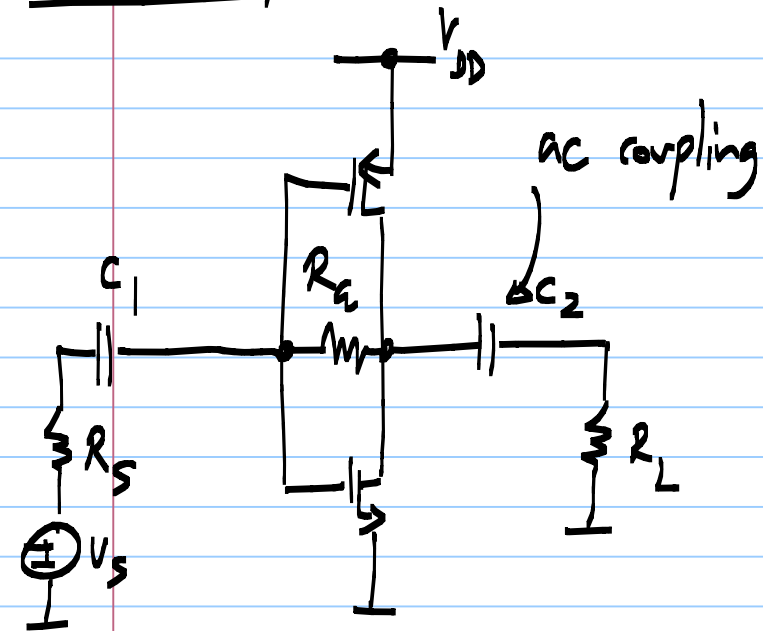
CS amplifier using a self-biased inverter





$$R_d \gg g_{m_n} R_L R_s \text{ OR } R_L$$

$$R_d \gg \frac{g_{m_n} R_s}{[g_{s_n} + g_{s_p} + g_L]} ; R_d \gg \frac{1}{g_{s_n} + g_{s_p} + g_L}$$

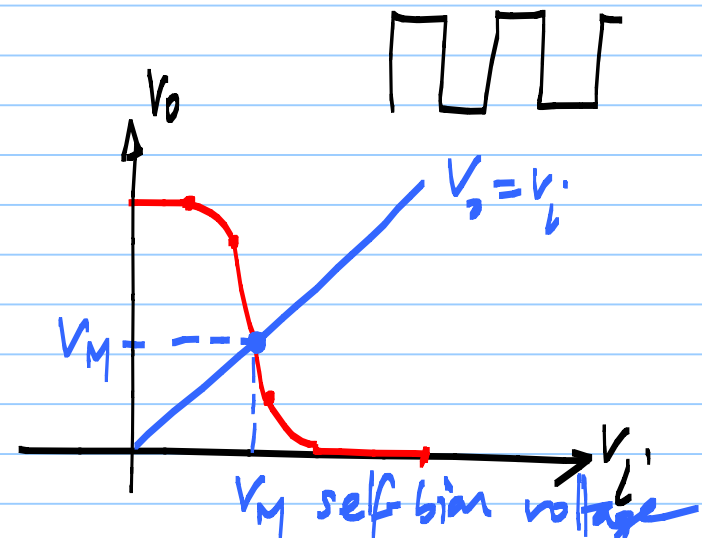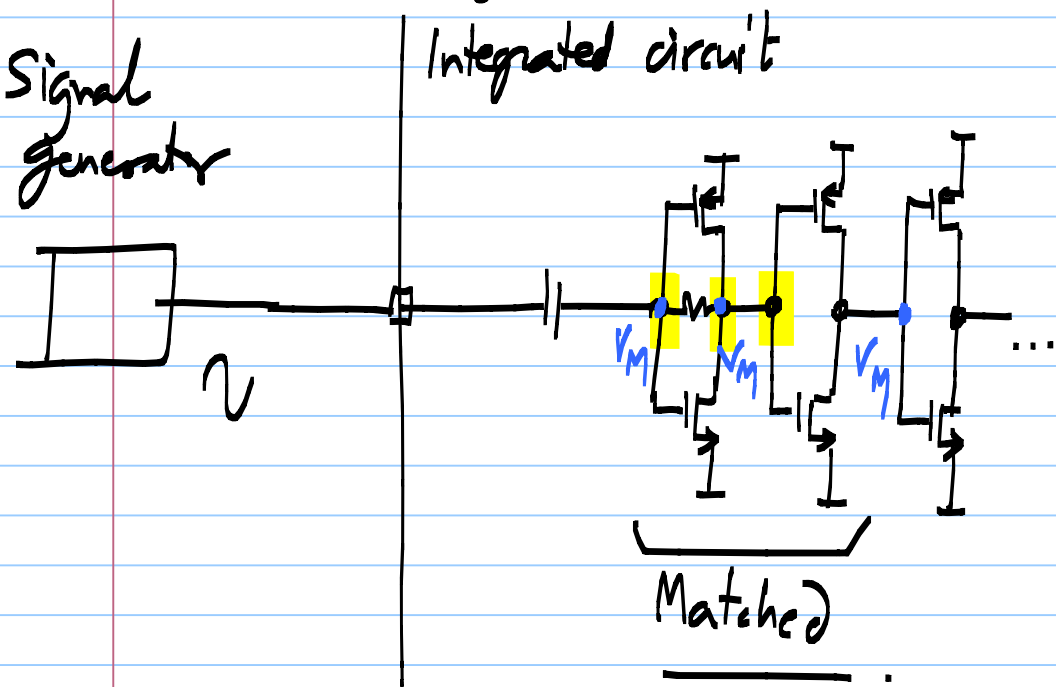Application of CS amplifier using a self-biased inverter



Self-biased inverter

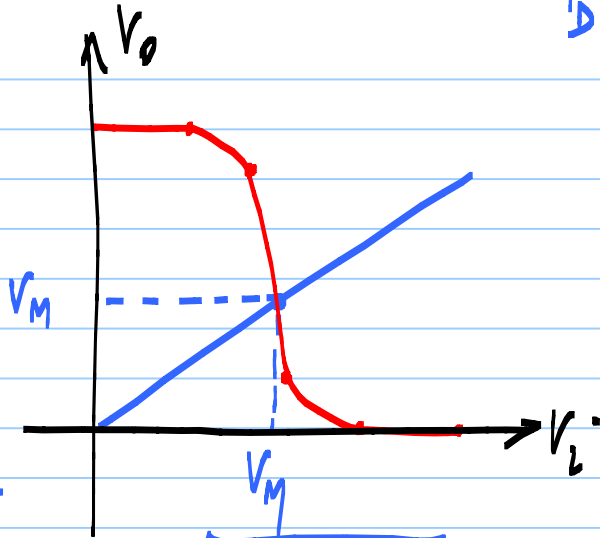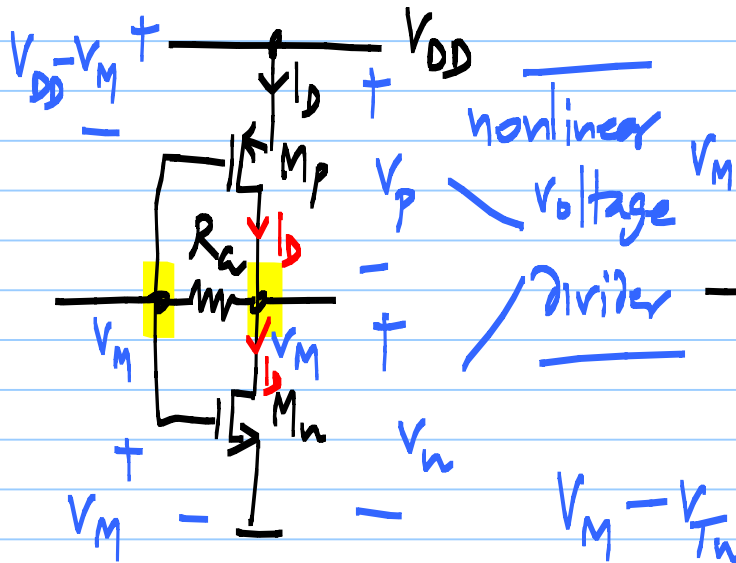

$$V_M - V_{Tn} = \underbrace{\sqrt{\frac{\mu_p}{\mu_n} \cdot \frac{W_p/L_p}{W_n/L_n}}}_{\alpha} \cdot (V_{DD} - V_M - V_{Tp}) \quad \left[\frac{V_{DD}}{2} \right] \quad \alpha = 1$$

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W_n}{L_n} (V_{in} - V_{TN})^2$$

$$= \frac{\mu_{p\text{box}}}{2} \cdot \frac{W_p}{L_p} (V_{DD} - V_M - V_{TP})^2$$

$$V_M = \frac{\alpha \cdot V_{DD} + V_{Tn} - \alpha V_{Tp}}{1 + \alpha}$$

$$\alpha = 1$$

$$\left[\frac{V_{DD}}{2} \right]$$

$$I_D = \frac{\mu_n C_{ox}}{2} \cdot \frac{W_n}{L_n} \left(\frac{\alpha V_{DD} + V_{Tn} - \alpha V_{Tp}}{1 + \alpha} - V_{Tn} \right)^2$$

$$= \frac{\mu_n C_{ox}}{2} \cdot \frac{W_n}{L_n} \left[\frac{\alpha (V_{DD} - V_{Tp} - V_{Tn})}{1 + \alpha} \right]^2$$

$$= \frac{\mu_n C_{ox}}{2} \cdot \frac{W_n}{L_n} \left(\frac{\alpha}{1 + \alpha} \right)^2 \cdot (V_{DD} - V_{Tp} - V_{Tn})^2$$

$$\alpha = \sqrt{\frac{\mu_p \cdot W_p / L_p}{\mu_n \cdot W_n / L_n}}$$

Current drawn from the supply is strongly dependent on V_{DD}

Calculate g_{mn} , g_{mp}

→ Increase with V_{DD}

