


Amplifier characteristics

Note Title

6/9/2015

Two port (input & output) network N

is passive

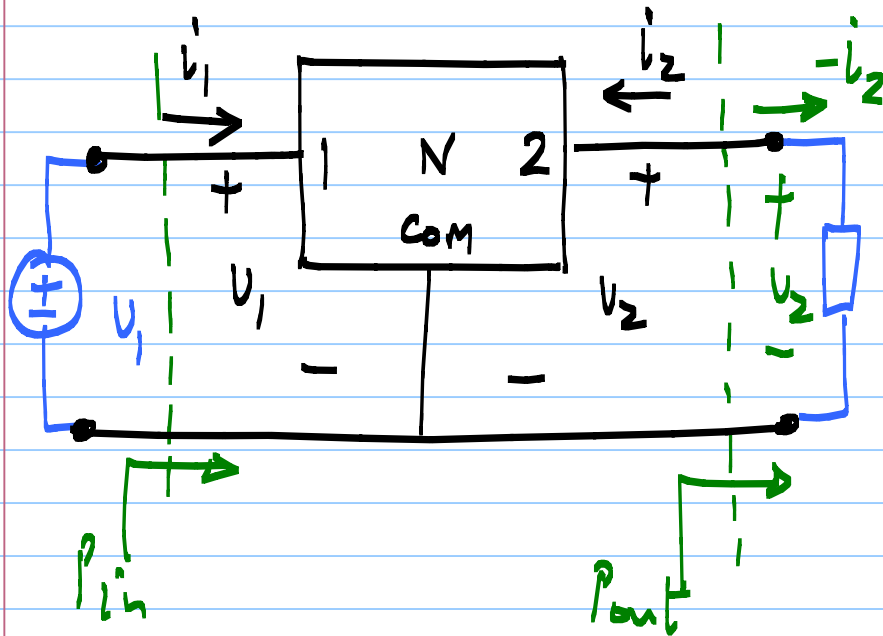

$$v_1 i_1 + v_2 i_2 \geq 0$$


Amplifier: $P_{out} > P_{in}$

$$P_{in} = v_1 \cdot i_1 ; P_{out} = -v_2 i_2$$

$$-v_2 i_2 \leq v_1 i_1 ; \underline{P_{out} \leq P_{in}}$$

N: Linear two port network

Passive

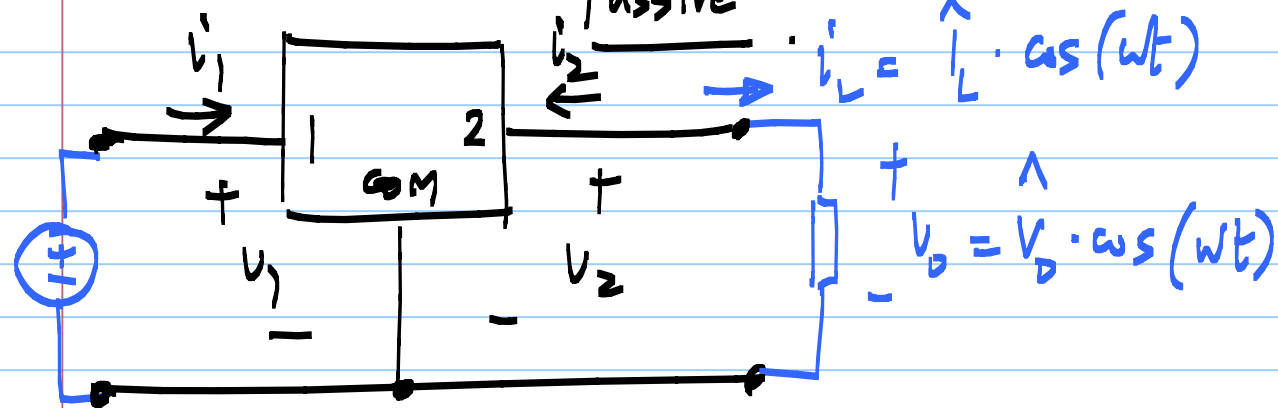


$$i_L = \hat{I}_L \cdot \cos(\omega t)$$

$$v_D = \hat{V}_D \cdot \cos(\omega t)$$

$$v_1 = \hat{V}_1 \cdot \cos \omega t$$


$$-v_2 i_2 \leq v_1 i_1$$

Linear network

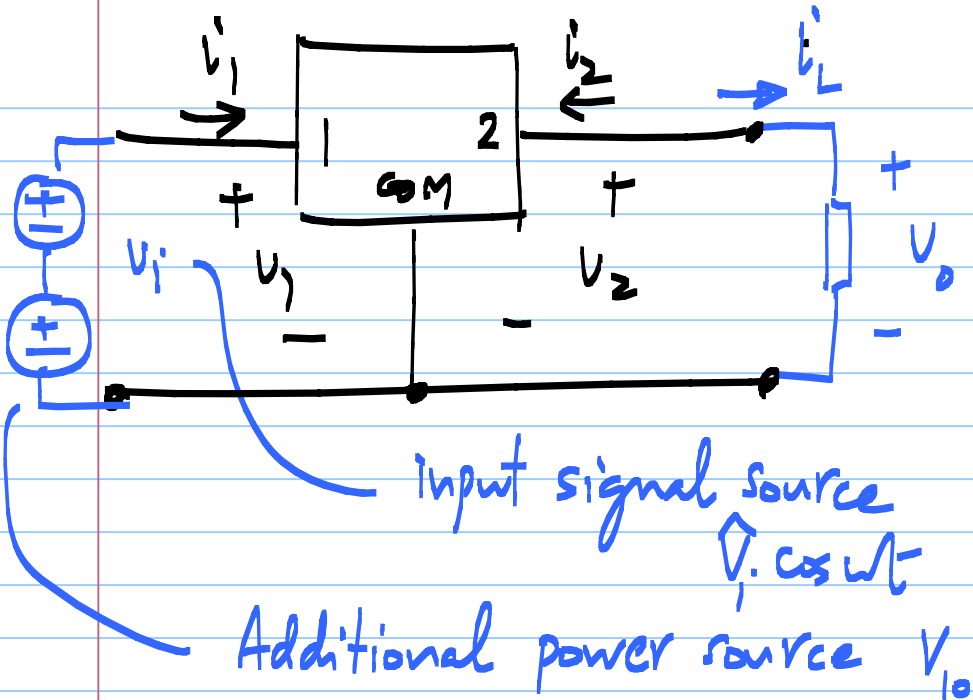

Component due to V_1
Component due to V_{10}

Linear network


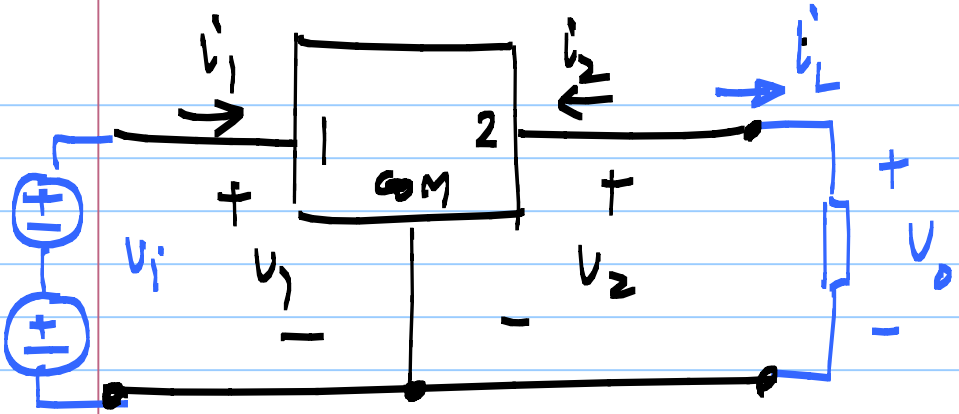


$$-V_2 i_2 \leq V_1 i_1$$

$$P_{o, \text{signal}} \leq P_{i, \text{signal}}$$

$$\hat{V}_i \cos(\omega t)$$

Linear network

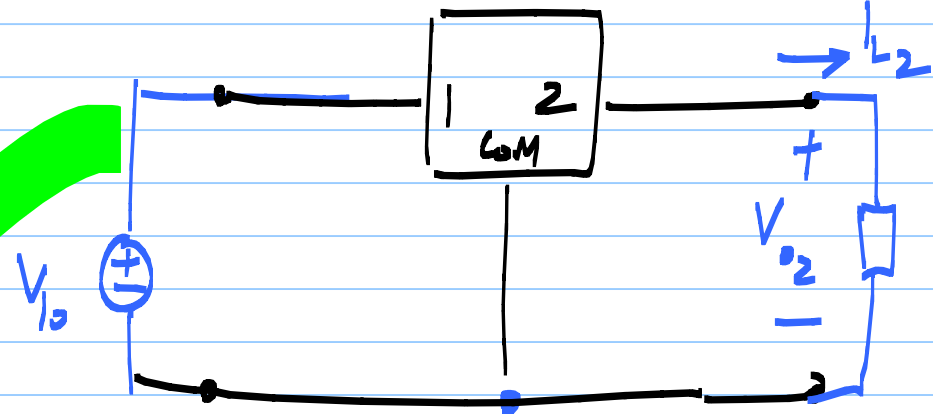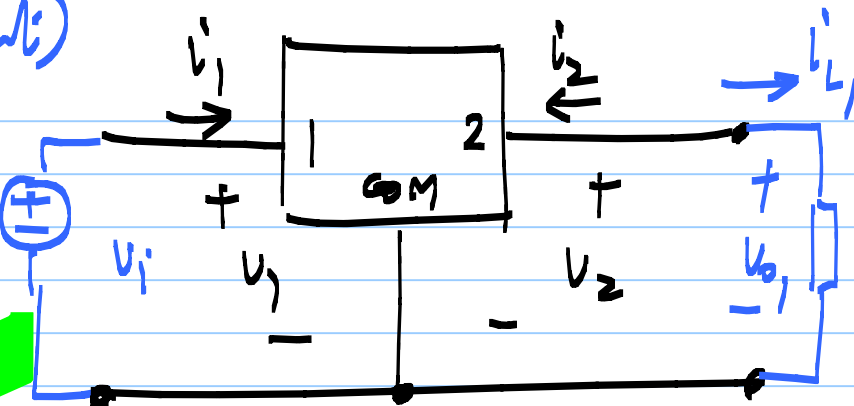


* Passive devices $\Rightarrow P_o \leq P_{in} \Rightarrow$ No power amplification
if signal source is the
only power source

* Additional power source \Rightarrow Can convert some power from
this into signal component

\Rightarrow Linear, passive device $\rightarrow P_{o, \text{signal}} \leq P_{in, \text{signal}}$
output due to the signal source independent of the
additional source

We need nonlinear devices!

Analysis of nonlinear circuits

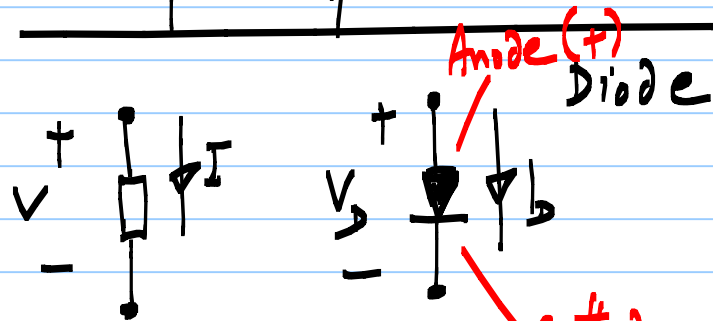

$$I = f(V) \quad I_D = I_s \left(\exp\left(\frac{V_D}{V_t}\right) - 1 \right)$$

$$I = \frac{V}{R}$$

I_s : saturation current

$$I_s = 10^{-15} \text{ A}$$

$$V_t = \frac{kT}{q}$$

k : Boltzmann's constant

T : Absolute temperature


q : Electron charge

$\frac{kT}{q}$: Thermal voltage

room temp. $V_t =$

$$\frac{kT}{q} = 25.9 \text{ mV}$$

$$\approx 25 \text{ mV}$$

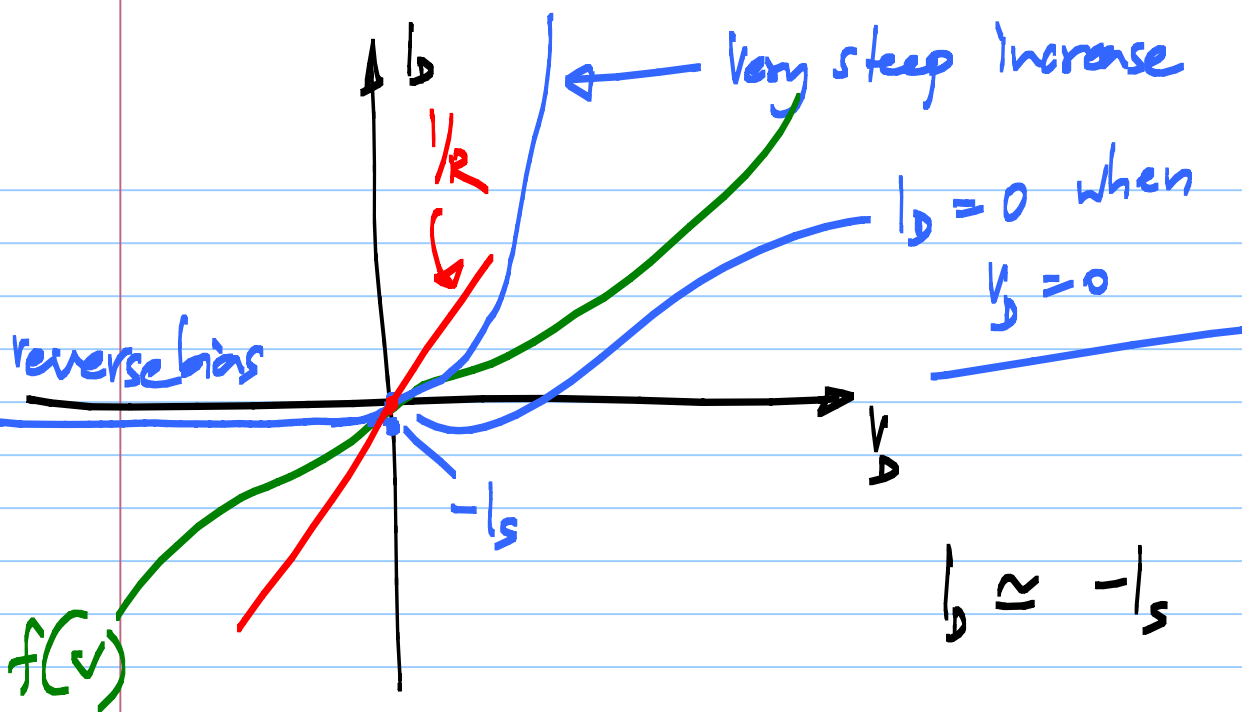

$$I_D = I_s \left(\exp\left(\frac{V_D}{V_t}\right) - 1 \right)$$

$V_D > 0$: significant currents can flow: forward bias

$V_D < 0$: very small currents reverse bias

V_D : large & negative
 $-V_D \gg V_t$

passive element
 \Rightarrow characteristic only in 1st & 3rd quadrants


\Rightarrow has to pass through the origin

Nonlinear circuit analysis

Can be solved numerically


$$\frac{V_s - V_D}{R} = f(V_D) = I_s \left(\exp\left(\frac{V_D}{V_t}\right) - 1 \right)$$

V_s changes
6.7V

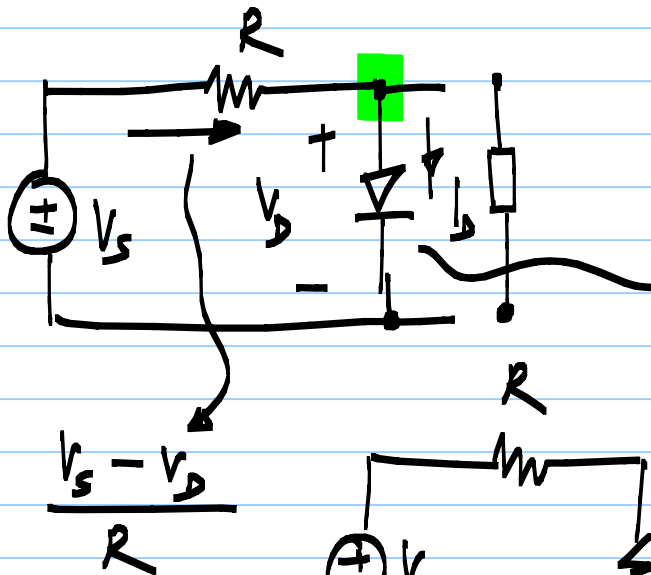

$$I_D = f(V_D)$$
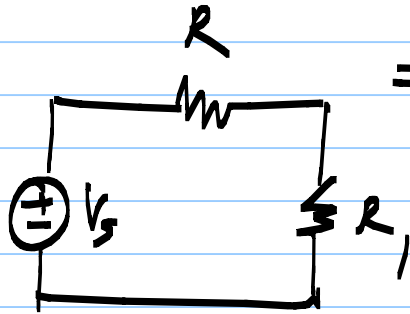
$$= I_s \left(\exp\left(\frac{V_D}{V_t}\right) - 1 \right)$$



$$\frac{V_s - V_D}{R} = I_s \left(\exp\left(\frac{V_D}{V_T}\right) - 1 \right)$$

$$\frac{V_s - V_D}{R} \quad \text{vs. } V_D$$

$$V_D = 0 \quad \frac{V_s}{R}$$

$$V_D = V_s \quad 0$$


$$\text{slope } \left(-\frac{1}{R} \right)$$


$$V_s = 5.7V, R = 5k\Omega$$

$$I_s = 10^{-15}A$$


$$V_D \approx 0.72V \quad \text{solution}$$


$$I_D \approx 1mA$$

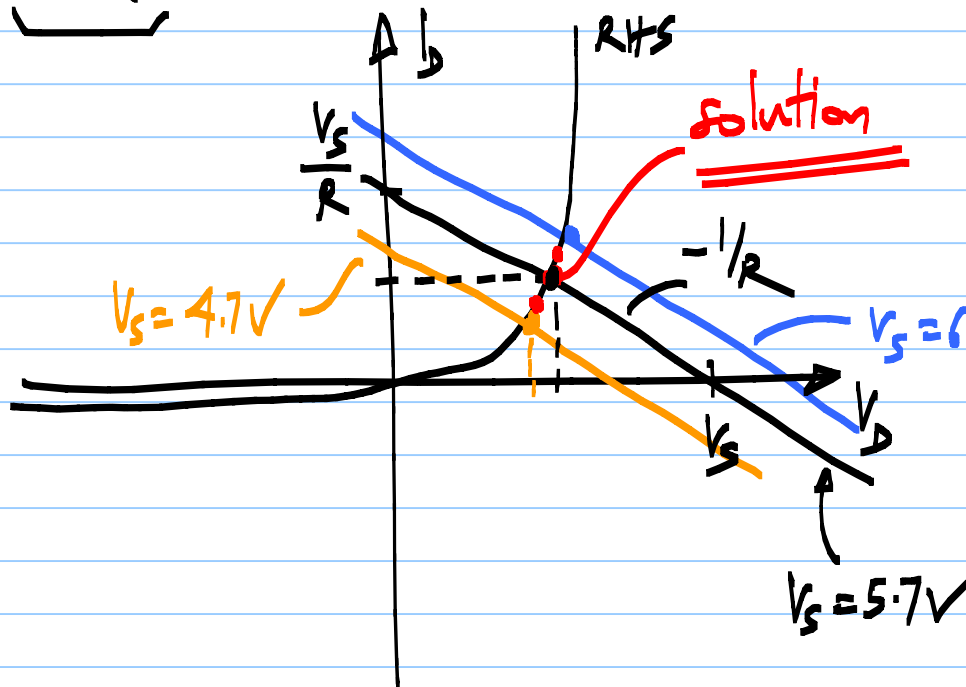

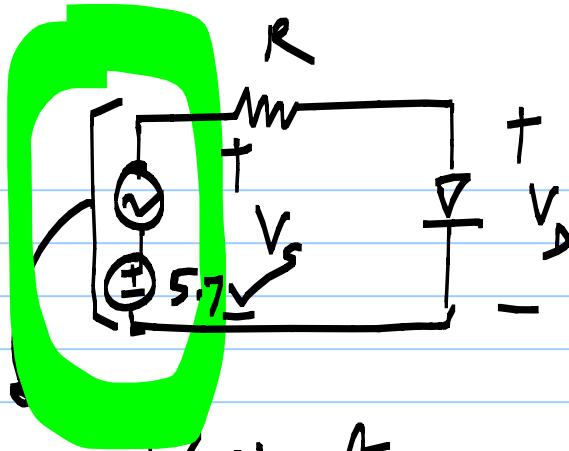


$V_s: 1V \cdot \sin \omega t$
 "signal"

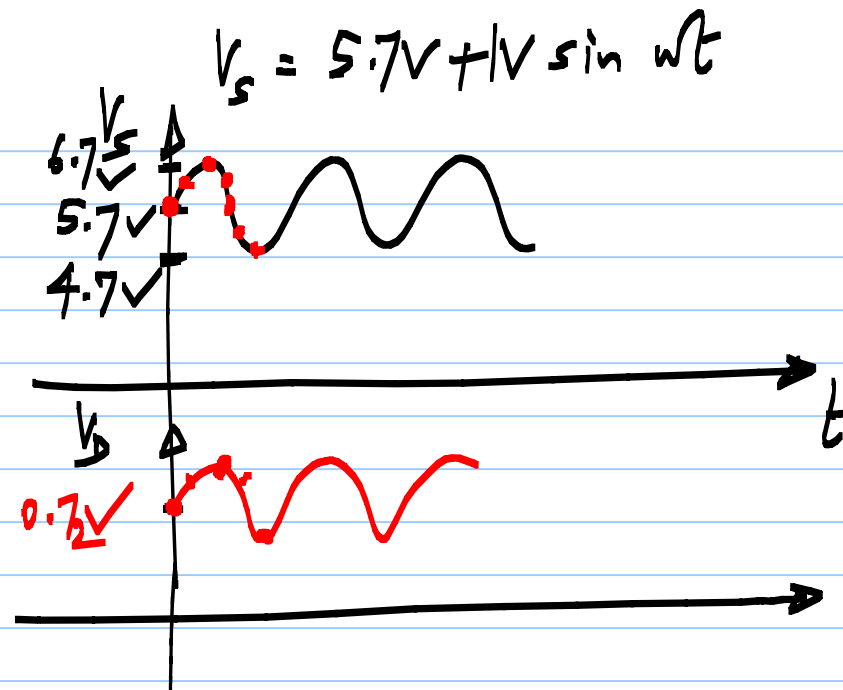

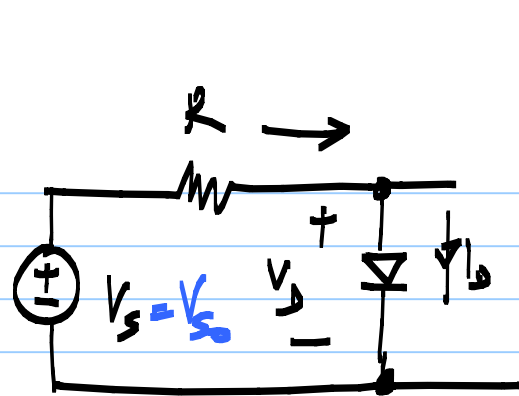

- Numerically
- Graphically
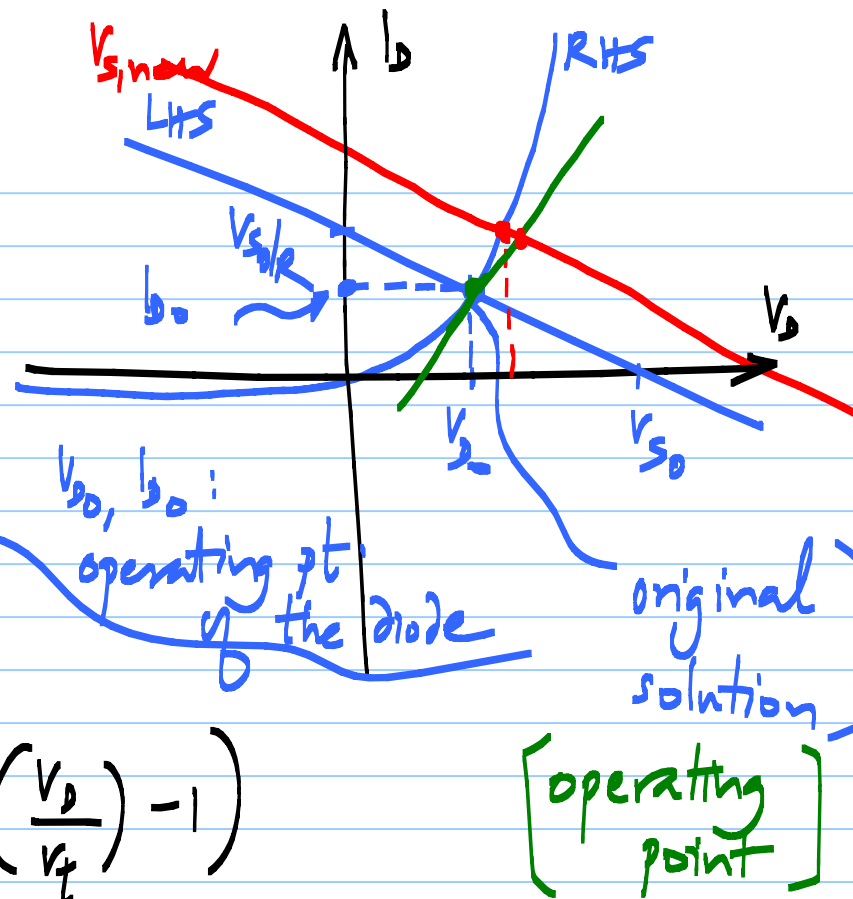
$$\frac{V_s - V_D}{R} = I_s \left(\exp\left(\frac{V_D}{V_T}\right) - 1 \right)$$



If the change is "small", approximating n.l. curve by its tangent yields a good enough solution

$$\frac{V_s - V_D}{R} = f(V_D) = I_s \left(\exp\left(\frac{V_D}{V_T}\right) - 1 \right)$$

$$I_s = 10^{-15} \text{ A}, V_s = 5.7 \text{ V}, R = 5 \text{ k}\Omega$$

$$V_{D_0} = 0.716 \text{ V}; I_{D_0} = 1 \text{ mA}$$

1st solution: operating point: $V_s = V_{s_0}$
Solve using nonlinear analysis

@ op. point $V_D = V_{D_0}; I_D = I_{D_0}$

$V_s = V_{s_0} + u_s$ new V_s represented as old value
6.7V = 5.7V + 1.0V + increment u_s

$$V_D = V_{D_0} + u_D$$

All quantities represented as (original) operating point
+ increments


$$\frac{V_s - V_D}{R} = I_s \left(\exp\left(\frac{V_D}{V_t}\right) - 1 \right)$$

$$\frac{V_{s0} - V_{D0}}{R} = I_s \left(\exp\left(\frac{V_{D0}}{V_t}\right) - 1 \right)$$

$$\frac{V_{s0} + v_s - V_{D0} - v_D}{R} = I_s \left(\exp\left(\frac{V_{D0} + v_D}{V_t}\right) - 1 \right)$$

$$\frac{V_s - V_D}{R} = f(V_D) \quad \text{gen. equation}$$
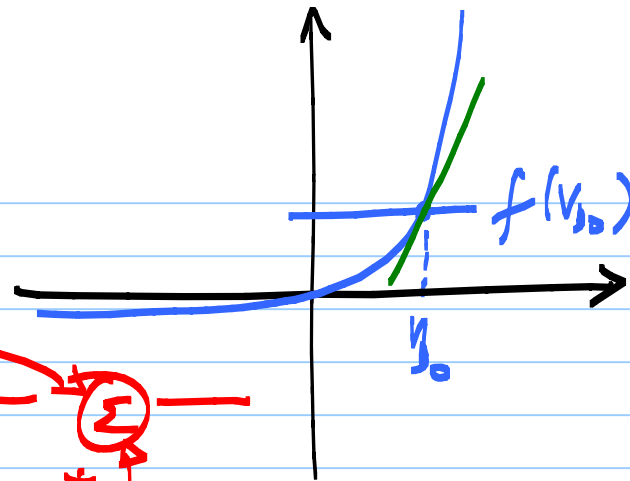
$$\frac{V_{s0} - V_{D0}}{R} = f(V_{D0}) \quad \text{op. point}$$



$$\frac{V_{s0} + v_s - V_{D0} - v_D}{R} = f(V_{D0} + v_D) = f(V_{D0}) + f' \Big|_{V_{D0}} \cdot v_D$$

Taylor series about V_{D0}

+ ~~h.o.t.~~



$$f(v) = f(v_0 + v) = f(v_0) + f' \Big|_{v_0} \cdot v + \frac{f''}{2!} \Big|_{v_0} v^2 + \frac{f'''}{3!} \Big|_{v_0} v^3 + \dots$$

Can always find v small enough
to neglect h.o.t

$$\frac{V_s - V_D}{R} = \left[f' \Big|_{V_D} V_D \right] \quad \text{Linear in the}$$

increment V_D

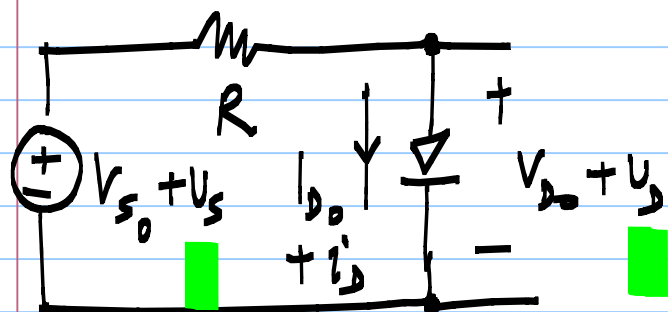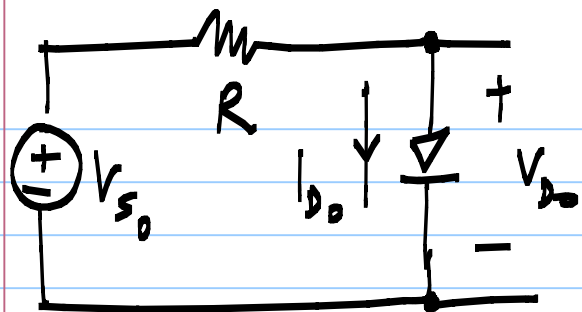Incremental quantities related by a
linear equation






$$\frac{V_S - U_D}{R} = f' \bigg|_{V_{D_0}} \cdot U_D$$

$$f(V_D) = I_D$$


$$f' = \frac{\partial I_D}{\partial V_D} \div \text{conductance}$$

$$U_D = U_S \cdot \frac{1/f' \big|_{V_{D_0}}}{R + 1/f' \big|_{V_{D_0}}}$$

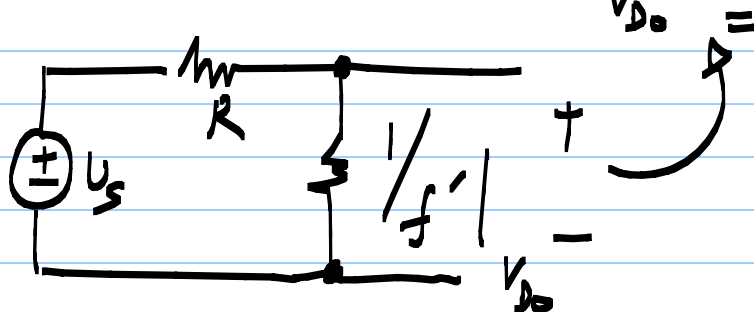

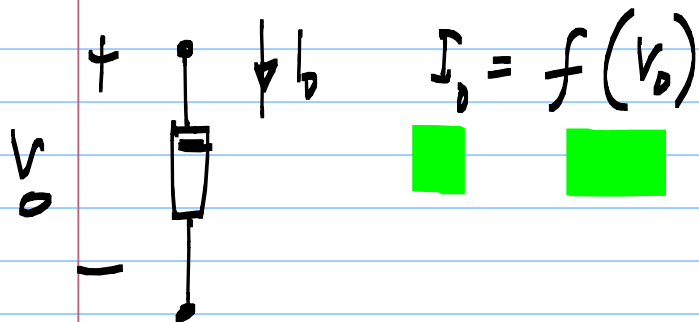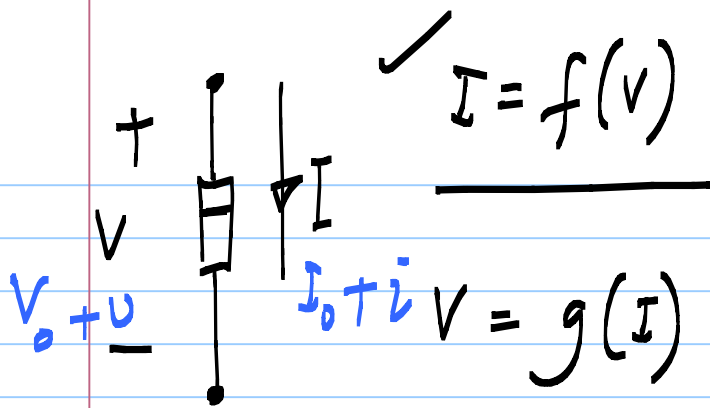

op. point

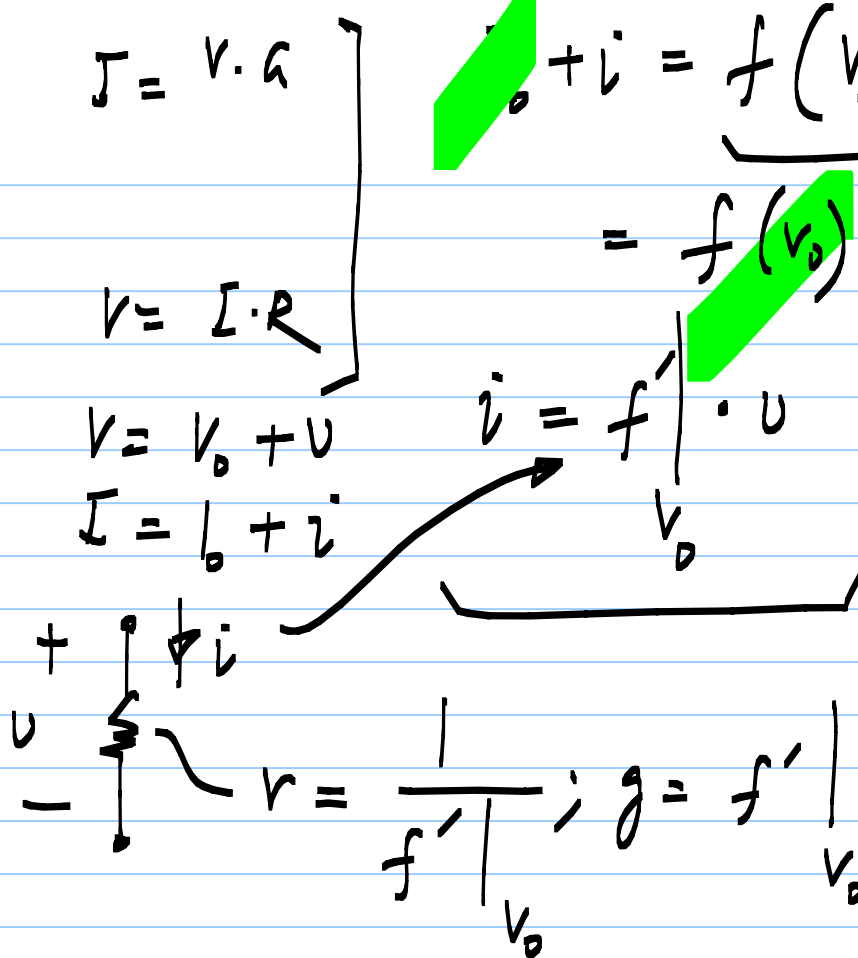


$$V_0 + i = f(V_0 + v)$$

$$= f(V_0) + f'|_{V_0} \cdot v + \text{h.o.t.}$$

$$i = f'|_{V_0} \cdot v$$


$$V = h(I)$$

$$r = h' \Big|_{\substack{I_0 \\ \text{op. p.} \sim t}} \quad ; \quad g' = \frac{1}{h' \Big|_{I_0}}$$

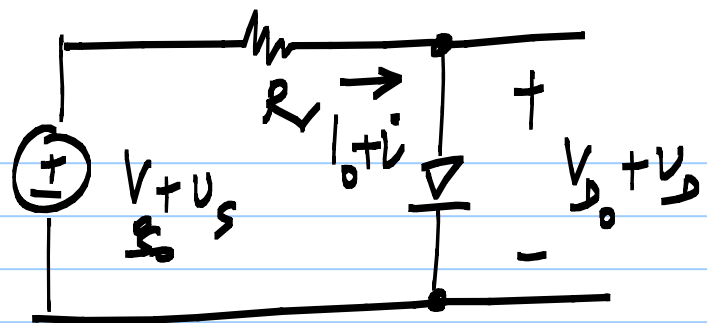

$$v_D = v_s \cdot \frac{r}{r + R}$$


$$i = \frac{v_s}{r + R}$$

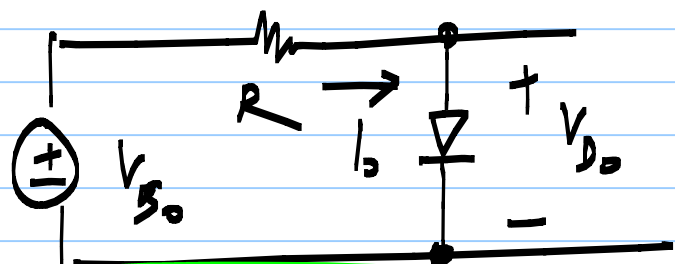


Incremental
resistance at the
o.p.

$$r = \frac{1}{f' |_{V_{D0}}}$$

Small signal
incremental
eq. circuit-

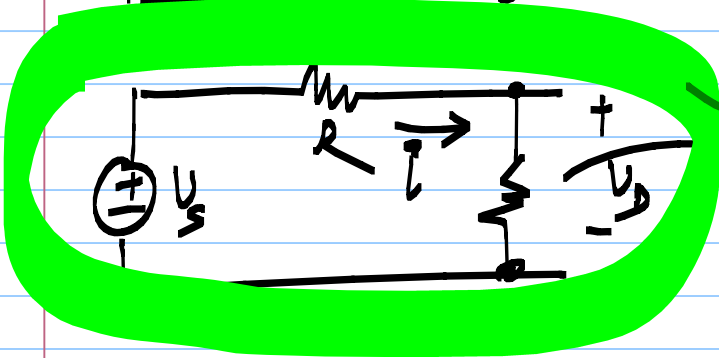

Diode model

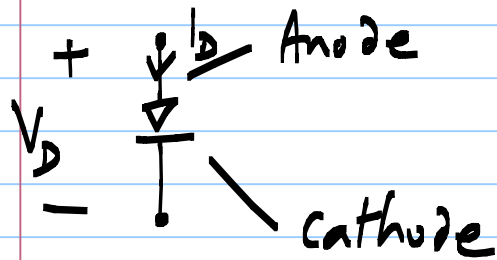


$$I_D = I_s \left(\exp\left(\frac{V_D}{V_t}\right) - 1 \right)$$

I_s : reverse saturation current

$$V_t = \frac{kT}{q} \quad \text{Thermal voltage}$$

$\approx 25\text{mV} @ 300\text{K}$

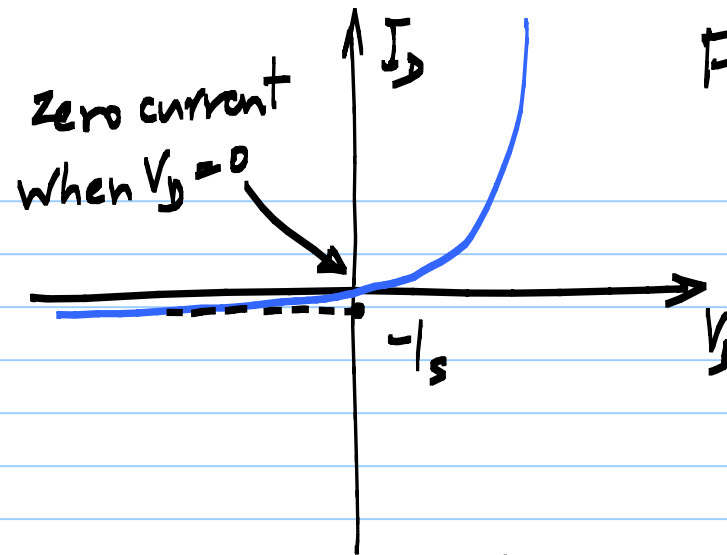


$$V_D = V_t \cdot \ln\left(\frac{I_D}{I_s}\right)$$

Forward bias
with $I_D \gg I_s$

$$\exp\left(\frac{V_D}{V_t}\right) \gg 1$$
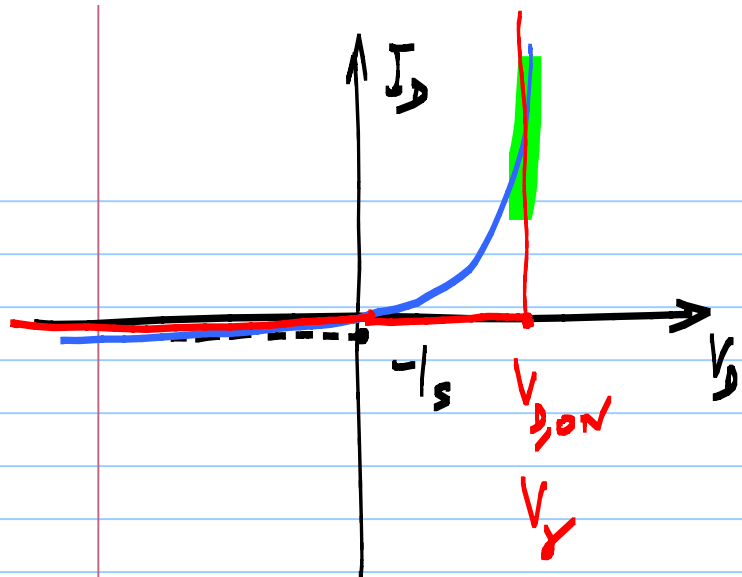
$$I_D \approx I_s \exp\left(\frac{V_D}{V_t}\right)$$



$$V_D \approx V_t \ln \left(\frac{I_D}{I_s} \right)$$

V_D changes slowly with I_D ,


V_D : Constant with I_D

$V_{D,on} : 0.7V \checkmark \checkmark$

$V_{D,on} : 1V$ (high currents)


$|I_D| \ll I_s$ in reverse bias

$I_D \approx 0$ in reverse bias


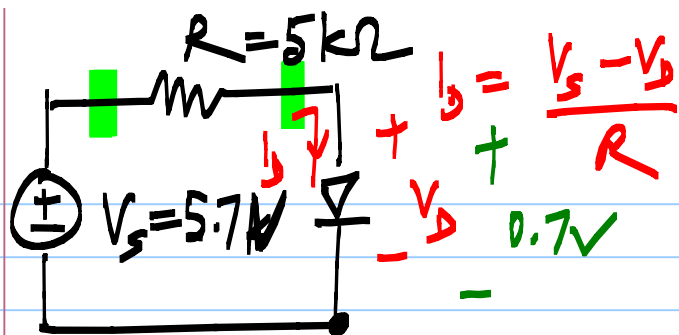


$V_D = V_{D, on}$ when there is a forward current
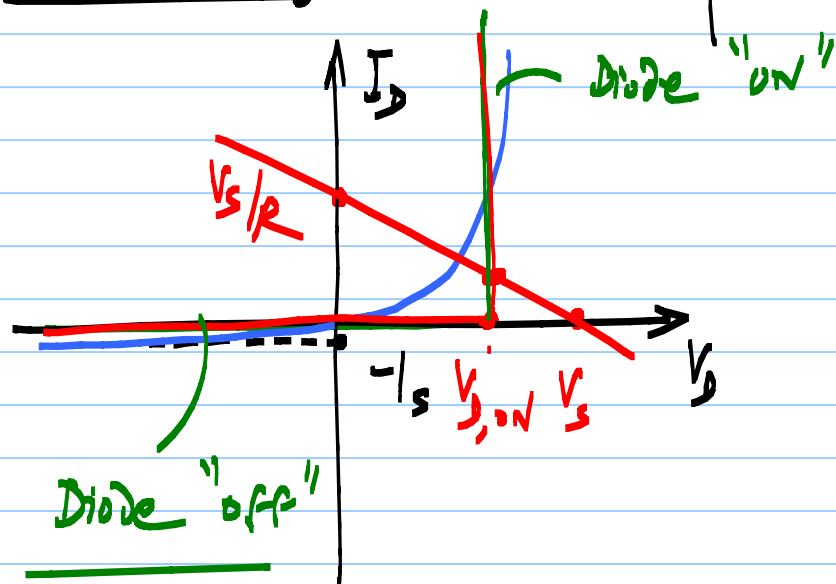
$$I = \frac{5.7V - 0.7V}{5k\Omega} = 1mA$$



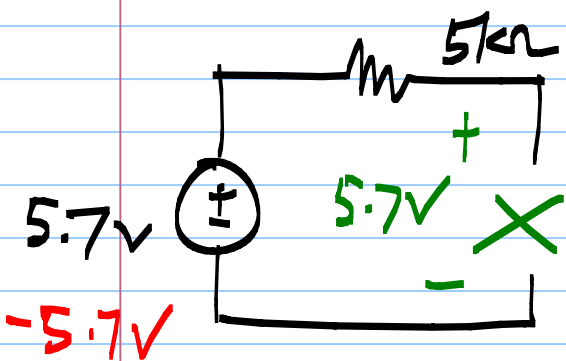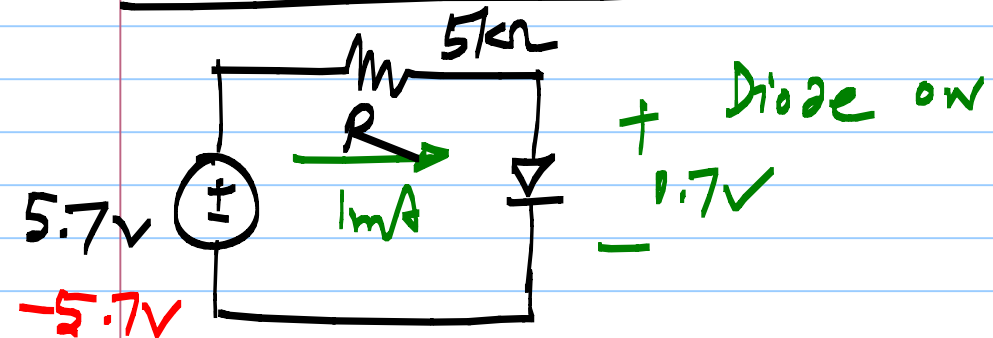
Solving diode problems using the approx. characteristic



Contradictory
Diode off
open circuit



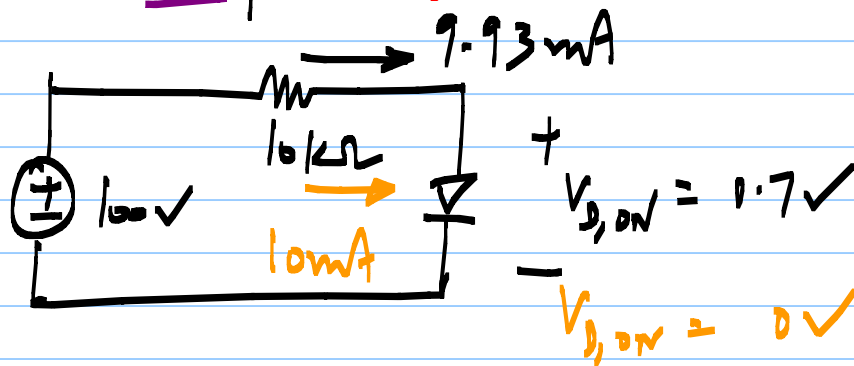$V_{D,on} \approx 0$ Forward bias
 $I_D = 0$ Reverse bias



"Large signal" characteristics of a diode
Total \Rightarrow not "increments"

Exact: $I_D = I_S \left(\exp \left(\frac{V_D}{\eta V_T} \right) - 1 \right)$


$$\left[\begin{array}{ll} I_D \approx I_S \exp \left(\frac{V_D}{\eta V_T} \right) & \text{Fwd bias} \\ \approx -I_S & \text{Rev bias} \end{array} \right.$$

$$I_D = 0 \text{ when } V_D < 0.7 \text{ V} \quad \text{Rev. bias}$$

$$V_D = 0 \text{ V}$$

$$\underline{V_D = 0.7 \text{ V}} \text{ when } I_D > 0 \quad \text{Fwd bias}$$

Diode: Small signal characteristics

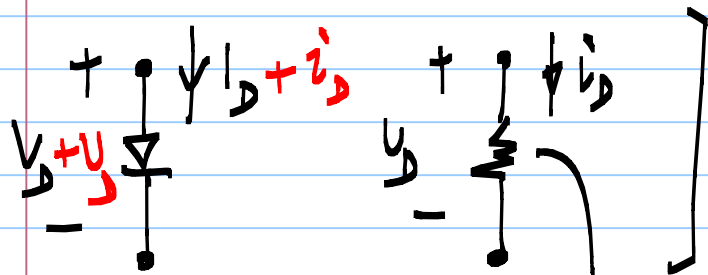

only incremental currents & voltages

$$I_D = f(V_D)$$

$$I_D + i_D = f(V_D + u_D)$$

$$i_D \approx f' \big|_{V_D} u_D$$

$$r = \frac{1}{f' \big|_{\text{op. point}}}$$

$$I_D = I_S \left(\exp \left(\frac{V_D}{V_T} \right) - 1 \right)$$

$$g_D = \frac{I_D}{V_T} \exp \left(\frac{V_D}{V_T} \right) \quad V_D = V_{D0} \text{ (op. point)}$$

FWD. BIAS $g_D = \frac{I_{D0}}{V_T} \quad (I_{D0}: \text{op. point current})$

REV. BIAS $g_D = 0 \quad (\text{OPEN CIRCUIT})$


$$r = \frac{1}{g_D} = \frac{V_T}{I_{D0}}$$

$$V_t \approx 25\text{mV} @ 300\text{K}$$

$$r_d = \frac{V_t}{I_D} = \frac{25\text{mV}}{1\text{mA}} = \underline{25\Omega}$$

$(I_D = 1\text{mA})$
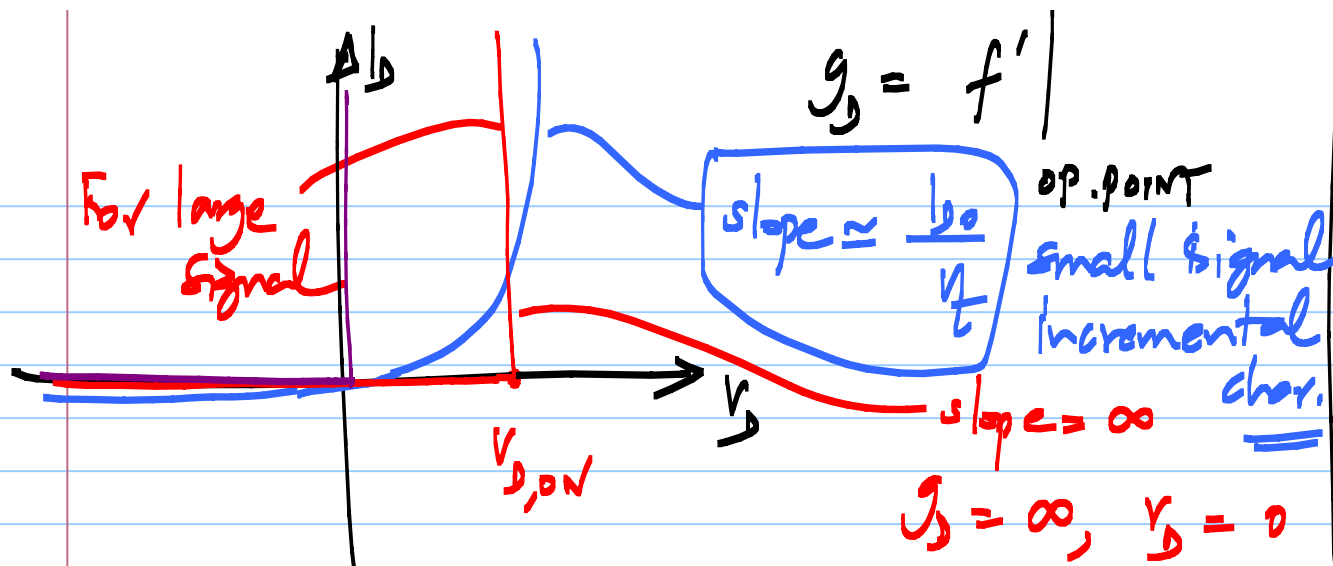
$$g_d = \frac{1\text{mA}}{25\text{mV}} = 40\text{mS}$$







Fwd bias:

Diode incremental short



Rev. bias:

incremental open

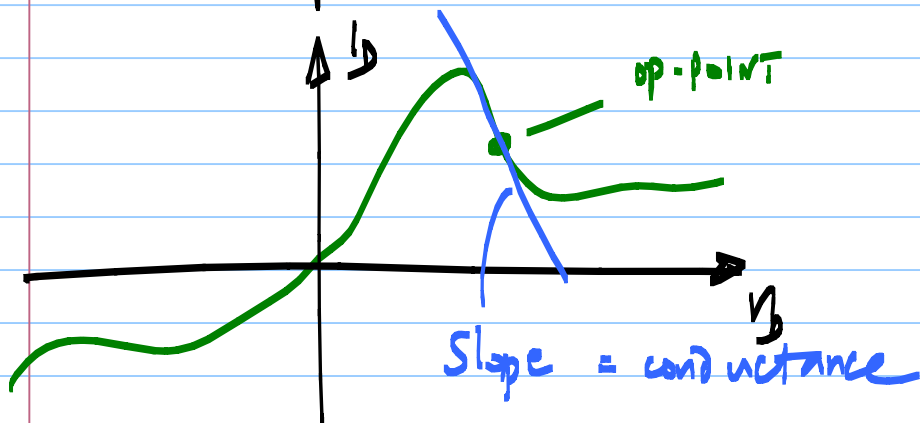

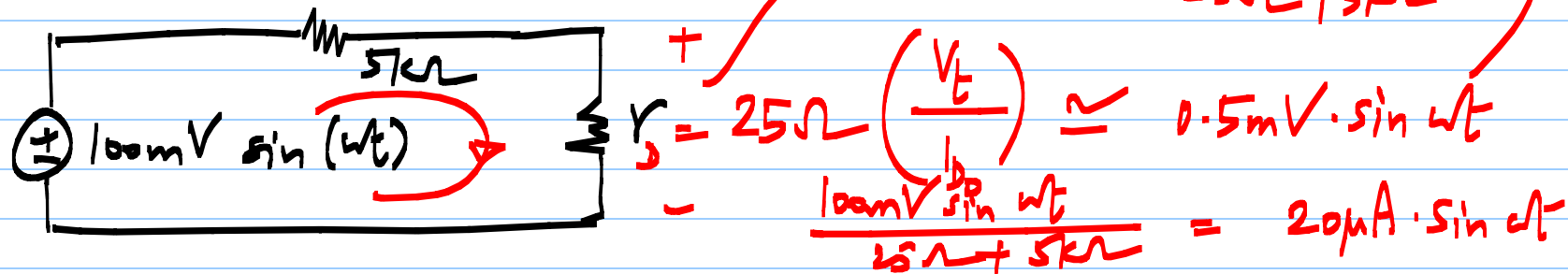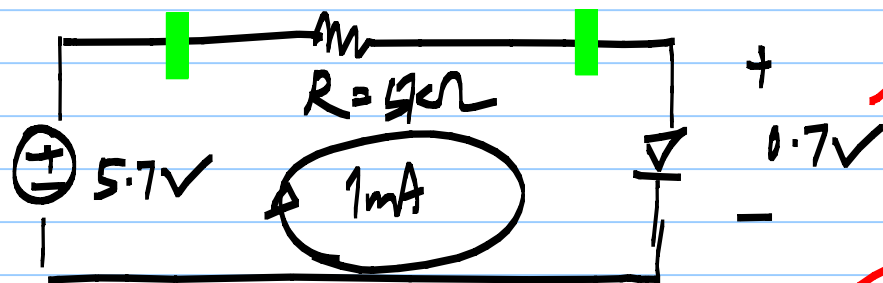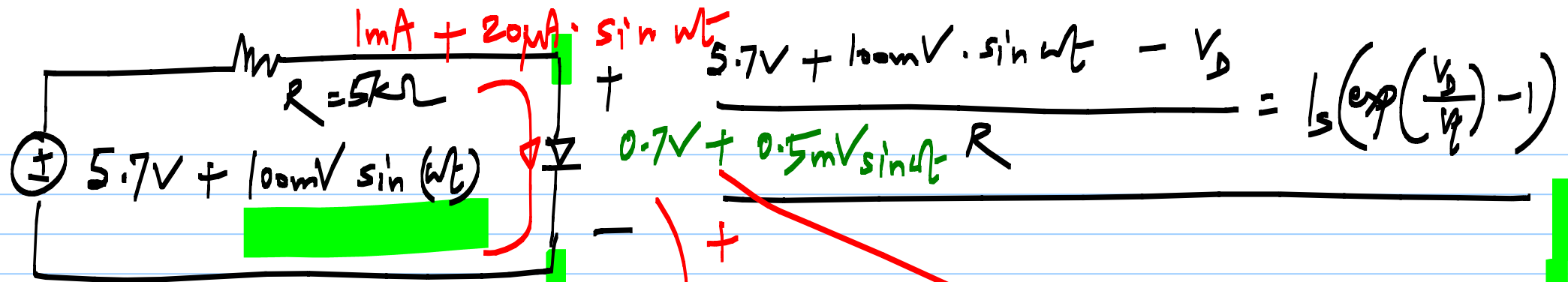


Large signal model of a diode

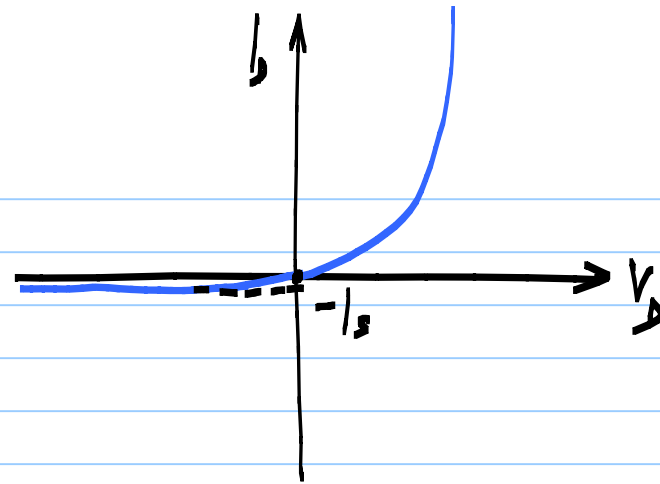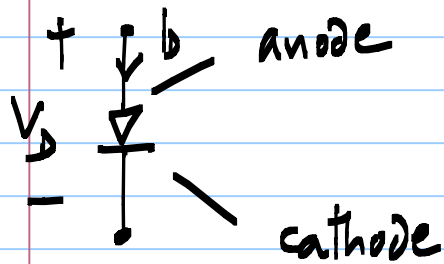

$$I_D = I_s \left(\exp\left(\frac{V_D}{V_t}\right) - 1 \right)$$

I_s : reverse saturation current
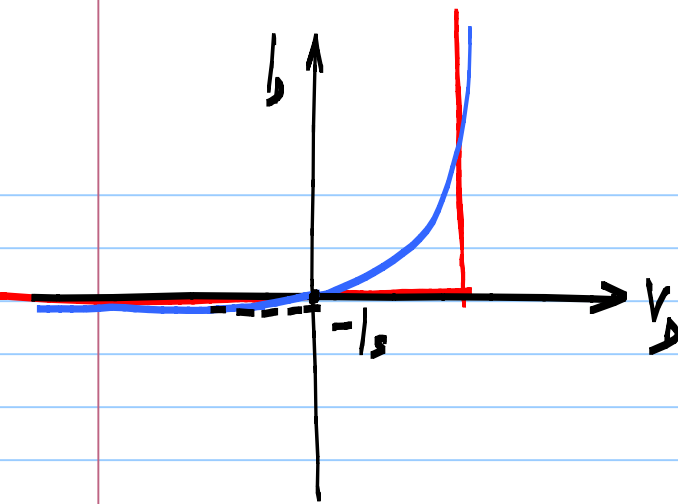
$$V_t = \frac{kT}{q} : \text{Thermal voltage} \approx 25\text{mV} @ 300\text{K}$$



$$I_D = I_S \left(\exp\left(\frac{V_D}{V_T}\right) - 1 \right)$$

$$\underline{V_D \gg V_T} \quad I_D \approx I_S \exp\left(\frac{V_D}{V_T}\right)$$

$$V_D < 0 \Rightarrow I_D = 0$$

$$V_D = V_T \cdot \ln\left(\frac{I_D}{I_S}\right)$$


$$I_D \rightarrow 2I_D$$

$$V_T \ln\left(\frac{2I_D}{I_S}\right) = V_T \ln\left(\frac{I_D}{I_S}\right)$$

$$+ \underbrace{V_T \cdot \ln(2)}$$

$$\underline{\underline{17.5 \text{ mV}}}$$

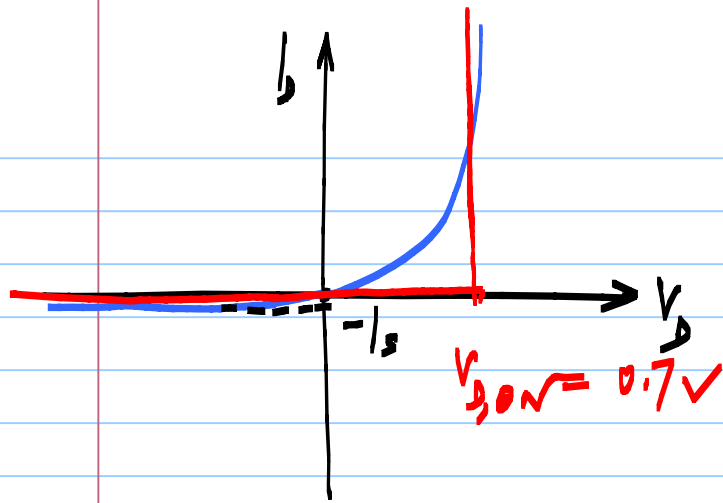Diode voltage constant
when there is a current
in the fwd direction



Forward bias: (substantial I_D flowing in the fwd direction)



(Diode on)

$$V_D = V_{D,ON} = 0.7V$$

~~Reverse bias:~~

(Diode off)
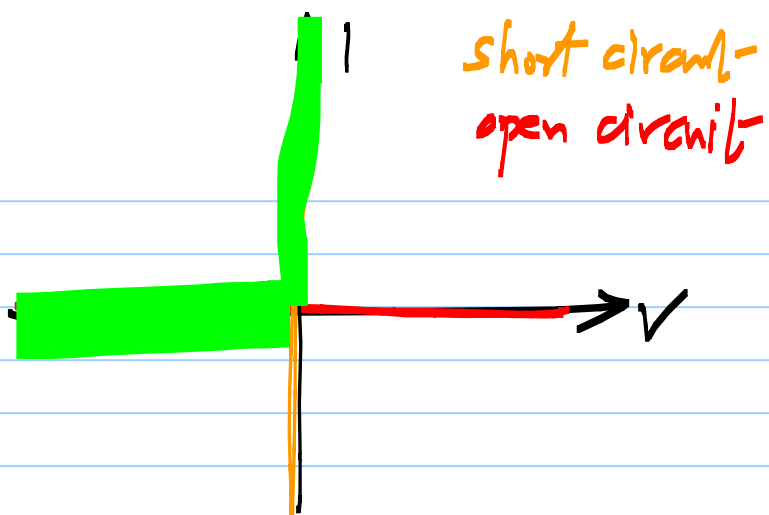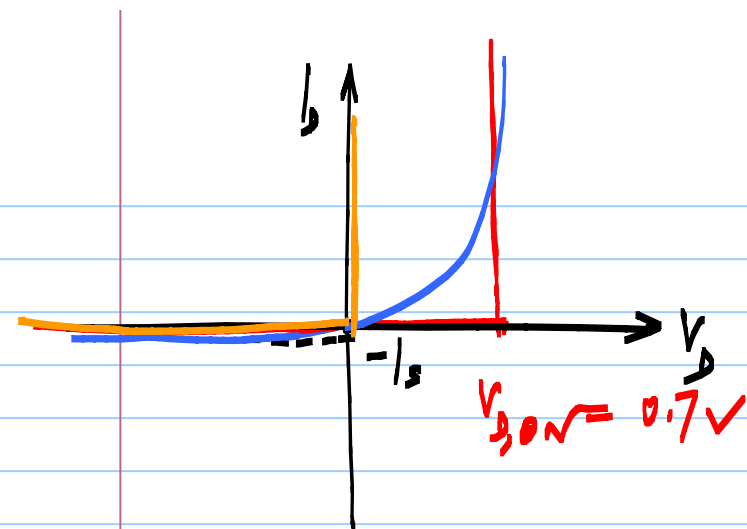
$$V_D < \underset{V_{D,ON}}{0.7V} \Rightarrow I_D = 0$$



We approximate $V_{D,on} \approx 0V$

"Exact": $I_D = I_S \left(\exp\left(\frac{V_D}{V_T}\right) - 1 \right)$


(1) : $I_D = I_S \exp\left(\frac{V_D}{V_T}\right) \quad V_D \gg V_T$
 $= 0 \quad V_D < 0$

(2) If $I_D > 0$, $V_D = V_{D,ON} = 0.7V$ (on)

If $V_D < V_{D,ON}$, $I_D = 0$ (off)

(3) If $I_D > 0$, $V_D = 0$ (on)

If $V_D < 0$, $I_D = 0$ (off)

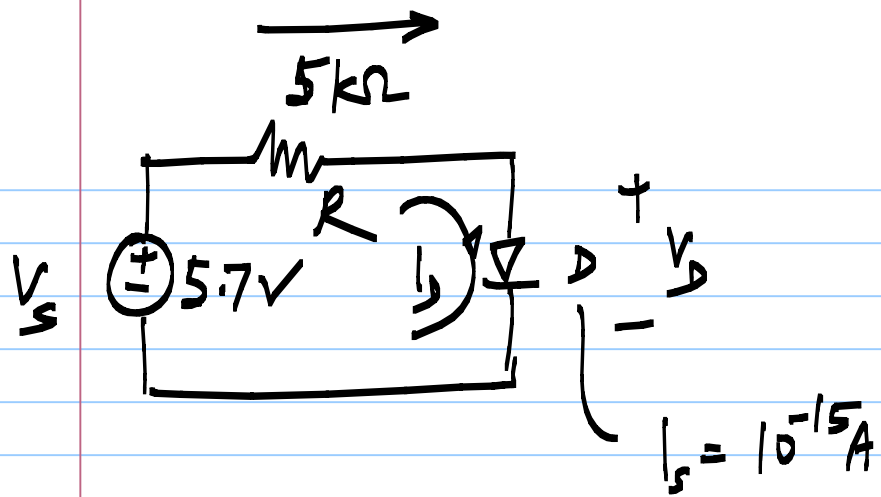



$$\frac{V_s - V_D}{R} = I_s \left(\exp\left(\frac{V_D}{V_T}\right) - 1 \right)$$

$$\underline{V_D = 0.72V}$$



$$V_D = V_{D,on} \quad \text{if } I_D > 0$$

$$I_D = 0 \quad \text{if } V_D < V_{D,on}$$

circuit with N diodes, 2^N possibilities

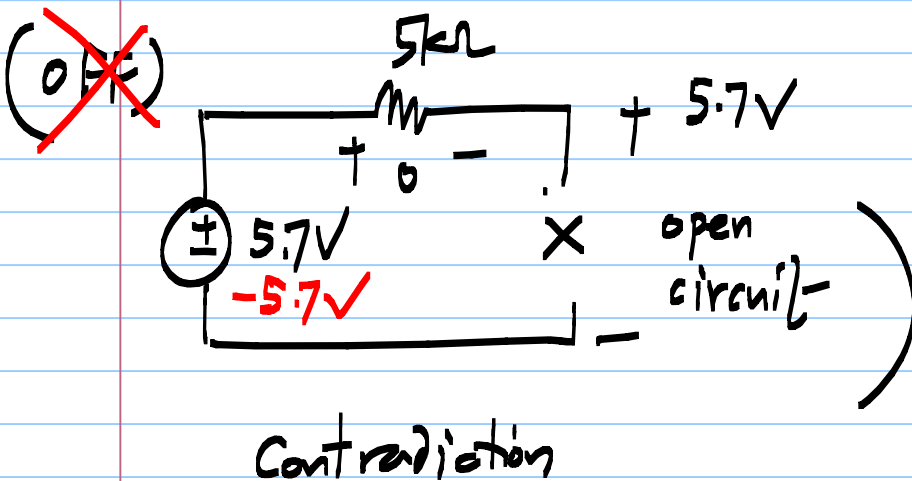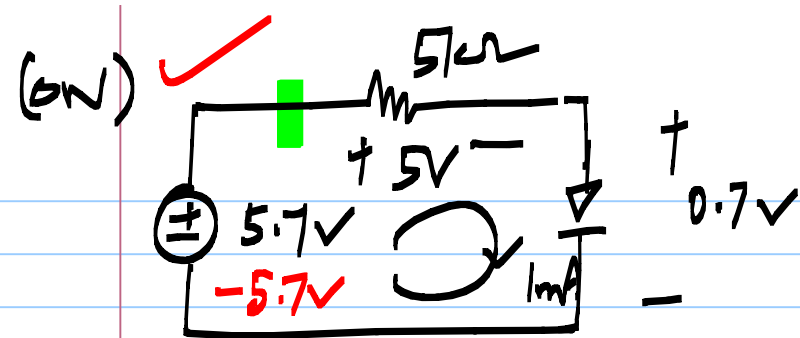

$$I_D = f(V_D)$$

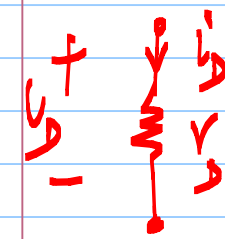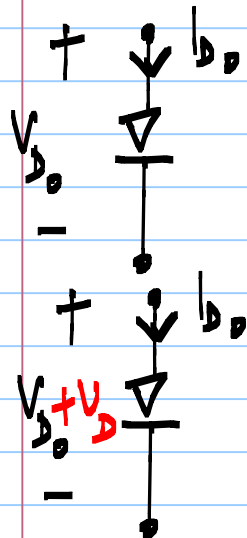

I_{D0}, V_{D0} : operating point of the diode

$V_{D0} = 0.7V$; I_{D0} : circuit analysis

$$I_D \approx \frac{I_{D0}}{0.7V} (if I_D > 0)$$

i_d, v_d : increments over the op. point

$$r_D = \frac{1}{f'_D|_{op}} ; g_D = f'_D|_{op}$$

r_D : small signal incremental resistance

$$R = \frac{V_R}{I_R} ; I_R = \frac{V_R}{R} ; g_R = \frac{1}{R} ; r_R = R$$


$$I_D = I_S \left(\exp\left(\frac{V_D}{V_T}\right) - 1 \right) \approx I_S \exp\left(\frac{V_D}{V_T}\right) \quad V_D \gg V_T$$

$$g_D = \left. \frac{\partial I_D}{\partial V_D} \right|_{op} = \left. I_S \cdot \exp\left(\frac{V_D}{V_T}\right) \right|_{op} = \frac{I_{D0}}{V_T} \quad (\text{op. point current})$$

$$r_D = \frac{1}{g_D} = \frac{V_T}{I_{D0}}$$



$$I_{D0} = 1 \text{ mA} \quad g_D = \frac{1 \text{ mA}}{25 \text{ mV}} = 40 \text{ mS}; \quad r_D = 25 \Omega$$


(room temp.)

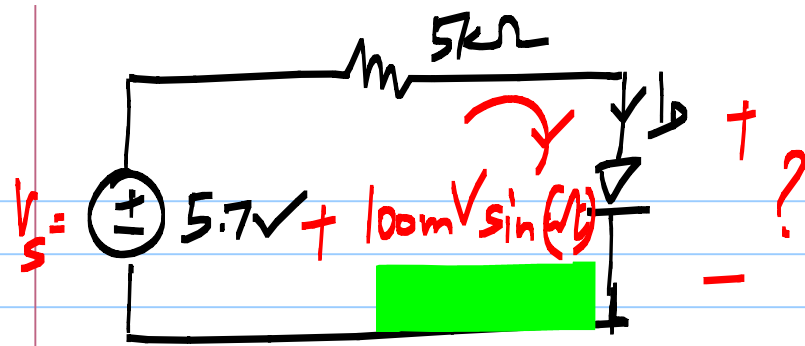

$$\frac{V_s - V_D}{R} = I_s \left(\exp\left(\frac{V_D}{V_T}\right) - 1 \right)$$
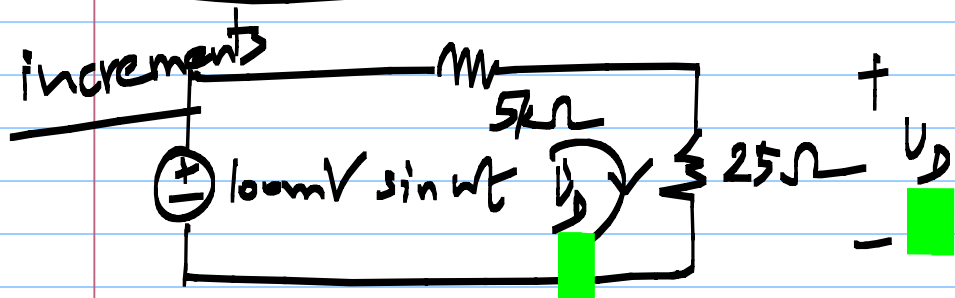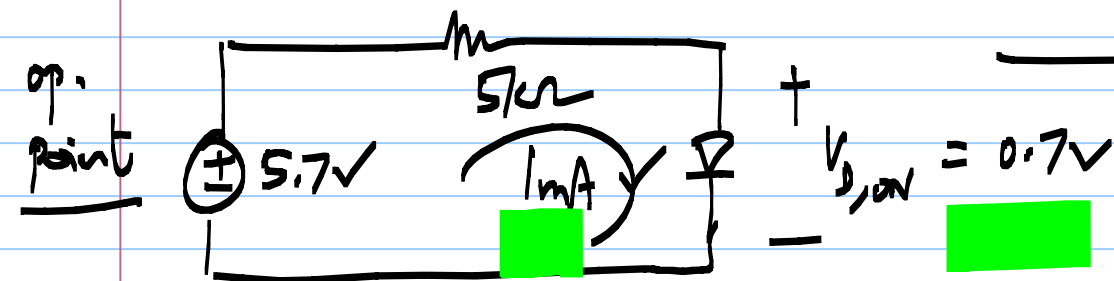
$$\frac{5.7V + 100mV \sin \omega t - V_D}{5k\Omega} = 10^{-15} \left(\exp\left(\frac{V_D}{V_T}\right) - 1 \right)$$



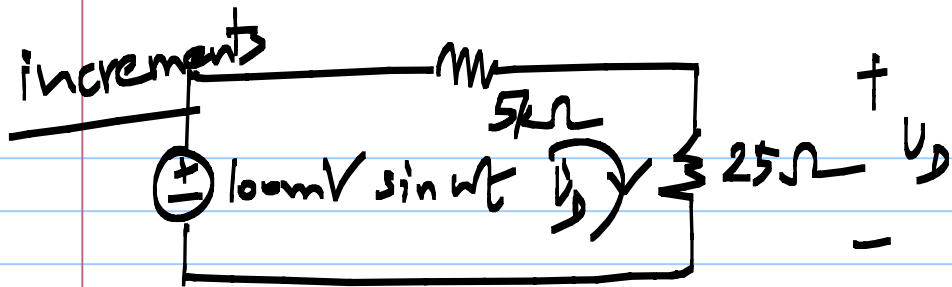

$$v_D = \frac{100\text{mV} \cdot \sin \omega t \cdot 25\Omega}{5\text{k}\Omega + 25\Omega} = 0.5\text{mV} \sin \omega t$$

$$i_D = \frac{100\text{mV} \sin \omega t}{5\text{k}\Omega + 25\Omega} = 20\mu\text{A} \cdot \sin \omega t$$