
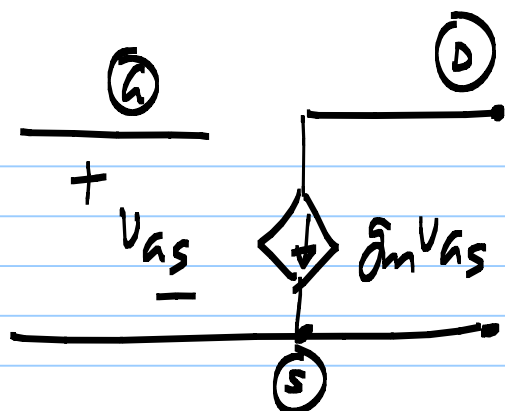


MOS:

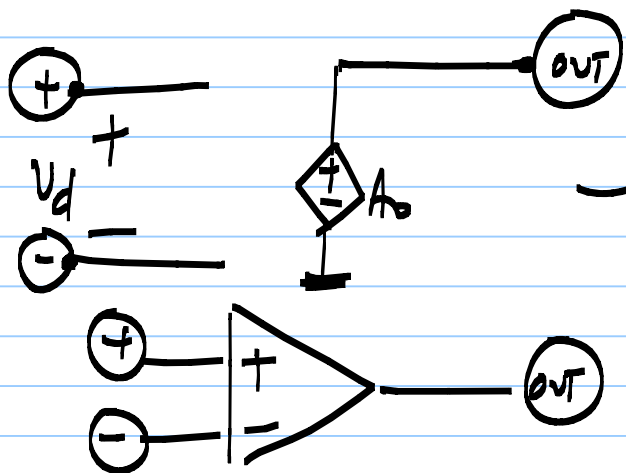

VCVS




VCVS & CCVS using negative fb.
& this device is an opamp

VCVS

$$v_o = k \cdot v_i$$

Error: $k v_i - v_o$


$v_i - \frac{v_o}{k}$

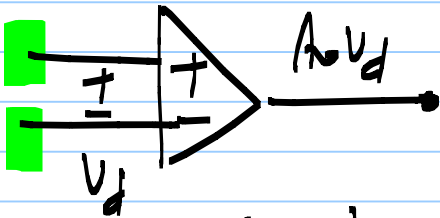

$v_i > 0$: o/p large positive

$v_i - \frac{v_o}{k} > 0$ output must be increased

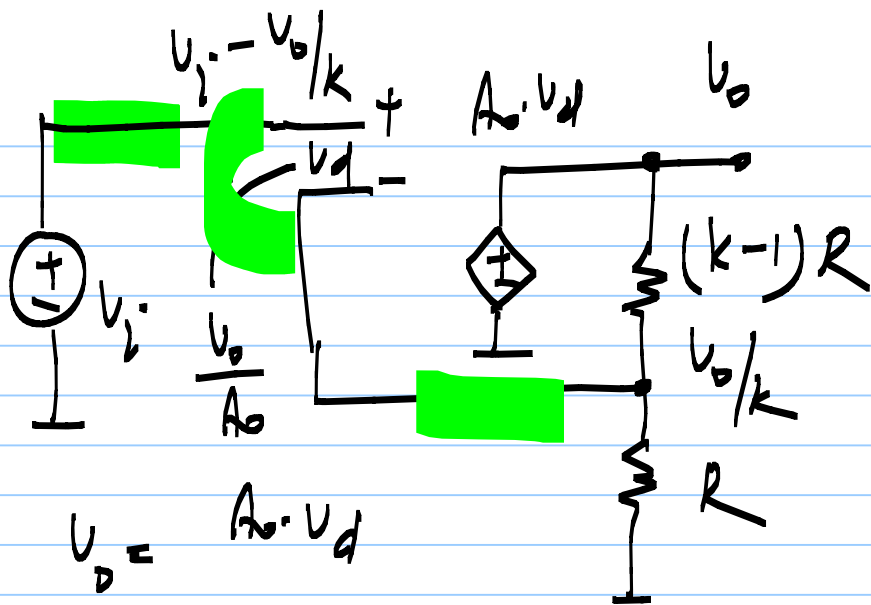$v_i - \frac{v_o}{k} < 0$ output must be decreased




$$v_i - \frac{v_o}{A_o} = \frac{v_o}{k}$$

$$\frac{v_o}{v_i} = \frac{1}{\frac{1}{A_o} + \frac{1}{k}} = \frac{k}{1 + \frac{k}{A_o}}$$

$$= \frac{A_o}{1 + \frac{A_o}{k}}$$

$$v_d = \frac{v_o}{A_o}$$
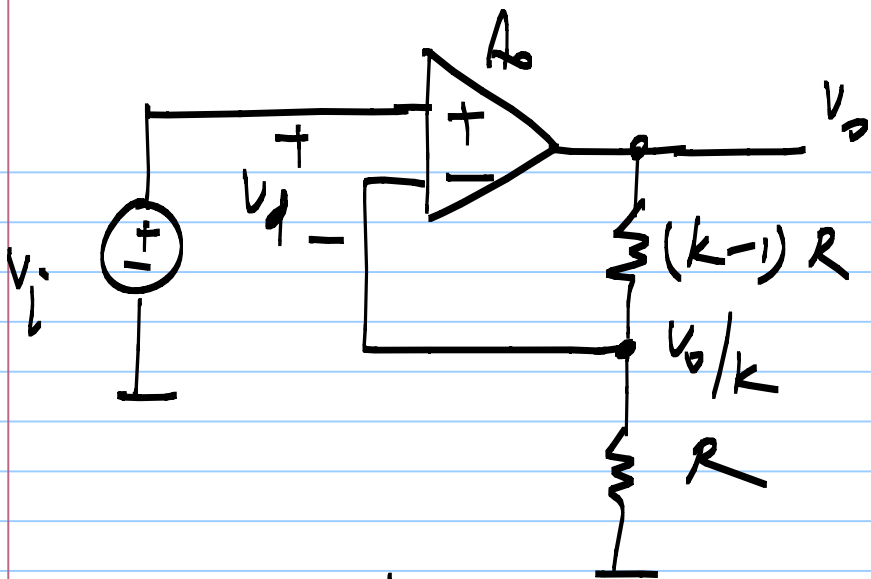
$$\frac{v_o}{v_i} \approx k : \frac{A_o}{k} : \text{very large}$$



$$k = 10$$

$$A_o = 1000 \rightarrow 2000$$

$$\frac{v_o}{v_i} = \frac{10}{1 + \frac{10}{\cancel{1000}^{2000}}} \approx 10 \left(\underbrace{0.995}_{1.99} \right) = 9.95$$


$$\frac{v_o}{v_i} = \frac{k}{1 + \frac{k}{A_o}} R \quad \text{if} \quad \frac{A_o}{k} \gg 1$$

ECVS using an opamp.

$$v_o = i_i \cdot R_m$$

$v_o - i_i \cdot R_m > 0$, output must be reduced

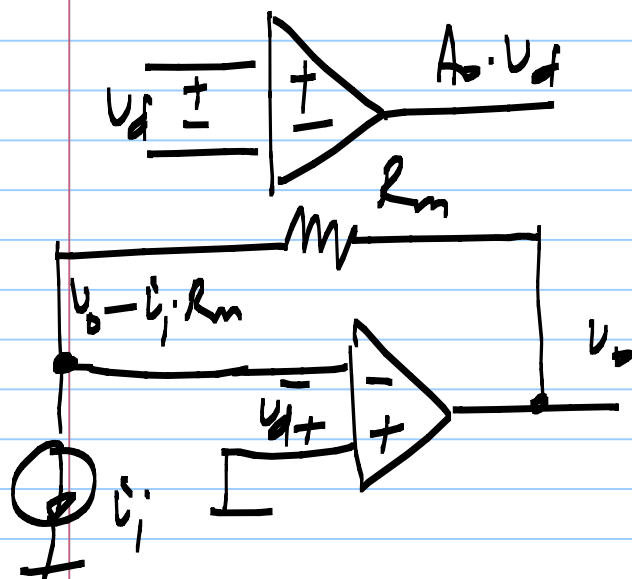
$v_o - i_i \cdot R_m < 0$, output must be increased



$$v_d > 0$$

$$v_d = -(v_o - i_i \cdot R_m)$$

CCVS using an opamp:


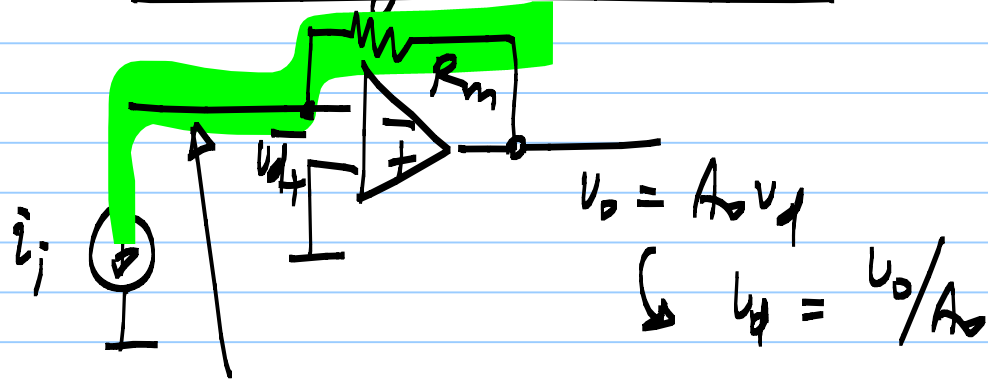


$$v_o = A_o v_d$$


$$\hookrightarrow v_d = v_o / A_o$$

$$v_o - i_j R_m = -v_d = \frac{v_o}{A_o}$$
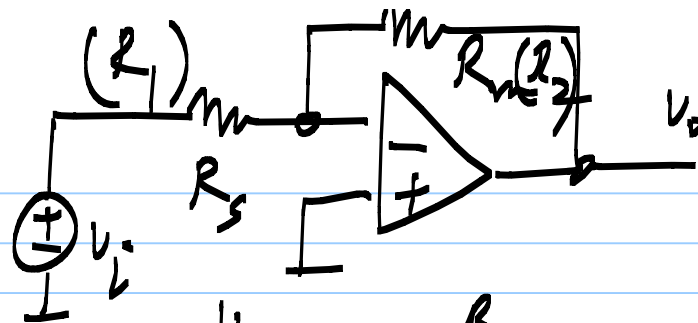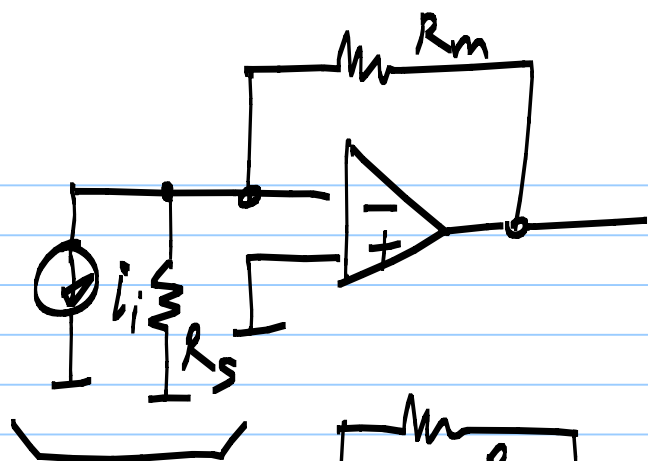
$$\frac{v_o}{i_j} = \frac{R_m}{1 + \frac{1}{A_o}} \approx R_m \quad \text{if } A_o \rightarrow \infty$$


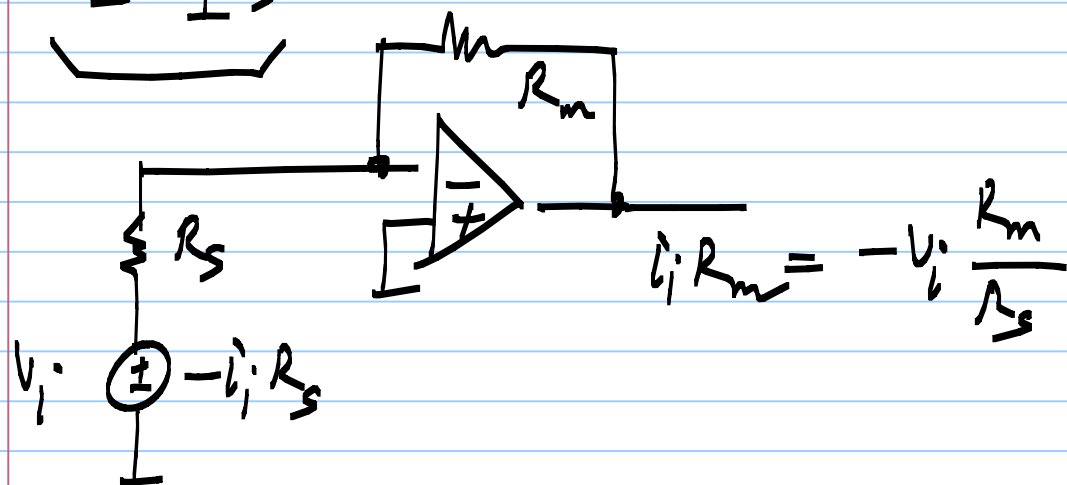
$$\frac{v_o}{v_i} = - \frac{R_m}{R_s} = - \frac{R_2}{R_1}$$



VCVS

$$= \left(1 + \frac{R_2}{R_1}\right) V_i$$

$$V_o = k V_i$$

if $A_o \rightarrow \infty$



CCVS

$$V_o = i_i R_m$$

if $A_o \rightarrow \infty$


Non-Inverting
amp.

Inverting
amp.

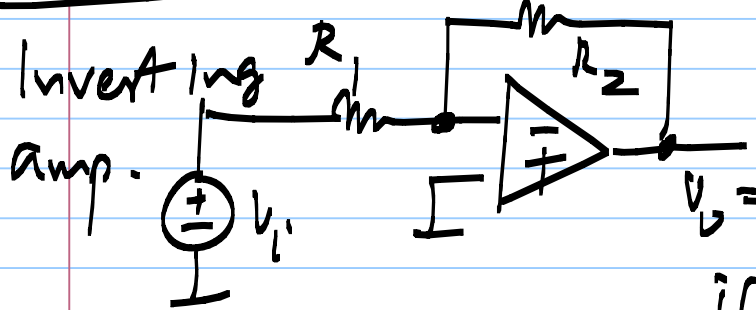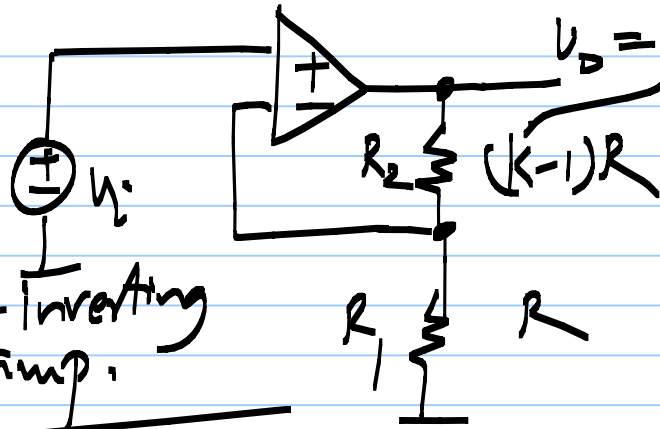

$$V_o = -\frac{R_2}{R_1} \cdot V_i$$

if $A_o \rightarrow \infty$

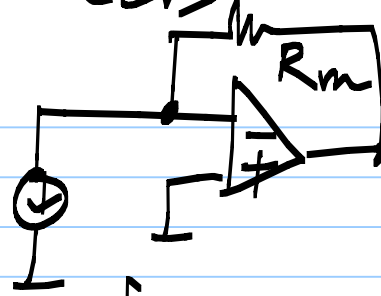



Negative feedback and virtual short


$$V_o = V_i \cdot \frac{k}{1 + k/A_o} \rightarrow k \text{ as } A_o \rightarrow \infty$$

VCRS - Non-inverting amplifier

$$V_d = \frac{V_o}{A_o} = V_i \cdot \frac{k/A_o}{1 + k/A_o}$$

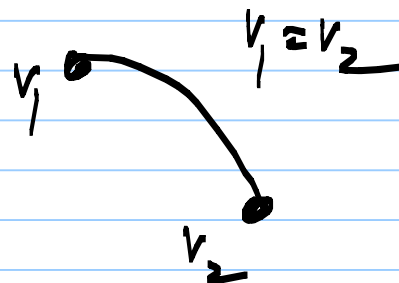
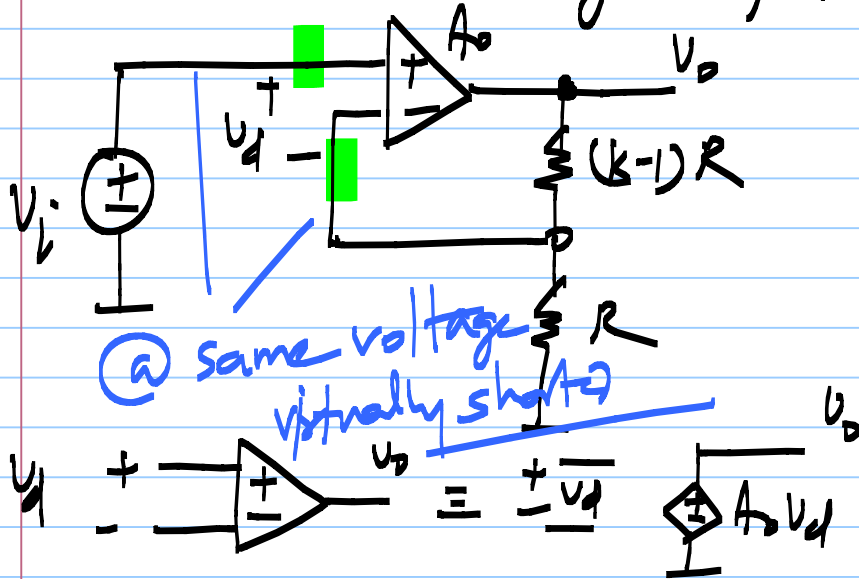
$$V_d \rightarrow 0 \text{ as } A_o \rightarrow \infty$$



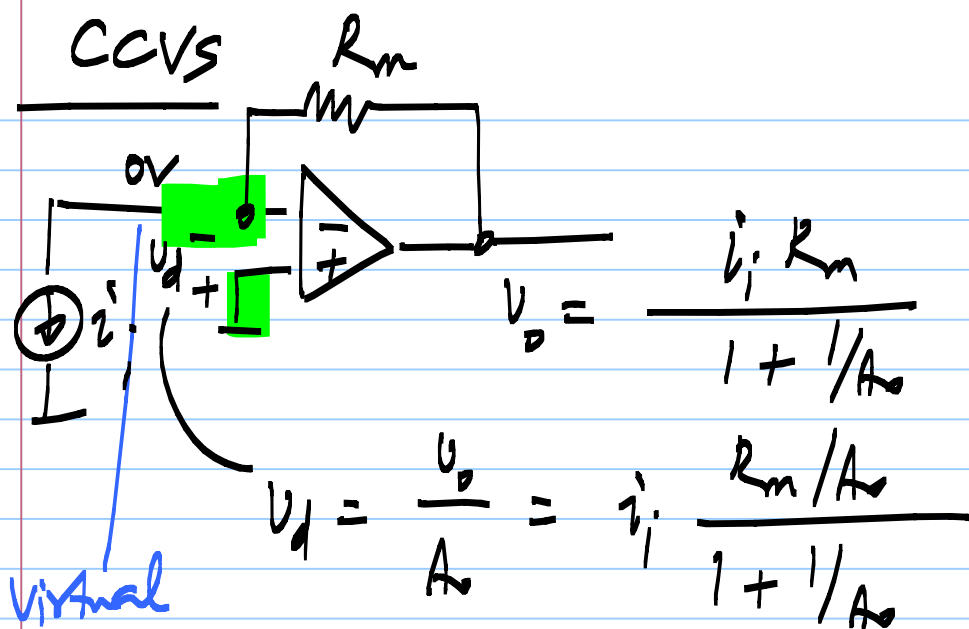

virtual ground

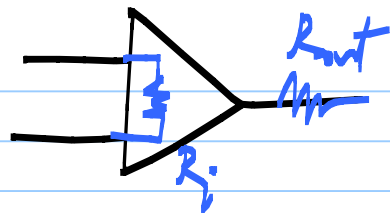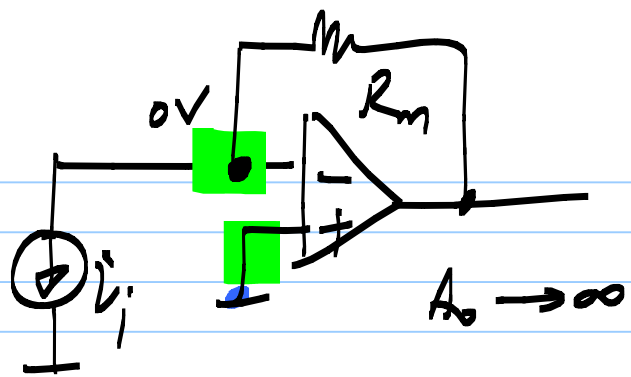
$$v_d \rightarrow 0 \text{ as } A_o \rightarrow \infty$$



Virtual short in circuits with transistors in -ve feedback

Source follower

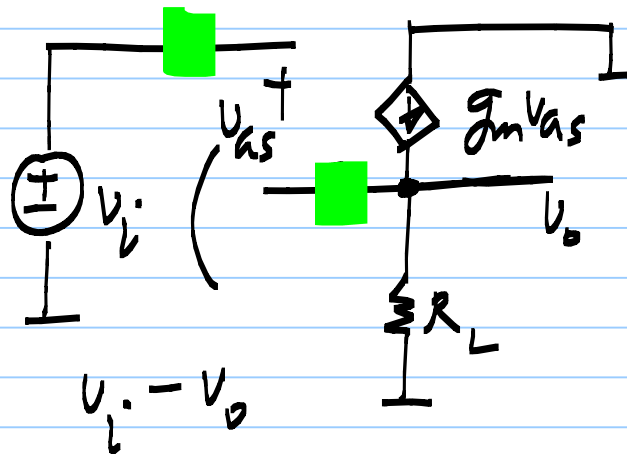
$$V_o = V_i \cdot \frac{g_m R_L}{1 + g_m R_L}; \quad V_{gs} = \frac{1}{1 + g_m R_L}$$



$$g_m R_L \rightarrow \infty : \quad \underline{V_{gs} \rightarrow 0}$$

Virtual short between
gate and source

VCCS

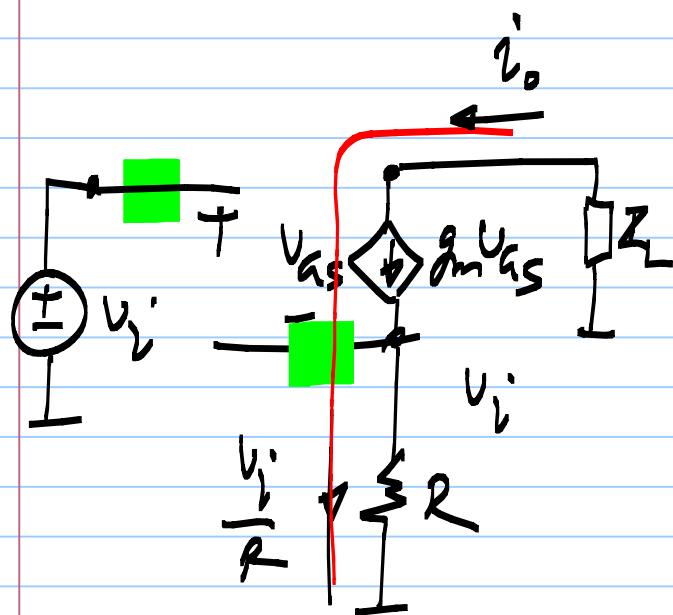


$$i_o' = U_i' \cdot \frac{g_m}{1 + g_m R} \approx U_i' \cdot \frac{1}{R} \text{ if } g_m R \rightarrow \infty$$

$$U_{gs} = U_i' \cdot \frac{1}{1 + g_m R} \rightarrow 0 \text{ as } g_m R \rightarrow \infty$$

Source follower

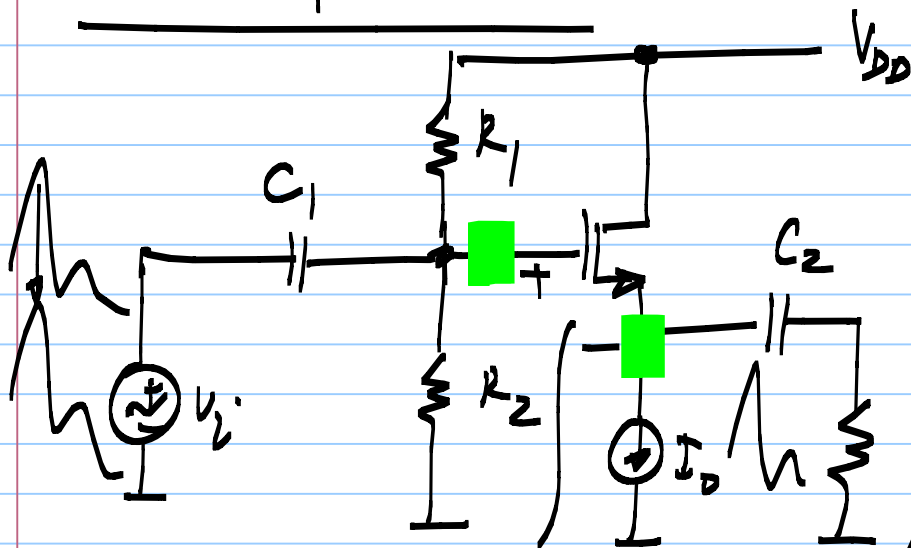incremental $V_{GS} = 0$ if $g_m R_L \rightarrow \infty$



$$\text{op. point } V_{GS} = V_T + \sqrt{\frac{2I_D}{\mu_n C_{ox} W/L}}$$

Transistor

VCVS $v_o = v_i$

VCCS


CCCS $i_o = i_i$

CCVS

Opamp


VCVS $v_o = k v_i$

CCVS

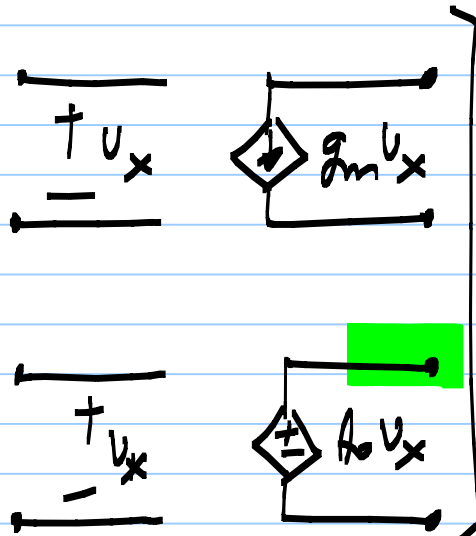

with any gain

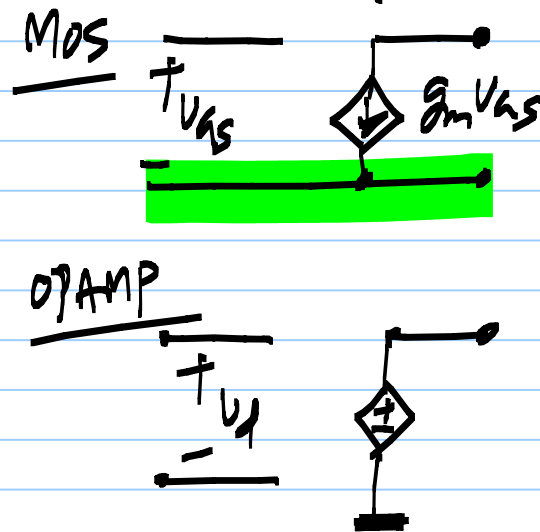
Using these any controlled source can be built using negative feedback



\Rightarrow VCVS, CCCS: gain = 1






~~CCCS~~, ~~VCVS~~

MOS VCVS, CCCS $k > 1$?

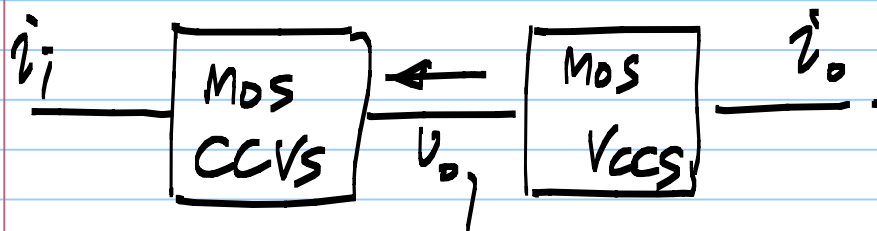


$$i_o = G_m \cdot v_i \quad ; \quad v_o = R_m' \cdot i_o$$

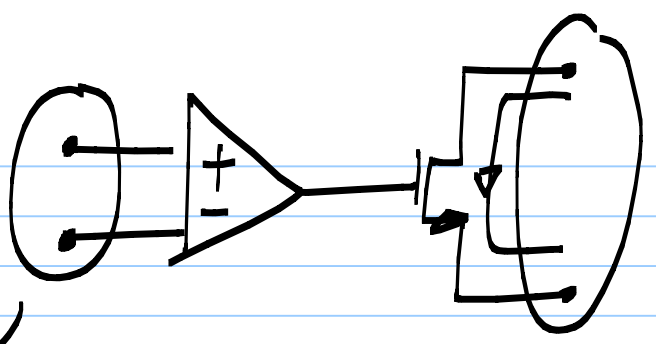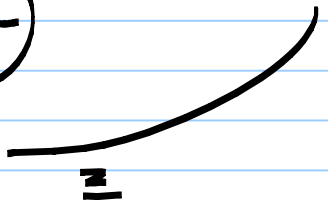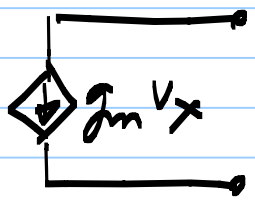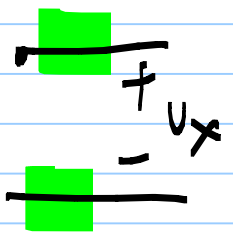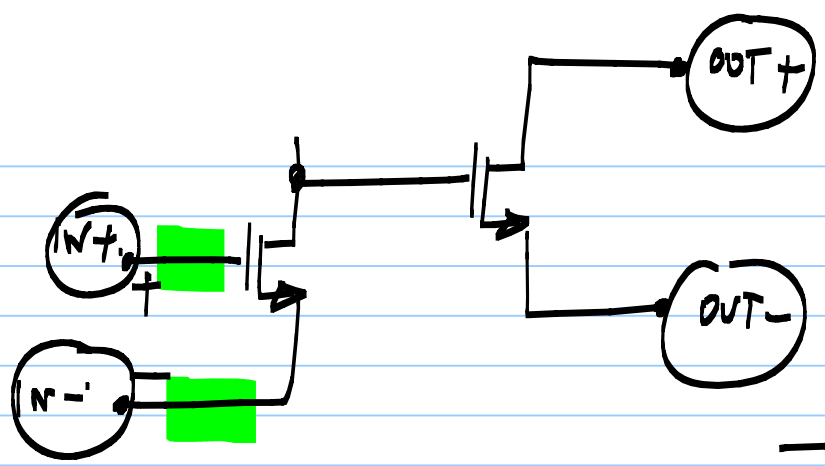
$$v_o = \underbrace{G_m \cdot R_m'}_{> 1} v_i$$




Common Source Amplifier

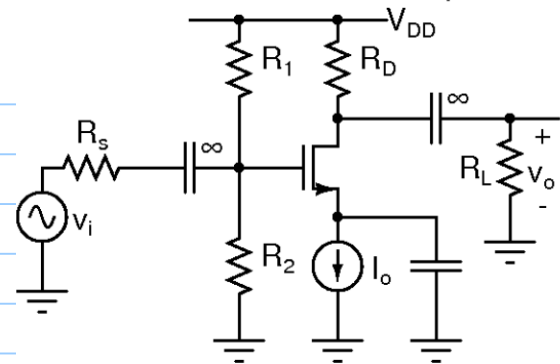

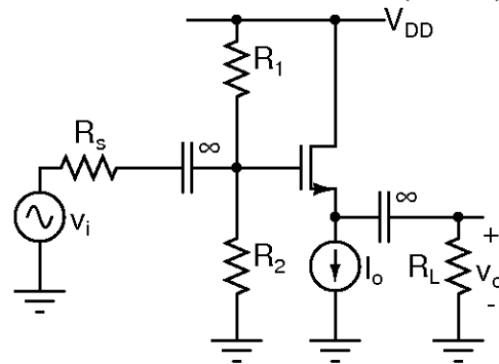
Common Drain Amplifier
Source Follower (VCVS)




Source Degeneration
(VCCS)

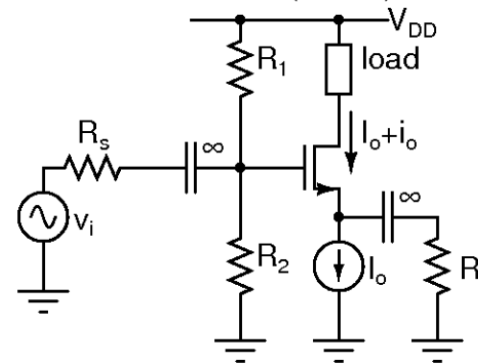


Common Gate Amplifier
(CCCS)

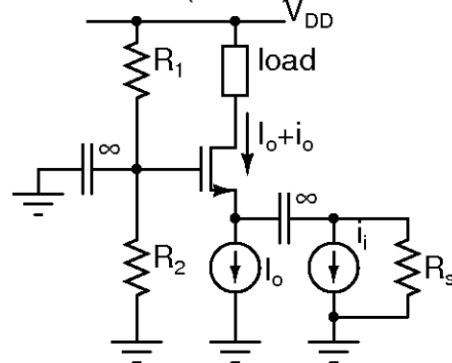


Drain Feedback Amplifier
(CCVS)

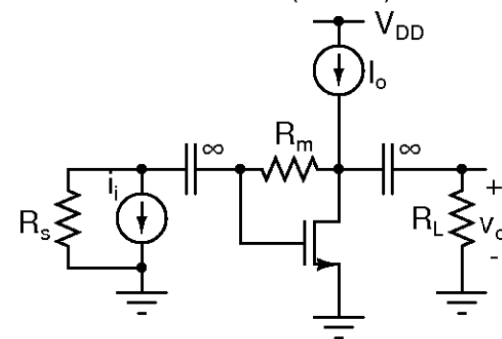


Common Source Amplifier

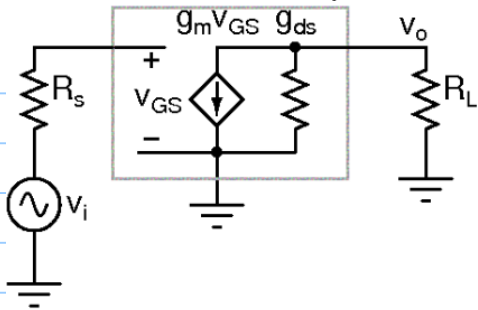

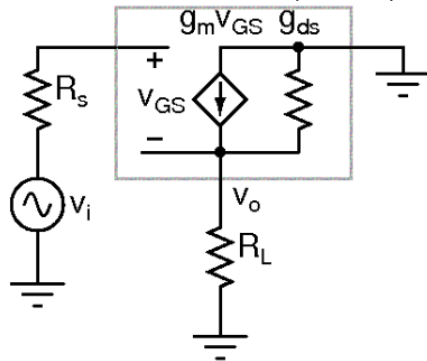
Common Drain Amplifier
Source Follower (VCVS)




Source Degeneration
(VCCS)

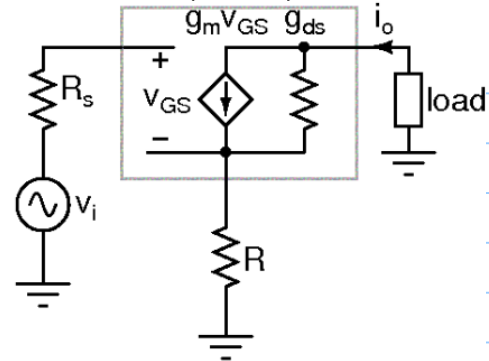


Common Gate Amplifier
(CCCS)

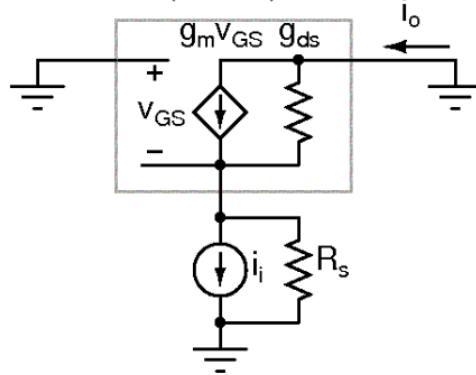


Drain Feedback Amplifier
(CCVS)

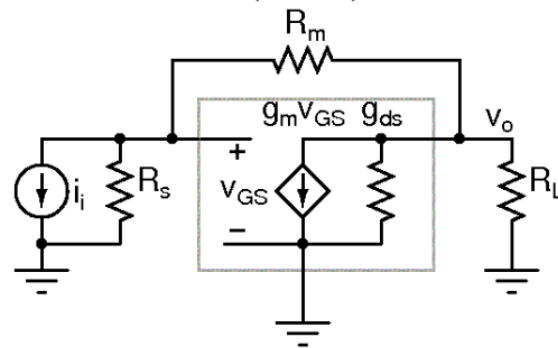


Common Source Amplifier

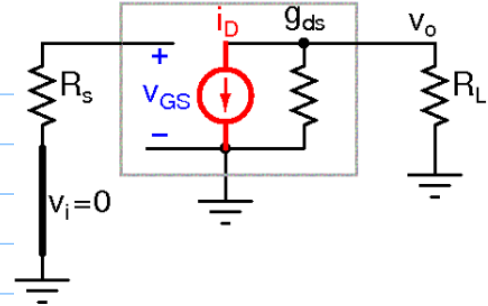

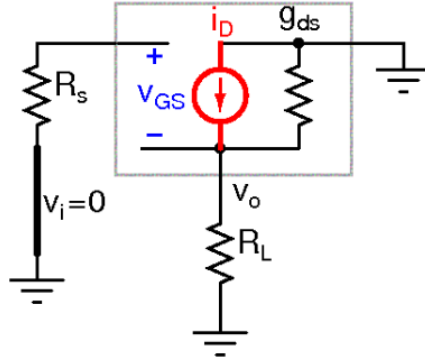
Common Drain Amplifier
Source Follower (VCVS)




Source Degeneration
(VCCS)

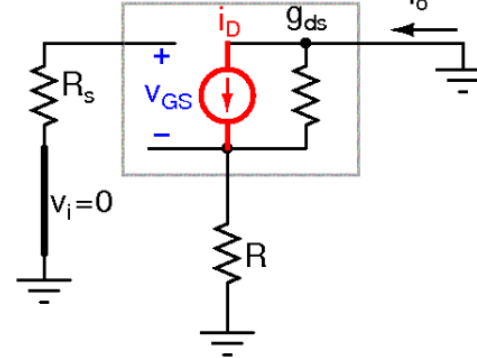

Common Gate Amplifier
(CCCS)

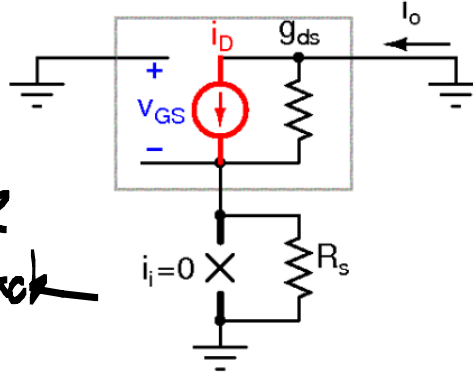

Drain Feedback Amplifier
(CCVS)

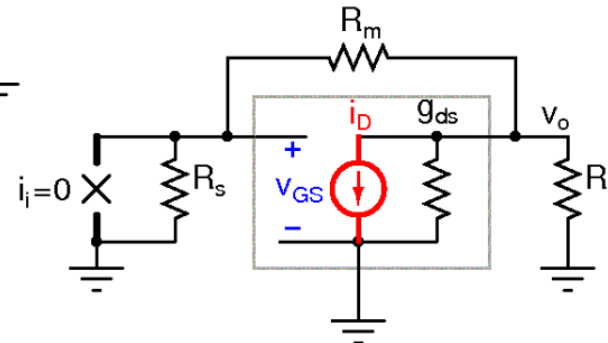


$$v_{as} = (\alpha) \cdot i_D$$

$\alpha \neq 0 \Rightarrow \text{feedback}$

$\alpha < 0 \Rightarrow \text{negative feedback}$

Amplifiers (or any other electronic circuit)

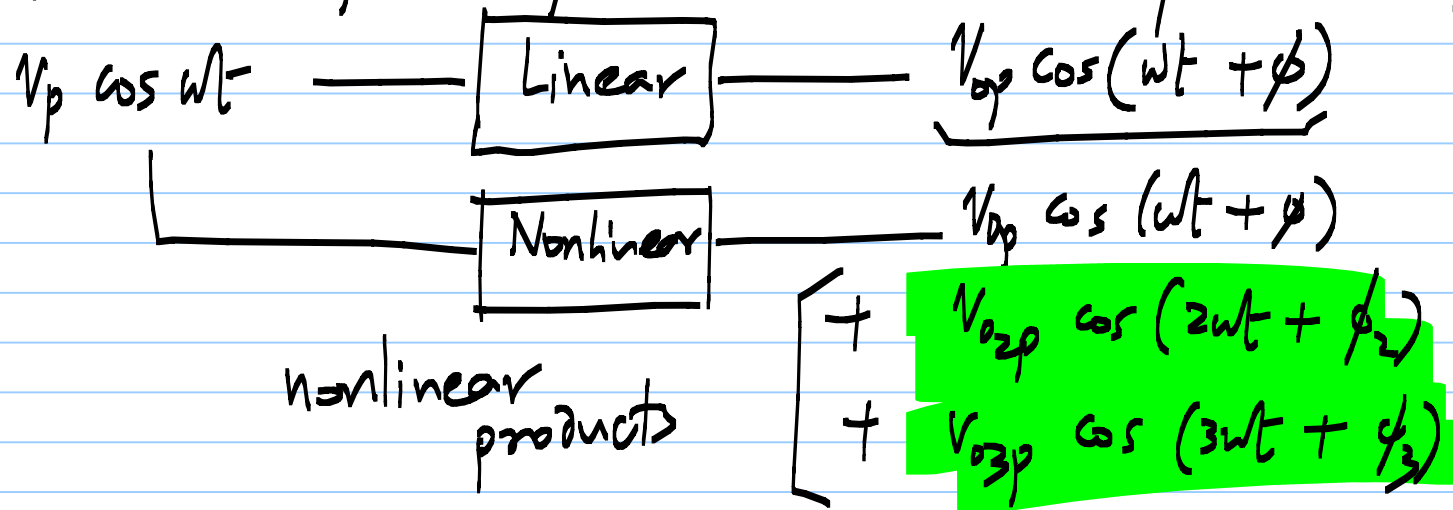* Maximum input amplitude is limited by nonlinearity



Swing limits of amplifiers

→ Limits on input (or output) such that transistors remain in saturation region

CS amplifier


$$\mu_n C_{ox} = 100 \mu A/V^2$$

$$W/L = 1$$


$$V_T = 1V$$

$$\frac{R_2}{R_1 + R_2} = \frac{4}{15}$$


$$-g_m (R_D || R_L) v_i$$

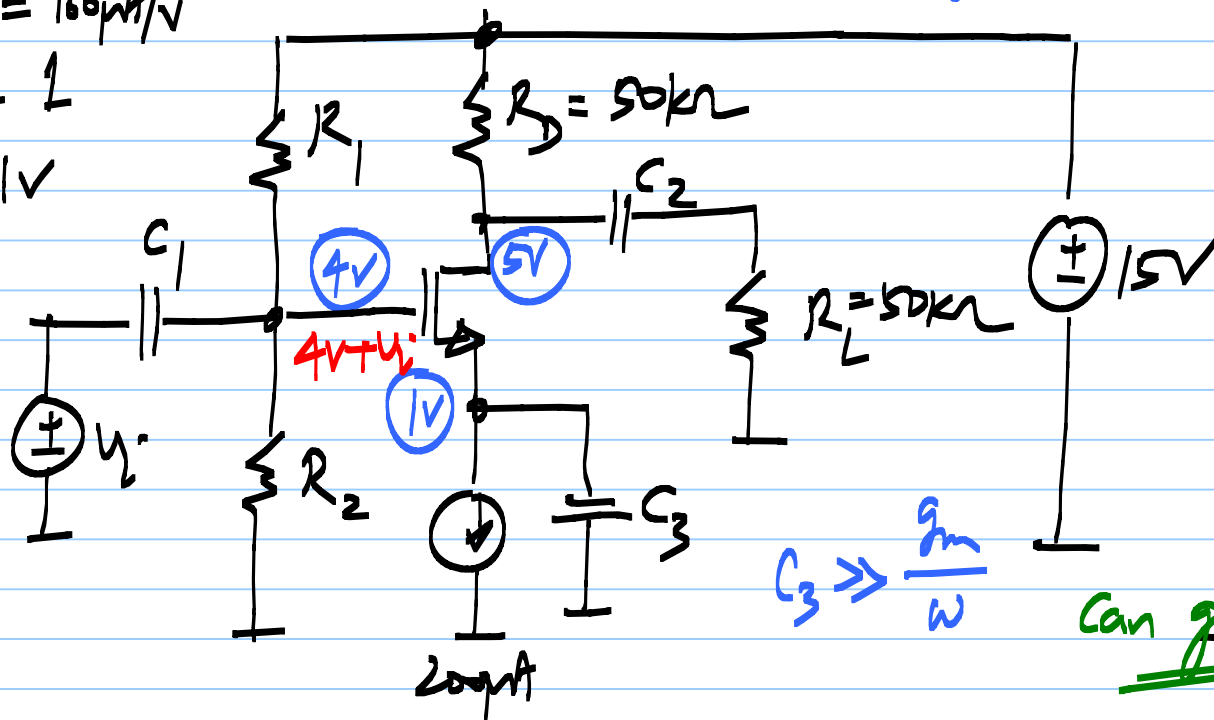

$$C_3 \gg \frac{g_m}{\omega}$$

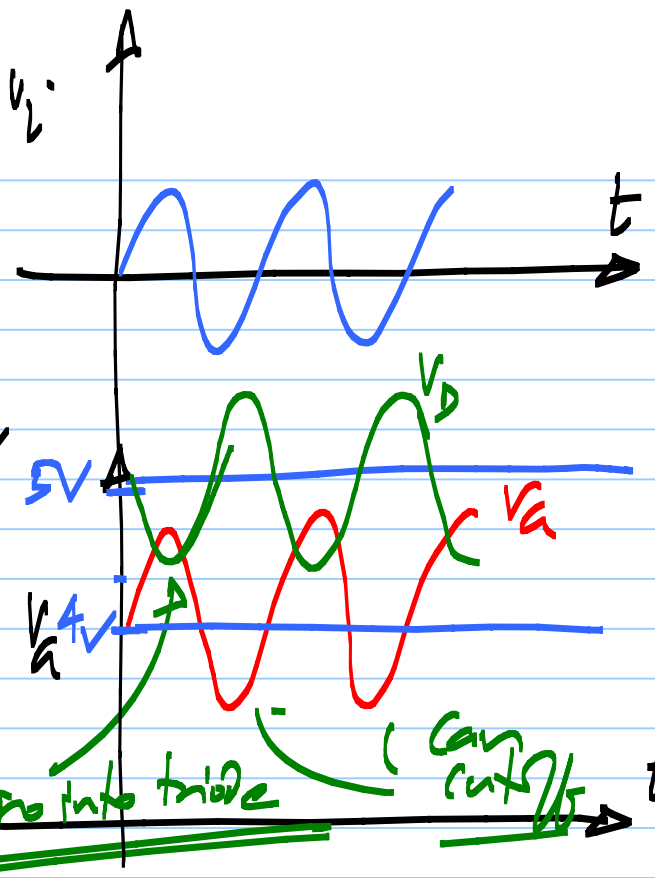

$$-200\mu S(25k\Omega) = -5$$

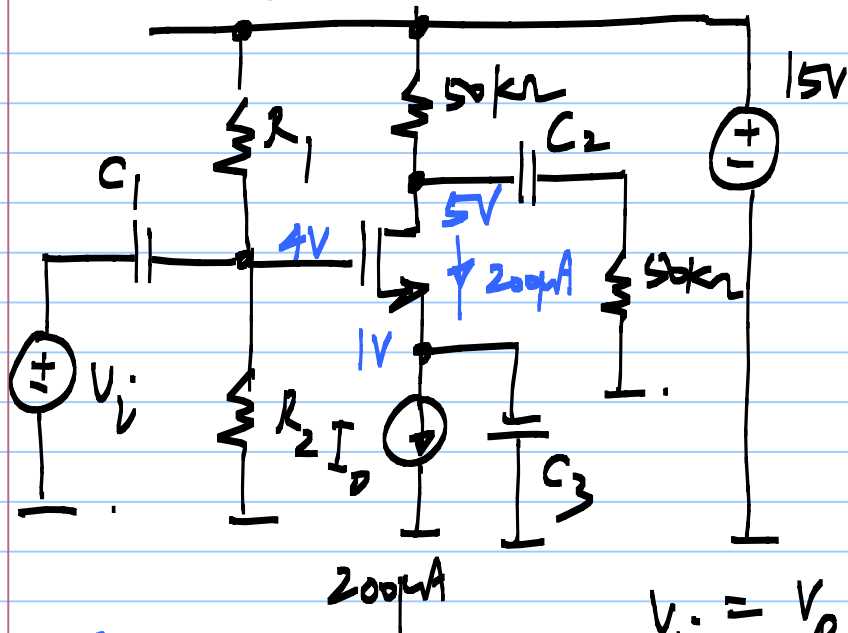

op. point

$$V_{GS0} = 3V \quad (+)$$

$$V_{DS0} = 4V \quad (+)$$

$$I_{D0} = 200\mu A \quad (+)$$

incremental quantities

$$v_{GS} = v_i$$

$$v_{DS} = -g_m(R_D || R_L)v_i = -5v_i$$


$$i_D = g_m v_i = 200\mu S \cdot v_i$$

$$-1V \leq v_i \leq \frac{1}{3}V$$

$$v_i = v_p \cos(\omega t)$$

$$v_p < \frac{1}{3}V$$

$$\frac{R_2}{R_1 + R_2} = \frac{4}{15}$$

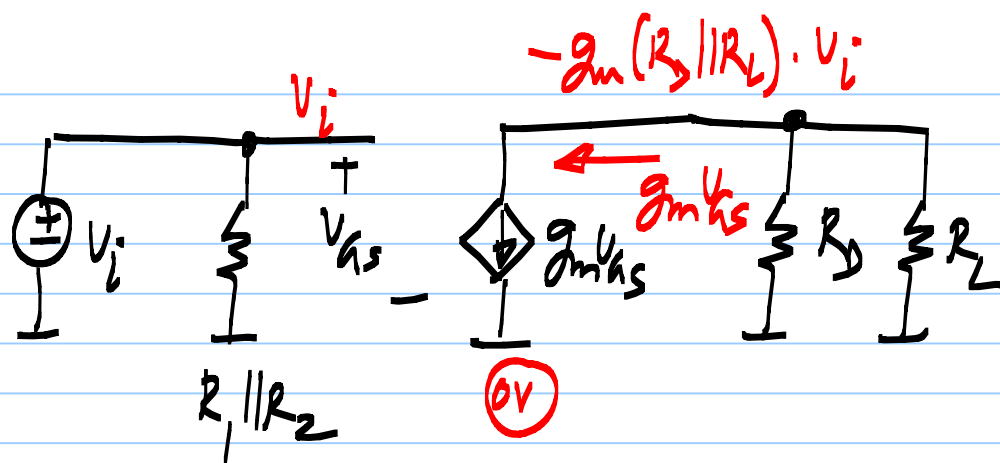

Total quantities:


$$V_{as,tot} = V_{as0} + v_i = 3V + v_i$$

$$V_{ds,tot} = V_{ds0} - g_m (R_D \parallel R_L) v_i = 4V - 5v_i$$

$$I_{D,tot} = I_{D0} + g_m v_i = 200\mu A + 200\mu S \cdot v_i$$

Limit imposed by the triode region:

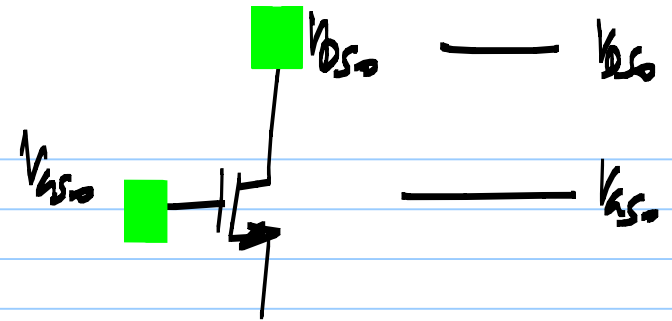In saturation if $V_{DS,tot} \geq V_{GS,tot} - V_T$



$$V_{DS0} - g_m (R_D || R_L) v_i \geq V_{GS0} + v_i - V_T$$

$$v_i \leq \frac{V_{DS0} - V_{GS0} + V_T}{1 + g_m (R_D || R_L)}$$

(Ensures that the transistor is)
in saturation

cut-off limit :

To avoid cut-off, $I_{D1} > 0$

$$I_{D0} + g_m V_i > 0$$

$$V_i > -\frac{I_{D0}}{g_m} ; V_i > -\frac{(V_{DS} - V_T)}{2}$$


$$g_m = \frac{2 \cdot I_{D0}}{(V_{DS} - V_T)}$$

Cutoff limit: $V_{AS} < V_T$

To avoid cutoff, $V_{AS, tot} > V_T$

$$V_{AS0} + V_i > V_T$$

$$V_i > -(V_{AS0} - V_T)$$

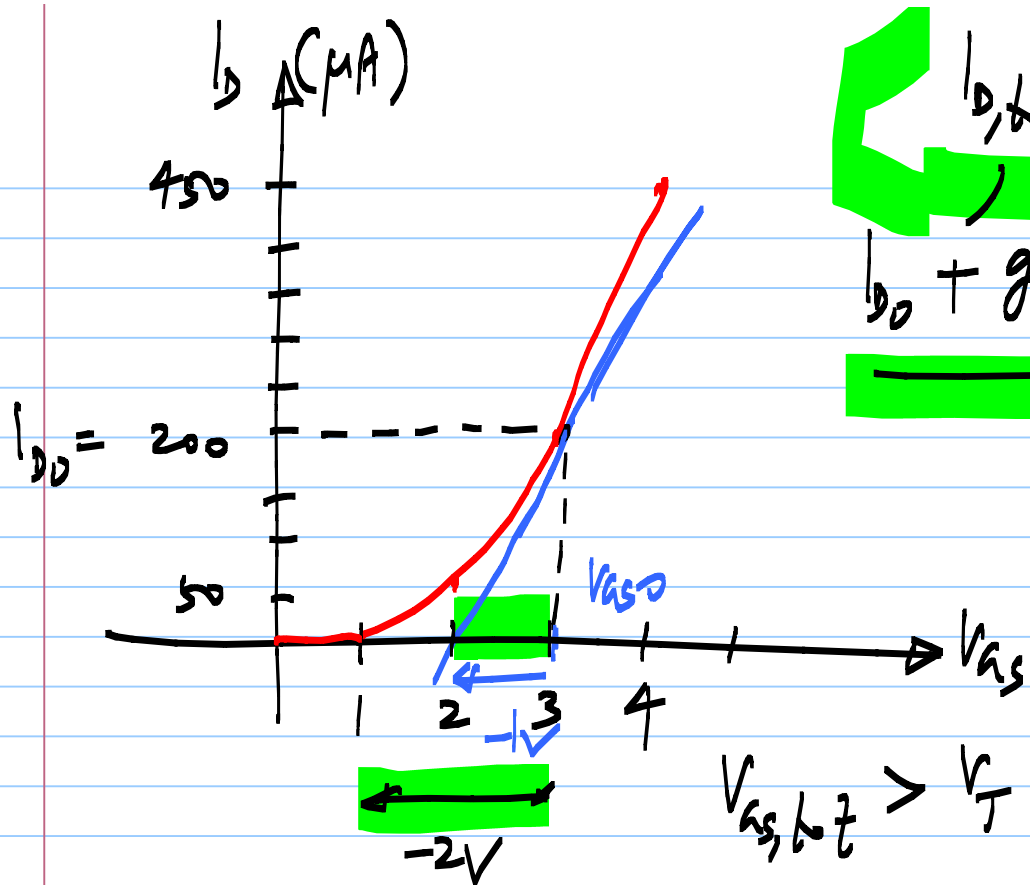

$$I_{D, tot} > 0$$

$$I_{D0} + g_m V_i$$

Triode region limit

in sat. region if $V_i \leq$

$$\frac{V_{DS0} - V_{GS0} + V_T}{1 + g_m(R_D \parallel R_L)} = \frac{4V - 3V + 1V}{1 + 5}$$


$$V_i \leq \frac{2}{6} = \frac{1}{3}V$$

Cutoff limit: $V_i \geq -\frac{I_{D0}}{g_m} = -\frac{200\mu A}{200\mu S} = -1V$ ✓

$$V_i \geq -\left(\underset{3V}{V_{GS0}} - \underset{1V}{V_T}\right) = -2V$$

CS amplifier using drain feedback
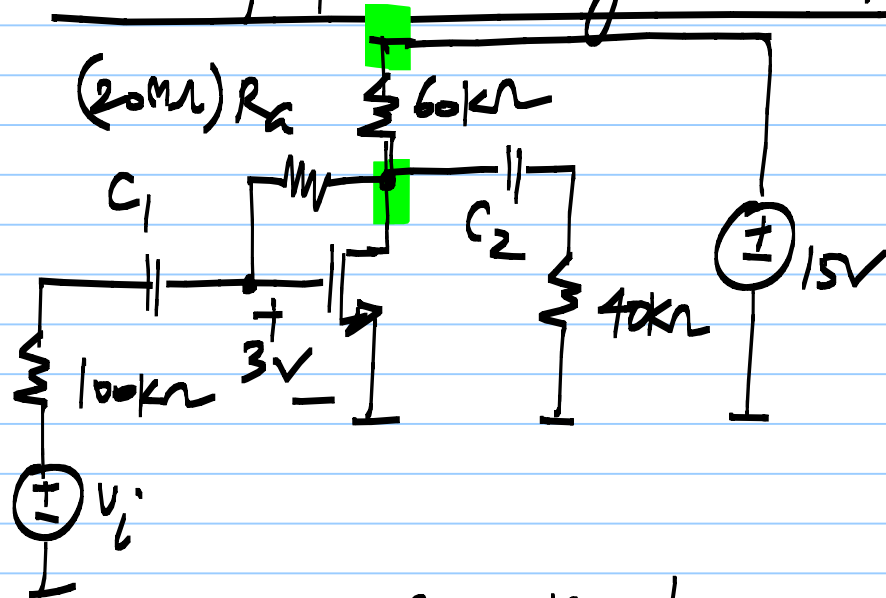
$$\begin{array}{c} +12V \\ \downarrow \\ \text{20mA} \\ \uparrow \\ - \end{array} \equiv \begin{array}{c} \downarrow \\ \frac{12V}{0.2mA} = 60k\Omega \\ \uparrow \end{array}$$



C_1, C_2, R_A : very large

Total
 V_{GS}, V_{DS}, I_D
 op. point
 +
 increment


$$V_{GS, TOT} \geq V_{GS, TOT} - V_T$$

$$V_{DS, TOT} \geq V_{GS, TOT} - V_T$$

$$\mu_n C_{ox} = 100 \mu A/V^2$$

$$V_T = 1V$$

$$W/L = 1$$

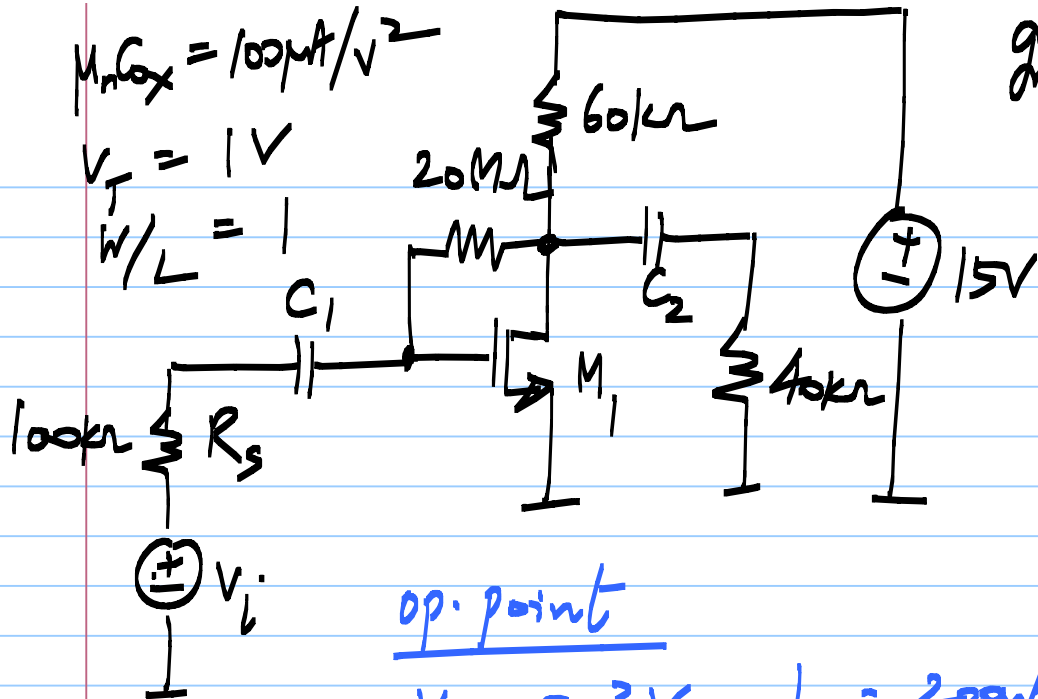


op. point

$$V_{GS0} = 3V, \quad I_{D0} = 200 \mu A$$

$$V_{DS0} = 3V$$

$$g_m = 200 \mu S$$

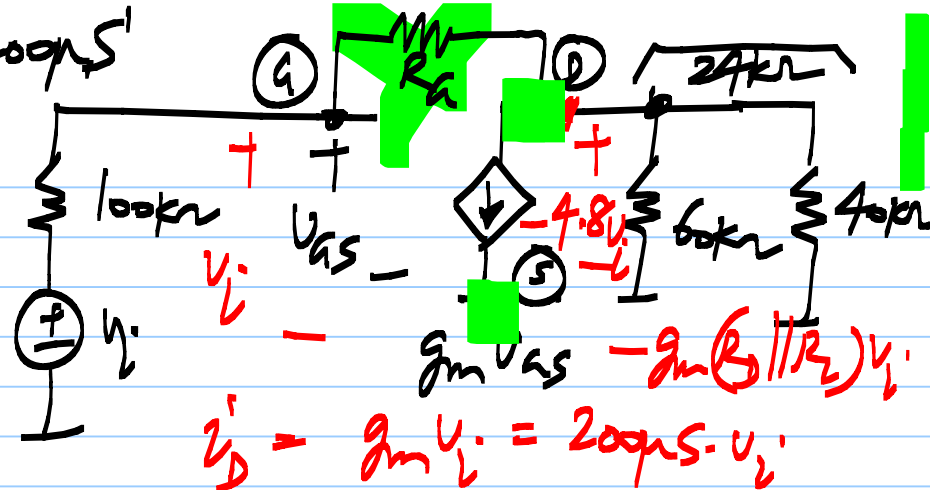

increment

$$v_{GS} = v_i, \quad i_D = 200 \mu S \cdot v_i$$

$$v_{DS} = -4.8 v_i$$

Total:

$$V_{as,tot} = 3V + V_i$$

$$V_{ds,tot} = 3V - 4.8V_i$$

$$i_{D,tot} = 200\mu A + 200\mu S \cdot V_i$$

To prevent M_1 from going into triode region,

$$V_{ds,tot} > V_{as,tot} - V_T$$

$$V_{ds0} + g_m(R \parallel R_L) V_i > V_{as0} + V_i - V_T$$

$$V_i < \frac{V_{ds0} - V_{as0} + V_T}{1 + g_m(R \parallel R_L)}$$

$$V_i < \frac{1V}{5.8} = \underline{0.17V}$$

To prevent cut-off of M_1 ($V_{ds,tot} > V_T$)


$$v_{d,tot} > 0$$

$$I_{D0} + g_m v_i > 0$$

$$v_i > -\frac{I_{D0}}{g_m} = \frac{-200 \mu A}{200 \mu S} = -1V$$

$$\frac{-1V < v_i \leq 0.17V}{\text{cut-off} \quad \text{Triode}}$$

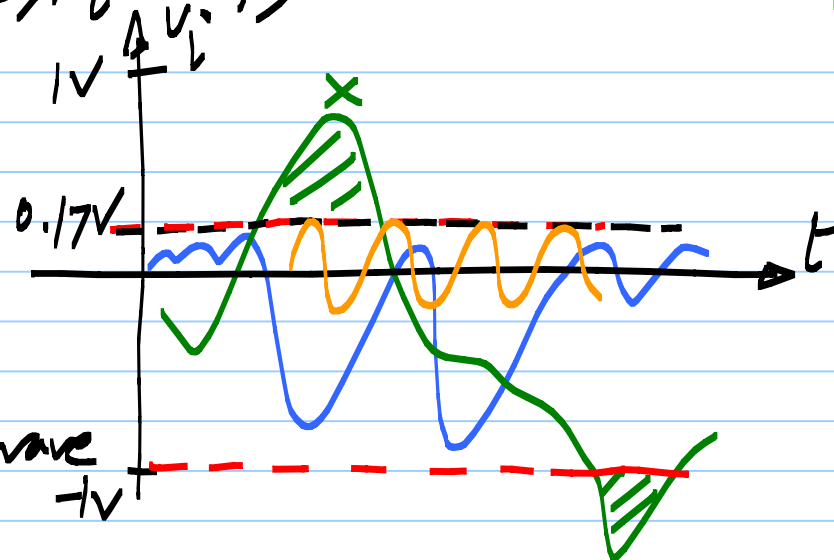Max. Sine wave
amplitude
 $\approx 0.17V$



$$v_o = -4.8v_i$$


$$-1V \leq v_i \leq 0.17V$$

noise


$$-0.83V \leq v_o \leq 4.8V$$

cut off

$$V_i = 0.17V$$

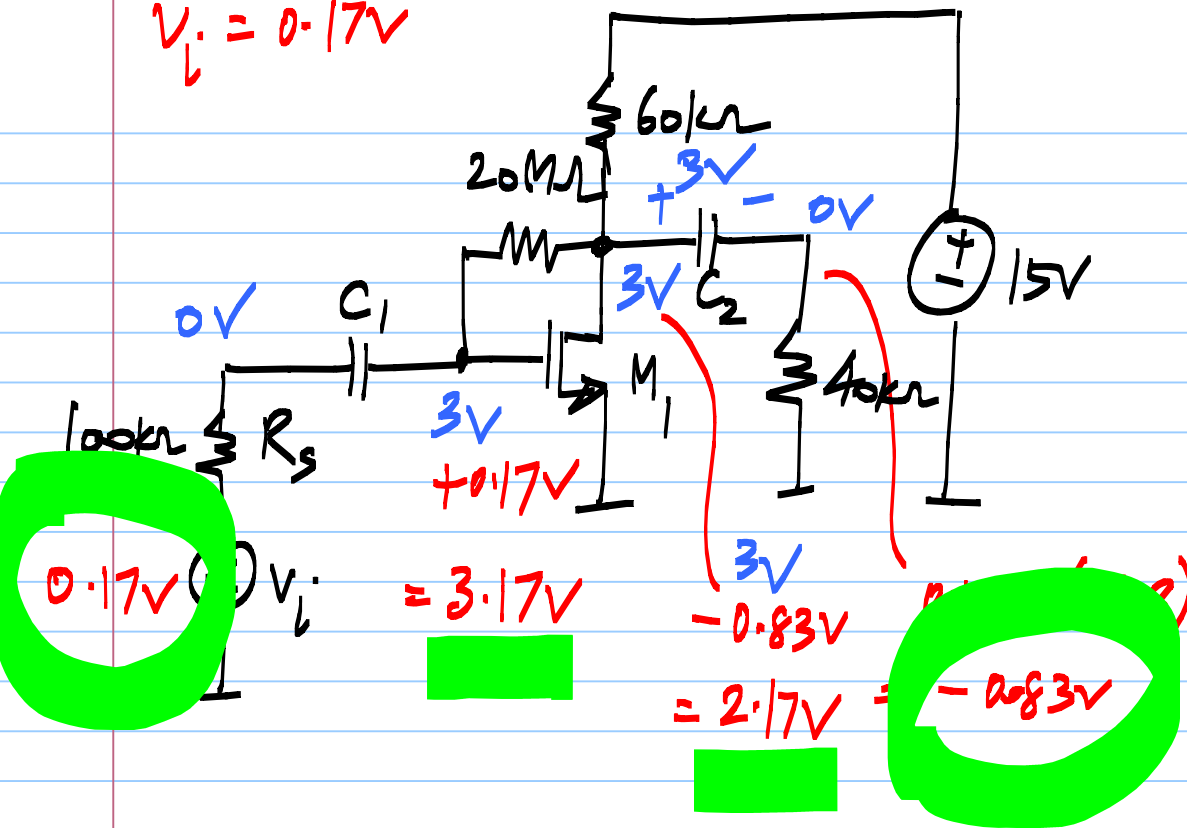


Cut-off limit:

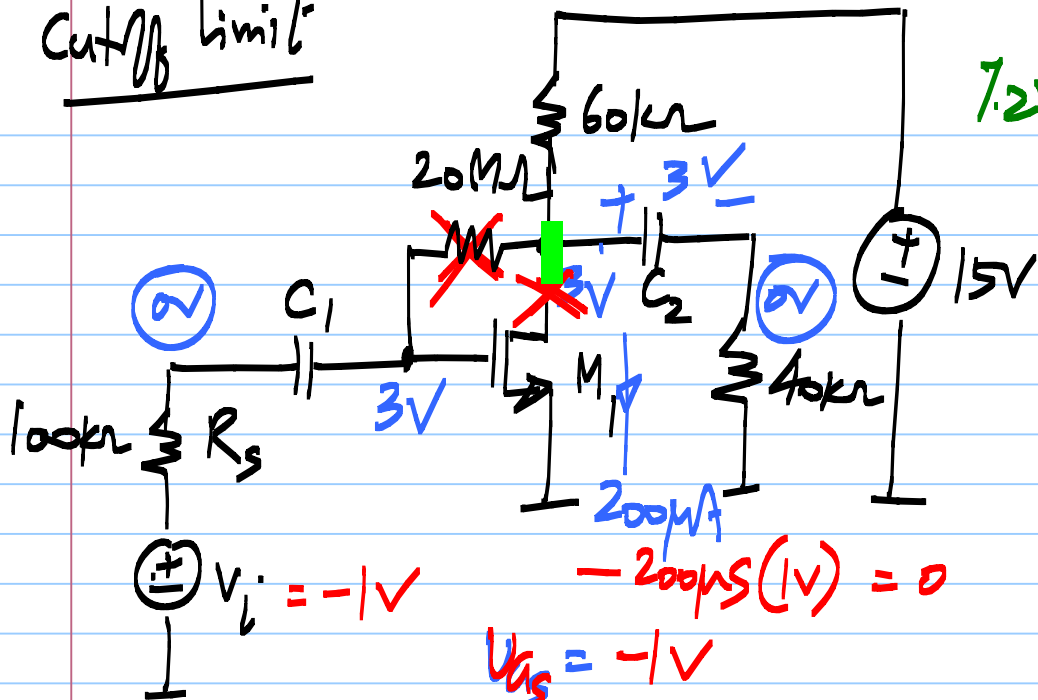

$$-200pS(1V) = 0$$

$$V_{GS} = -1V$$

$$g_m V_{GS} = 200pS(-1V)$$

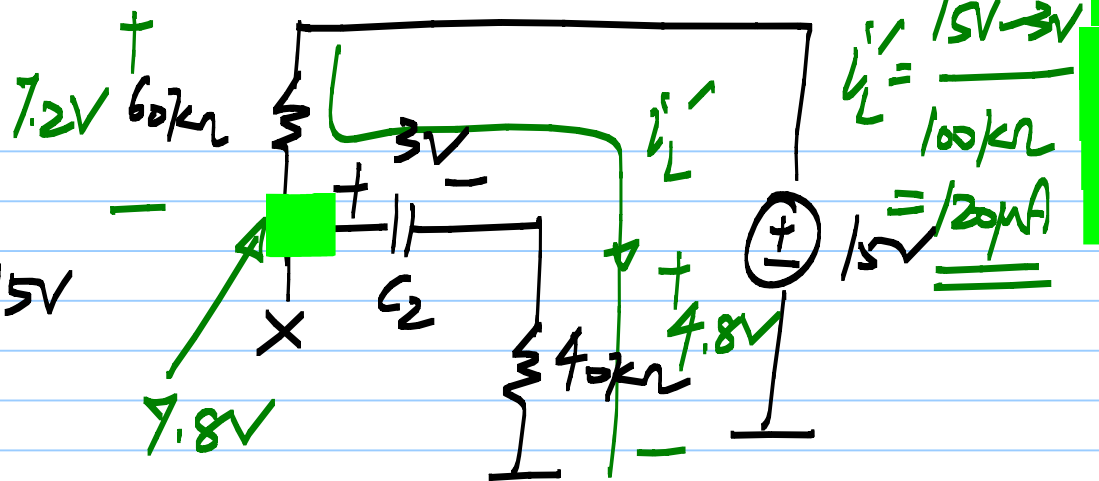

$$3V + 4.8V = 7.8V$$

$$i_L' = \frac{15V - 3V}{100k\Omega} = 120\mu A$$

Swing limit calculation Summary.

* Evaluate $V_{GS,tot}$, $V_{DS,tot}$ & $i_{D,tot}$

* $t_{ot} = \text{op. point} + \underbrace{\text{incremental}}_{\substack{\text{s.s linear eq.} \\ \text{ckt}}}$

* Apply triode & cut-off limits
in terms of v_i or v_o

Circuits with multiple transistors

* Calculate triode/cutoff limit for one transistor at a time

$$M_1, -1.5V \leq v_i \leq \underline{0.5V}$$

$$M_2, \underline{-0.75V} \leq v_i \leq 1V$$

$$\underline{-0.75V} \leq v_i \leq \underline{0.5V}$$