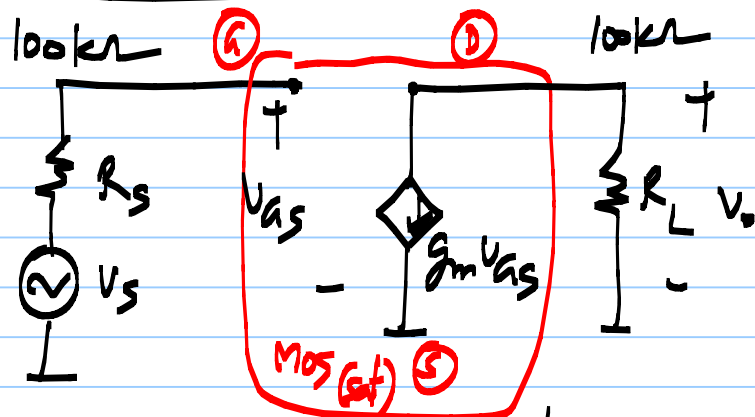


## Two-port amplifier

$$\left. \begin{aligned} \mu_n C_{ox} &= 100 \mu\text{A}/\text{V}^2 \\ W/L &= 1 \end{aligned} \right\} K_n = 100 \mu\text{A}/\text{V}^2, \quad V_T = 1\text{V}$$



$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)$$






$$\Rightarrow V_{GS} - V_T = 2\text{V} \Rightarrow$$


$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2$$


$$V_o = (-g_m R_L) V_S \quad |A_v| = 20$$

$$\underbrace{-20}_{-20} = -g_m R_L \quad g_m = \frac{-20}{-100\text{k}\Omega} = 200 \mu\text{S}$$


$$V_{DSO} \geq V_{GS} - V_T \quad 2V$$

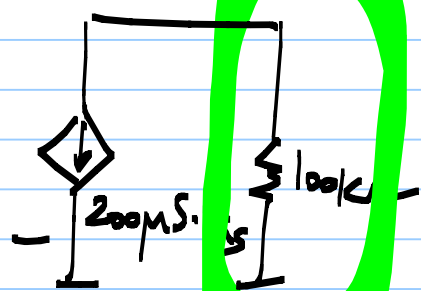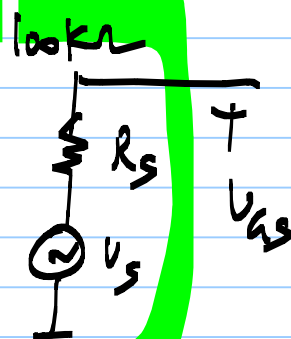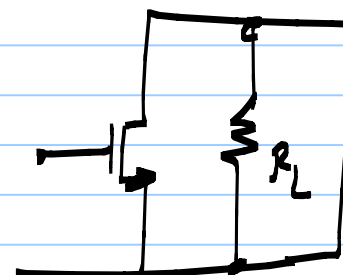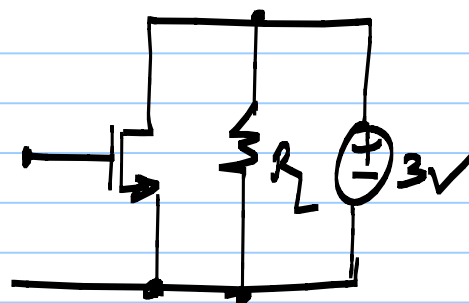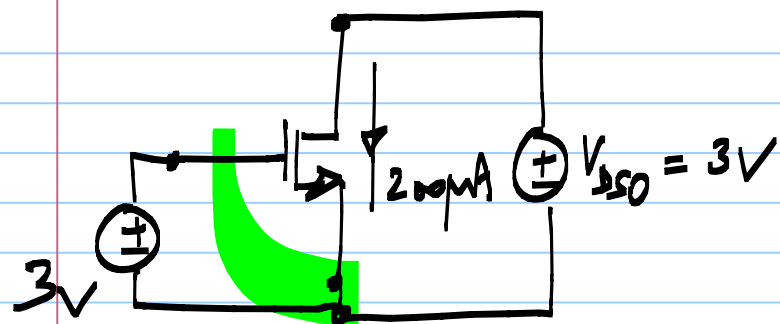


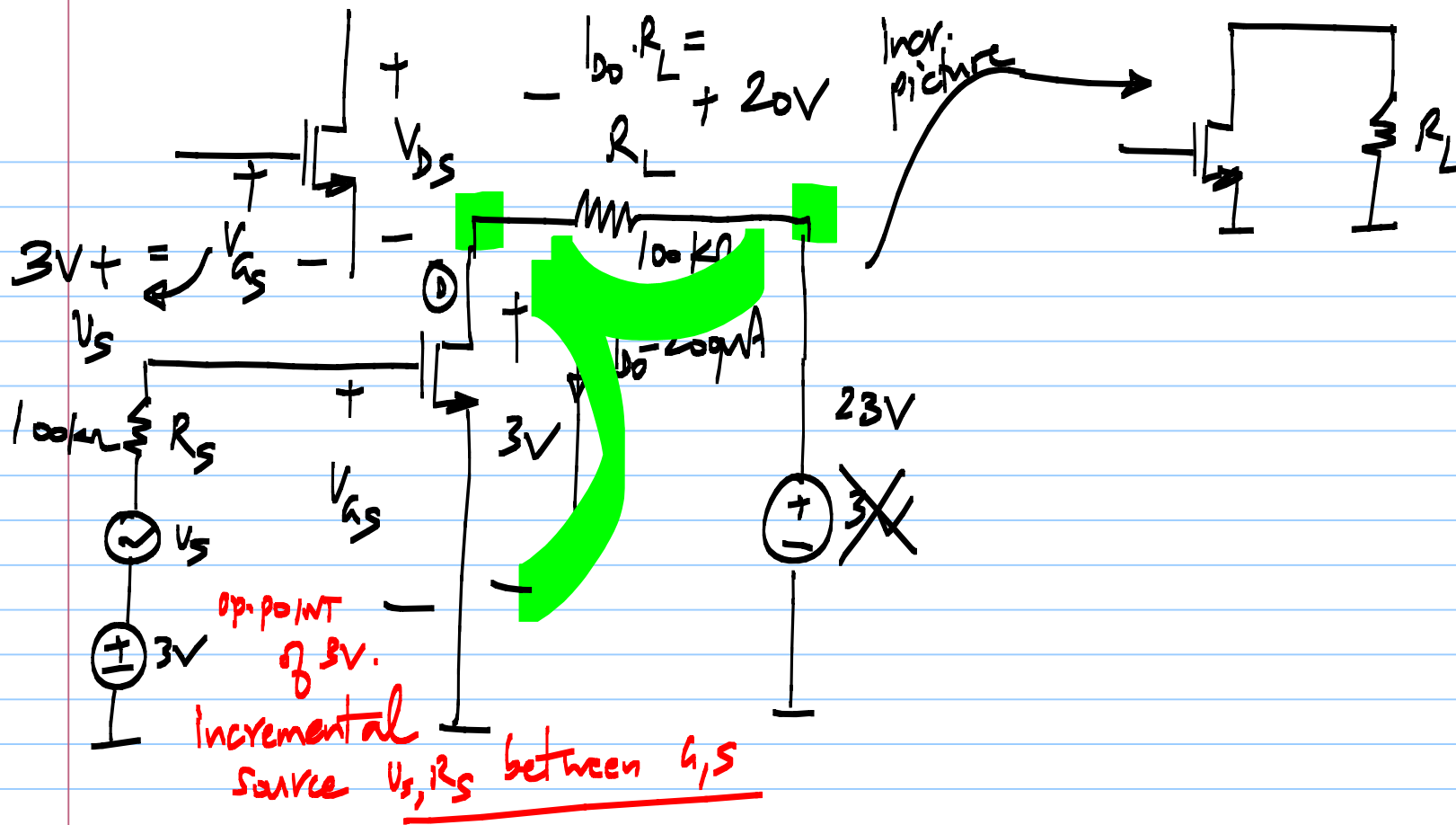


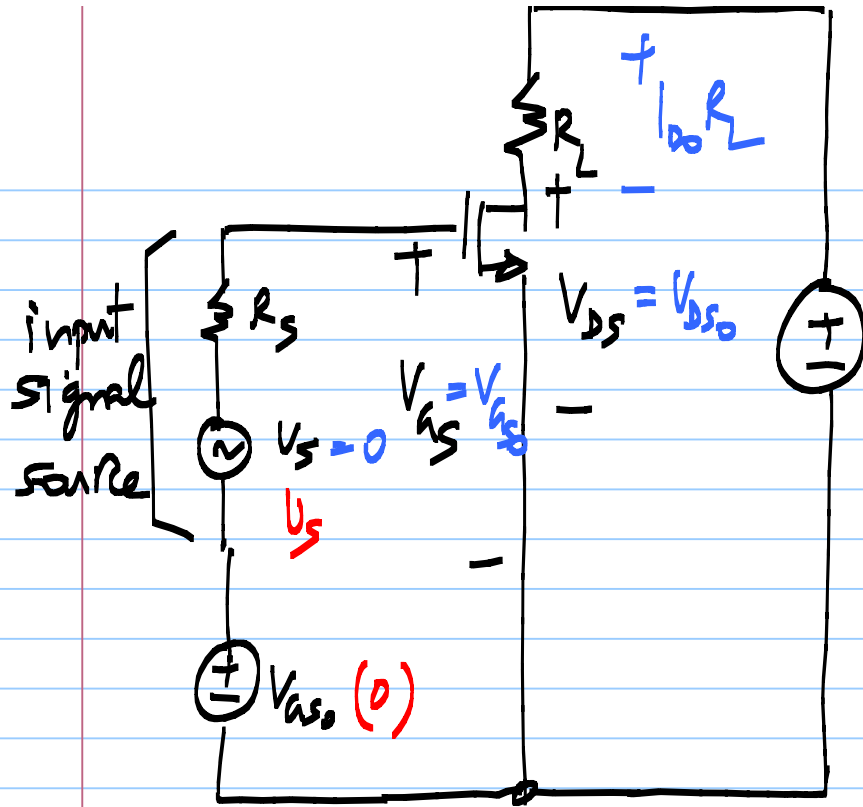



op. point  
incr. picture

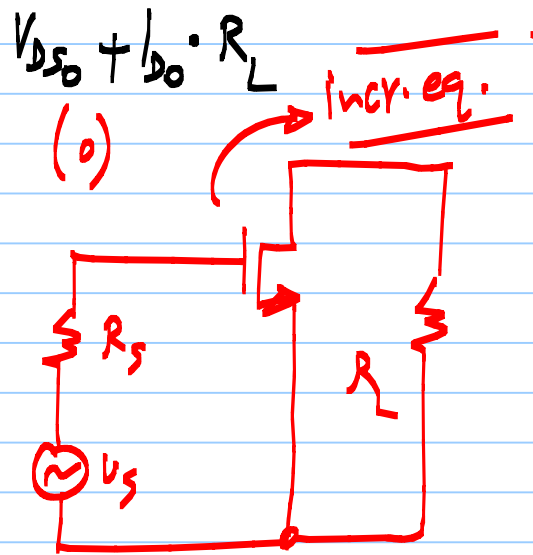

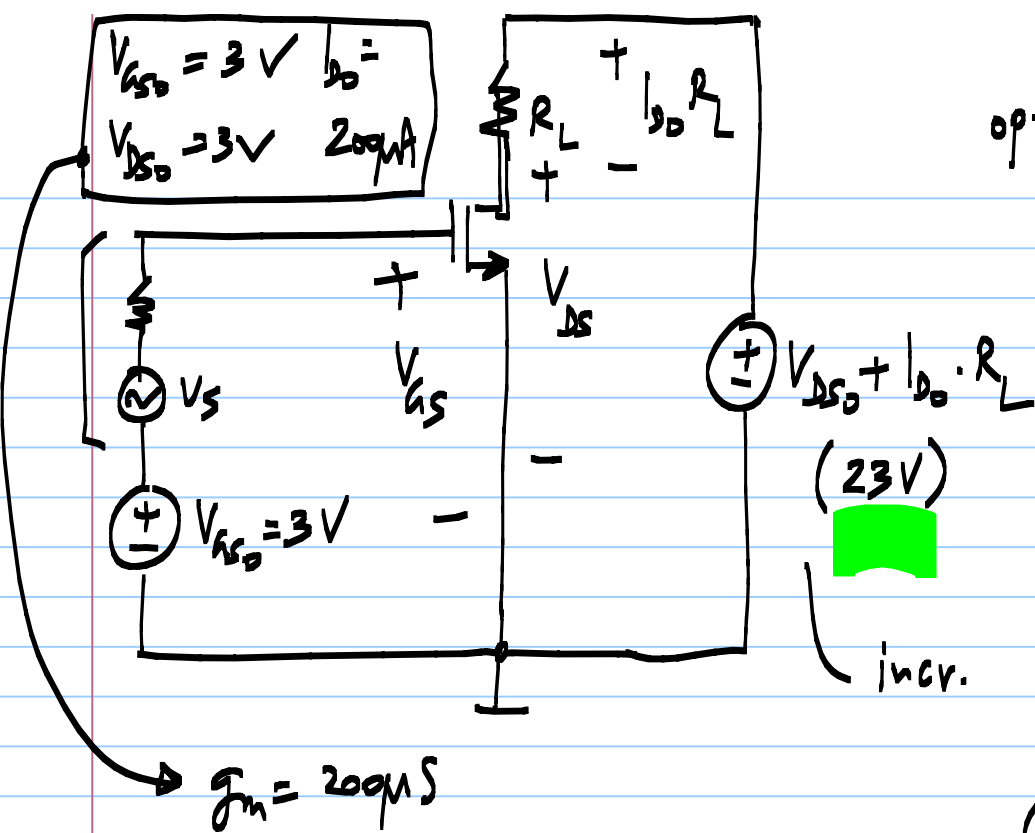


op. point

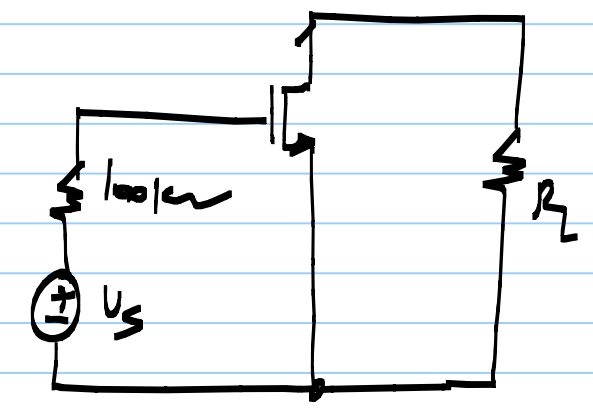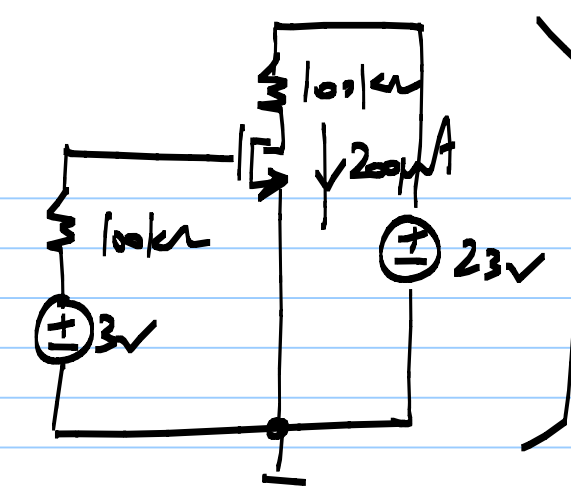


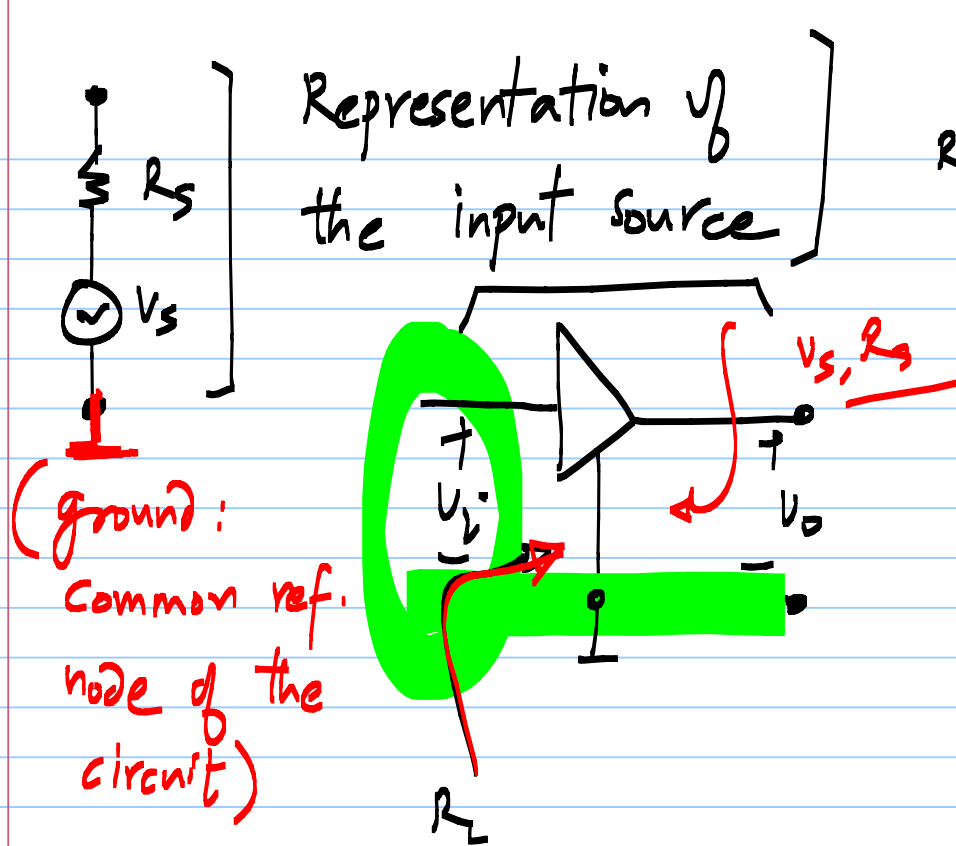


\* The source & load are not ground referenced  
 \* Needs multiple dc bias sources

23V, 3V

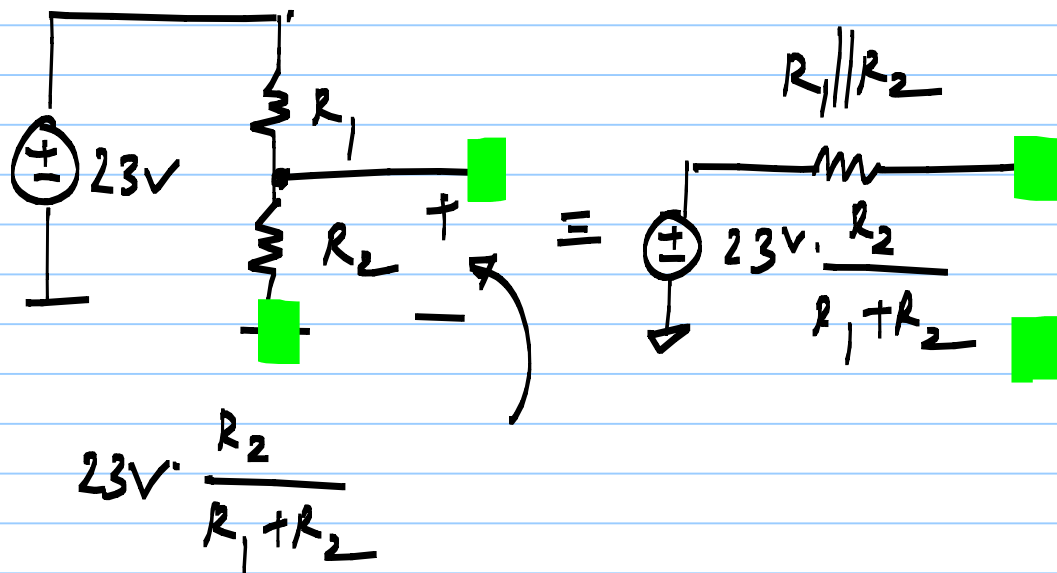

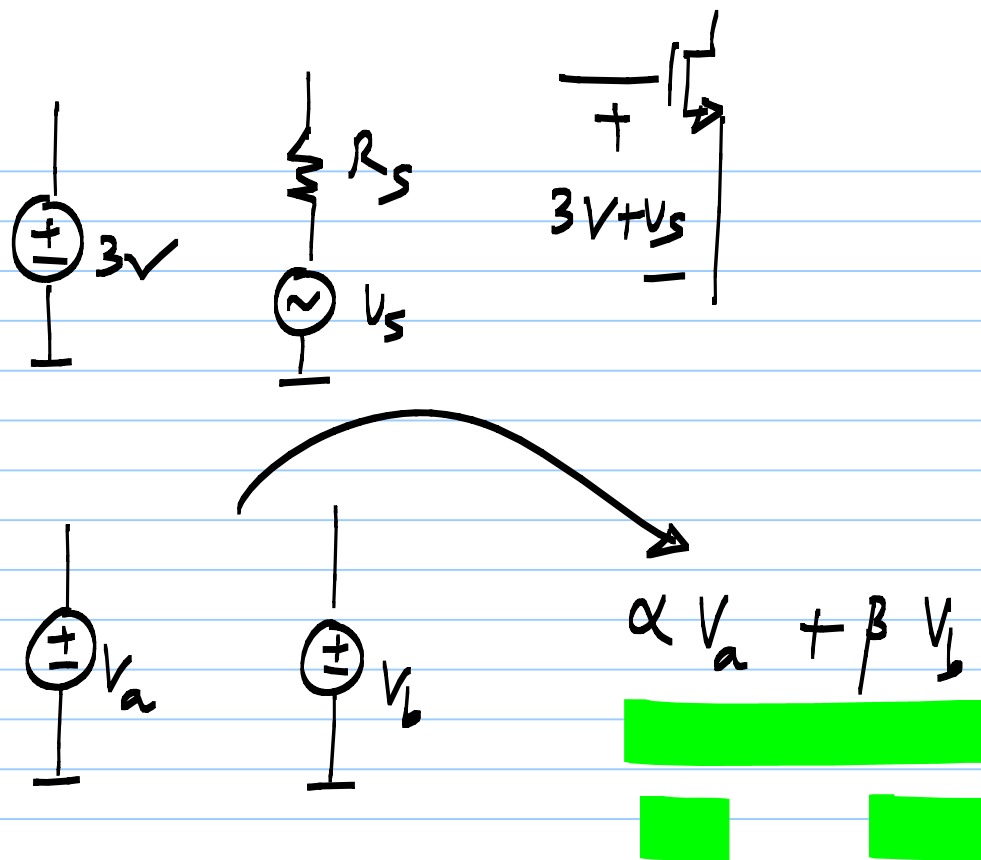

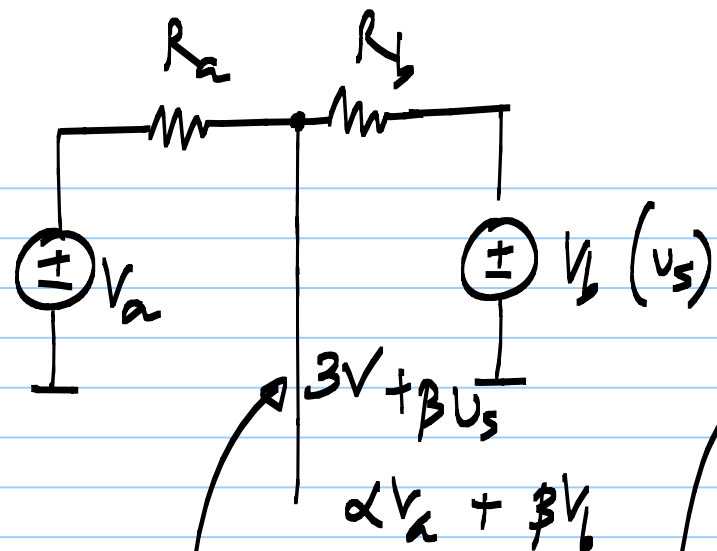


linear combination  
of  $V_a$  &  $V_b$

$$V_a \cdot \frac{R_b}{R_a + R_b} + V_b \cdot \frac{R_a}{R_a + R_b}$$

$V_a$ : dc bias

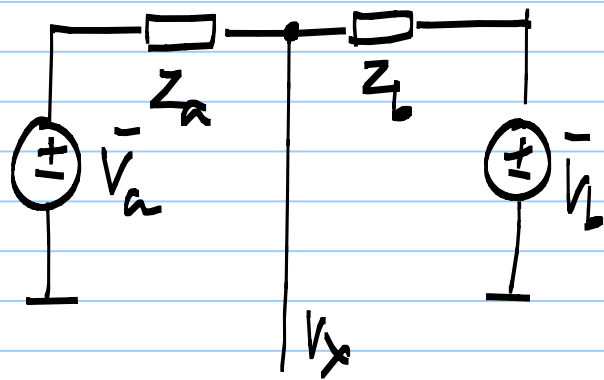
$V_b$ : signal - sinusoid of some frequency  $\omega_b > 0$



Sinusoidal steady state analysis  
(Phasor analysis)

$$\bar{V}_x = \bar{V}_a \cdot \frac{Z_b}{Z_a + Z_b} + \bar{V}_b \cdot \frac{Z_a}{Z_a + Z_b}$$

dc,  $\omega_0$

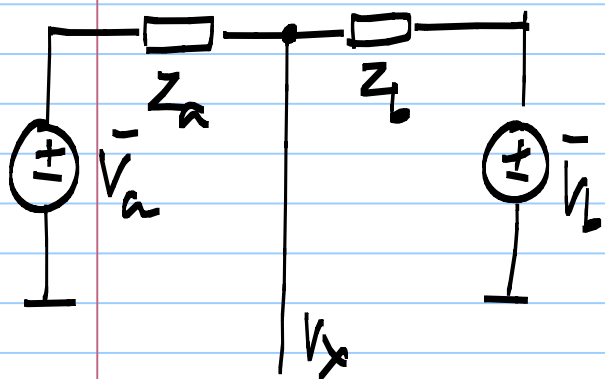

dc

$$\frac{\bar{V}_a \cdot \frac{Z_b(0)}{Z_a(0) + Z_b(0)} + 0}{\approx 1, Z_b(0) \gg Z_a(0)}$$


$\omega_0$

$$\frac{0 + \bar{V}_b \cdot \frac{Z_a(\omega_0)}{Z_a(\omega_0) + Z_b(\omega_0)}}{\approx 1, Z_a(\omega_0) \gg Z_b(\omega_0)}$$



$$\bar{V}_x = \bar{V}_a \cdot \frac{Z_b}{Z_a + Z_b} + \bar{V}_b \cdot \frac{Z_a}{Z_a + Z_b}$$

$$Z_b(0) \gg Z_a(0)$$

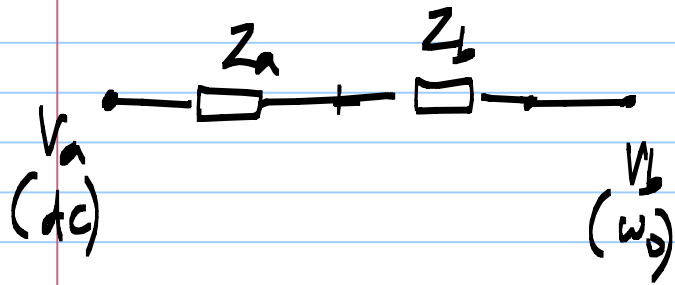
$$\Rightarrow Z_a(\omega_0) \gg Z_b(\omega_0)$$






|   | $Z_a$  | $Z_b$                                   |
|---|--|---|
| ① | $R$  | $C$<br>$\{R \gg \frac{1}{\omega_0 C}\}$ |
| ② | $L$<br>$\{\omega_0 L \gg R\}$                  | $R$                                     |
| ③ | $L$<br>$(\omega_0 L \gg \frac{1}{\omega_0 C})$ | $C$                                     |

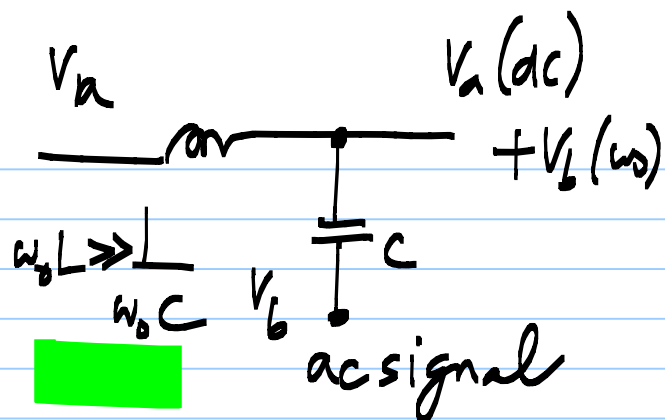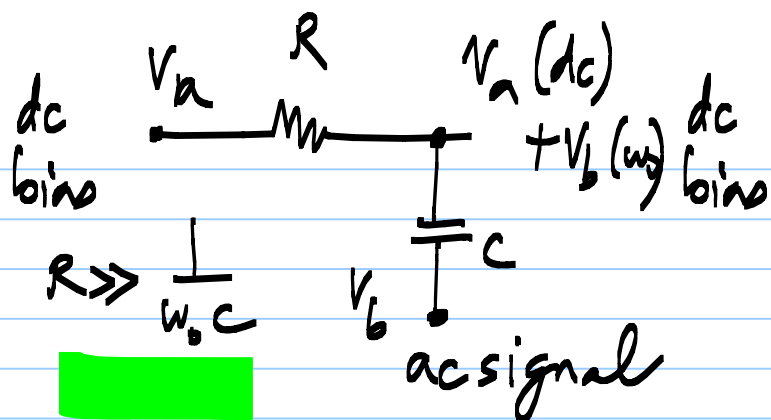


ac coupling networks

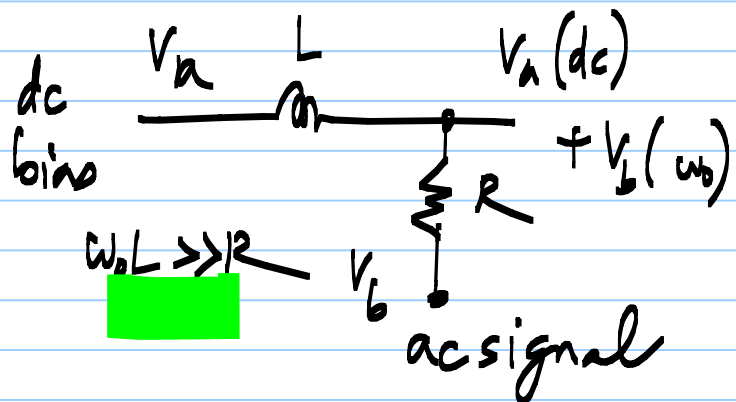


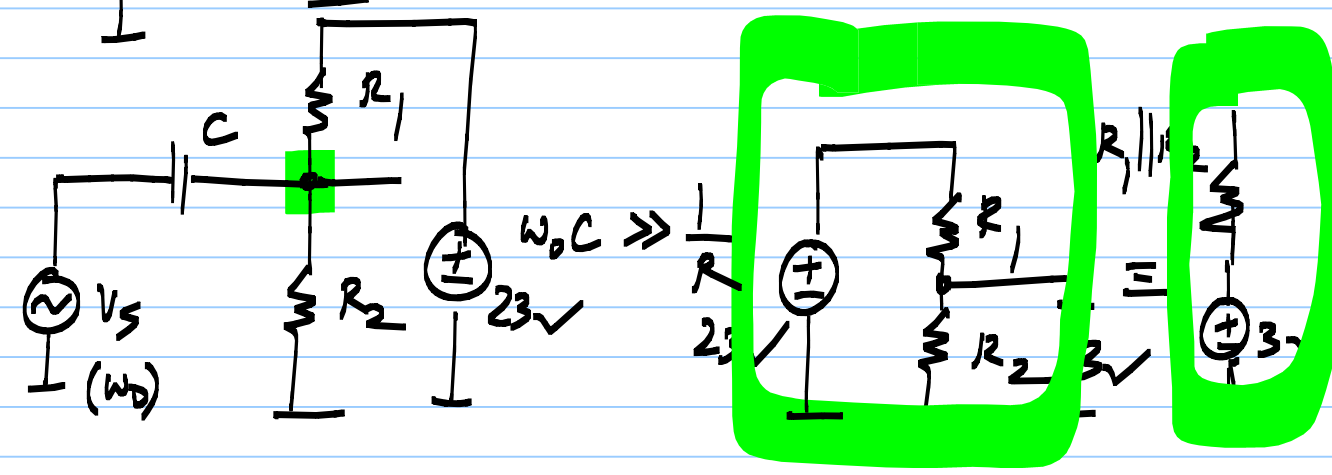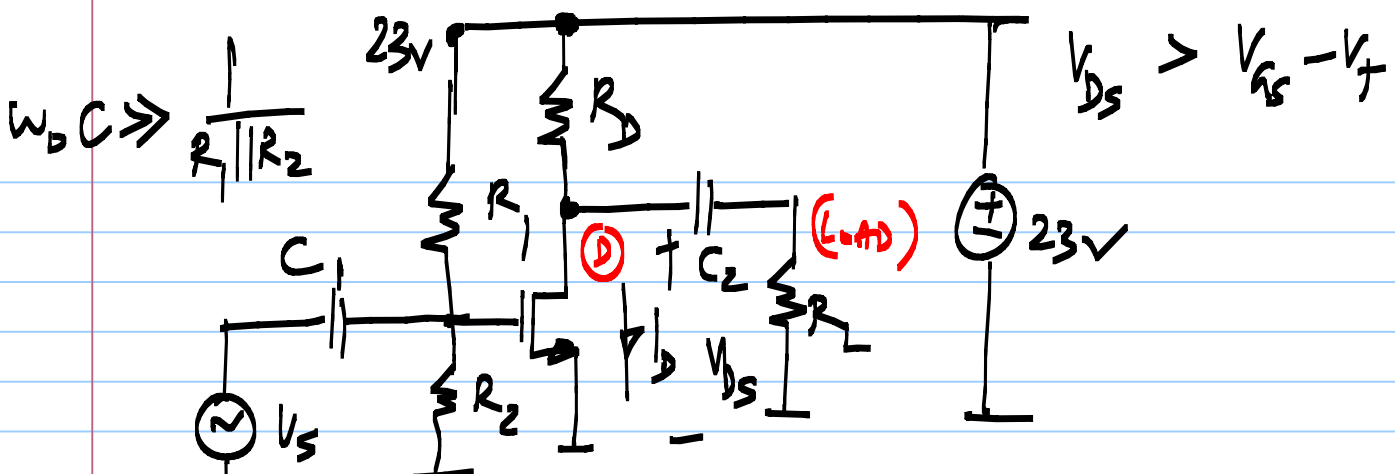


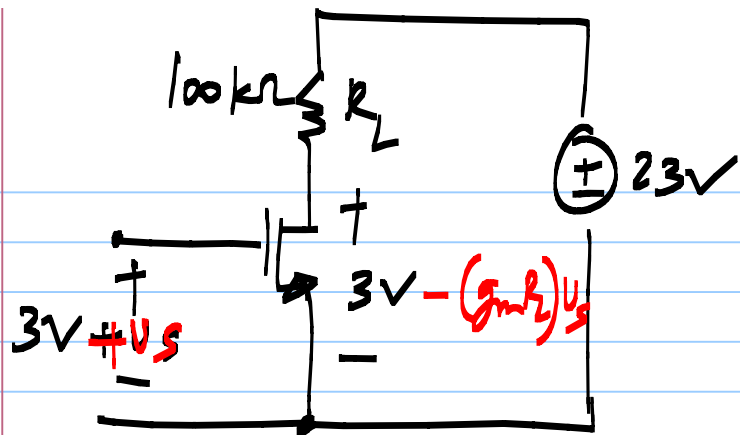


$$\frac{1}{\omega_0 C_2} \ll R_L$$

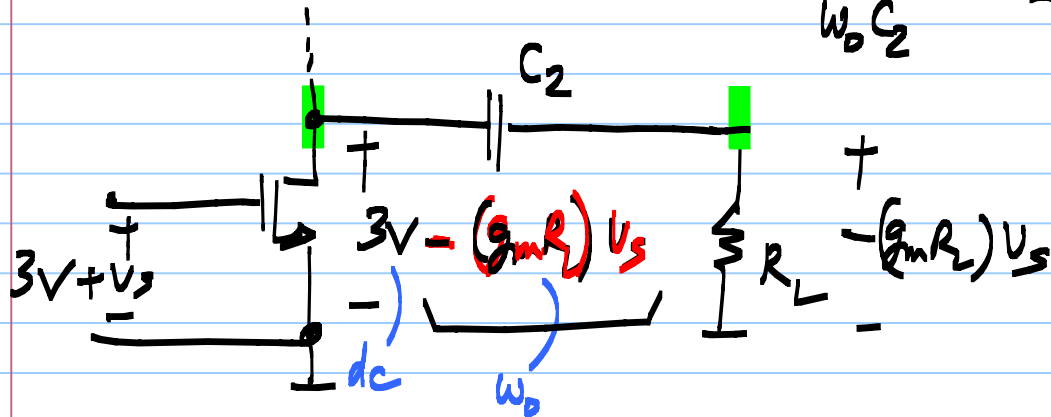


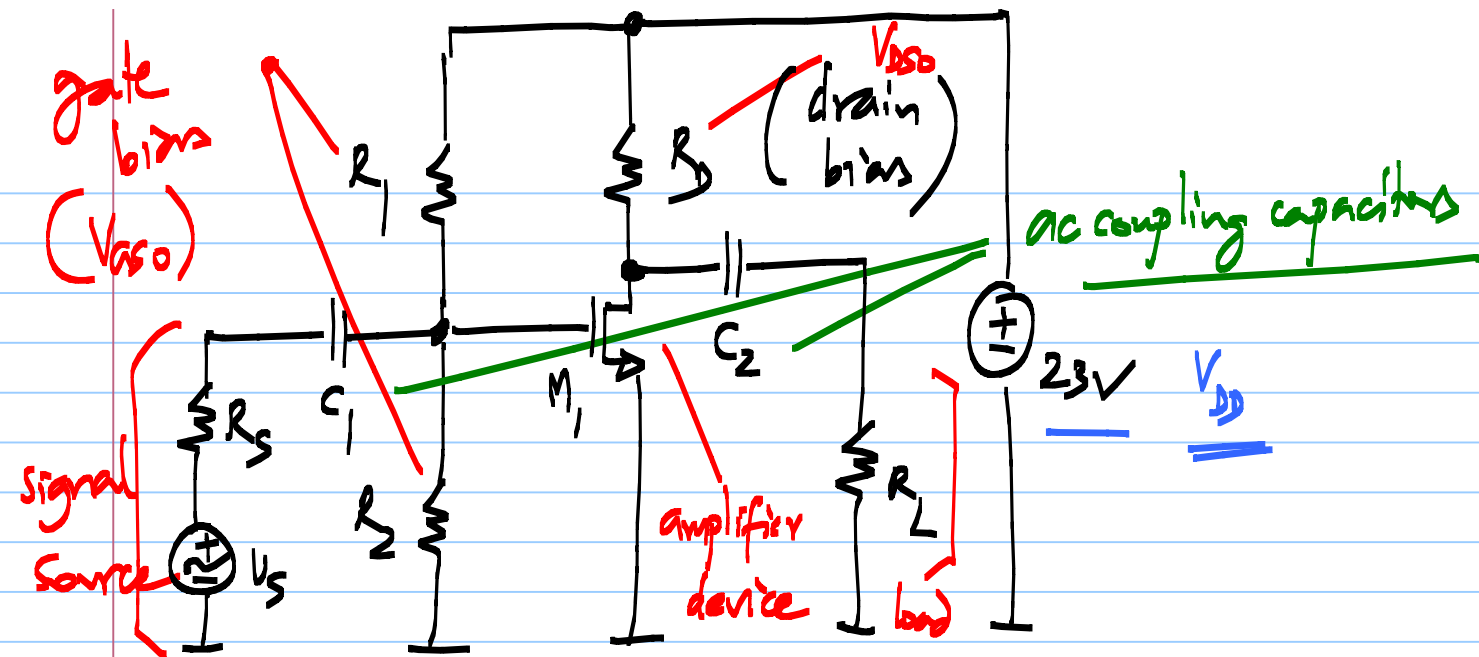

MOS common-source amplifier

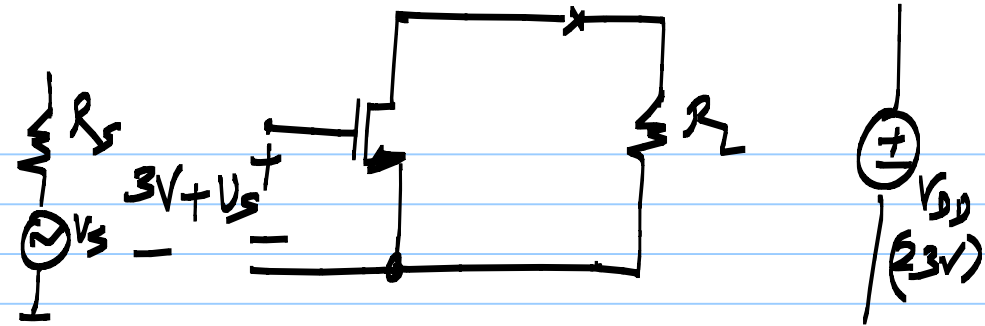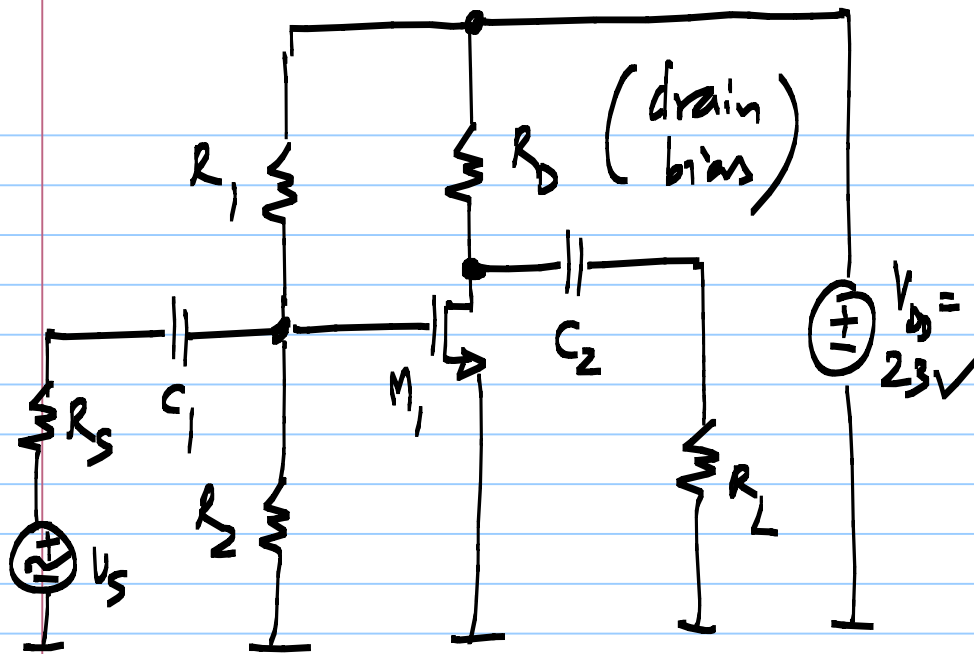

MOS common source amplifier

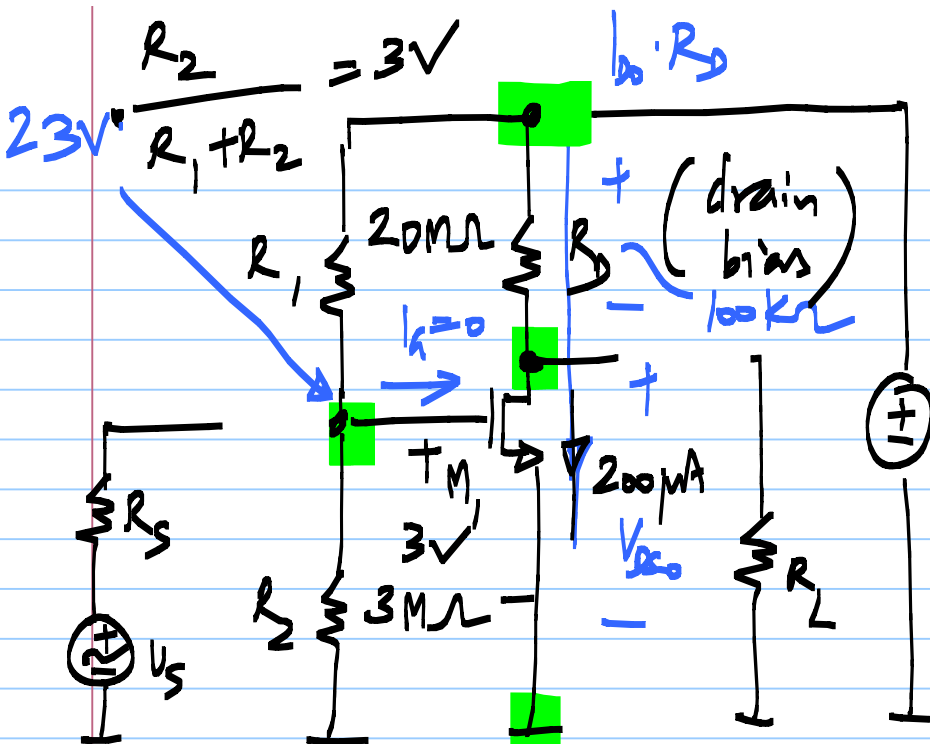

MOS common source amplifier

operating point (dc)  
open circuit capacitors  
short circuit inductors

$$V_{DS} = V_{DD} - I_{DQ} R_D = 3V$$

$$V_{GS} = 3V$$


$$V_{DS} = 3V$$

$$I_{DQ} = 200\mu A$$


$$K_n = \mu_n C_{ox} \frac{W}{L} = 100\mu A/V^2$$

$$V_T = 1V$$


# Incremental equivalent circuit

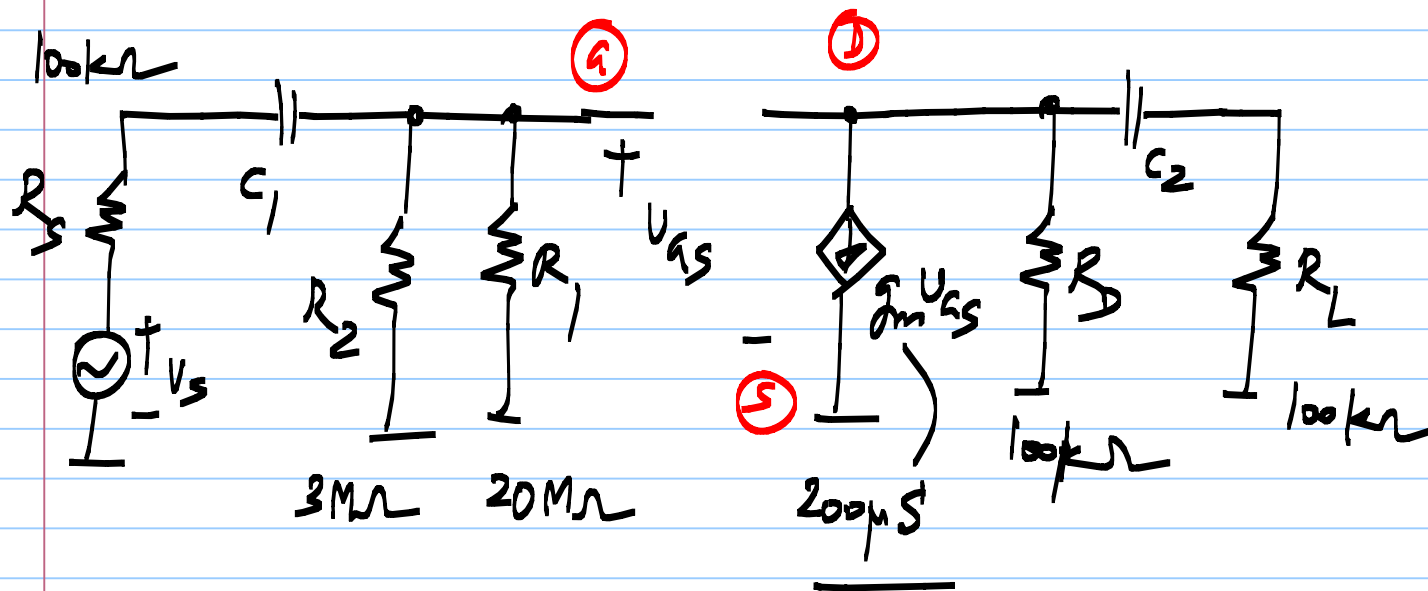

$w_0$

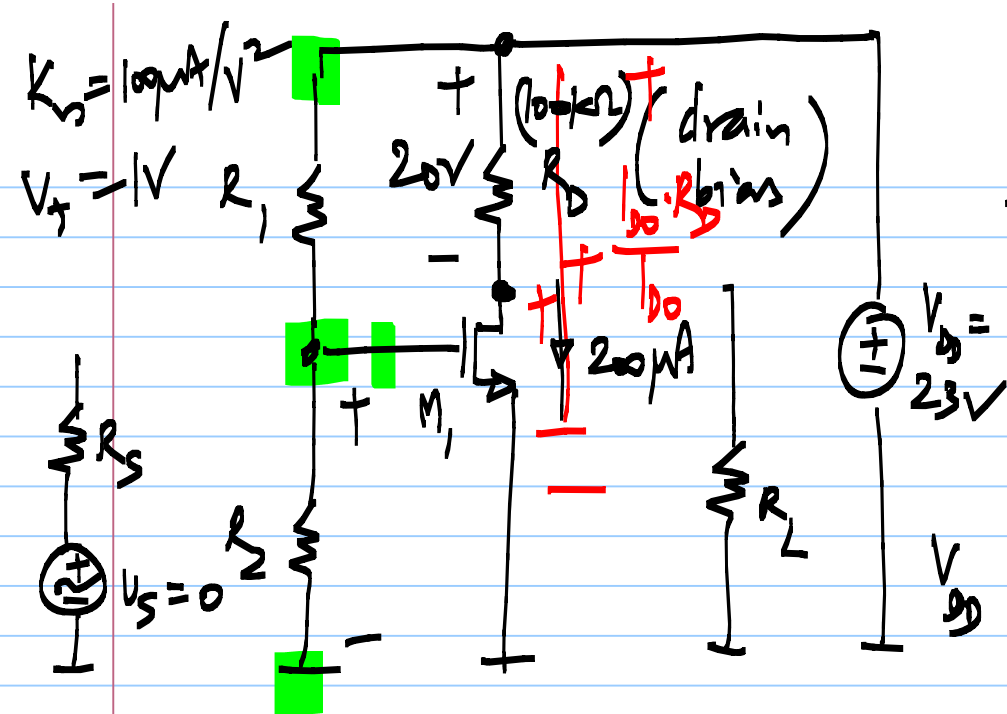


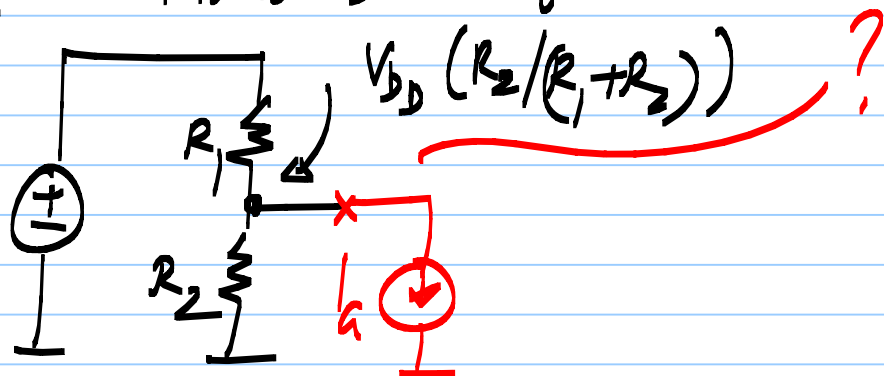dc operating point:  
 \* signal sources set to zero  
 \* capacitors open circuited  
 inductors short circuited



MOS common source amplifier
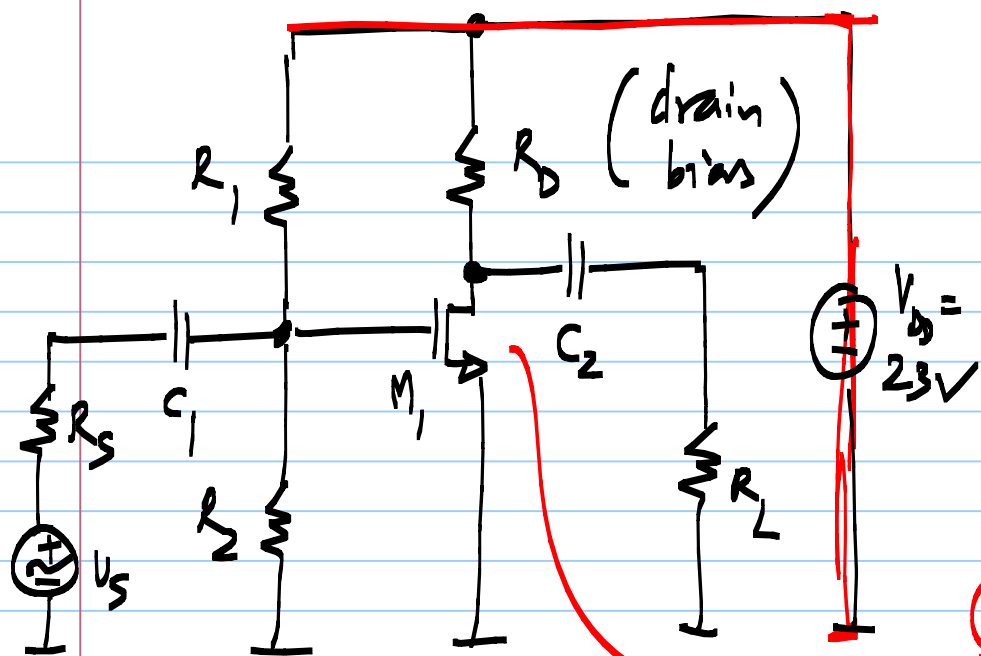
$$\checkmark V_{DS} (=3V) > V_{GS}(3V) - V_T(1V)$$




MOS common source amplifier

To obtain small-signal incremental eq. ckt,


\* Reduce fixed voltages & currents to zero

\* Replace nonlinear elements by small signal equivalents

\* Linear elements don't change

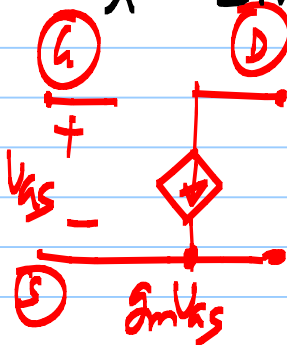

# Small signal incremental eq. circuit

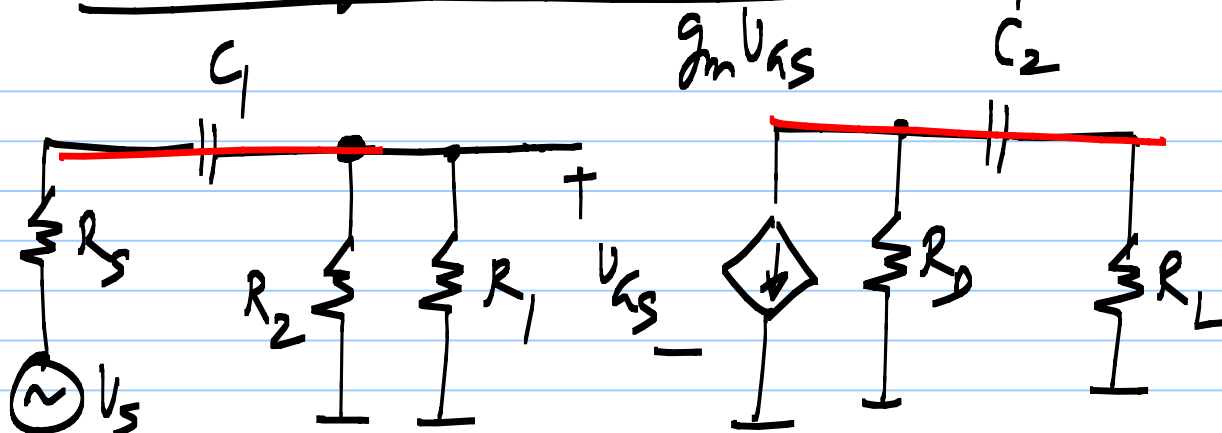


$C_1, C_2$  : very large ( $\rightarrow \infty$ )

$\omega_0$  :

$$\underbrace{\frac{1}{\omega_0 C_1}} \ll ( ) ; \underbrace{\frac{1}{\omega_0 C_2}} \ll ( )$$

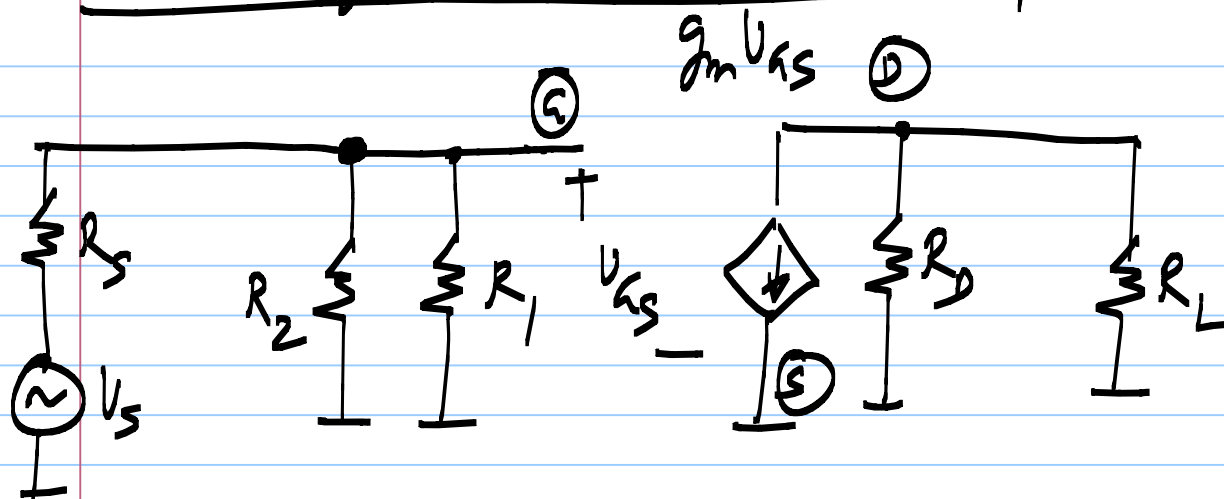Small signal incremental eq. circuit (large capacitors)




COMMON SOURCE AMPLIFIER

input: gate - source

output: drain - source

# CS amplifier

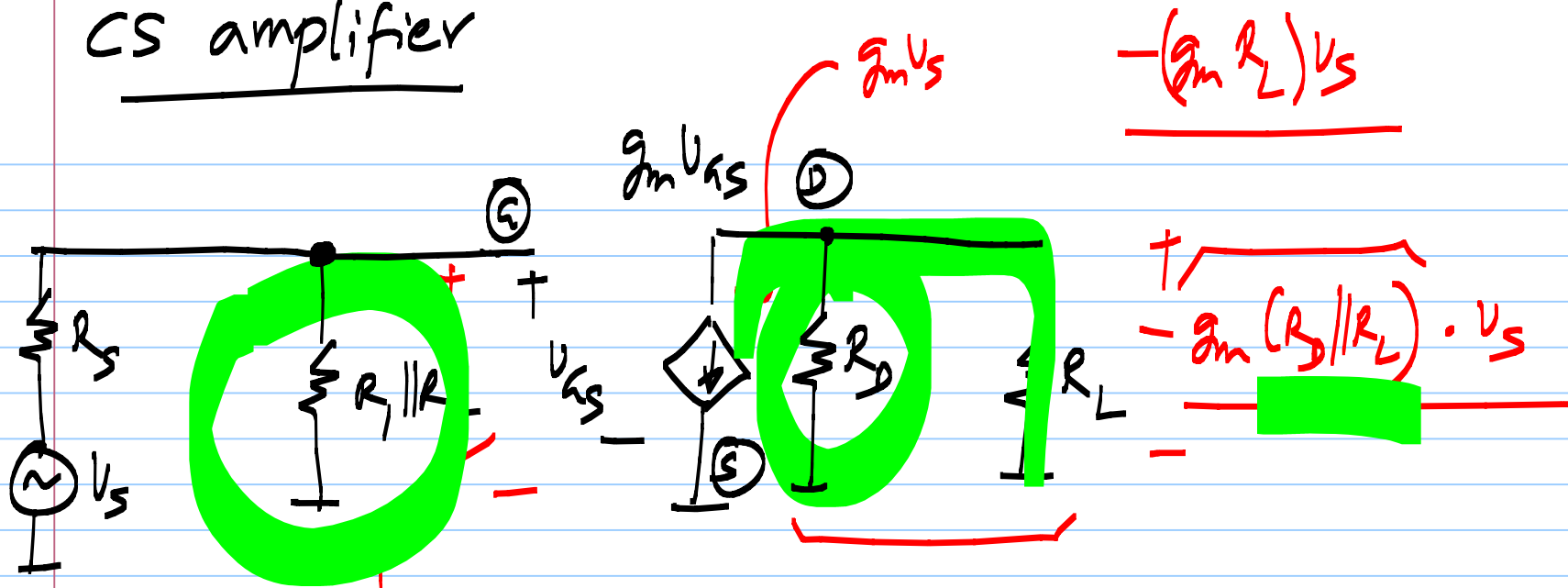

$$v_s \cdot \left( \frac{R_1 || R_2}{R_1 || R_2 + R_s} \right) \approx v_s \text{ if } \underline{\underline{R_1 || R_2 \gg R_s}}$$

$R_1, R_2 \gg R_s$

op. point

$$V_{DS} = \underline{\underline{V_{DD} - I_D \cdot R_D}}$$


$$\underline{V_{DS} > V_{GS} - V_T}$$

$$\left[ V_{DD} = \underline{V_{DS}} + I_D \cdot R_D \right]$$

- \* For a fixed  $V_{DD}$ , increasing  $R_D$  drives the transistor into triode region
- \* For a fixed  $V_{DS}$ , increasing  $R_D$  requires an increase in  $V_{DD}$

$\omega$ : frequency of  $V_s$
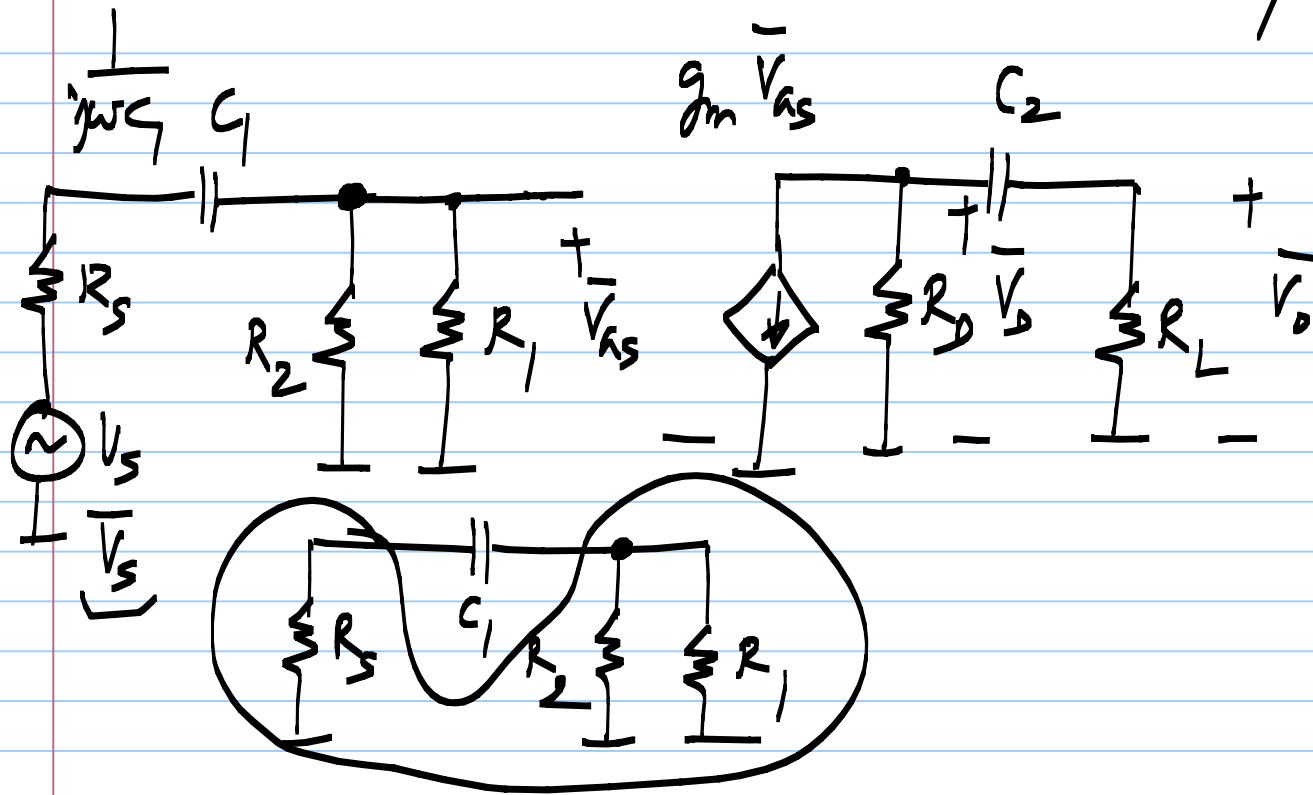
$$\frac{\bar{V}_{as}}{\bar{V}_s} ; \frac{\bar{V}_o}{\bar{V}_{as}}$$



$$\frac{V_{as}}{V_s} = \frac{(R_1 \parallel R_2)}{R_1 \parallel R_2 + R_s + \frac{1}{j\omega C_1}} = \frac{j\omega C_1 (R_1 \parallel R_2)}{1 + j\omega C_1 ((R_1 \parallel R_2) + R_s)}$$


$C_1$ : large if  $\omega C_1 ((R_1 \parallel R_2) + R_s) \gg 1$

$$\frac{V_{as}}{V_s} \approx \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_s}$$

$$\frac{1}{\omega C_1} \ll (R_1 \parallel R_2) + R_s \quad \text{Time constant} \gg \frac{1}{\omega} \text{ rad/s}$$

$$C_1 \Rightarrow \frac{1}{\omega(R_1 || R_2 + R_s) \cdot 10nF}$$

$$C_1 = 10 \times 10nF = 100nF$$

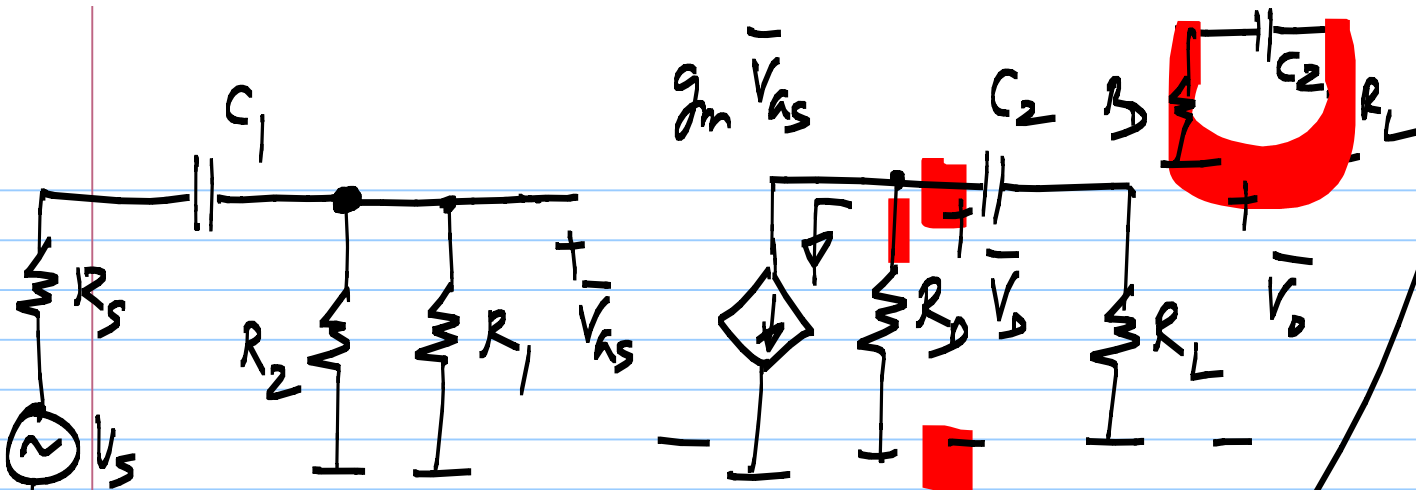

$$\frac{1}{\omega C_2} \ll (R_D + R_L)$$

$$\frac{V_o}{V_{gs}} = -g_m \cdot \frac{R_D}{R_D + R_L + \frac{1}{j\omega C_2}} \cdot R_L$$

$$-g_m \cdot \frac{j\omega C_2 (R_D R_L)}{1 + j\omega C_2 (R_D + R_L)}$$

$\omega C_2 (R_D + R_L) \gg 1$

$$\frac{V_D}{V_{as}} = -g_m \cdot \frac{R_D \cdot \left(R_L + \frac{1}{j\omega C_2}\right)}{R_D + R_L + \frac{1}{j\omega C_2}} = -g_m \frac{R_D (1 + j\omega C_2 R_L)}{1 + j\omega C_2 (R_D + R_L)}$$

$$\omega C_2 R_L \gg 1$$

$$\omega C_2 (R_D + R_L) \gg 1$$

$$\omega C_2 R_L \gg 1$$

Drain-source signal voltage  
= output voltage


\* Consider one capacitor at a time

\* Assume all other capacitors are shorts

only first order circuits

$I_D - V_{DS}$  (output) characteristics of the MOS transistor
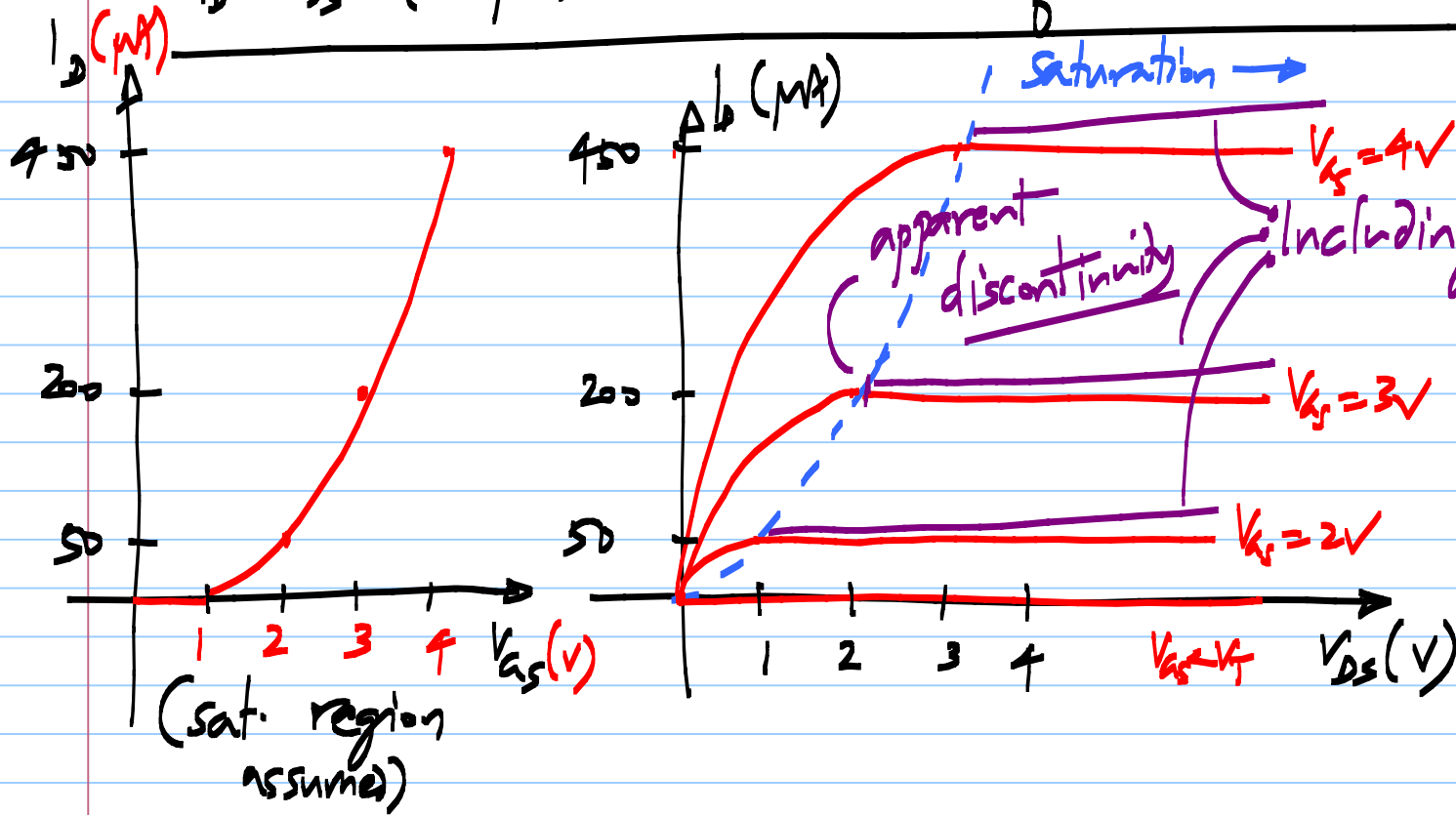
$$V_T = 1V, \quad k_n = \mu_n C_{ox} \frac{W}{L} = 100 \mu A/V^2$$



Current increases (or not) with  $V_{DS}$  in saturation region


$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) \quad V_{DS} > V_{GS} - V_T$$

$$\lambda = 0.05 \text{ V}^{-1}$$

channel length modulation

$$\lambda = \frac{k_A}{L}$$

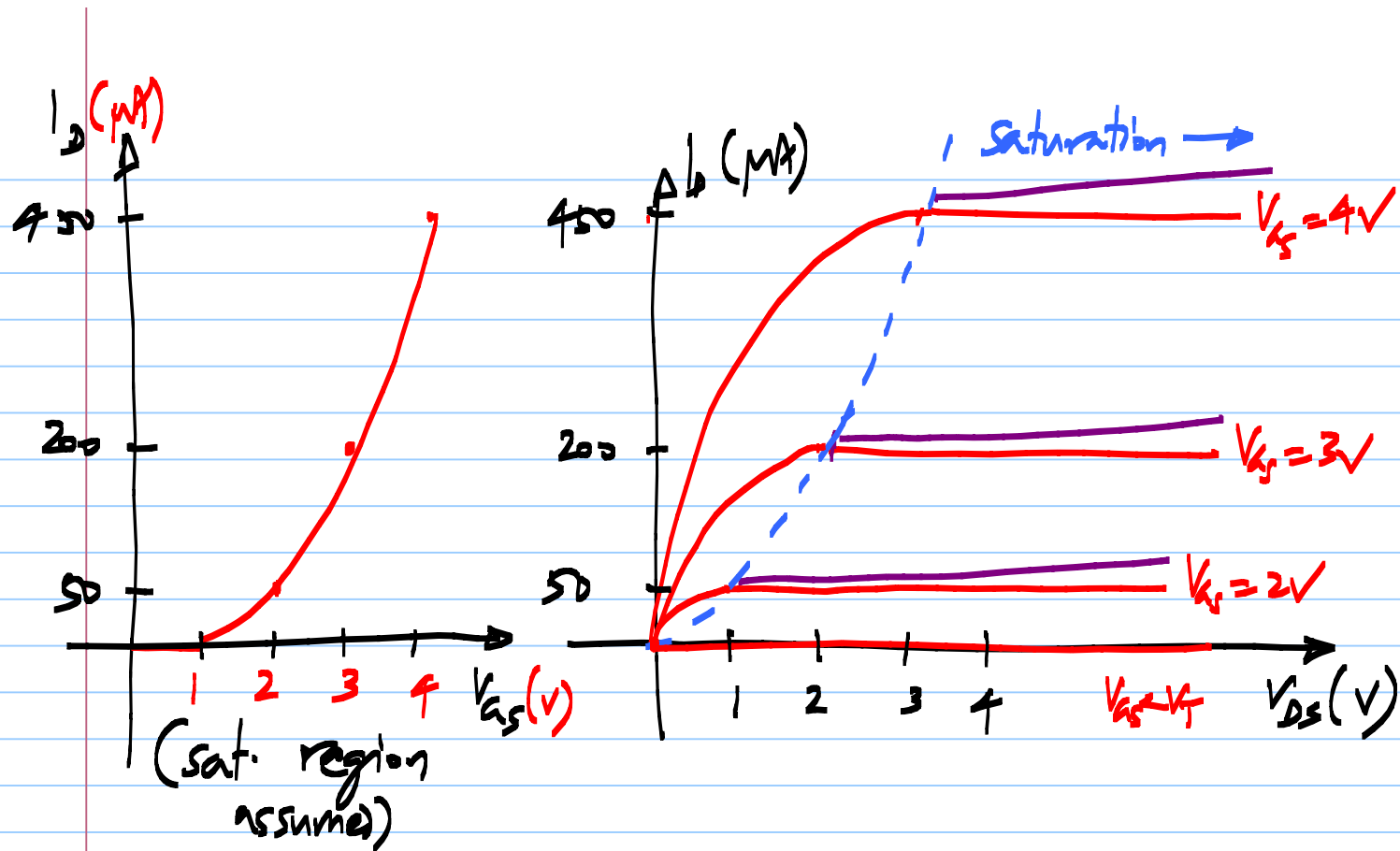$\lambda$ : inversely varies  
as transistor length





$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T) (1 + \lambda V_{DS})$$

$$g_{ds} = \frac{\partial I_D}{\partial V_{DS}} = \lambda \cdot \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} (V_{GS} - V_T)^2$$

non-zero drain-source conductance

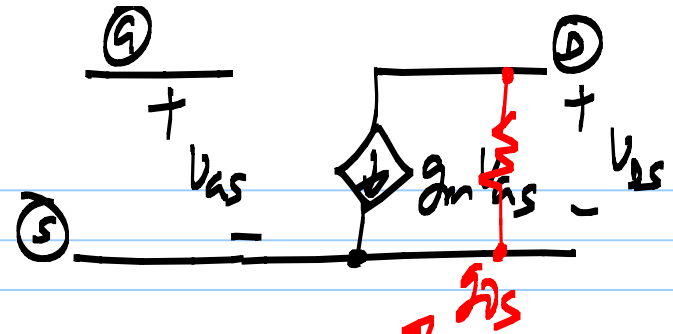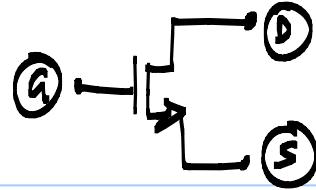

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

For op. point calculations  
 $1 + \lambda V_{DS}$  ignored

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T) (1 + \lambda V_{DS})$$

$$g_{ds} = \lambda \cdot \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 \approx \lambda \cdot I_D$$

$I_D$

$$\lambda = 0.05 \text{ V}^{-1}$$

$$V_{GS} = 3 \text{ V}$$

$$\lambda = 0$$

$$V_T = 1 \text{ V}, \quad \mu_n C_{ox} \frac{W}{L} = 100 \mu\text{A}/\text{V}^2$$

$$I_D = 200 \mu\text{A} \left( 1 + \frac{\lambda \cdot V_{DS}}{0.5} \right)$$

230  $\mu\text{A}$

$$V_{DS} = 3 \text{ V}$$

↓  
saturation

$$I_D = 200 \mu\text{A}$$

$$g_m = 200 \mu\text{S}$$

$$g_m = 200 \mu\text{S} \left( 1 + \frac{\lambda V_{DS}}{0.5} \right)$$


230  $\mu\text{S}$

$$g_{ds} = 0$$


10  $\mu\text{S}$

$$g_{ds} = \lambda \cdot 200 \mu\text{A}$$

= 10  $\mu\text{S}$

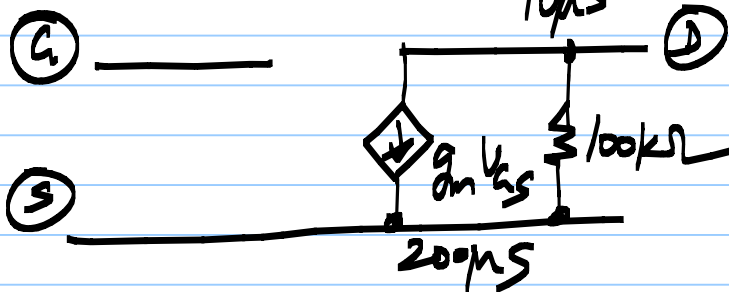
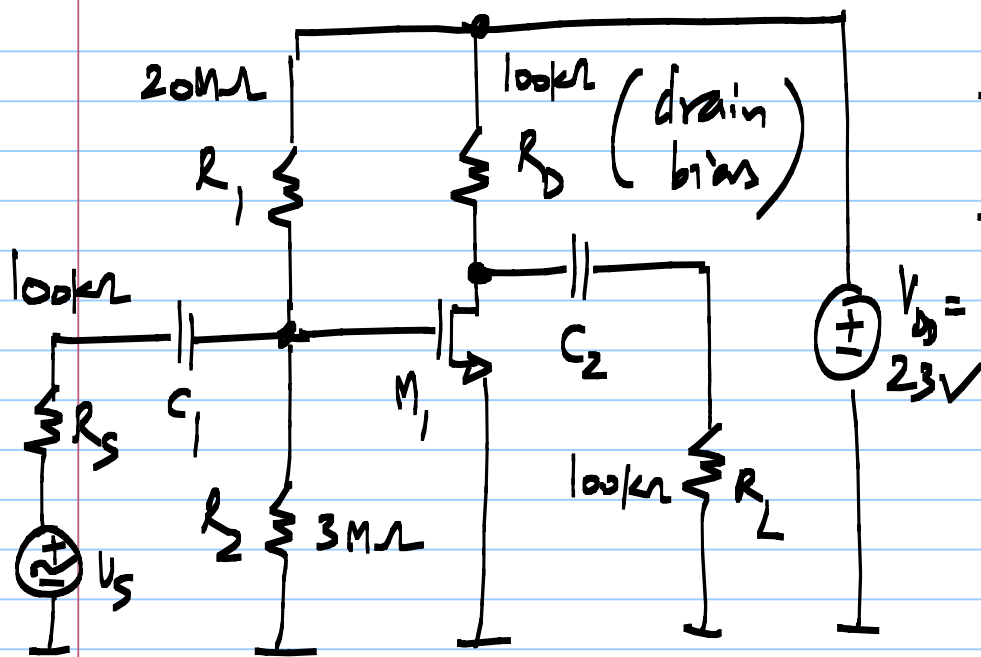
## Effect of $g_{ds}$ on the CS amplifier



$$V_{GS} = 3V, V_{DS} = 3V, I_D = 200\mu A$$


$$g_m = 200\mu S$$

$C_1, C_2$ : very large;  $R_1, R_2 \gg R_S$

$$g_{ds} \approx \lambda_b \quad \lambda = 0.05 \text{ V}^{-1}$$

$$\frac{1}{10 \mu\text{S}} = \frac{1}{100 \text{ k}\Omega}$$
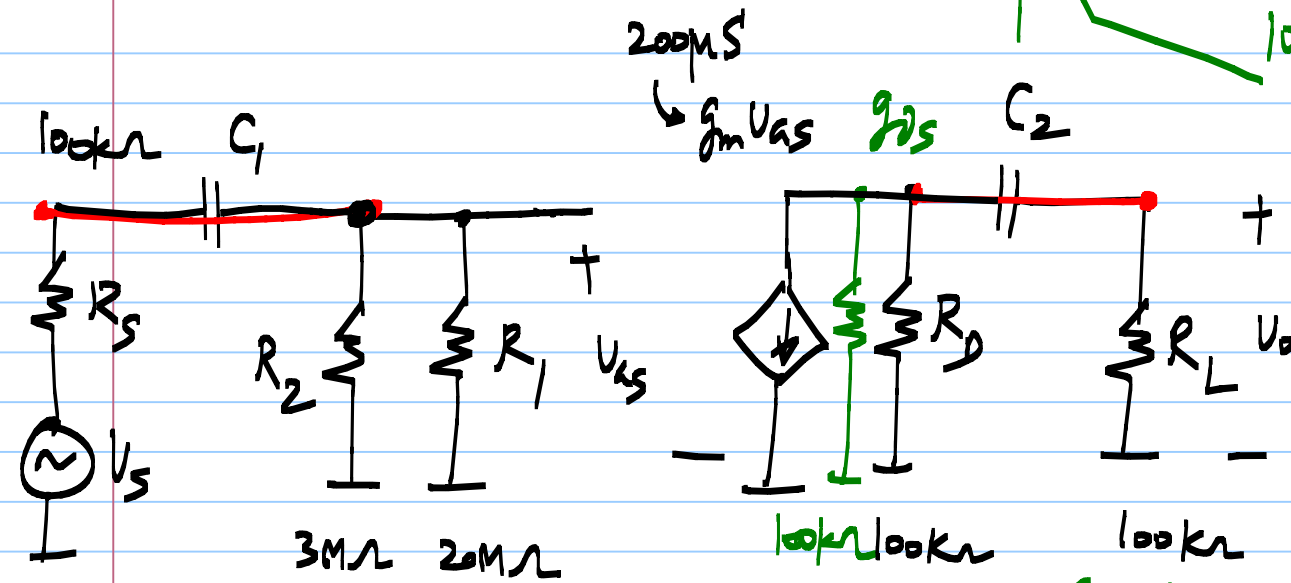
$$r_{ds} = 100 \text{ k}\Omega = 1/g_{ds}$$



$$-g_m R_L = -20$$

$$-g_m (R_D \parallel R_L) = -10$$

$$-g_m (r_{ds} \parallel R_D \parallel R_L) = \underline{-6.7}$$

$$\underline{\frac{v_o}{v_s} = -g_m (R_D \parallel R_L)}$$

$$\frac{v_o}{v_{gs}} = -g_m (r_{ds} \parallel R_D \parallel R_L)$$

$$\left| \frac{V_o}{V_s} \right| = +g_m (R_D \parallel R_L \parallel r_{ds}) < \underline{\underline{g_m \cdot r_{ds}}} \quad \rightarrow \text{Inherent gain limit of a transistor}$$

