
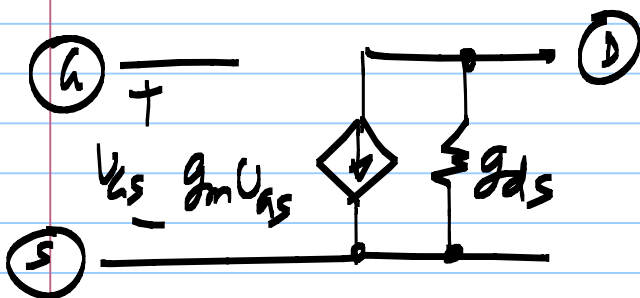


op. point : V_{gs}, V_{ds}, I_D

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_T) ; g_{ds} = \lambda \cdot I_D$$

Fix V_{gs} to the desired value

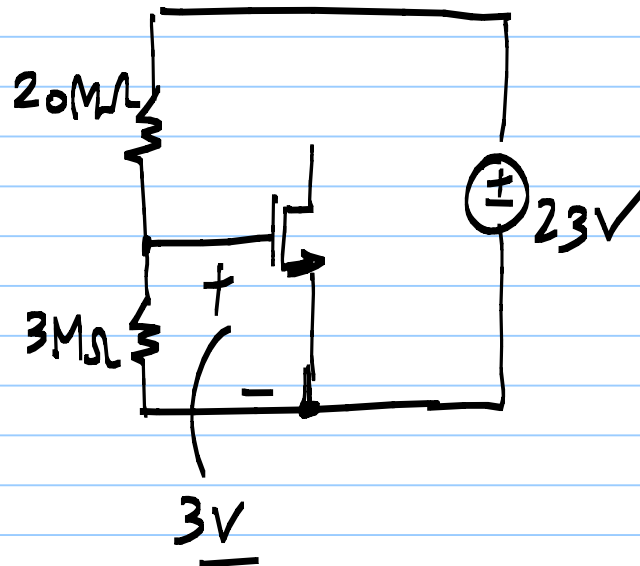

$$g_m = \underbrace{\mu_n C_{ox} \frac{W}{L}}_{\text{fixed @ } 3V} (V_{GS} - V_T) ;$$

$200 \mu S$

$$V_T = 1V, \quad \mu_n C_{ox} \frac{W}{L} = 100 \mu A/V^2$$

$$g_m \propto \underbrace{\mu_n C_{ox} \frac{W}{L}}$$

$$V_T = 0.8V \quad V_{GS} - V_T = 2.2V$$

$$g_m = 220 \mu S$$

$$V_T = 1.2V \quad V_{GS} - V_T = 1.8V$$

$$g_m = 180 \mu S$$

g_m varies with V_T & $\mu_n C_{ox} \frac{W}{L}$

V_T & $\mu_n C_{ox}$ vary with temperature

$$V_{GS} - V_T = \frac{2I_D}{(\mu_n C_{ox} \frac{W}{L})}$$


$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 \rightarrow V_{GS} - V_T = \sqrt{\frac{2 \cdot I_D}{\mu_n C_{ox} \frac{W}{L}}}$$

$$g_m = \mu_n C_{ox} \cdot \frac{W}{L} (V_{GS} - V_T)$$

$$= \sqrt{2 \cdot \mu_n C_{ox} \frac{W}{L} \cdot I_D} = \frac{2I_D}{V_{GS} - V_T}$$

$$g_m = \underbrace{K_n \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)}_{\text{Both } K_n \text{ \& } V_T \text{ appear}} = \underbrace{\sqrt{2 \cdot \mu_n C_{ox} \frac{W}{L} \cdot I_D}}_{\text{only } K_n \text{ appears}} \quad \blacksquare$$

Saturation

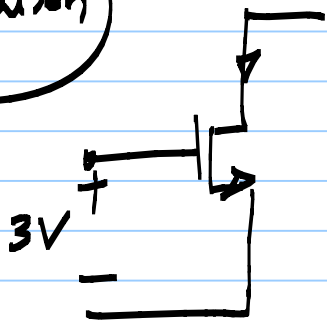

V_{GS} fixed @ 3V

$$V_T' = V_T + \Delta V_T$$

$$g_m' = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T - \Delta V_T)$$

$$\frac{g_m'}{g_m} = 1 - \frac{\Delta V_T}{V_{GS} - V_T}$$

Fixed V_{GS}


$$K_n \rightarrow K_n'$$

$$g_m' = K_n' (V_{GS} - V_T)$$

$$\frac{g_m'}{g_m} = \frac{K_n'}{K_n}$$

Fixed $I_D = 200 \mu A$
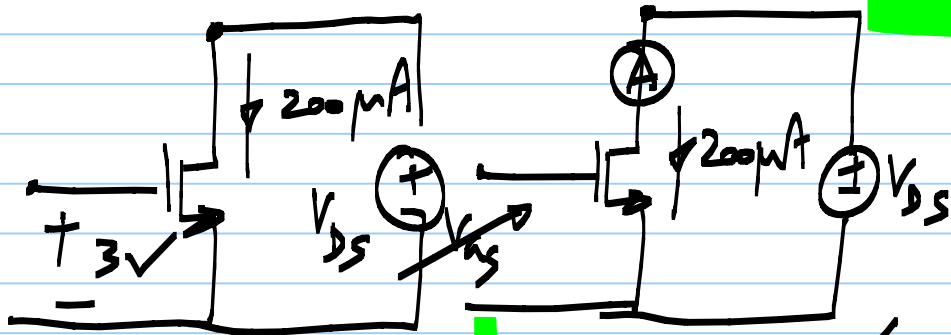
$$g_m = \sqrt{2 \cdot \mu_n C_{ox} \frac{W}{L} \cdot I_D} = \sqrt{2 \underbrace{K_n'} \cdot I_D}$$



$$V_T' = V_T + \Delta V_T$$

$$g_m' = g_m$$



$$K_n \rightarrow K_n'$$

$$\frac{g_m'}{g_m} = \sqrt{\frac{K_n'}{K_n}}$$

nominal V_T, k_n (1V) (100 μ A/V ²)	Fixed V_{AS} (eg. 3V)	Fixed I_D (100 μ A)	$\sqrt{1+x} \approx 1 + \frac{x}{2}$
$V_T' = V_T + \Delta V_T$ $k_n' = k_n$	$\frac{g_m'}{g_m} = 1 - \frac{\Delta V_T}{V_{AS} - V_T}$	$\frac{g_m'}{g_m} = 1$	$\sqrt{1.1} = \sqrt{1+0.1}$ ≈ 1.05
$V_T' = V_T$ $k_n' \neq k_n$ $k_n' = 1.1 \cdot k_n$	$\frac{g_m'}{g_m} = \frac{k_n'}{k_n}$ $= 1.1$	$\frac{g_m'}{g_m} = \sqrt{\frac{k_n'}{k_n}} \approx 1.05$ $\frac{g_m'}{g_m}$: much closer to 1 in this case	

Biasing the transistor at a given I_D : lower sensitivity of g_m to transistor parameters How?



Transistor: Unilateral

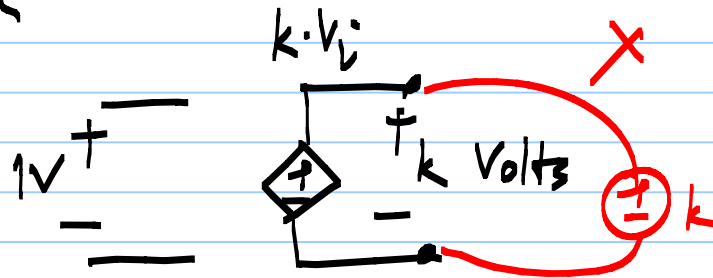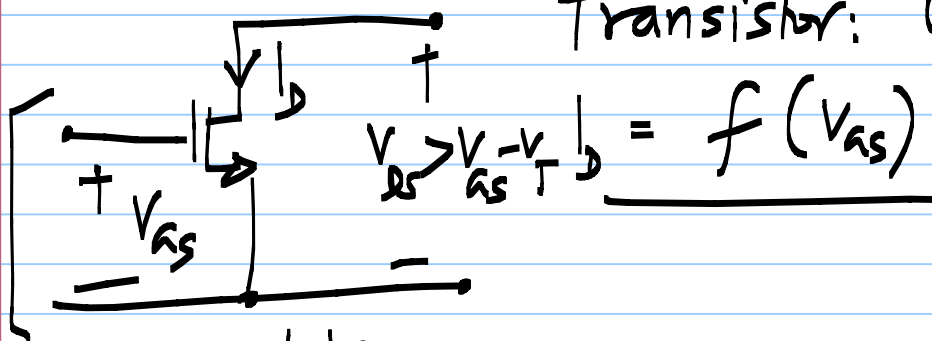

$$V = I \cdot R$$


$$I = V/R$$

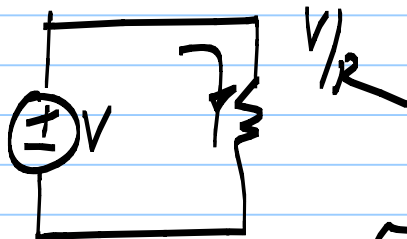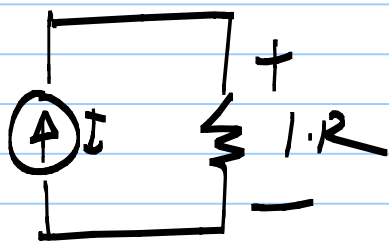Apply V_{GS} : $I_D = \frac{K_n}{2} (V_{GS} - V_T)^2$ flows into the drain




$$I_D = \frac{K_n}{2} (V_{GS} - V_T)^2$$

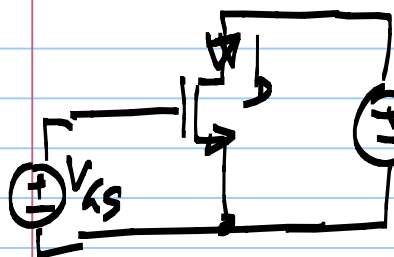
$$V_{GS} = V_T + \sqrt{\frac{2I_D}{K_n}}$$



$$V_{GS} > V_{GS} - V_T$$

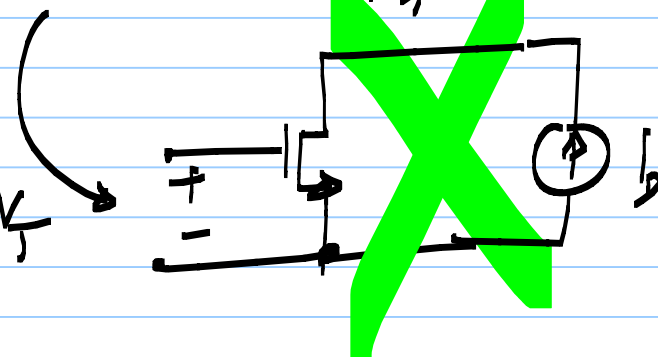

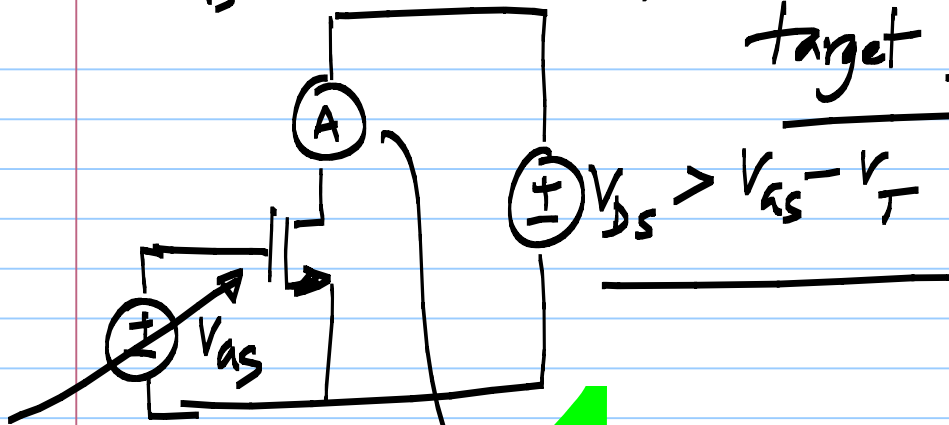V_{GS} controls I_D , not vice versa
target $I_D = 200 \mu A$




$$V_{DS} > V_{GS} - V_T$$

negative
feedback

observe the actual drain current,
compare it to the desired I_D
increase or decrease V_{GS} (200 μA) as required

Biasing a transistor at a given current

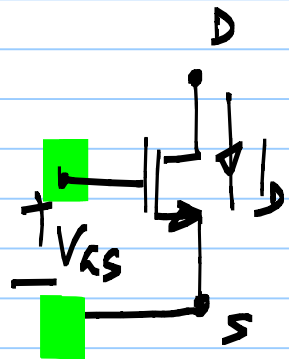

I_D : accessed at the drain or source

Varying voltage: applied to gate or source

4 possible bias circuits

keep one of $\{G, S\}$

at a constant voltage

& vary the other terminal

✓ measure (compare) @ drain, control the gate voltage
measure (") @ source, control the source voltage
" " @ drain, control the source voltage
" " @ source, control the gate voltage

measure (compare) @ drain, control the gate voltage


compare I_D with I_0 $\frac{I_0 - I_D}{I_0}$ or $I_D - I_0$
adjust V_a

If $I_D < I_0$ ($I_0 - I_D > 0$), $V_D \uparrow$

If $I_D > I_0$ ($I_0 - I_D < 0$), $V_D \downarrow$


If $I_D < I_0$: we must increase V_a

If $I_D > I_0$: we must reduce V_a

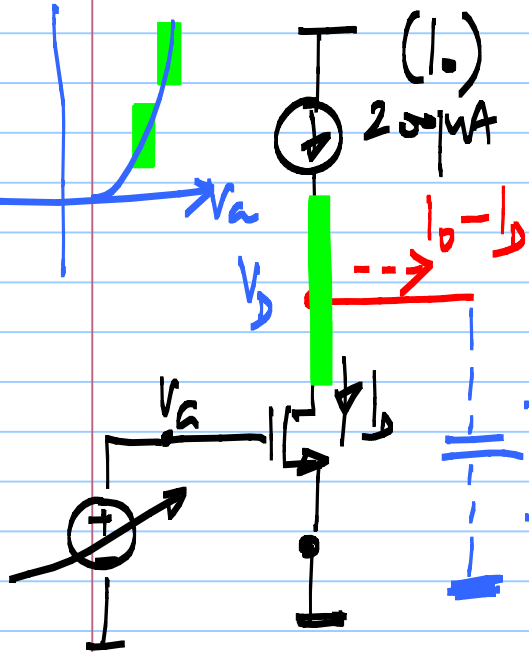

Connect gate to the drain
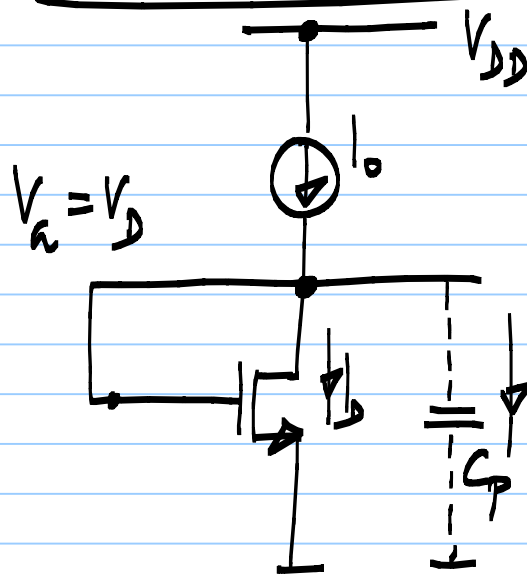
$$V_k \uparrow \Rightarrow I_D \uparrow$$



$I_D < I_0$: V_D increases continuously

$I_D > I_0$: V_D decreases continuously


$I_D = I_0$: V_D stays constant

stops here

$$V_k \downarrow \Rightarrow I_D \downarrow$$


Drain feedback
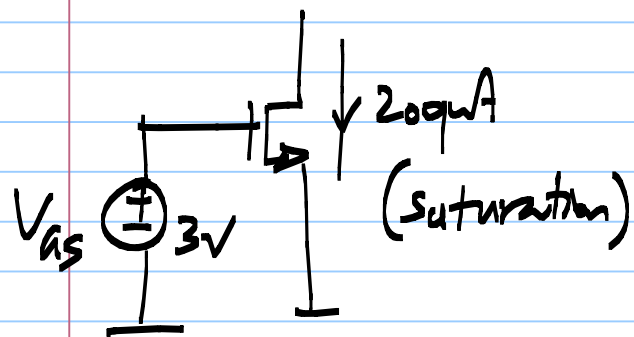
$$V_{DS} = V_{GS} \Rightarrow V_{DS} > V_{GS} - V_T \quad (V_T > 0)$$



$$I_D = I_B = \frac{K_n}{2} (V_{GS} - V_T)^2$$


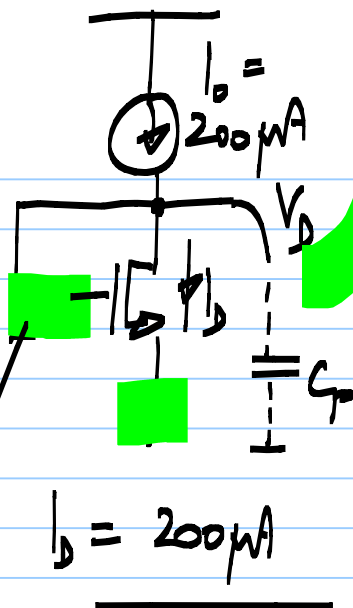
$$V_{GS} = V_T + \sqrt{\frac{2 \cdot I_D}{K_n}}$$



$$g_m = K_n (V_{GS} - V_T)$$


$$= \sqrt{2 \cdot K_n \cdot I_D}$$

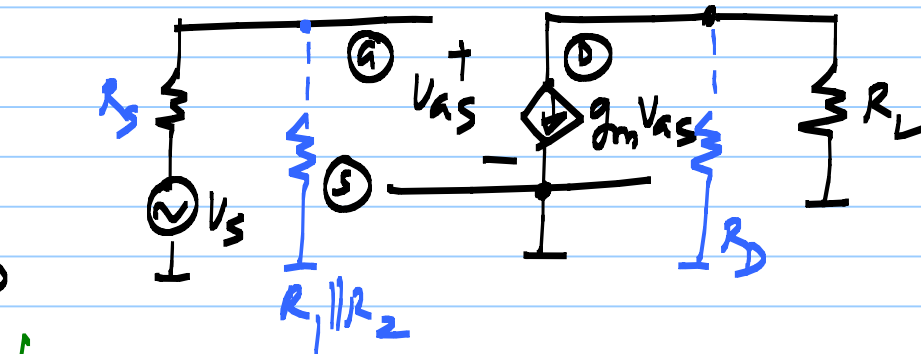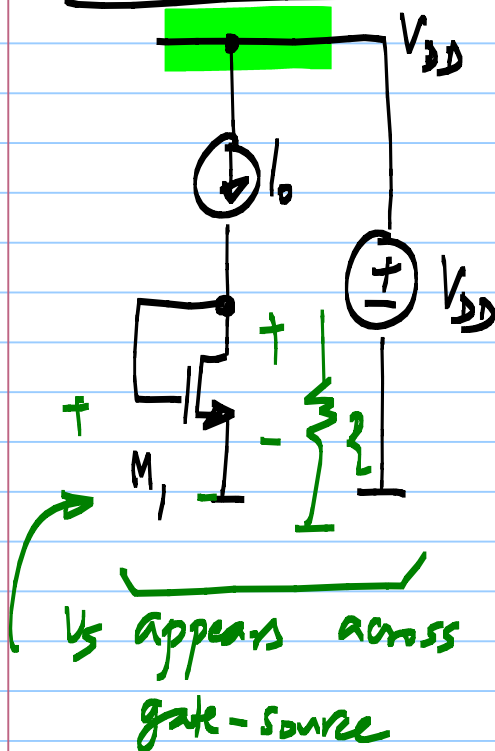Common source amplifier using drain feedback bias




load appears across drain source

signal is at a frequency $\geq \omega_0$

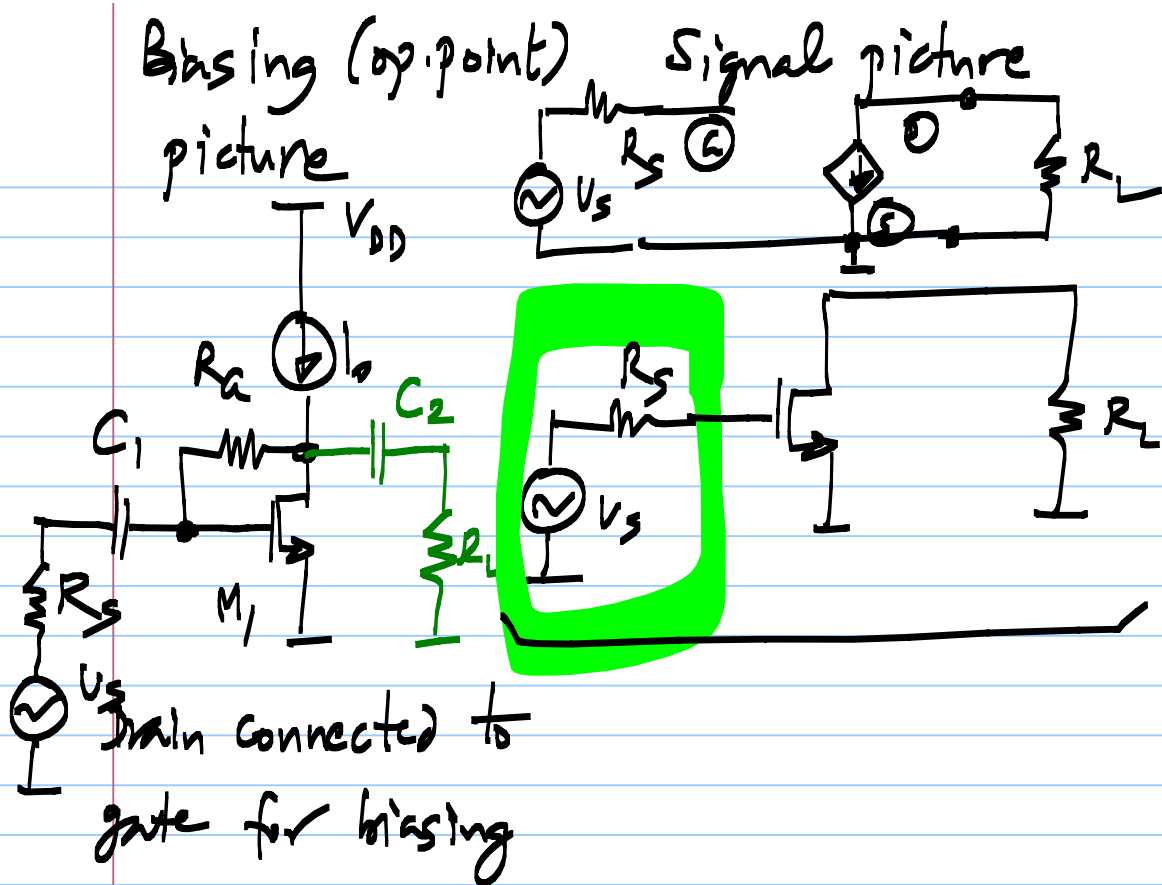


Gate $\begin{cases} \text{dc} & \text{to drain} \\ \text{ac} & (V_s, R_s) \text{ signal source} \end{cases}$

CS amplifier

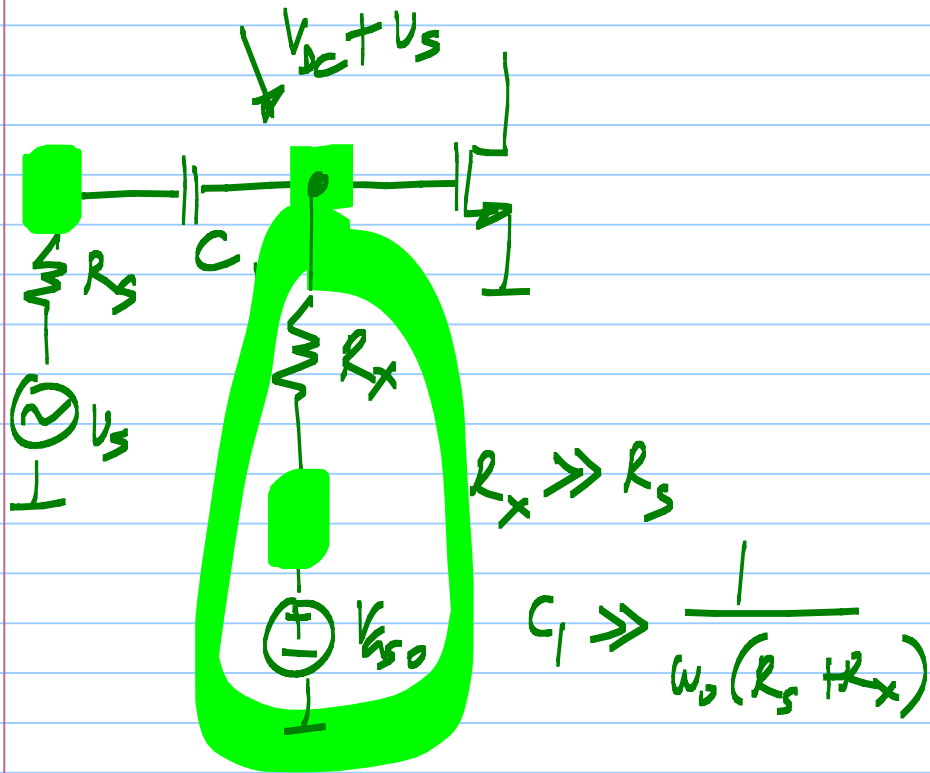

CS amplifier using drain feedback:


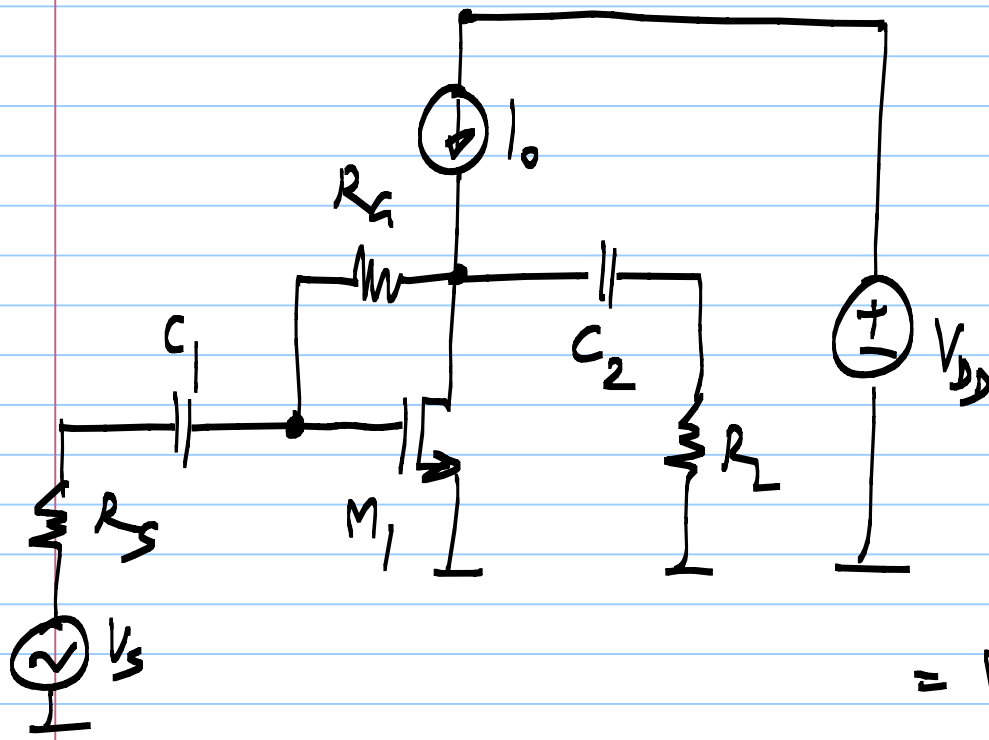


Determine constraints on C_1 & C_2


Analyze the effect of R_a

op. point
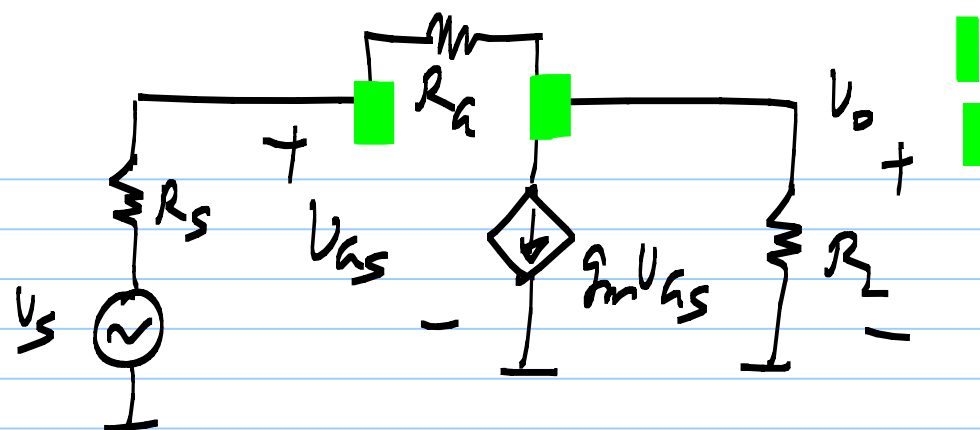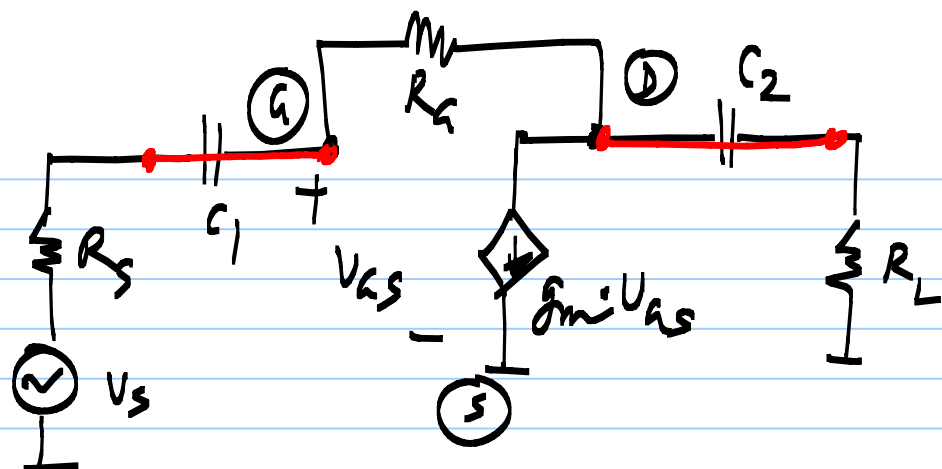
$$V_{GS} = \frac{V_{DS}}{2} = \frac{V_{DD}}{2} = V_T + \sqrt{\frac{2I_o}{\mu_n C_{ox} W/L}}$$



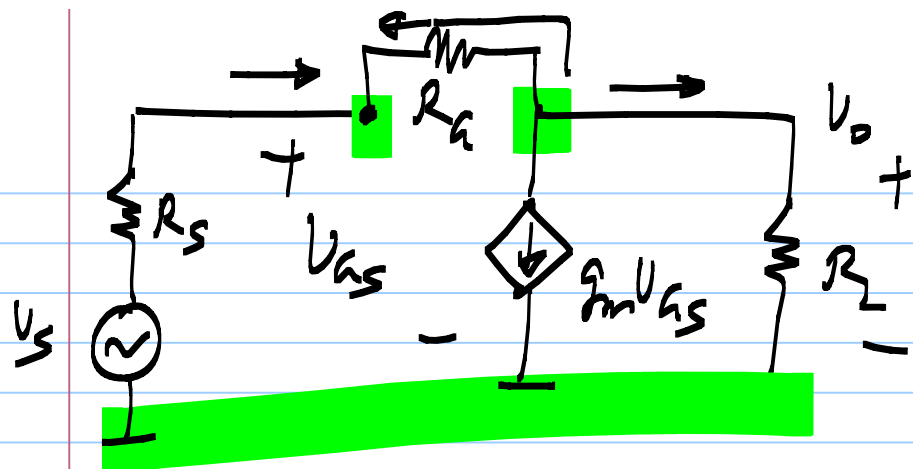C_1, C_2 : short circuits for the desired
signal frequency ω_0



$$\left. \begin{aligned} \frac{v_s - v_{gs}}{R_s} + \frac{v_o - v_{gs}}{R_a} &= 0 \\ g_m v_{gs} + \frac{v_o - v_{gs}}{R_a} + \frac{v_o}{R_L} &= 0 \end{aligned} \right\} \begin{array}{l} \text{solve} \\ \text{for} \\ v_{gs}, \\ v_o \end{array}$$

$$\frac{v_o}{v_s} = - \frac{(g_m R_a R_L - R_L)}{g_m R_L R_s + R_s + R_L + R_a}$$

CS. Amp: $\frac{v_o}{v_s} = -g_m R_L$

$$\frac{V_o}{V_s} = - \frac{(g_m R_a R_L - \cancel{R_L})}{g_m \cancel{R_L} R_s + \cancel{R_s} + \cancel{R_L} + R_a} \approx - \frac{g_m R_a R_L}{R_a} = - \underline{\underline{g_m R_L}} \quad R_s = 0$$

$$R_a \gg \underline{g_m R_L R_s}, R_s, R_L$$

$$R_a \gg \underbrace{g_m R_L R_s} \text{ OR } \underbrace{R_L}$$



$$- \frac{g_m R_a R_L - \cancel{R_L}}{\cancel{R_L} + R_a}$$




$$g_m R_a R_L \gg R_L$$

$$\underline{g_m R_a \gg 1}$$

$$g_m R_L > 1 \quad R_a \gg g_m R_L R_s$$


If R_s is very small, $R_a \gg R_L$

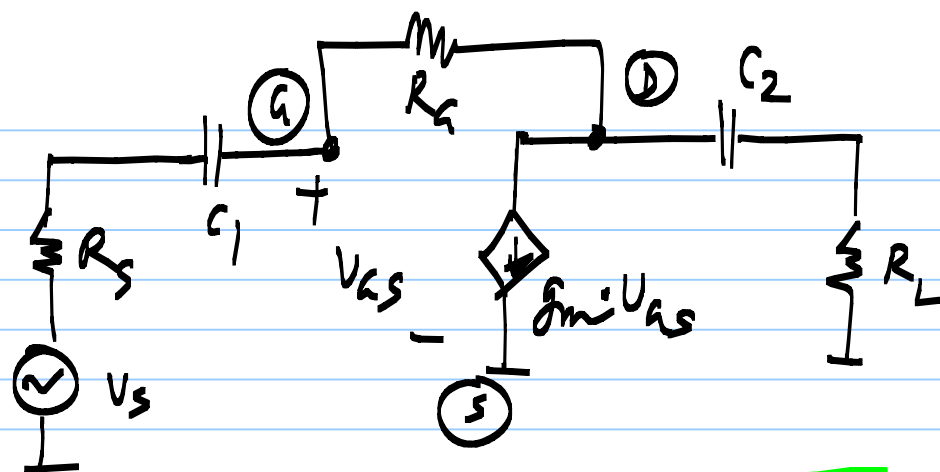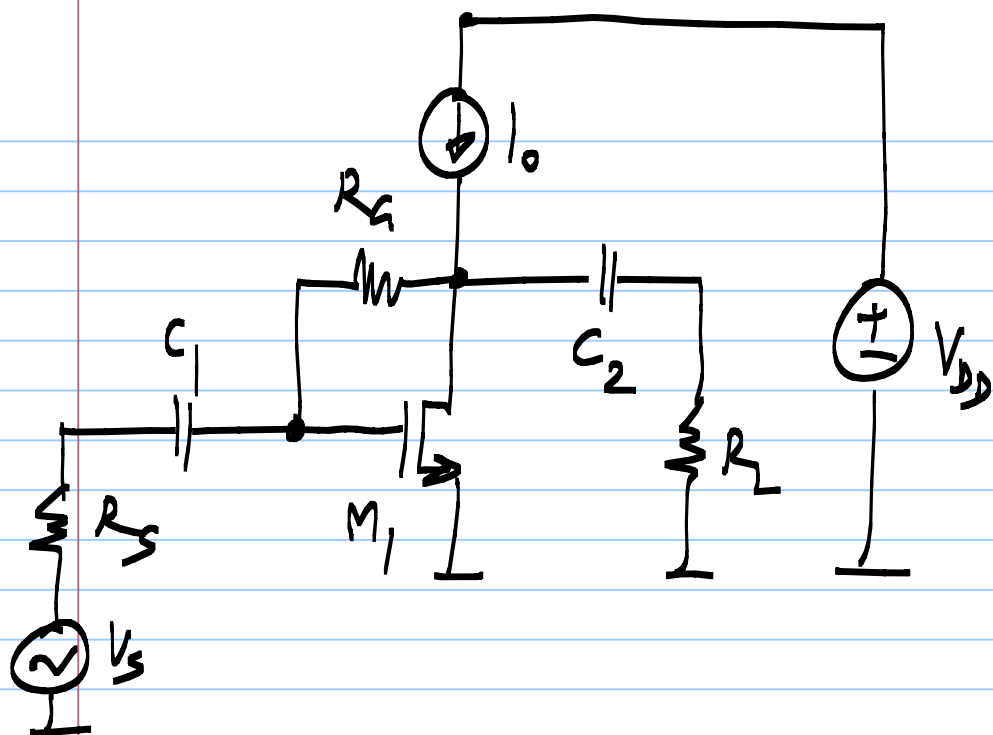

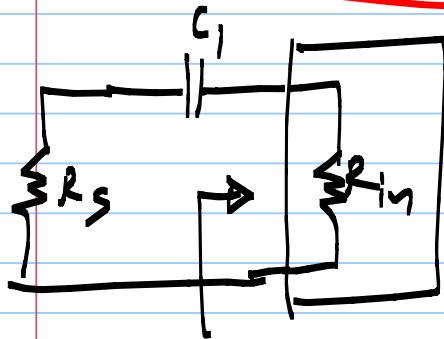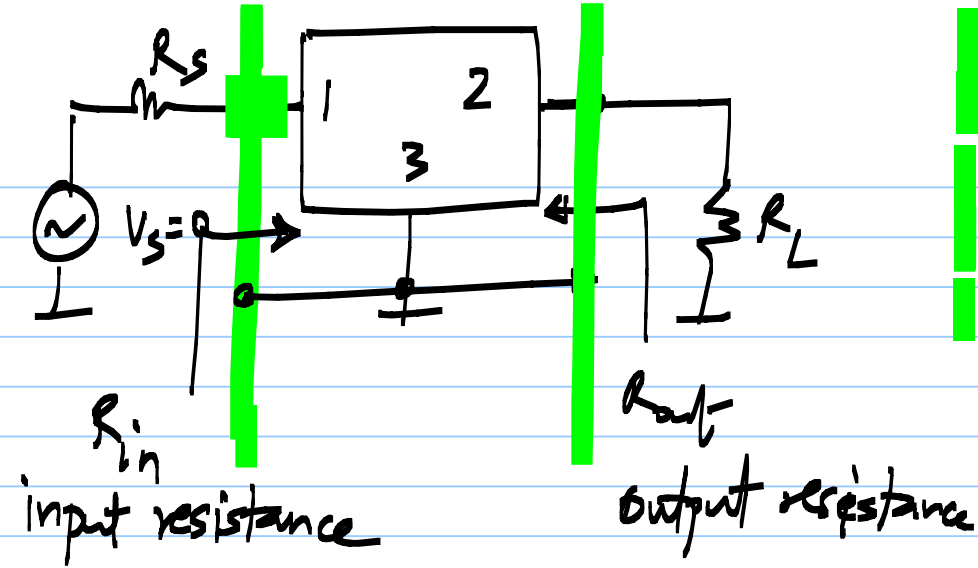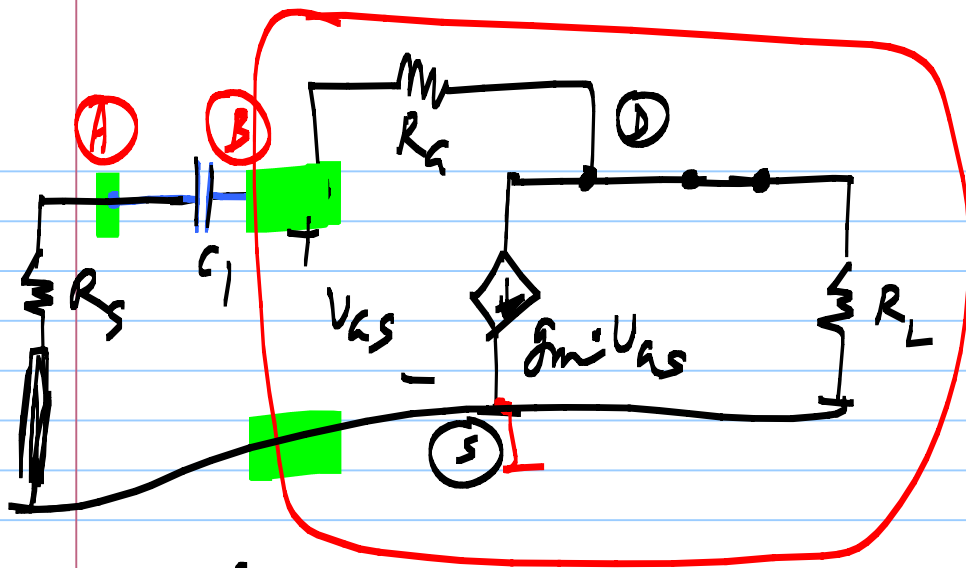

$$\frac{R_S + R_{in}}{1} \ll \frac{1}{\omega_b C_1}$$
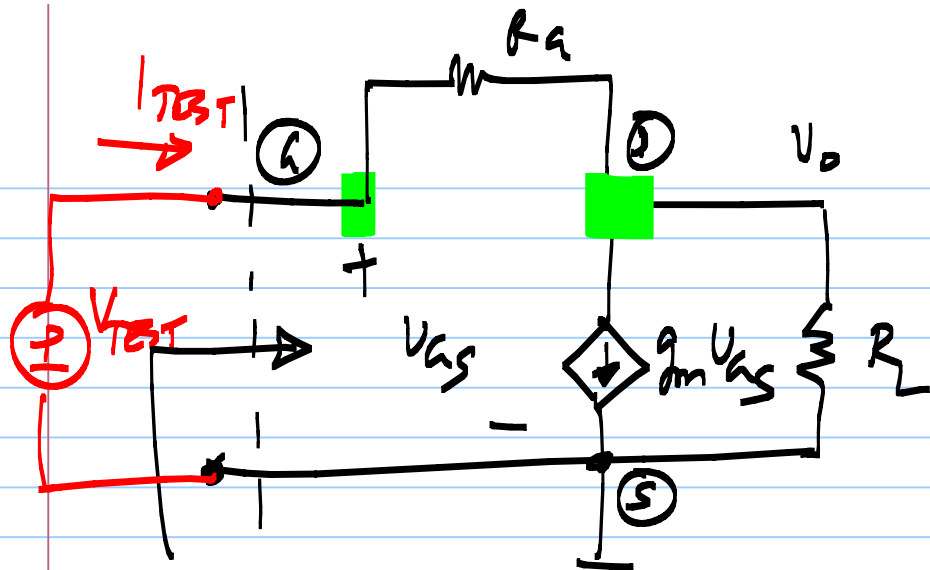
$$C_1 \gg \frac{1}{\omega_b (R_S + R_{in})}$$



$$R_{in} = \frac{V_{TEST}}{I_{TEST}} = \frac{R_a + R_L}{g_m R_L + 1}$$



\Rightarrow

$$w_o \left(R_s + \frac{R_a + R_L}{g_m R_L + 1} \right)$$

$$R_{in} = \frac{V_{TEST}}{I_{TEST}}$$

$$\frac{V_{TEST} - V_o}{R_a} = g_m \cdot V_{TEST} + \frac{V_o}{R_L}$$

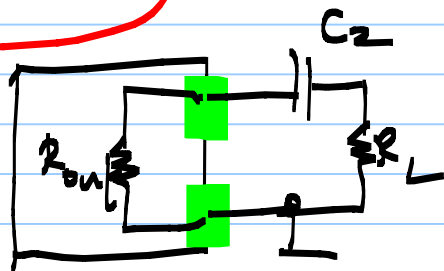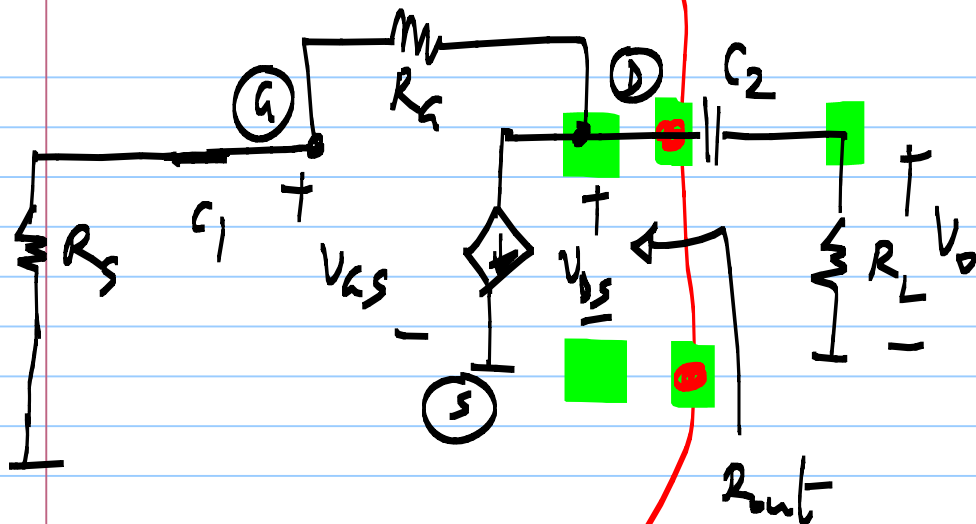
$$I_{TEST} = \frac{V_{TEST} - V_o}{R_a}$$





$$\frac{1}{\omega_0 C_2} \ll R_L + R_{out}$$


$$\Rightarrow \frac{1}{\omega_0 (R_L + R_{out})}$$
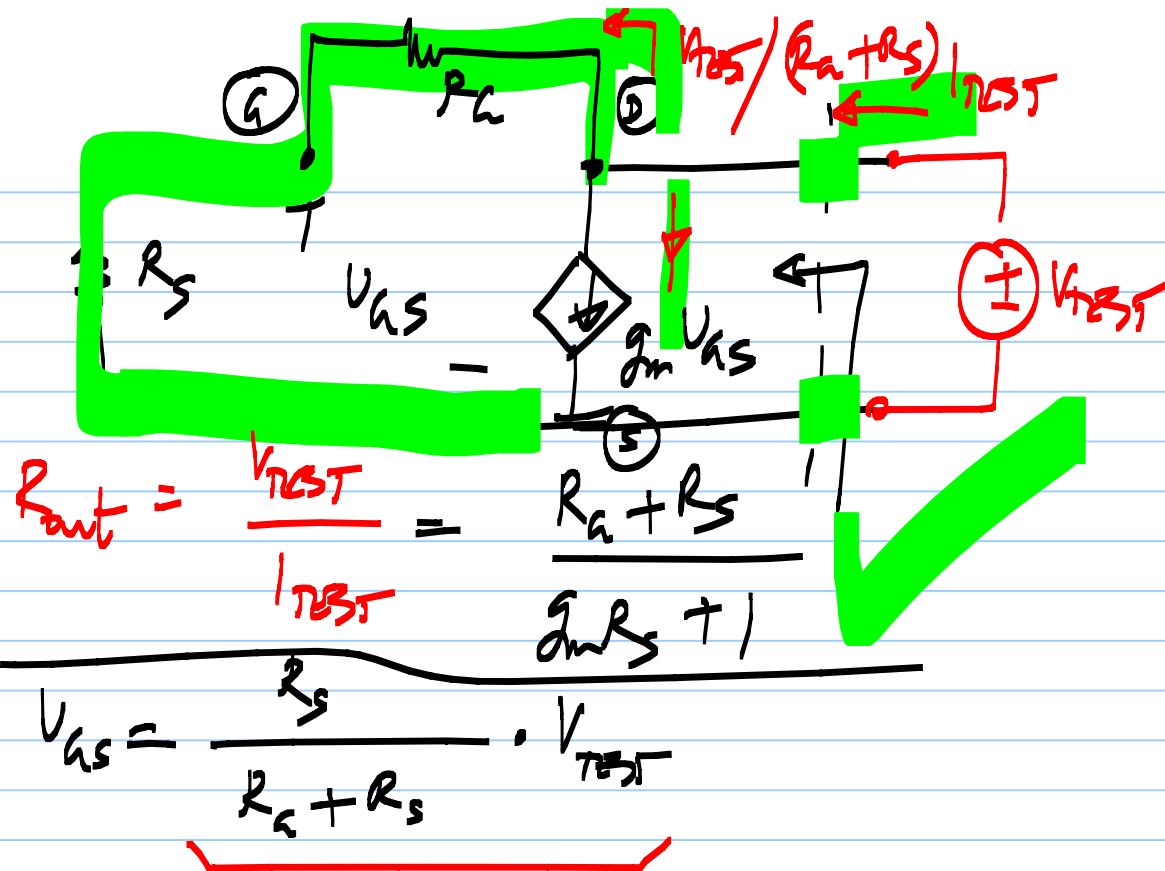
$$\Rightarrow \frac{1}{\omega_0 R_L} \quad \text{(stronger condition)}$$



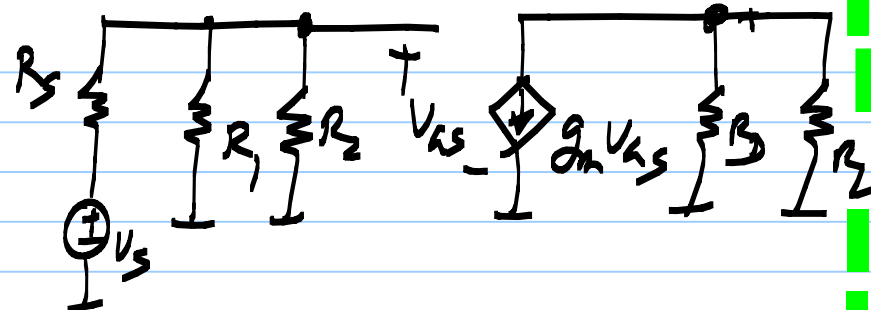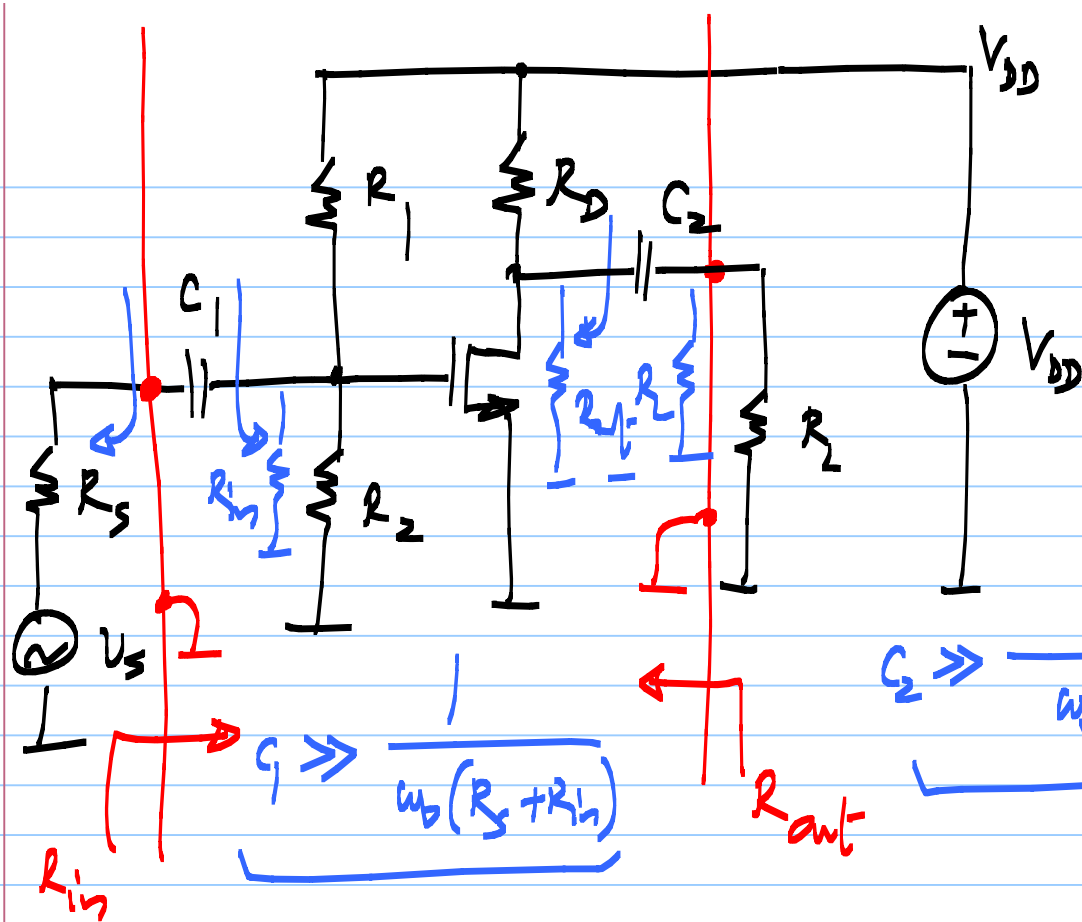
$$I_{test} = \frac{V_{test}}{R_L + R_S} + g_m \cdot V_{test} \cdot \frac{R_S}{R_L + R_S}$$



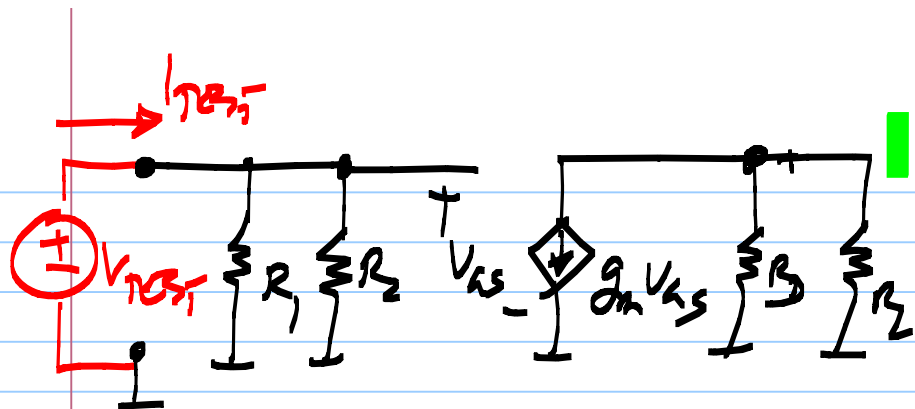

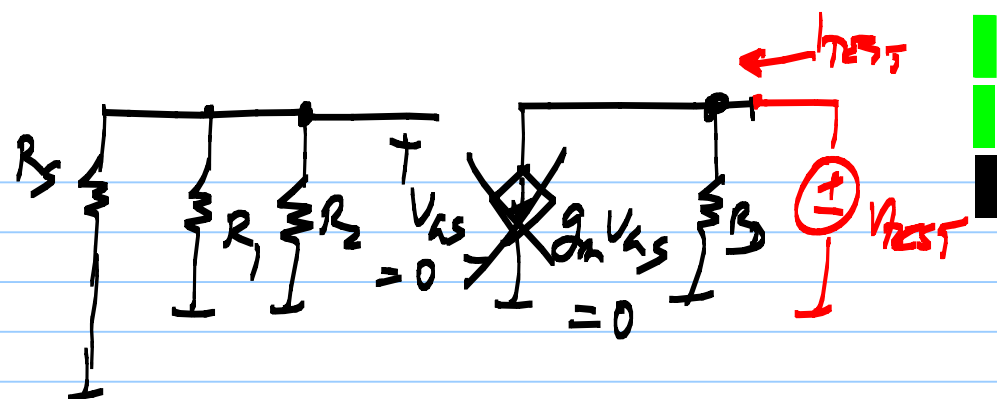
$$R_{in} = \frac{V_{TEST}}{I_{TEST}} = R_1 \parallel R_2$$



$$\underline{R_{out} = R_D}$$


Sense @ drain
fb to gate

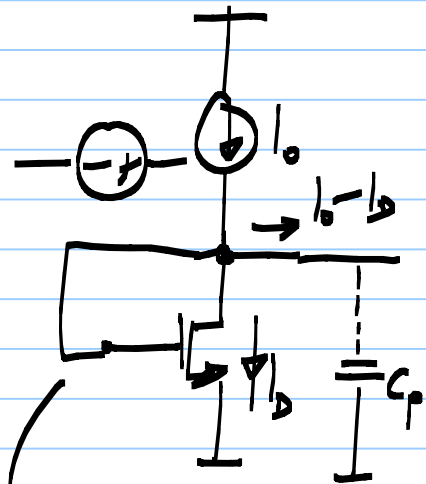

$$I_D = I_0$$


$$V_T + \sqrt{\frac{2 \cdot I_0}{\mu_n C_{ox} W/L}}$$

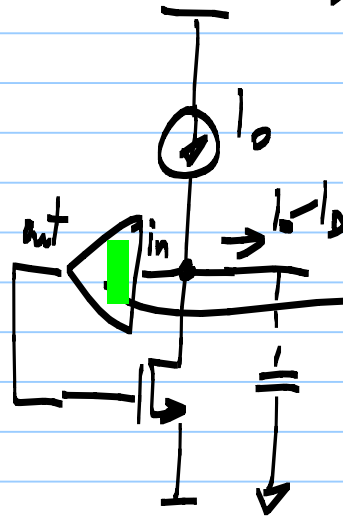$I_D < I_0$, V_D increases
 V_A must increase



V_A must increase
when V_D increases


+ve incremental
gain

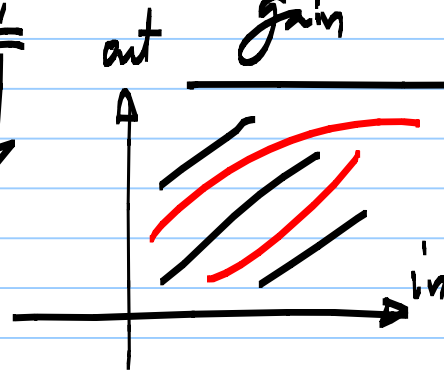

$$I_D \left(V_T + \sqrt{\frac{2I_D}{\mu_n C_{ox} W/L}} \right)$$

Current mirror

replicate & scale

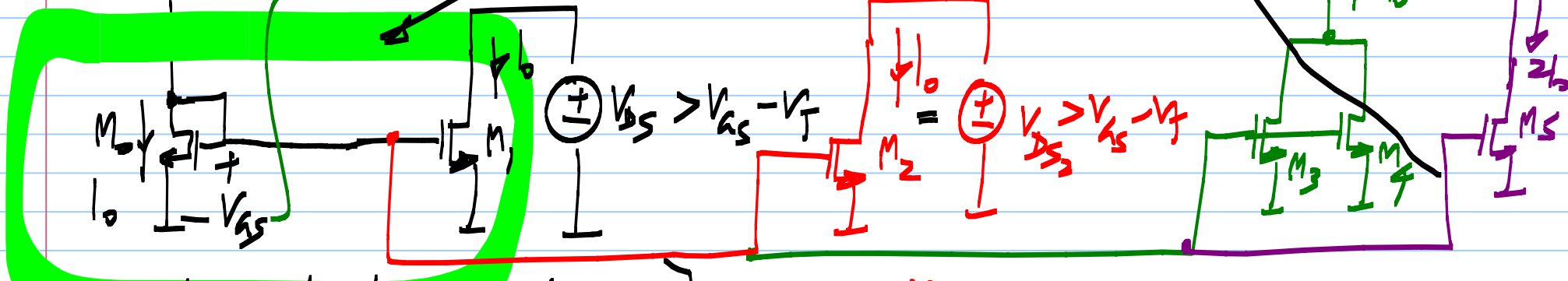

On a chip, closely spaced transistors, their characteristics will be nearly identical


$$M_0 = M_1 = M_2$$


$$M_0 = M_3 = M_4$$

$$M_0: W/L; M_5: 2W/L$$



CS amplifier using current mirror bias


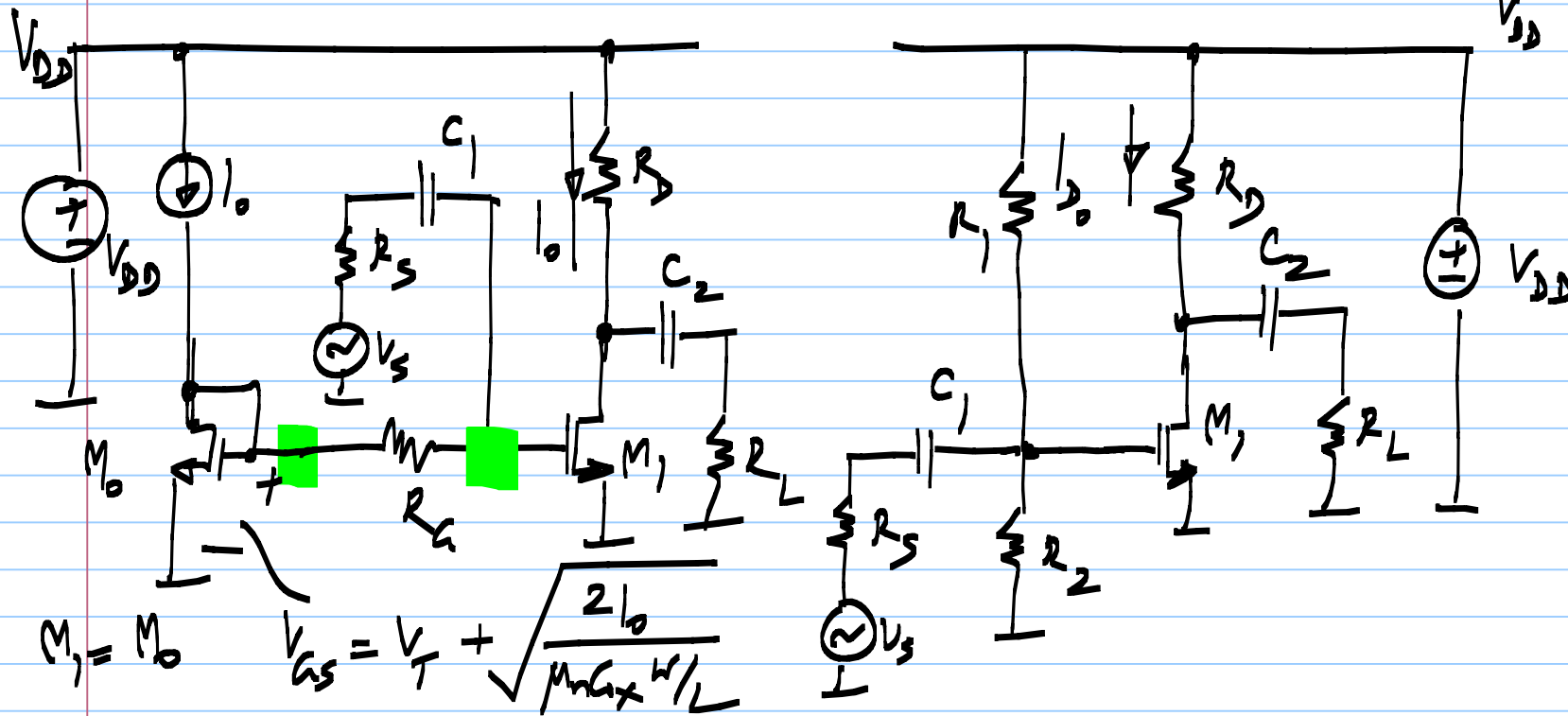
$$V_{GS, \text{required}} = \frac{R_2}{R_1 + R_2} \cdot V_{DD}$$



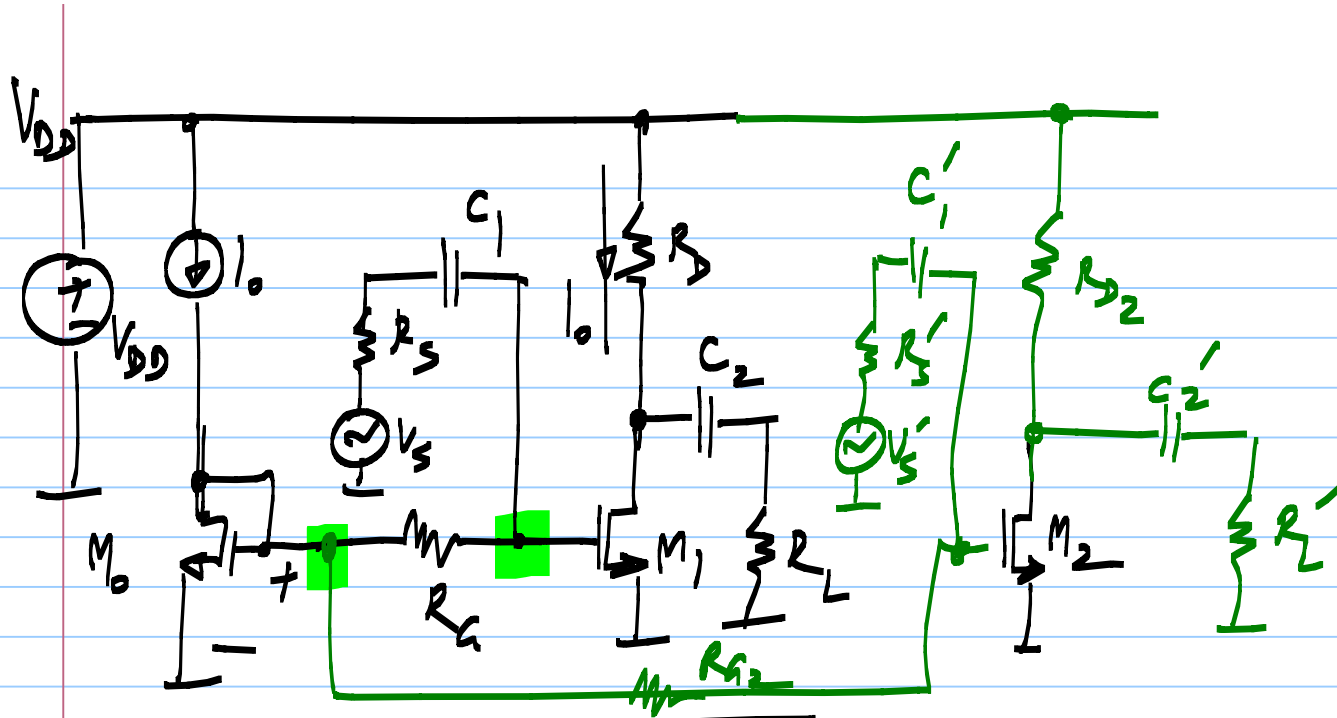



CS amplifier using current mirror bias.

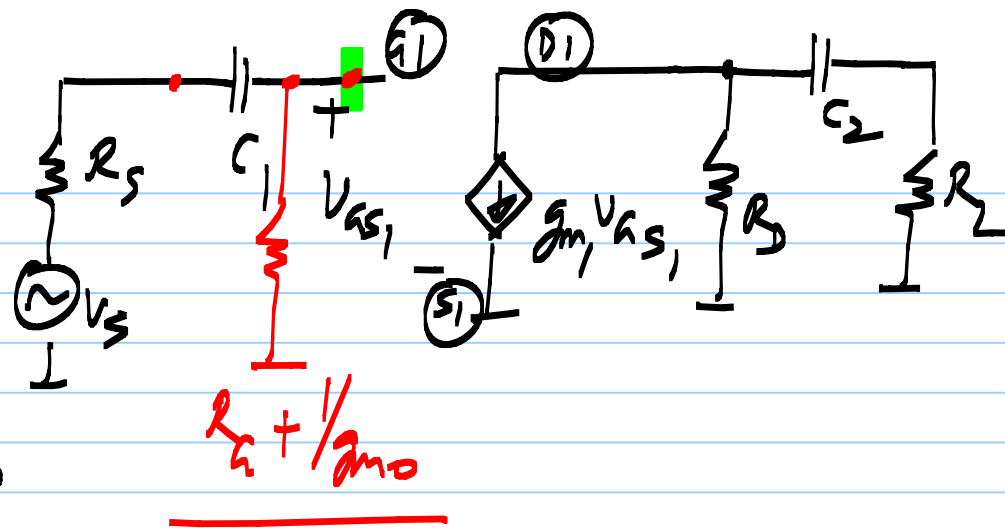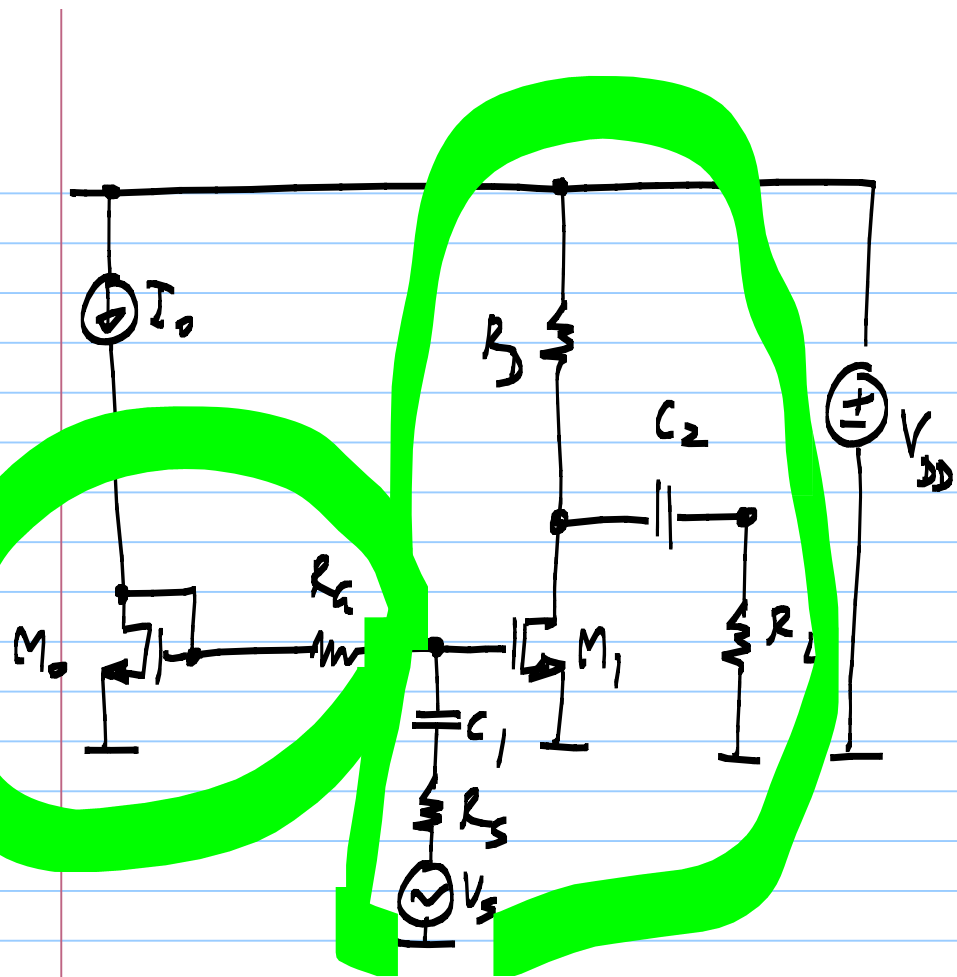

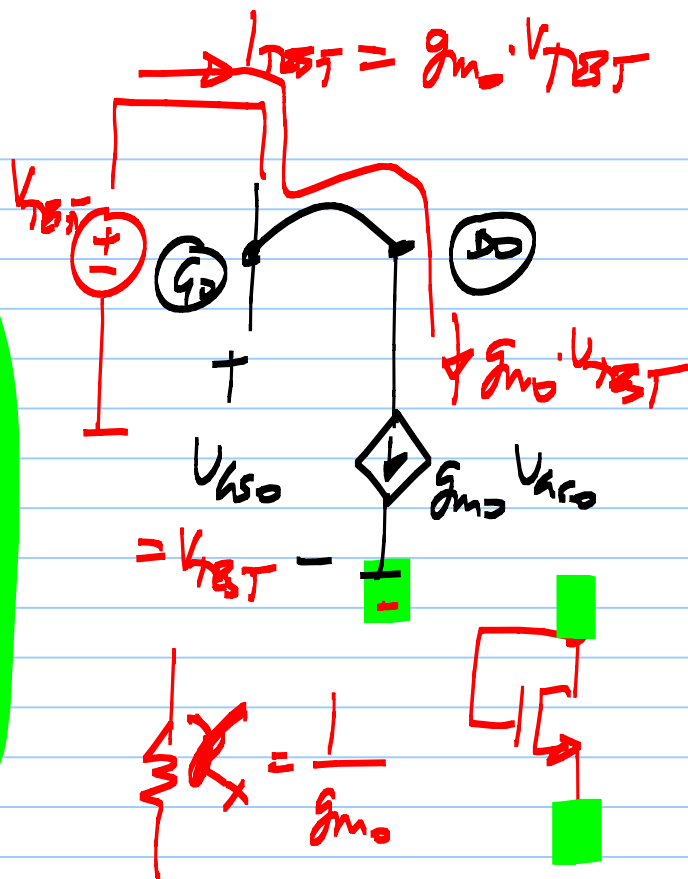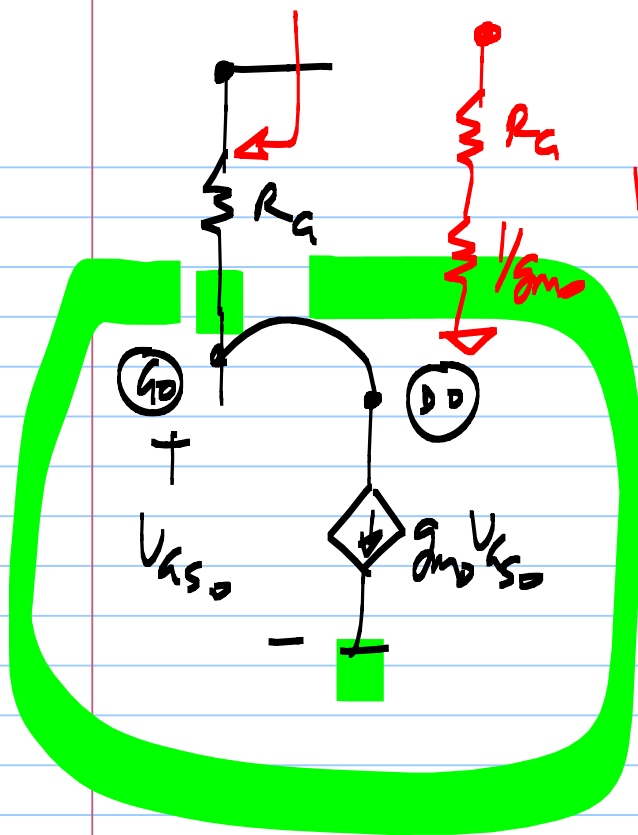
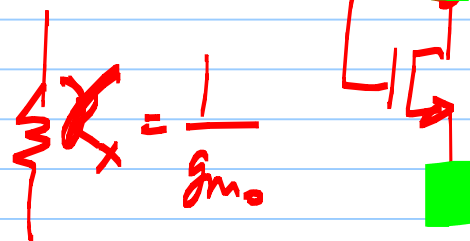
$$\frac{v_{test}}{i_{test}} = \frac{1}{g_m}$$




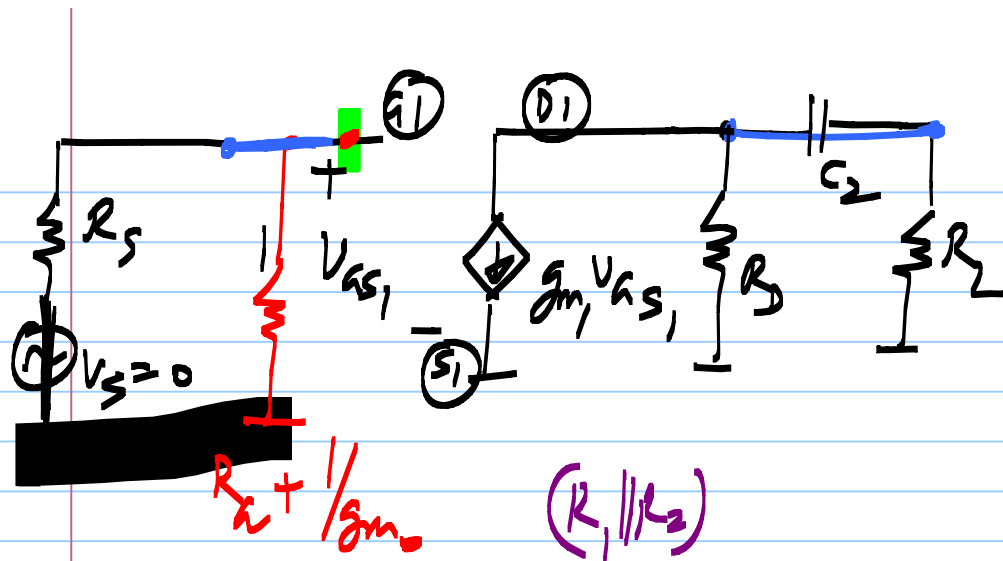


$$C_1: \frac{1}{\omega C_1} \ll \underbrace{R_s + R_a + \frac{1}{g_{m0}}}_{(R_1 \parallel R_2)}$$

$$C_2: \frac{1}{\omega C_2} \ll \underbrace{R_D + R_L}_{\checkmark}; \quad \frac{1}{\omega C_2} \ll \underbrace{R_L}_{\checkmark}$$


$$\frac{v_{GS1}}{v_s} = \frac{R_a + \frac{1}{g_{m0}}}{R_a + \frac{1}{g_{m0}} + R_s} \approx 1$$

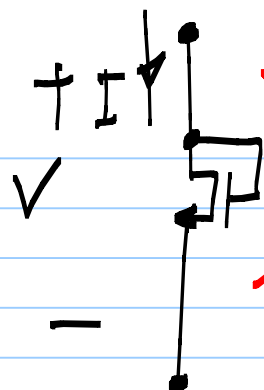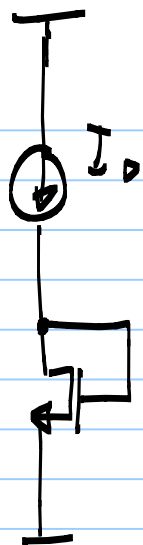$\underbrace{R_a + \frac{1}{g_{m0}} \gg R_s}_{R_1, R_2 \gg R_s}$



Diode
connected
transistor

$$V_{DS} > 0, V_{GS} > 0$$

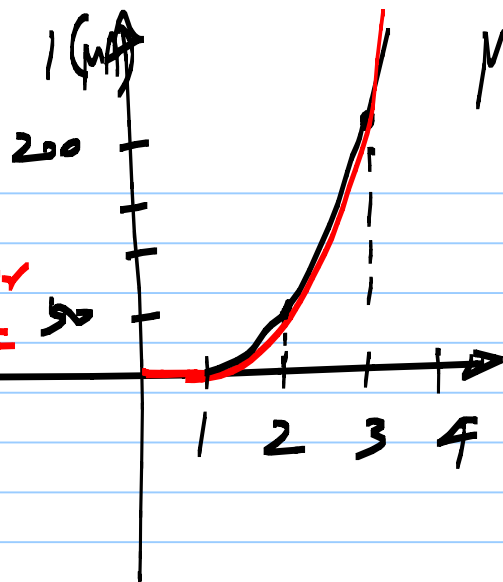

$$\mu_n C_{ox} \frac{W}{L} = 100 \mu A/V^2$$

$$V_T = 1V$$

$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2$$

$$V_T > 0$$

saturation
cutoff

$$V_{DS} < V_{GS} - V_T$$

$$V_{DS} = V_{GS}$$

Diode connected transistor: incremental picture

