

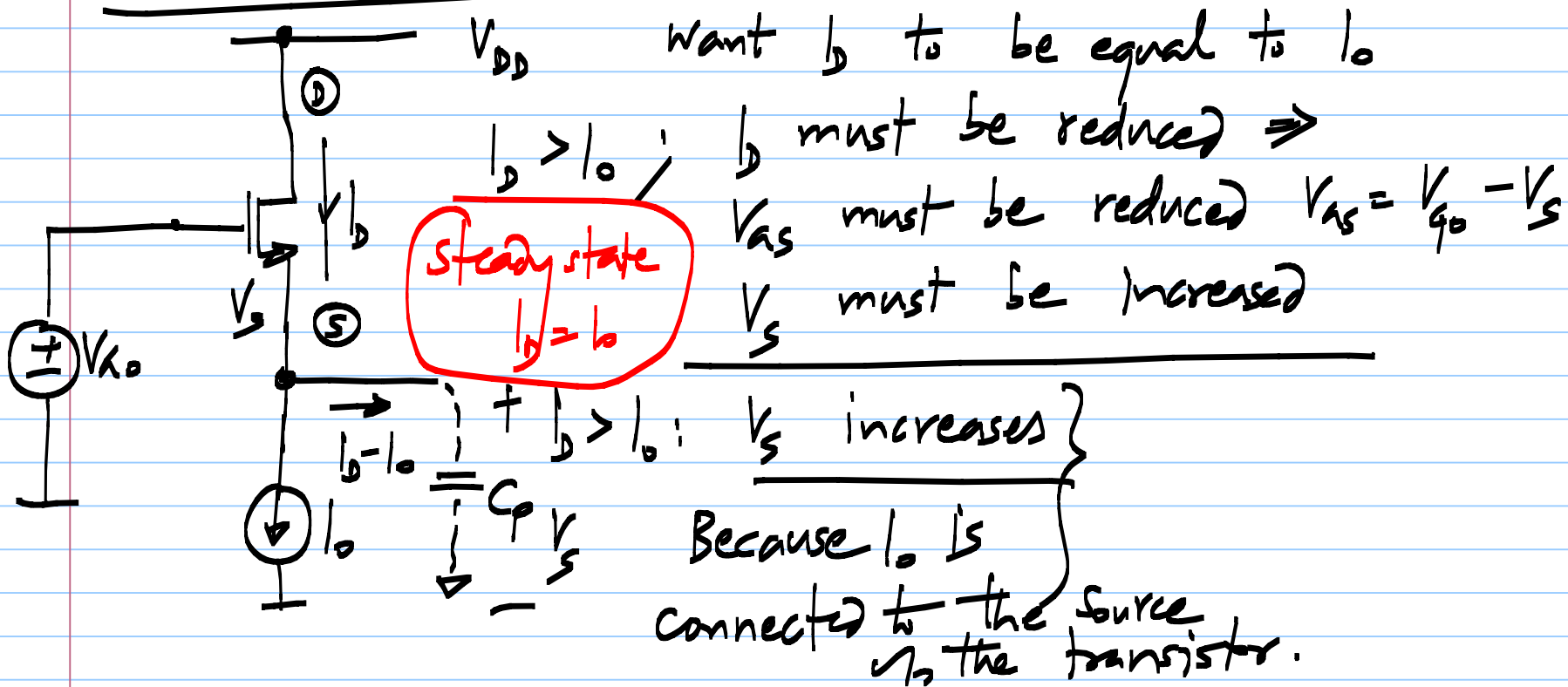


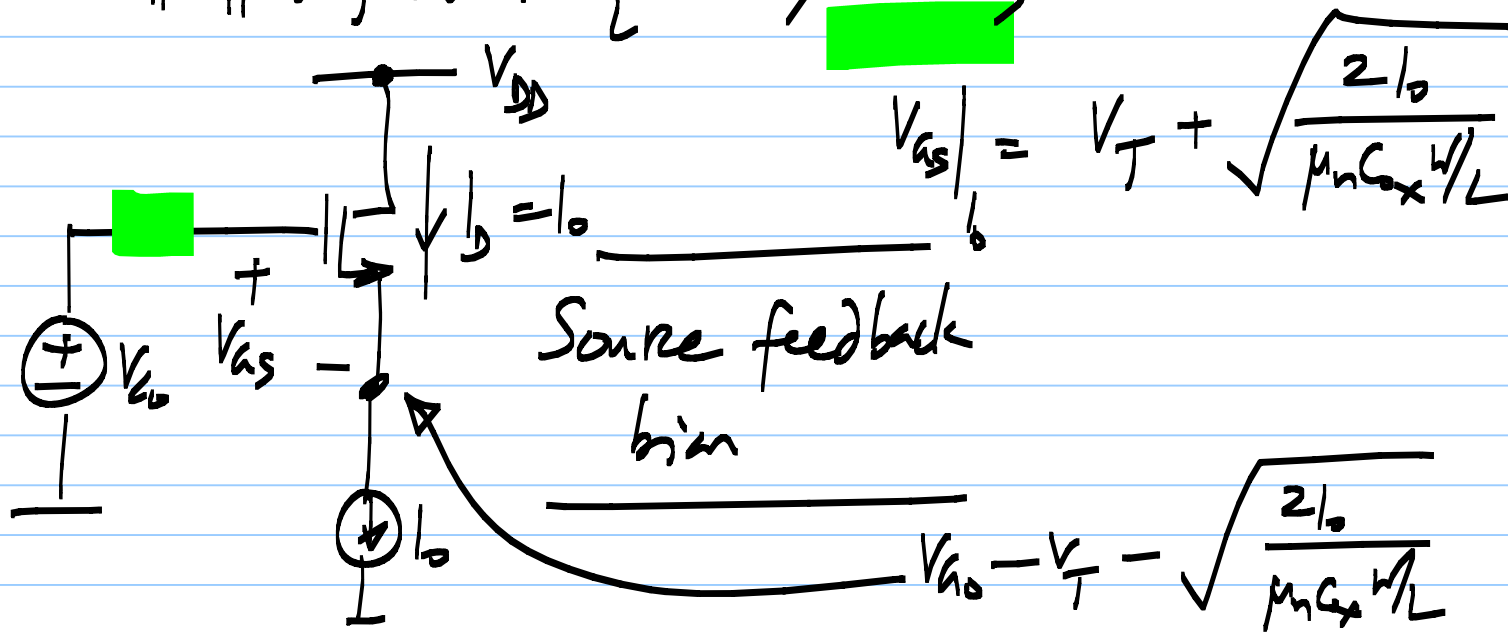Biasing @  $I_D$ : Sense at the source and feedback to the source




Controlling part: {gate, source}



Controlled part: {drain, source}

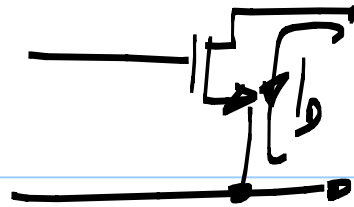


# CS amplifier using source feedback bias

$$\frac{V_o}{V_i} = -g_m R_L$$

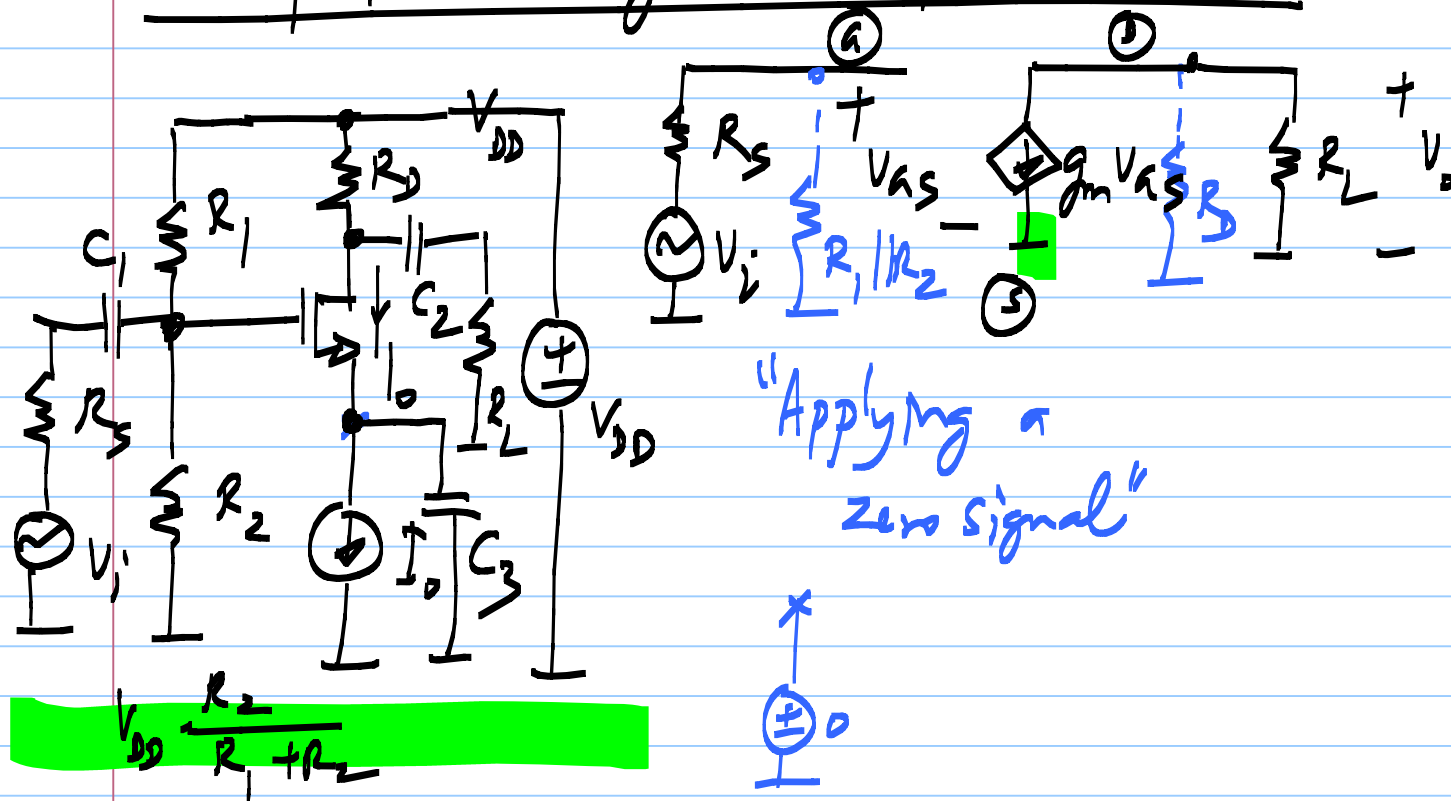


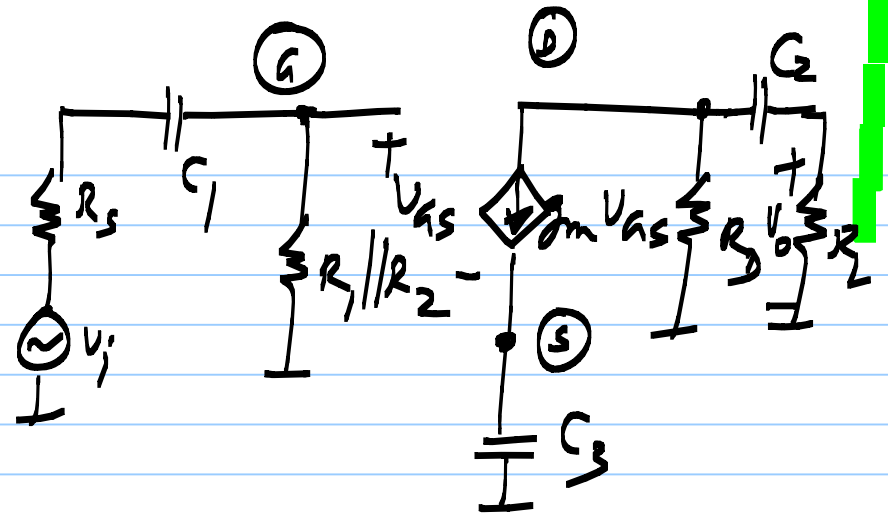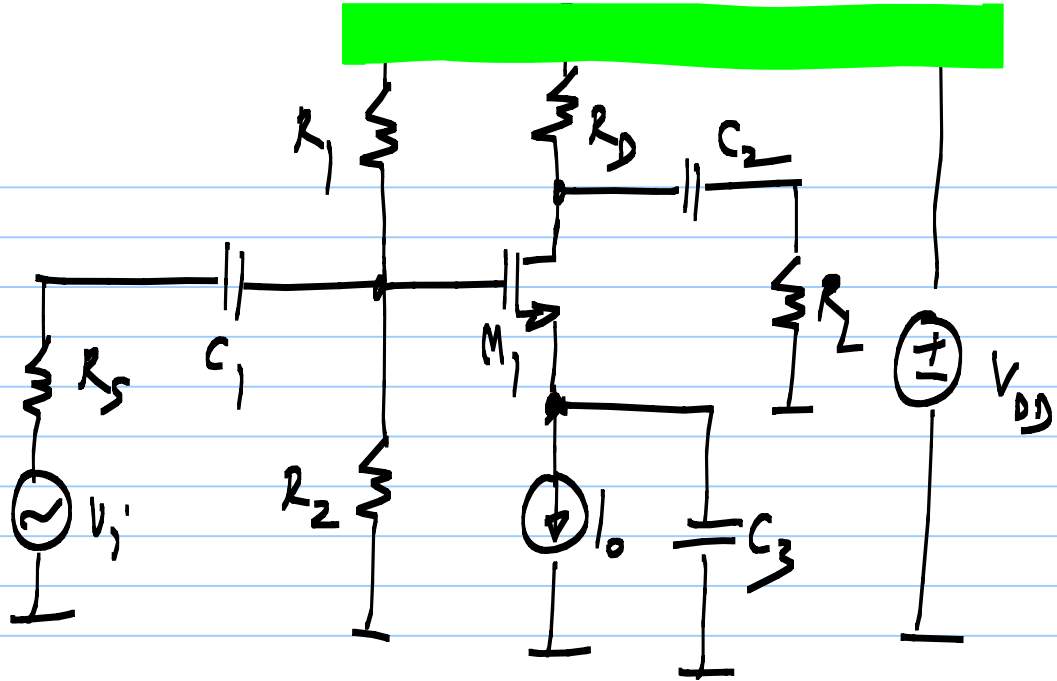

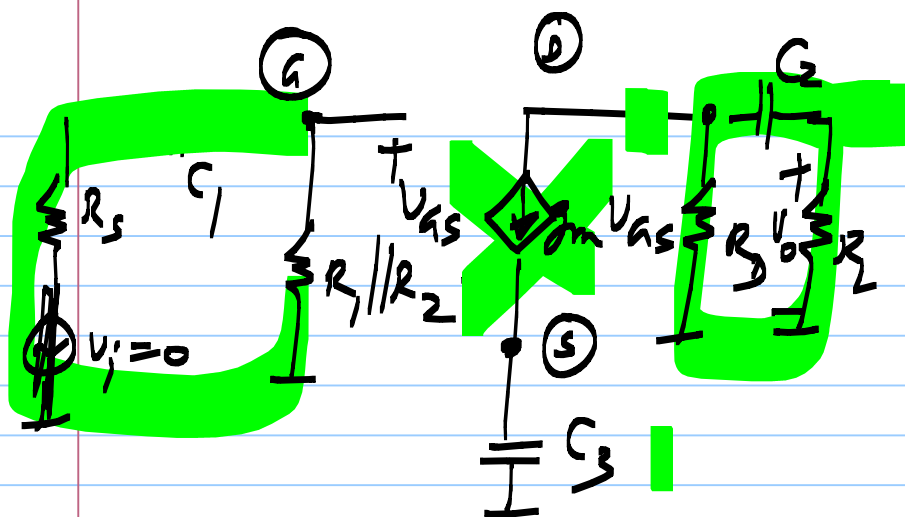

$$\frac{1}{\omega C_3} \ll R_s + (R_1 \parallel R_2)$$
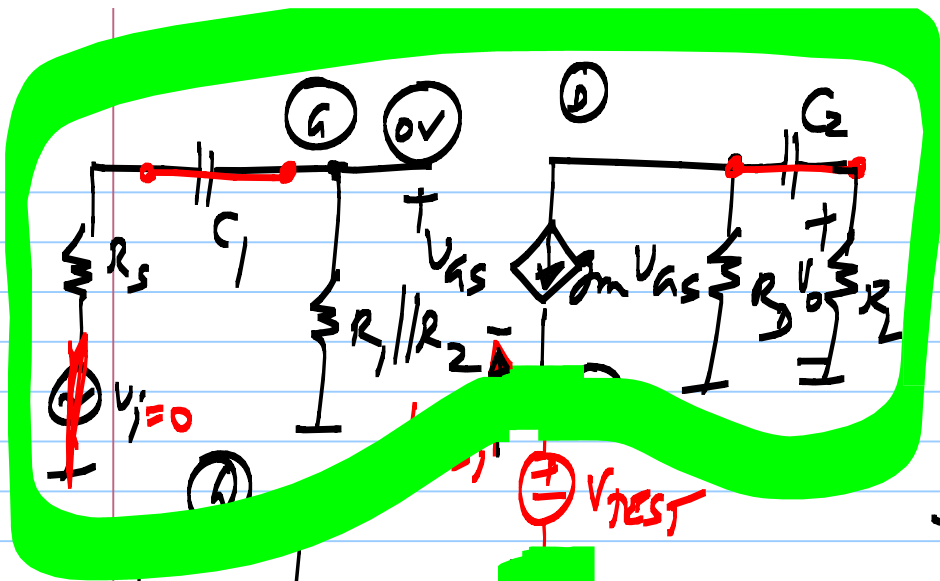
$$\left. \frac{1}{\omega C_2} \ll R_3 + R_L \right\} \frac{1}{\omega C_2} \ll R_L$$





$$V_{GS} = -V_{TEST}$$

$$I_{TEST} = -g_m V_{GS} = g_m V_{TEST}$$

$$\frac{V_{TEST}}{I_{TEST}} = \frac{1}{g_m}$$
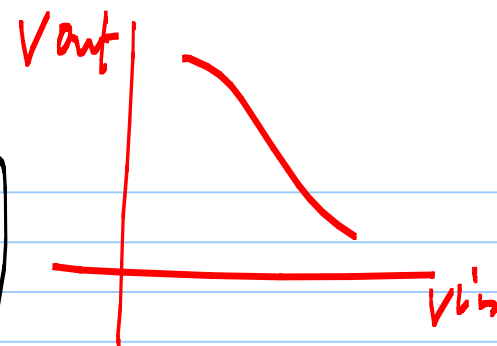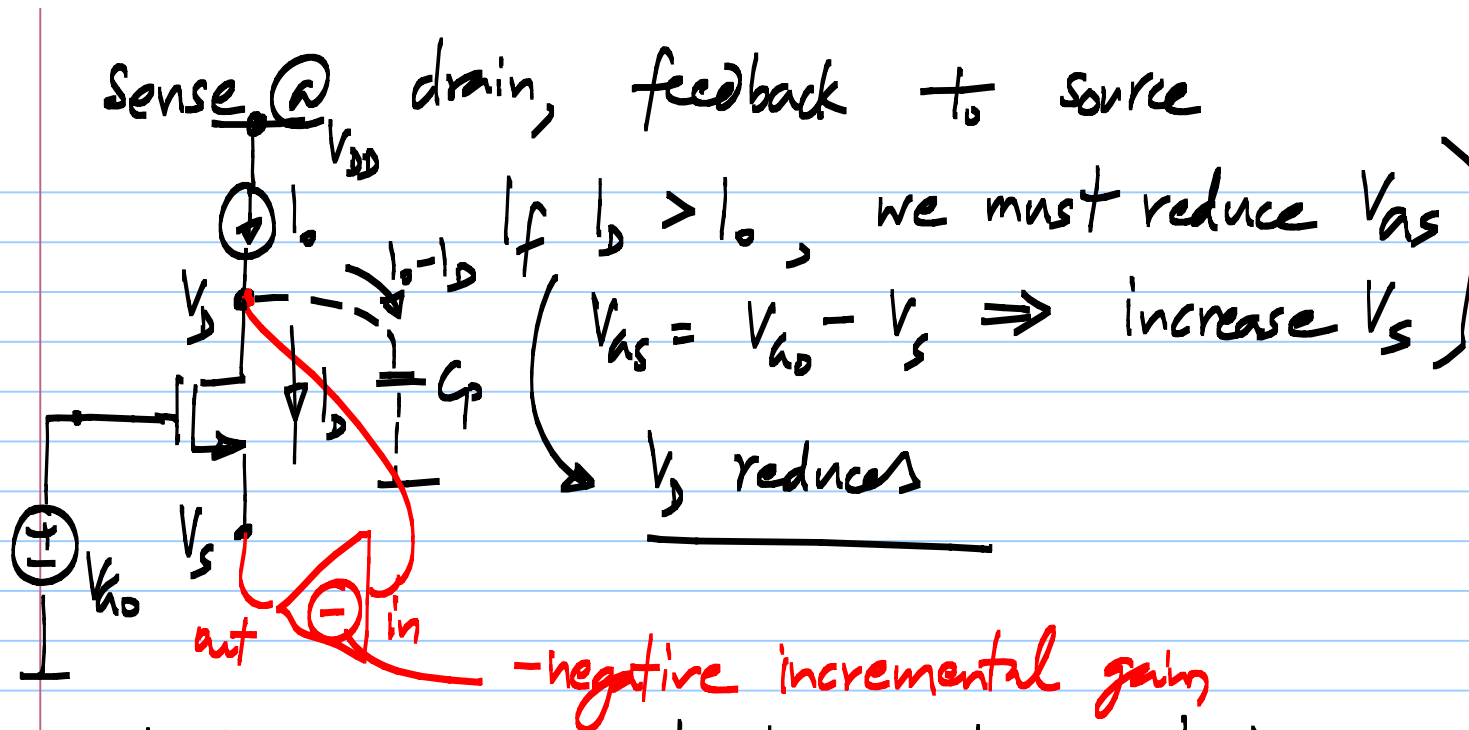
$$\frac{1}{\omega C_3} \ll \frac{1}{g_m}$$




If  $V_D$  reduces  $\Rightarrow I_D > I_0 \Rightarrow V_S$  must increase

" increases  $\Rightarrow I_D < I_0 \Rightarrow$  " decrease


Ideal opamp:


If the opamp is arranged to be in negative feedback,  $V_1 \rightarrow 0$   
virtual short

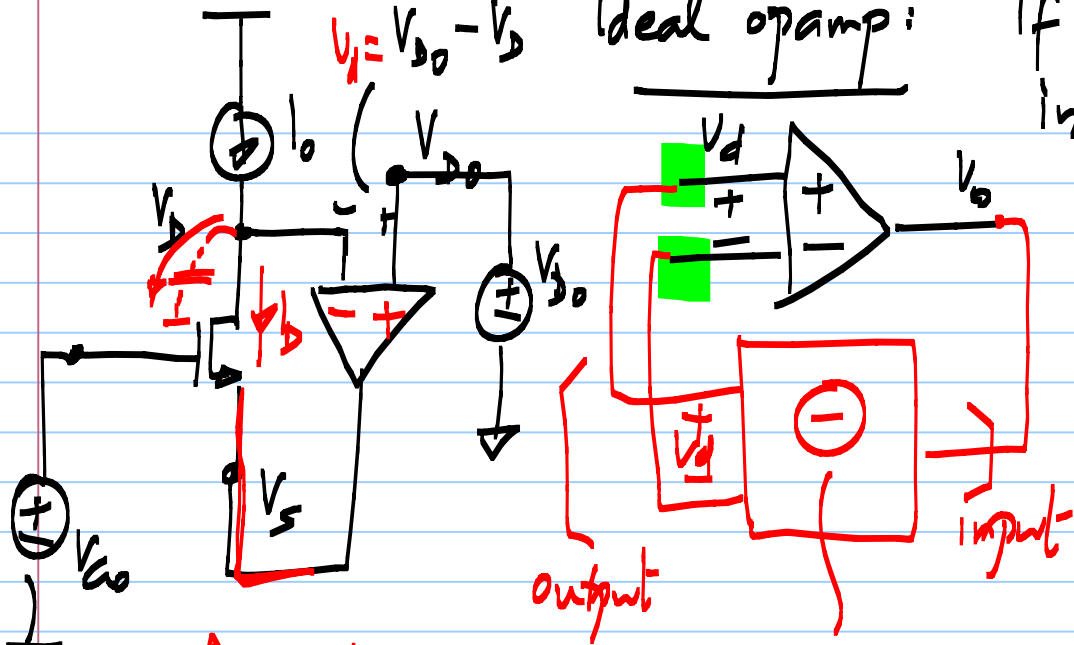
$$v_s \uparrow \Rightarrow b \downarrow \Rightarrow v_s \uparrow$$
$$V_d = V_o - V_D$$

$V_d$  reduces if  $V_o$  increases

sense @ source, fb to gate

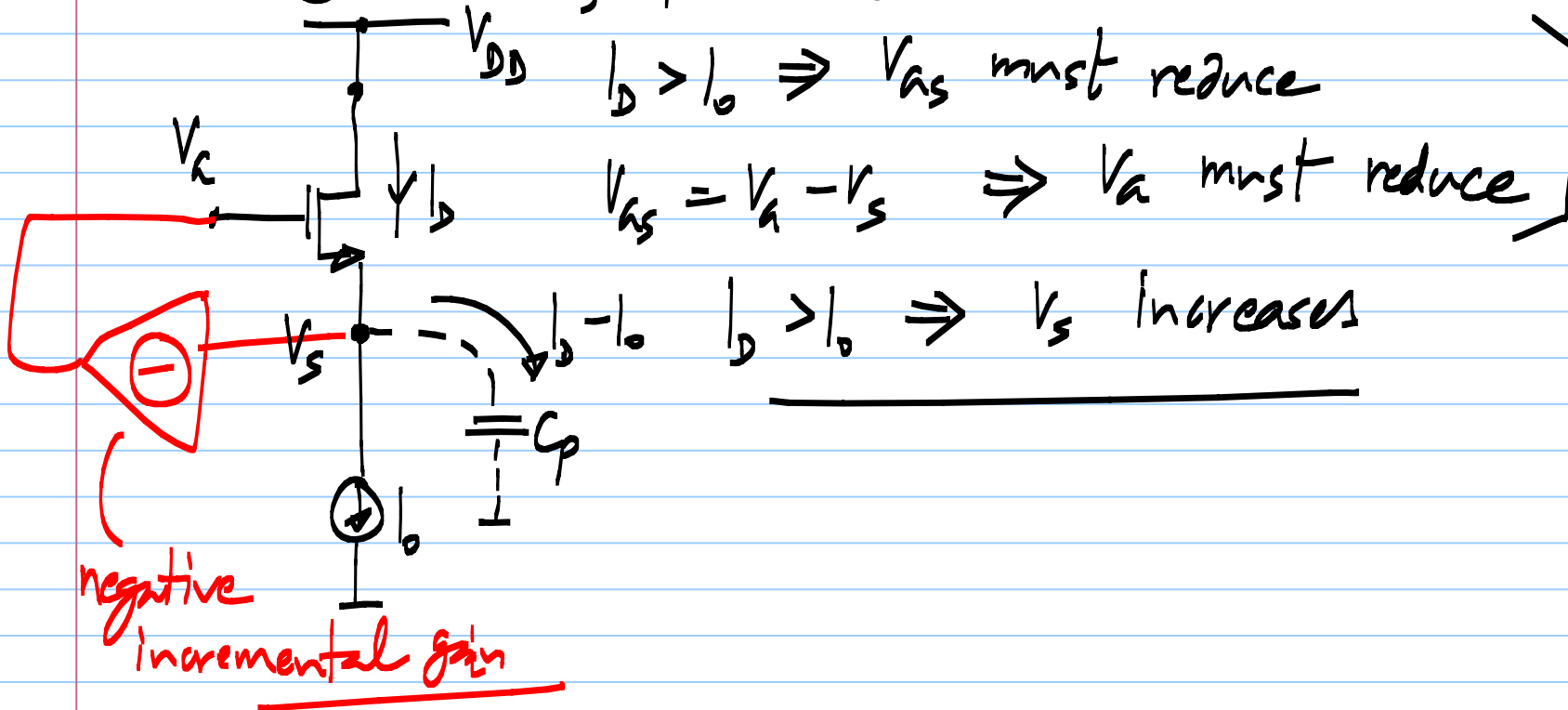

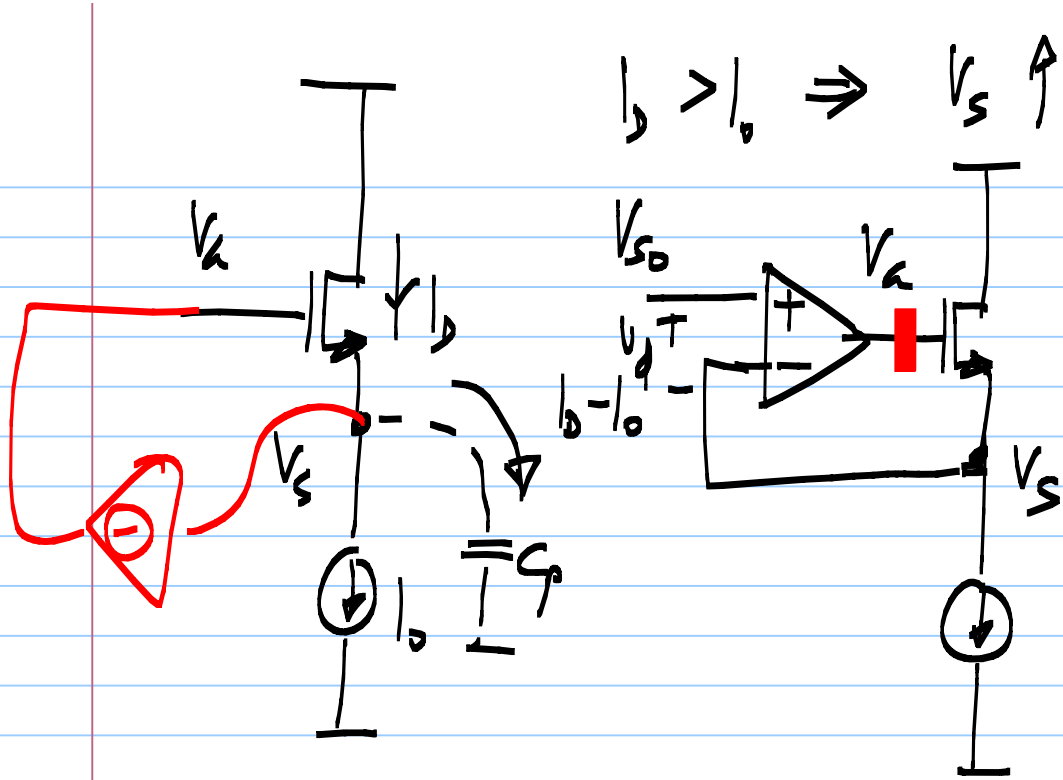

sense :

drain

source

drain

source






fb :

gate

source


source

gate

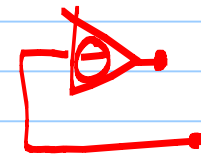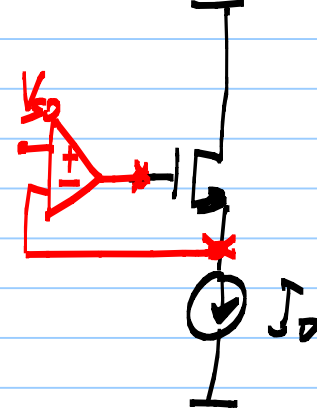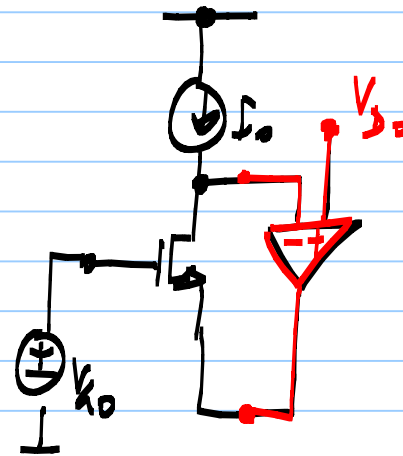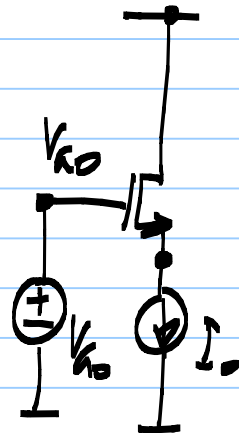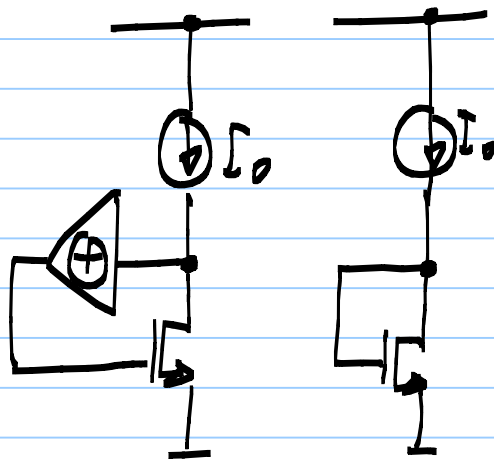




$$\underline{V_{DS} > V_{GS} - V_T}$$

Saturation region

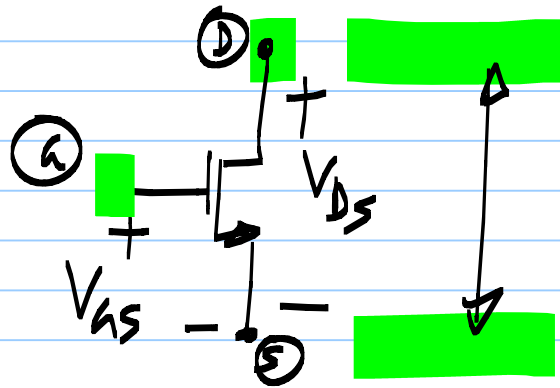


$$V_{DS} > V_{GS} - V_T ; \quad V_D > V_G - V_T$$
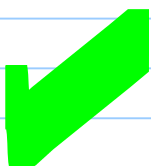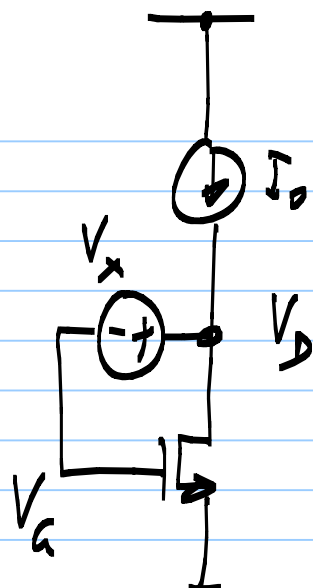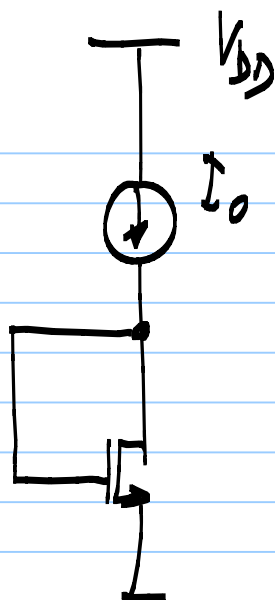
$$V_D - \cancel{V_S} > V_G - \cancel{V_S} - V_T \quad \begin{matrix} V_G - 1V \\ 3V - 1V \end{matrix} \quad \frac{V_{GD} < V_T}{\text{---}}$$




$$\left. \begin{aligned} V_D &= V_A + V_x \\ V_D &> V_A - V_T \end{aligned} \right\} \underline{V_x > -V_T}$$

$$V_{DD} > V_{A0} - V_T$$

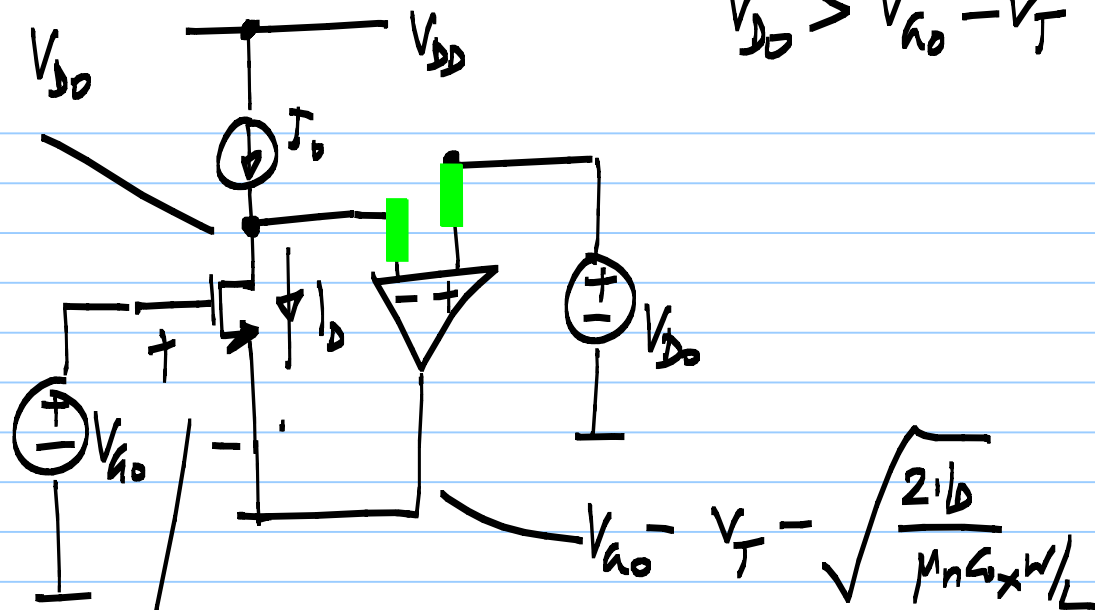


$$V_{A0} = V_T + \sqrt{\frac{2 \cdot I_D}{\mu_n C_{ox} W/L}}$$


sense : drain  
fb : gate

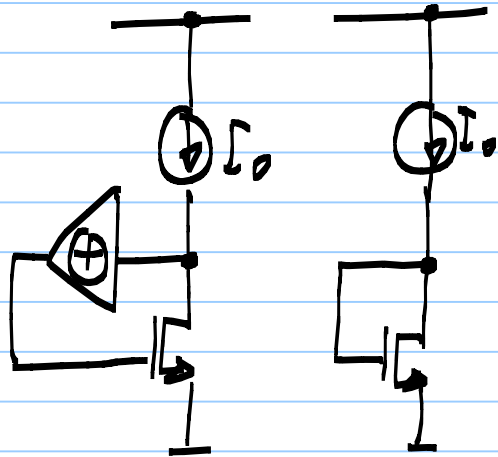


source  
source

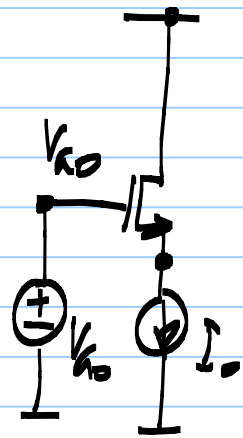


drain  
source

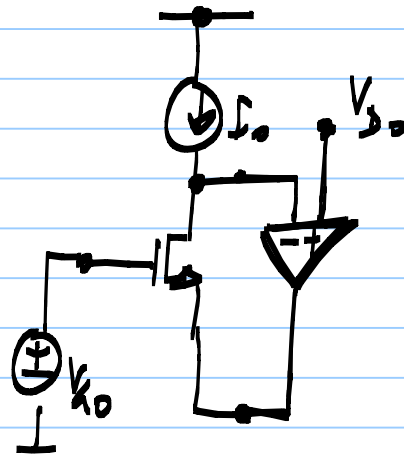


source  
gate

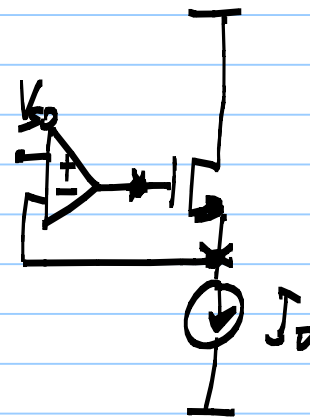




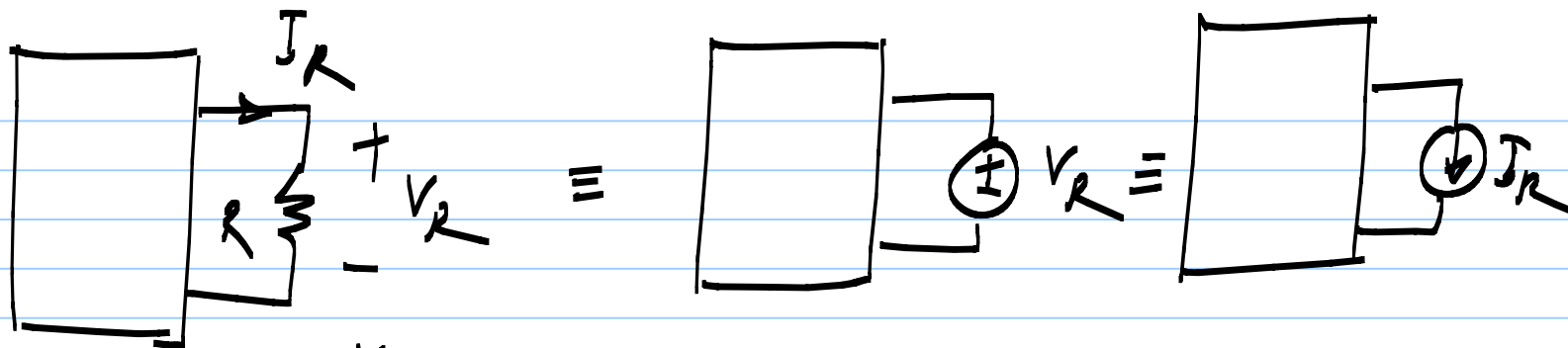

$$\underline{R = \frac{V_R}{I_R}}$$

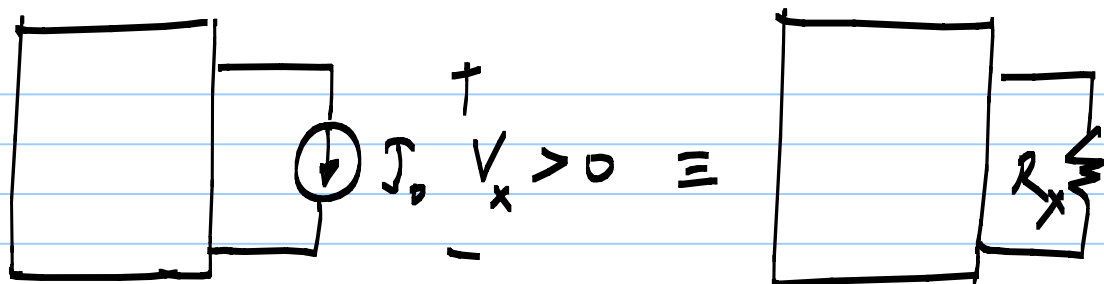

$$r_x = \frac{V_x}{i_o}$$

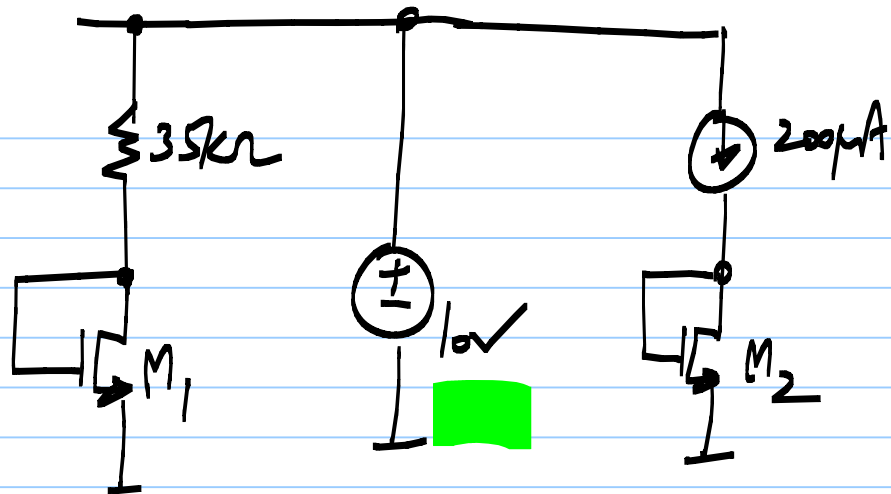


$V_T \uparrow$  :  $M_2$  :  $I_D = 200\mu A$  ;  $g_m = 200\mu S$   
 (no change)

$V_T \uparrow$  :  $M_1$  :  $I_D \downarrow$  ;  $g_m \downarrow$

Other electronic devices.


Triode (plate)

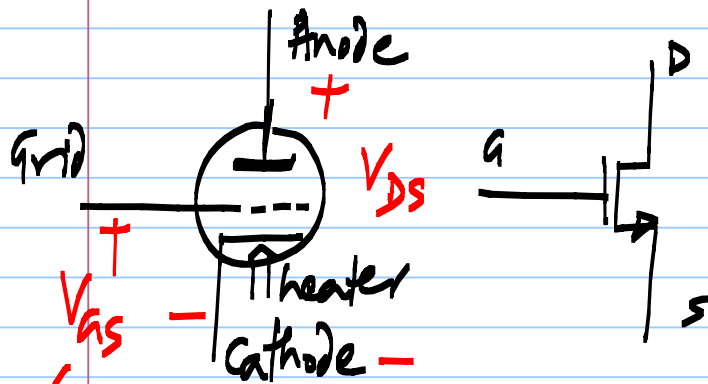


$V_{GS}$


$V_{GS} < 0$

$V_{DS} \sim 100s\ of\ V$

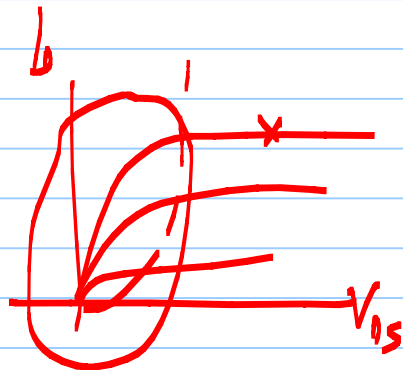


Triode:  $I_{out}$  vs.  $V_{out}$

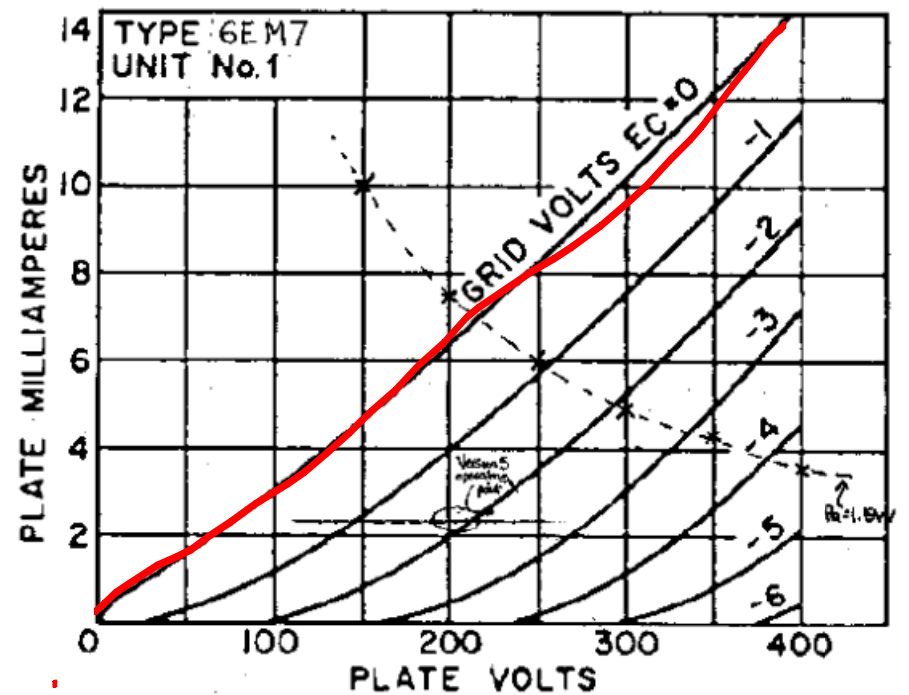


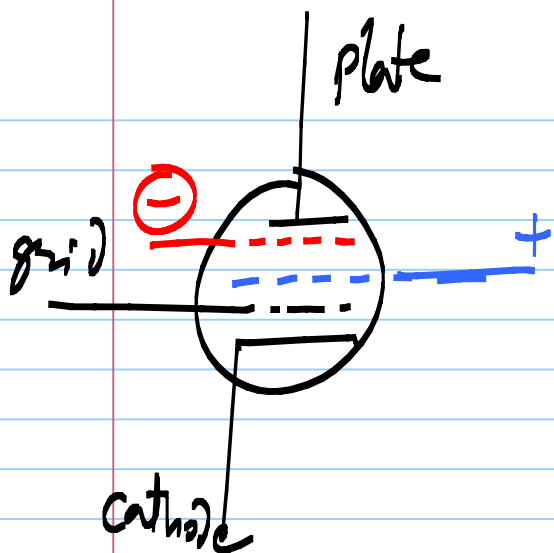

Tetrode  
Pentode


Pentode:  $I_{out}$  vs.  $V_{out}$

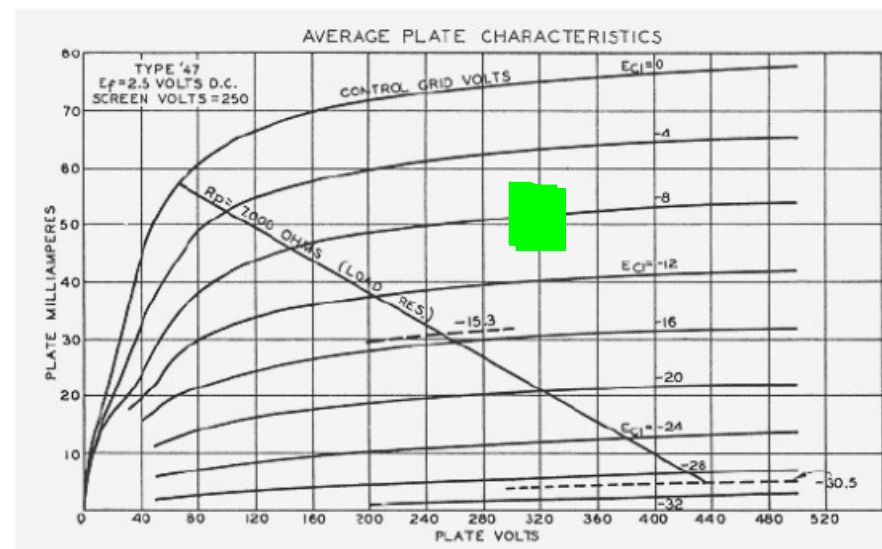


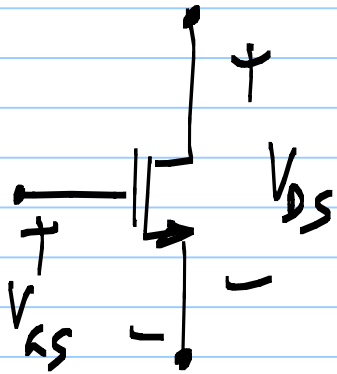


## nMOS: $I_{out}$ vs. $V_{out}$

$V_{GS}$ : 0 to 1.5V in 0.25V steps

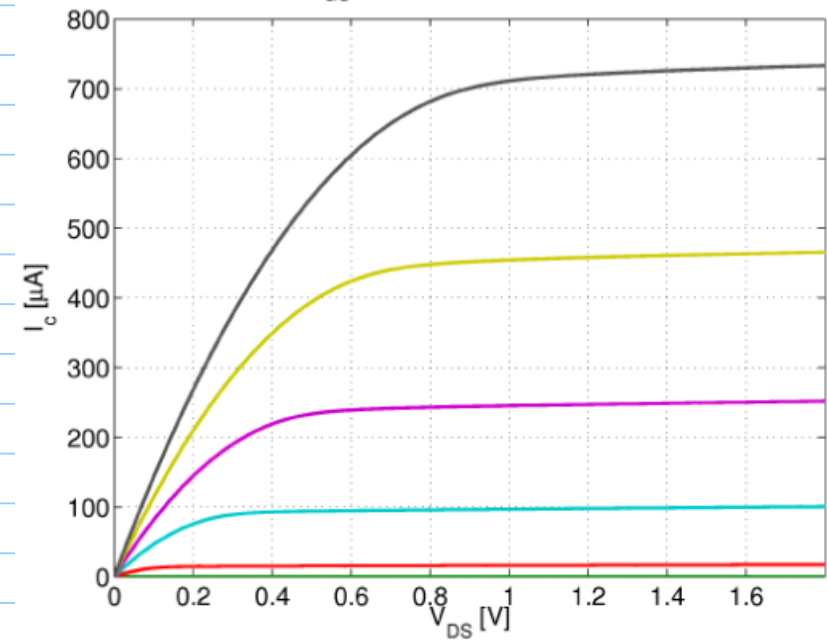

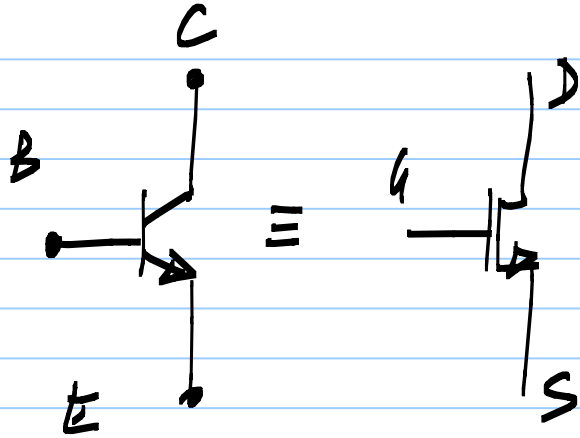


NPN:  $I_{out}$  vs.  $V_{out}$

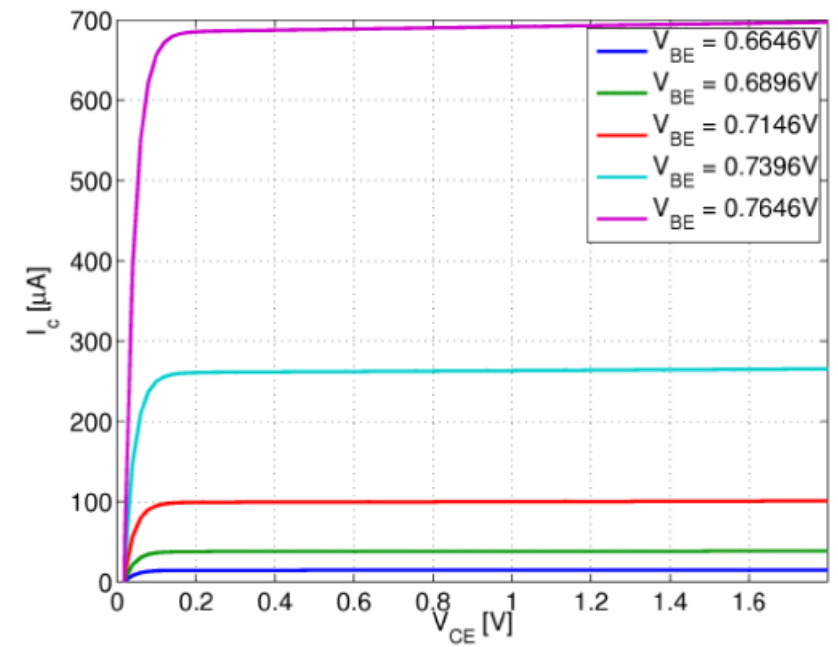

Commercially  
available


$I_D$  vs  $V_{DS}$


## 2N7000 (MOS): $I_{out}$ vs. $V_{out}$

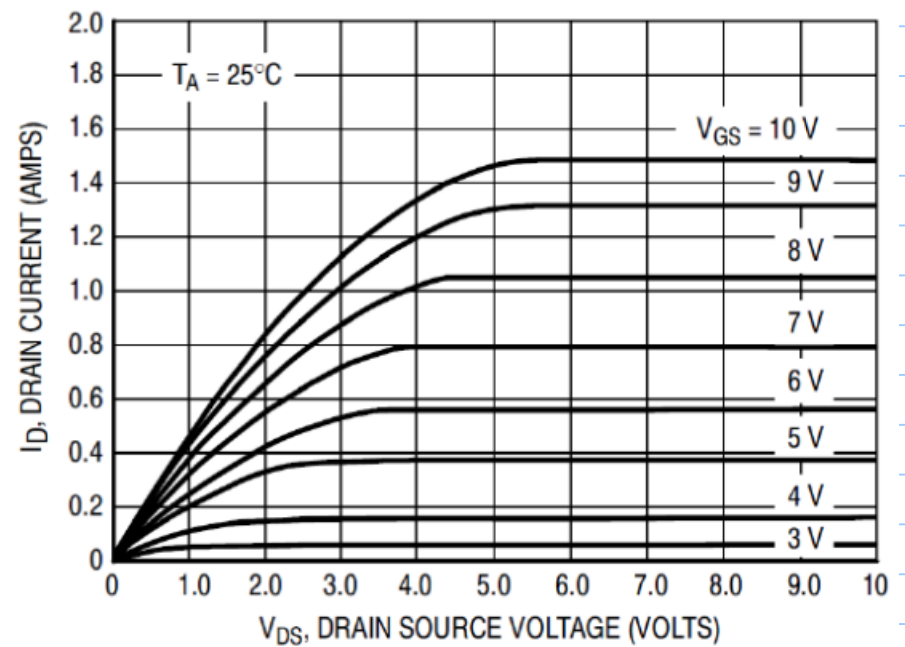


$I_D$  vs  $V_{GS}$

2N7000 (MOS):  $I_{out}$  vs.  $V_{in}$

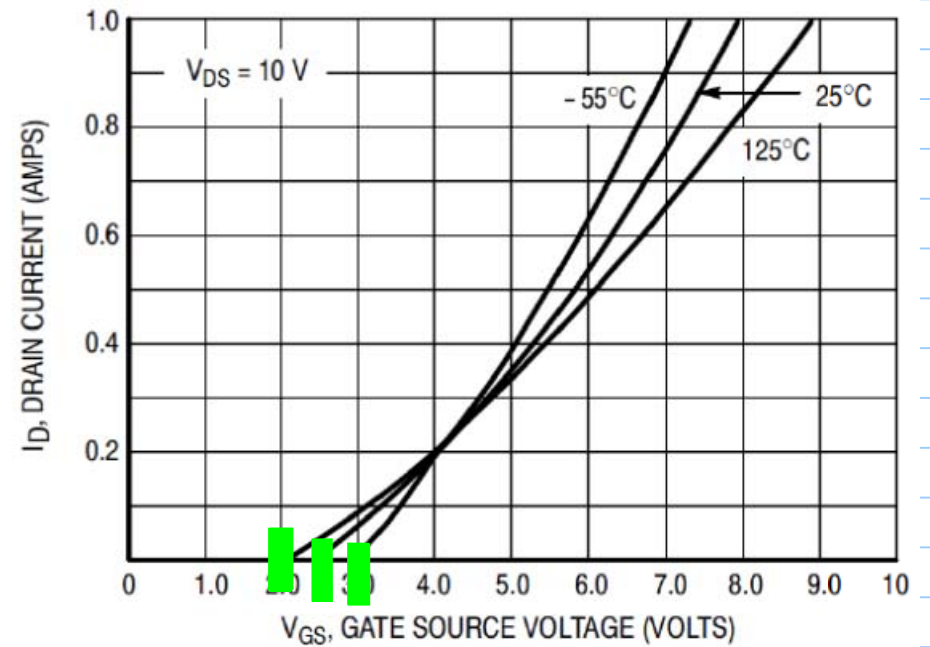

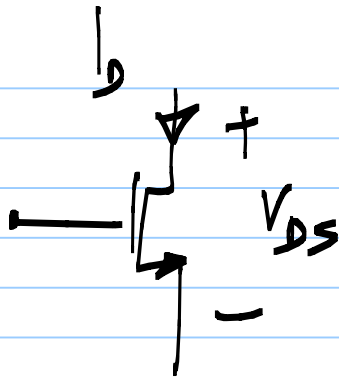


## Graphene FET: $I_{out}$ vs. $V_{in}$

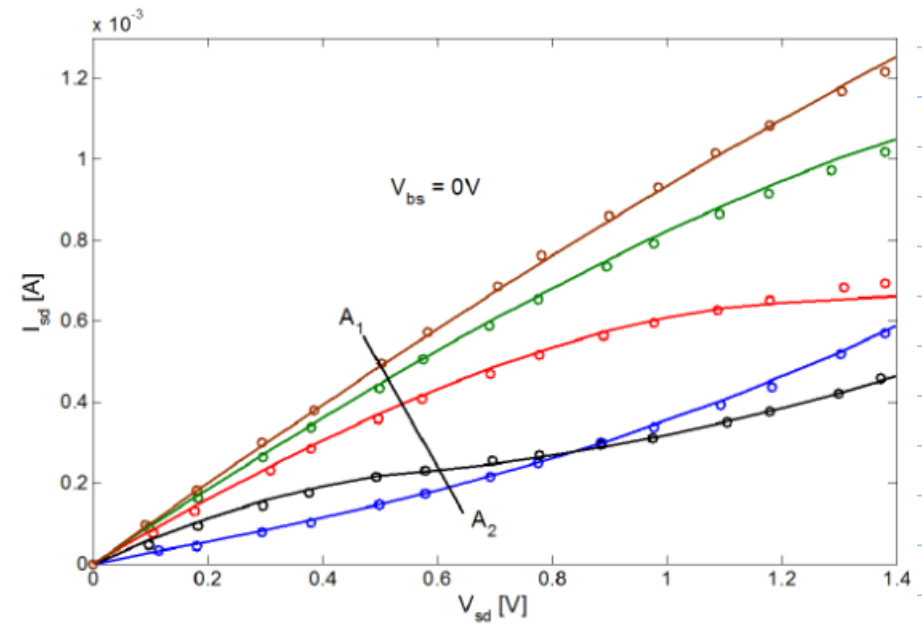

Source: [http://www.cnt.ecs.soton.ac.uk/gfet\\_web/model.htm](http://www.cnt.ecs.soton.ac.uk/gfet_web/model.htm)


# Organic transistors

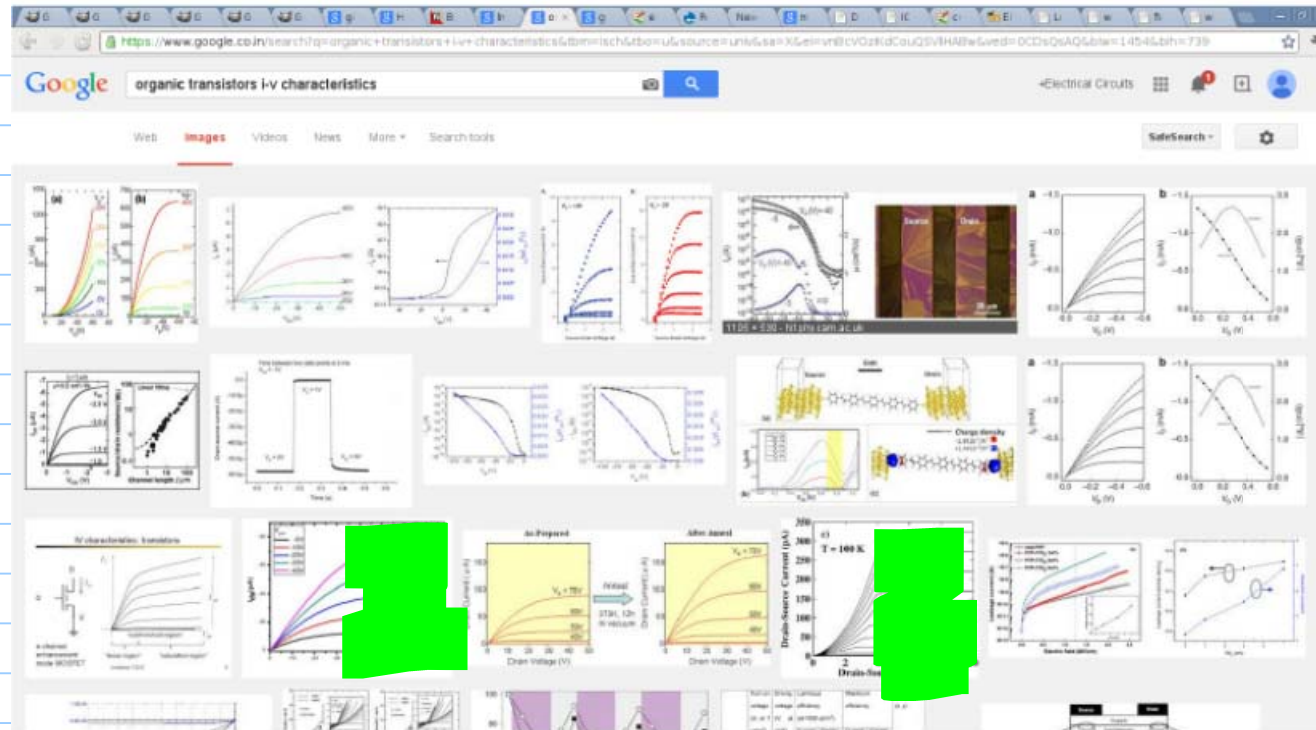


Source: Google image search "organic transistors i-v characteristics"

<https://www.google.co.in/search?q=organic+transistors+i-v+characteristics&tbm=isch&tbo=u&source=univ&sa=X&ei=vnBcVOzKdCauQSVIHABw&ved=0CDsQsAQ&biw=1454&bih=739>

## TFT transistors

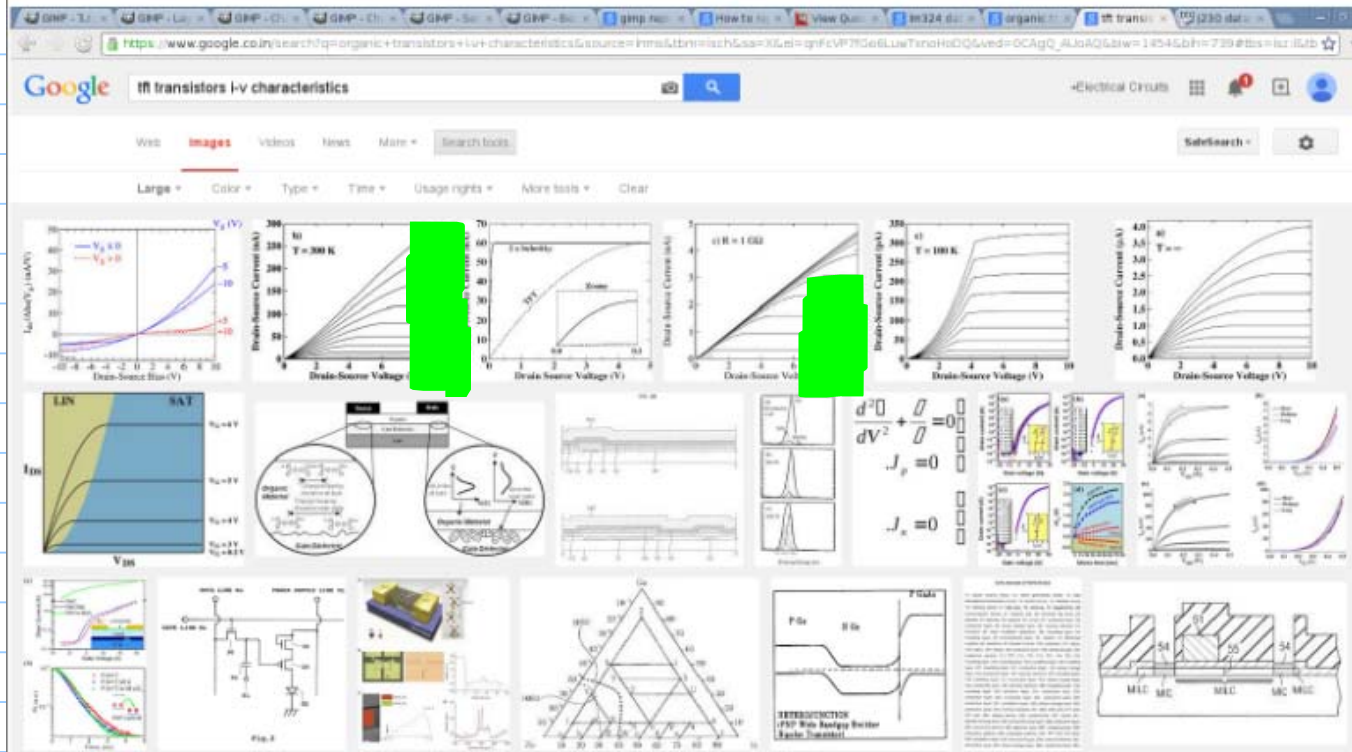

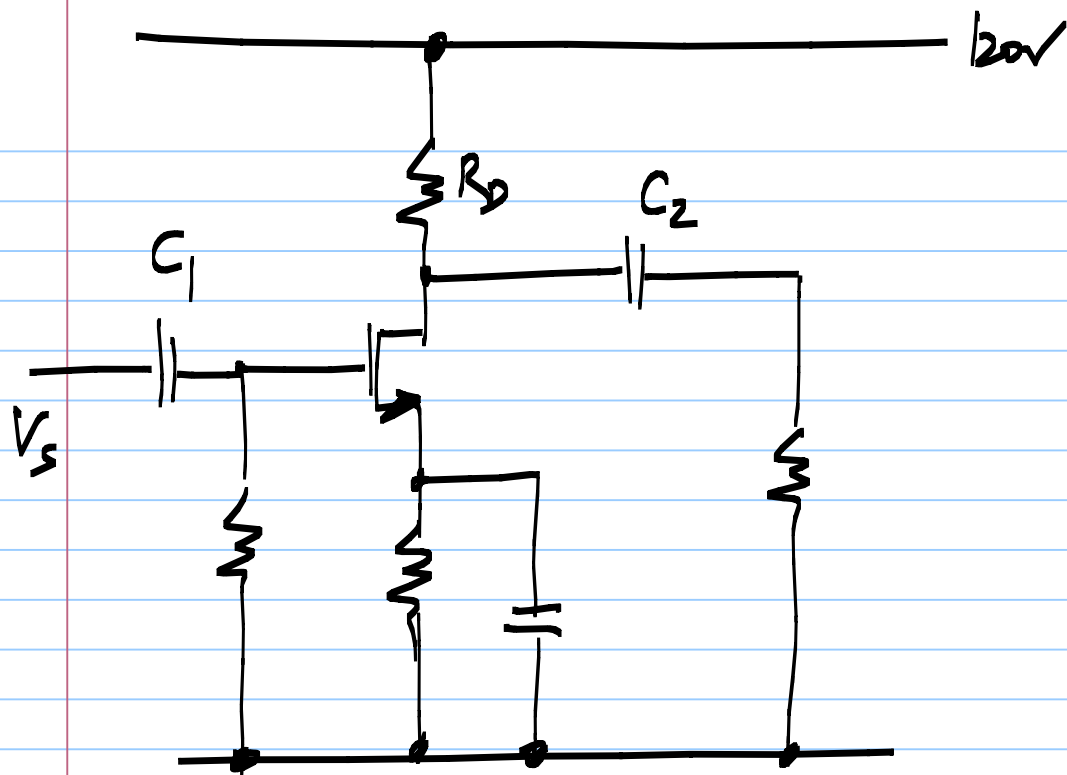Source: Google image search "tft transistor i-v characteristics" [https://www.google.co.in/search?q=tft+transistor+i+v+characteristics&source=inms&tbm=isch&sa=X&ei=EatgVjIAHIPvUQT45IKYAQ&ved=0CAgQ\\_AUoAQ&biw=1454&bih=739](https://www.google.co.in/search?q=tft+transistor+i+v+characteristics&source=inms&tbm=isch&sa=X&ei=EatgVjIAHIPvUQT45IKYAQ&ved=0CAgQ_AUoAQ&biw=1454&bih=739)



$$V_{gs} = -2.5V$$


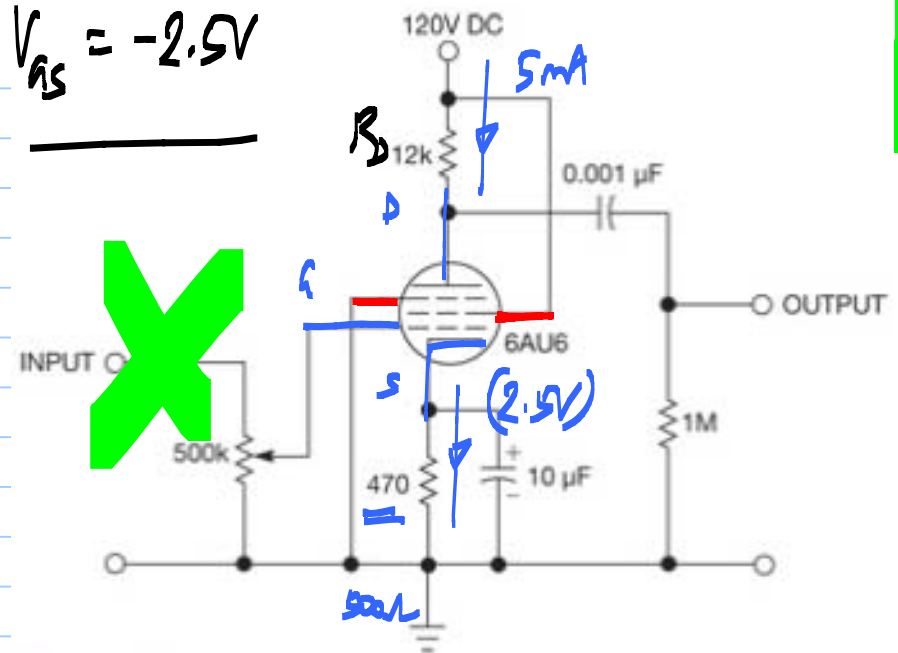



Figure 1 A 6AU6 pentode vacuum tube needs a quiescent plate current of approximately 5 mA.

Triode (plate)

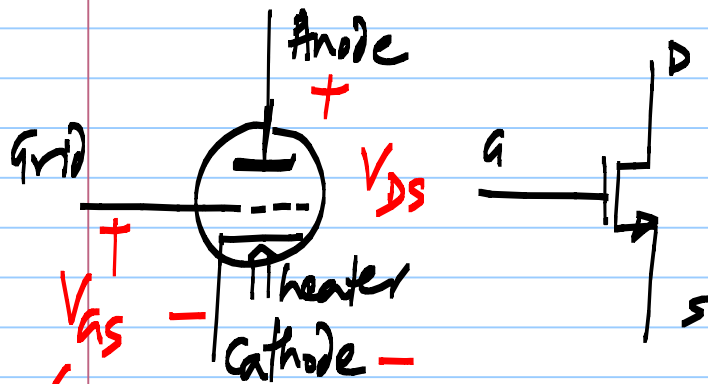


$$V_{GS} < 0$$


$$V_{DS} \sim 100s \text{ of } V$$

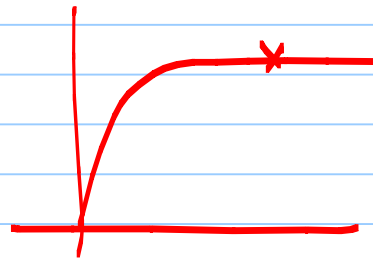

Triode:  $I_{out}$  vs.  $V_{out}$

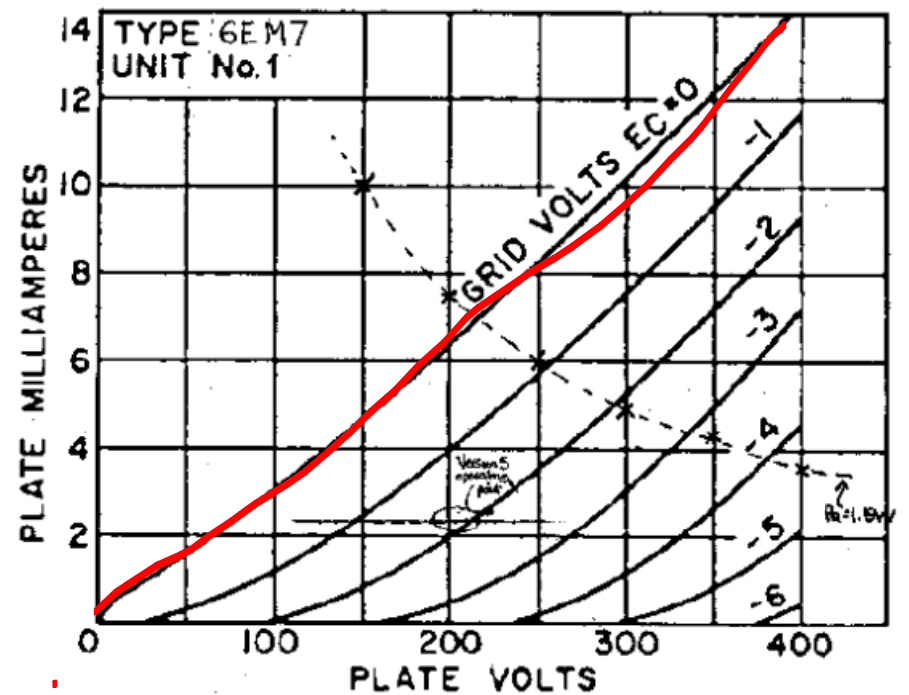

## CS amplifier

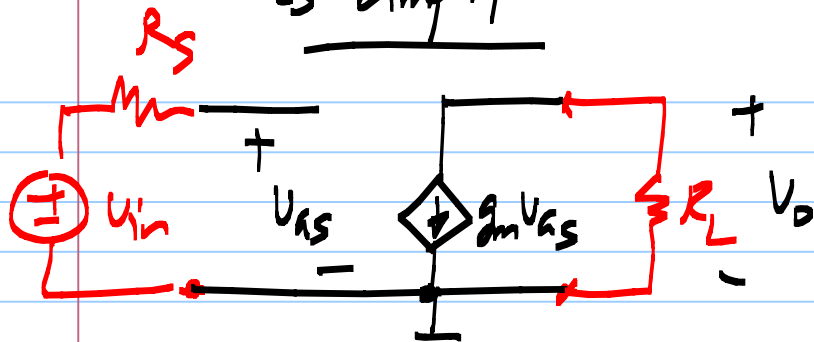

$$\frac{v_o}{v_{in}} = -g_m R_L$$


## Controlled sources

VCVS

VCCS




CCCS

CCVS

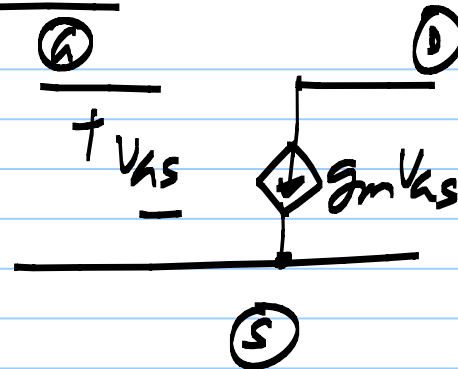


-ve fb: sense difference between desired & actual;  
drive the actual output in a way that  
reduces the difference.

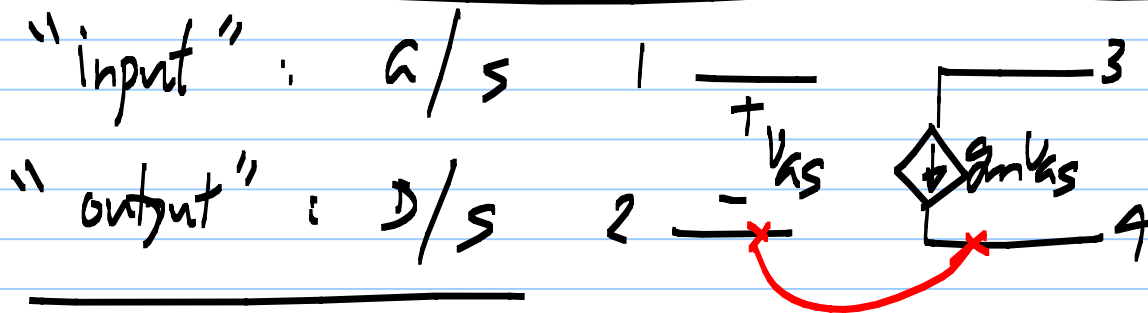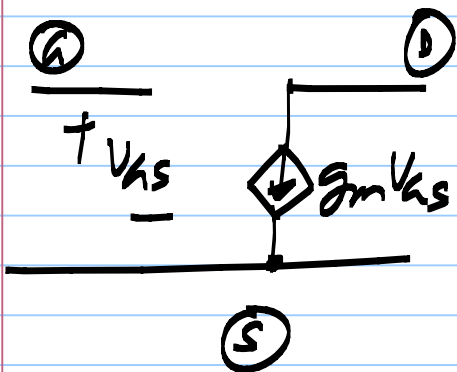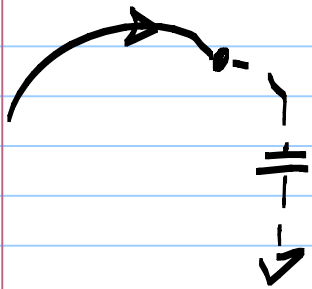Increase node voltage: push a current into it  
 Reduce node voltage: pull a current out of it



# Voltage controlled voltage source

$$V_o = k \cdot V_i$$

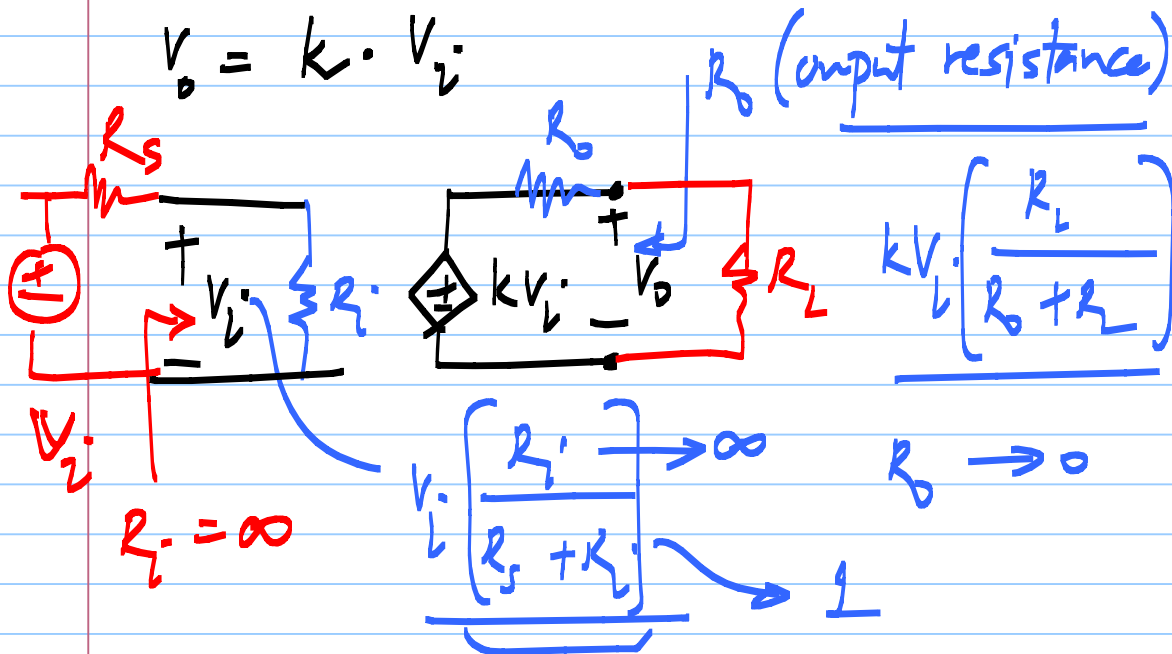

$$R_i = \infty ; R_o = 0$$


$R_i$  very large  $\Rightarrow$  expected  $R_s$

$R_o$  very small  $\leftarrow$  expected  $R_L$

$\rightarrow 1$

Realizing a VCVS using an MOS transistor.

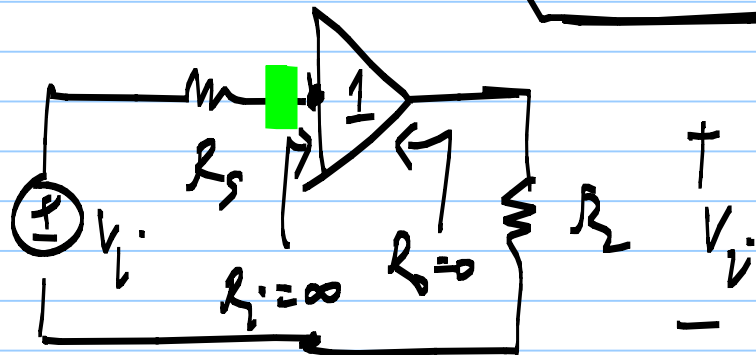VCVS  $k=1$   $V_o = V_i$   $R_i \rightarrow \infty$  ;  $R_o \rightarrow 0$




Voltage buffer


VCVS with  $K=1$
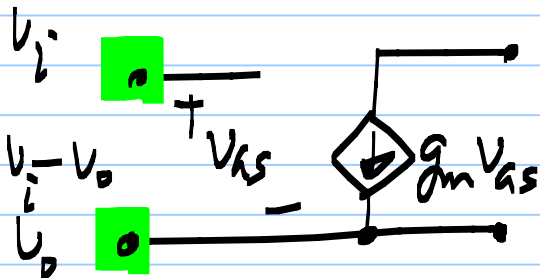
## Voltage buffer using a MOS transistor

$$V_o = V_i$$

$$V_{gs}: \left. \begin{array}{l} V_i - V_o \\ V_o - V_i \end{array} \right\} V_o = V_i$$




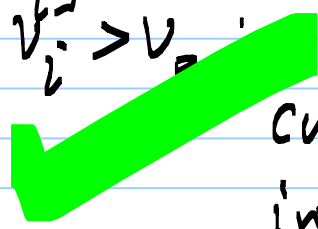  $V_i > V_o$  :  $V_o$  must be pushed up  
current must be pushed into the o/p node


$V_i < V_o$  :  $V_o$  must be pulled down

$V_{gs} > 0$  : current is pushed into the source  
of the MOS  
transistor

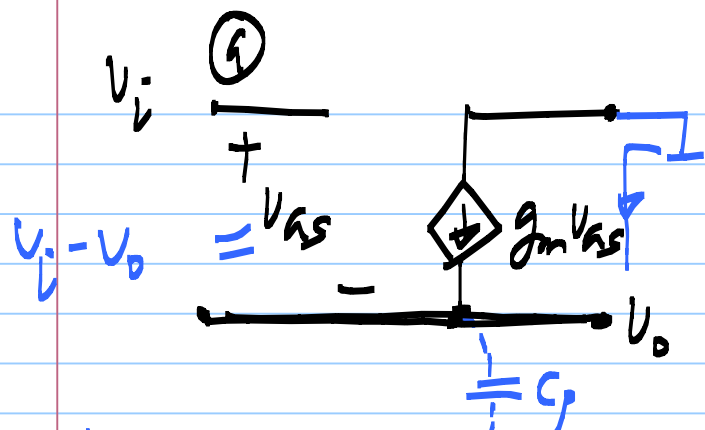current must be pulled  
out of the o/p node



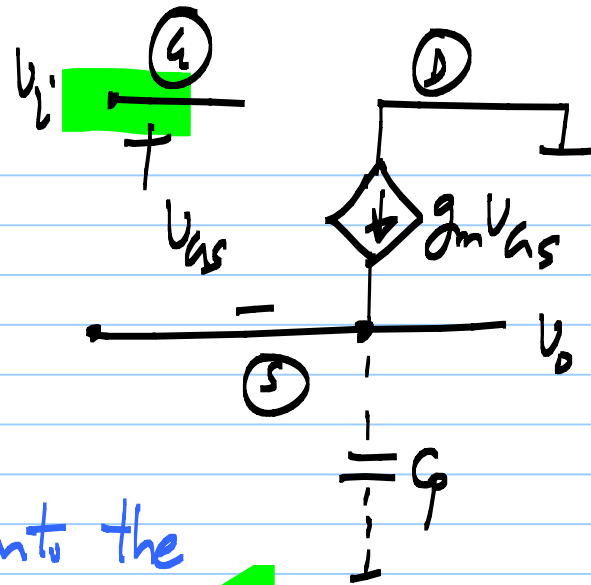
$v_i > v_o$ : current pushed into the  
 source node  
 $v_o$  increases



In steady state  
 $v_o = v_i$   


---

 $k = 1$   
 $R_i = \infty$

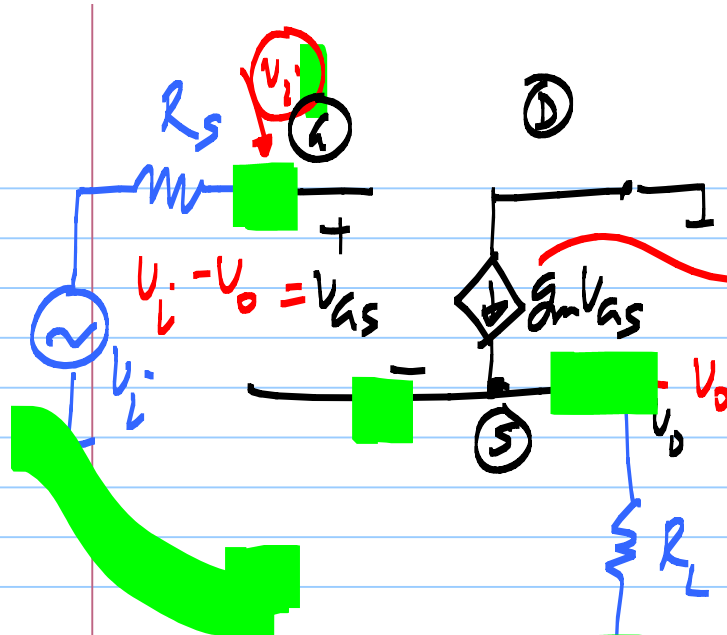

$$v_o = v_i$$


$$v_o = \frac{g_m R_L}{1 + g_m R_L} \cdot v_i \approx \frac{g_m}{g_m + g_L} \cdot v_i$$

$R_i = \infty$   
 $R_o = 0$


$\approx 1$  if  $g_m R_L \gg 1$   
 $g_m \gg g_L$

load conductance  $g_L = 1/R_L$
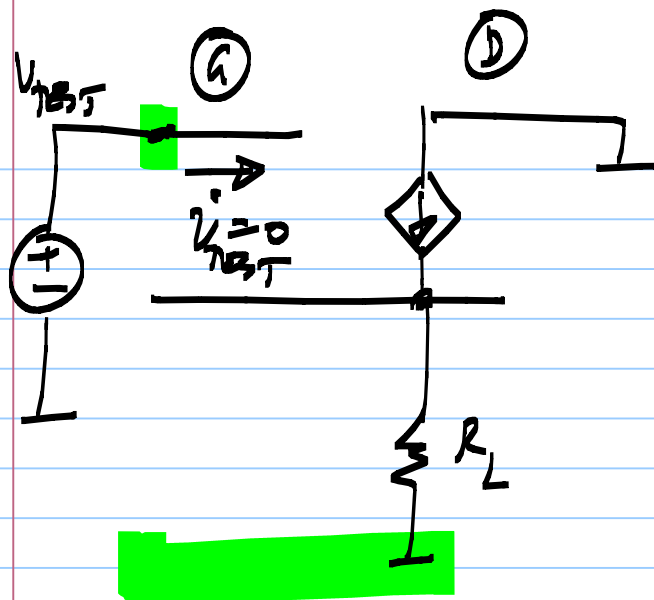
$$g_m(v_i - v_o) = v_o/R_L = v_o \cdot g_L$$


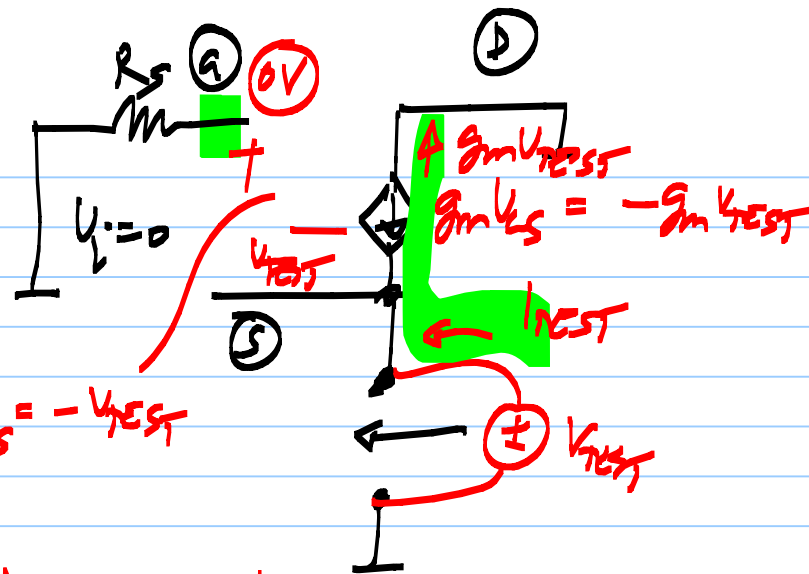
$$R_{in} = \frac{V_{TEST}}{i_{TEST}} = \infty$$



$$R_{out} = \frac{V_{TEST}}{i_{TEST}} = \frac{V_{TEST}}{g_m V_{TEST}} = \frac{1}{g_m}$$

$$R_{out} = 0 \text{ (ideal)}$$


$$R_{out} = \frac{1}{g_m}$$

$R_{out} \ll R_L$  in a VCVS

$$\left. \begin{array}{l} \frac{1}{g_m} \ll R_L \\ g_m R_L \gg 1 \\ g_m \Rightarrow \frac{1}{R_L} \end{array} \right\} \text{Same on the condition to get } v_o/v_i = 1$$

$$\frac{v_o}{v_i} = \frac{g_m R_L}{g_m R_L + 1} \approx 1 \quad \text{if } g_m R_L \gg 1$$
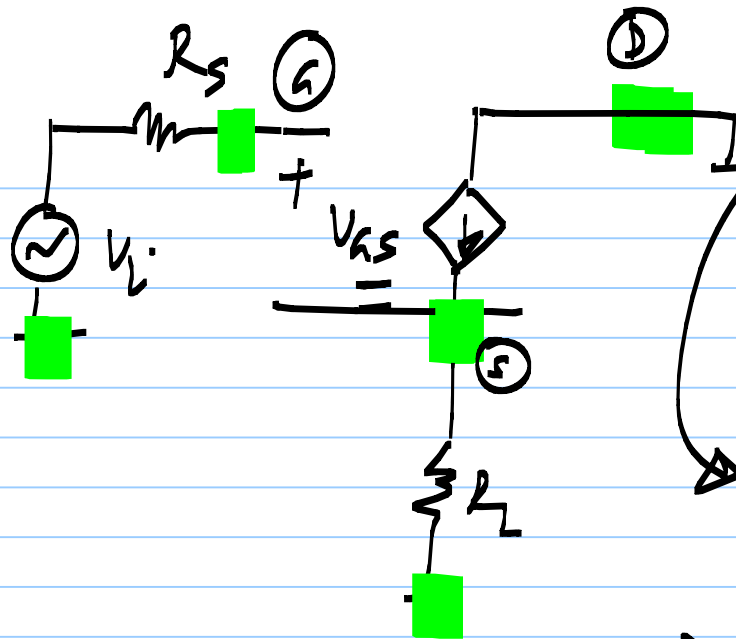
$$R_{in} = \infty ; \quad R_{out} = \frac{1}{g_m} \ll R_L$$




Common drain amplifier

$$V_o = V(\text{source}) \simeq V_i = V(\text{gate})$$

Source voltage follows the gate voltage

→ Source follower

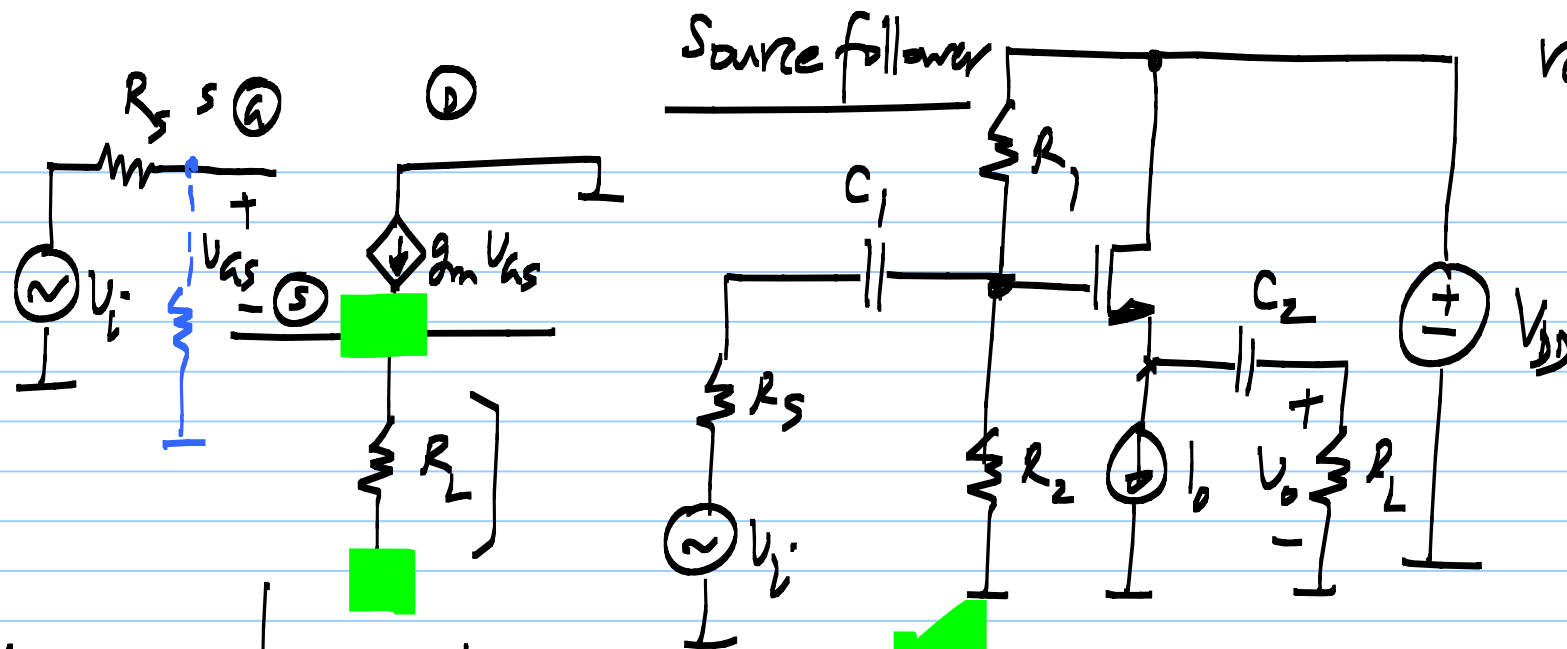Input between gate-drain  
o/p between source-




$$V_{CVS} \quad \frac{V_o}{V_i} = 1$$

$$g_m R_L \gg 1$$


$\omega_{min} > 0$

$$CS \quad \frac{V_o}{V_i} = -g_m R_L = -1 \quad g_m R_L \gg 1$$
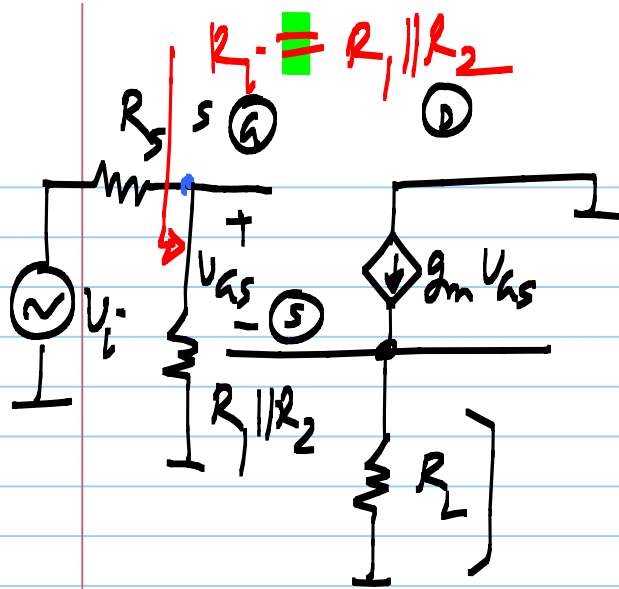
$$G \quad \frac{V_o}{V_i} = \frac{g_m R_L}{1 + g_m R_L} \approx 1 \quad g_m R_L \gg 1$$




$$C_1, C_2 \rightarrow \infty$$

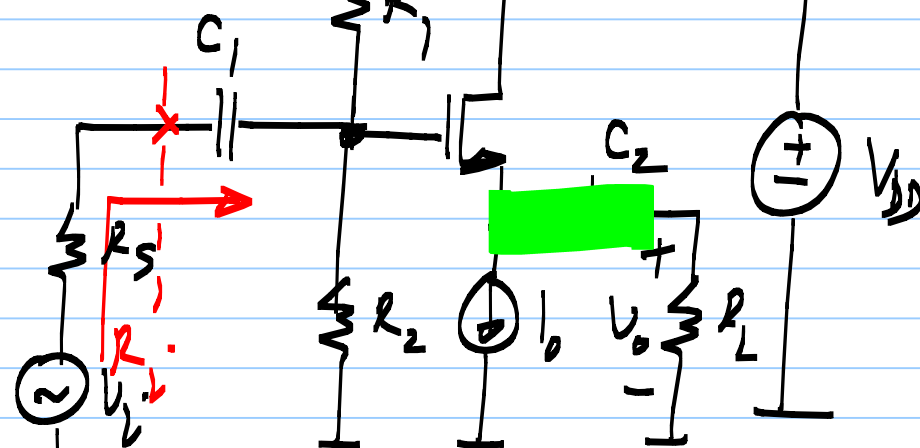


$$V_g = v_i \left[ \frac{R_1 \parallel R_2}{R_s + (R_1 \parallel R_2)} \right] \approx v_i \quad R_1, R_2 \gg R_s$$

Source follower

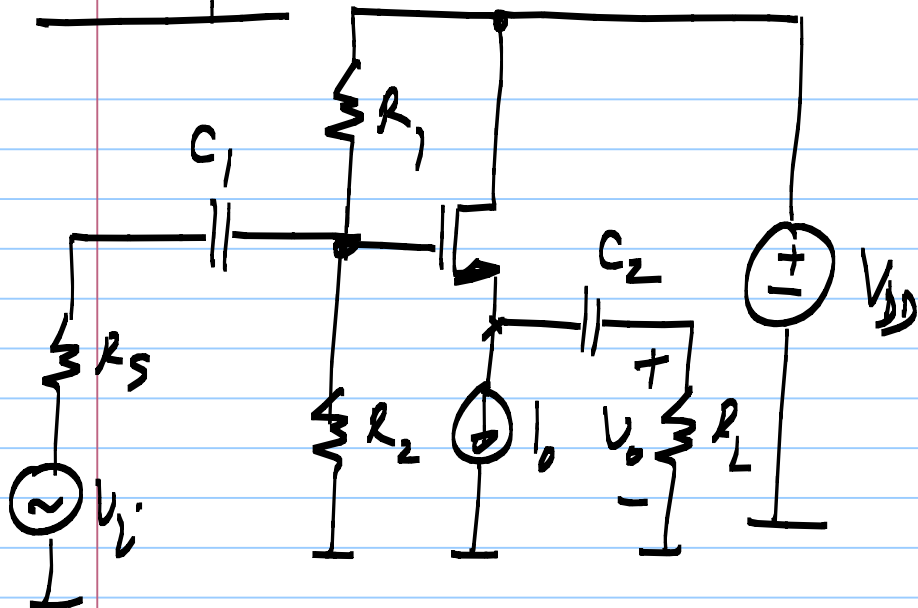

\* Effect of  $\lambda$

\* Find constraints on  $C_1$  &  $C_2$

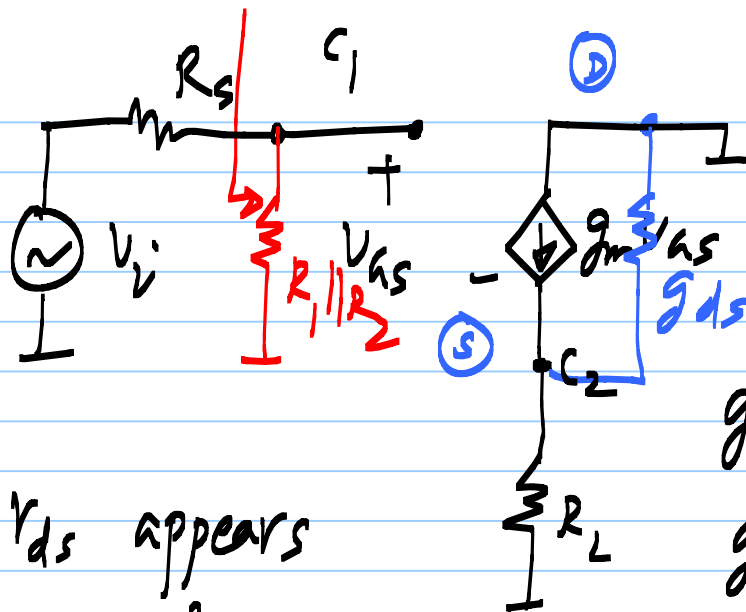

$r_{ds}$  appears  
across  $R_L$


$$R_L \longrightarrow R_L \parallel r_{ds}$$


$$\frac{v_o}{v_i} = \frac{g_m R_L}{1 + g_m R_L} \Rightarrow \frac{g_m (R_L \parallel r_{ds})}{1 + g_m (R_L \parallel r_{ds})}$$

$$g_m \cdot R_L \parallel r_{ds} \gg 1$$

$$g_m \gg g_L + g_{ds}$$



$$= \frac{g_m}{g_m + g_L + g_{ds}}$$

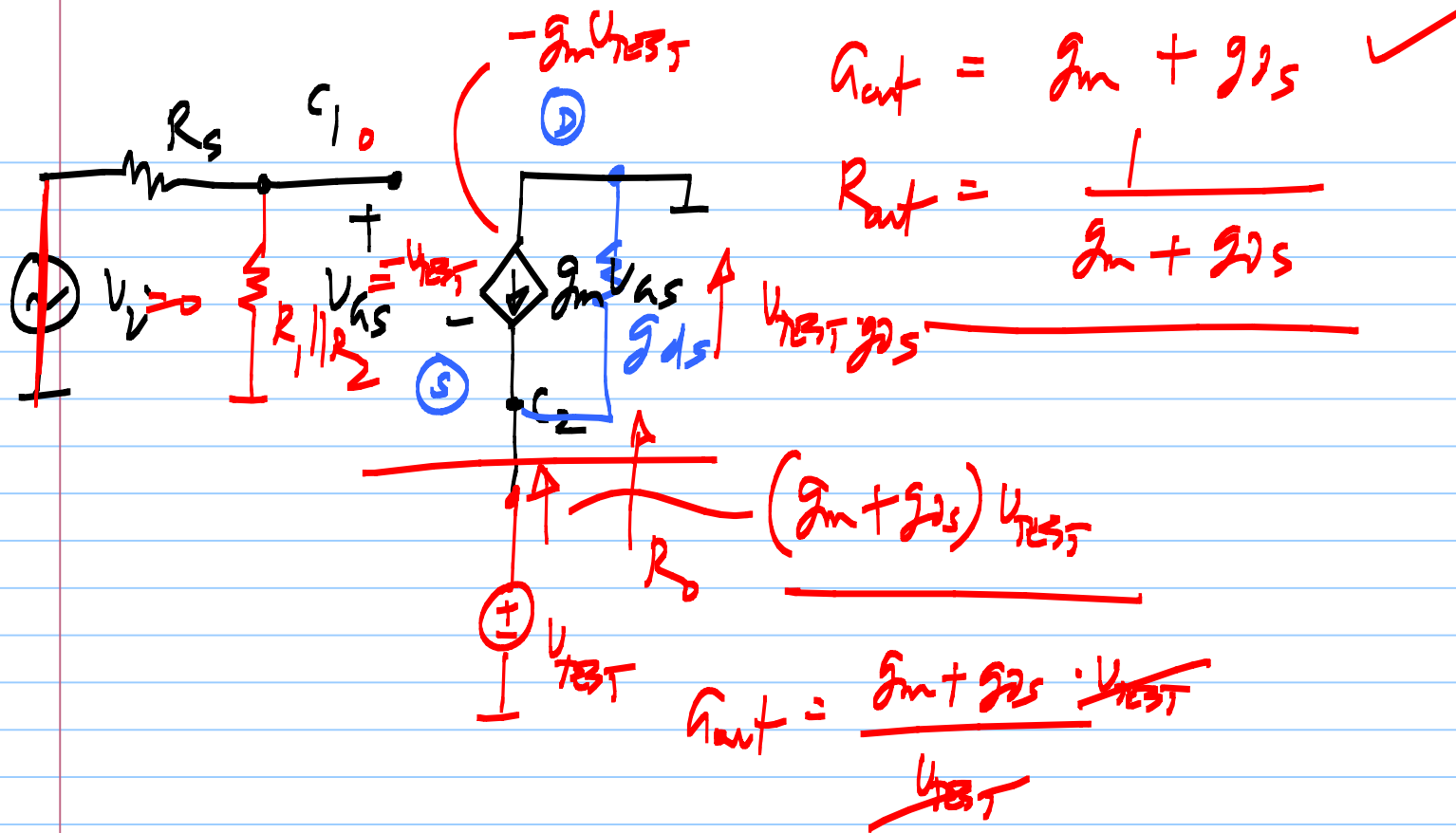

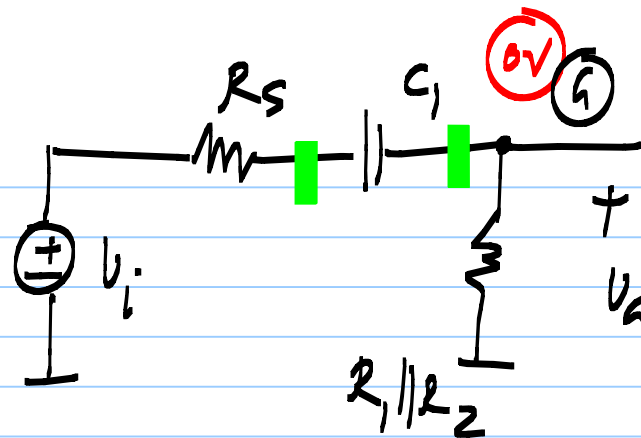

Resistance across  $C_1$ :
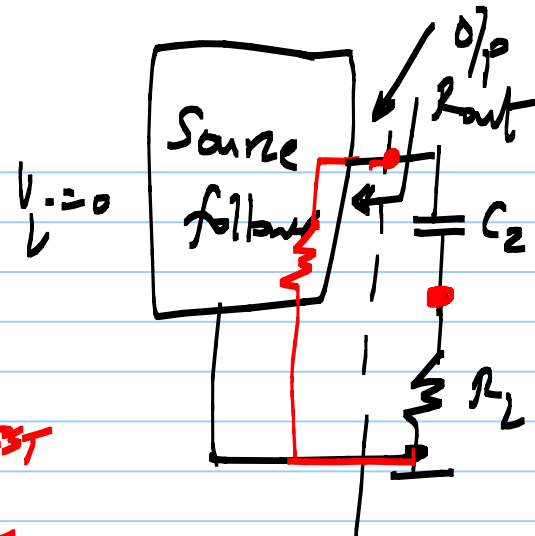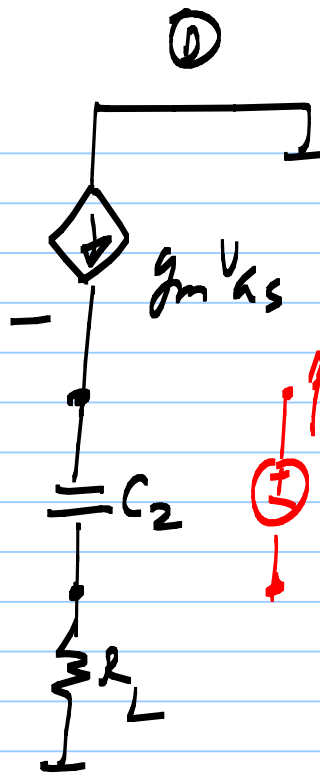
$$C_1 \gg \frac{1}{\omega (R_s + R_1 \parallel R_2)}$$



$$\text{Resistance across } C_2 = R_L + R_{out} \rightarrow \frac{1}{g_m} ; \frac{1}{g_m + g_{gs}}$$

$$C_2 \gg \frac{1}{\omega \left( R_L + \frac{1}{g_m} \right)} \approx \frac{1}{\omega R_L}$$

---


$$g_m R_L \gg 1 \quad R_L \gg \frac{1}{g_m}$$

$$\frac{v_o}{v_i} = \frac{g_m R_L}{1 + g_m R_L} \rightarrow \frac{g_m (R_L \parallel r_{ds})}{1 + g_m (R_L \parallel r_{ds})}$$

( $g_m R_L \gg 1$ )

$$R_i = R_1 \parallel R_2$$

$$R_{out} = \frac{1}{g_m} \rightarrow \frac{1}{g_m + g_{ds}}$$

$$C_1 \gg \frac{1}{\omega (R_S + R_1 \parallel R_2)}$$

$$C_2 \gg \frac{1}{\omega (R_L + 1/g_m)}$$