
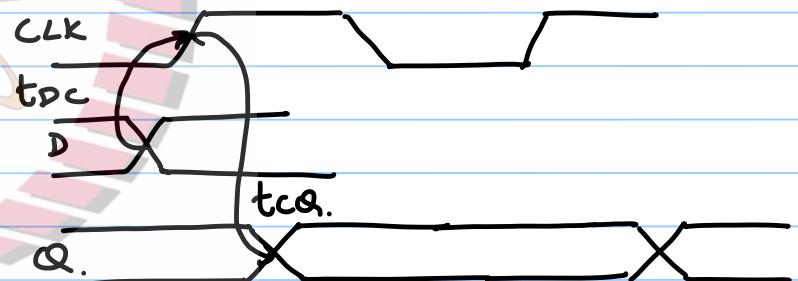
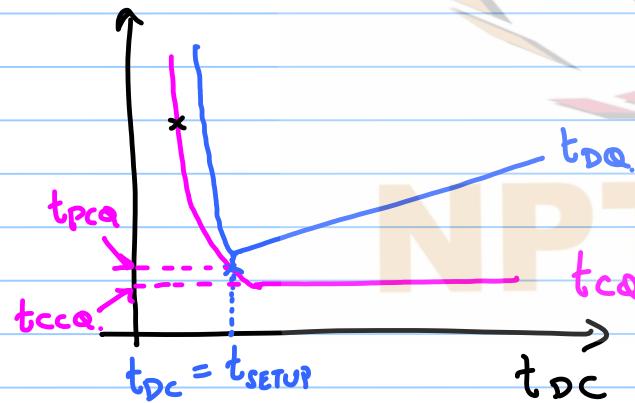



07/11/2019

EE5311


MODULE - 5 - SEQUENTIAL CIRCUITS

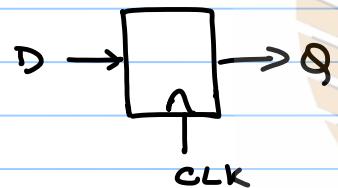

$$t_{DQ} = t_{DC} + t_{CQA}$$

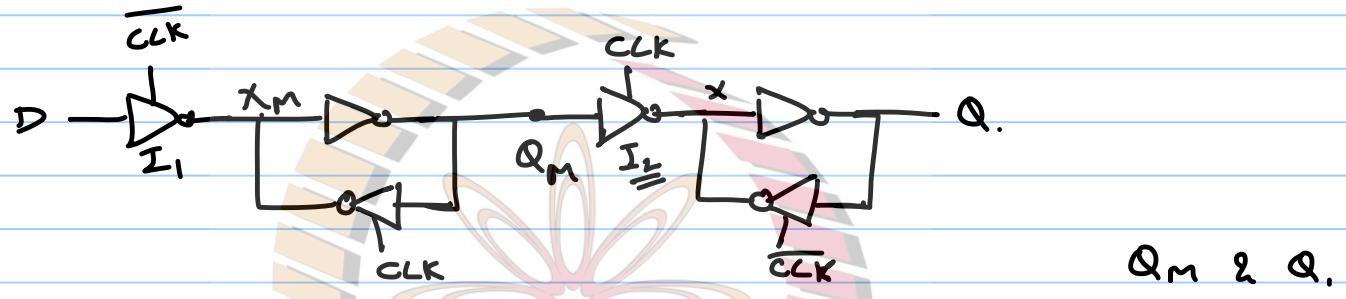



$Q_M \neq Q$ .

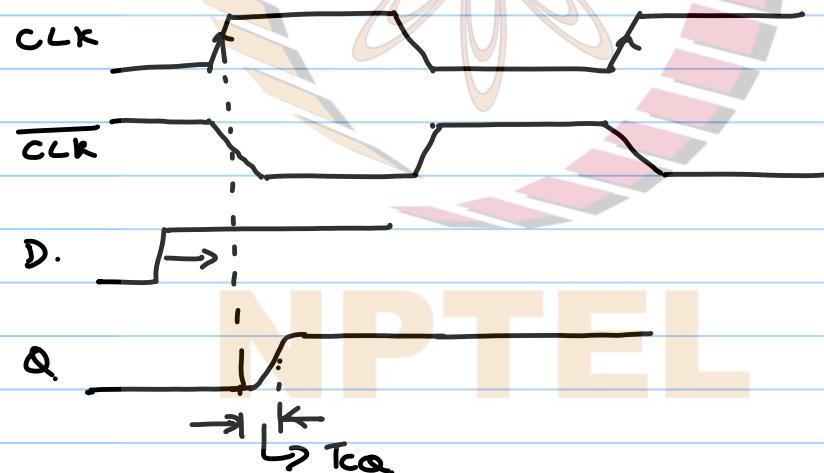


COMB BLOCKS  $\rightarrow$   $t_{CD}$ ,  $t_{PD}$ .


SEQ ELEMENTS  $\rightarrow$   $t_{CCA}$ ,  $t_{PCQ}$ ,  $t_{SETUP}$ ,  $t_{HOLD}$ .

SYSTEM DELAY CONSTRAINTS

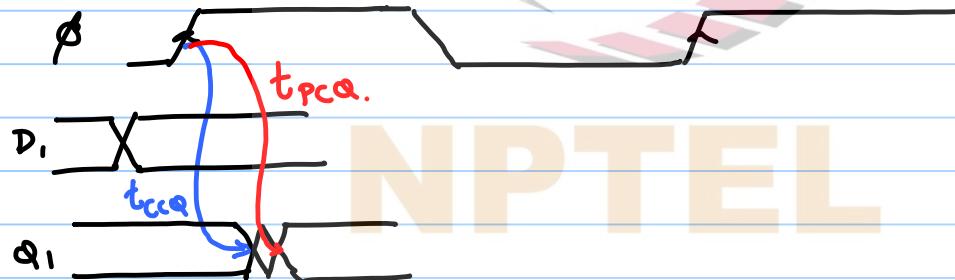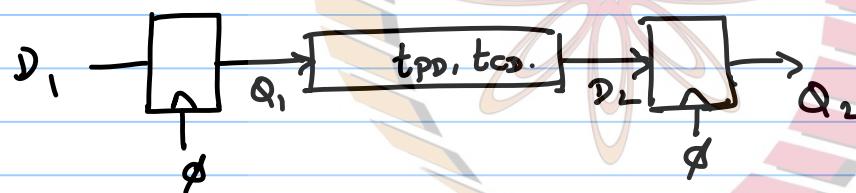

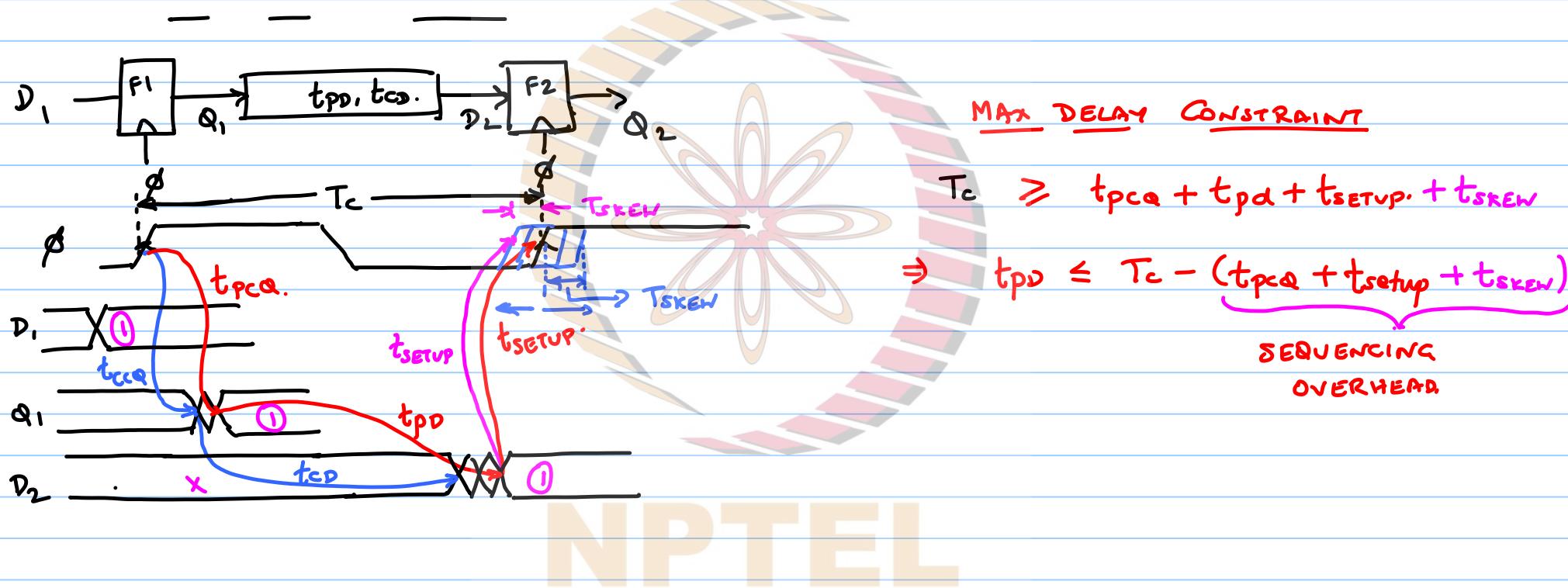

# NPTEL

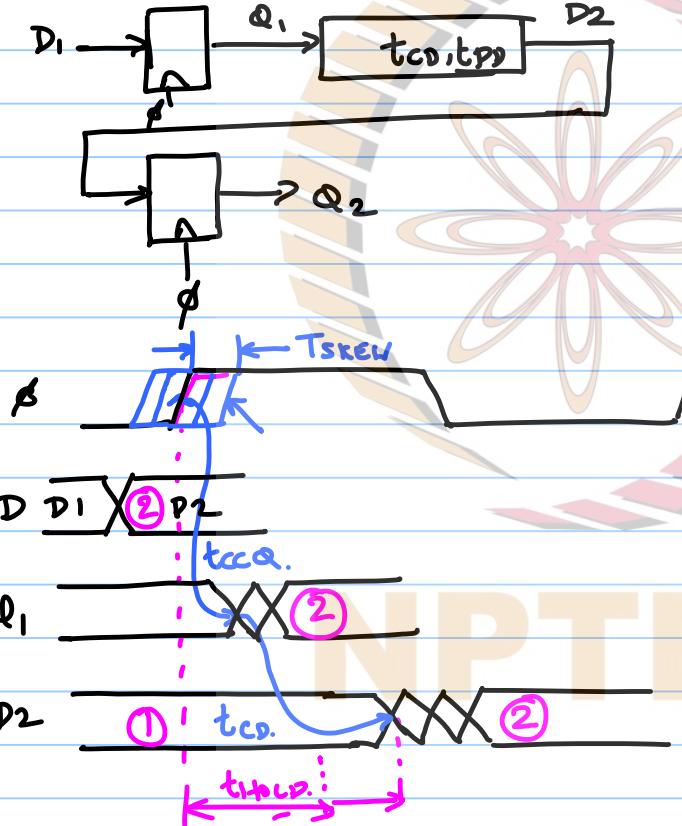

MIN DELAY CONSTRAINT

$$t_{SKEW} + t_{HOLD} \leq t_{CQ} + t_{CD} \quad \text{--- (1)}$$

$$\Rightarrow t_{CD} \geq t_{HOLD} - t_{CQ} - t_{SKEW} \quad \text{--- (2)}$$