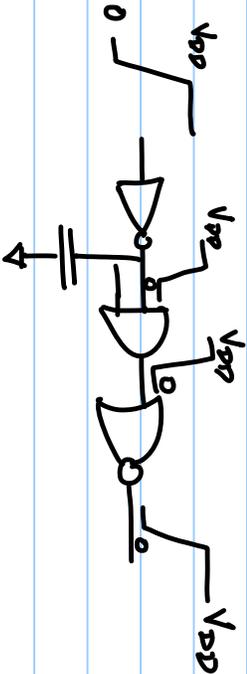


26/08/2019

EES311

MODULE - 3 - THE INVERTER




CHARGING / DISCHARGING A CAPACITANCE

NMOS	CH
PMOS	DIS


NMOS : DRAIN \rightarrow SOURCE CURRENT FLOW
 (IDEAL \Rightarrow NO LEAKAGE)

DISCHARGING

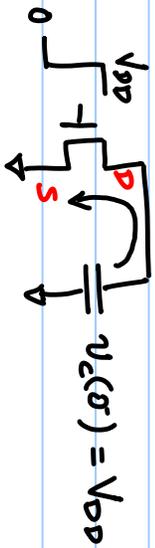

$$V_{GS}(t) = V_{DD} > V_T \quad \forall t$$

CHARGING:

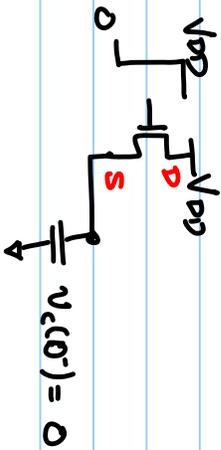


$$V_{GS}(t) = V_{DD} - V_C(t) > V_T$$

$$V_C(t) < V_{DD} - V_T \quad (\text{MAX VALUE THAT})$$

AN NMOS CAN P.A.S)

* VERY SLOW CHARGING

PMOS : S → D CURRENT FLOW

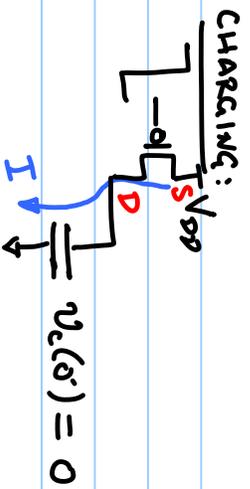

$$V_{GS}(t) = -V_{DD} < V_{TP}$$

CAP CAN CHARGE TO V_{DD}

DISCHARGING:




$$V_{GS}(t) = -V_c(t) < V_{TP}$$

OR $V_c(t) > |V_{TP}|$

⇒ PMOS CAN PASS ONLY UNTIL $|V_{TP}|$

NMOS : DISCHARGING

PMOS : CHARGING

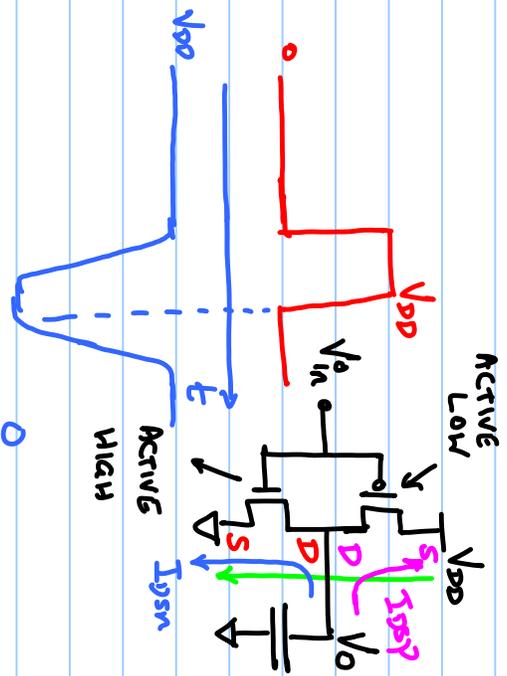

CMOS GATE (INVERTER)

	V_{GS}	V_{DS}
NMOS	V_{in}	V_o
PMOS	$V_{in}-V_{DD}$	V_o-V_{DD}

$$\boxed{I_{Dsn} = -I_{Dsp}} \quad \forall t$$

If $V_{in} = 0 \Rightarrow V_{GSn} = 0 (< V_{tn})$

$\Rightarrow I_{Dsn} = 0 \Rightarrow I_{Dsp} = 0$



$\Rightarrow V_{osp} = 0 \Rightarrow V_o - V_{DD} = 0$

$\therefore V_o = V_{DD}$

If $V_{in} = V_{DD} \Rightarrow V_{asp} = V_{in} - V_{DD} = 0 (> V_{Tp})$
 $\Rightarrow I_{Dsp} = 0 \Rightarrow I_{Dsn} = 0$

$\therefore V_{Dsn} = 0 \Rightarrow V_o = 0$

VOLTAGE TRANSFER CHAR (VTC)

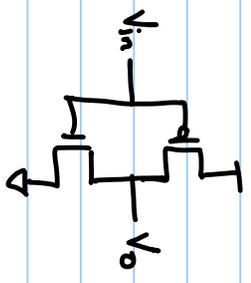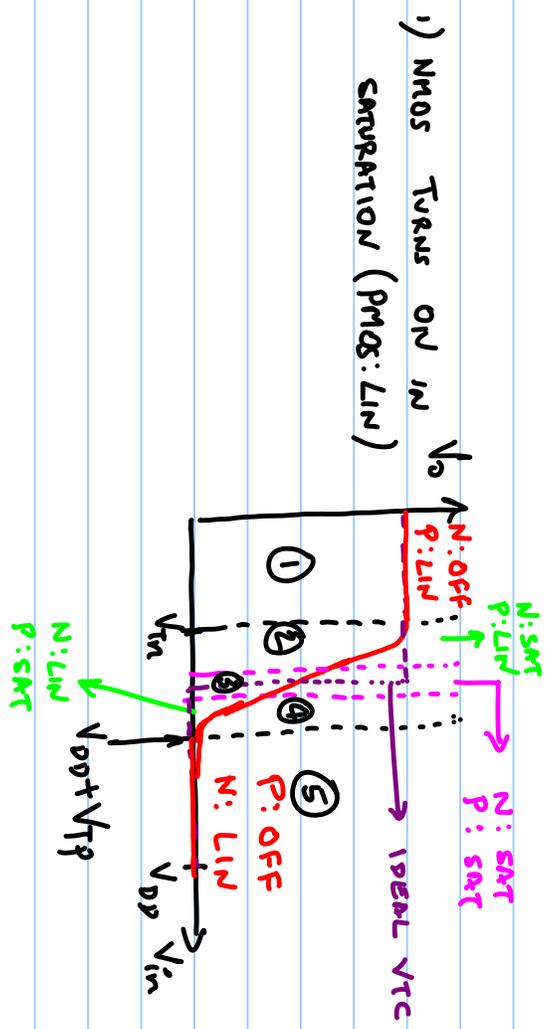

$V_{asn} = V_{in}$ $V_{asp} = V_{in} - V_{DD}$
 $V_{dsn} = V_o$ $V_{dsp} = V_o - V_{DD}$
 $I_{Dsn} = -I_{Dsp}$

$V_{asp} < V_{Tp}$
 $\Rightarrow V_{in} - V_{DD} < V_{Tp}$
 $\Rightarrow V_{in} < V_{DD} + V_{Tp}$