


20/09/2019

EE5811


# MODULE 4- COMBINATIONAL CIRCUITS

$$Y = f(A, B, C, \dots) \\ = \sum m(0, 1, 2, \dots)$$

①  $\bar{Y} = \bar{f}(A, B, C, \dots)$

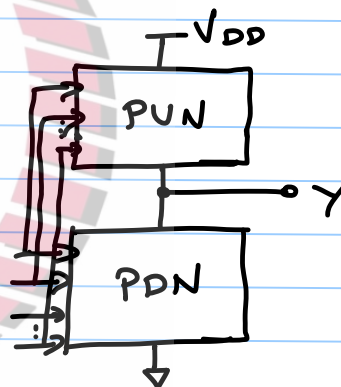


NAND2:

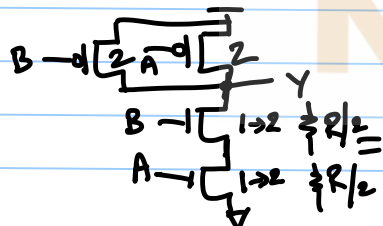

$$Y = \overline{AB}$$


$$\text{---} \square \text{---} \Rightarrow \frac{1}{3}R$$

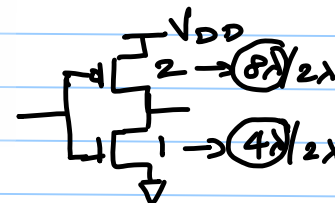

NAND3:


$$Y = \overline{ABC}$$

$$\overline{Y} = ABC$$

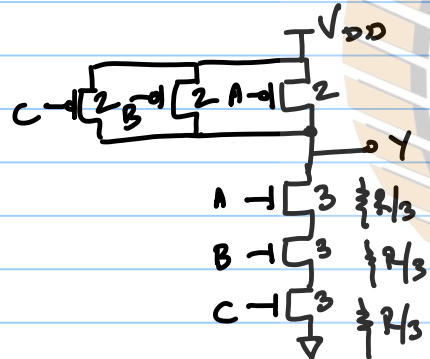

NOR2


$$Y = \overline{A+B}$$

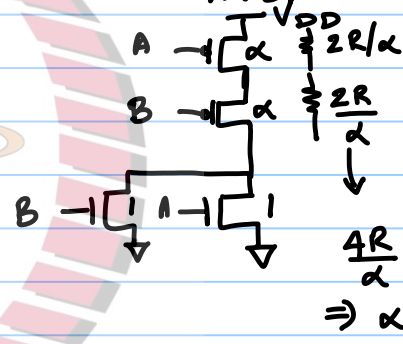

$$\frac{4R}{\alpha} = R \Rightarrow \alpha = 4$$


$$R_N = \frac{3V_{DD}}{4I_{SAT-N}}$$

$$R_P = \frac{3V_{DD}}{4I_{SAT-P}}$$

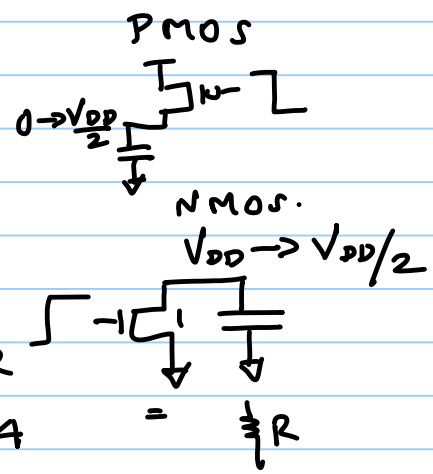

NPTEL

$$Y = \overline{(A+BC)D}$$

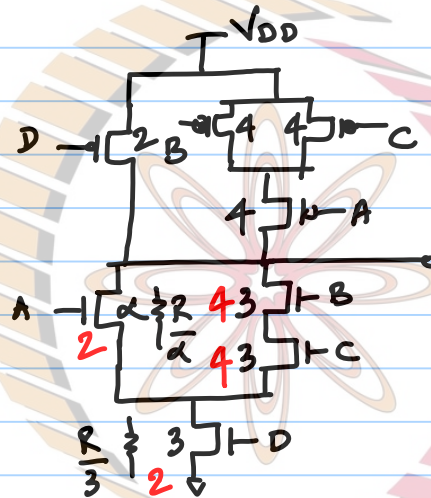


$$\sum W_p = 12$$

$$\sum W_n = 10.5$$

$$\frac{R}{\alpha} + \frac{R}{3} = R$$

$$\therefore (\alpha = 3/2)$$

## CAPACITANCE

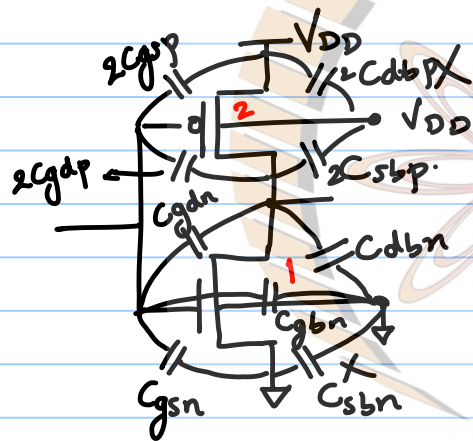




ALL CAPS SCALE AS  $\propto W$



$$C_{gsn} = C_{gsp}$$

ASSUMPTIONS :

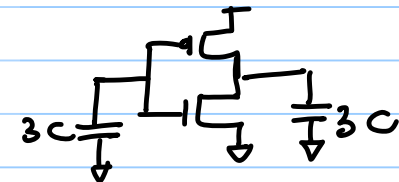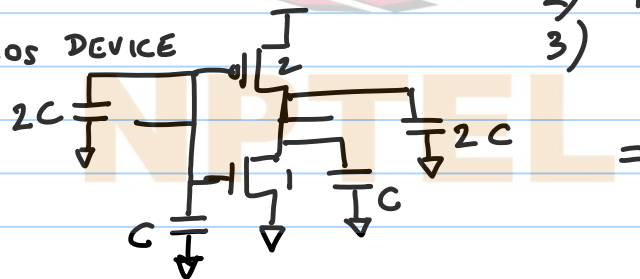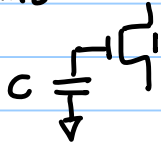- 1) LUMP ALL CAPS.
- 2) ALL CAPS TO AC GND
- 3) ALL CAPS ARE EQUAL





$C \rightarrow$  GATE CAP OF A UNIT NMOS DEVICE




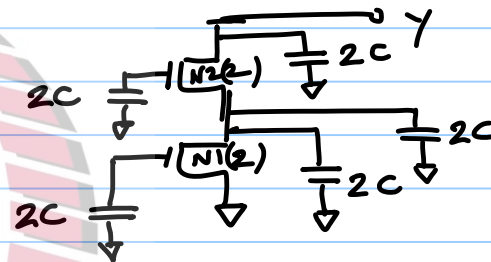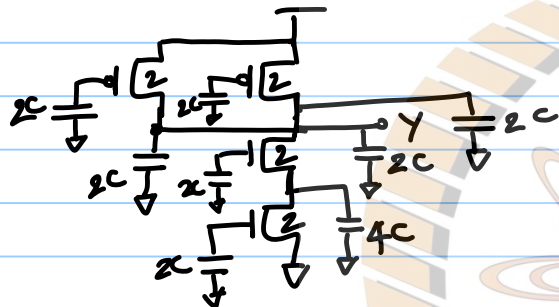

UNCONTACTED  
SHARED  
DIFFUSION

=> DO NOT  
DOUBLE  
COUNT  
CAP

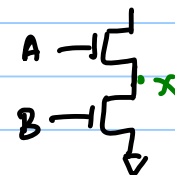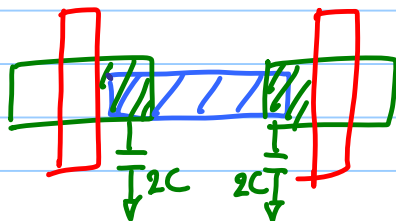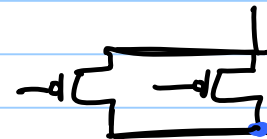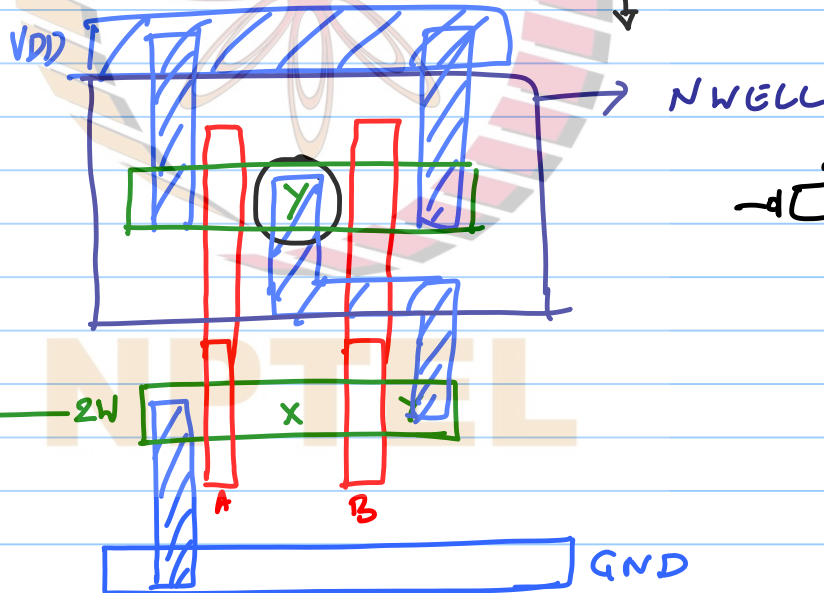

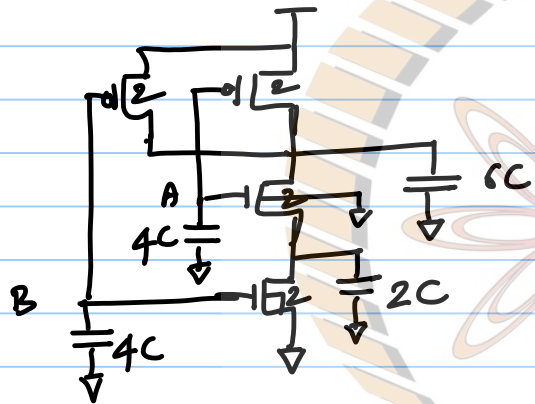

NPTEL