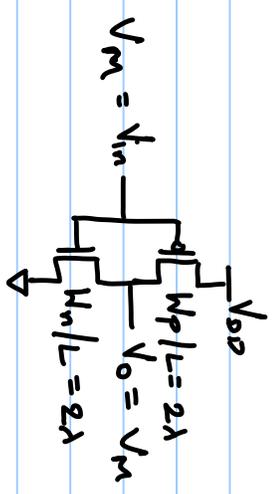


6/07/2019

EE5311  
MODULE-3 - THE INVERTER


LONG CHANNEL



ASSUMPTION:

BOTH N & P ARE IN SATURATION

$V_{GS}$	$V_m$	$V_m$
$V_{DS}$	$V_m$	$V_m - V_{DD}$

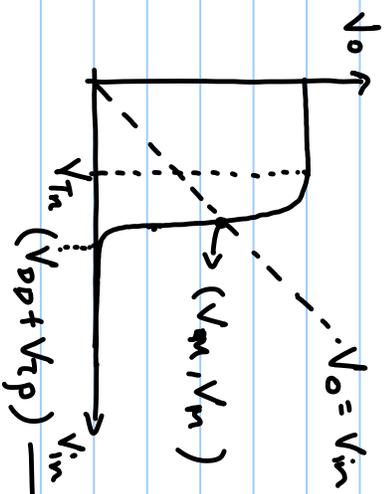

$$I_{Dsn} = \frac{1}{2} k_n' (W_n/L) (V_m - V_{tn})^2$$

$$I_{Dsp} = \frac{1}{2} k_p' (W_p/L) (V_m - V_{DD} - V_{tp})^2$$


$$V_{tn} \leq V_m \leq V_{DD} + V_{tp}$$

$$\Rightarrow V_m - V_{tn} > 0$$

$$(V_m - V_{DD} - V_{tp}) < 0$$




# NOISE MARGIN ANALYSIS

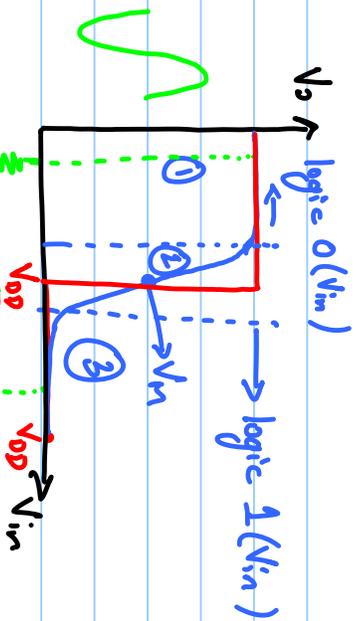


$V_{in} < V_m \Rightarrow V_m$  is logic 0  $\Rightarrow V_o = \text{logic } 1$   
 $V_{in} > V_m \Rightarrow V_m$  is logic 1  $\Rightarrow V_o = 0$

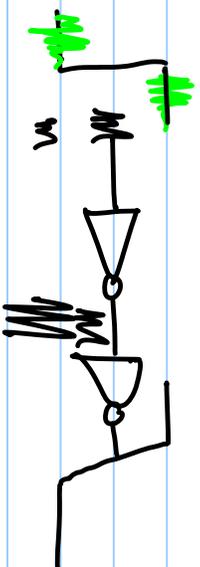$\frac{dV_o}{dV_{in}} = 0$  ( $V_m$ )  
 $\frac{dV_o}{dV_{in}} = 0$  ( $V_m$ )  
 $(g_{ai} = 0)$   $\frac{dV_o}{dV_{in}} = 0$  ( $g_{ai} = 0$ )  
 $(g_{ai} \gg 0)$




$$\frac{dV_o}{dV_{in}} = g_{ai} = -1$$

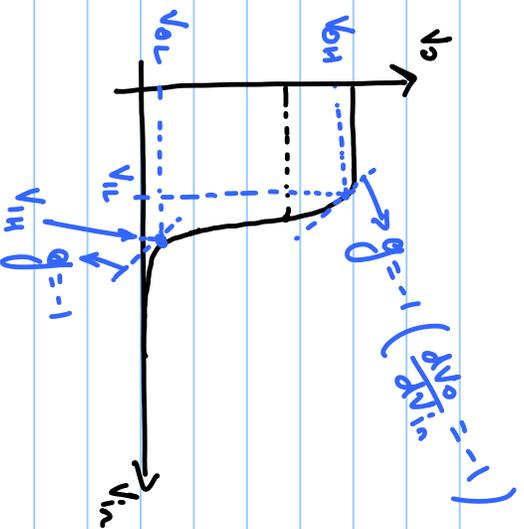

if  $V_{in} > V_{IH} \Rightarrow$  input is logic 1  
 $V_{in} < V_{IL} \Rightarrow$  ~ ~ ~ ~ ~ 0

$V_{IL} \leq V_{in} \leq V_{IH}$  ?  
 $\Rightarrow$   $V_o$  will be

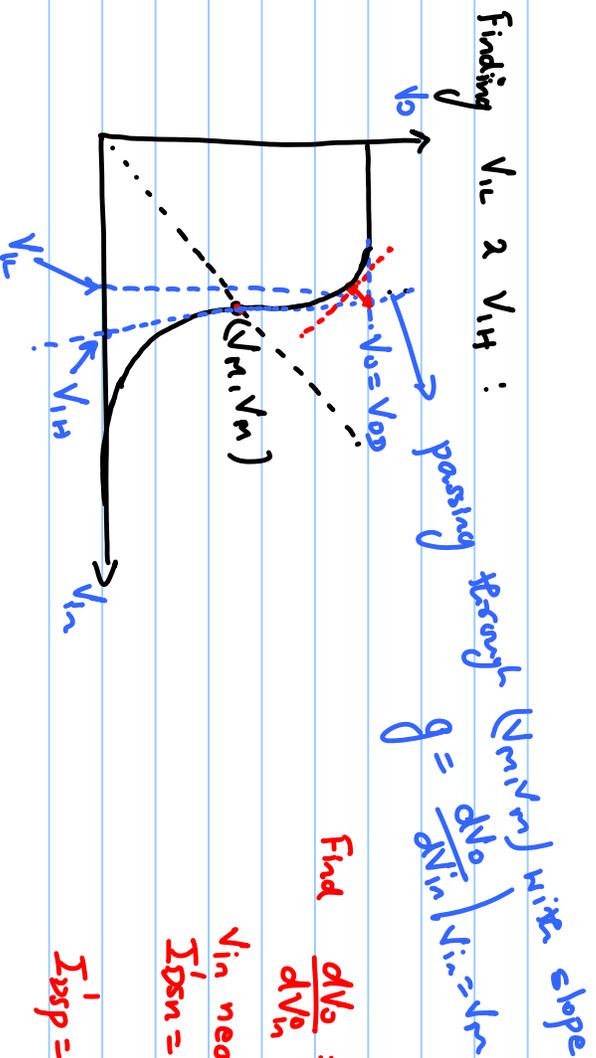Logic 0/1 depending on  
 noise (gain is very high)



Find  $\frac{dV_0}{dV_n} = g$  @  $V_{in} = V_0 = V_n$

$V_{in}$  near  $V_n$   
 $I_{DSN} = k_n \frac{W_n}{L} V_{DSATN} \left[ (V_{in} - V_{tn}) - \frac{V_{DSATN}}{2} \right]$

$I_{DSP} = k_p \frac{W_p}{L} V_{DSATP} \left[ (V_{in} - V_{DD} - V_{tp}) - \frac{V_{DSATP}}{2} \right]$

$\frac{dV_0}{dV_{in}} = g \Big|_{V_{in}=V_0=V_n}$

$g =$

$I_{DSN} = I_{DSN}' (1 + \lambda_n V_0)$


$I_{DSP} = I_{DSP}' (1 + \lambda_p (V_0 - V_{DD}))$

$g = dV_0 / dV_{in} \Big|_{V_{in}=V_0=V_n}$

$$g = -\frac{1}{I_D(V_M)} \frac{k_n V_{DSATn} + k_p V_{DSATp}}{\lambda_n - \lambda_p} \frac{1}{1+r}$$

$$g \approx \frac{1}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$
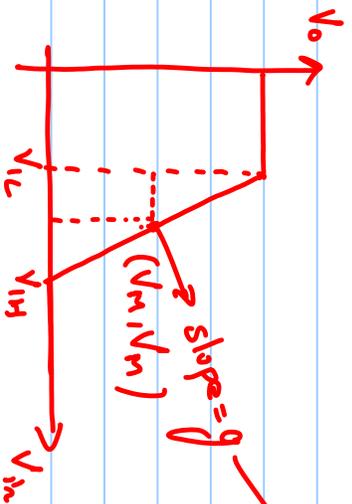
$$r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}}$$



$$g \propto \frac{1}{(\lambda_n - \lambda_p)}$$

$$\lambda_p = -\lambda_n$$

$$g \propto \frac{1}{2\lambda_n}$$

$$g = \frac{-V_M}{V_{IH} - V_M}$$

$$\therefore V_{IH} = V_M - \frac{V_M}{g} > V_M$$

$$g = \frac{V_M - V_{DD}}{V_M - V_{IL}} \Rightarrow V_{IL} = V_M - \frac{(V_M - V_{DD})}{g}$$