


8/9/2019

EES311


Module 4 - Combinational Circuits

$$Y = f(A, B, C, \dots)$$
$$= \sum m(0, 1, 2, \dots)$$

①  $\bar{Y} = \bar{f}(A, B, C, \dots)$

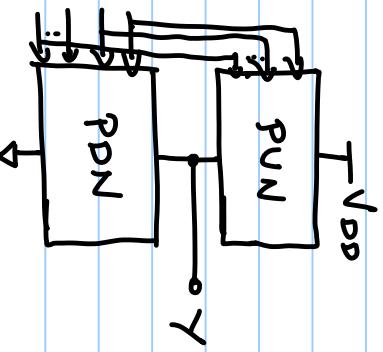


NAND2!

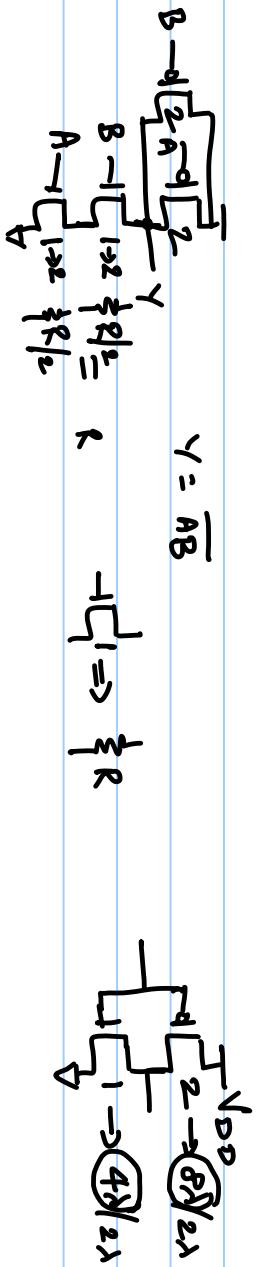

NAND3:

$$Y = \overline{ABC}$$

$$\bar{Y} = ABC$$

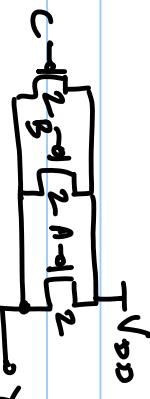

NOR2

$$Y = \overline{A+B}$$

$$A \rightarrow \begin{cases} 1 & \text{if } A \\ 0 & \text{if } \bar{A} \end{cases}$$

$$B \rightarrow \begin{cases} 1 & \text{if } B \\ 0 & \text{if } \bar{B} \end{cases}$$

$$V_{DD} \rightarrow \frac{V_{DD}}{2}$$

$$B - 1 \rightarrow \begin{cases} 1 & \text{if } B \\ 0 & \text{if } \bar{B} \end{cases}$$

$$\Rightarrow \alpha = 4$$

$$= \frac{4R}{\alpha}$$

PMOS


$$N\text{MOS.}$$

$$\overline{A} = \frac{1}{3}R \quad R_N = \frac{3V_{DD}}{4I_{DSAT-N}}$$

$$\overline{A} = \frac{1}{3}R \quad R_P = \frac{3V_{DD}}{4I_{DSAT-P}}$$

$$\alpha = \frac{2R}{\alpha}$$

$$Y = \frac{A + BC}{D}$$

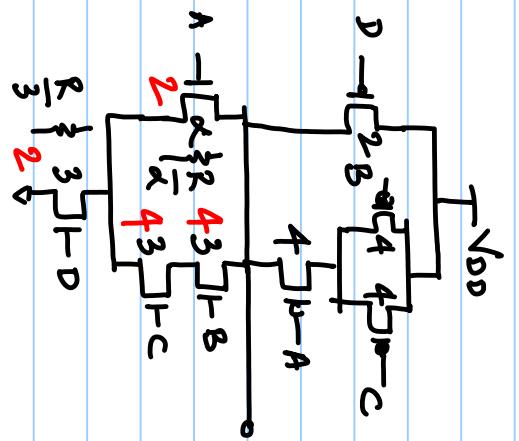


$$\sum M_i = 12$$

$$\sum M_i = 10.5$$

$$\frac{R}{\lambda} + \frac{R}{3} = R$$

$$\therefore (\lambda = 3/2)$$

## CAPACITANCE

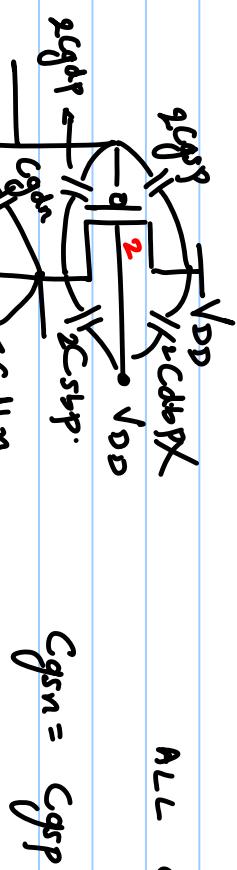

ALL CAPS SCALE AS  $\propto W$

ASSUMPTIONS :

- 1) LUMPS ALL CAPS.
- 2) ALL CAPS TO AC GND
- 3) ALL CAPS ARE EQUAL

$$\begin{aligned}
 & C \xrightarrow{\frac{1}{T}} \left[ \frac{1}{T} \right] \xrightarrow{\frac{1}{T}} \frac{1}{T^2} C = \\
 & 2C \xrightarrow{\frac{1}{T}} \left[ \frac{1}{T} \right] \xrightarrow{\frac{1}{T}} \frac{1}{T^2} 2C = \\
 & C \xrightarrow{\frac{1}{T}} \left[ \frac{1}{T} \right] \xrightarrow{\frac{1}{T}} \frac{1}{T^3} C
 \end{aligned}$$

