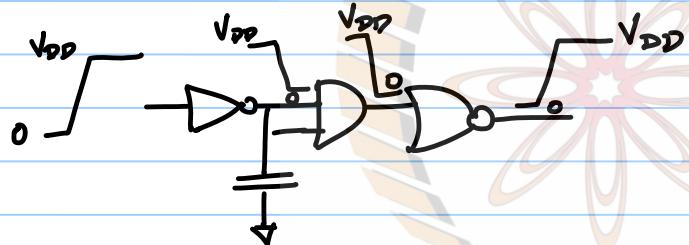


26/08/2019

EES311

MODULE - 3 - THE INVERTER



CHARGING / DISCHARGING A CAPACITANCE


N MOS
P MOS

CH
DIS

NPTEL


NMOS: DRAIN \rightarrow SOURCE CURRENT FLOW
(IDEAL \Rightarrow NO LEAKAGE)

DISCHARGING

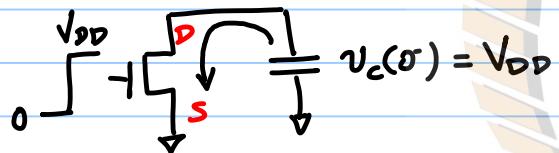

$$v_{GS}(t) = V_{DD} > V_T \quad \forall t$$

CHARGING:

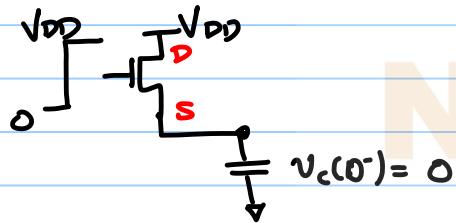


$$v_{GS}(t) = V_{DD} - v_c(t) > V_T$$

$$v_c(t) < V_{DD} - V_T \quad (\text{MAX VALUE THAT AN NMOS CAN PULL})$$

* VERY SLOW CHARGING

PMOS : S \rightarrow D CURRENT FLOW


CHARGING:

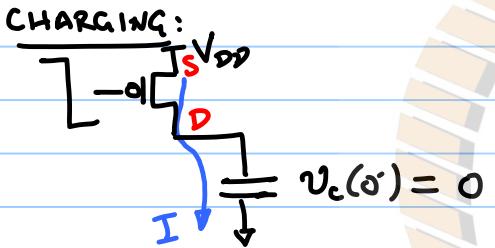

$$V_{GS}(t) = -V_{DD} < V_{TP}$$

CAP CAN CHARGE TO V_{DD}

DISCHARGING:

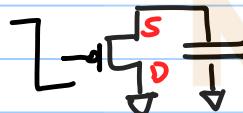


$$V_{GS}(t) = -V_C(t) < V_{TP}$$

$$\text{OR } V_C(t) > |V_{TP}|$$


\Rightarrow PMOS CAN PASS ONLY UNTIL (V_{TP})

NMOS : DISCHARGING

PMOS : CHARGING

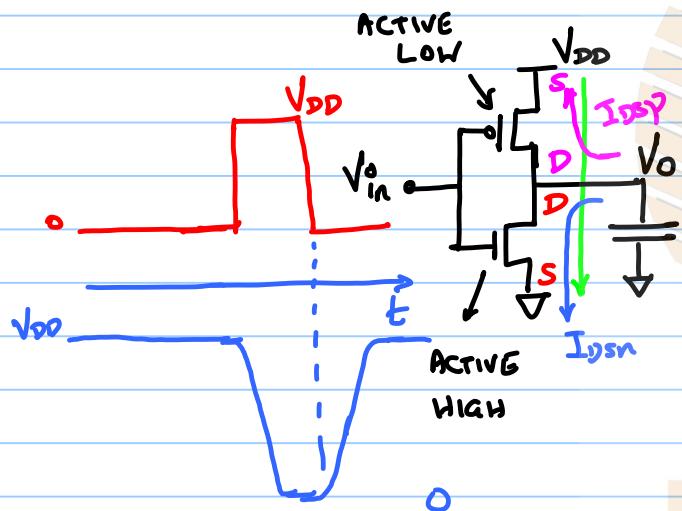

CMOS GATE (INVERTER)

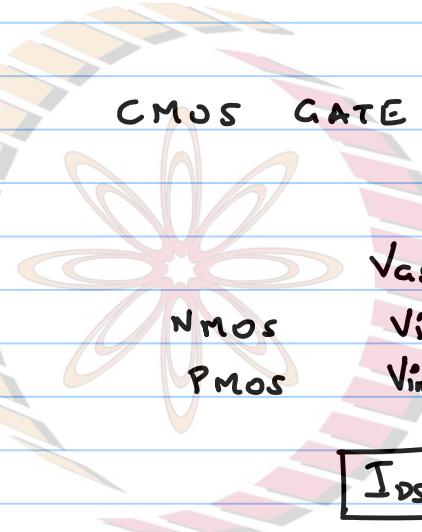

$$\begin{aligned}V_{DS} &= V_o - V_{DD} \\V_{in} &= V_{GS} \\V_{in} - V_{DD} &= V_{GS} - V_{DD}\end{aligned}$$

$$V_{DS}$$

$$V_o$$

$$V_o - V_{DD}$$

$$I_{DSn} = -I_{DSP} \quad \forall t$$


$$\begin{aligned}\text{If } V_{in} = 0 &\Rightarrow V_{GSn} = 0 (< V_{Tn}) \\&\Rightarrow I_{DSn} = 0 \Rightarrow I_{DSP} = 0\end{aligned}$$

$$\begin{aligned}\Rightarrow V_{DSP} &= 0 \Rightarrow V_o - V_{DD} = 0 \\&\therefore V_o = V_{DD}\end{aligned}$$

$$\text{If } V_{in} = V_{DD} \Rightarrow V_{GSp} = V_{in} - V_{DD} = 0 (> V_{Tp}) \\ \Rightarrow I_{Dsp} = 0 \Rightarrow I_{Dsn} = 0$$

$$\therefore V_{Dsn} = 0 \Rightarrow V_o = 0$$

VOLTAGE TRANSFER CHAR (VTC)

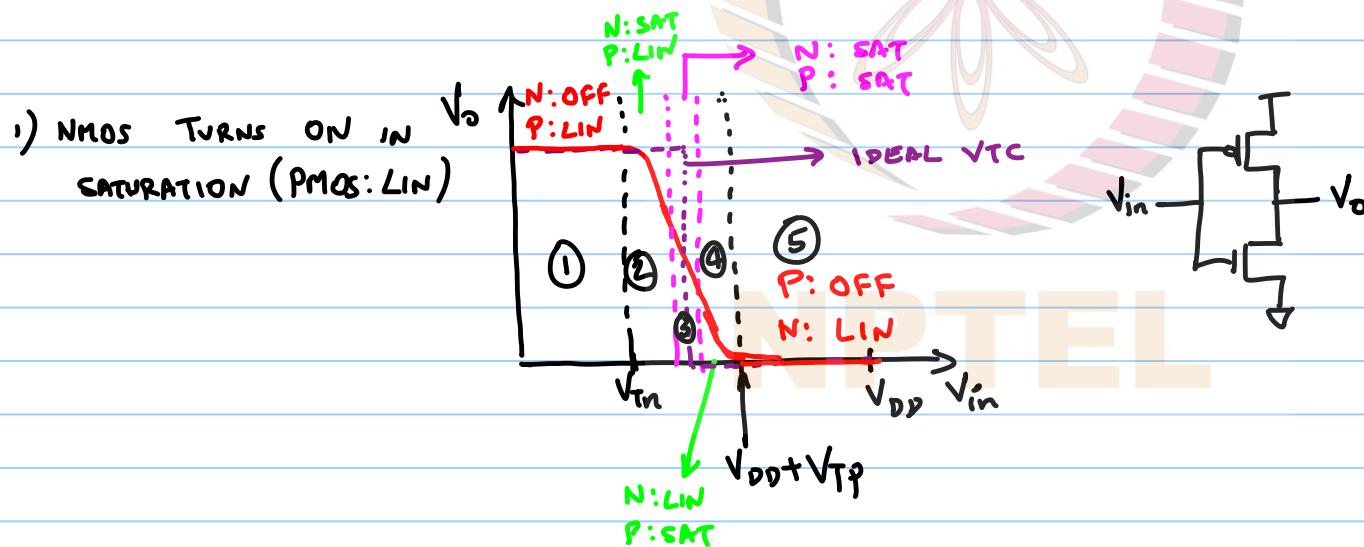

$$V_{GSp} = V_{in} - V_{DD} \quad V_{Dsp} = V_o - V_{DD}$$

$$V_{Dsn} = V_o \quad V_{asp} = V_o - V_{DD}$$

$$I_{Dsn} = -I_{Dsp}$$

$$V_{asp} < V_{Tp} \\ \Rightarrow V_{in} - V_{DD} < V_{Tp} \\ \Rightarrow V_{in} < V_{DD} + V_{Tp}$$