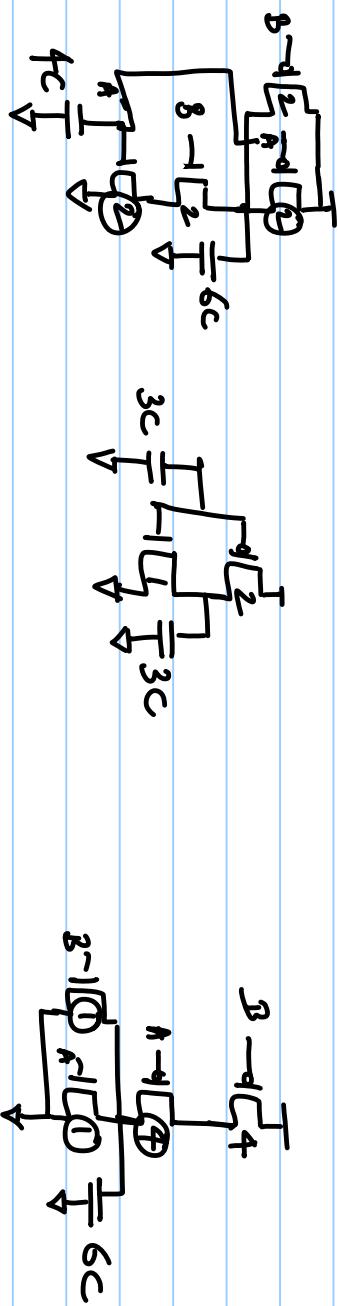


27/09/2019

EES311

Module-4 - Comb Circuits



$$J = \frac{4}{3} \quad (\text{LOGICAL EFFORT})$$


$$P = \frac{6c}{3c} = 2 \quad (\text{PARASTIC EFFORT})$$

$$C_A = C_B = 5c$$

$$g_A = g_B = 5c/3c = 5/3$$

$$P = 6c/3c = 2$$

N input NAND & NOR.

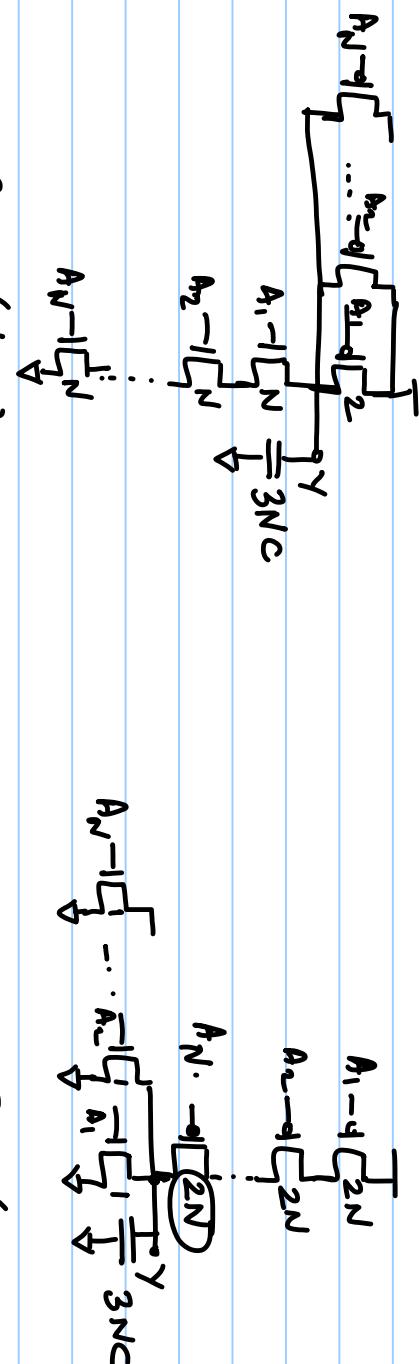

$$C_{Ak} = (N+2)c$$

$$C_{Ak} = (2N+1)c$$


$$\therefore g_{Ak} = \frac{(N+2)c}{3c} = \left(\frac{N+2}{3}\right)$$

$$g_{Ak} = \frac{(2N+1)c}{3c} = \frac{(2N+1)}{3}$$

$$p = \frac{3Nc}{3c} = N$$

$$p = \frac{3Nc}{3c} = N$$

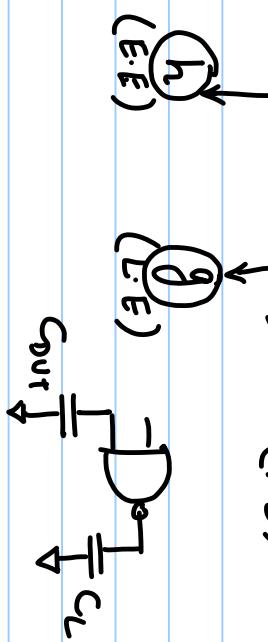
$$\text{delay}_j = \left(\frac{C_L}{C_{\text{out}}} \right) \cdot \left(\frac{C_{\text{unit}}}{C_{\text{inv}}} \right) + p_j$$



$$\hat{d} = gh + p_j \quad (\text{NORM. DELAY})$$

$$T = 3RC$$


$$d = \hat{d} \cdot T$$

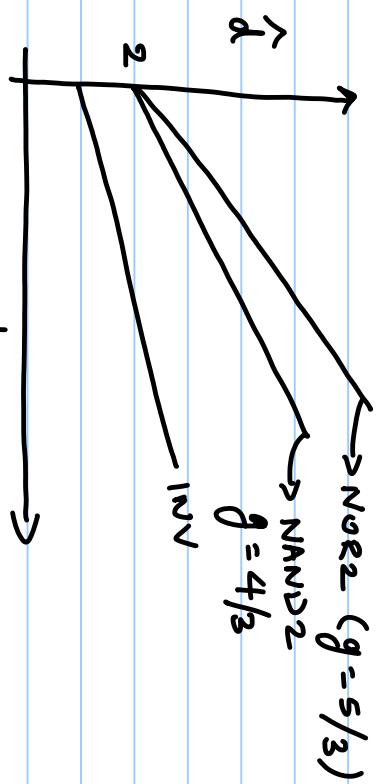

$$g = 4/3$$

$$h = 12kc / 3kc = 4 \quad \frac{C_{in}}{3ck} \xrightarrow{\text{INV}} \frac{1}{3} C_L = 12ck \quad h = C_L / C_{in} = 12c / 3c = 4$$
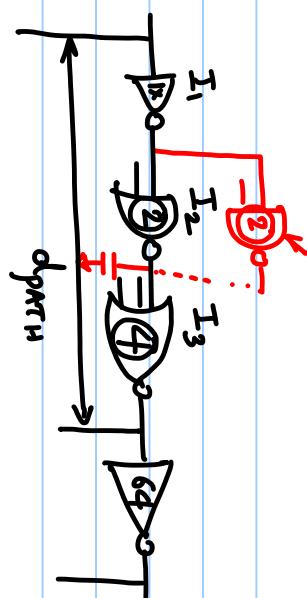
$$F_04 \text{ DELAY} = (gh+p)\tau = (1 \times 4 + 1)\tau = 5\tau$$




$$d_{pmt4} = \sum d_i$$

	I_1	I_2	I_3
C_{in}	$3C$	$8C$	$28C$
C_L	$(8C+8C)$	$28C$	$192C$
h	$(8/3)$	$(7/2)$	$(48/7)$

$(gh+p)$	d	$(11/3)$	$(20/3)$	19
g	1	$4/3$	$7/3$	

Path Delay Optimization

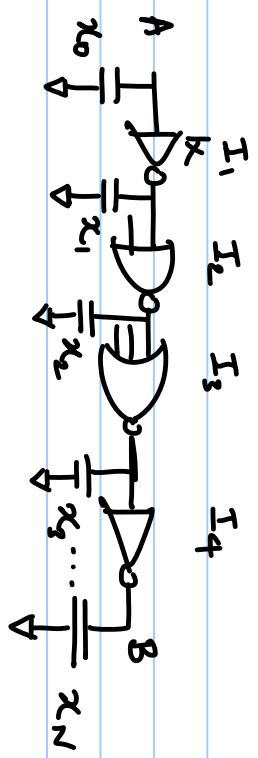

MINIMIZE DELAY ψ_W A 2 B.

Let $x_k \rightarrow$ Input cap of gate ($k+1$)

$$d_i = g_i h_i + p_i$$

$$h_i = x_i / x_0$$

$$h_k = (x_k / x_{k-1})$$

$$d = \sum g_{khk} + p_k.$$

$$= \sum g_{khk} + \underbrace{\sum p_k}_{\text{constant number}}.$$

$$\min \left(\sum_{k=1}^N g_k \left(\frac{x_k}{x_{k-1}} \right) \right)$$

$$F = \prod_{k=1}^N g_k h_k. = \underbrace{\prod_{k=1}^N g_k}_{G} \cdot \underbrace{\prod_{k=1}^N h_k}_{H} \rightarrow \frac{x_1}{x_0} \cdot \frac{x_2}{x_1} \cdot \frac{x_3}{x_2} \cdots \frac{x_N}{x_{N-1}}$$

$$= \frac{x_N}{x_0}$$

Let $f_k = g_{khk}$. $\min \sum f_k$. $\prod f_k = \text{const}$

$$\frac{\sum_{f_k}}{N} \geq (\pi_{f_k})^{y_n}$$

$$A.M \geq C.M$$