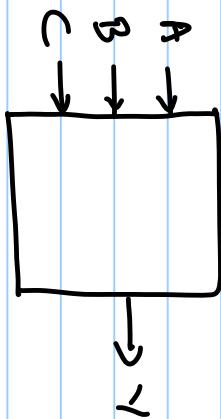


19/09/2019

EE5311

MODULE-4 : COMBINATIONAL CIRCUITS

IMPLEMENTING ANY BOOLEAN FUNCTION



A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1

$Y = \text{SUM OF PRODUCTS}$

.

$$= \sum m(0, 3, 7) = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + ABC$$

1 1 1

0

$$Y = m_0 + m_1 + m_2 \quad (\text{SOP})$$

$$\bar{A}\bar{B}\bar{C} + \bar{A}BC + ABC$$

↑
OR SUM

Product (AND)

$$x \begin{array}{c} A \\ \diagdown \\ \diagup \\ B \end{array} \rightarrow Y = Y = (A \cdot B)x$$

$$Y = (AB)x$$

$$x \begin{array}{c} A \\ \diagdown \\ \diagup \\ B \end{array} \rightarrow Y = Y = (A \cdot B)x$$

NMOS TRANSISTORS \rightarrow Pull Down Logic

$$Y = ABC + \bar{A}\bar{B}\bar{C}$$


WHEN $A=1, B=1, C=1 \Rightarrow ABC = 1 \Rightarrow Y = 1$
 $\bar{A} = \bar{B} = \bar{C} = 1 \Rightarrow \bar{A}\bar{B}\bar{C} = 1 \Rightarrow Y = 1$
 \Rightarrow (USE NMOS)

$$Y = f(A, B, C)$$

STEP 1: INVERT Y
 $\Rightarrow \bar{Y} = \bar{f}(A, B, C)$

$$Y = \overline{AB+CD}.$$

$$\Rightarrow \bar{Y} = AB+CD$$

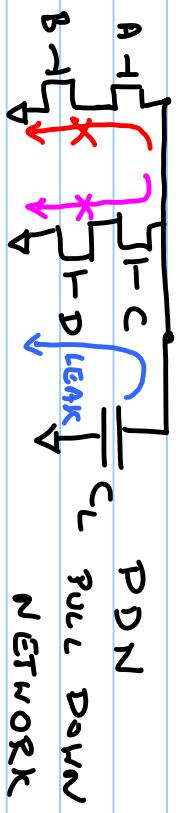

$$\left. \begin{array}{l} A=1, B=1, Y=0 \\ C=1, D=1, Y=0 \end{array} \right\}$$

SIMILAR CONDITIONS

$$A=B=C=D=1, Y=0$$

OR THE CONDITIONS \longrightarrow O/P IS "FLOATING" OR HIGH STATE (z)

$$\bar{Y} = AB + CD$$


$$Y = \bar{\bar{Y}} = \overline{AB+CD} = \overline{\left(\frac{1}{A}+\frac{1}{B}\right)\left(\frac{1}{C}+\frac{1}{D}\right)}$$

PUN - PULL UP N/L


$$A \rightarrow \begin{cases} 1 & X \\ 0 & \end{cases} \quad Y = \bar{A}X$$



μ_{PUN}

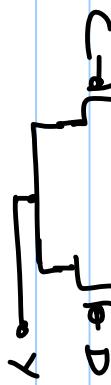


μ_D

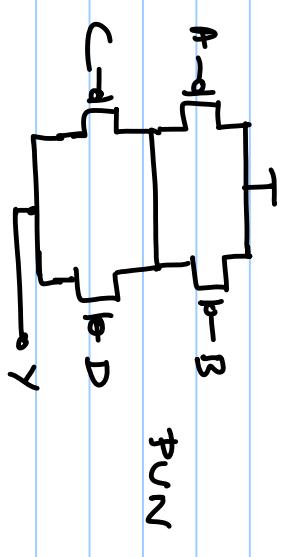

$$Y = AB + CD$$

$$Y = \overline{AB + CD}$$


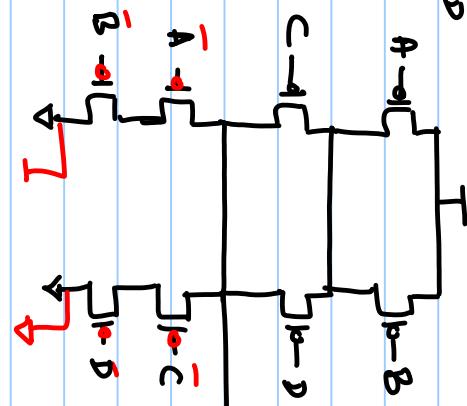


$$Y = \bar{A} \cdot \bar{B} + \bar{C} \cdot \bar{D}$$

$$Y = \overline{A + BC}$$

- ① INVERT $Y \Rightarrow \overline{Y} = A + BC$
 ② IMPLEMENT PDN


$$Y = \overline{A + B(C+D)}$$

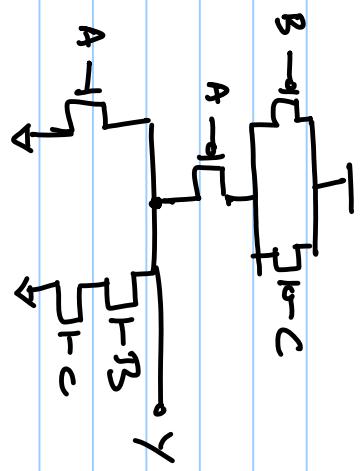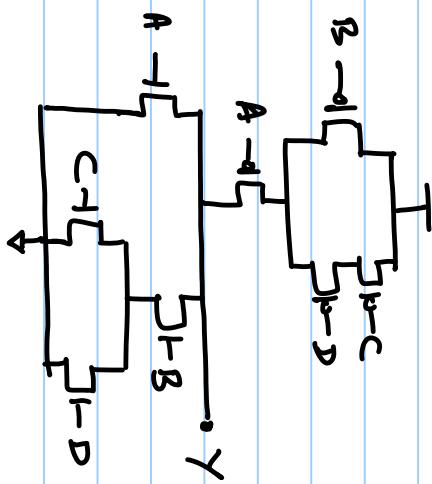

$$Y_{PDN} = \overline{\overline{A} + \overline{BC}}$$

$$Y_{PDN} = \overline{\overline{A}} (\overline{B} + \overline{C})$$

SIRING:

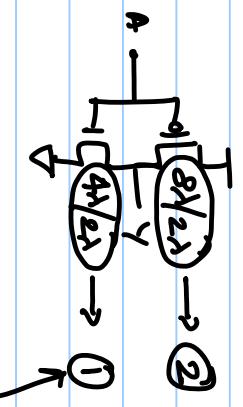

DELAY IS SYM


$$W_p = 2W_n$$

REFERENCE

CMOS


INVERTER

WORST CASE PU/PD
RESISTANCE

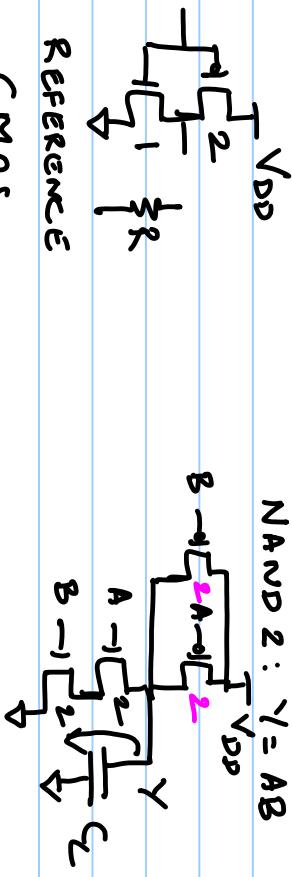

$$R = \frac{3V_{DD}}{4 \cdot I_{DSAT}}$$

PDN RESISTANCE

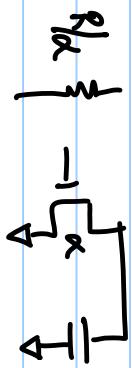

$$R_K = \frac{3V_{DD}}{4 \cdot \alpha \cdot I_{DSAT}} = \frac{R}{\alpha}$$

$$\Rightarrow \frac{2R}{\alpha} = R$$