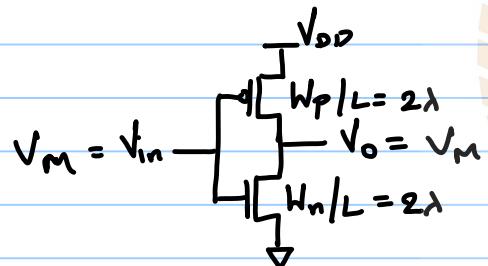


29/08/2019

EES311
MODULE-3 - THE INVERTER

LONG CHANNEL



ASSUMPTION:

BOTH N & P

ARE IN

SATURATION

NMOS

PMOS

V_{GS}


V_M

V_{DS}

V_M

$V_M - V_{DD}$

$V_M - V_{DD} - V_{TP}$

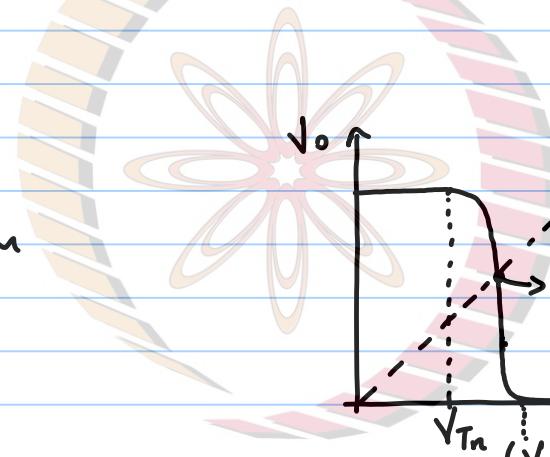

$$\begin{aligned} V_o &= V_m \quad (V_m < V_{in} < V_{Tn}) \\ V_o &= V_{in} \quad (V_{in} > V_m) \end{aligned}$$

$$\begin{aligned} V_{Tn} &\leq V_m \leq V_{DD} + V_{T_P} \\ \Rightarrow V_m - V_{Tn} &\geq 0 \\ (V_m - V_{DD} - V_{T_P}) &< 0 \end{aligned}$$

$$(V_{DD} - |V_{T_P}|) \rightarrow (V_{DD} - V_{T_P})$$

$$I_{DSn} = \frac{1}{2} K_n^i (W_n/L) (V_m - V_{Tn})^2$$

$$I_{DSP} = \frac{1}{2} K_p^i (W_p/L) (V_m - V_{DD} - V_{T_P})^2$$

$$I_{Dn} = -I_{Dp}$$

$$\Rightarrow k_n' W_n (V_m - V_{Tn})^2 = -k_p' W_p (V_m - V_{DD} - V_{Tp})^2$$

$$\gamma = -\frac{k_p' W_p}{k_n' W_n} = \frac{|k_p'| W_p}{k_n' W_n} > 0$$

$$\therefore (V_m - V_{Tn})^2 = \gamma (V_m - V_{DD} - V_{Tp})^2$$

$$(V_m - V_{Tn}) = \pm \sqrt{\gamma} (V_m - V_{DD} - V_{Tp})$$

↓ ↓


+ve -ve

$$\therefore V_m - V_{Tn} = -\sqrt{\gamma} (V_m - V_{DD} - V_{Tp})$$


$$\Rightarrow V_m = \frac{V_{Tn} + \sqrt{\gamma} (V_{DD} + V_{Tp})}{1 + \sqrt{\gamma}}$$

$$\sqrt{x^2} = |x|$$

NOISE MARGIN ANALYSIS

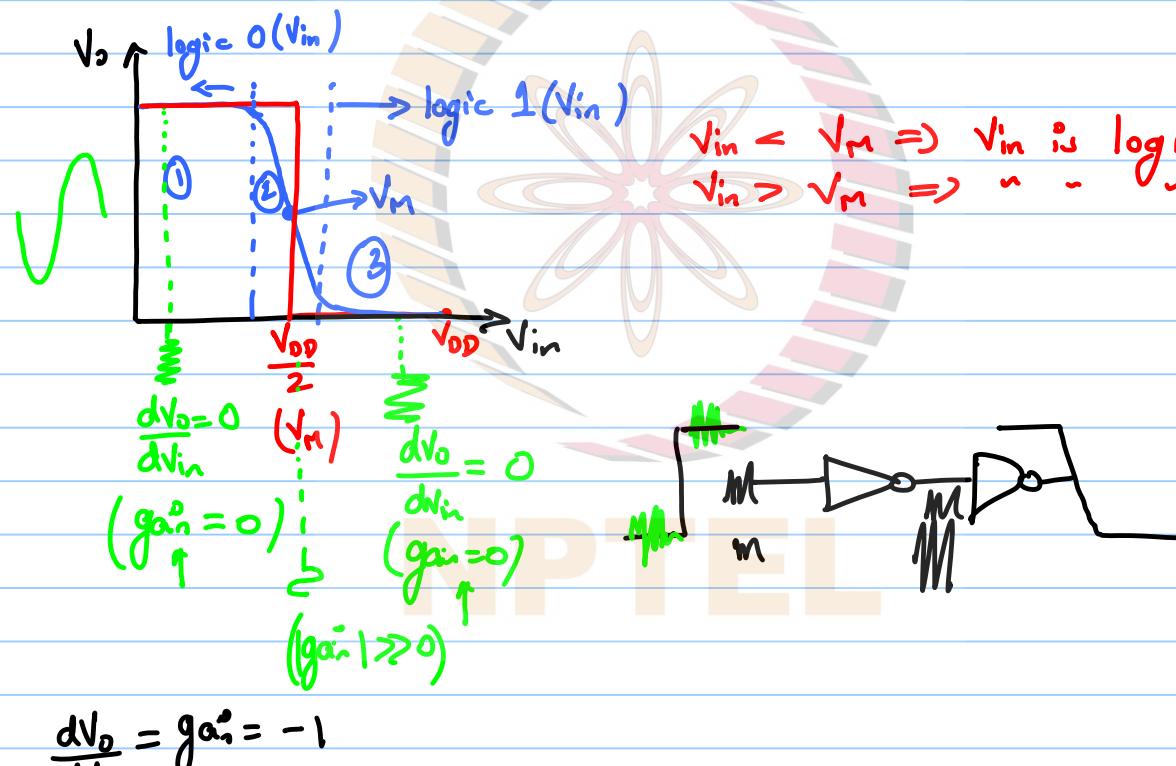

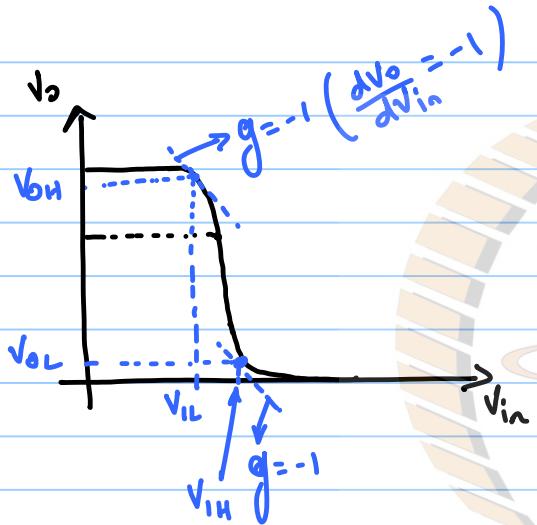$V_{in} < V_M \Rightarrow V_{in} \text{ is logic } 0 \Rightarrow V_o = \text{logic } 1$
 $V_{in} > V_M \Rightarrow V_{in} \text{ is logic } 1 \Rightarrow V_o = \text{logic } 0$




if $V_{in} > V_{IH} \Rightarrow$ input is logic 1
 $V_{in} < V_{IL} \Rightarrow$ ~ ~ ~ 0

$V_{IL} \leq V_{in} \leq V_{IH}$?

$\Rightarrow V_o$ will be logic 0/1 depending on noise (gain is very high)

NPTEL

Finding V_{IL} & V_{IH} :

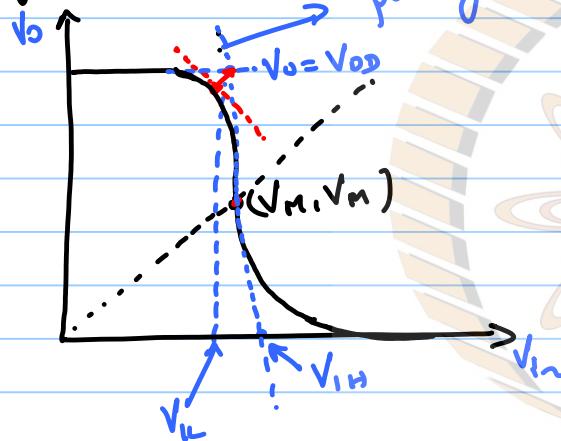

passing through (V_m, V_m) with slope

$$g = \frac{dV_o}{dV_{in}} \Big|_{V_{in}=V_m}$$

Find $\frac{dV_o}{dV_{in}} = g$ @ $V_{in} = V_o = V_m$

V_{in} near V_m

$$I_{DSn}' = K_n W_n \frac{V_{DD} - V_{in}}{L} \left[(V_m - V_{in}) - \frac{V_{DSmin}}{2} \right]$$

$$I_{DSP}' = K_p W_p \frac{V_{DD} - V_{in}}{L} \left[(V_m - V_{DD} - V_{TP}) - \frac{V_{DSamp}}{2} \right]$$

$$\frac{dV_o}{dV_{in}} = g \quad \Big|_{V_{in}=V_o=V_m}$$

$$I_{DSn} = I_{DSn}' (1 + \lambda_n V_o)$$

$$I_{DSP} = I_{DSP}' (1 + \lambda_p (V_o - V_{DD}))$$


$$g =$$

$$g = dV_o / dV_{in} \quad | \quad V_{in} = V_o = V_m$$

$$g = -\frac{1}{I_D(V_M)} \frac{k_n V_{DSATn} + k_p V_{DSATp}}{\lambda_n - \lambda_p}$$

$$g \approx \frac{1+r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$
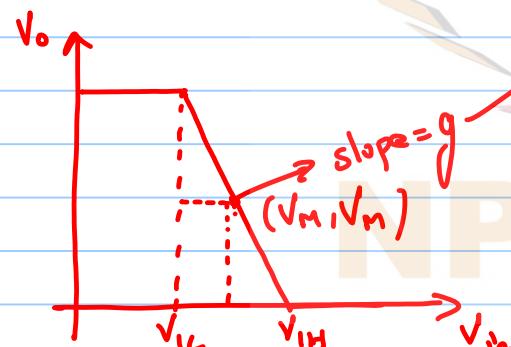
$$r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}}$$



$$g \propto \frac{1}{(\lambda_n - \lambda_p)}$$

$$\lambda_p = -\lambda_n$$

$$g \propto \frac{1}{2\lambda_n}$$

$$g = \frac{-V_M}{V_{IH} - V_M}$$

$$\therefore V_{IH} = V_M - \frac{V_M}{g} > V_M$$

$$g = \frac{V_M - V_{DD}}{V_M - V_{IL}} \Rightarrow V_{IL} = V_M - \frac{(V_M - V_{DD})}{g}$$