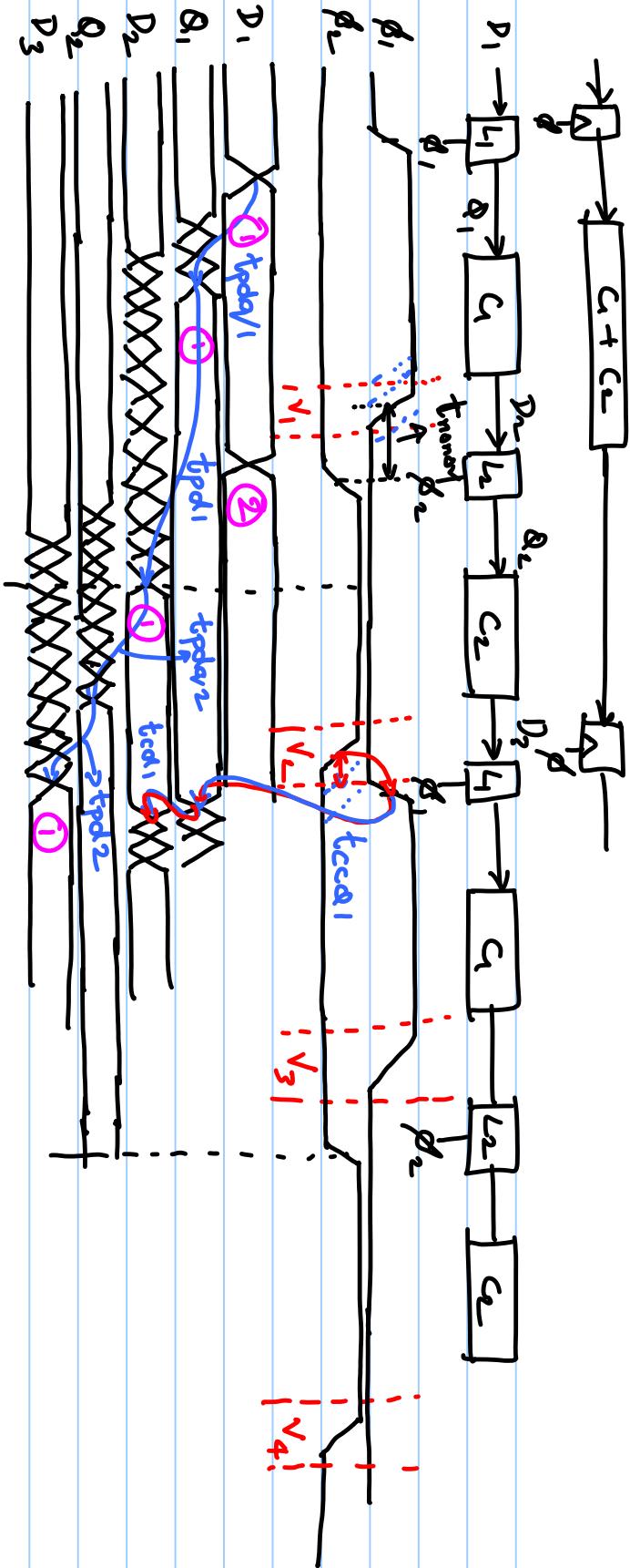


~~11/11/2019~~

EES311

MODULE -S - SEQUENTIAL CIRCUITS



$$T_c \geq t_{pdav1} + t_{pdav2} + t_{pdav3}$$

Skew Tolerant \Rightarrow

$$\frac{tpd_1 + tpd_2}{tpd} \leq T_c - (t_{pdav1} + t_{pdav2})$$

$$t_{skew} + t_{hold} \leq t_{nonov} + t_{ccal_1} + t_{cd_1}$$


$$\Rightarrow$$

$$t_{cd_{1,2}} \geq t_{hold} - t_{nonov}$$

MARK DECAY


$$tpd \leq T_c - \{ t_{pc_0} + t_{cd_{1,2}} \}$$

MIN DELAY

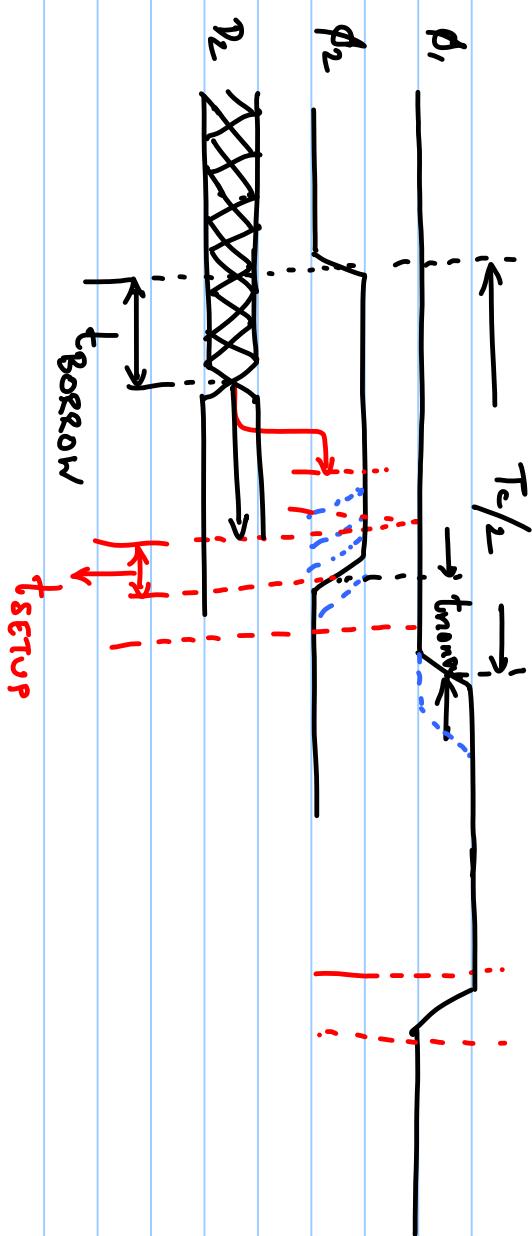

$$\Rightarrow \frac{T_c}{2} \geq t_{borrow} + t_{setup} + t_{hold} + t_{skew}$$
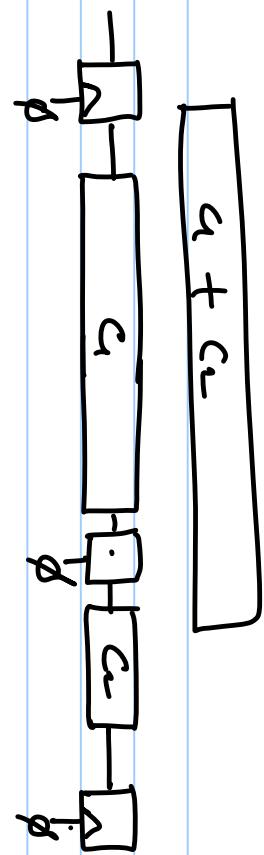
$$\Rightarrow t_{borrow} \leq \frac{T_c}{2} - t_{setup} - t_{hold} - t_{skew}.$$



$$T_c \geq t_{pc,a} + t_{pd,1,2} + t_{cusp}$$

$$T_c \geq t_{pc,a} + \max(t_{pd_1}, t_{pd_2}) + t_{cusp} - \text{Flop.}$$

$$T_c \geq (\underbrace{t_{pd,1} + t_{pd,2}}) + t_{pd,a} + t_{pd,a} - \text{latch}$$

