

16/08/2019

EE5311




MODULE 1: THE TRANSISTOR

PMOS TRANSISTOR $\rightarrow \{k'_p, \lambda_p, V_{DSATp}, V_{rop}, \gamma_p\}$ all are -ve numbers.

$$I_{DS} = k' \frac{W}{L} V_{max} \left[(V_{GS} - V_T) - \frac{V_{max}}{2} \right] (1 + \lambda V_{DS})$$

NPTEL

CAPACITANCE CHARGING / DISCHARGING

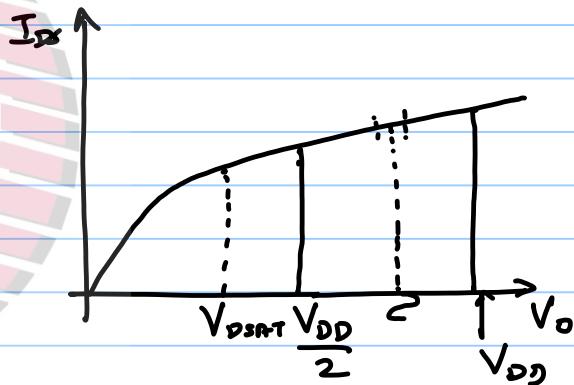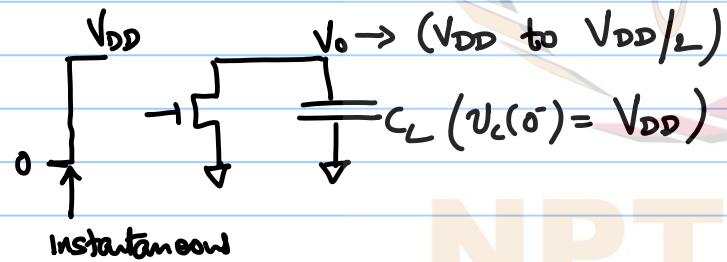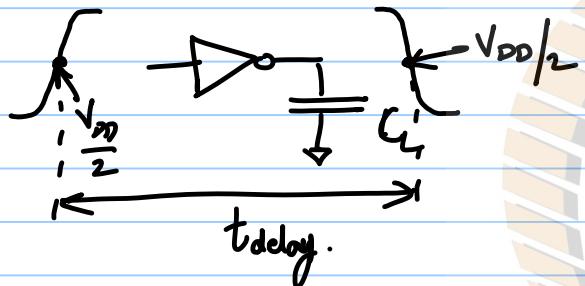

$$I_{DS} = k' \frac{W}{L} V_{DSATn} \left[(V_{DD} - V_{Tn}) - \frac{V_{DSATn}}{2} \right] (1 + \lambda V_o)$$

$$= I_0 (1 + \lambda V_o)$$


$$R(V_o) = \frac{V_o}{I_o(1+\lambda V_o)}$$

$$R_{eq} = \frac{1}{(\frac{1}{V_f - V_i}) \int_{V_i}^{V_f} R(V_o) dV_o} \sim \frac{1}{(-V_{DD}/2)} \int_{V_{DD}}^{V_{DD}/2} \frac{V_o}{I_o} (1 - \lambda V_o) dV_o$$


$$= \frac{1}{I_o} \cdot \frac{2}{V_{DD}} \int_{V_{DD}/2}^{V_{DD}} V_o (1 - \lambda V_o) dV_o$$

$$= \frac{3}{4} \frac{V_{DD}}{I_o} - \frac{7}{12} \frac{\lambda V_{DD}^2}{I_o}$$

$$\Rightarrow R_{eq} = \frac{3}{4} \frac{V_{DD}}{I_o} \quad (\text{if } \lambda = 0)$$

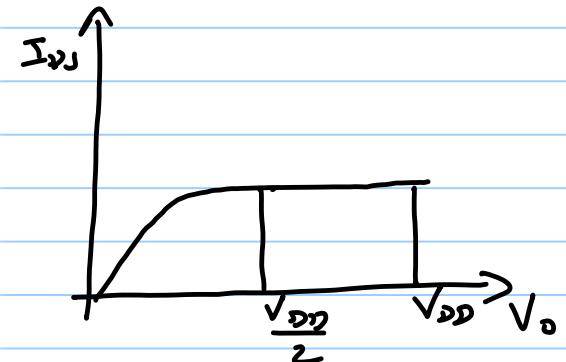


METHOD 2 :

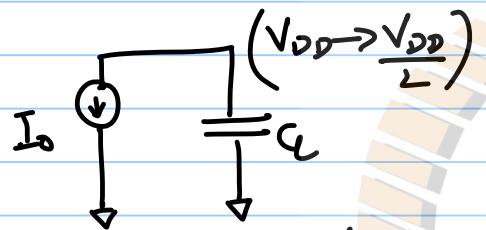


$$V_o(t) = V_{DD} - \frac{I_o}{C} t \leftarrow$$

$$\tau = \frac{C \Delta V}{I_o} = \frac{C (V_{DD}/2)}{I_o}$$

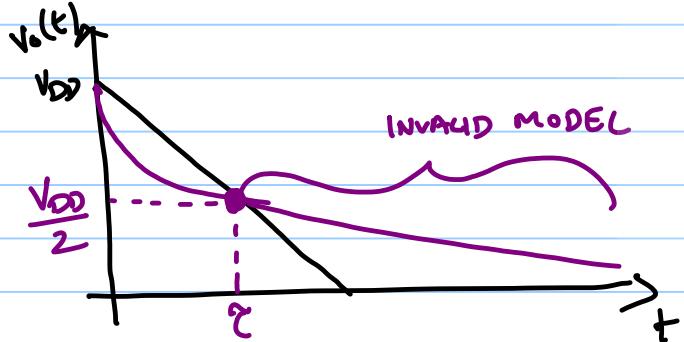

METHOD 1 :

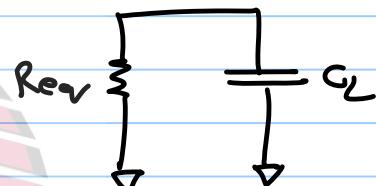

$$V_o(t) = V_{DD} e^{-t/\tau'}$$

$$R_{eq} = \frac{3}{4} \frac{V_{DD}}{I_o}$$

$$\Rightarrow \tau' = R_{eq} C$$

$$\tau = 0.693 \cdot \frac{3}{4} \frac{V_{DD} C}{I_o} \approx 0.5 \frac{V_{DD} C}{I_o}$$

$$R_{eq} = \frac{3}{4} \frac{V_{DD}}{I_0}$$

$$R_{eq} \propto \frac{1}{W}$$


if V_{DD} LARGE ie $V_{DD} - V_{Tn} - \frac{V_{DSATn}}{2} \sim V_{DD}$

R_{eq} not a fn of V_{DD}



$$I_0 = \begin{cases} k_n \frac{W}{L} V_{DSATn} [(V_{DD} - V_{Tn}) - \frac{V_{DSATn}}{2}] & \hookrightarrow VEL \text{ SAT (SC)} \\ \frac{1}{2} k_n \frac{W}{L} (V_{DD} - V_T)^2 & - \text{SAT (LONG)} \end{cases}$$

NPTEL



CAPACITANCE:

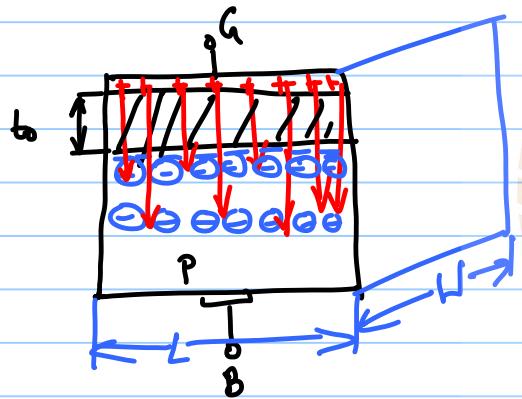

$$C_0 = C_{ox} \times W L$$

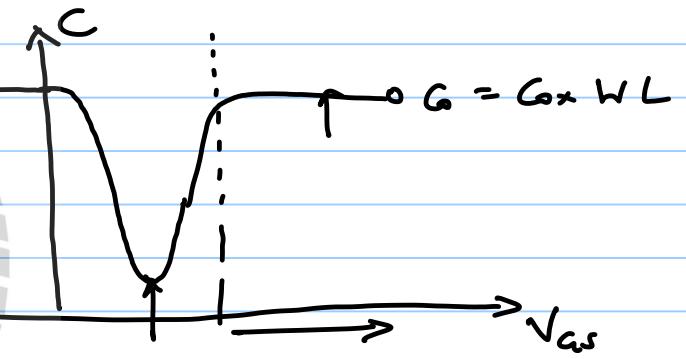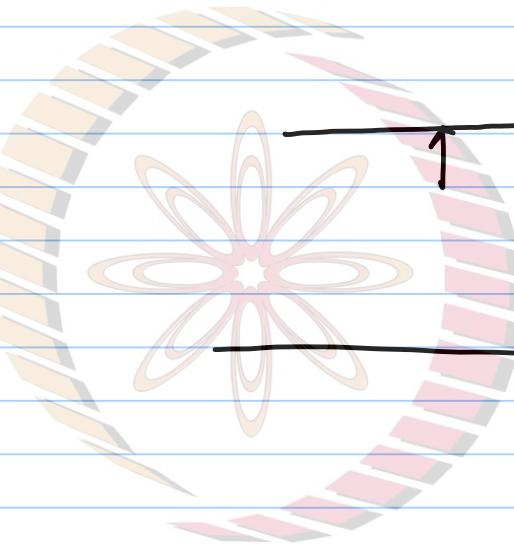

NPTEL

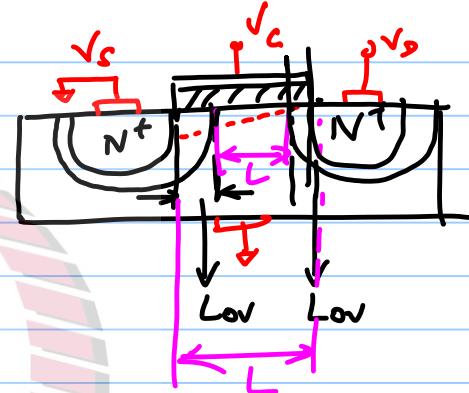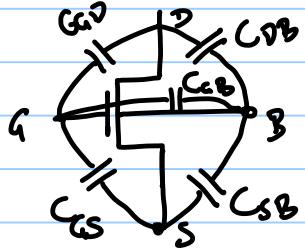


$$C_g = \underline{C_{GS}} + \underline{C_{GD}} + \underline{C_{DS}} = \textcircled{C_{ox} \cdot W \cdot L} \rightarrow \textcircled{C_0}$$

$$C_{ov} = C_{ox} \cdot W \cdot L_{ov}$$

$$\begin{aligned} \text{TOTAL GATE CAP} &= C_g + 2C_{ov} = (C_{ox} \cdot W \cdot L + 2C_{ox} \cdot W \cdot L_{ov}) \\ &= W(C_{ox} \cdot L + 2C_{ox} \cdot L_{ov}) \end{aligned}$$

C_{DB} & C_{SG}

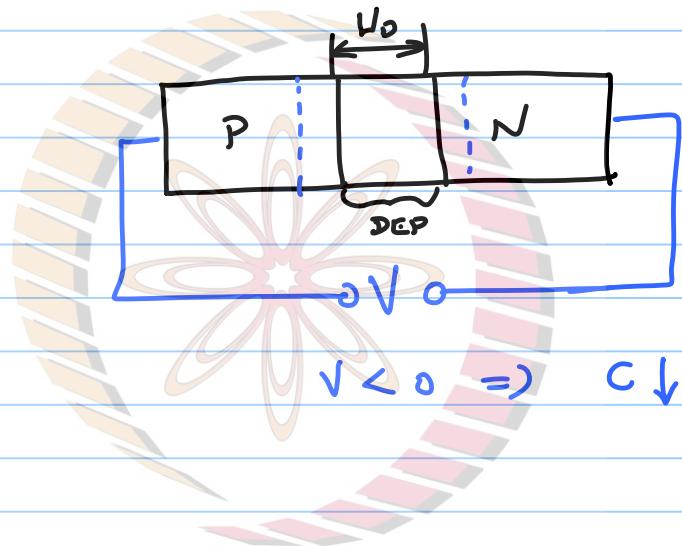

NPTEL