
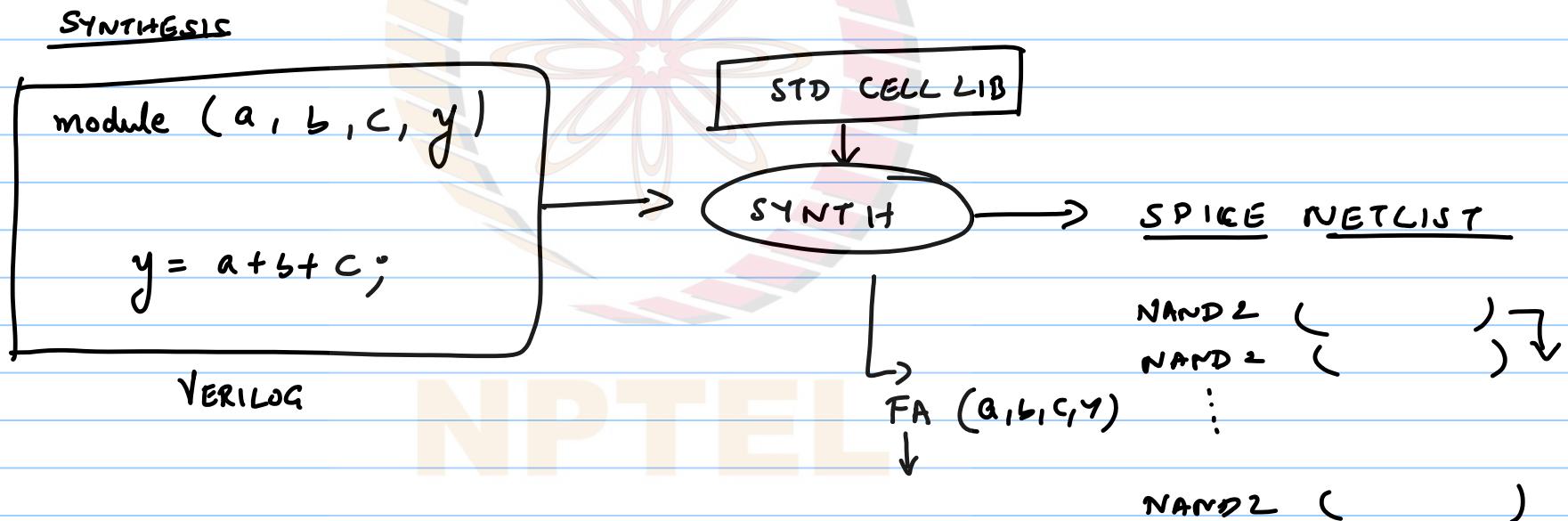


16/09/2019

EES311


MODULE - 4 - COMBINATIONAL CIRCUITS

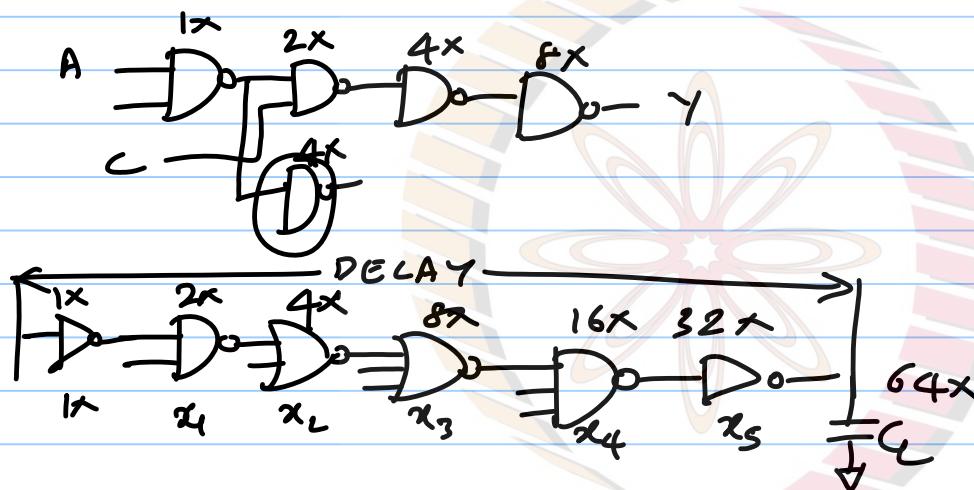




ESTIMATING GATE DELAY


ESTIMATING PATH DELAY

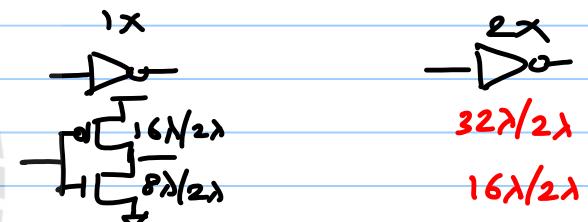

GATE DELAY OPTIMIZATION

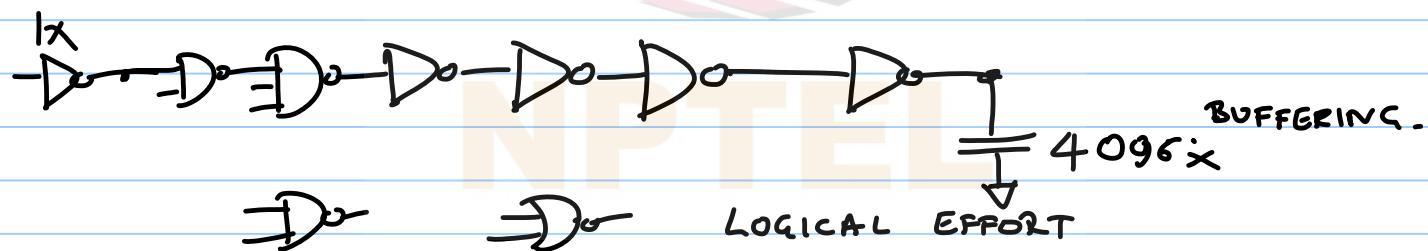

BASICS

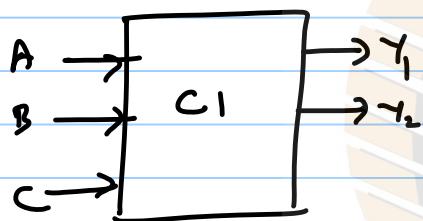

A	B	C	Y_1	Y_2
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
1	1	1	1	0


$$Y_1 = \sum m(0, 3, 5) \quad \left. \right\} \text{SUM OF PRODUCTS.}$$

$$Y_2 = \sum m(1, 2, 7)$$


$$Y_1 = \overbrace{\bar{A}\bar{B}\bar{C}}^0 + \overbrace{\bar{A}B\bar{C}}^3 + \overbrace{A\bar{B}\bar{C}}^5$$

OR

ACTIVE HIGH SWITCHES

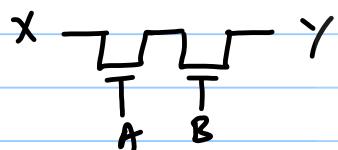


$$y = AB \cdot x$$

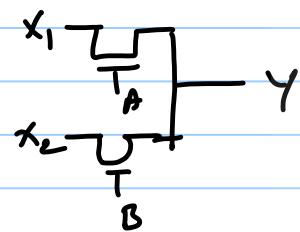


$$y = Ax_1 + Bx_2$$

ACTIVE LOW SWITCHES

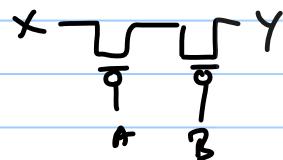

$$y = \bar{A}\bar{B}x$$

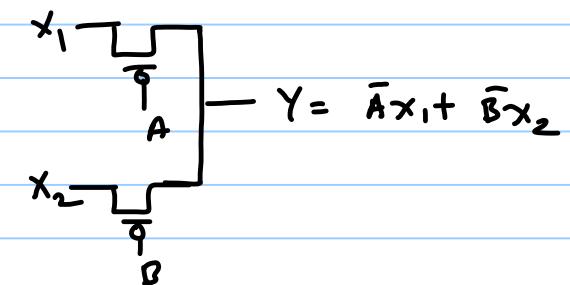

$$y = \bar{A}x_1 + \bar{B}x_2$$