


24/10/2019

EES311

MODULE - 6 - ADDERS


MIRROR ADDER

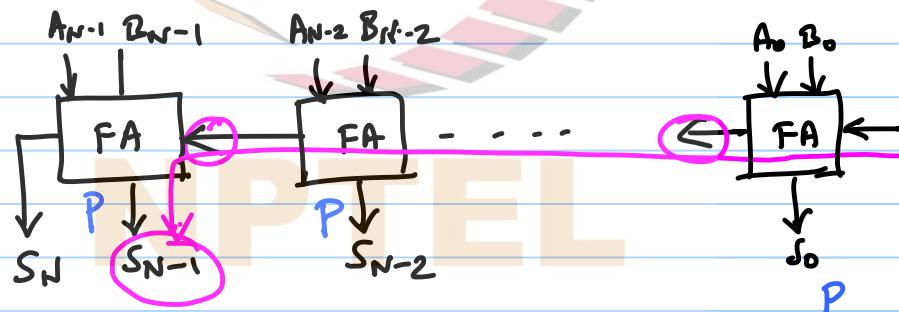- 1) MIRROR IDEA TO REDUCE PMOS STACK SIZE
- 2) C_{in} (TIMING CRITICAL) \rightarrow TO TRANSISTOR OF LEAST LE
- 3) C_{in} CONNECTED TO \sim CLOSEST TO O/P.
- 4) OPTIMIZED SUM TO BE GEN FROM \bar{C}_0





$$\begin{aligned} P &= A \oplus B \\ G &= AB \\ S &= P \oplus C_{in} \\ C_{out} &= \underline{G} + \underline{P} \underline{C_{in}} \end{aligned}$$
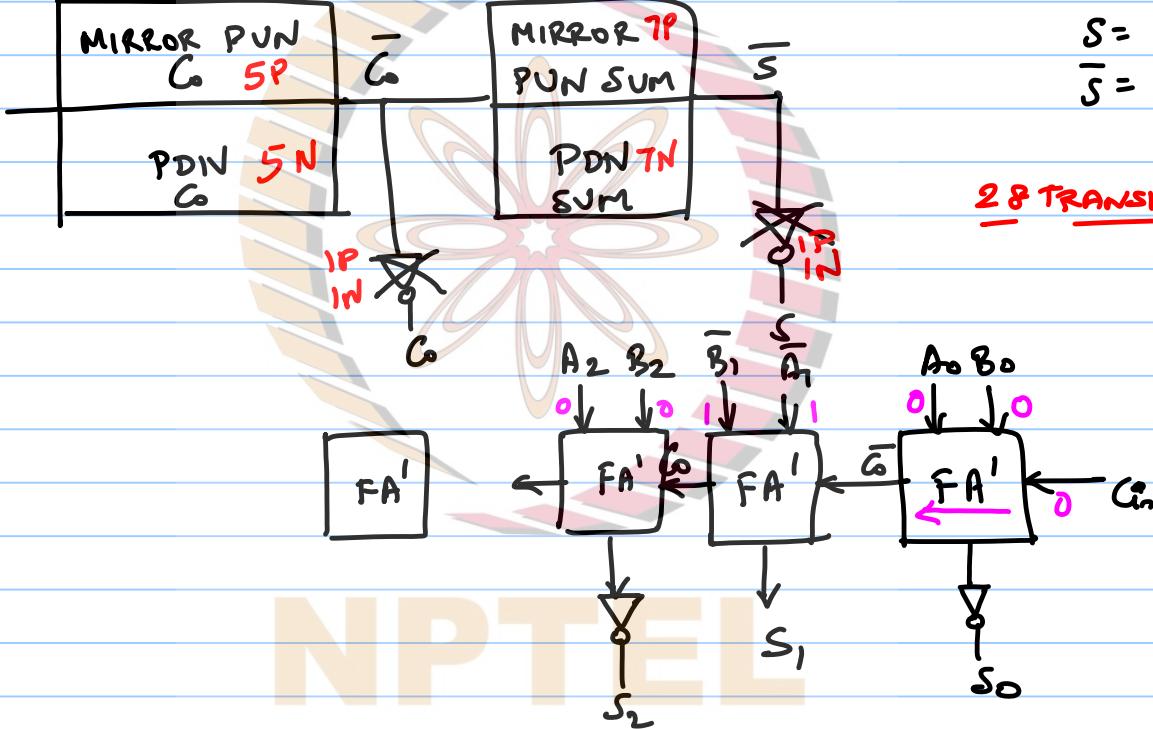
$$t_{\text{tripple}} = t_{\text{sum}} + (N-1)t_{\text{carry}}$$



$$S = f(A, B, C)$$

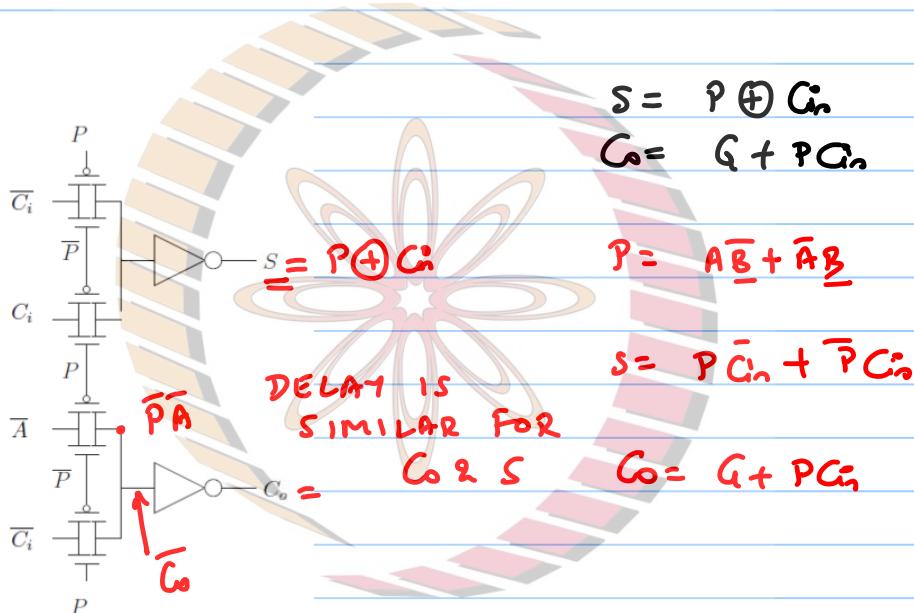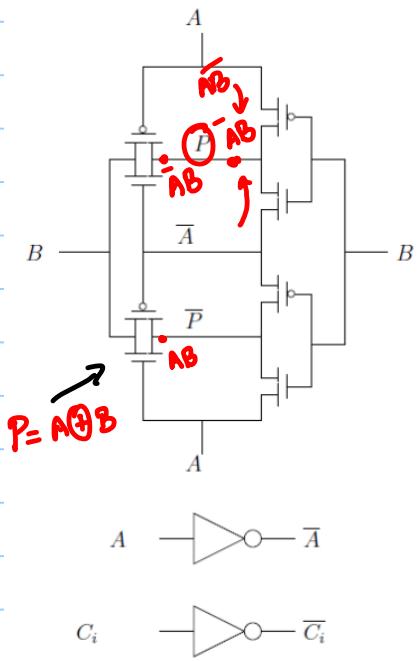
$$\bar{S} = f(\bar{A}, \bar{B}, \bar{C})$$



NPTEL

SERVER : 128


CARRY SKIP ADDER

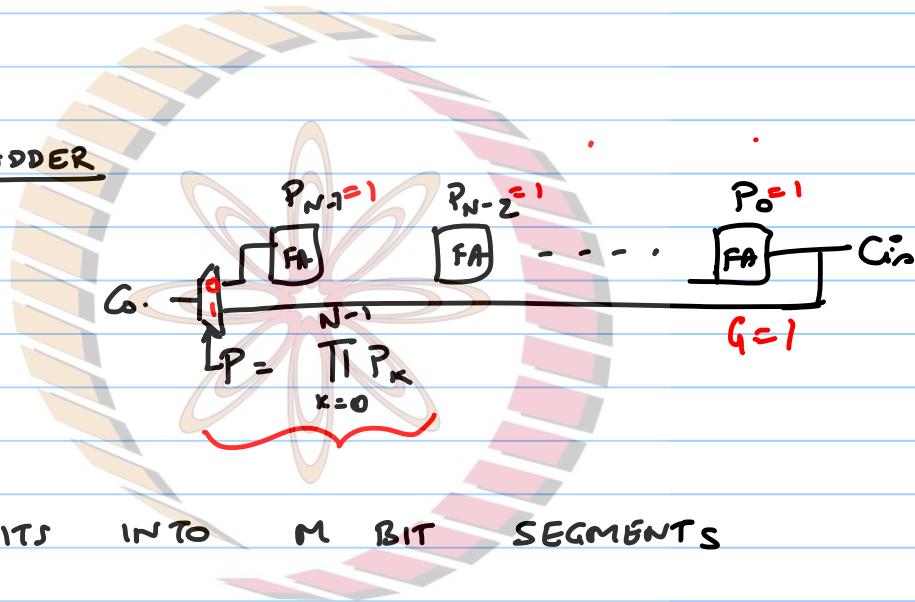


PARTITION N BITS INTO M BIT SEGMENTS

STAGES =

$$\frac{N}{M}$$

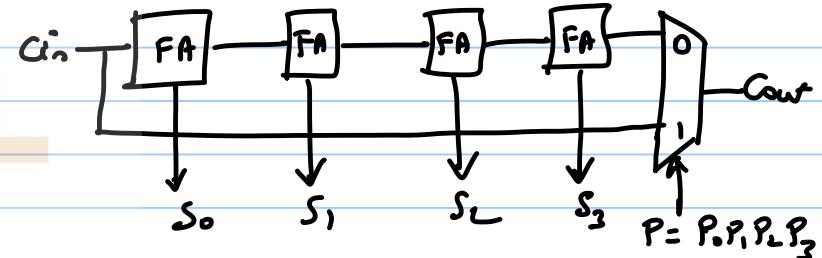

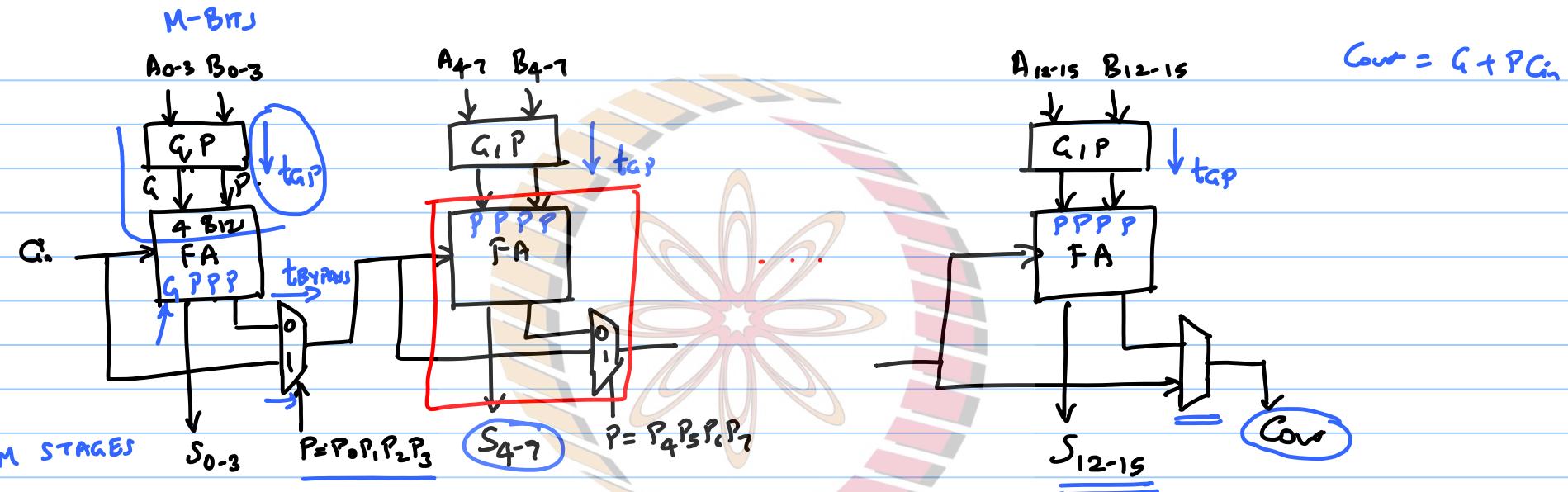

$t_{GP} = \text{CREATE GEN/PROP SIGNALS.}$

$t_{sum} = \text{FA TIME TO CREATE SUM}$

$t_{carry} = \text{TIME TO CREATE CARRY}$

$t_{BYPASS} = \text{MUX TIME}$

$t_{carry-sk1p} = t_{GP} +$

$M t_{carry}$

$$+ \left(\frac{N-1}{M}\right) t_{BYPASS} + (M-1) t_{carry} + t_{sum}$$