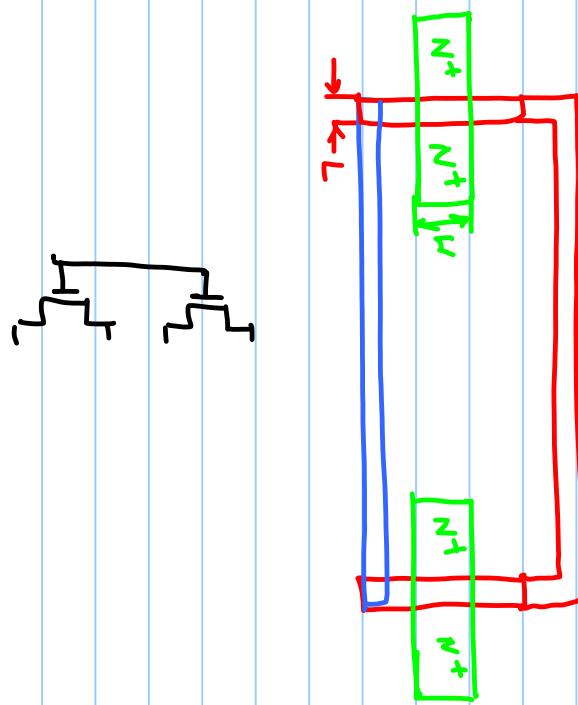


~~30/08/2019~~

EE5311




MODULE - 3

NOISE MARGIN



$$g @ V_{in} = V_o = V_m = \frac{dV_o}{dV_{in}} \Big|_{V_{in}=V_o=V_m}$$

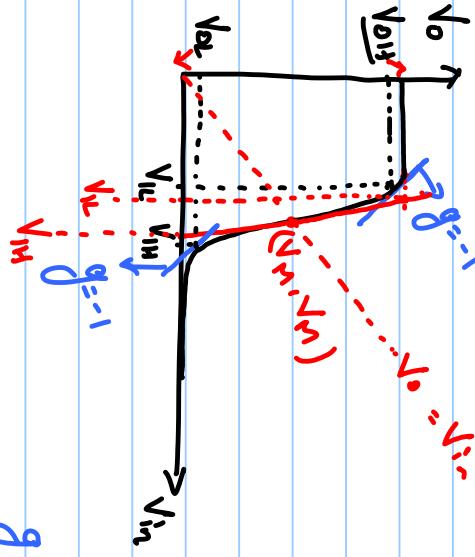


$$g = \frac{dV_o}{dV_{in}}$$

$$V_{1L} = V_m + \left(\frac{V_{od} - V_m}{g} \right)$$

$$V_{1H} = V_m - \frac{V_m}{g}$$

Works ONLY WHEN CM is > 0

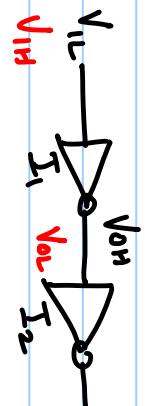


$$V_{DD} - \frac{NM_H}{V_{IH}} V_{IH}$$

$$V_{OH} > V_{IH}$$

$$V_{OL} - \frac{NM_L}{V_{IL}} V_{IL}$$

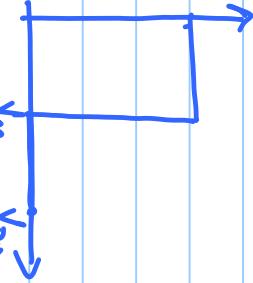
$$\text{NOISE MARGIN HIGH} = NM_H = V_{OH} - V_{IH}$$



$$V_{OL} < V_{IL}$$

$$V_{DD} - \left(V_m - \frac{V_m}{g} \right)$$
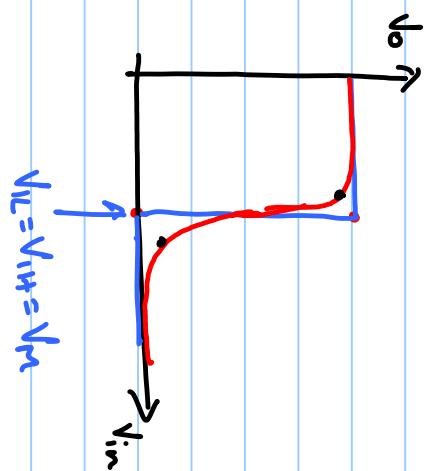
$$\begin{aligned} NM_L &= V_{IL} - V_{OL} \\ &= V_{IL} = V_m + \left(\frac{V_{DD} - V_m}{g} \right) \end{aligned}$$



$$V_L = V_H = V_m$$

$$g \propto \frac{1}{2\lambda n} \quad (\text{if } \lambda n = -\lambda p)$$

$$\textcircled{2} \quad I_{DSS} = \frac{1}{2} K_m \frac{W}{L} (V_m - V_{Tn})^2$$

$$I_{DSR} = \frac{1}{2} K_p \frac{W}{L} (V_m - V_{Tp} - V_{Tn})^2$$

$$V_m = V_H = V_o$$