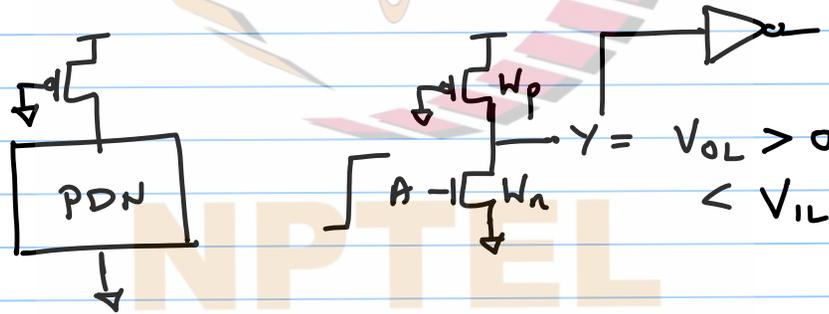


4/10/2019

EE5311


MODULE - 4 - COMBINATIONAL CIRCUITS

RATIO'ED CIRCUIT / PSEUDO NMOS LOGIC



$$V_{OL} \propto \frac{W_p}{W_n} ; \text{ Let } \frac{W_p}{W_n} = \alpha < 1 .$$


UNIT INVERTER

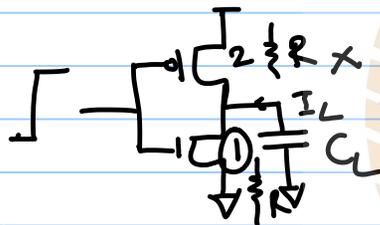

$I_L = |I_n|$
OK

$I_L = |I_p|$


UNIT INV

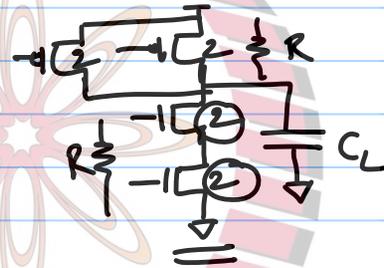

PULL UP/DOWN RES = R


$\tau = \frac{3}{4} \frac{V_{DD}}{I} \times 0.693 \cdot C$

$\tau = \frac{C \Delta V}{I}$

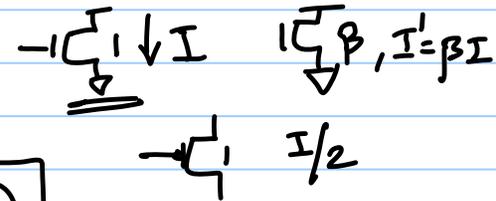

Let $W_n = \beta$

$\Rightarrow W_p = \alpha \beta$

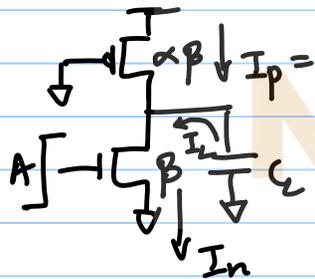

$\beta = 1 ??$

$I_n = I_p + I_L$

$I_n = \beta I$

$I_p = (\alpha \beta / 2) I$

$$\beta \frac{d}{2} = \frac{\alpha \beta d}{2} + d$$


$$\Rightarrow \beta(1 - \alpha/2) = 1$$

$$\therefore \beta = \frac{1}{(1 - \alpha/2)}$$

$$\alpha = 1/2$$


$$\Rightarrow \beta = 4/3$$

UNIT INV: (PSEUDO NMOS)

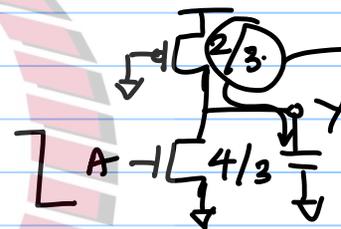

$$C_A = \frac{4}{3} C$$

PULL UP:

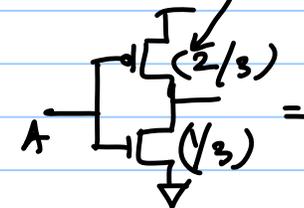


$$C_A = C$$

$$\therefore g_{pu} = 4/3 > 1$$


NPTEL

PULL DOWN:

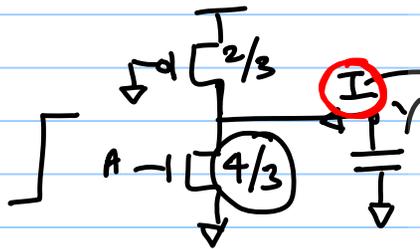

$$C_A = \frac{4}{3} C$$



REF INV:

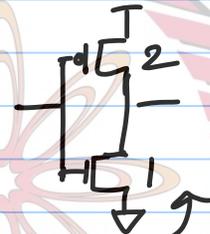


$$C_A = 3 \cdot C$$

$$\therefore g_{pd} = 4/9 < 1$$


NPTEL

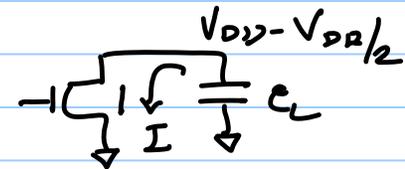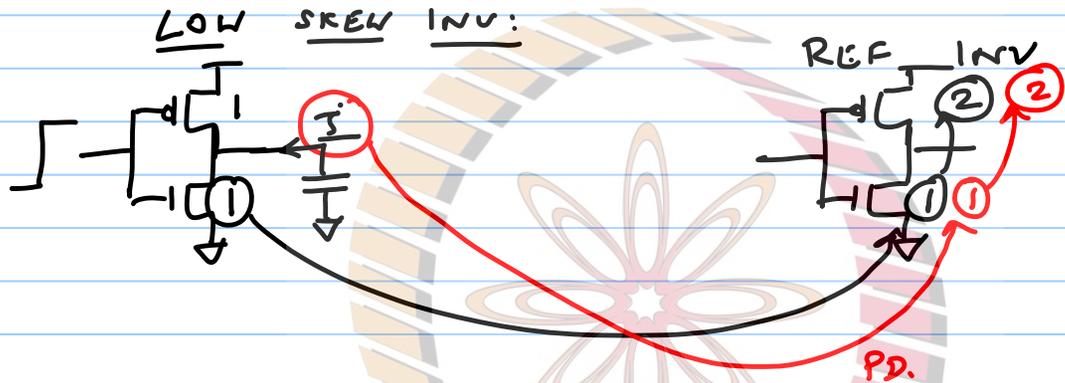



PSEUDO NMOS: PULL UP

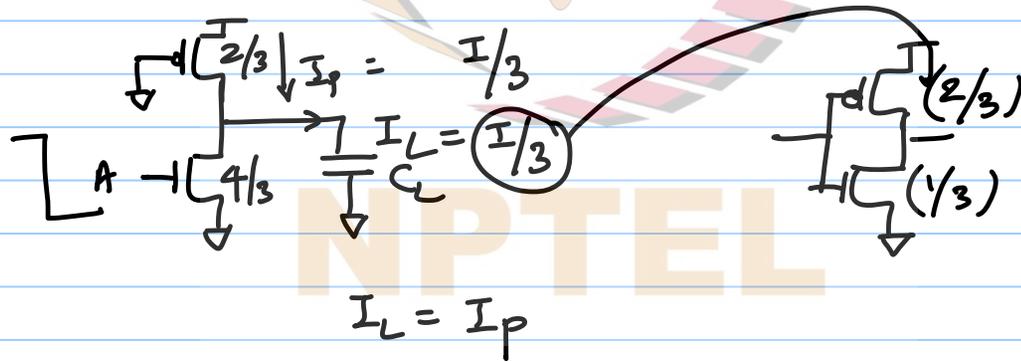


NAND-2 (PSEUDO NMOS)

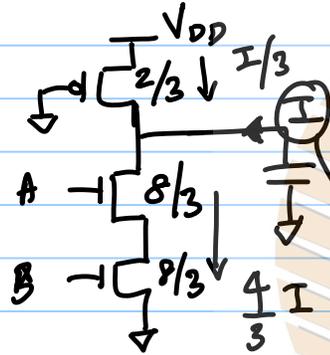

$$C_A = C_B = \frac{8}{3} C$$

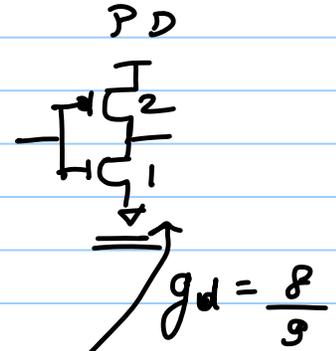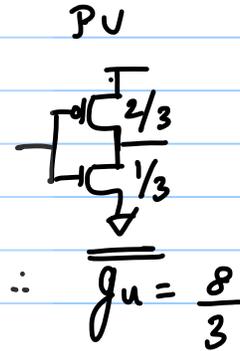

NOR-3

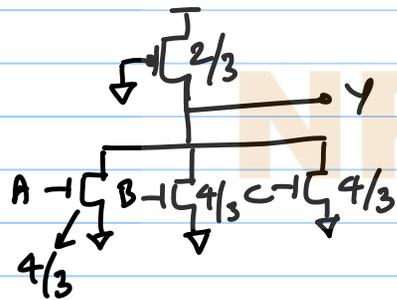


$$g_u = \frac{4}{3}$$

$$g_d = \frac{4}{9}$$

CASCADE VOLTAGE SWITCH LOGIC

INVERTER

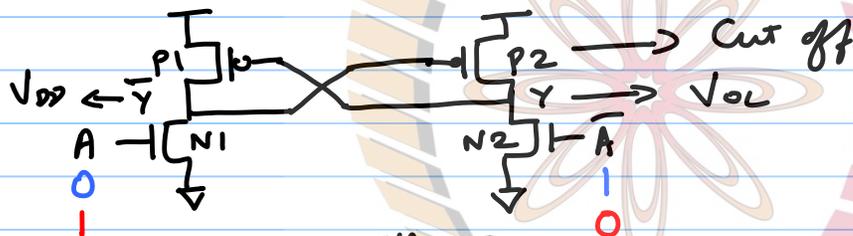

NAND2

