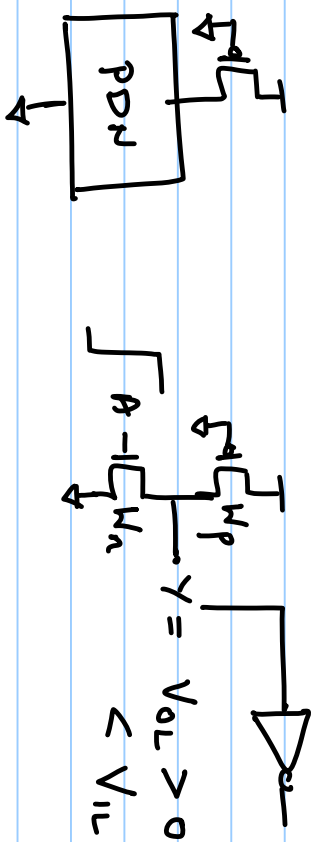


14/10/2019

EE5311


Module - 4 - Combinational Circuits

Ratioed Circuit / Pseudo Nmos Logic



$$V_{OL} \propto \frac{W_p}{W_n} \quad ; \quad \text{Let } \frac{W_p}{W_n} = \alpha < 1$$

UNIT INVERTER

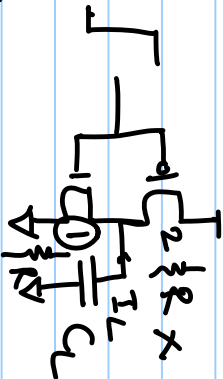


UNIT INV

$$I_L = |I_n|$$

OK

$$I_L = |I_p|$$

PULL UP/DOWN RES = R

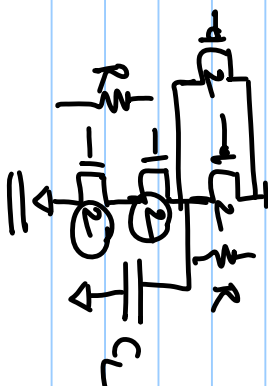


$$\tau = \frac{C \Delta V}{I}$$

$$\tau = \frac{3}{4} \frac{V_{DD}}{I} \times 0.693 \cdot C$$

$$\text{Let } W_n = p$$

$$\Rightarrow W_p = \alpha p$$

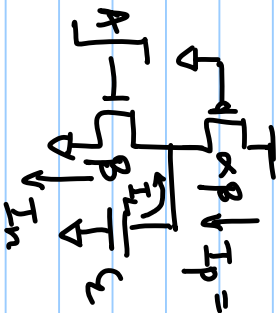

$$\beta = 2 \quad ??$$

$$I_n = \beta I$$

$$I_p = (\alpha \beta / 2) I$$

$$I_n = I_p + I_L$$

$$-I_p \uparrow I \quad I_p \uparrow I$$

$$I/2$$

$$\beta \frac{W}{L} = \frac{\alpha \beta \frac{W}{L}}{2} + \frac{W}{L}$$


$$\Rightarrow \beta (1 - \alpha/2) = 1$$

$$\therefore \beta = 1/(1 - \alpha/2)$$


$$\alpha = 1/2$$

$$\Rightarrow \beta = 4/3$$

UNIT INV: (PSEUDO NMOS)

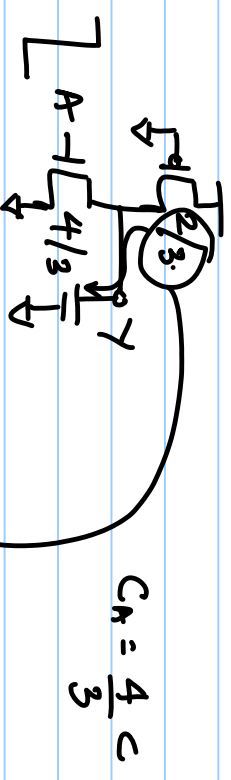


PULL UP:

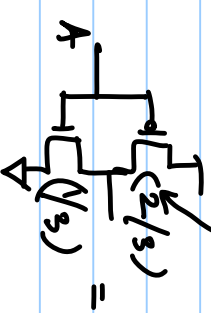

$$C_A = C$$

$$\therefore g_{pu} = 4/3 > 1$$

Rule Down:

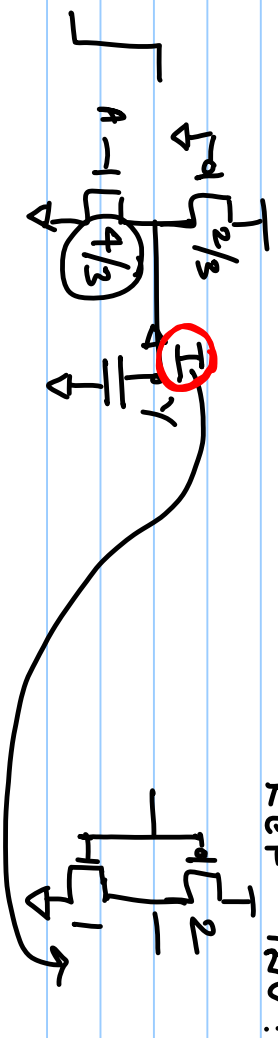


$$C_A = \frac{4}{3} C$$


$$C_A = 3 \cdot C$$

$$\therefore g_{pd} = 4/9 < 1$$


LOW SKEW INV:

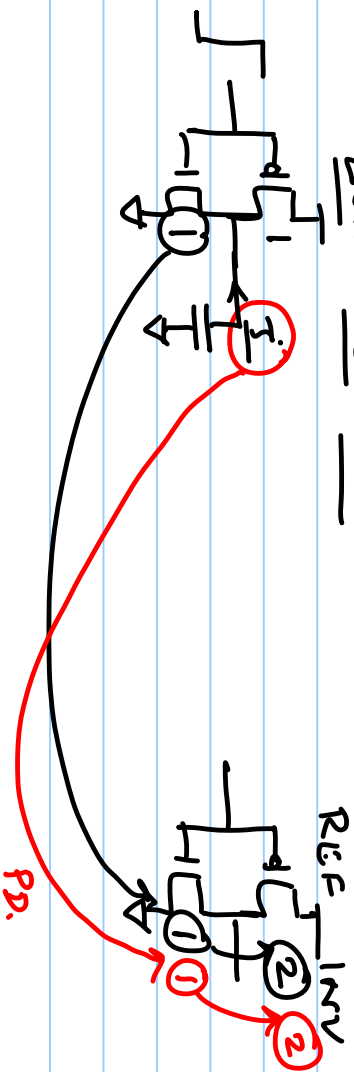


Pseudo Nmos: Pull UP

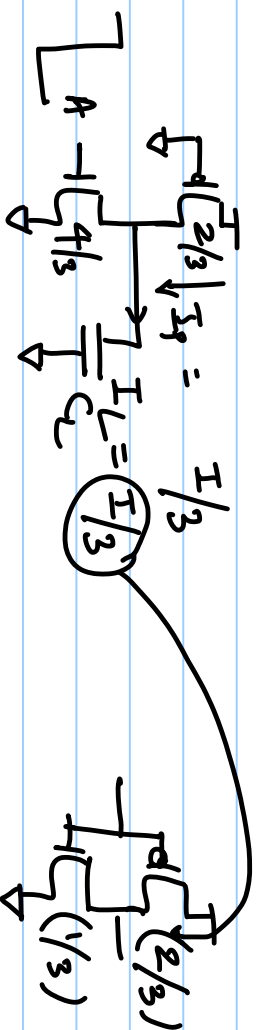

$$I_L = I_P$$

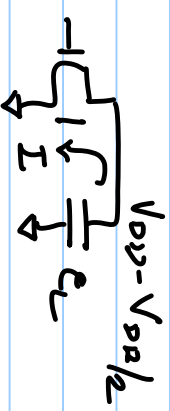

NAND-2 (PSEUDO NMOS)

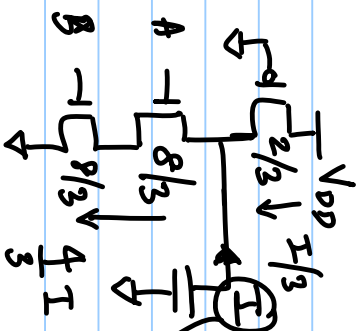

$$C_A = C_B = \frac{8}{3} C$$


PV

$$\therefore \overline{g_u} = \frac{8}{3}$$

PD

$$g_d = \frac{8}{9}$$

NDR 3

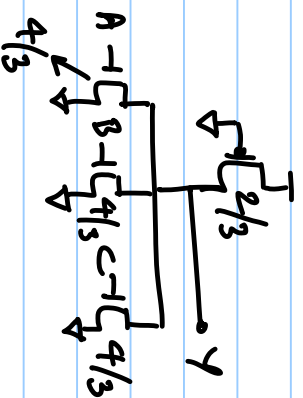


$$g_u = \frac{4}{3}$$


$$g_d = \frac{4}{9}$$

CASCODE Voltage Switch Logic

INVERTER

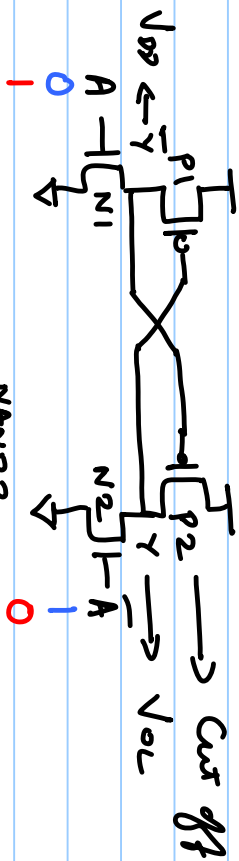

NAND2

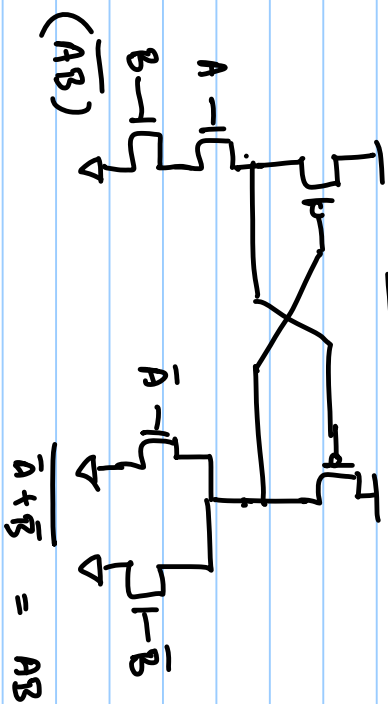

$$\overline{A+B} = AB$$

