

~~09/09/2019~~

EE5311

MODULE - 3 - THE INVERTER


POWER:

- 1) Dynamic power
- 2) Short circuit power
- 3) Leakage power


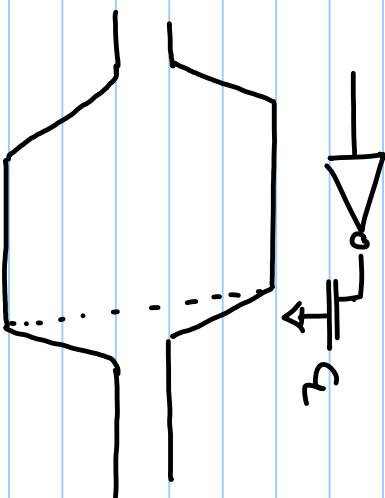
1) Dynamic Power:

$$P_{dyn} = \frac{1}{2} C_L V_{DD}^2$$

$$P_{dyn} = \frac{1}{2} C_L \frac{V_{DD}^2}{T}$$



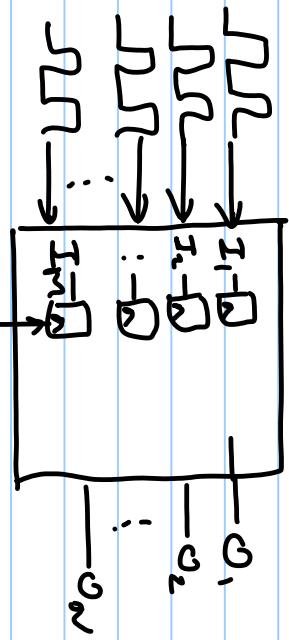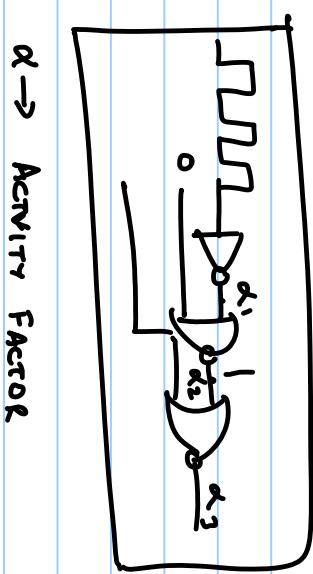For every charge/discharge cycle Energy =  $C_L V_{DD}^2 (J)$



$\alpha \rightarrow$  ACTIVITY FACTOR

$$\text{AVERAGE ENERGY PER NODE} = \alpha C_L V_{DD}^2$$



$$P_{Din} = \alpha C_L V_{DD}^2 f_{clk}$$

$$\rightarrow D_{out} \frac{1}{f_{clk}}$$

Strongest Control
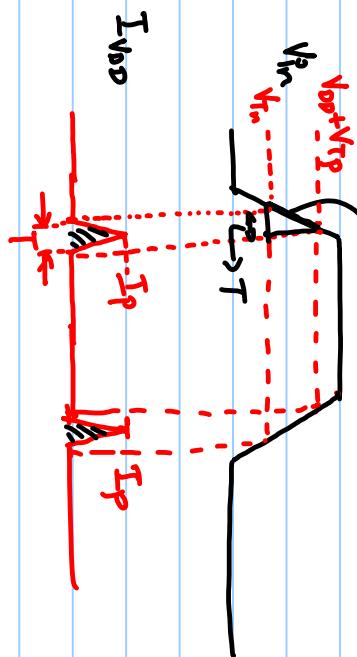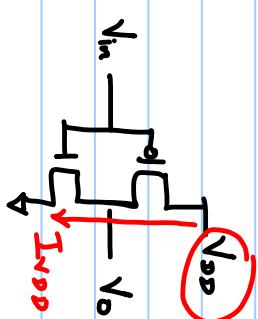
### SHORT CIRCUIT POWER

$$\text{slope} = \text{curr} = \frac{V_{DD}}{\tau_{rise}}$$



$\rightarrow t$

$$E_{SC} = \int_0^T V_{DD} \cdot I_{V_{DD}}(t) dt = \frac{1}{2} V_{DD} \cdot I_P (\tau) \rightarrow$$

$$\frac{V_{DD}}{t_{rise}} = \frac{V_{DD} + V_{rrp} - V_{rn}}{(T)} \Rightarrow T = \frac{(V_{DD} - 2V_{rn})}{V_{DD}} t_{rise} \quad (\text{if } V_{rn} = -V_{rrp})$$

$$E_{sc} = \sqrt{V_{DD}} \cdot I_p \left( \frac{(V_{DD} - 2V_{Th})}{\sqrt{V_{DD}}} \right) \cdot t_{rise}$$

$$= I_p \left( \frac{(V_{DD} - 2V_{Th})}{\sqrt{V_{DD}}} \right) t_{rise}$$

$$P_{sc} = \alpha E_{sc} \cdot f_{sc,k}$$



$$= \alpha \cdot I_p (V_{DD} - 2V_{Th}) \cdot t_{rise} \cdot f_{sc,k}$$

$$\text{Transient Power} = P_{DW} + P_{sc} = \alpha f_{sc,k} \cdot (C_L V_{DD}^2 + I_p (V_{DD} - 2V_{Th}) t_{rise})$$

↑  
Dominant

Reduce  $f_{sc,k}$  to reduce  $P_{trans}$ .

## LEAKAGE Power

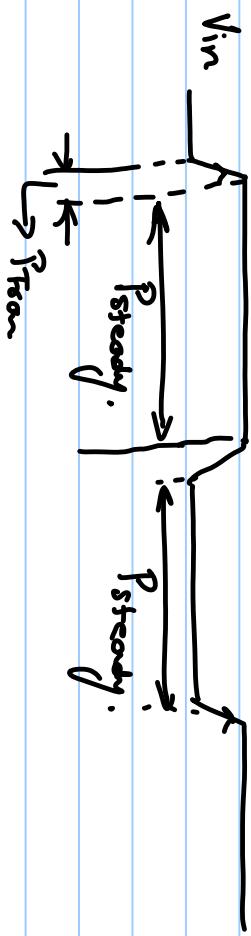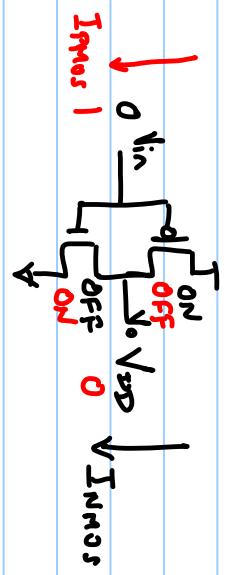

$$\text{Power from } V_{DD} = V_{DD} \cdot I_{INmos} / V_{DD} \cdot I_{IPmos}$$

$$\text{Avg Pow} = V_{DD} \left( \frac{I_{INmos} + I_{IPmos}}{2} \right)$$

$$I_{IPmos} = \frac{N}{L} I_s \left( e^{\frac{V_{BS}-V_{in}}{n\beta_L}} \right) \left( 1 - e^{-V_{DS}/\phi_L} \right)$$

## Stacking Effect

1-stack

2-stack.

$$0 \rightarrow \boxed{I_1} \downarrow I_1'$$

$$0 \rightarrow \boxed{\frac{N_1}{N_1 + N_2} V_{in}} \downarrow I_1' \equiv -\boxed{\frac{V_{in}}{N_2}}$$

ASSUME:  
 1) No Body Effect ( $V = 0$ )  
 2) No DIBL ( $\eta = 0$ )  
 3)  $V_{DD}$  is Large  
 4) Intrinsic Factor =  $n = 1$

(a)

$$\boxed{I_1 = I_2}$$

$V_{as}$

$V_{os}$

$$\begin{bmatrix} N_1 & -V_R & V_{os} \\ N_2 & 0 & V_x \end{bmatrix}$$

(b)

$$I_1 = \frac{N_1 I_{os} e^{\frac{-V_x - V_{in}}{qT_b}}}{L}$$

$$I_2 = \frac{N_2 I_{os} e^{\left(\frac{-V_{in}}{qT_b}\right)} \left(1 - e^{\frac{-V_x}{qT_b}}\right)}{L}$$

$\Rightarrow V_x$  closer to GND

N1: Large  $V_{as}$  (0)  $\Rightarrow V_{os}$  is small

$$I_1 = I_2$$

$$\Rightarrow \frac{N}{L} e^{\frac{-V_{Tn}}{q_t}} = \frac{N}{L} e^{\frac{-V_{Tn}}{q_t}} (1 - e^{-V_{Tn}/q_t})$$

$$\Rightarrow V_T = q_t \ln(e)$$

$$I_1 = \frac{N}{L} \cdot I_0 e^{\frac{(-q_t \ln(e) - V_{Tn})}{q_t}}$$

$$\therefore I_1 = \frac{1}{2} \left( \frac{N}{L} \right) \cdot I_0 e^{\frac{-V_{Tn}}{q_t}}$$

$$I_1' = \frac{N}{L} \cdot I_0 e^{-\frac{V_{Tn}}{q_t}}$$

## V<sub>TH</sub> DIBL

$$0 - \boxed{V_{DD}} \uparrow \quad 0 - \boxed{V_{DD}} \uparrow \\ \downarrow \qquad \qquad \qquad \downarrow$$

DIBL EFFECT ON

$$V_{TH} = \gamma V_{DD}$$

DIBL EFFECT ON

$$N_1 = \gamma (V_{DD} - V_x)$$

$$\downarrow \\ V_{in}$$