
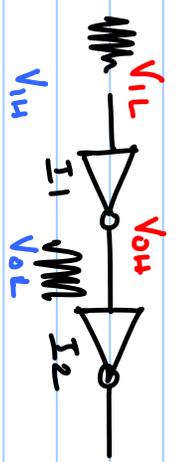


04/09/2019

EE5311

MODULE - 3 - THE INVERTER

NOISE MARGIN

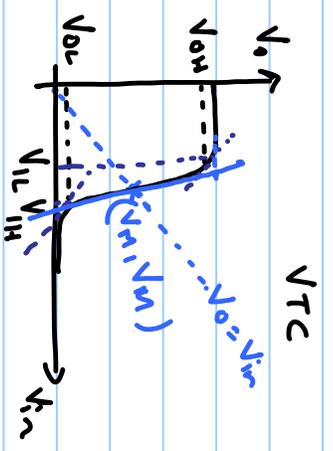


$NM_H = V_{OH} - V_{IH}$


$NM_L = V_{IL} - V_{OL}$

LONG CHANNEL INVERTERS (ALL SCE = 0)

$$g = \frac{dV_o}{dV_{in}} \Big|_{V_{in}=V_o=V_M} \propto \frac{1}{(\lambda_n - \lambda_p)} \rightarrow \frac{1}{2\lambda_n} \quad (\lambda_p = -\lambda_n)$$

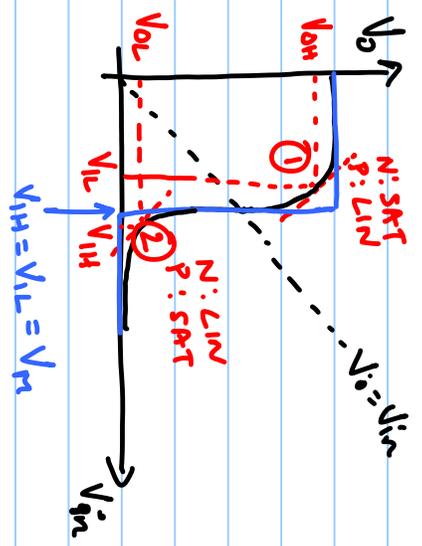

$$\frac{dV_o}{dV_{in}} = -1$$

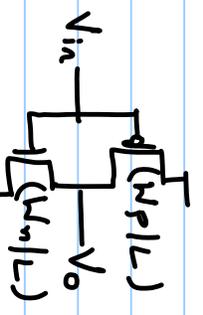

$V_{DS}$	$V_{GS}$	NMOS	$V_{in}$	PMOS	$V_{in} - V_{DD}$
			$V_o$		$V_o - V_{DD}$

$$I_{DSN} = \frac{1}{2} k_n' \frac{W_n}{L} (V_{in} - V_{tn})^2 \quad (\text{SAT})$$

$$I_{Dsp} = k_p' \frac{W_p}{L} (V_o - V_{DD}) \left( V_{in} - V_{DD} - V_{Tp} - \frac{(V_o - V_{DD})}{2} \right)$$

$$I_{DSN} = -I_{Dsp}$$

$$\Rightarrow \frac{1}{2} k_n' W_n (V_{in} - V_{tn})^2 = -k_p' \frac{W_p}{L} (V_o - V_{DD}) \left( V_{in} - V_{DD} - V_{Tp} - \frac{(V_o - V_{DD})}{2} \right)$$

Diff wrt  $V_{in}$

$$\Rightarrow k_n' W_n (V_{in} - V_{tn}) = -k_p' W_p \left[ \left( \frac{dV_o}{dV_{in}} \right) \left( V_{in} - V_{DD} - V_{Tp} - \frac{(V_o - V_{DD})}{2} \right) + (V_o - V_{DD}) \left( 1 - \frac{1}{2} \frac{dV_o}{dV_{in}} \right) \right]$$

$$\text{Let } -k_p' W_p / k_n' W_n = \alpha$$

$$\Rightarrow (V_{IL} - V_{Tn}) = \alpha \left[ (-1) (V_{IL} - V_{DD} - V_{Tp}) - \left( \frac{V_{OH} - V_{DD}}{2} \right) + (V_{OH} V_{DD}) \left( \frac{3}{2} \right) \right]$$

$$\therefore V_{IL} = \frac{V_{Tn} + \alpha (V_{DD} + V_{Tp} + 2(V_{OH} - V_{DD}))}{(1 + \alpha)}$$

For  $V_{IH}$

$P_{MOS} \rightarrow SMT$

$N_{MOS} \rightarrow LIN$

$$I_{DSP} = \frac{1}{2} k_p' \frac{W_p}{L_p} (V_{in} - V_{DD} - V_{Tp})^2$$

$$I_{DSN} = k_n' \frac{W_n}{L_n} V_0 \left[ (V_{in} - V_{Tn}) - \frac{V_0}{2} \right]$$

$$\Rightarrow I_{DSN} = -I_{DSP}$$

$$\Rightarrow k_n' \frac{W_n}{L_n} V_0 \left[ (V_{in} - V_{Tn}) - \frac{V_0}{2} \right] = -k_p' \frac{W_p}{L_p} (V_{in} - V_{DD} - V_{Tp})^2$$

$$\left( \frac{dV_0}{dV_{in}} = -1 \right) \quad \sigma \quad -k_p' \frac{W_p}{L_p} / k_n' \frac{W_n}{L_n} = \sigma$$

$$\Rightarrow \frac{dV_0}{dV_{in}} \left[ (V_{in} - V_{Tn}) - \frac{V_0}{2} \right] + V_0 \left[ \left( 1 - \frac{1}{2} \frac{dV_0}{dV_{in}} \right) \right] = \sigma (V_{in} - V_{DD} - V_{Tp})^2$$

$$V_{in} = V_{IH}$$

$$V_0 = V_{OL}$$

$$\Rightarrow (1+\gamma)V_{IH} = V_{Tn} + 2V_{OL} + r(V_{DD} + V_{TP})$$

$$\Rightarrow V_{IH} = \frac{V_{Tn} + 2V_{OL} + r(V_{DD} + V_{TP})}{1+\gamma} = \frac{V_{Tn} + r(V_{DD} + V_{TP}) + 2V_{OL}}{1+\gamma}$$


$$V_{IL} = \frac{V_{Tn} + r(V_{DD} + V_{TP}) + 2(V_{OH} - V_{DD})}{(1+\gamma)} = \frac{V_{Tn} + r(V_{DD} + V_{TP}) + 2r(V_{OH} - V_{DD})}{1+\gamma}$$

$$\Delta V_{IH} = V_{IH} - V_{IL} = \frac{2V_{OL} - 2r(V_{OH} - V_{DD})}{(1+\gamma)}$$

Let  $V_{OL} = V_{DD} - V_{OH}$

$$\Rightarrow \Delta V_{IH} = \frac{2V_{OL} + 2r(V_{OL})}{(1+\gamma)} = 2V_{OL} \leftarrow$$

## PASS TRANSISTORS

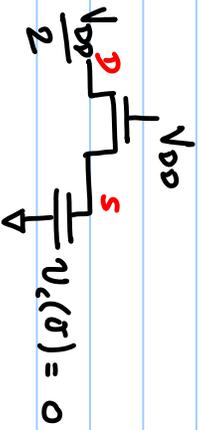


$$t \rightarrow \infty \quad \text{If } V_S(t) = V_{DD} - V_{th} \quad (\text{If } I_{qff} = \text{source TH LEAKAGE} = 0)$$

$$V_{DD} - V_S \geq V_{th}$$


$$\Rightarrow V_S \leq V_{DD} - V_{th}$$
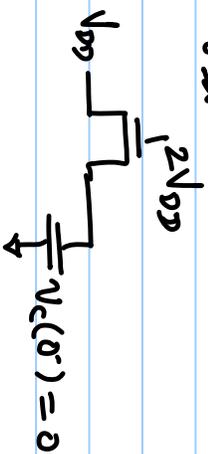
$$\Rightarrow \text{If } t \rightarrow \infty \quad V_S(t) = \frac{V_{DD}}{2}$$




$$t \rightarrow \infty \quad \text{If } V_S(t) = \min(V_G - V_T, V_D)$$

$$V_S(t) = 0$$

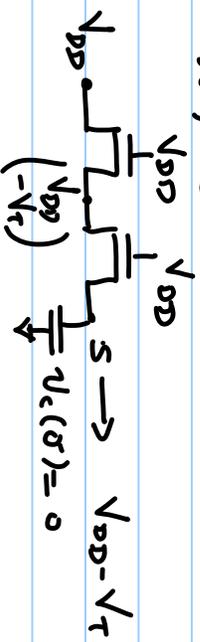

$$\text{If } V_S(t) = 0$$

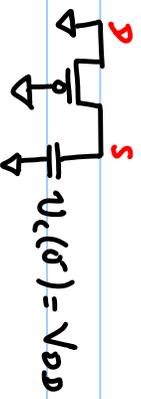

$$V_s - V_{Tp} \leq 0$$

$$-V_s - V_{Tp} \leq 0$$

$$\therefore -V_s \leq +V_{Tp}$$

$$\Rightarrow V_s \geq (V_{Tp})$$