
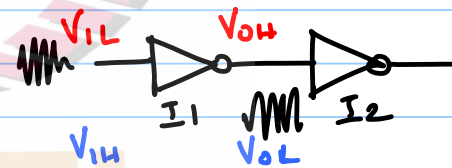


04/09/2019

EE5311

### MODULE -3 - THE INVERTER

#### NOISE MARGIN

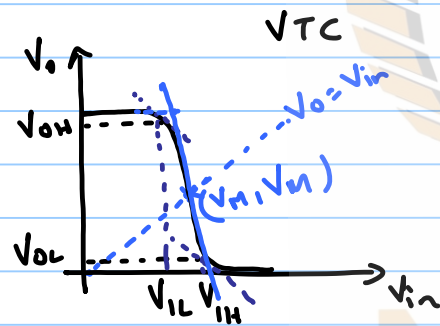



$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

NPTL

## LONG CHANNEL INVERTERS (ALL SCE = 0)

$$g = \left. \frac{dV_o}{dV_{in}} \right|_{V_{in}=V_o=V_M} \propto \frac{1}{(\lambda_n - \lambda_p)} \rightarrow \frac{1}{2\lambda_n} \quad (\lambda_p = -\lambda_n)$$

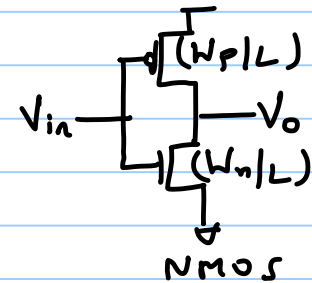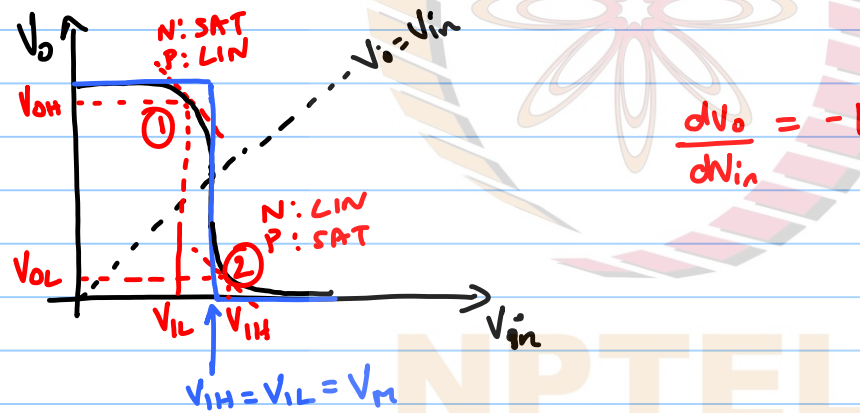

$V_{GS}$   
 $V_{DS}$

$V_{in}$   
 $V_o$

PMOS  
 $V_{in} - V_{DD}$   
 $V_o - V_{DD}$

$$I_{Dsn} = \frac{1}{2} k_n' \frac{W_n}{L} (V_{in} - V_{Tn})^2 \quad (\text{SAT})$$

$$I_{Dsp} = k_p' \frac{W_p}{L} (V_o - V_{DD}) \left( V_{in} - V_{DD} - V_{Tp} - \frac{(V_o - V_{DD})}{2} \right)$$

$$I_{Dsn} = -I_{Dsp}$$

$$\Rightarrow \frac{1}{2} k_n' W_n (V_{in} - V_{Tn})^2 = -k_p' \frac{W_p}{L} (V_o - V_{DD}) \left( V_{in} - V_{DD} - V_{Tp} - \frac{(V_o - V_{DD})}{2} \right)$$

Diff wrt  $V_{in}$

$$\Rightarrow k_n' W_n (V_{in} - V_{Tn}) = -k_p' W_p \left[ \left( \frac{dV_o}{dV_{in}} \right) \left( V_{in} - V_{DD} - V_{Tp} - \frac{(V_o - V_{DD})}{2} \right) + (V_o - V_{DD}) \left( 1 - \frac{1}{2} \frac{dV_o}{dV_{in}} \right) \right]$$

$$\text{Let } -k_p' W_p / k_n' W_n = \gamma$$

$$\Rightarrow (V_{IL} - V_{TN}) = \gamma \left[ (-1) (V_{IL} - V_{DD} - V_{TP}) - \left( \frac{V_{OH} - V_{DD}}{2} \right) + (V_{OH} - V_{DD}) \left( \frac{3}{2} \right) \right]$$

$$\therefore V_{IL} = \frac{V_{TN} + \gamma (V_{DD} + V_{TP} + 2(V_{OH} - V_{DD}))}{(1 + \gamma)}$$

NPTTEL

for  $V_{in}$

PMOS  $\rightarrow$  SAT

NMOS  $\rightarrow$  LIN

$$I_{Dsp} = \frac{1}{2} K_p' \frac{W_p}{L} (V_{in} - V_{DD} - V_{Tp})^2$$

$$I_{Dsn} = K_n' \frac{W_n}{L} V_o \left[ (V_{in} - V_{Tn}) - \frac{V_o}{2} \right]$$

$$\Rightarrow I_{Dsn} = -I_{Dsp}$$

$$\Rightarrow K_n' W_n V_o \left[ (V_{in} - V_{Tn}) - \frac{V_o}{2} \right] = -K_p' W_p (V_{in} - V_{DD} - V_{Tp})^2$$

$$\left( \frac{dV_o}{dV_{in}} = -1 \right) \quad \& \quad -K_p' W_p / K_n' W_n = \gamma$$

$$\Rightarrow \frac{dV_o}{dV_{in}} \left[ V_{in} - V_{Tn} - \frac{V_o}{2} \right] + V_o \left[ 1 - \frac{1}{2} \frac{dV_o}{dV_{in}} \right] = \gamma (V_{in} - V_{DD} - V_{Tp}) \quad \begin{matrix} V_{in} = V_{IH} \\ V_o = V_{OL} \end{matrix}$$

$$\Rightarrow (1+\gamma)V_{IH} = V_{TN} + 2V_{OL} + \gamma(V_{DD} + V_{TP})$$

$$\Rightarrow V_{IH} = \frac{V_{TN} + 2V_{OL} + \gamma(V_{DD} + V_{TP})}{1+\gamma} = \frac{V_{TN} + \gamma(V_{DD} + V_{TP}) + 2V_{OL}}{1+\gamma}$$


$$V_{IL} = \frac{V_{TN} + \gamma(V_{DD} + V_{TP} + 2(V_{OH} - V_{DD}))}{(1+\gamma)} = \frac{V_{TN} + \gamma(V_{DD} + V_{TP}) + 2\gamma(V_{OH} - V_{DD})}{1+\gamma}$$

$$\Delta V_{ILH} = V_{IH} - V_{IL} = \frac{2V_{OL} - 2\gamma(V_{OH} - V_{DD})}{(1+\gamma)}$$

$$\text{Let } V_{OL} = V_{DD} - V_{OH}$$

$$\Rightarrow \Delta V_{ILH} = \frac{2V_{OL} + 2\gamma(V_{OL})}{(1+\gamma)} = 2V_{OL} \leftarrow$$

## PASS TRANSISTORS

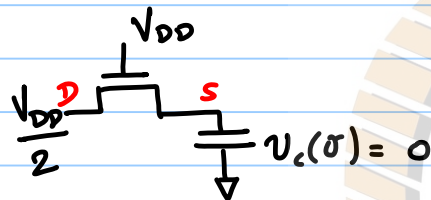


$$\text{If } V_s(t) = V_{DD} - V_{TN} \quad (I_{off} = \text{SUB TH LEAKAGE} = 0) \quad t \rightarrow \infty$$


$$V_{DD} - V_s \geq V_{TN}$$


$$\Rightarrow V_s \leq V_{DD} - V_{TN}$$
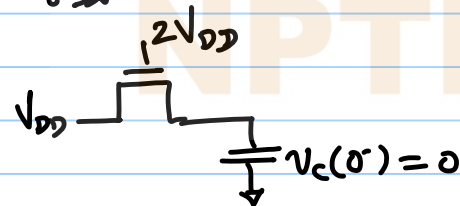
$$\Rightarrow \text{If } V_s(t) = \frac{V_{DD}}{2} \quad t \rightarrow \infty$$


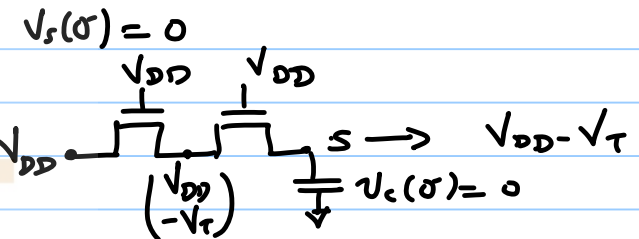
$$\text{If } V_s(t) = \min(V_G - V_T, V_D) \quad t \rightarrow \infty$$



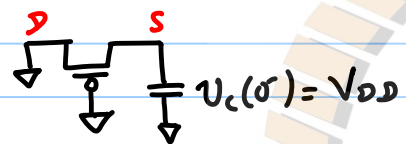

$$v_{gs} - V_{TP} \leq 0$$
$$-v_s - V_{TP} \leq 0$$

$$\therefore -v_s \leq +V_{TP}$$
$$\Rightarrow v_s \geq (V_{TP})$$

NPTTEL