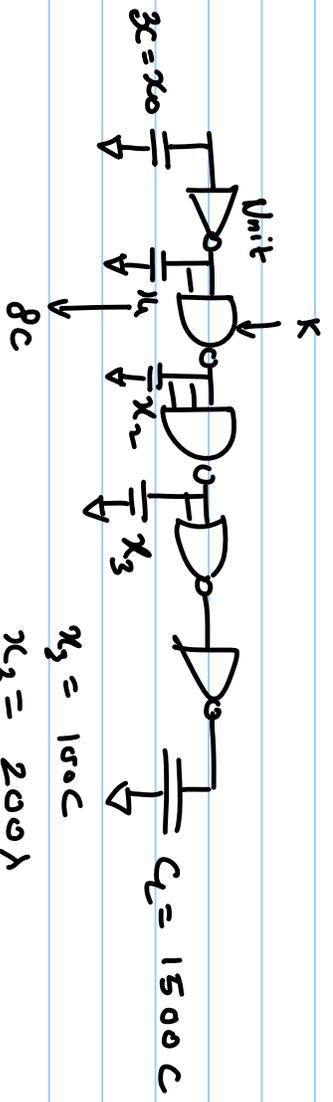



17/10/2019

EE5311

TUTORIAL-3




$SFC = 8000$
 $\therefore K = 20$

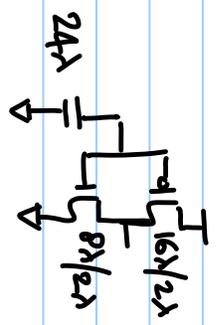


$4K\Omega = 80$
 $\therefore K = 2$

$R4 = 48\Omega$



$C_L = 2250\mu F$

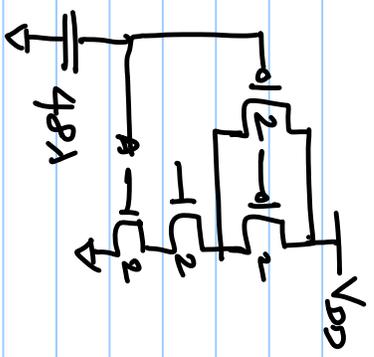

Module 4:

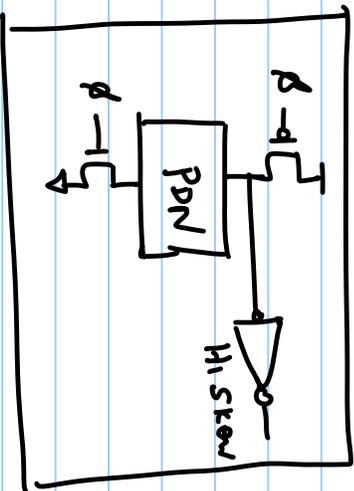


CVSL

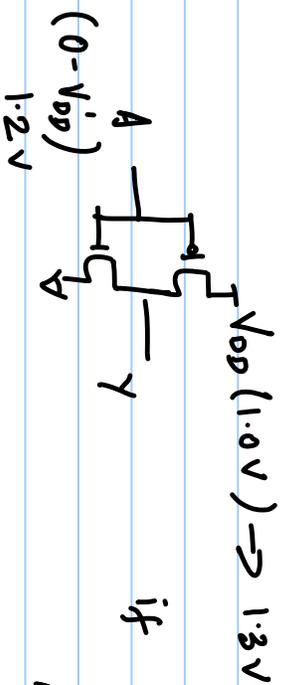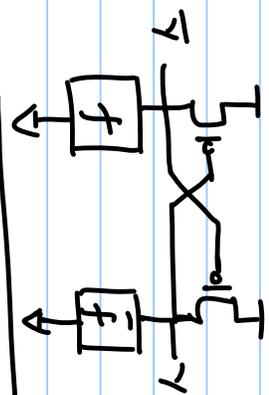

if $V_{DD} > V_{DD}$

$$A = V_{DD}' = 1.2 \text{ V} \Rightarrow V_{asp} = 1.0.2 \text{ V}$$

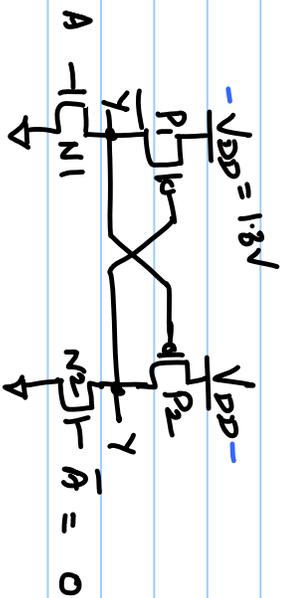
if $V_{DD} = 0.8 \text{ V}$ & $A = V_{DD}' = 0.8$
 $V_{asp} = -0.2 \text{ V}$






$A = 0.8V$

- $A = 0.8V \Rightarrow N1 \text{ is ON}$
- \Rightarrow GATE OF $P2 = \text{Low Voltage}$
- $\Rightarrow P2 \text{ TURN ON}$
- $\Rightarrow Y = V_{DD}$ ($N2 \text{ is OFF}$)
- $\Rightarrow V_{esp} \text{ OF } P1 = 0$
- $\Rightarrow P1 \text{ IS OFF}$

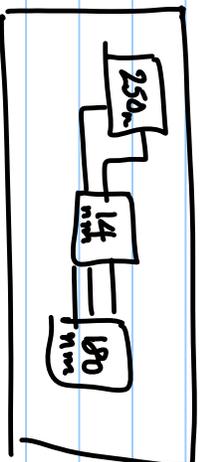\Rightarrow CYSL IS GOOD FOR LEVEL TRANSITION FROM LOW TO HIGH V_{DD} DOMAIN



$3.3V$

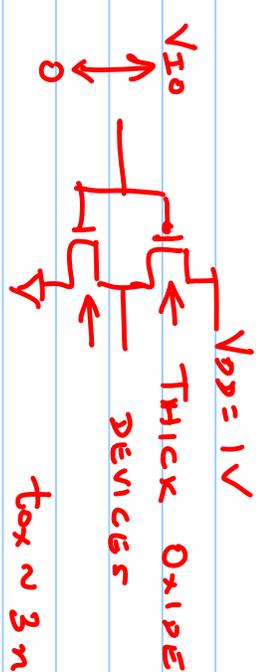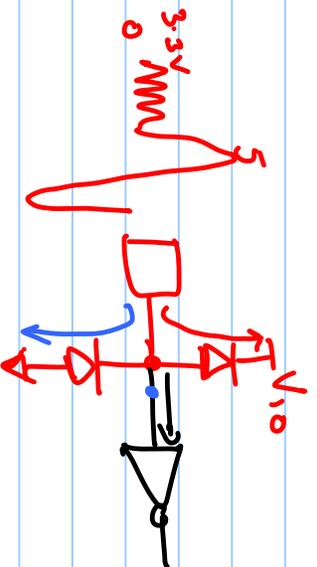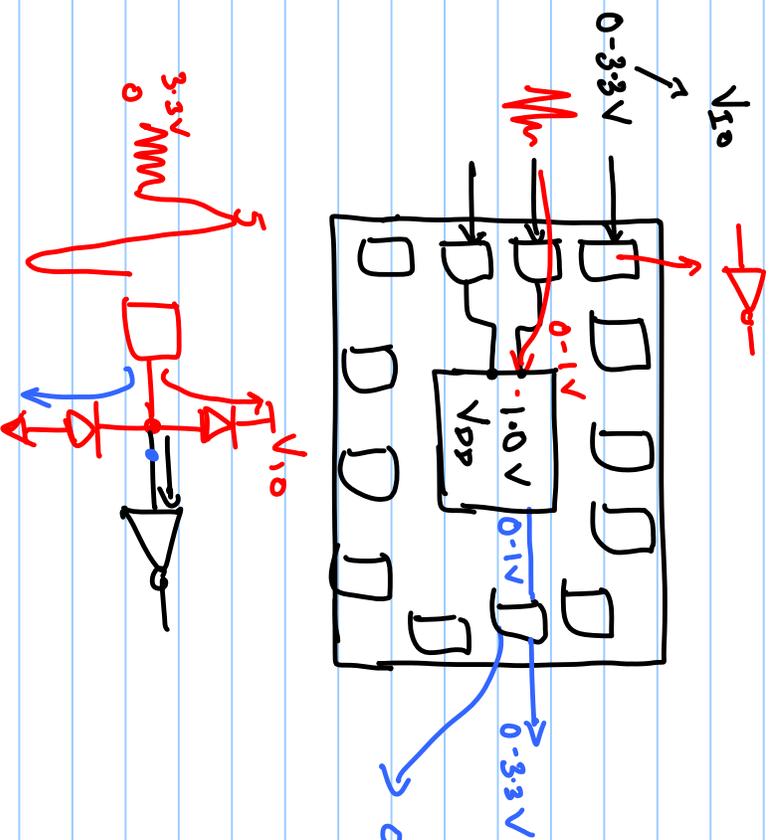

o/p PAD
 LT LIKE CURL LOGIC
 For Thin Oxide
 tox ~ 1nm
 in 14nm tech

