


23/08/2019


EE5311

MODULE - 2 - INTERCONNECTS

INTER CONNECT.

VIA/CONTACT

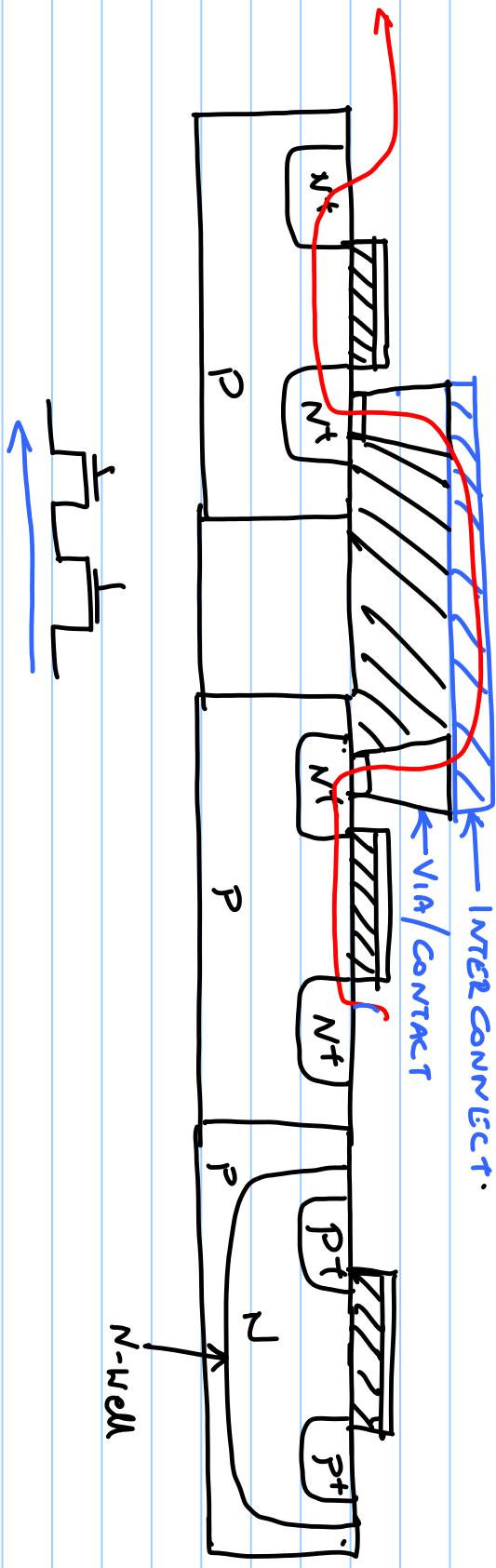


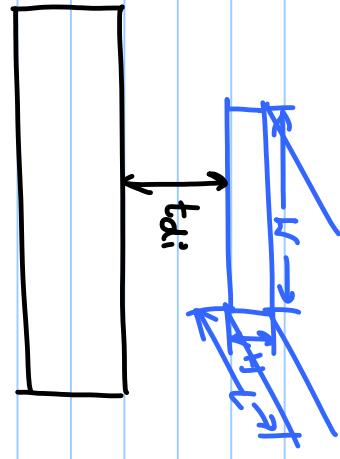


$$C = \frac{E_{ox} u L}{t_{di}} + 2\pi \frac{E_{ox} L}{\ln\left(\frac{t_{di}}{H}\right)}$$

$$= C_{wire} \cdot L$$

$$C_{wire} = \frac{E_{ox} u}{t_{di}} + \frac{2\pi E_{ox}}{\ln\left(\frac{t_{di}}{H}\right)} \quad (f_F / \text{Nm})$$
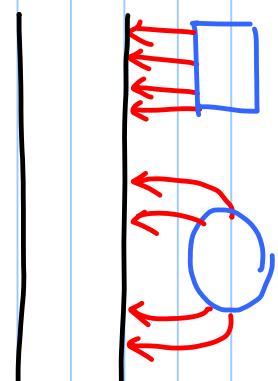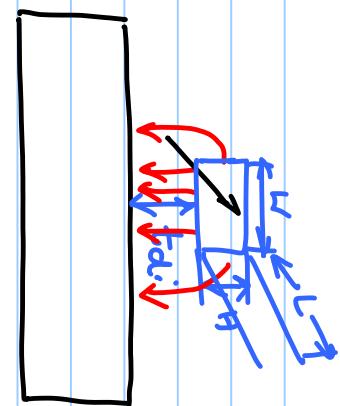
$$\Leftrightarrow \frac{1}{L} C_{wire} L$$




Resistance :

$$R = \frac{\rho L}{A} = \left( \frac{\rho}{H} \right) \frac{L}{W} = R_0 \frac{L}{W} \quad (R_0 \rightarrow \Omega/\square)$$

$$R = \tau_{\text{wire}} \cdot L$$
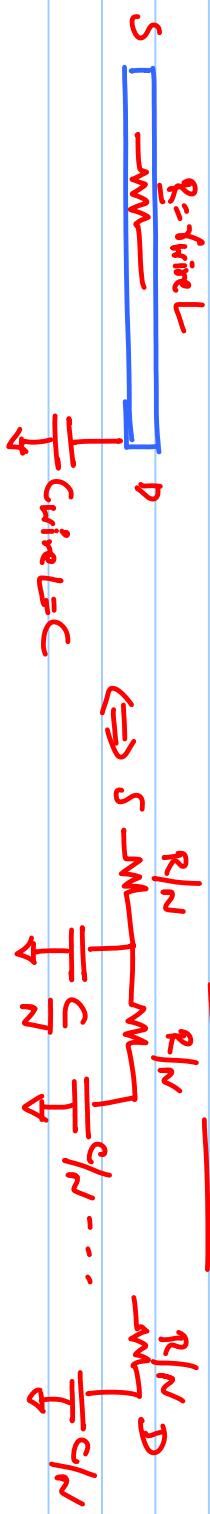
$$\tau_{\text{wire}} = \frac{R_0}{W} \quad (\Omega/\mu\text{m})$$




$$\text{ELMORE DELAY} = \frac{N(N+1)}{2} \cdot \frac{R}{N} \frac{C}{J}$$

$$\text{delay} = \lim_{N \rightarrow \infty} \frac{R \cdot C}{N^2} \frac{(N(N+1))}{2} = \frac{RC}{2}$$

$$= \frac{\text{time.Circe} \cdot L^2}{2} \quad (\text{ROUTE WITH SMALL LENGTH WIRES})$$

### LUMPED CAP MODEL

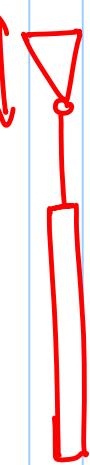

$t_{gate} > \frac{\text{time.Circe} L^2}{2} \Rightarrow$  use LUMPED C model

$$\Rightarrow L < \sqrt{\frac{2 t_{gate}}{\text{time.Circe}}}$$

