

3/10/2019

EE5311

MODULE-5 - SEQUENTIAL CIRCUITS

10 steps.



Total time = 1000 units


Pipeline


Total time = 110 units. ←

Every 6.5 Units we can feed a

block

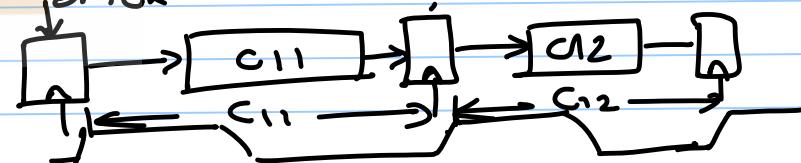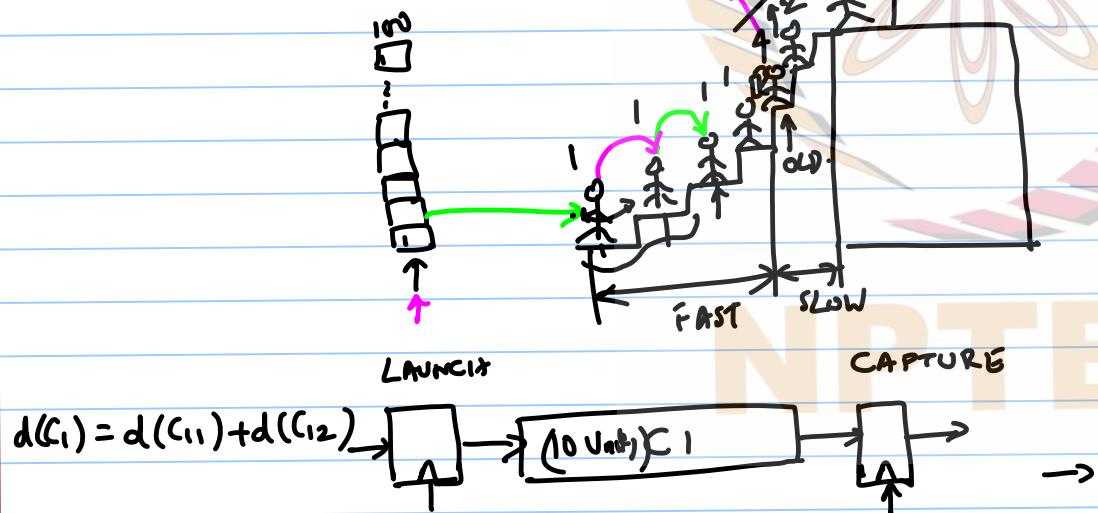

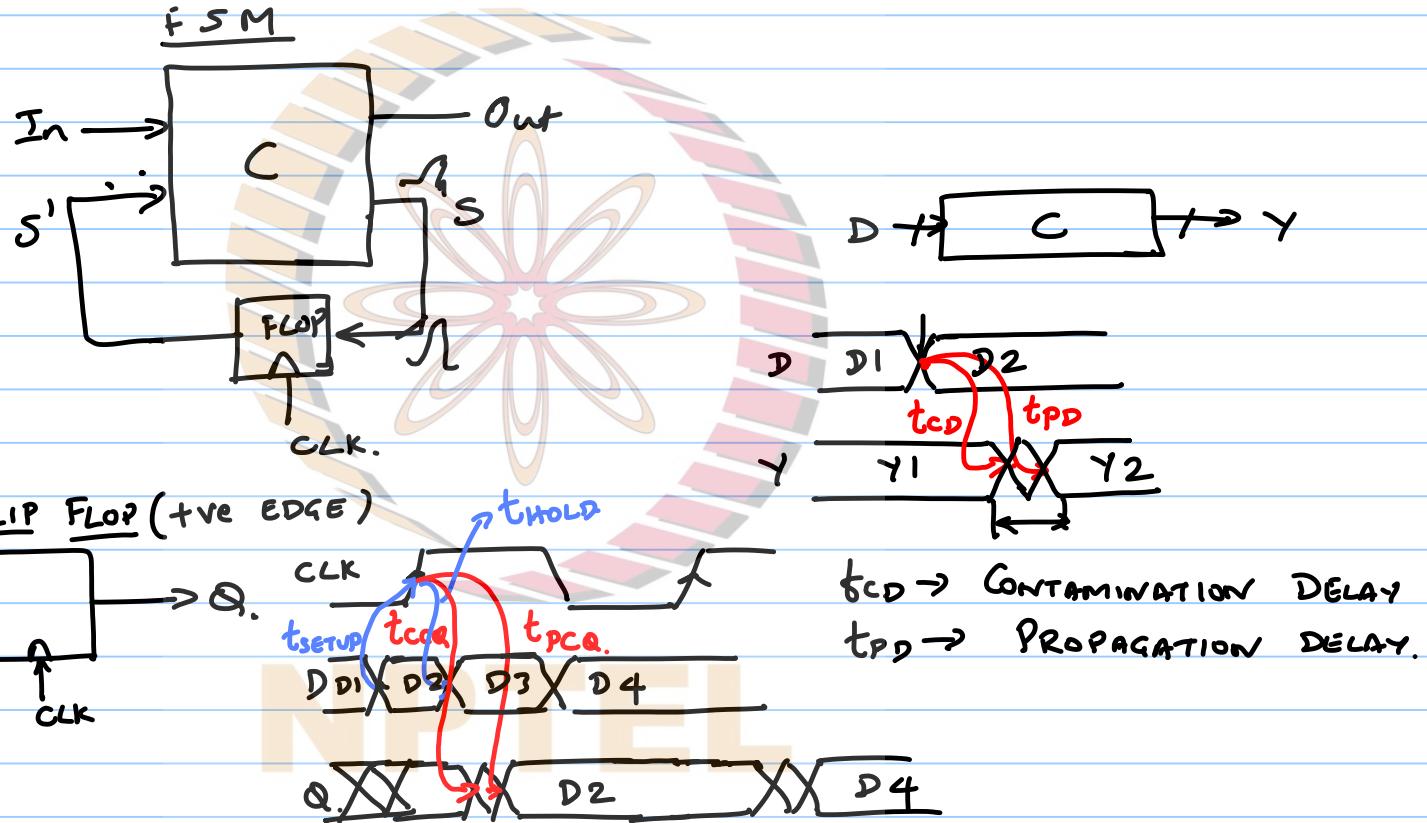

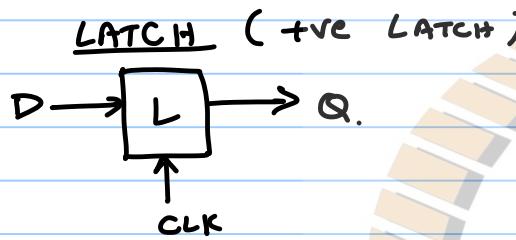

IF $CLK == 1$
 $\Rightarrow Q = D.$

IF $CLK == 0$
 HOLD $Q.$

