



IIT ROORKEE



**NPTEL ONLINE
CERTIFICATION COURSE**


Computer aided power system analysis

AC- DC Load Flow

Prof. Biswarup Das

Department of Electrical Engineering



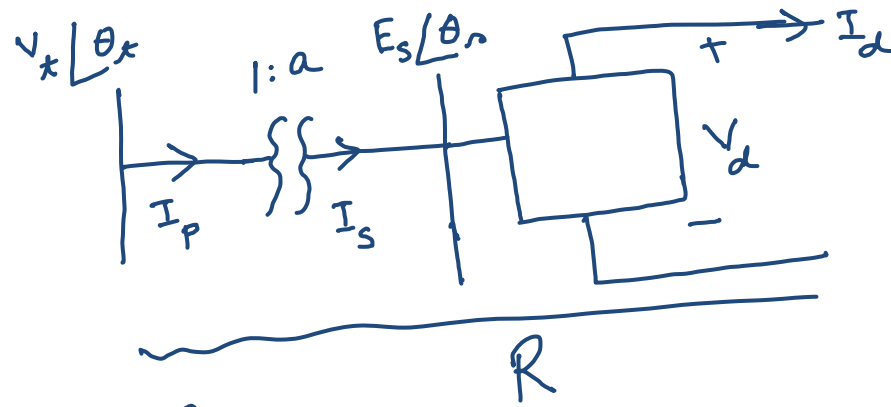

LCC-HVDC
Thyristor
based HVDC


$\overline{X}_{DC}$

Rectifier terminal
' α ' $\rightarrow$ firing angle
Inverter terminal
' γ ' $\rightarrow$ extinction angle
Power-factor at both
Rectifier and inverter.

Equations for the HVDC link.

Rectifier
Inverter
DC-link

LCC-HVDC
12-pulse

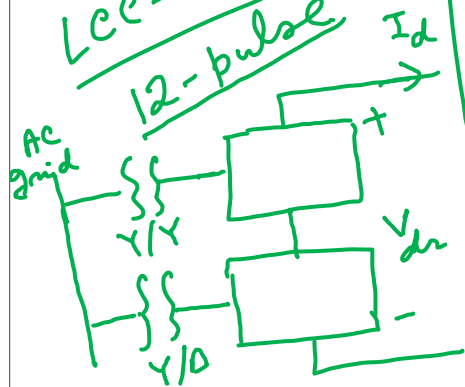

Rectifier

$$V_{dr} = \frac{3\sqrt{2}}{\pi} N_r a_r E_{tr} \cos \phi_r = V_{dor} \cos \phi_r \quad \text{--- (1)}$$

$$N_r = 2 \quad (\text{For 12-pulse converter})$$

$$V_{dr} = V_{dor} \cos \alpha - \frac{3}{\pi} X_{cr} N_r I_d \quad \text{--- (2)}$$

Inverter side

$$V_{di} = \frac{3\sqrt{2}}{\pi} N_i a_i E_{ti} \cos \phi_i = V_{doi} \cos \phi_i \quad \text{--- (3)}$$

$$V_{di} = V_{doi} \cos \gamma - \frac{3}{\pi} X_{ci} N_i I_d \quad \text{--- (4)}$$

$N_r(N_i)$ → number of 6-pulse converters connected in series at rectifier (inverter) side

$a_r(a_i)$ → transformer tap ratio at rectifier (inverter)

$E_{xr}(E_{xi})$ → AC terminal voltage at rectifier (inverter)

$X_{cr}(X_{ci})$ → Individual transformer leakage impedance at rectifier (inverter)

$\phi_r(\phi_i)$ → Power factor angle at rectifier (inverter)

HVDC link.

$$I_d = \frac{V_{dr} - V_{di}}{R_{dc}}$$

R_{dc} → DC link resistance

--(5)

At each side, the unknowns are chosen as:

$$[V_{dr} \quad I_d \quad a_r \quad \cos \alpha \quad \phi_r] \rightarrow \text{At rectifier}$$

$$[V_{di} \quad I_d \quad a_i \quad \cos \gamma \quad \phi_i] \rightarrow \text{At inverter}$$

Total unknowns

$$[V_{dr} \quad V_{di} \quad I_d \quad a_r \quad a_i \quad \cos \alpha \quad \cos \gamma \quad \phi_r \quad \phi_i] \rightarrow \text{total 9 unknown quantities.}$$



