



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Computer aided power system analysis

Fault Analysis (Contd.)


Prof. Biswarup Das
Department of Electrical Engineering



$$\begin{bmatrix} I_1^{abc} \\ I_2^{abc} \end{bmatrix} = \begin{bmatrix} Y_I & Y_{II} \\ Y_{III} & Y_{IV} \end{bmatrix} \begin{bmatrix} V_m^{abc} \\ V_n^{abc} \end{bmatrix}$$

$$\Rightarrow I_1^{abc} = Y_I V_m^{abc} + Y_{II} V_n^{abc}$$
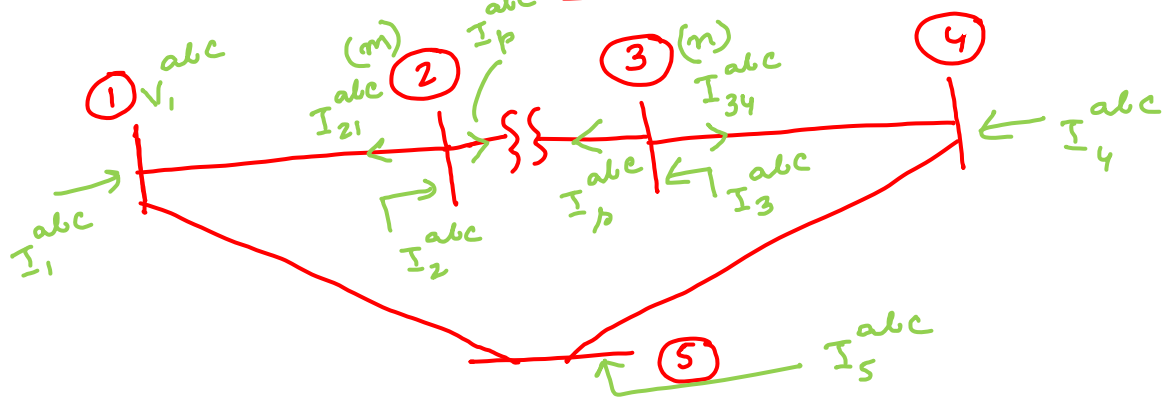
$$I_2^{abc} = Y_{III} V_m^{abc} + Y_{IV} V_n^{abc}$$



Line-models

I_{mn}^{abc}

$I_{mn,sh}^{abc}$

m	n
1	2
3	4
1	5
4	5



Bus-1

$$I_1^{abc} = y_{11}^{abc} V_1^{abc} - y_{12}^{abc} V_2^{abc} - y_{15}^{abc} V_5^{abc} \dots \textcircled{1}$$

$$y_{11}^{abc} = y_{12}^{abc} + y_{12, sh}^{abc} + y_{15}^{abc} + y_{15, sh}^{abc}$$

Transformer model

$$\begin{bmatrix} I_p^{abc} \\ I_s^{abc} \end{bmatrix} = \begin{bmatrix} Y_I & Y_{II} \\ Y_{III} & Y_{IV} \end{bmatrix} \begin{bmatrix} V_2^{abc} \\ V_3^{abc} \end{bmatrix}$$

$\Rightarrow$

$$\left. \begin{aligned} I_p^{abc} &= Y_I V_2^{abc} + Y_{II} V_3^{abc} \\ I_s^{abc} &= Y_{III} V_2^{abc} + Y_{IV} V_3^{abc} \end{aligned} \right\}$$

Bus-2

$$I_2^{abc} = I_p^{abc} + I_{21}^{abc}$$

$$= Y_I V_2^{abc} + Y_{II} V_3^{abc} + y_{12}^{abc} (V_2^{abc} - V_1^{abc}) +$$

$$\Rightarrow I_2^{abc} = -y_{12}^{abc} V_1^{abc} + (Y_I + y_{12}^{abc}) V_2^{abc} + Y_{II} V_3^{abc} \dots \textcircled{2}$$

$\xrightarrow{y_{12, sh}^{abc}}$



Bus-3

$$\begin{aligned}
 I_3^{abc} &= I_2^{abc} + I_{34}^{abc} \\
 &= Y_{III} V_2^{abc} + Y_{IV} V_3^{abc} + y_{34}^{abc} (V_3^{abc} - V_4^{abc}) + y_{34,sh}^{abc} V_3^{abc} \\
 &= Y_{III} V_2^{abc} + \left(Y_{IV} + y_{34}^{abc} + y_{34,sh}^{abc} \right) V_3^{abc} - y_{34}^{abc} V_4^{abc} \dots \dots \textcircled{3}
 \end{aligned}$$

Bus-4

$$\begin{aligned}
 I_4^{abc} &= -y_{34}^{abc} V_3^{abc} + y_{44}^{abc} V_4^{abc} - y_{45}^{abc} V_5^{abc} \dots \dots \textcircled{4} \\
 y_{44}^{abc} &= y_{34}^{abc} + y_{34,sh}^{abc} + y_{45,sh}^{abc} + y_{45}^{abc}
 \end{aligned}$$

Bus-5

$$\begin{aligned}
 I_5^{abc} &= -y_{15}^{abc} V_1^{abc} - y_{45}^{abc} V_4^{abc} + y_{55}^{abc} V_5^{abc} \dots \textcircled{5} \\
 y_{55}^{abc} &= y_{15}^{abc} + y_{15,sh}^{abc} + y_{45}^{abc} + y_{45,sh}^{abc}
 \end{aligned}$$




In matrix form

$$\begin{bmatrix} I_1^{abc} \\ I_2^{abc} \\ I_3^{abc} \\ I_4^{abc} \\ I_5^{abc} \end{bmatrix} = \begin{bmatrix} y_{11}^{abc} & -y_{12}^{abc} & 0 & 0 & -y_{15}^{abc} \\ -y_{12}^{abc} & Y_I + y_{12}^{abc} + y_{12,sh}^{abc} & Y_{II} & 0 & 0 \\ 0 & Y_{III} & Y_{IV} + y_{34}^{abc} + y_{34,sh}^{abc} & -y_{34}^{abc} & 0 \\ 0 & 0 & -y_{34}^{abc} & y_{44}^{abc} & -y_{45}^{abc} \\ -y_{15}^{abc} & 0 & 0 & -y_{45}^{abc} & y_{55}^{abc} \end{bmatrix} \begin{bmatrix} V_1^{abc} \\ V_2^{abc} \\ V_3^{abc} \\ V_4^{abc} \\ V_5^{abc} \end{bmatrix} \rightarrow (15 \times 1)$$

$\downarrow (15 \times 1)$
 $\downarrow (15 \times 15)$



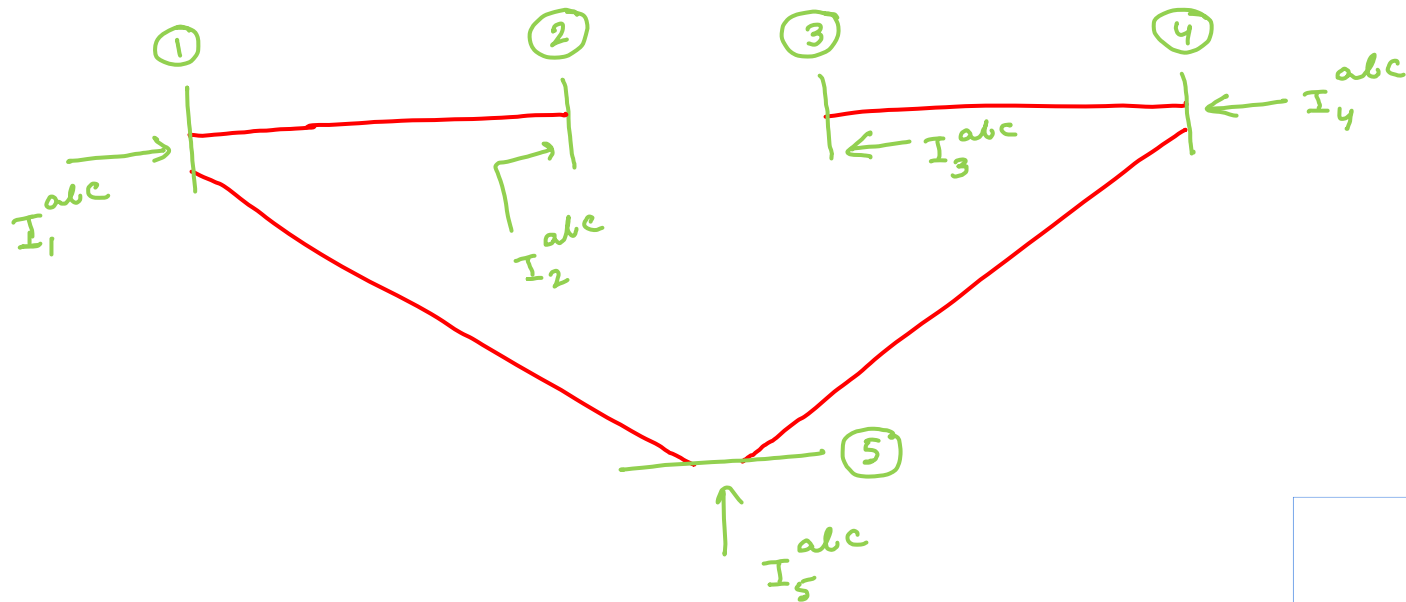Reconsider the system by removing the transformer



Write down the Y_{BUS} matrix of this reduced system.

