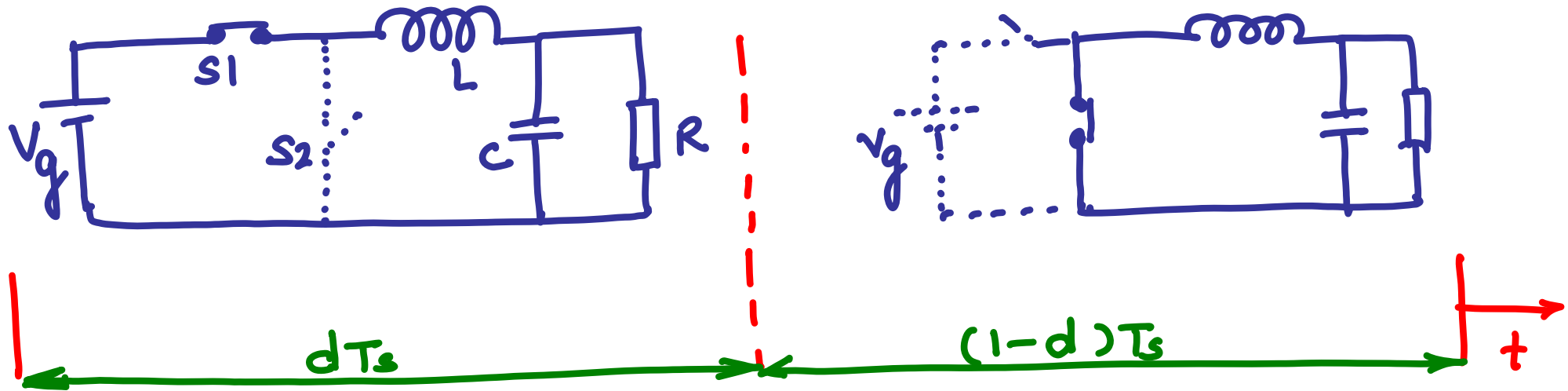


# Circuit Averaging Method





$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_C \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} [v_g] \quad T_s$$

$$v_o = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \end{bmatrix} [v_g]$$

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_C \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} [v_g]$$
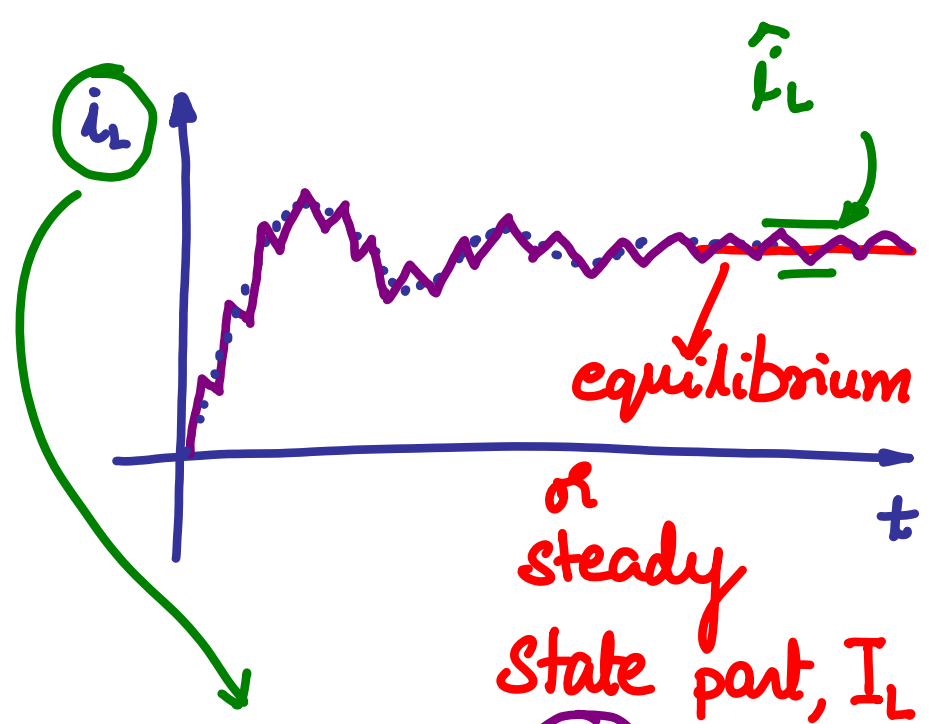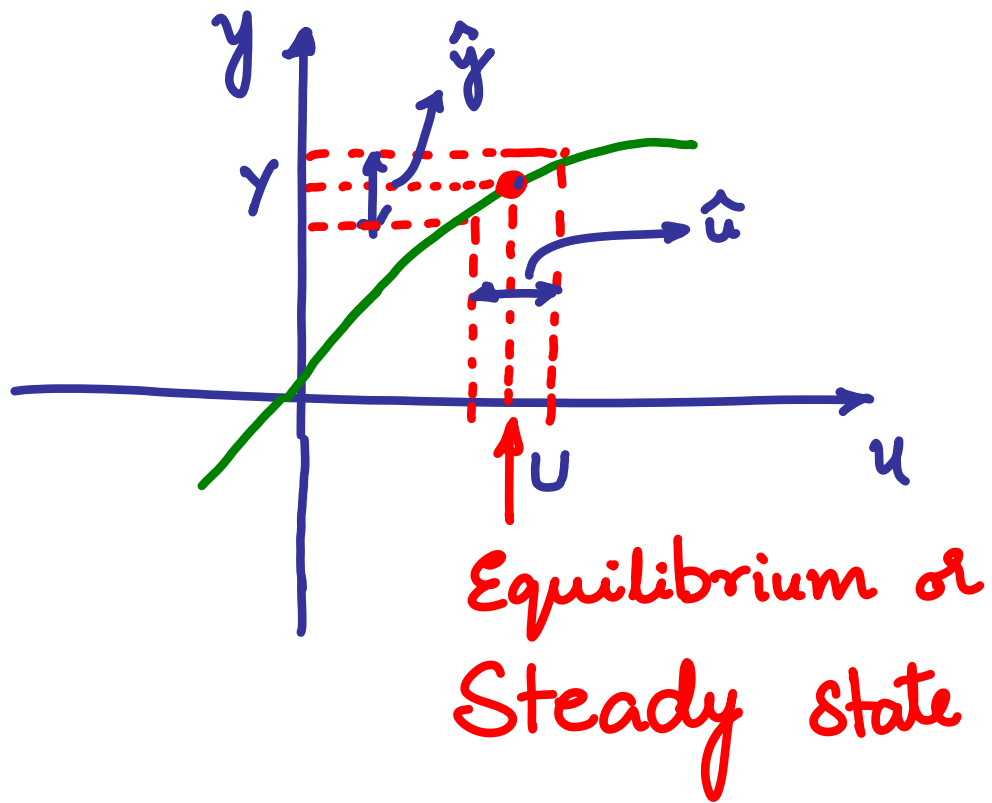
$$v_o = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \end{bmatrix} v_g$$



$$\hat{i}_L = I_L + \hat{i}_L$$

large signal      steady state      small signal

$$\begin{array}{lcl}
 u & = & U + \hat{u} \\
 \textcircled{d} & = & D + \hat{d} \\
 x & = & X + \hat{x} \\
 y & = & Y + \hat{y} \\
 \text{---} & & \text{---}
 \end{array}$$

$i_L$   
 $v_c$

$\diagup$   
 $\diagdown$

wherein  $\frac{\hat{u}}{U} \ll 1$

$$\frac{\hat{d}}{D} \ll 1$$

$$\frac{\hat{x}}{X} \ll 1$$

$$\frac{\hat{y}}{Y} \ll 1$$

$$\dot{x} = \underline{A}_1 x + \underline{B}_1 u$$

$$y = \underline{C}_1 x + \underline{D}_1 u$$

$dT_s$


large  
signal

$$\dot{x} = \underline{A}_2 x + \underline{B}_2 u$$

$$y = \underline{C}_2 x + \underline{D}_2 u$$

$(1-d)T_s$

large  
signal  
model

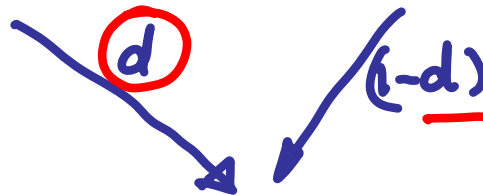

$$\dot{x} = A x + B u$$

$$y = C x + D u$$

Averaged  
large signal  
model

$$\begin{aligned} \underline{\hat{x}} &= \underline{A} \underline{x} + \underline{B} \underline{u} \\ \underline{y} &= \underline{C} \underline{x} + \underline{D} \underline{u} \end{aligned} \quad \left. \vphantom{\begin{aligned} \underline{\hat{x}} &= \underline{A} \underline{x} + \underline{B} \underline{u} \\ \underline{y} &= \underline{C} \underline{x} + \underline{D} \underline{u} \end{aligned}} \right\} \text{AVERAGED} \\ &\quad \text{LARGE SIGNAL} \\ &\quad \text{MODEL}$$

$$\rightarrow \underline{A} = \underline{A}_1 \cdot \underline{d} + \underline{A}_2 \cdot (1 - \underline{d})$$

$$\rightarrow \underline{B} = \underline{B}_1 \cdot \underline{d} + \underline{B}_2 \cdot (1 - \underline{d})$$

$$\underline{C} = \underline{C}_1 \cdot \underline{d} + \underline{C}_2 \cdot (1 - \underline{d})$$

$$\underline{D} = \underline{D}_1 \cdot \underline{d} + \underline{D}_2 \cdot (1 - \underline{d})$$

$$\dot{\underline{x}} = \underline{A} \underline{x} + \underline{B} \underline{u}$$

$$\underline{x} = \underline{X} + \hat{\underline{x}}$$

$$\underline{u} = \underline{U} + \hat{\underline{u}}$$

$$(\underline{X} + \hat{\underline{x}}) = \underline{A} \cdot (\underline{X} + \hat{\underline{x}}) + \underline{B} \cdot (\underline{U} + \hat{\underline{u}})$$

$$\underbrace{(\underline{X} + \hat{\underline{x}})}_{\substack{\downarrow \\ 0}} = \left[ \underbrace{A_1 d}_{(D+\hat{d})} + \underbrace{A_2 (1-d)}_{(1-D-\hat{d})} \right] \cdot (\underline{X} + \hat{\underline{x}}) + \left[ \underbrace{B_1 d}_{(D+\hat{d})} + \underbrace{B_2 (1-d)}_{(1-D-\hat{d})} \right] (\underline{U} + \hat{\underline{u}})$$

$$\underline{A} \underline{X} + \underline{B} \underline{U} = 0$$

①

$$X + \hat{x} \quad \frac{\hat{x}}{X} \ll 1$$

$$\underline{(\hat{x} \cdot \hat{d}) \Rightarrow \text{neglect}}$$

②

$$X \quad \frac{dX}{dt} = 0$$

$$\underline{\dot{X} = AX + BU = 0}$$

$$\dot{\hat{x}} = \underbrace{A_1 \cdot D + A_2(1-D)}_{\text{circled}} \hat{x} + \underbrace{B_1 \cdot D + B_2(1-D)}_{\text{circled}} \hat{u} + \underbrace{[(A_1 - A_2)X + (B_1 - B_2)U]}_{\text{wavy red line}} \hat{d}$$

$$y = Cx + Du$$

$$y + \hat{y} = [C_1 d + C_2(1-d)](X + \hat{x}) + (D_1 d + D_2(1-d)) \cdot (u + \hat{u})$$

$$\hat{y} = C \hat{x} + D \hat{u} + [(C_1 - C_2)X + (D_1 - D_2)U] \hat{d}$$



# Averaged Model of Buck converter


$$A = A_1 D + A_2 (1-D)$$

$$= \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \cdot D + \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} (1-D)$$

$$= \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix}$$

$$B = B_1 \cdot D + B_2 (1 - D)$$

$$= \begin{bmatrix} 1 \\ \frac{1}{L} \\ 0 \end{bmatrix} \cdot D + \begin{bmatrix} 0 \\ 0 \end{bmatrix} (1 - D)$$

$$= \begin{bmatrix} \frac{d}{L} \\ 0 \end{bmatrix} = \begin{bmatrix} \frac{D}{L} \\ 0 \end{bmatrix}$$


$$C = \begin{bmatrix} 0 & 1 \end{bmatrix}$$

$$D = \begin{bmatrix} 0 \end{bmatrix}$$

$$\begin{bmatrix} \dot{\hat{i}_L} \\ \hat{v}_C \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} \hat{i}_L \\ \hat{v}_C \end{bmatrix} + \underbrace{\begin{bmatrix} \frac{D}{L} \\ 0 \end{bmatrix}}_{\hat{v}_g} + \begin{bmatrix} \frac{D}{L} \cdot v_g \\ 0 \end{bmatrix} \hat{d}$$

$$\begin{bmatrix} \dot{\hat{i}_L} \\ \hat{v}_C \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} \hat{i}_L \\ \hat{v}_C \end{bmatrix} + \begin{bmatrix} \frac{D}{L} & \frac{Dv_g}{L} \\ 0 & 0 \end{bmatrix} \begin{bmatrix} \hat{v}_g \\ \hat{d} \end{bmatrix}$$

SMALL SIGNAL MODEL

$$\hat{y} = \mathbb{I} \hat{x} + \mathbb{D} \hat{u} +$$

$$\downarrow$$

$$0$$


$$= \mathbb{I} \hat{x}$$


$$= \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} \hat{i}_L \\ \hat{v}_C \end{bmatrix}$$

# Practice


1. Large signal model for each mode of switch operation.

2. Averaged large signal model.

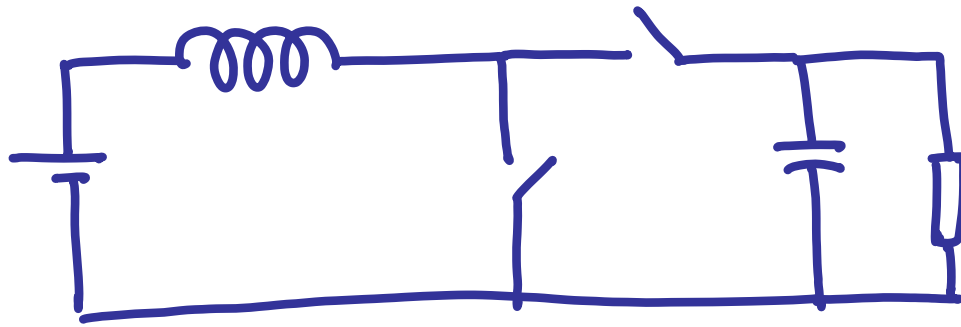3.  $AX + BU = 0$       Subtract the  
Steady the portion of  
Simplify  
Small  Signal Model



Boost

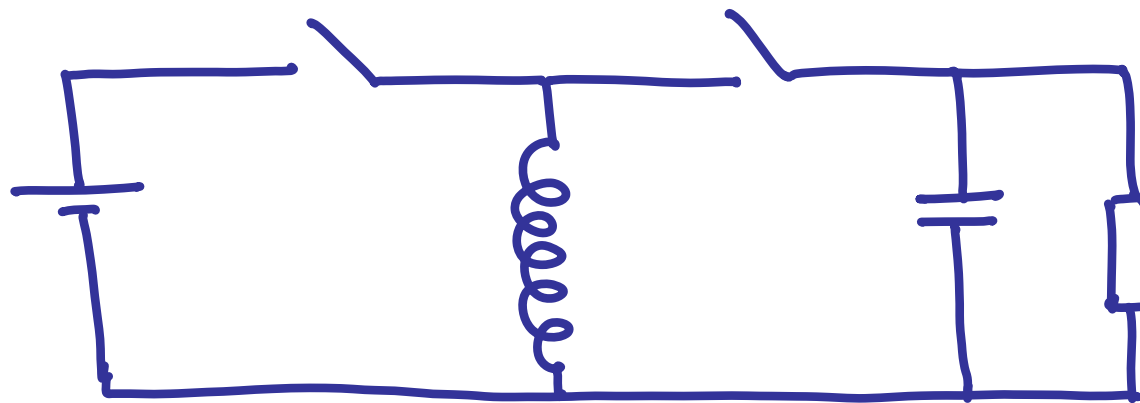

Buck-Boost converter