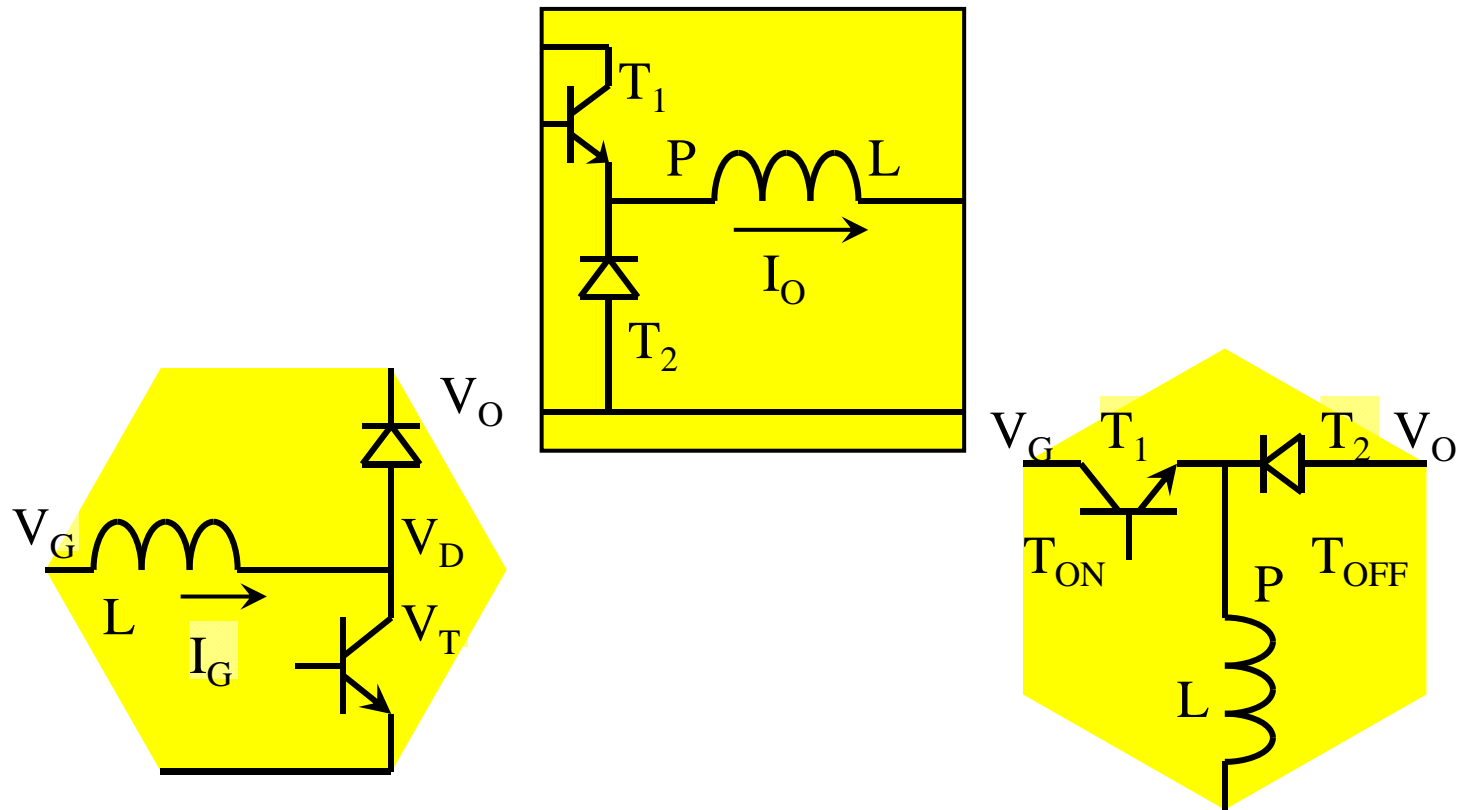


Switched Mode Power Conversion


Converters in Canonical Form



The SPDT Supports Unidirectional Current

Switched Mode Power Conversion



Operating Modes – CCM and DCM

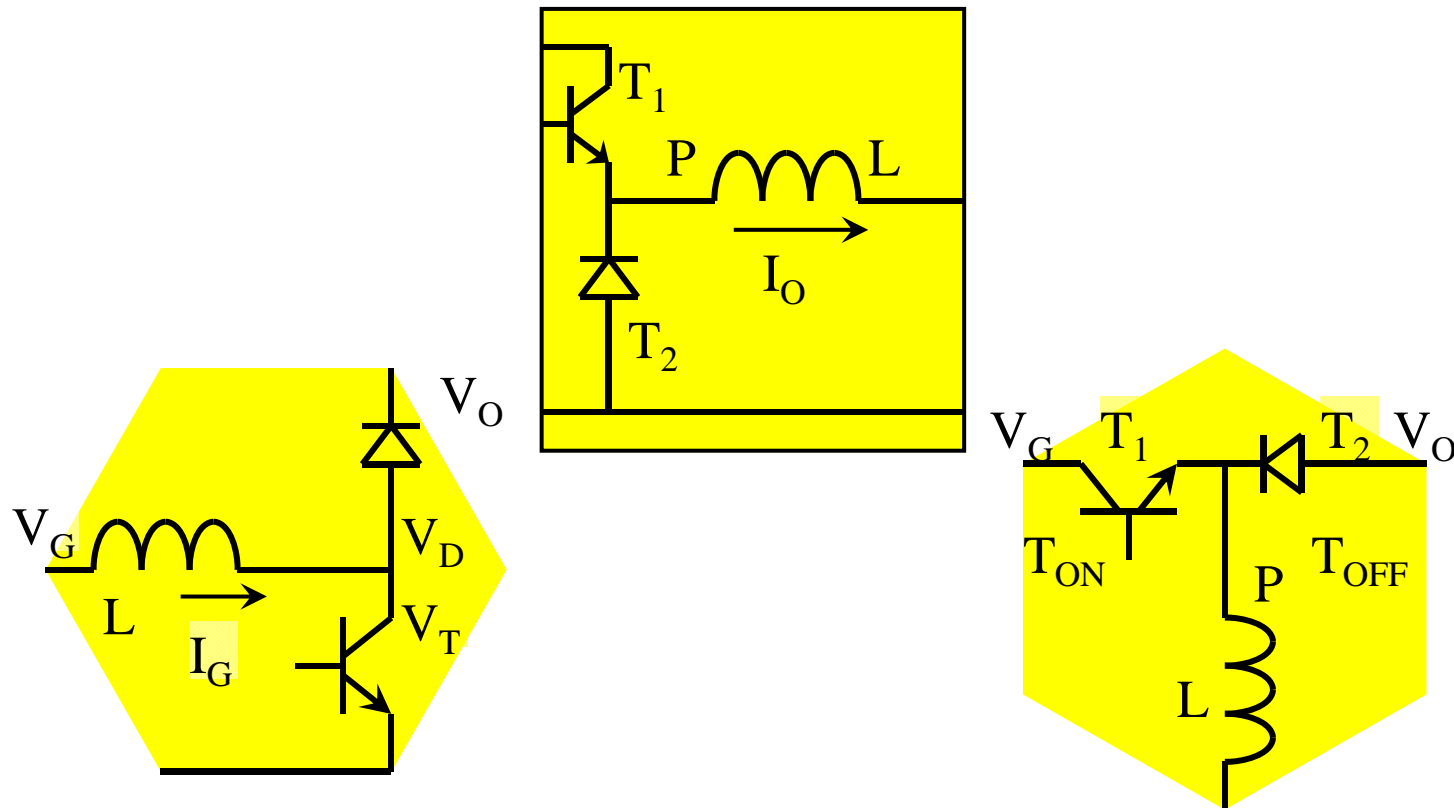

Inductor Current Cannot Reverse Direction

Switched Mode Power Conversion


Buck Converter – Inductor Current

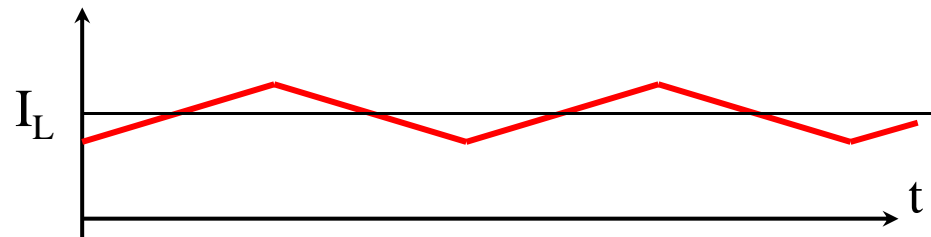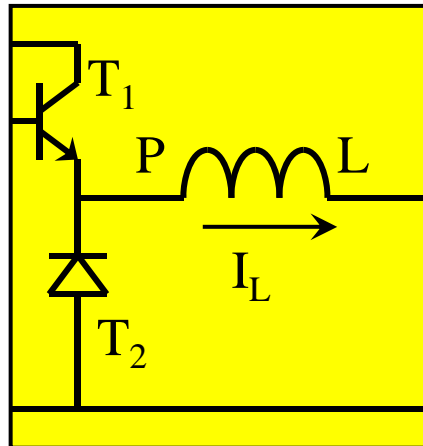

Inductor Current is Positive and Continuous

Switched Mode Power Conversion



Buck Converter – Inductor Current

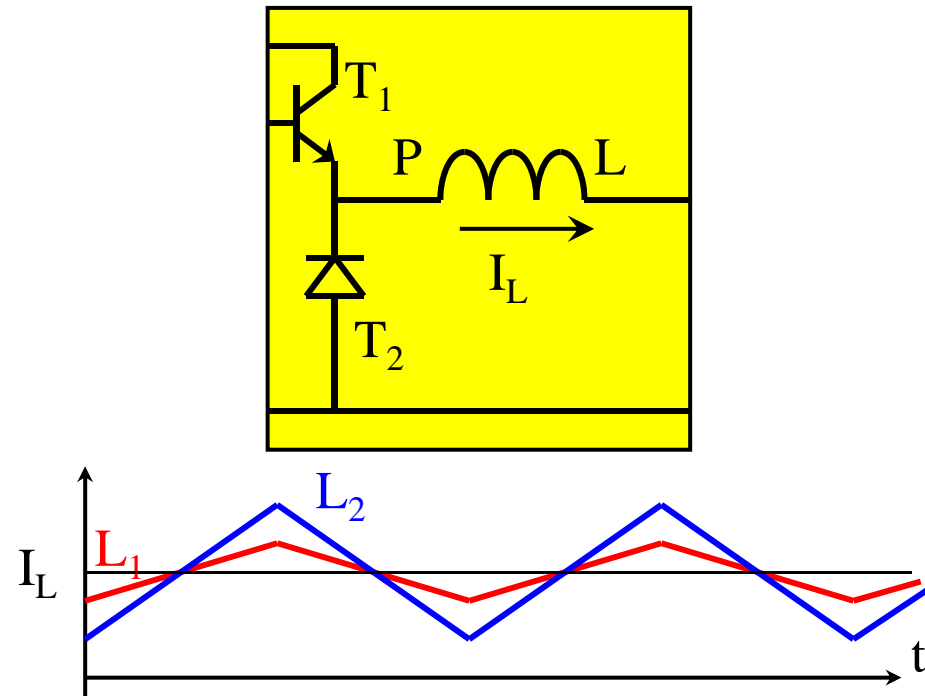

Inductor $L_2 < L_1$

Switched Mode Power Conversion


Buck Converter – Inductor Current

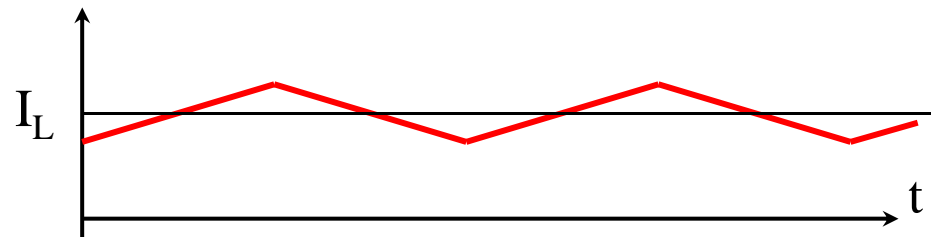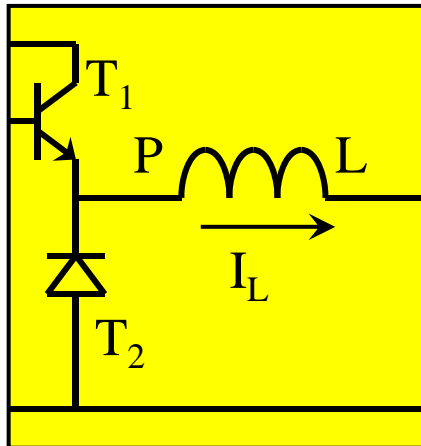

Inductor Current is Positive and Continuous

Switched Mode Power Conversion



Buck Converter – Inductor Current

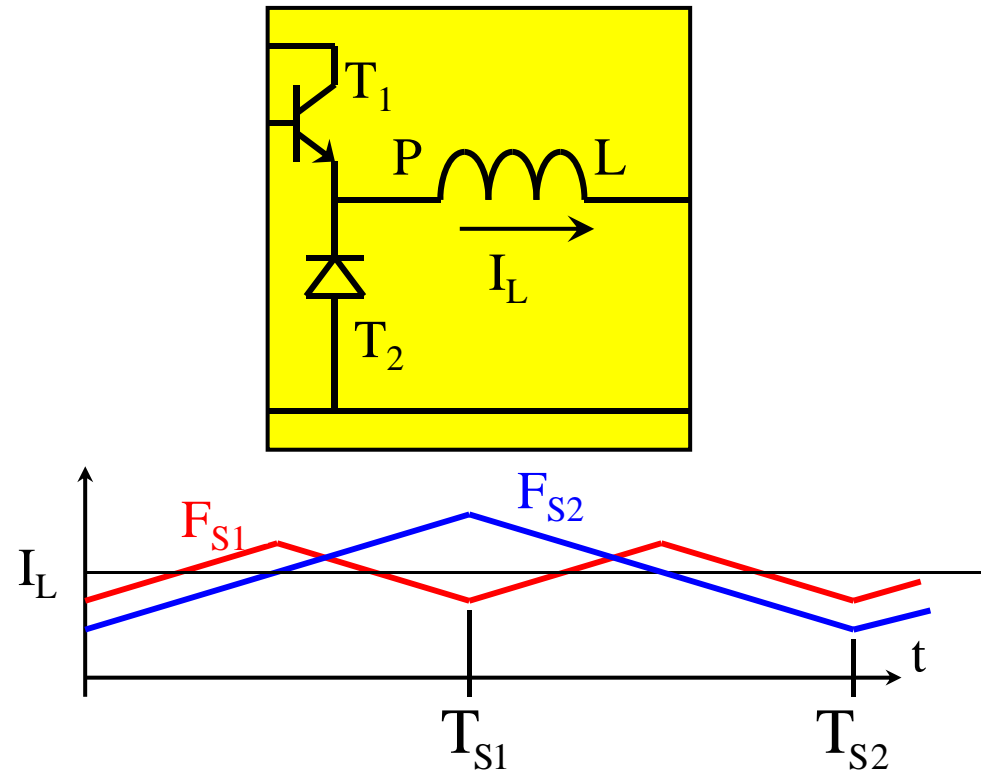

Frequency $F_{S2} < F_{S1}$; $T_{S1} < T_{S2}$

Switched Mode Power Conversion



Buck Converter – Inductor Current

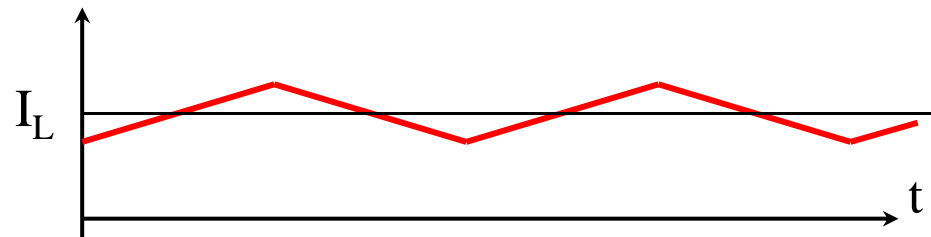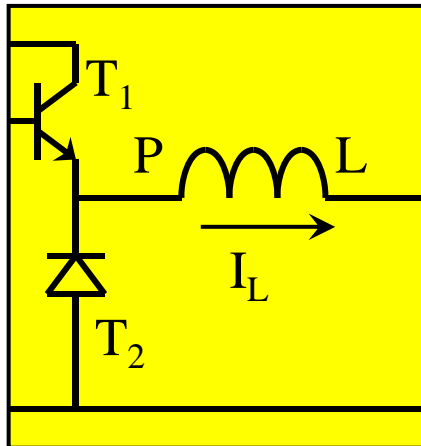

Inductor Current is Positive and Continuous

Switched Mode Power Conversion


Buck Converter – Inductor Current

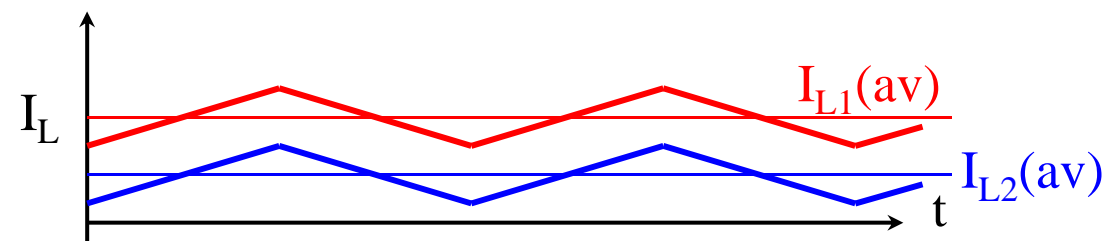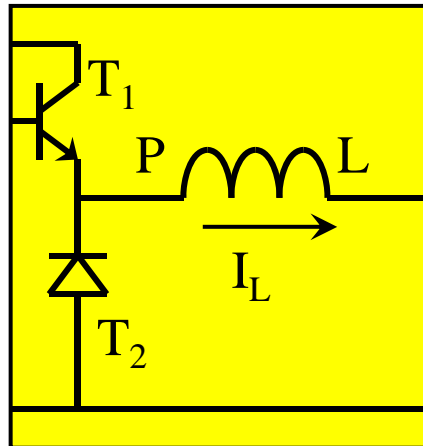

Load Current $I_{L1}(av) > I_{L2}(av)$

Switched Mode Power Conversion



Buck Converter – Inductor Current

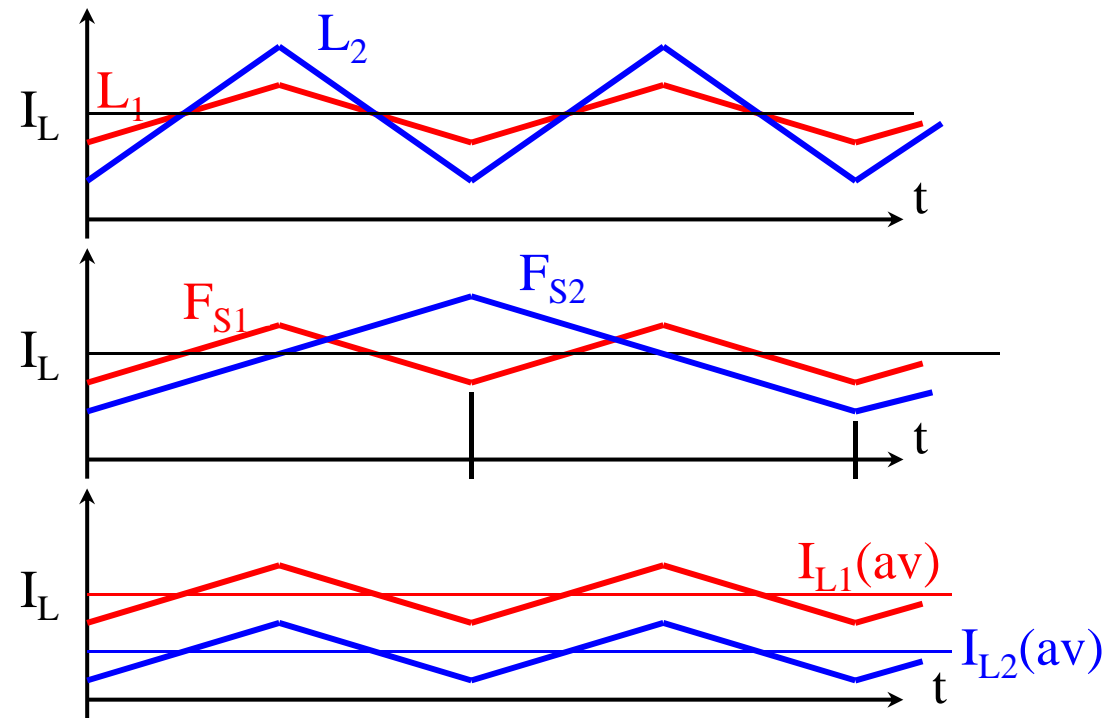

L, T_s, R

Switched Mode Power Conversion



Buck Converter – DCM

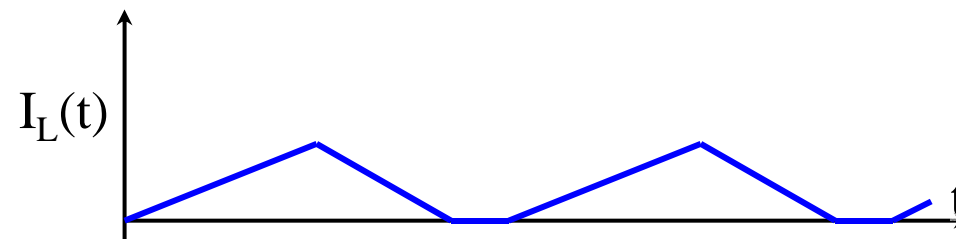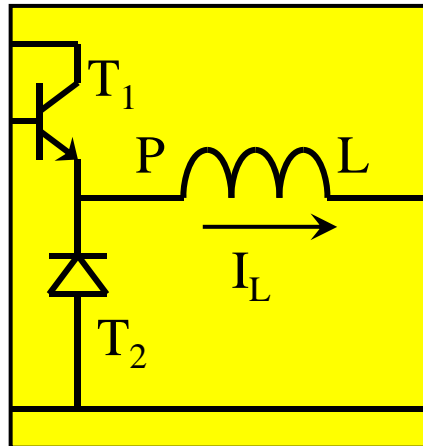

Third State: Transistor & Diode Both are OFF

Switched Mode Power Conversion



Buck Converter – DCM

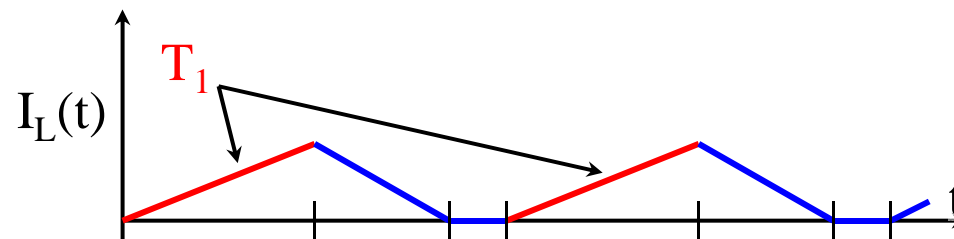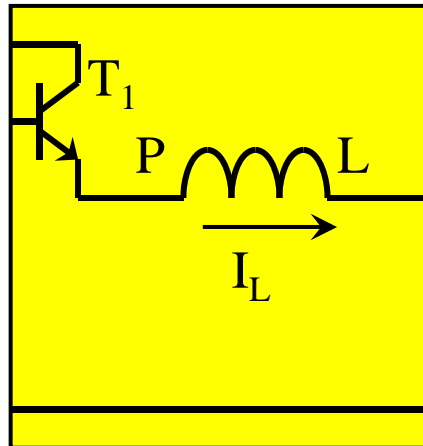

T_1 Transistor ON Time

Switched Mode Power Conversion


Buck Converter – DCM

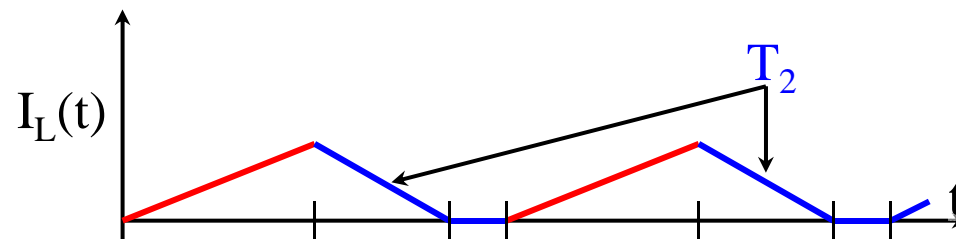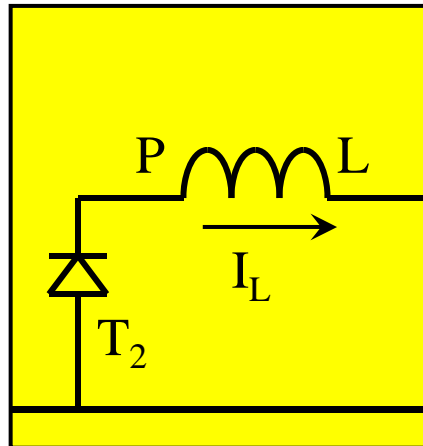

T_2 Diode ON Time

Switched Mode Power Conversion


Buck Converter – DCM

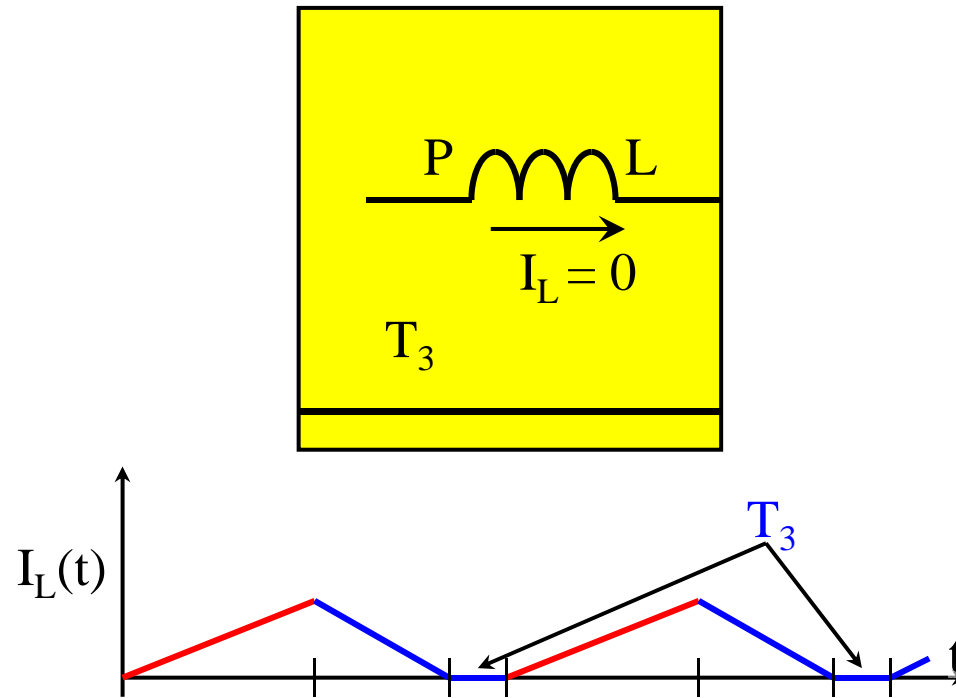

T_3 Transistor & Diode are Both OFF

Switched Mode Power Conversion


Buck Converter – DCM Conversion Ratio

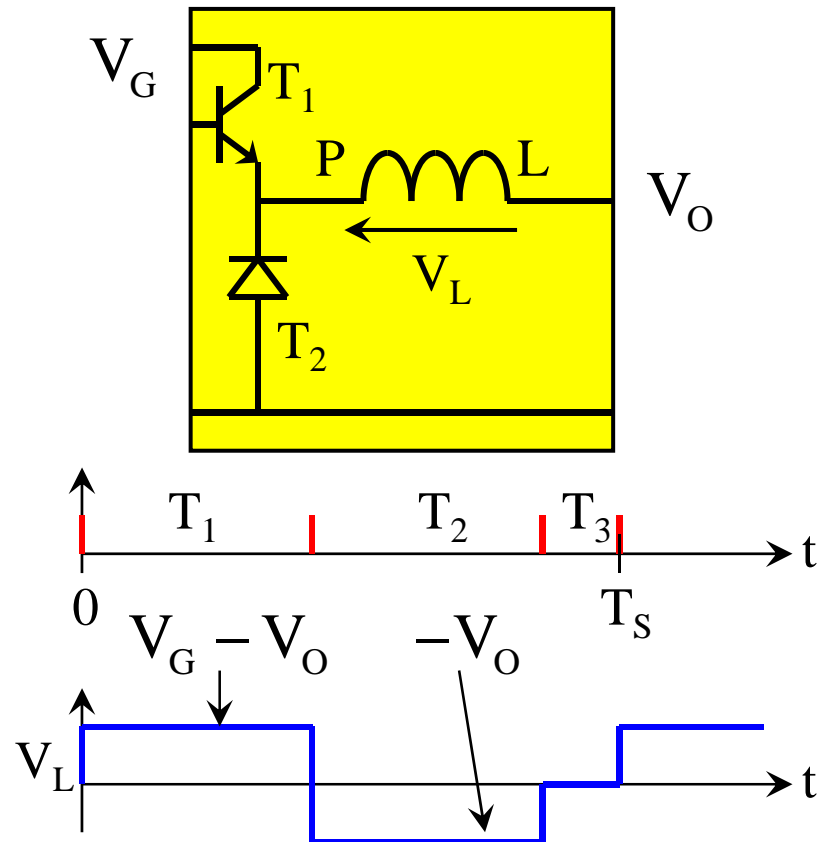

Inductor Volt-Sec Balance

Switched Mode Power Conversion

Buck Converter – DCM Conversion Ratio

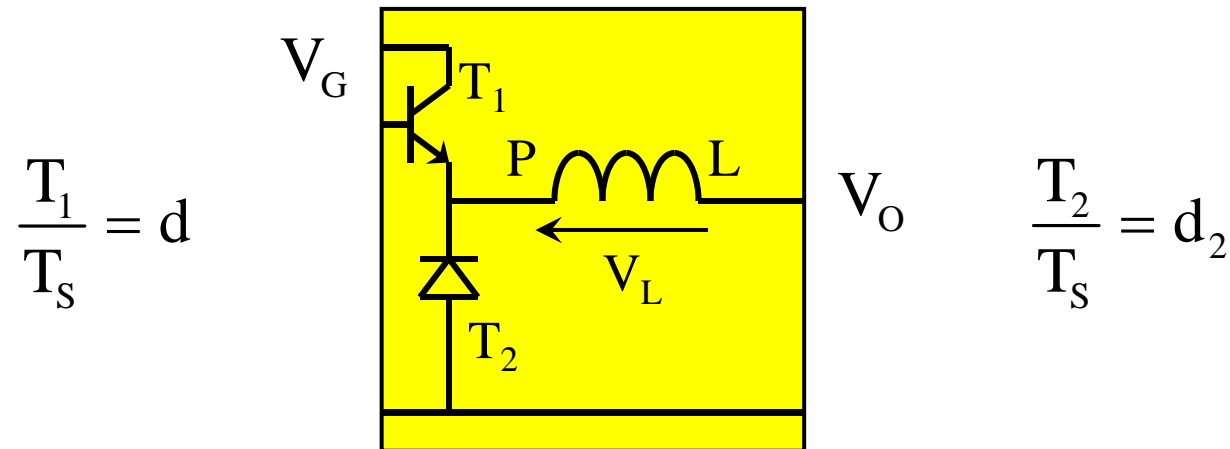


$$(V_G - V_O)T_1 - V_O T_2 = 0 \qquad dV_G = (d + d_2)V_O$$

$$\frac{V_O}{V_G} = M = \frac{d}{d + d_2}$$

Voltage Conversion Ratio

Switched Mode Power Conversion


Buck Converter – DCM Conversion Ratio

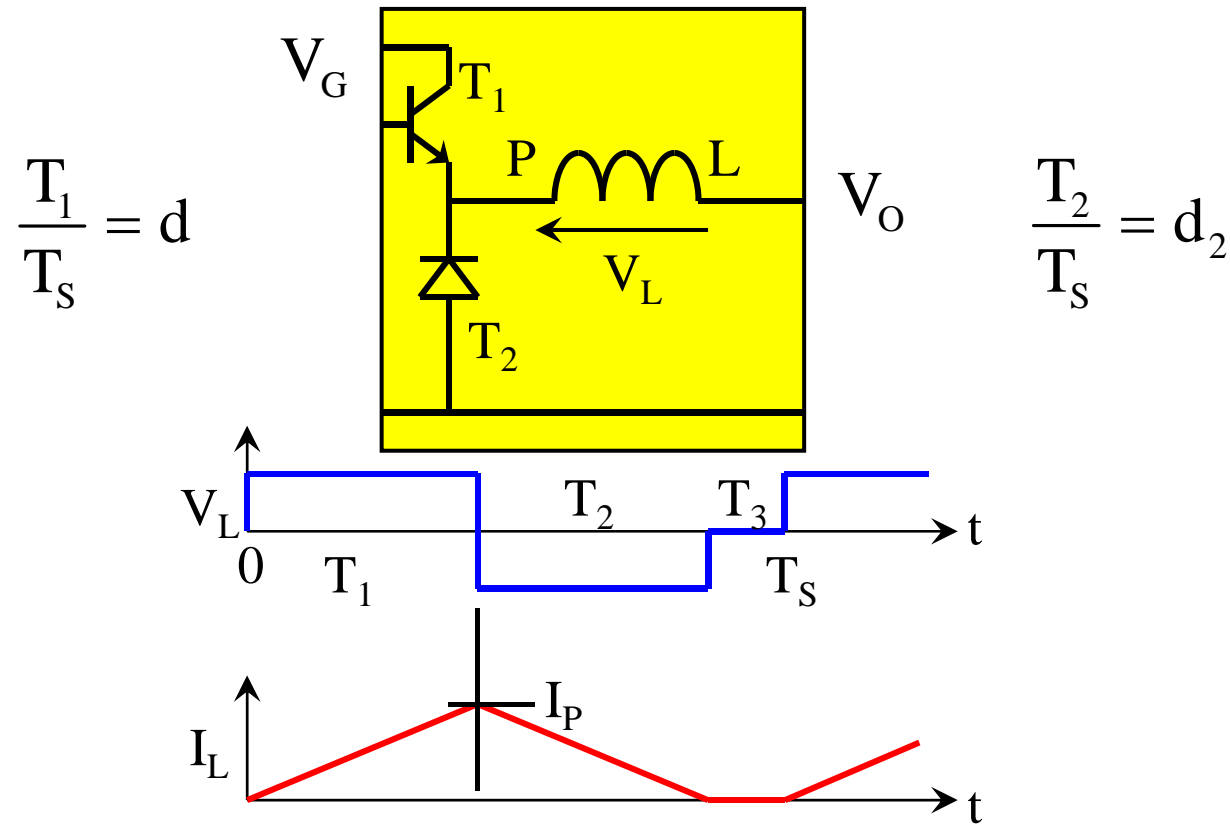

Resolving d_2 as a function of d

Switched Mode Power Conversion

Buck Converter – DCM Conversion Ratio

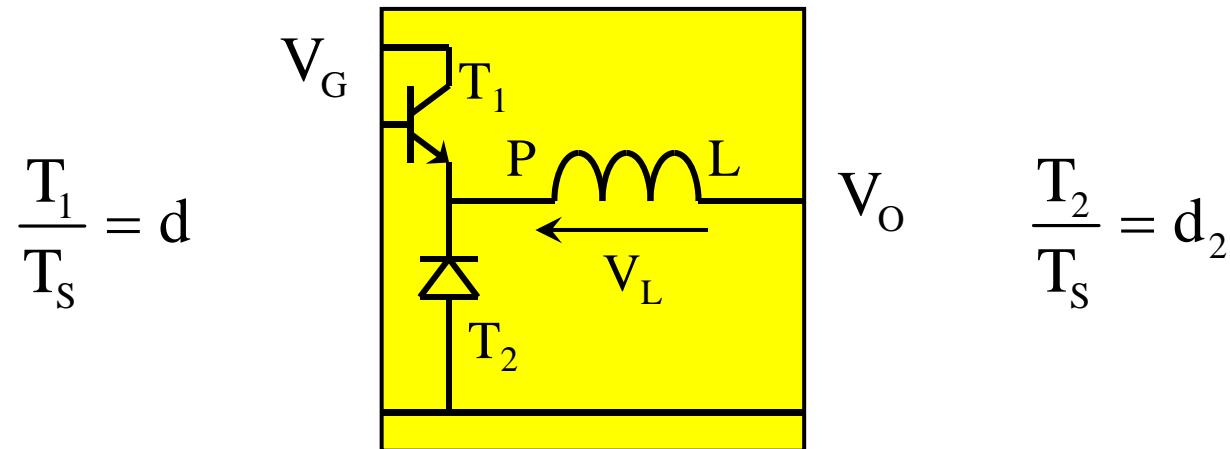


$$I_P = d_2 V_O T_s / L$$

$$I_O = \frac{V_O}{R} = \frac{1}{2} I_P (d + d_2) = \frac{1}{2} (d + d_2) \frac{d_2 T_s V_O}{L}$$

Resolving d_2 as a function of d

Switched Mode Power Conversion

Buck Converter – DCM Conversion Ratio

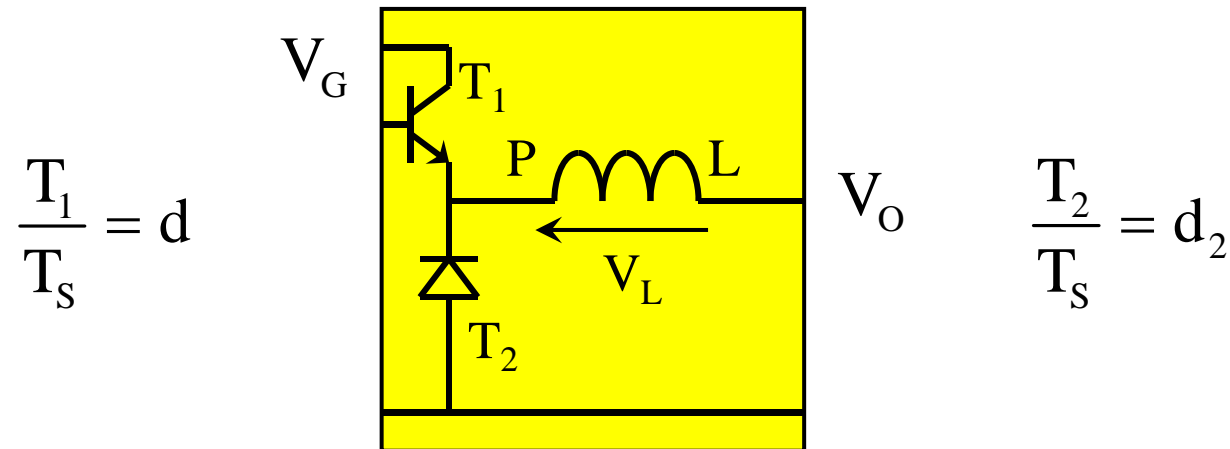


$$I_O = \frac{V_O}{R} = \frac{1}{2} I_P (d + d_2) = \frac{1}{2} (d + d_2) \frac{d_2 T_s V_O}{L}$$

$$d_2 (d + d_2) = \frac{2L}{RT_s} = K$$

d and d₂ are related through Conduction Parameter K

Switched Mode Power Conversion

Buck Converter – DCM Conversion Ratio

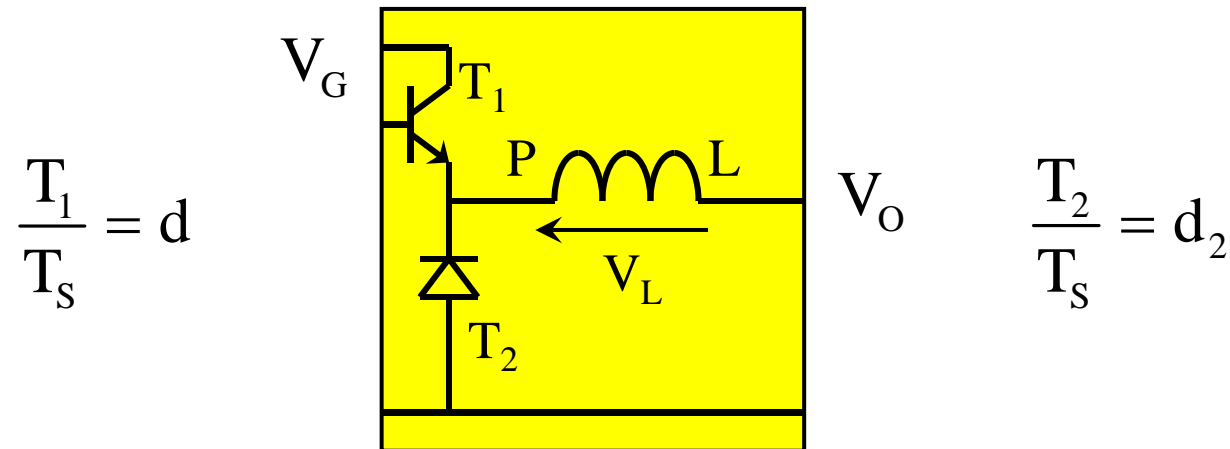

$$\frac{T_1}{T_s} = d$$

$$\frac{T_2}{T_s} = d_2$$


$$d_2 (d + d_2) = \frac{2L}{RT_s} = K$$

$$d_2 = \frac{-d + d \sqrt{1 + (4K/d^2)}}{2}$$

d and d_2 are related through Conduction Parameter K

Switched Mode Power Conversion

Buck Converter – DCM Conversion Ratio

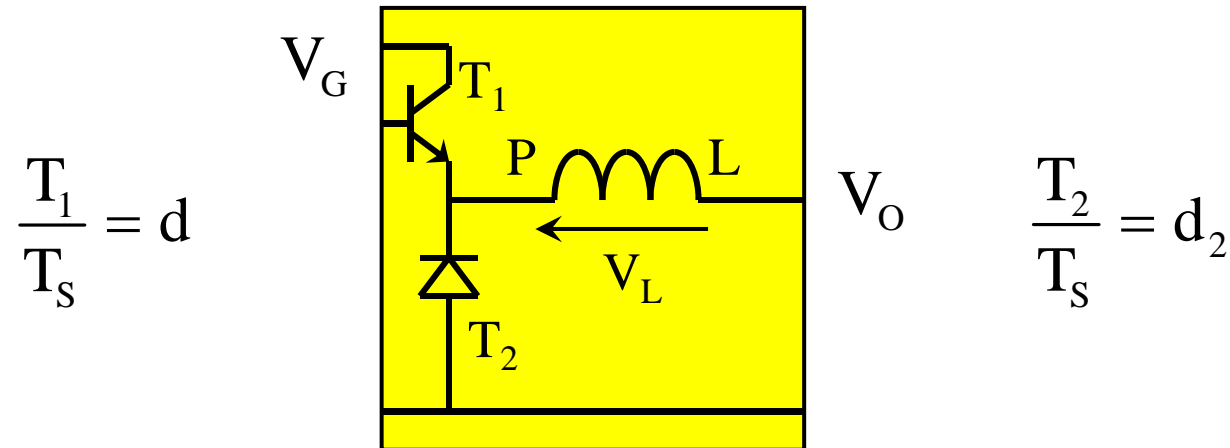


$$d_2 = \frac{-d + d \sqrt{1 + (4K / d^2)}}{2}$$

$$M = \frac{V_O}{V_G} = \frac{2}{1 + \sqrt{1 + (4K / d^2)}}$$

Conversion Factor is a Function of d and K

Switched Mode Power Conversion

Buck Converter – DCM Conversion Ratio

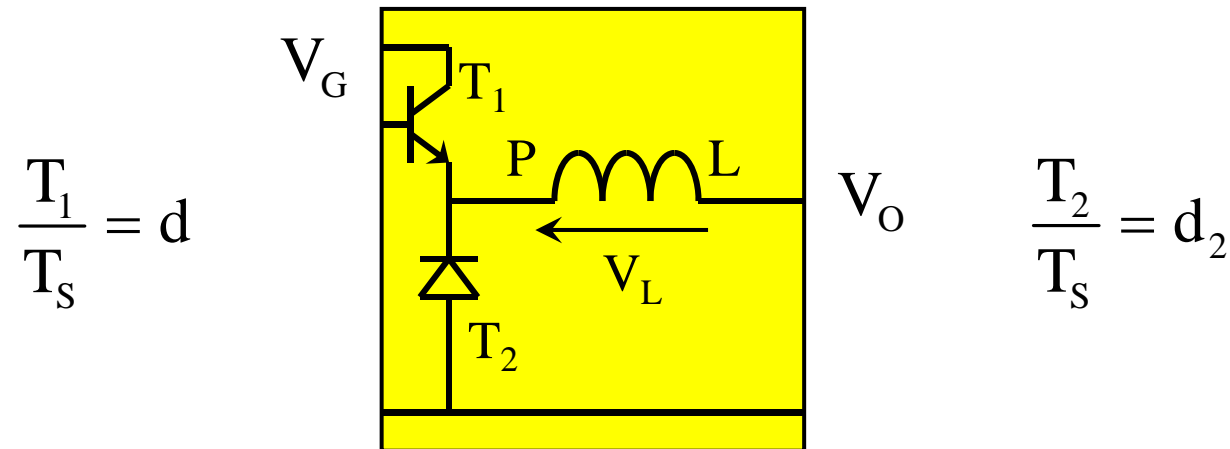


$$M = \frac{d}{d + d_2} > d \quad (\because (d + d_2) < 1)$$

Conversion Factor in DCM is More

Switched Mode Power Conversion

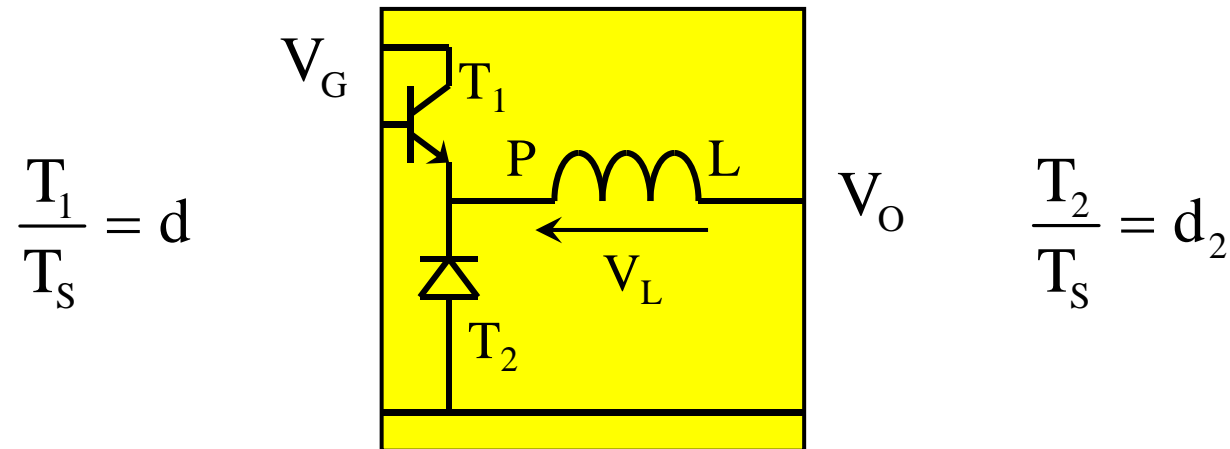Buck Converter – Border Between DCM & CCM




$$d_2 (d + d_2) = (1 - d) = \frac{2L}{RT_s} = K$$

$$\frac{2L}{RT_s} > (1 - d) \Rightarrow \text{Op.Mode is CCM} \quad \frac{2L}{RT_s} < (1 - d) \Rightarrow \text{Op.Mode is DCM}$$

Border of DCM and CCM

Switched Mode Power Conversion

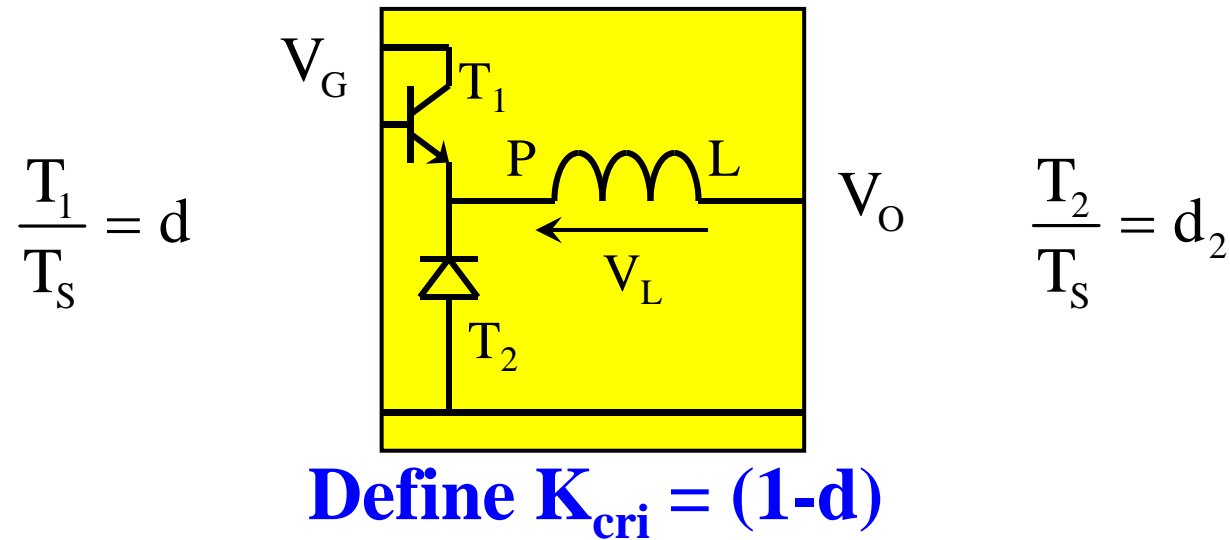Buck Converter – Border Between DCM & CCM




$K > K_{cri}$: CCM Operation

$K < K_{cri}$: CCM Operation

Border of DCM and CCM

Switched Mode Power Conversion

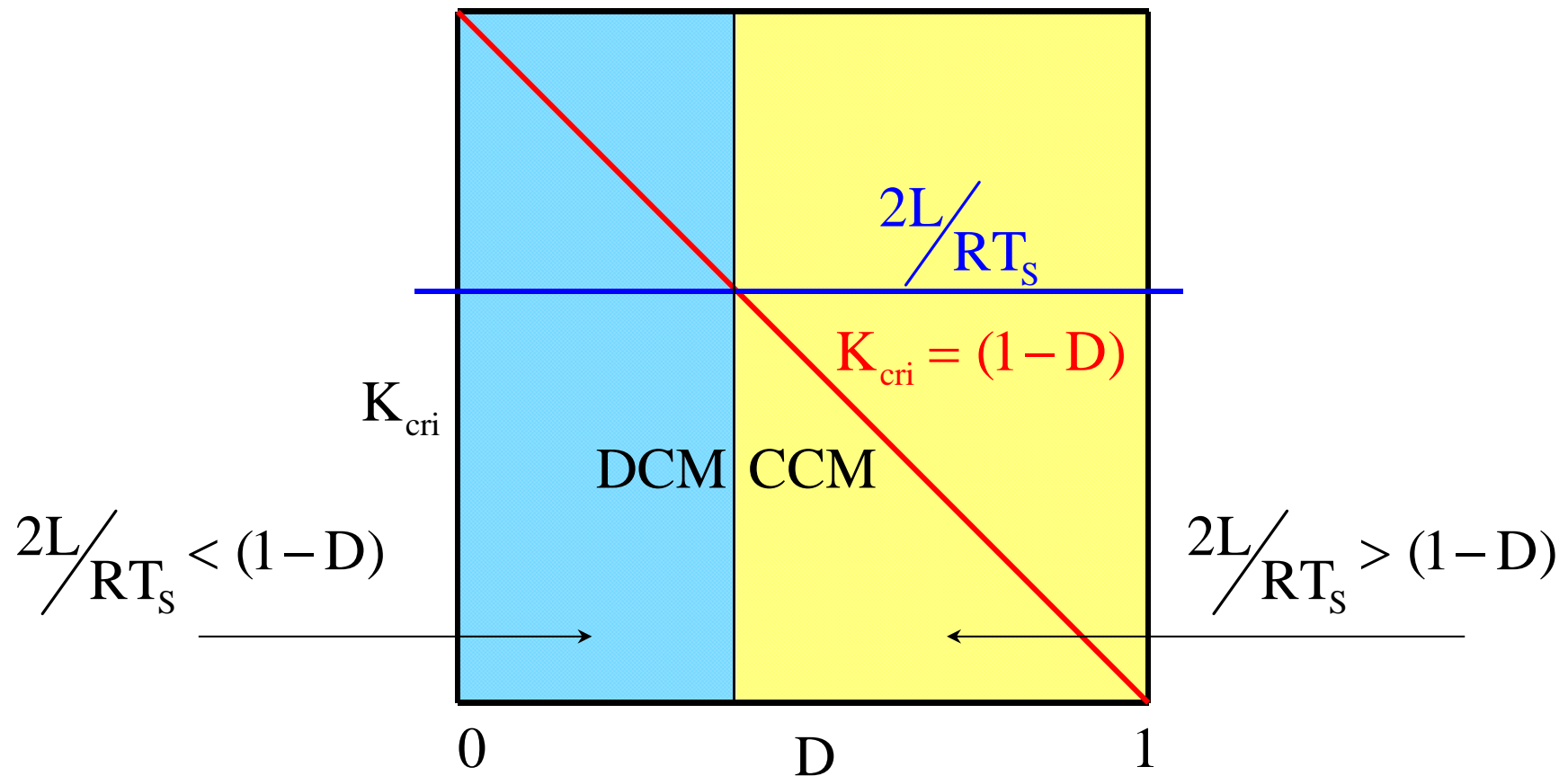
Buck Converter – Border Between DCM & CCM



Graphical Determination of DCM and CCM

Switched Mode Power Conversion


Buck Converter

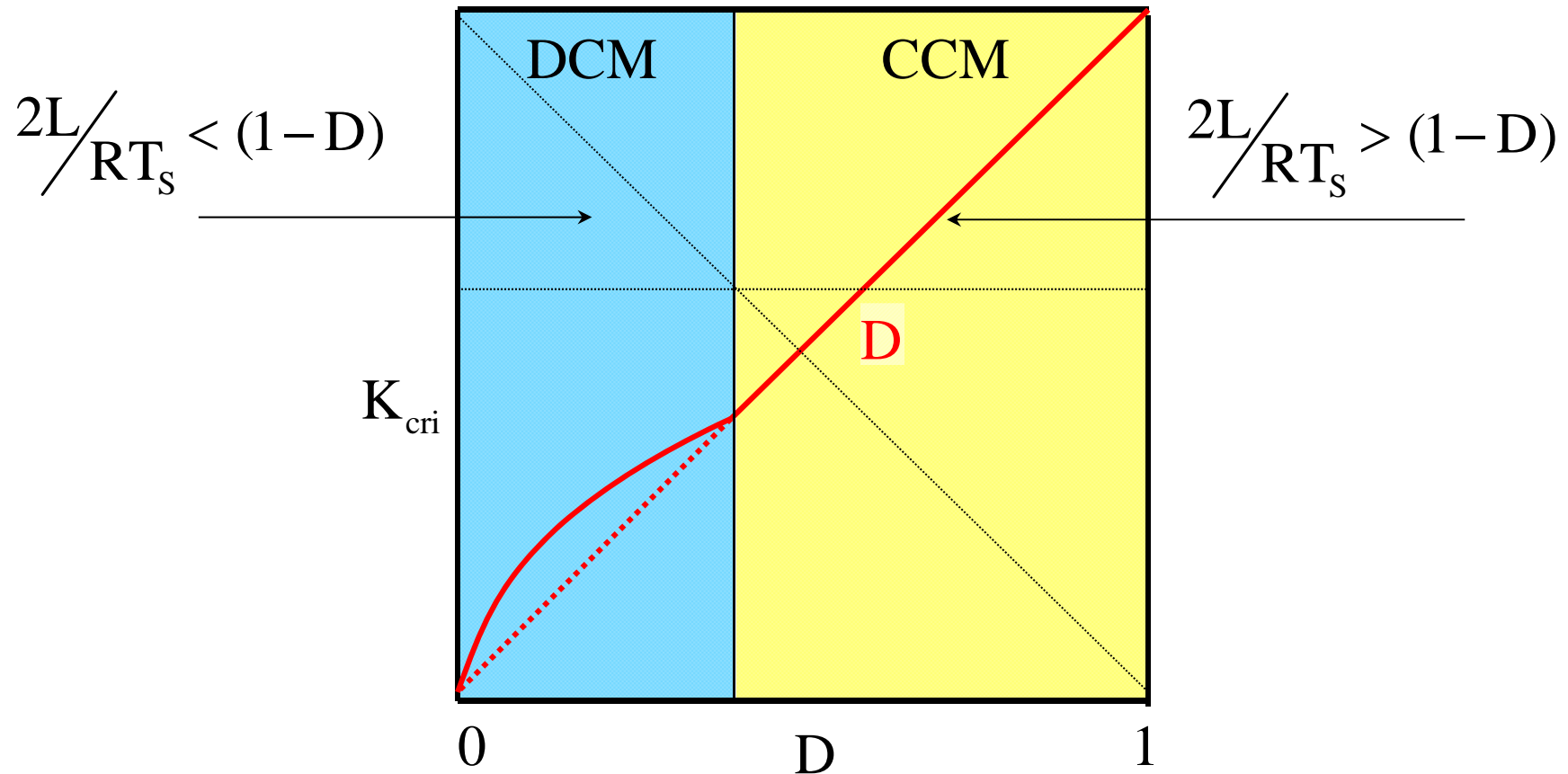

Gain is More in DCM

Switched Mode Power Conversion

DCM Operation – Salient Features

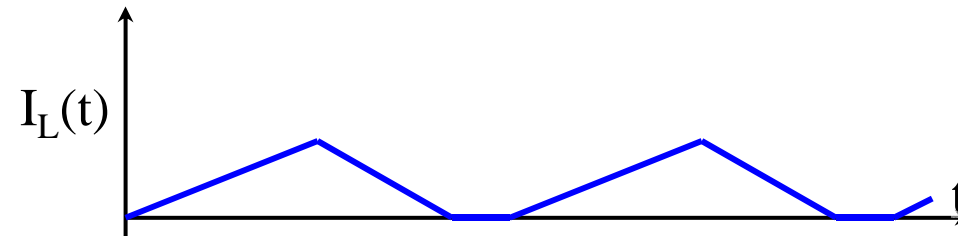

Zero (Low) Turn-on Loss

Soft Diode Recovery



Low Circuit Inductance

High Inductor Ripple

Inductor Current

Switched Mode Power Conversion


Boost Converter – Inductor Current

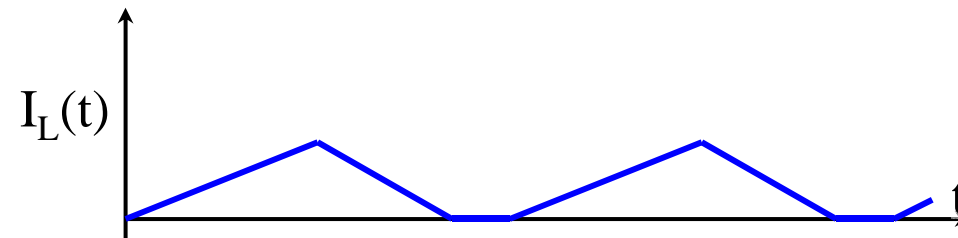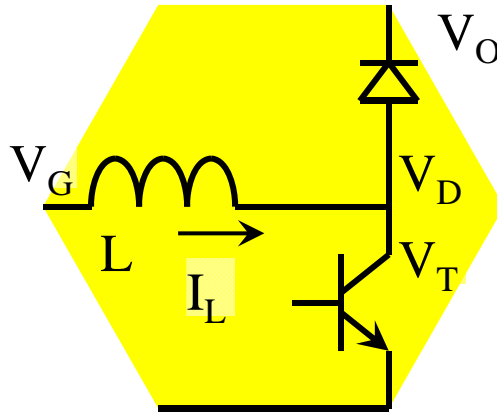

Inductor Current

Switched Mode Power Conversion


Boost Converter – DCM Conversion Ratio

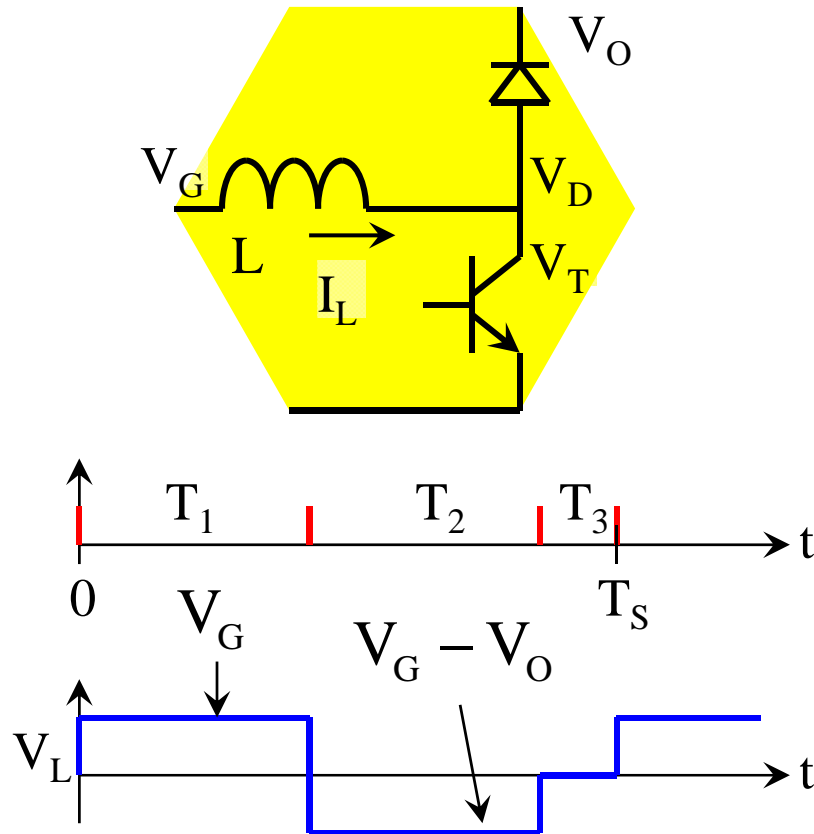

Inductor Volt-Sec Balance

Switched Mode Power Conversion

Boost Converter – DCM Conversion Ratio

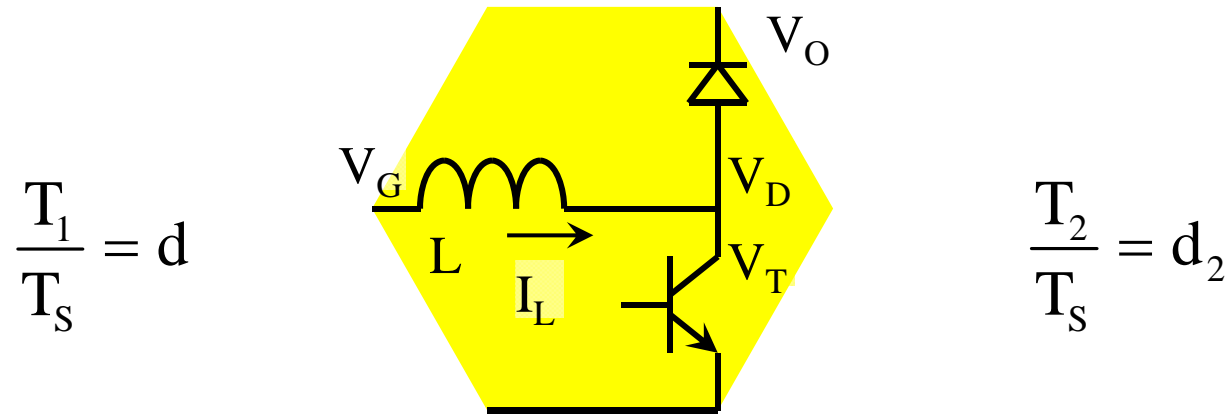



$$V_G T_1 + (V_G - V_O) T_2 = 0 \quad (d + d_2) V_G = d_2 V_O$$

$$\frac{V_O}{V_G} = M = \frac{d + d_2}{d_2}$$

Voltage Conversion Ratio

Switched Mode Power Conversion


Boost Converter – DCM Conversion Ratio

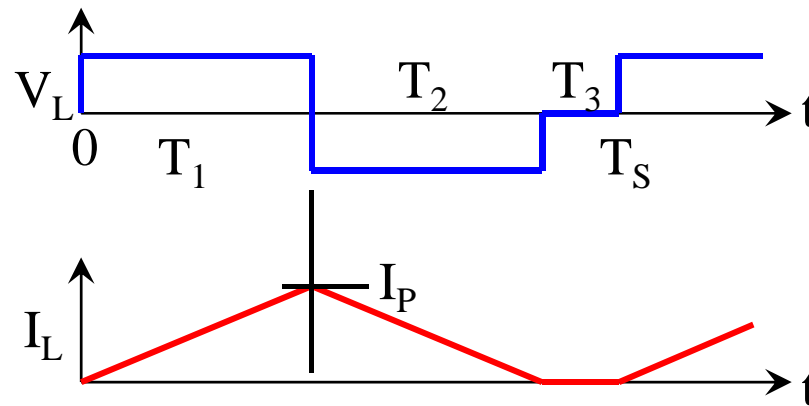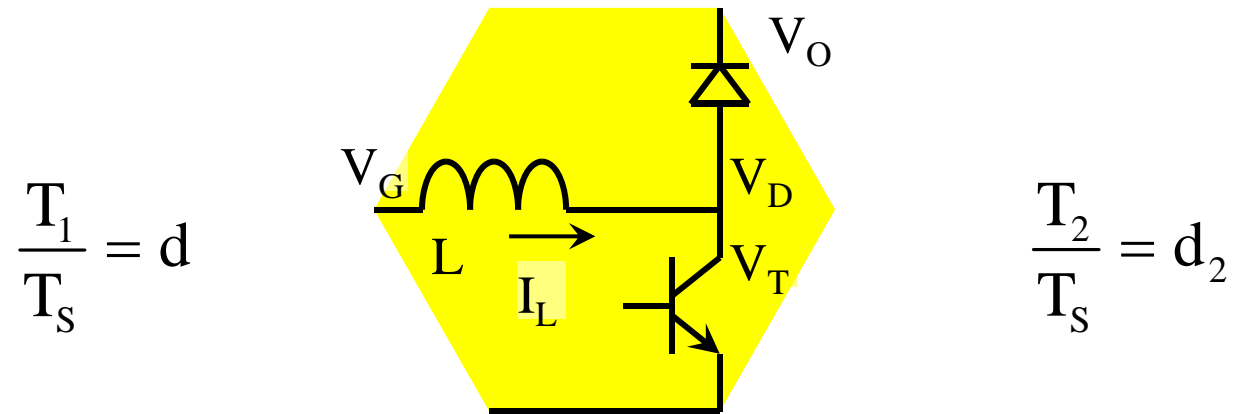

Resolving d_2 as a function of d

Switched Mode Power Conversion

Boost Converter – DCM Conversion Ratio

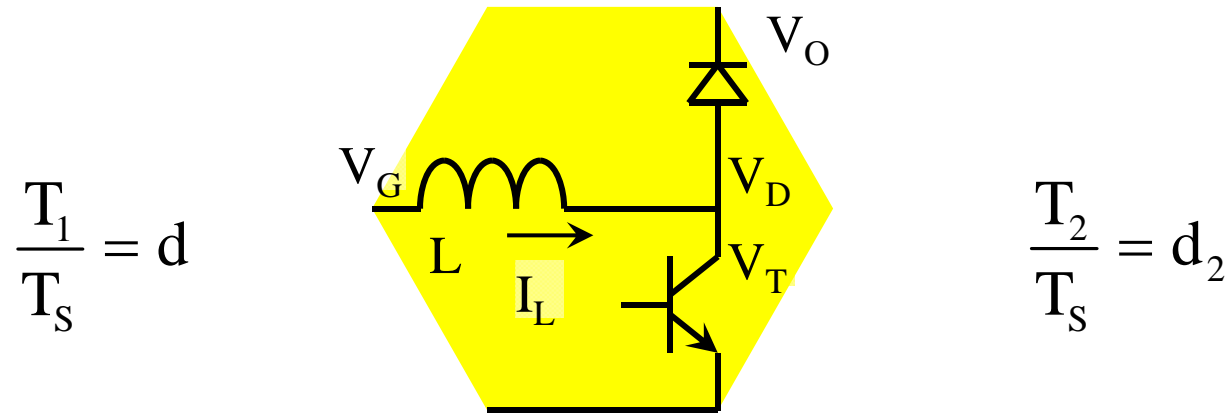

$$\frac{T_1}{T_s} = d$$

$$\frac{T_2}{T_s} = d_2$$


$$I_P = dV_G T_s / L$$

$$I_O = \frac{V_O}{R} = \frac{1}{2} I_P d_2 = \frac{1}{2} d_2 \frac{dT_s V_G}{L}$$

Resolving d_2 as a function of d

Switched Mode Power Conversion

Boost Converter – DCM Conversion Ratio

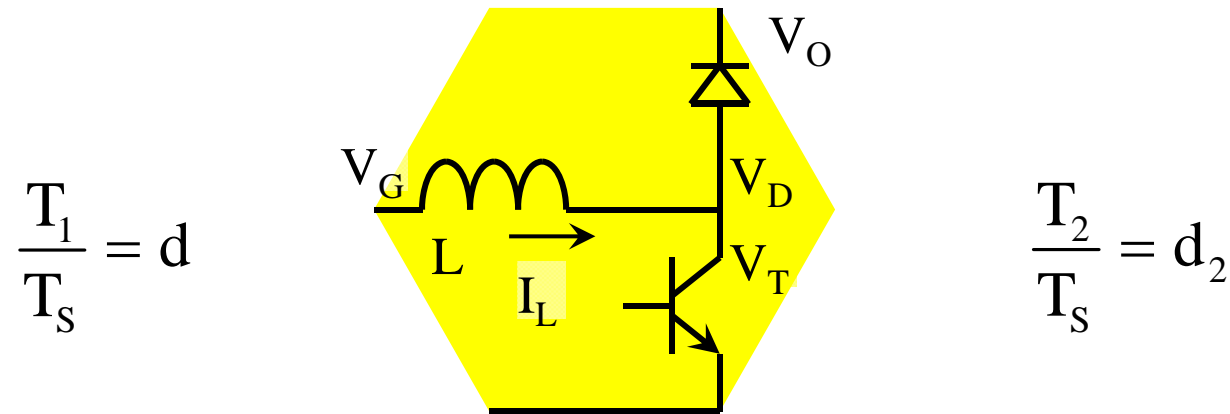

$$\frac{T_1}{T_s} = d$$

$$\frac{T_2}{T_s} = d_2$$


$$I_O = \frac{V_O}{R} = \frac{1}{2} I_P d_2 = \frac{1}{2} d_2 \frac{dT_s V_G}{L}$$

$$K(d + d_2) = dd_2^2 ; K = \frac{2L}{RT_s}$$

d and d_2 are related through Conduction Parameter K

Switched Mode Power Conversion

Boost Converter – DCM Conversion Ratio

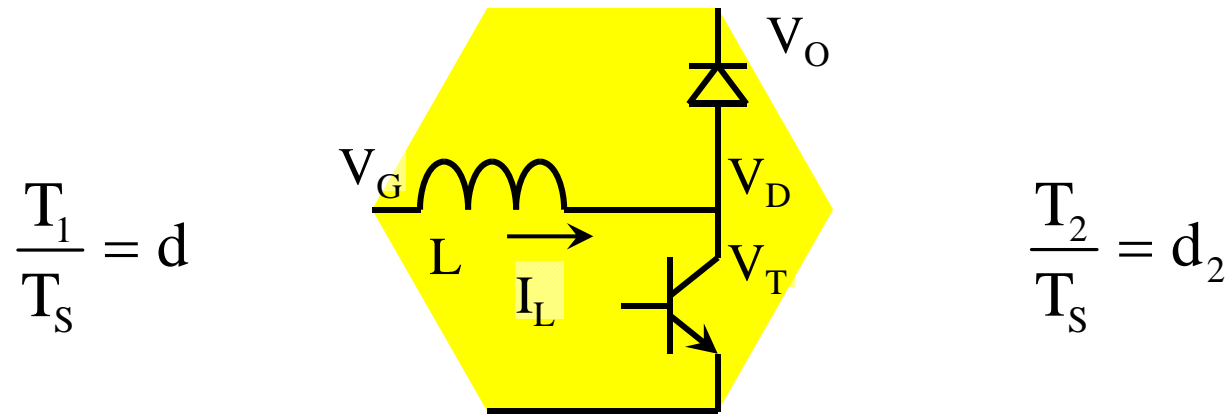

$$\frac{T_1}{T_s} = d$$

$$\frac{T_2}{T_s} = d_2$$


$$K(d + d_2) = dd_2^2$$

$$d_2 = \frac{K}{d} \frac{\left\{ 1 + \sqrt{1 + \left(4d^2 / K \right)} \right\}}{2}$$

d and d_2 are related through Conduction Parameter K

Switched Mode Power Conversion

Boost Converter – DCM Conversion Ratio

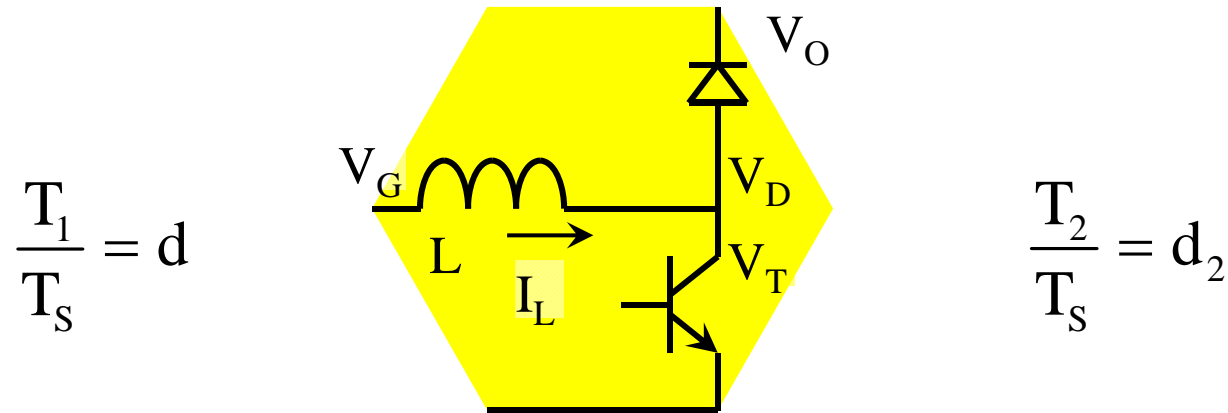


$$\frac{V_O}{V_G} = \frac{d + d_2}{d_2} = \frac{d}{K} d_2$$

$$\frac{V_O}{V_G} = \frac{\left\{ 1 + \sqrt{1 + (4d^2 / K)} \right\}}{2}$$

d and d_2 are related through Conduction Parameter K

Switched Mode Power Conversion

Boost Converter – DCM Conversion Ratio

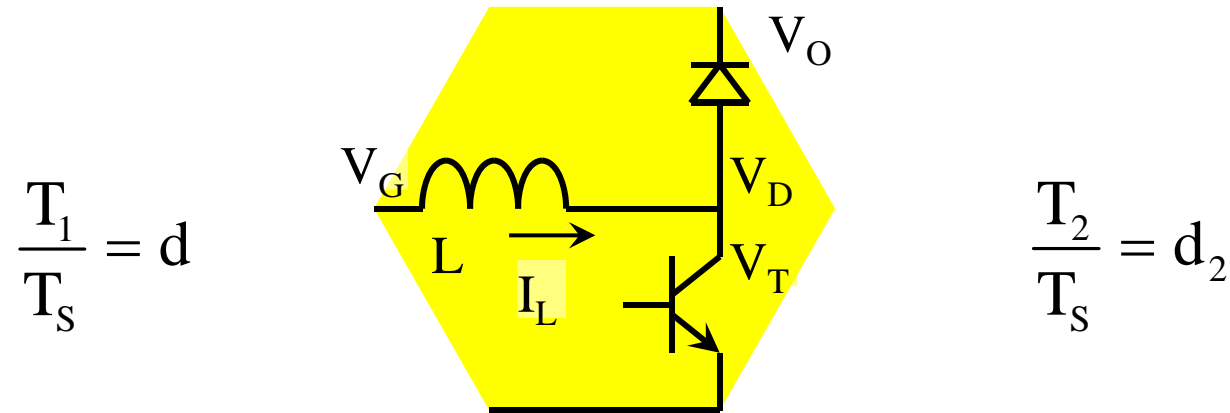


$$M = \frac{d + d_2}{d_2} > \frac{1}{(1 - d)} \quad (\because (d + d_2) < 1)$$

Conversion Factor in DCM is More

Switched Mode Power Conversion

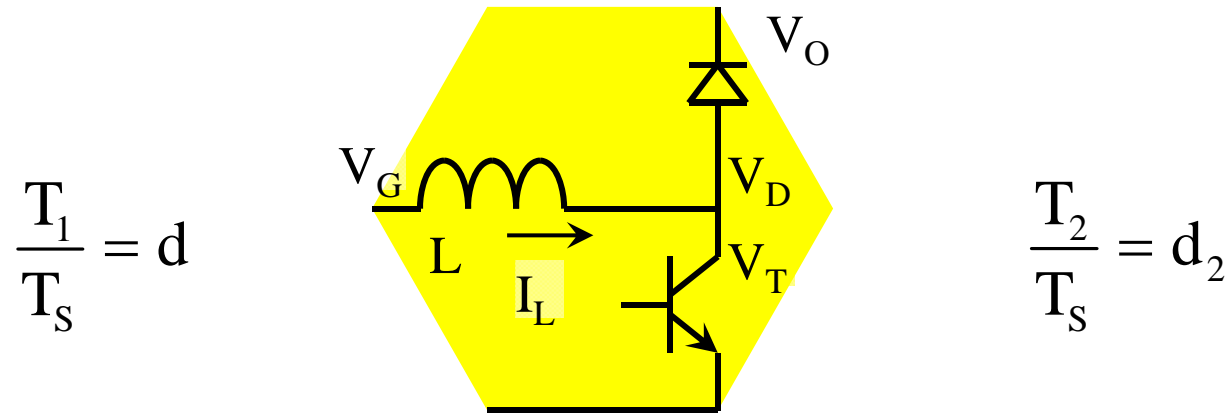Boost Converter – Border Between DCM & CCM




$$K(d + d_2) = dd_2^2$$

$$K_{\text{cri}} = d(1 - d)^2$$

Border of DCM and CCM

Switched Mode Power Conversion

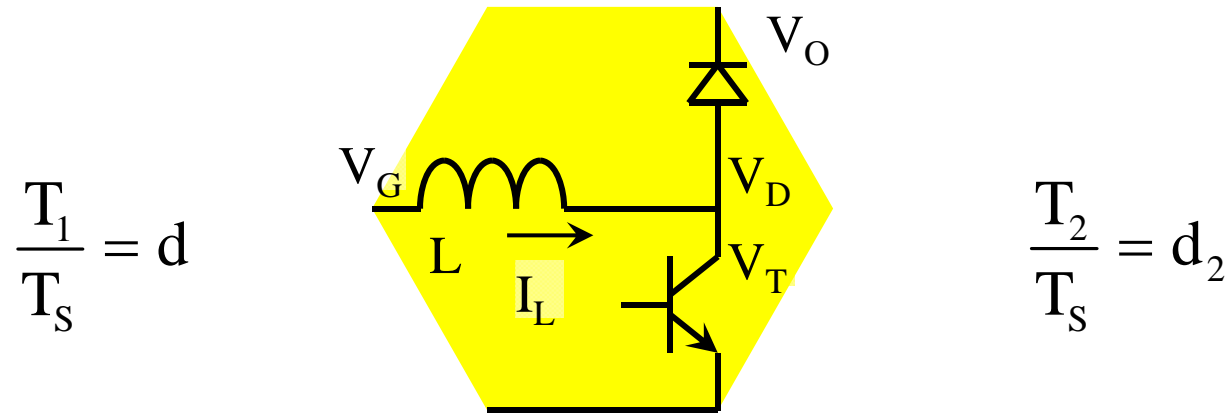Boost Converter – Border Between DCM & CCM



Define $K_{cri} = d(1-d)^2$


$K > K_{cri}$: CCM Operation

$K < K_{cri}$: DCM Operation

Border of DCM and CCM

Switched Mode Power Conversion

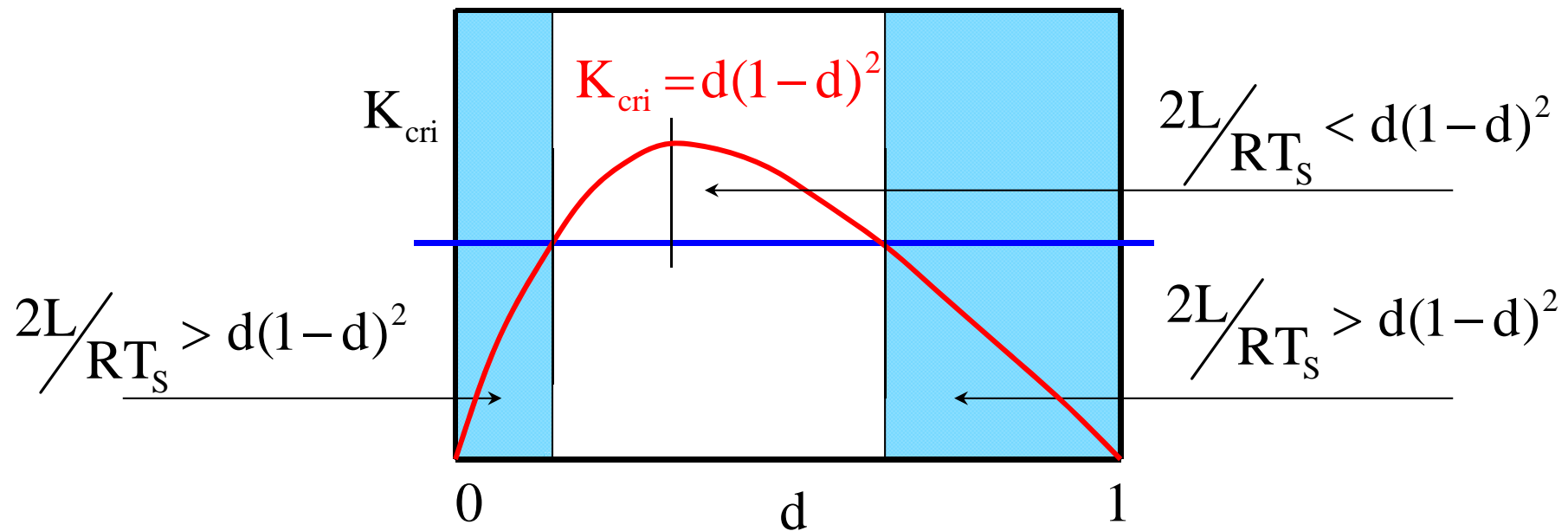
Boost Converter – Border Between DCM & CCM



Graphical Determination of DCM and CCM

Switched Mode Power Conversion

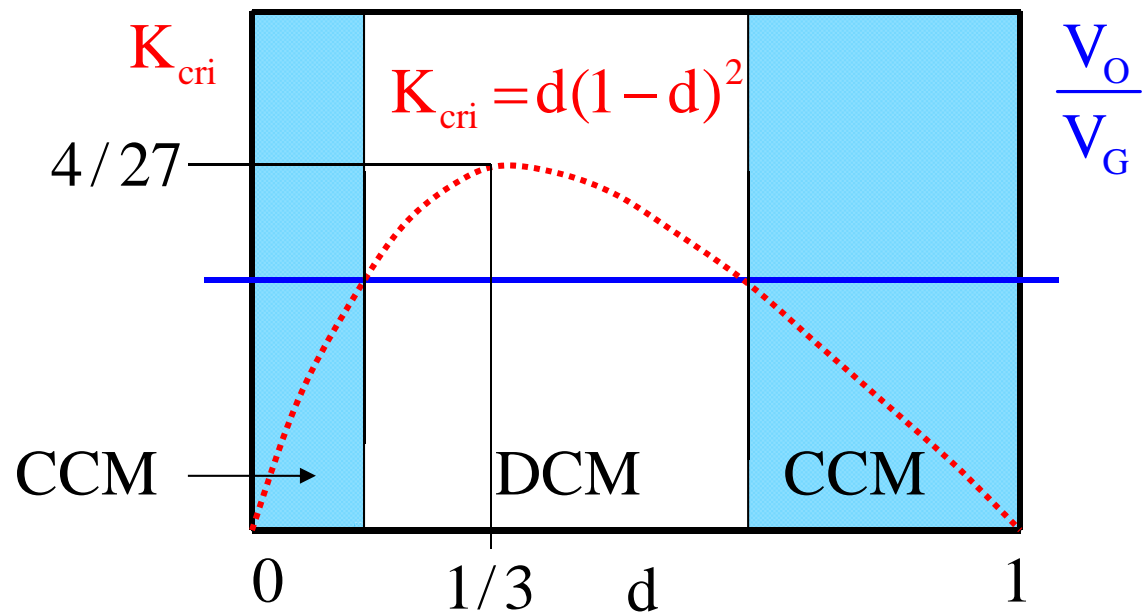
Boost Converter – Border Between DCM & CCM



Graphical Determination of DCM and CCM

Switched Mode Power Conversion


Boost Converter – DCM & CCM

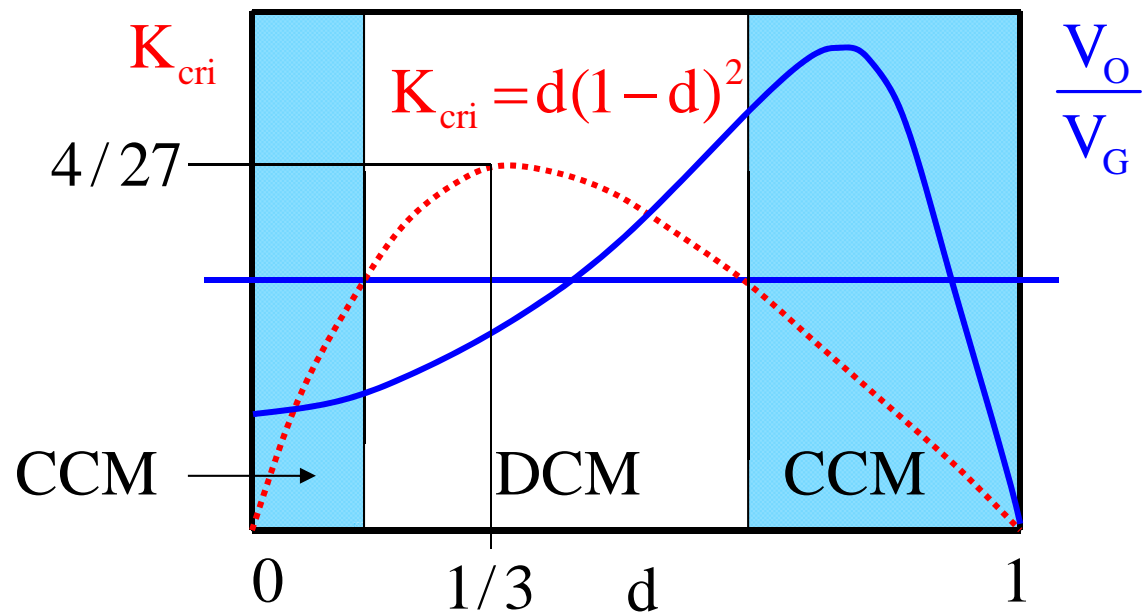

Graphical Determination of DCM and CCM

Switched Mode Power Conversion



Boost Converter – DCM & CCM

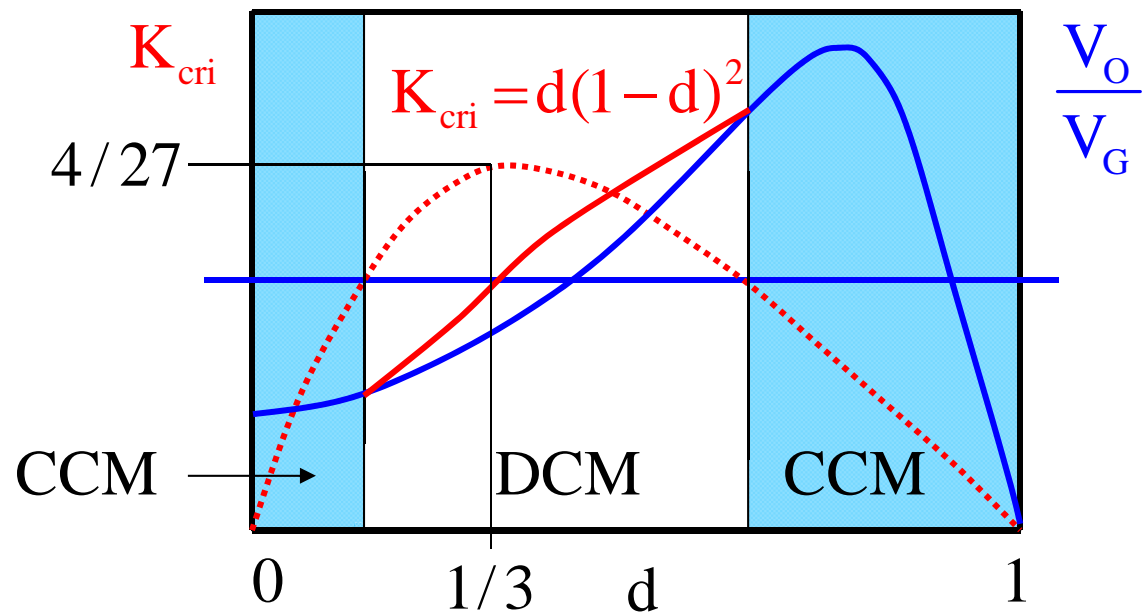

Gain in DCM is More than Gain in CCM

Switched Mode Power Conversion


Flyback Converter – Inductor Current

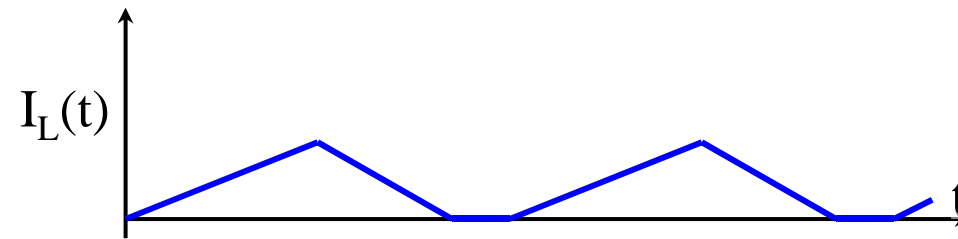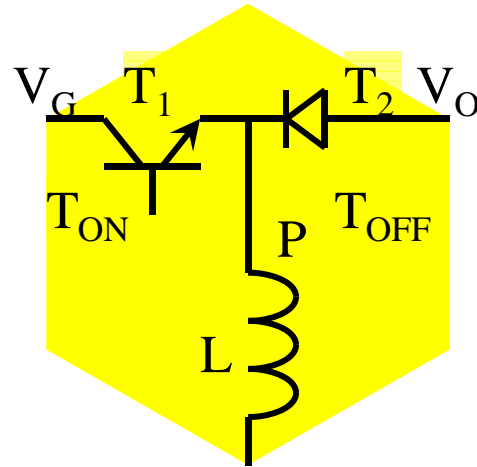

Inductor Current

Switched Mode Power Conversion


Flyback Converter – DCM Conversion Ratio

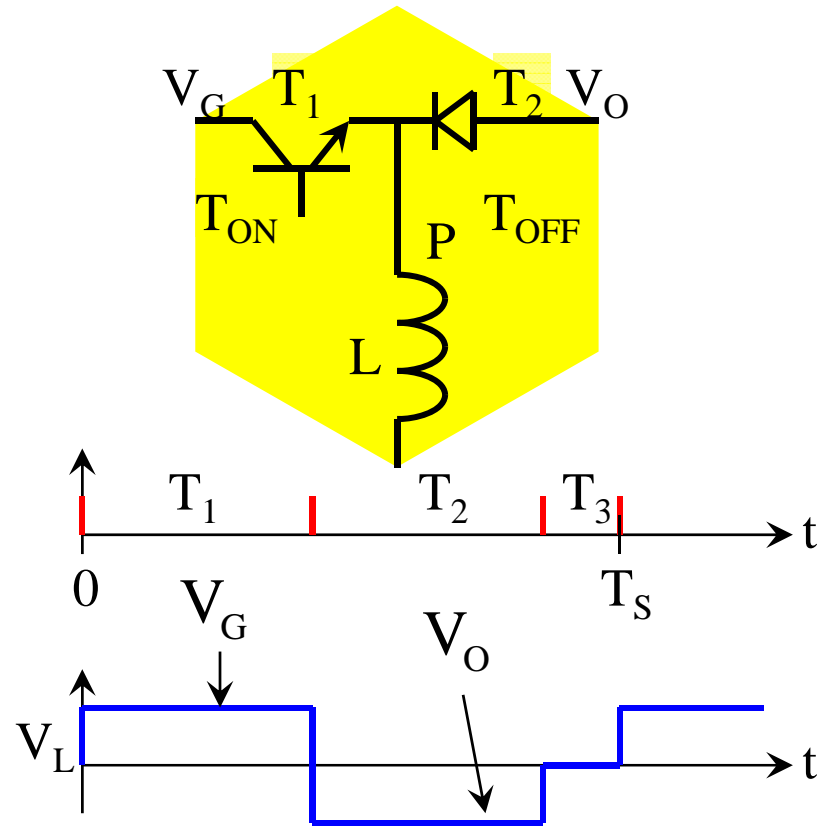

Inductor Volt-Sec Balance

Switched Mode Power Conversion

Flyback Converter – DCM Conversion Ratio

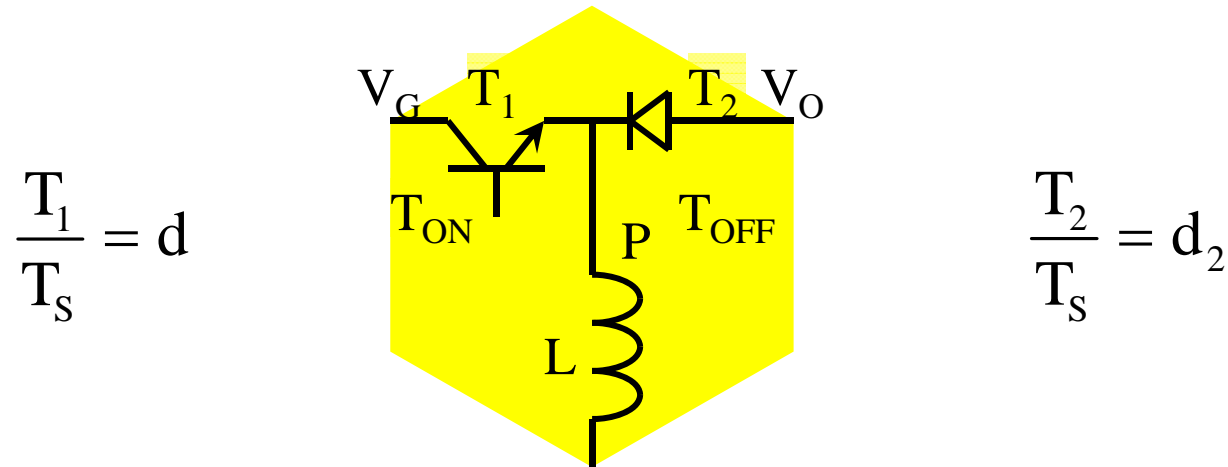

$$V_G T_1 + V_O T_2 = 0$$


$$dV_G = -d_2 V_O$$

$$\frac{V_o}{V_G} = M = -\frac{d}{d_2}$$

Voltage Conversion Ratio

Switched Mode Power Conversion


Flyback Converter – DCM Conversion Ratio

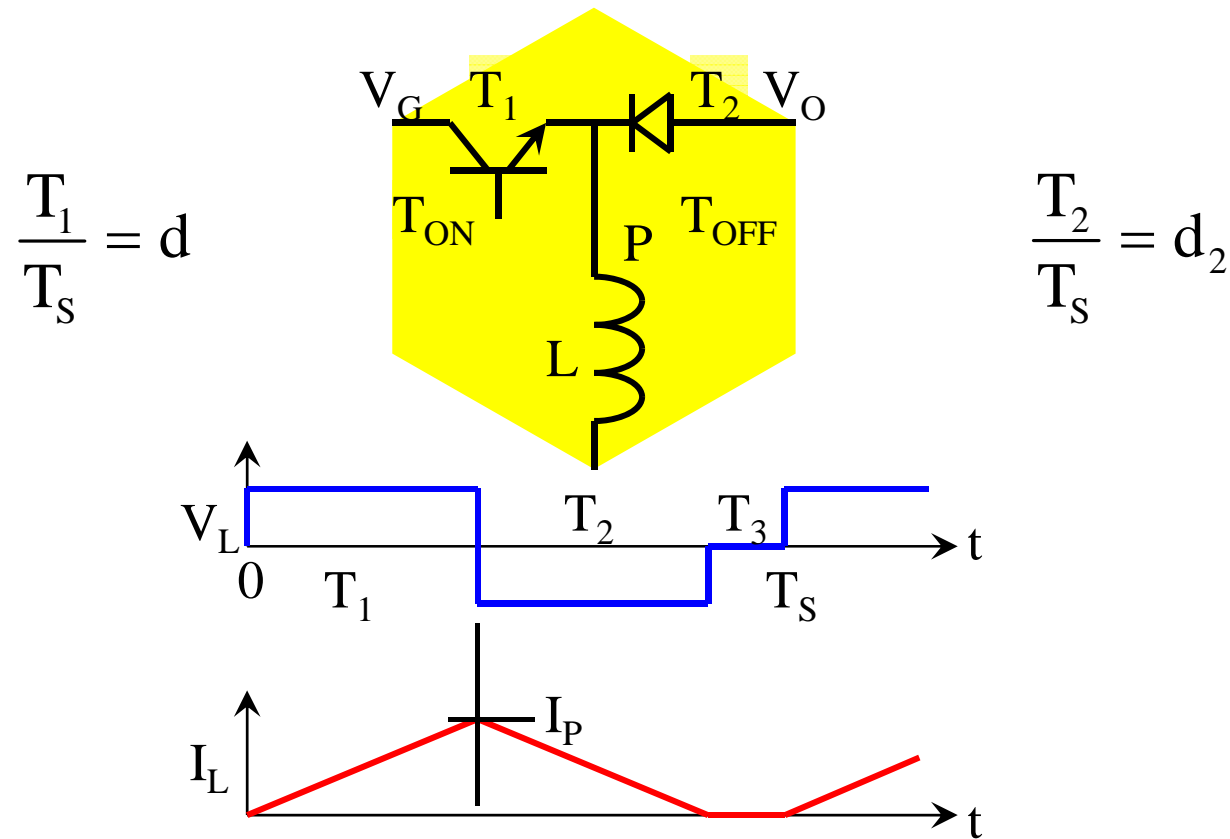

Resolving d_2 as a function of d

Switched Mode Power Conversion

Flyback Converter – DCM Conversion Ratio

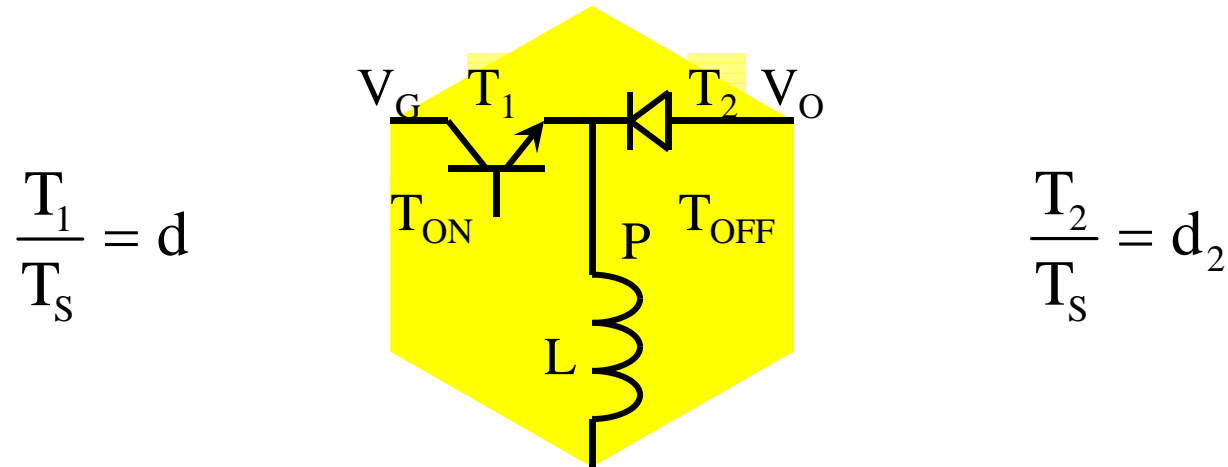

$$\frac{T_1}{T_s} = d$$

$$\frac{T_2}{T_s} = d_2$$


$$I_P = dV_G T_S / L$$

$$I_O = \frac{V_O}{R} = \frac{1}{2} I_P d_2 = \frac{1}{2} d_2 \frac{dT_S V_G}{L}$$

Resolving d_2 as a function of d

Switched Mode Power Conversion

Flyback Converter – DCM Conversion Ratio

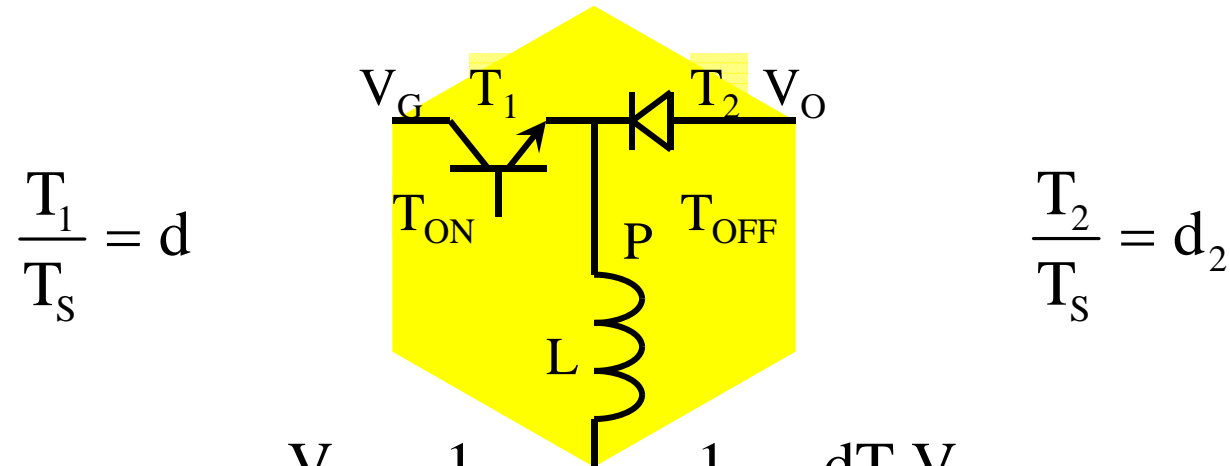

$$\frac{T_1}{T_s} = d$$

$$\frac{T_2}{T_s} = d_2$$


$$I_O = \frac{V_O}{R} = \frac{1}{2} I_P d_2 = \frac{1}{2} d_2 \frac{dT_s V_G}{L}$$

$$K = d_2^2 ; K = \frac{2L}{RT_s}$$

d and d₂ are related through Conduction Parameter K

Switched Mode Power Conversion


Flyback Converter – DCM Conversion Ratio

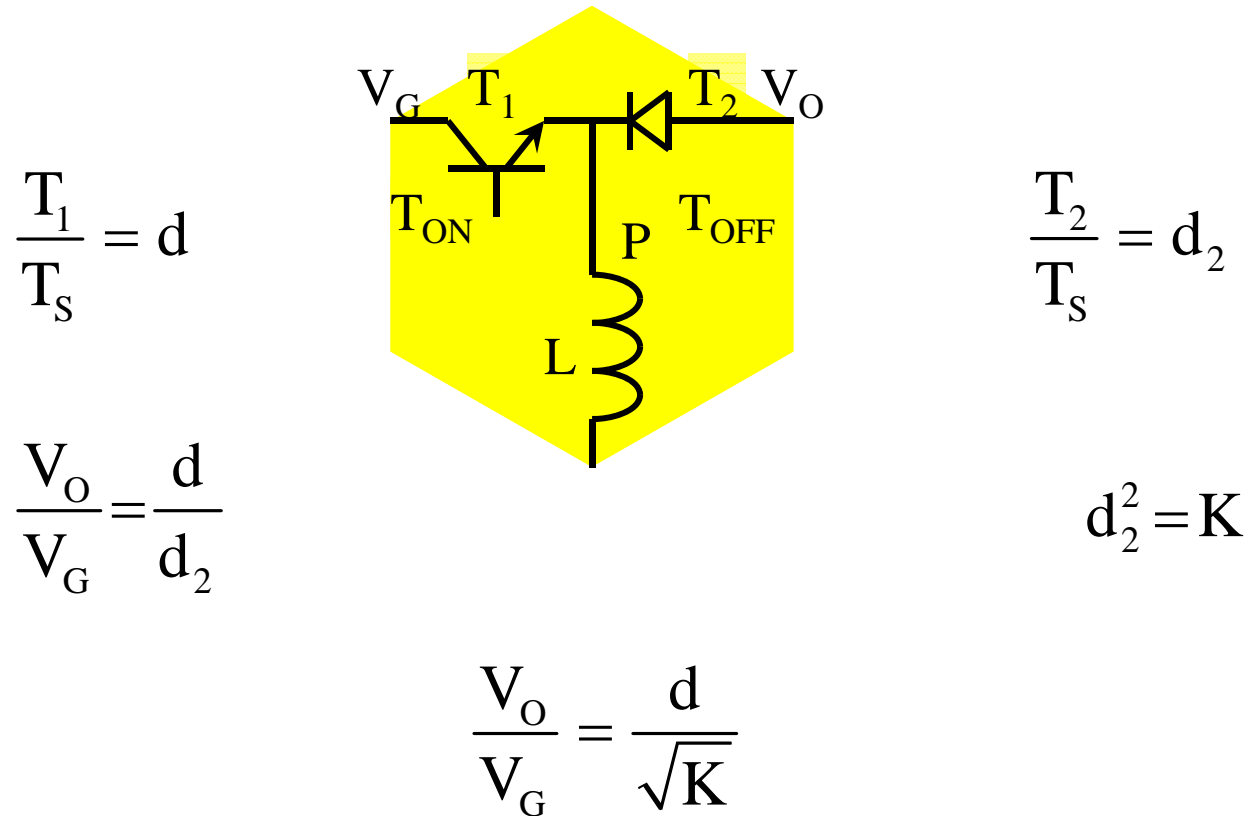

d and d₂ are related through Conduction Parameter K

Switched Mode Power Conversion

Flyback Converter – DCM Conversion Ratio

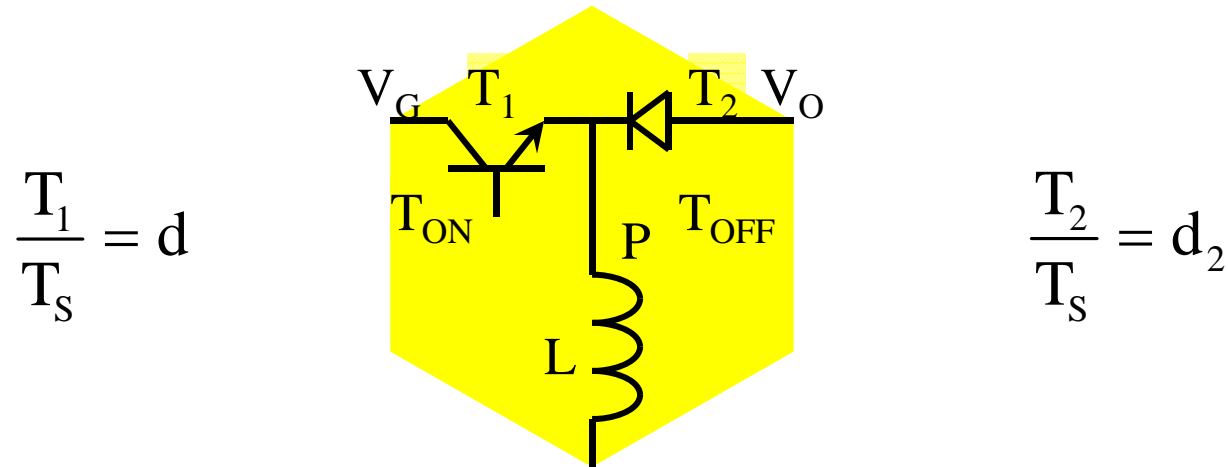


$$|M| = \frac{d}{d_2} > \frac{d}{(1-d)} \quad (\because (d + d_2) < 1)$$

Conversion Factor in DCM is More

Switched Mode Power Conversion

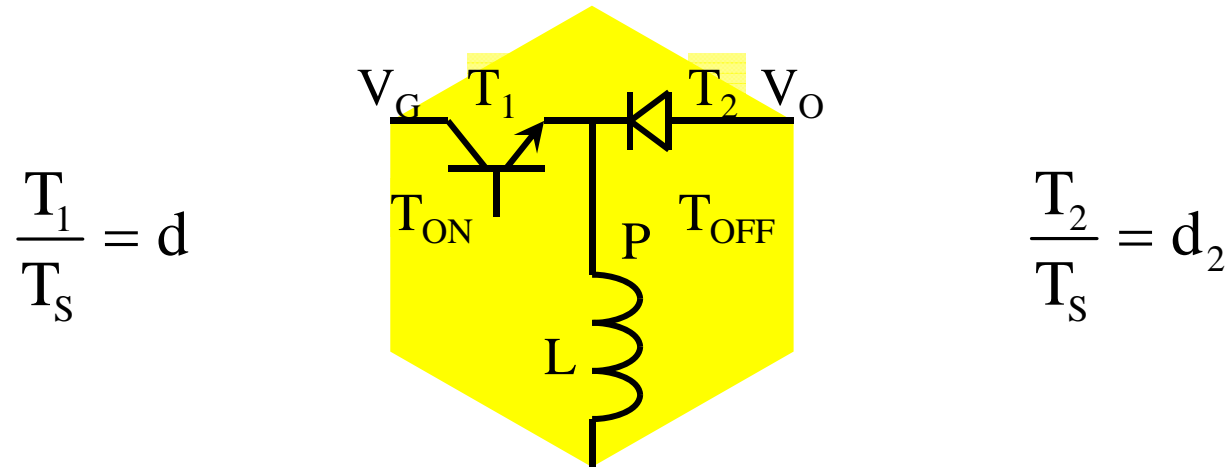Flyback Converter – Border Between DCM & CCM




$$K = d_2^2$$

$$K_{cri} = (1 - d)^2$$

Border of DCM and CCM

Switched Mode Power Conversion

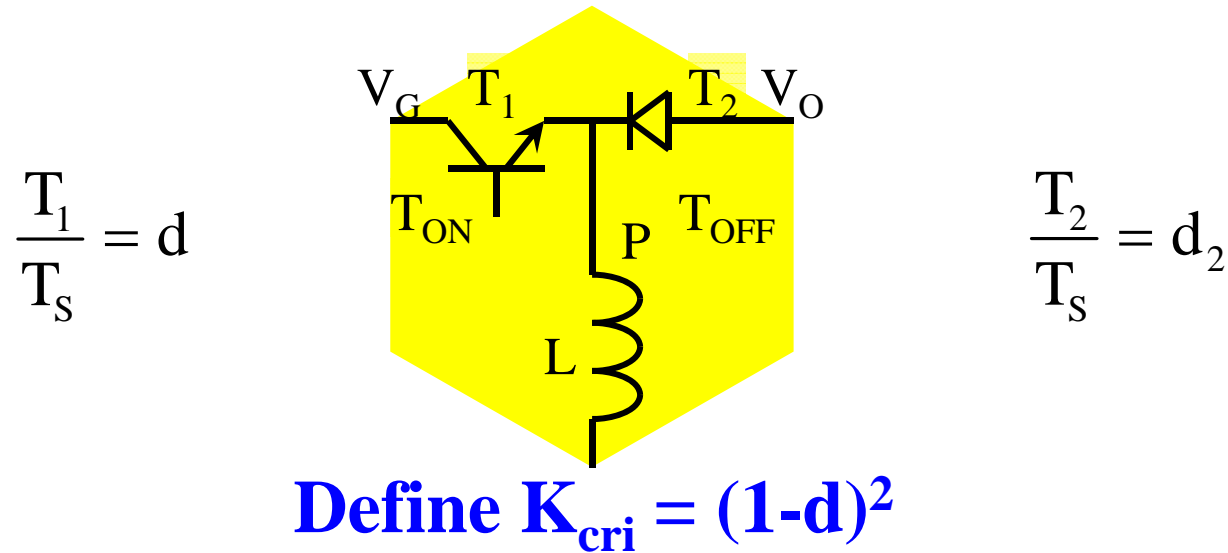Flyback Converter – Border Between DCM & CCM




$K > K_{cri}$: CCM Operation

$K < K_{cri}$: DCM Operation

Border of DCM and CCM

Switched Mode Power Conversion

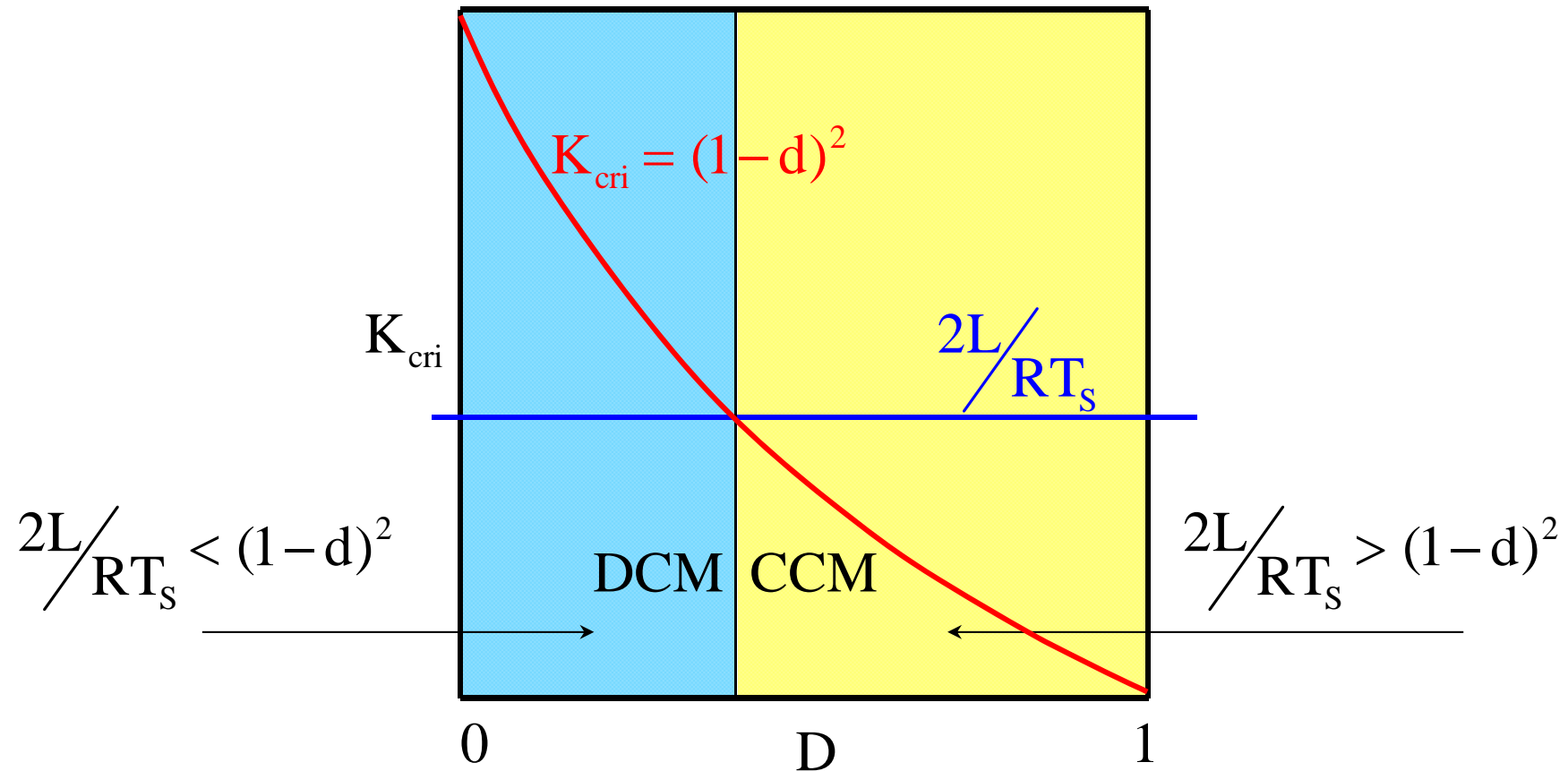
Flyback Converter – Border Between DCM & CCM



Graphical Determination of DCM and CCM

Switched Mode Power Conversion

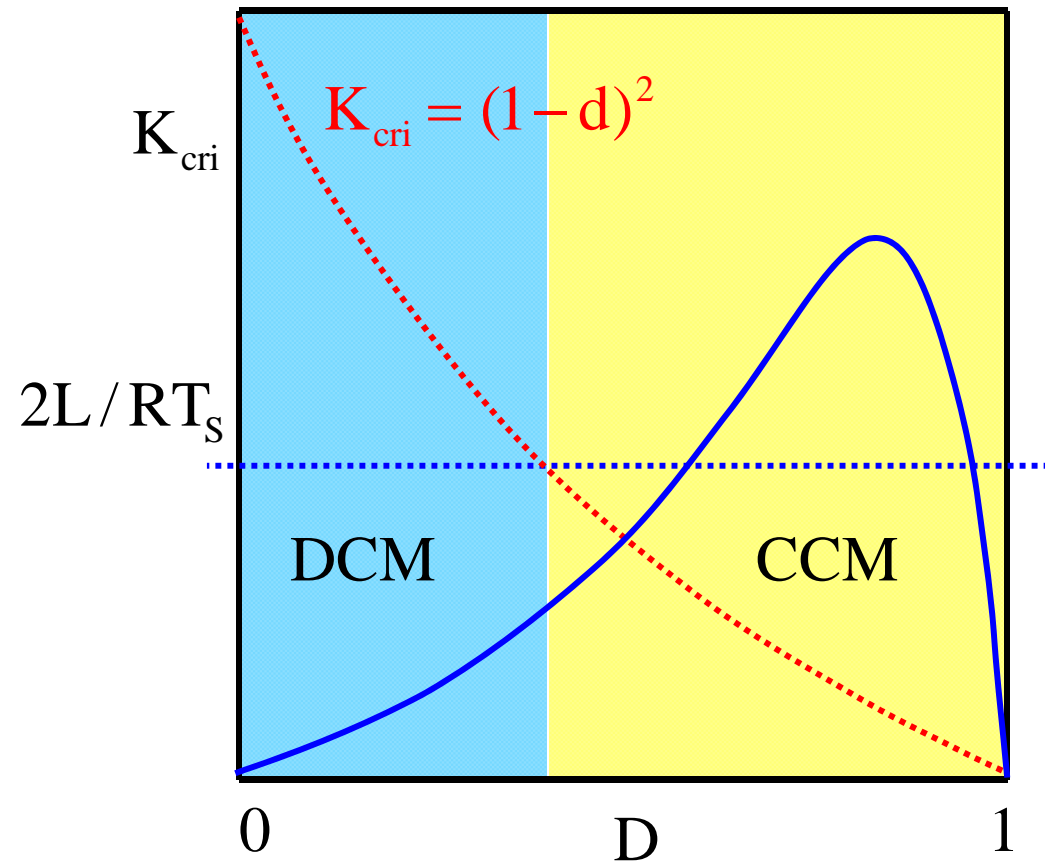
Flyback Converter – Border Between DCM & CCM



Graphical Determination of DCM and CCM

Switched Mode Power Conversion

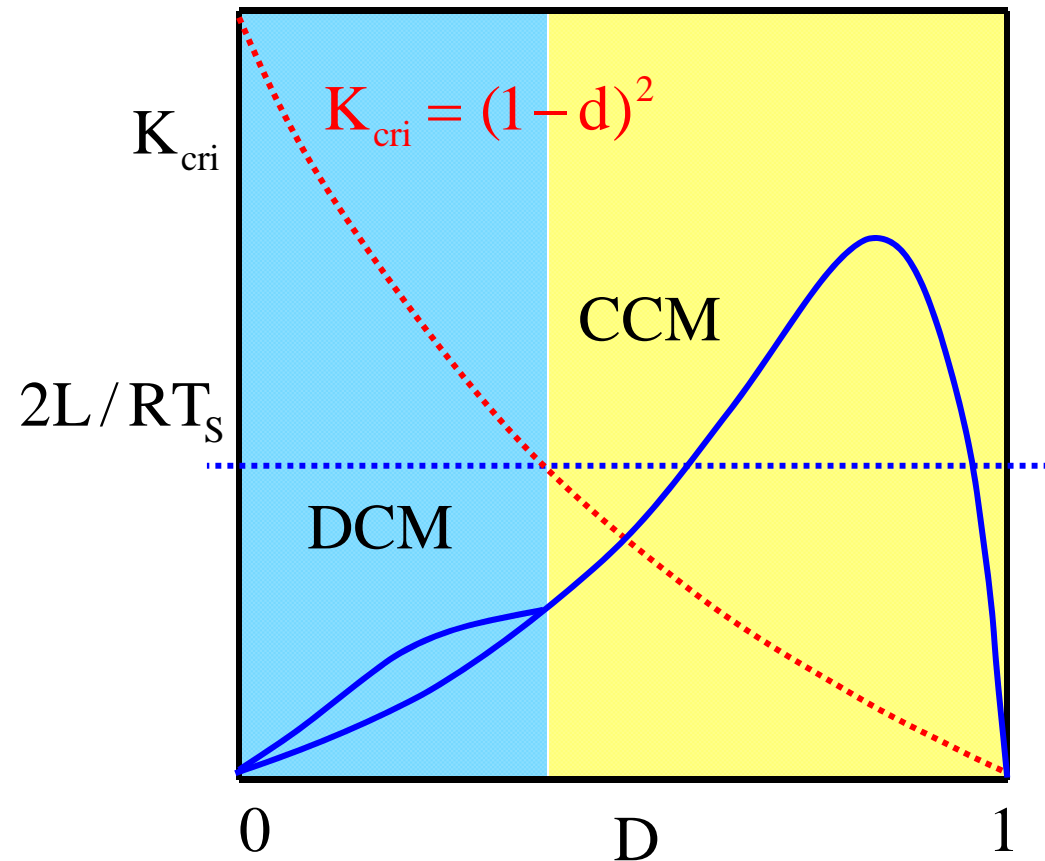
Flyback Converter – Border Between DCM & CCM



Graphical Determination of DCM and CCM

Switched Mode Power Conversion

DCM Operation – Salient Features

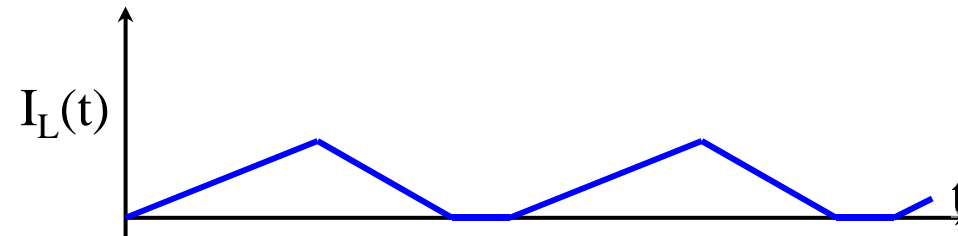

Zero (Low) Turn-on Loss

Soft Diode Recovery

Low Circuit Inductance

High Inductor Ripple

Inductor Current