

Switched Mode Power Conversion

Prior Art

How was Power Conversion Done


before the Introduction of Electronic Switches?

Switched Mode Power Conversion

Prior Art

DC-DC Converters

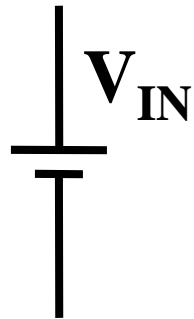A DC Voltage Source of V_{IN} is Available




Switched Mode Power Conversion

Prior Art

DC-DC Converters

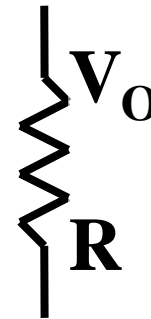A Resistive Load Requires a Voltage of V_o





Switched Mode Power Conversion

Prior Art

DC-DC Converters

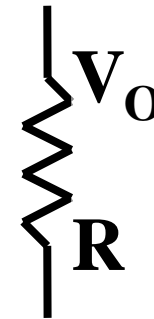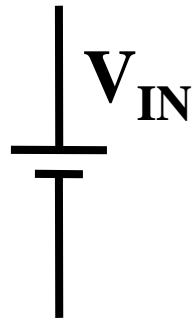**How to Deliver V_O to the Load from
A Source Voltage of V_{IN} ?**




Switched Mode Power Conversion

Prior Art

DC-DC Converters

Conceptual Solution

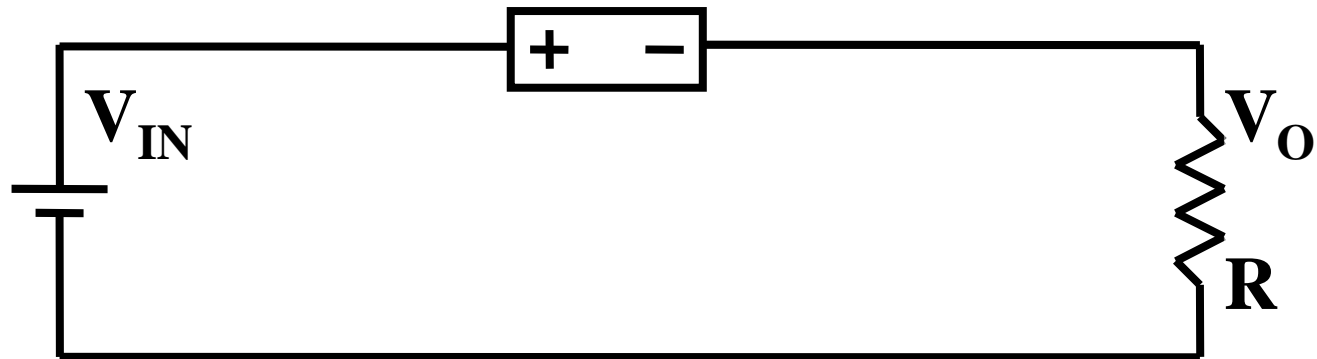


Drop the Excess Voltage in a Series Element

Switched Mode Power Conversion

Prior Art

DC-DC Converters

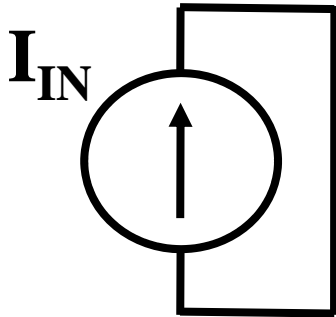A DC Current Source of I_{IN} is Available




Switched Mode Power Conversion

Prior Art

DC-DC Converters

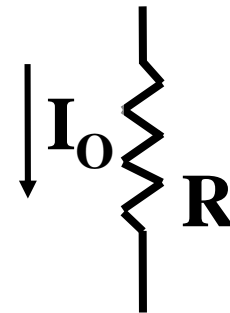A Resistive Load Requires a Current of I_o





Switched Mode Power Conversion

Prior Art

DC-DC Converters

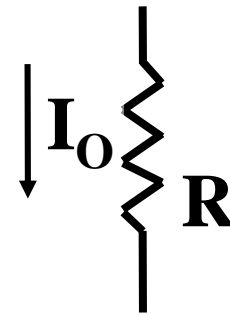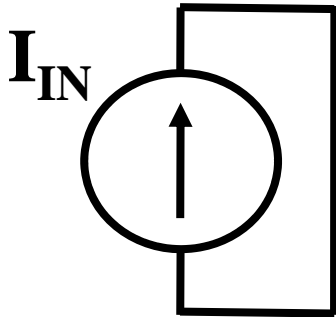**How to Deliver I_O to the Load from
A Source Current of I_{IN} ?**




Switched Mode Power Conversion

Prior Art

DC-DC Converters

Conceptual Solution

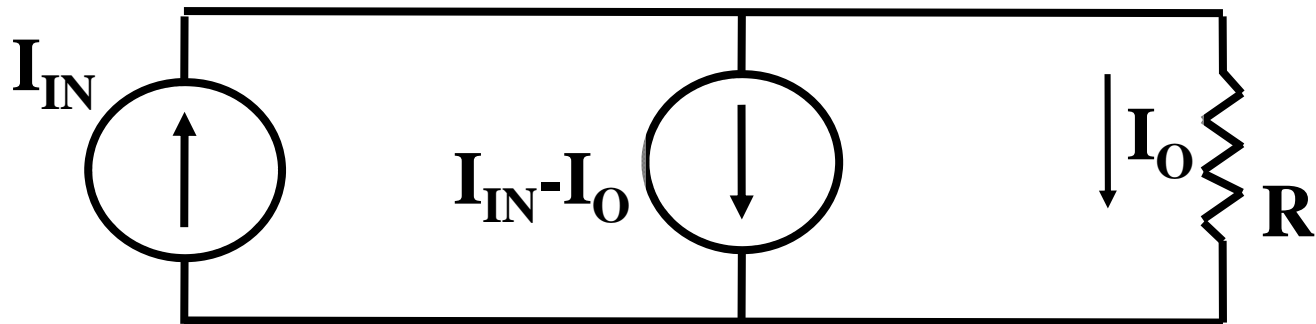


Divert the Excess Current in a Shunt Element

Switched Mode Power Conversion

Prior Art

DC-DC Converters

Conceptual Solution

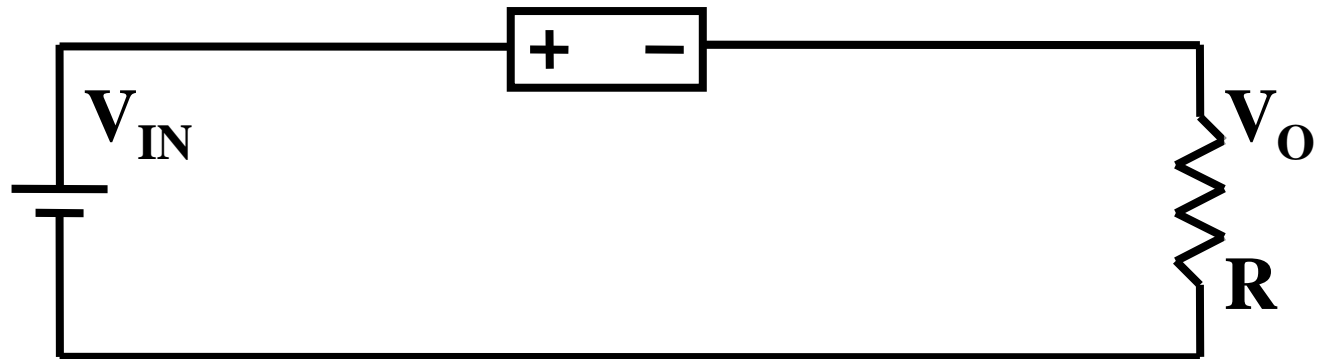


Drop the Excess Voltage in a Series Element

Switched Mode Power Conversion

Prior Art

DC-DC Converters

Circuit Model

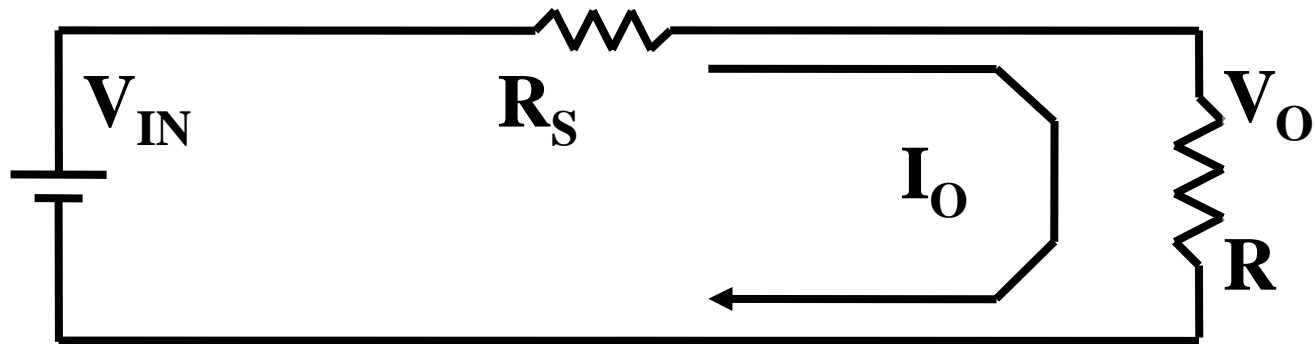

Drop the Excess Voltage in a Series Resistor


Switched Mode Power Conversion

Prior Art

Selection of R_s

$$V_O = V_{IN} \frac{R}{R + R_s}$$
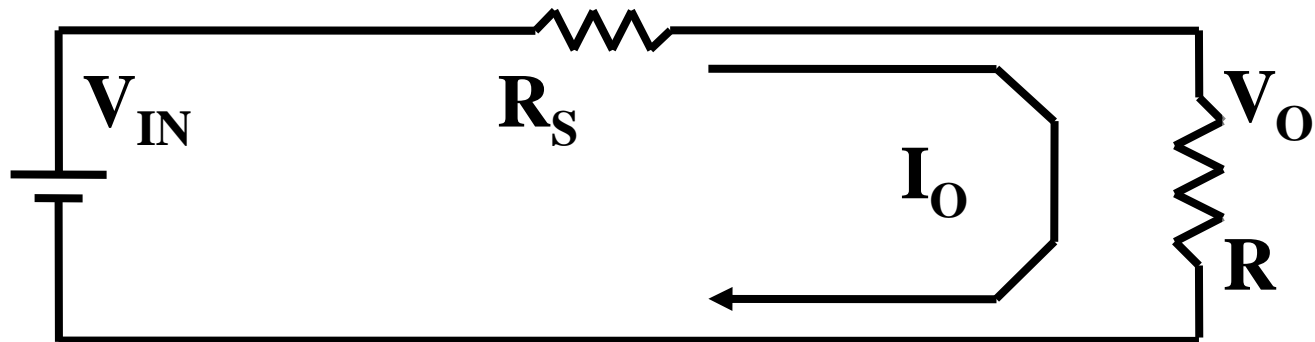
$$R_s = R \left(\frac{V_{IN}}{V_O} - 1 \right)$$




Switched Mode Power Conversion

Prior Art

Efficiency of Power Conversion
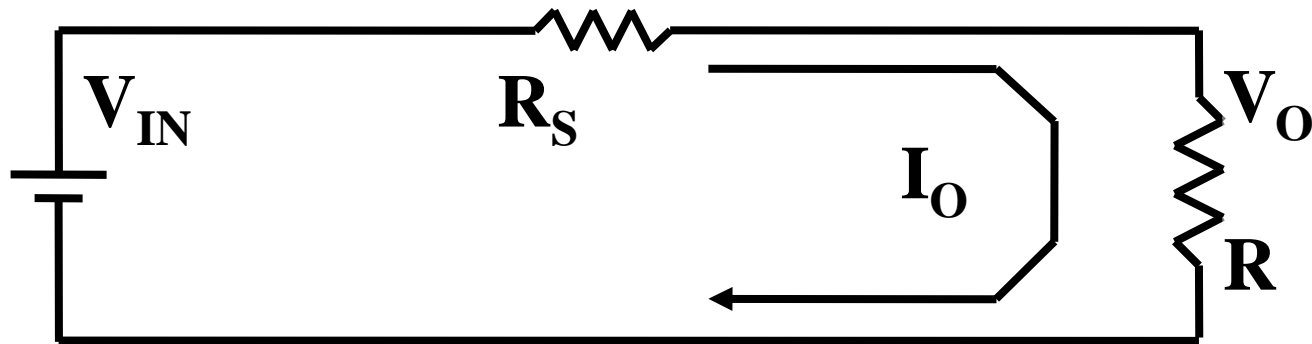
$$\eta = \frac{P_O}{P_{IN}} = \frac{V_O I_O}{V_{IN} I_O} = \frac{V_O}{V_{IN}}$$




At Low Ratio of Conversion η is very Poor

Switched Mode Power Conversion

Prior Art

DC-DC Converters

Conceptual Solution

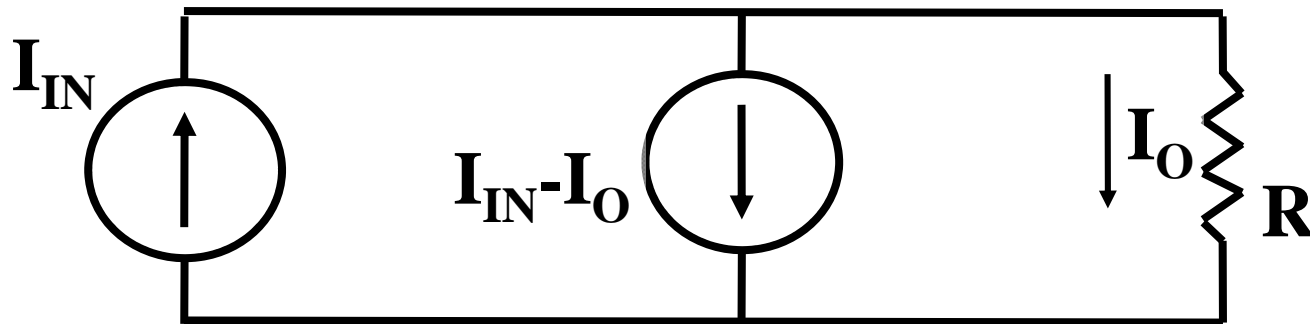


Divert the Excess Current in a Shunt Element

Switched Mode Power Conversion

Prior Art

DC-DC Converters

Circuit Model

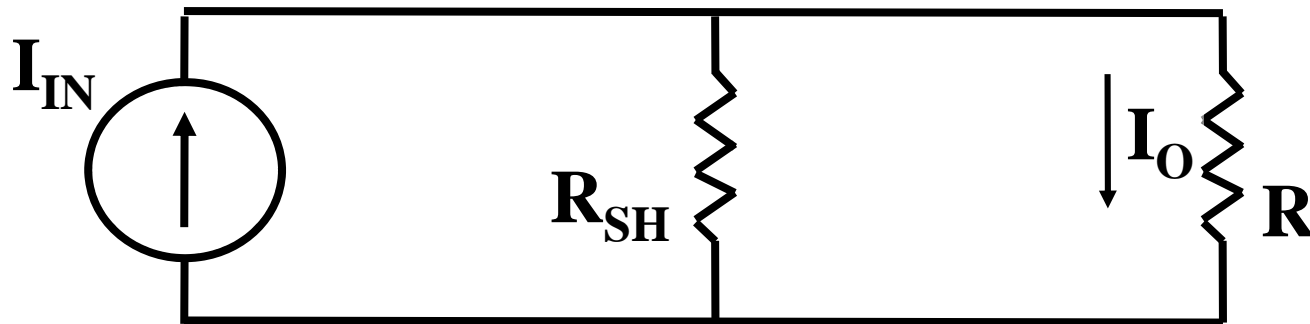

Divert the Excess Current in a Shunt Resistance


Switched Mode Power Conversion

Prior Art

Selection of R_{SH}

$$I_O = I_{IN} \frac{R_{SH}}{R + R_{SH}}$$
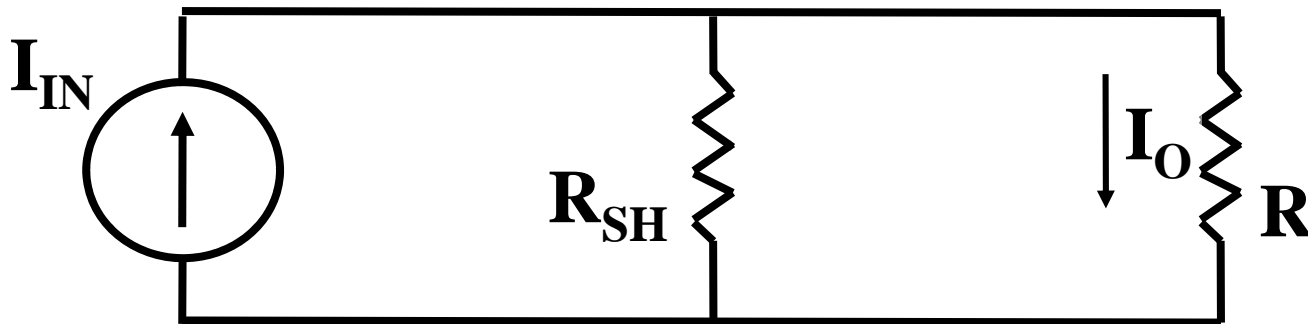
$$R_{SH} = \frac{R}{\left(\left(I_{IN} / I_O\right) - 1\right)}$$




Switched Mode Power Conversion

Prior Art

Efficiency of Power Conversion
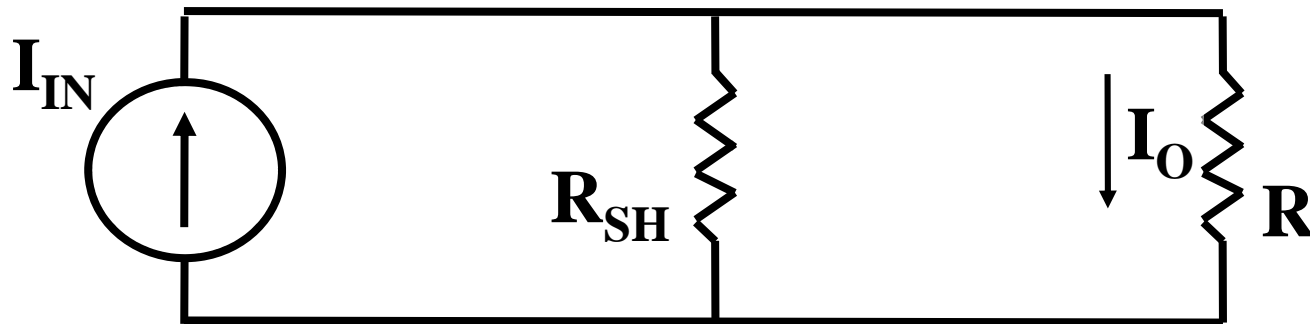
$$\eta = \frac{P_O}{P_{IN}} = \frac{V_O I_O}{V_{IN} I_{IN}} = \frac{I_O}{I_{IN}}$$




At Low Ratio of Conversion η is very Poor

Switched Mode Power Conversion

Prior Art


General Linear Power Converter

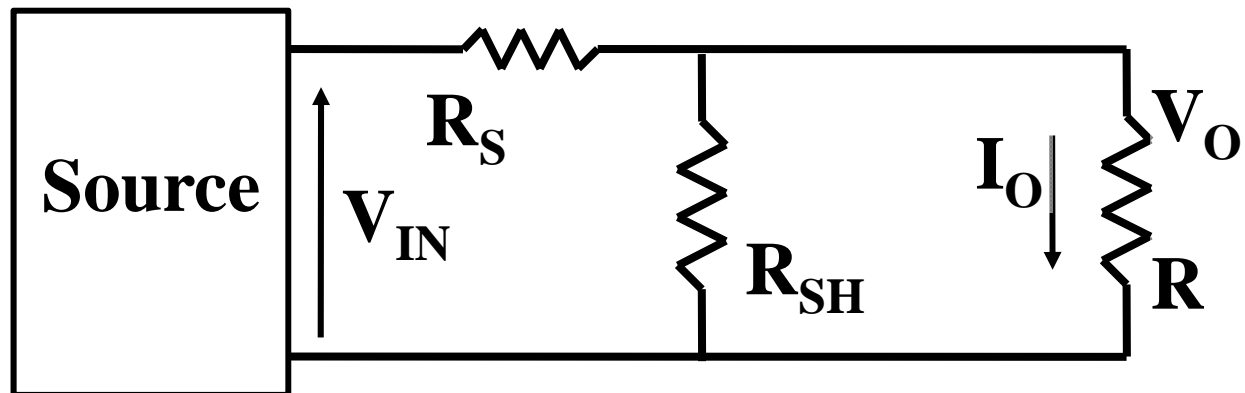

Switched Mode Power Conversion

Prior Art


Shunt Controlled Converter

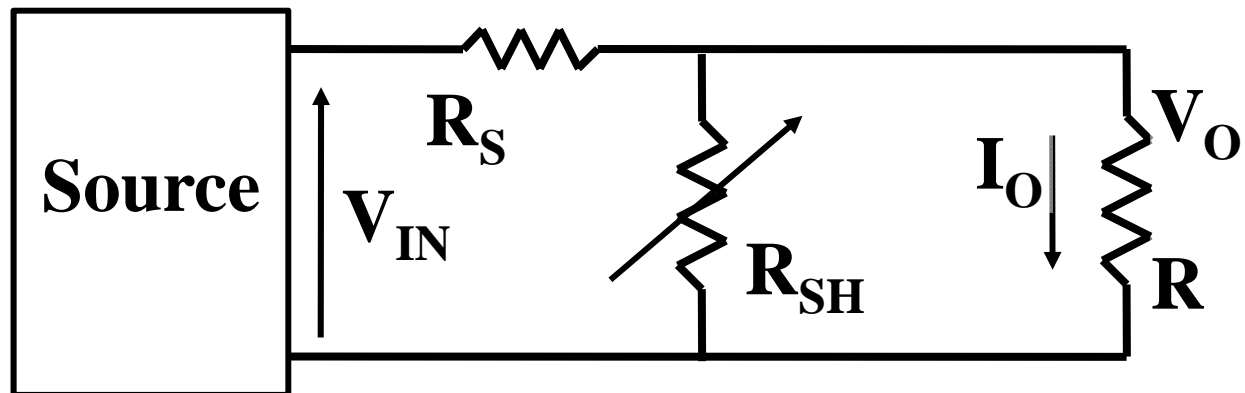

Switched Mode Power Conversion

Prior Art


Series Controlled Converter

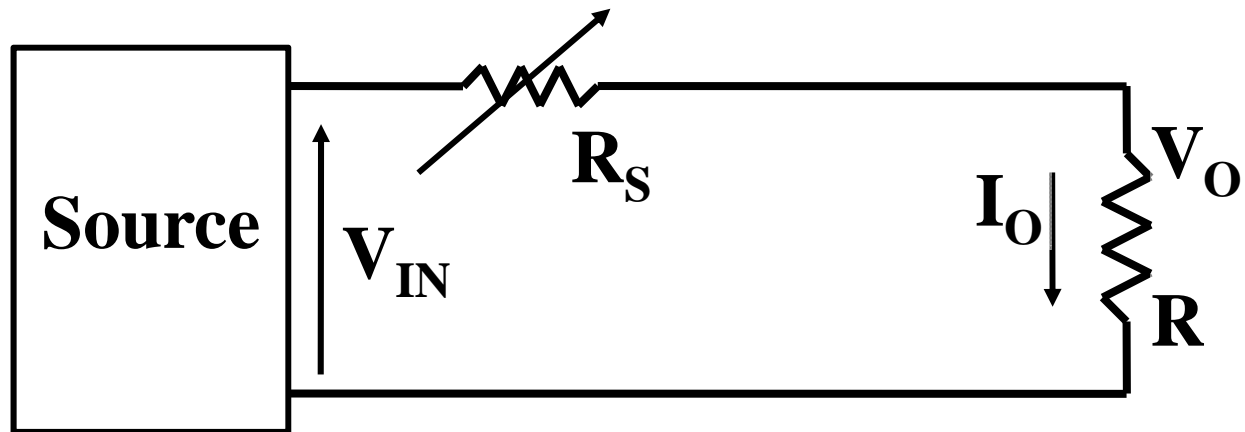

Shunt Controlled Converter

Sample Design


Zener Regulator

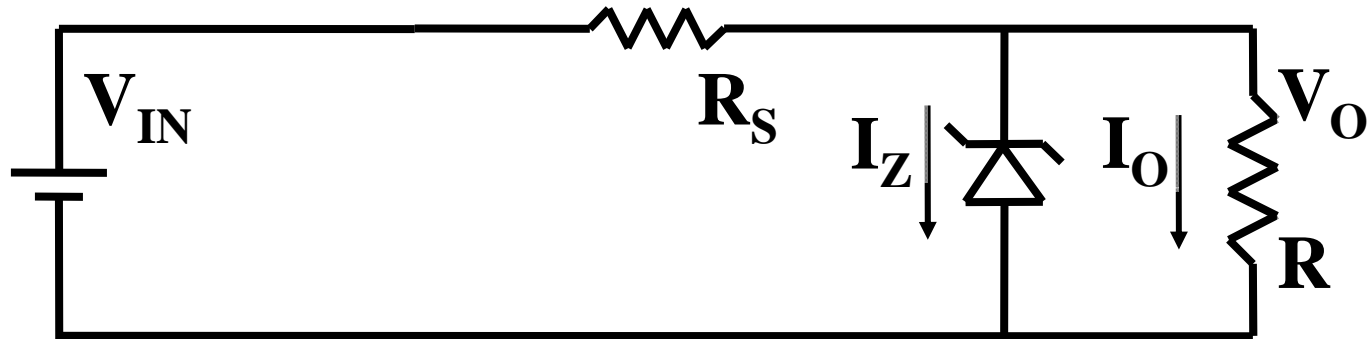

Shunt Controlled Converter

Sample Design



Zener Regulator

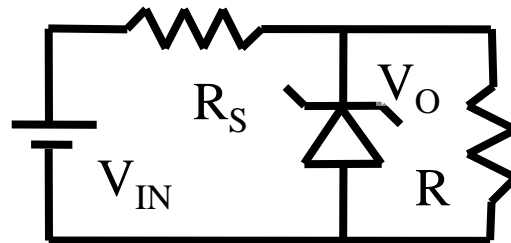

Shunt Controlled Converter

Sample Design



Zener Regulator

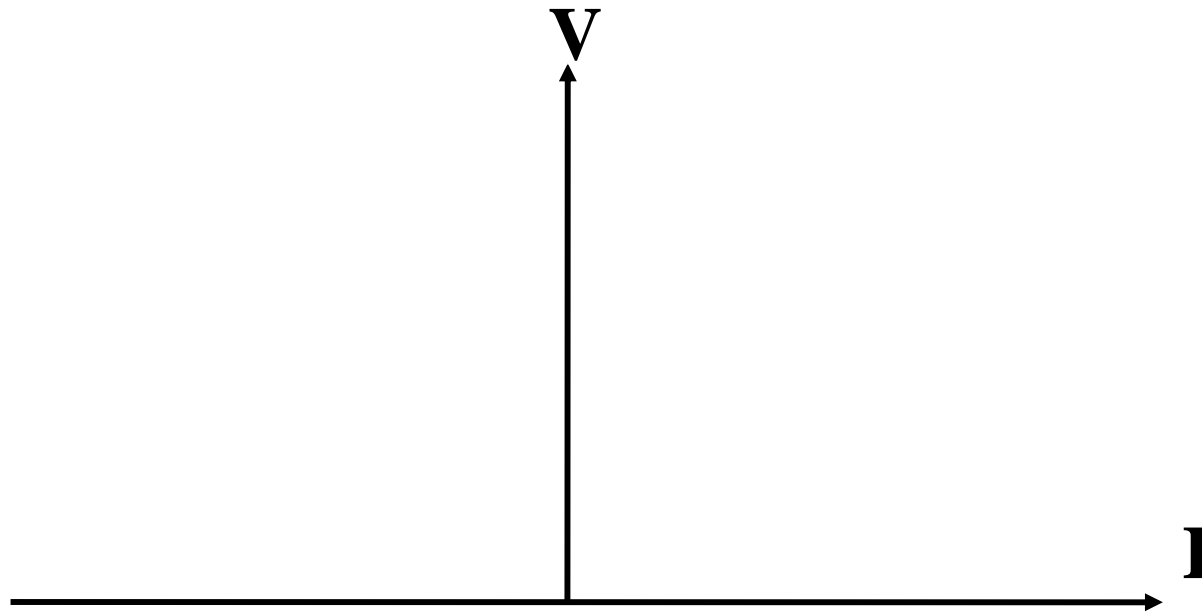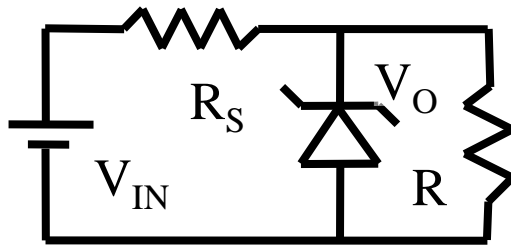

Shunt Controlled Converter

Load Line



Zener Regulator

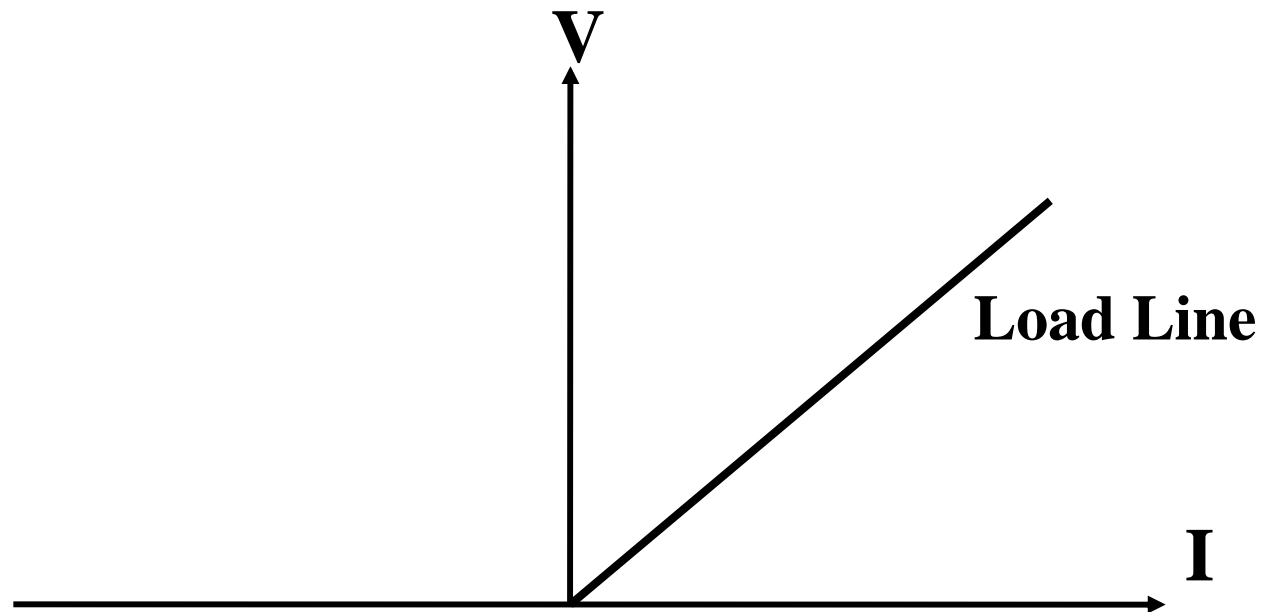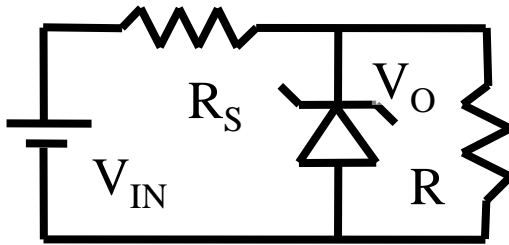

Shunt Controlled Converter

Output Voltage



Zener Regulator

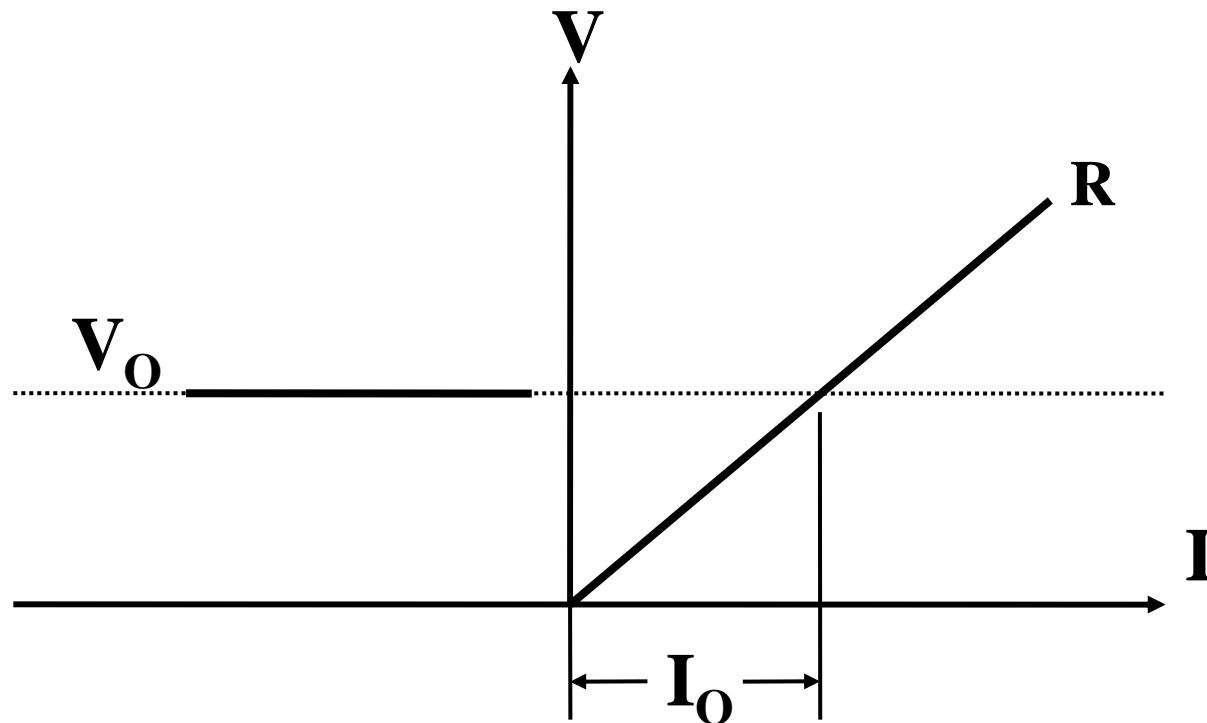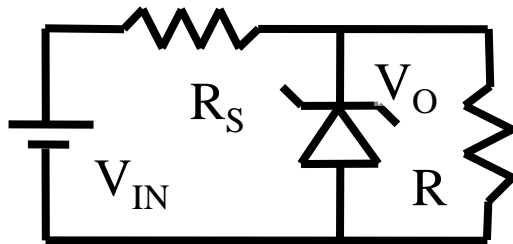

Shunt Controlled Converter

Load Variation



Zener Regulator

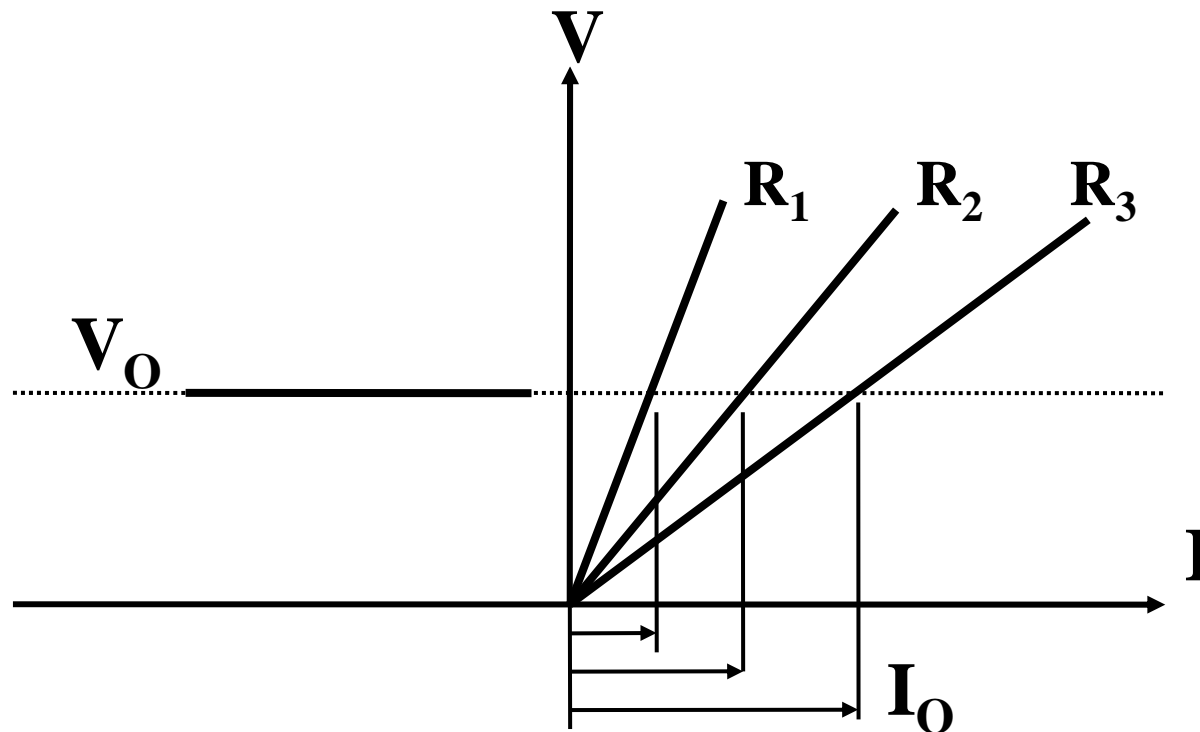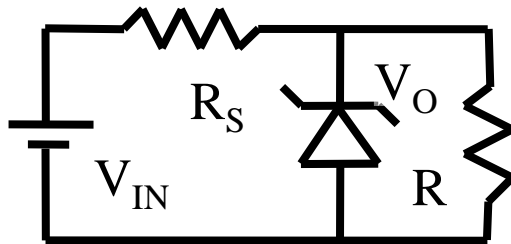

Shunt Controlled Converter

No Load & Full Load Lines



Zener Regulator

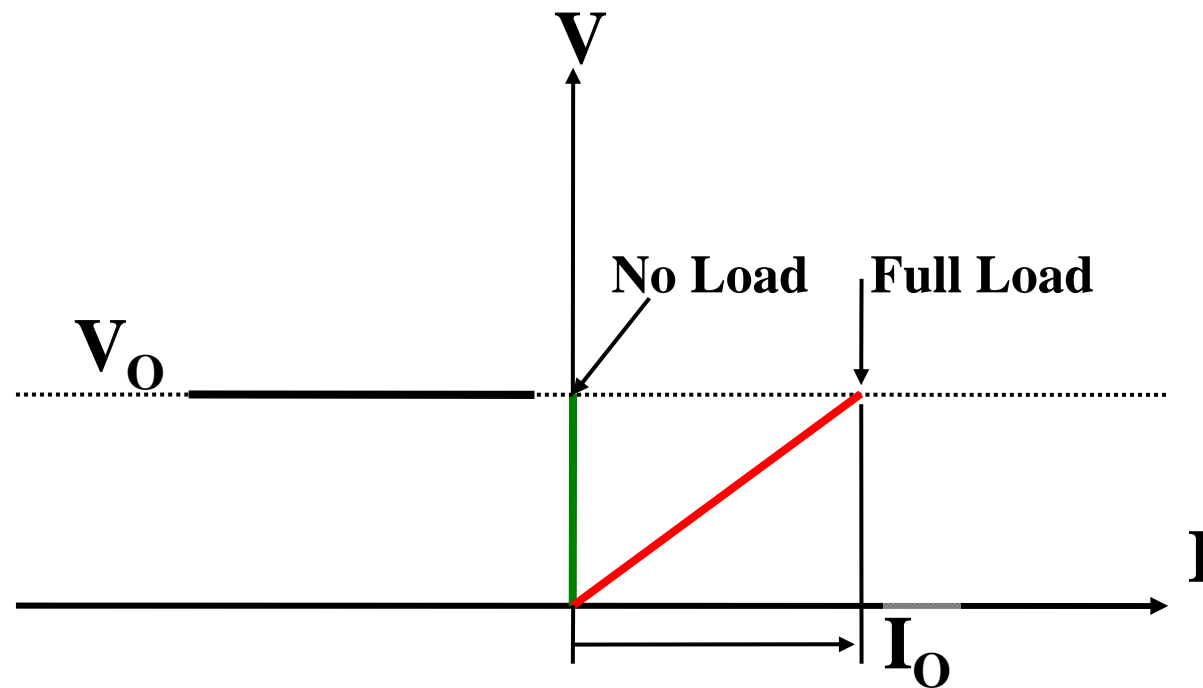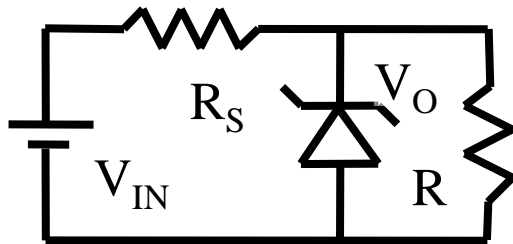

Shunt Controlled Converter

Source Line



Zener Regulator

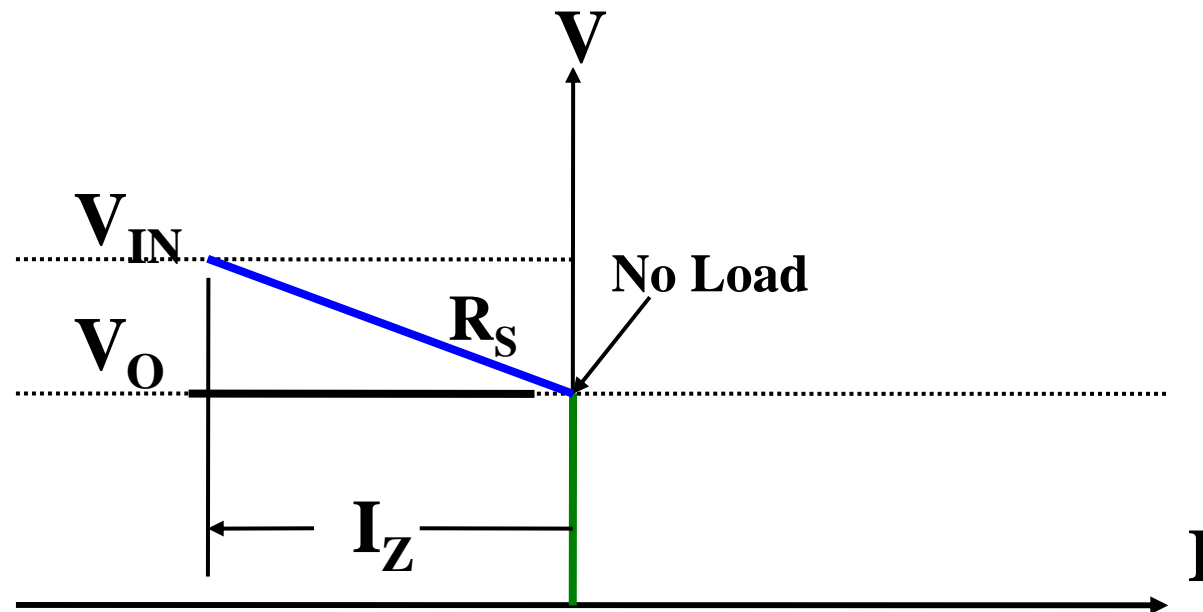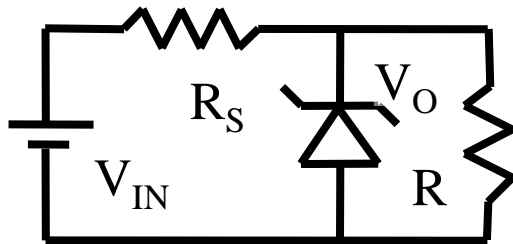

Shunt Controlled Converter

Minimum Zener Current



Zener Regulator

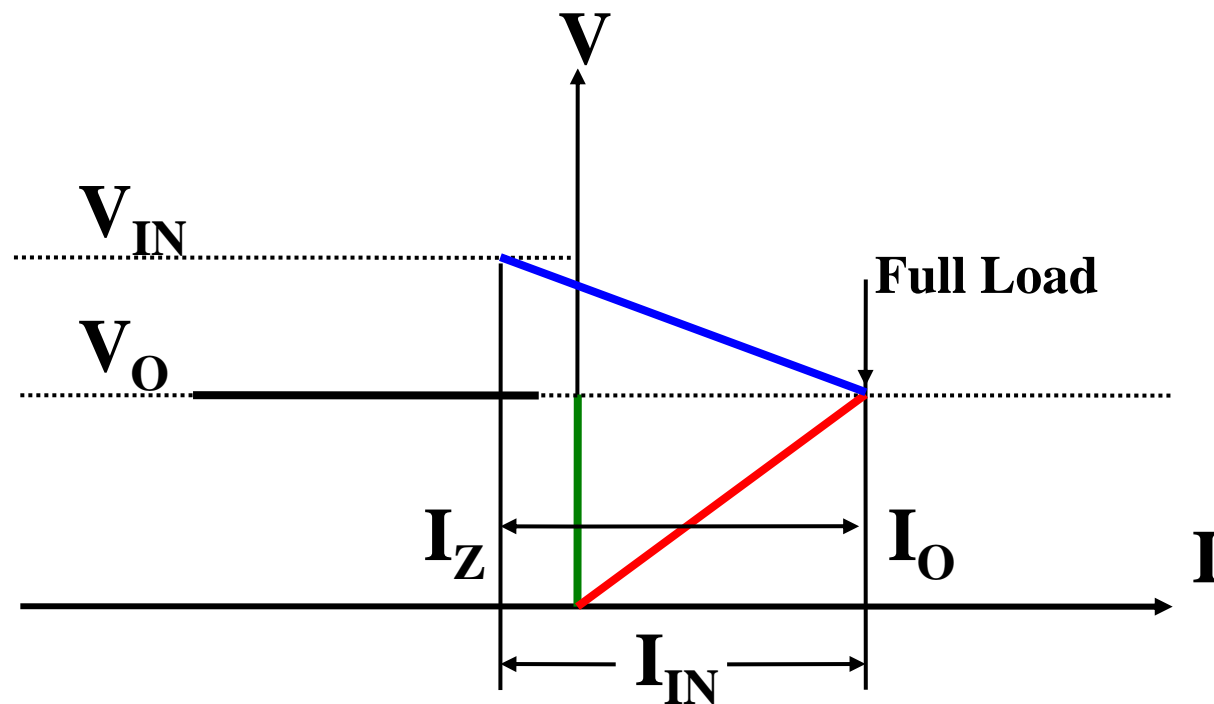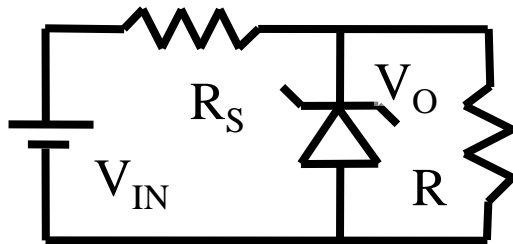

Shunt Controlled Converter

Zener Current Variation



Zener Regulator

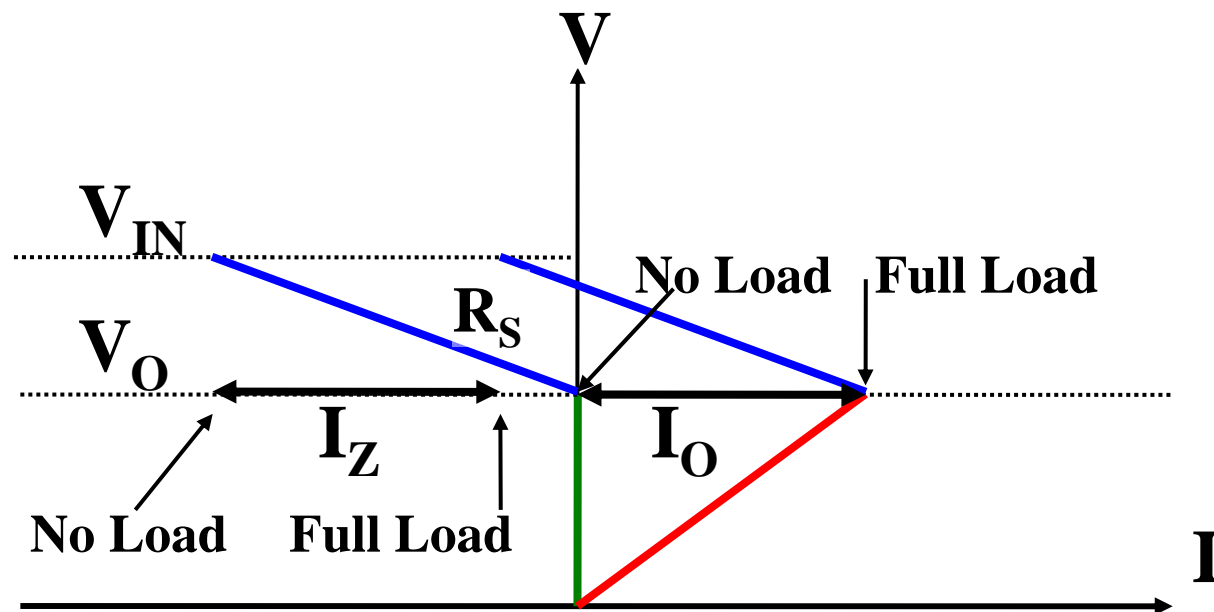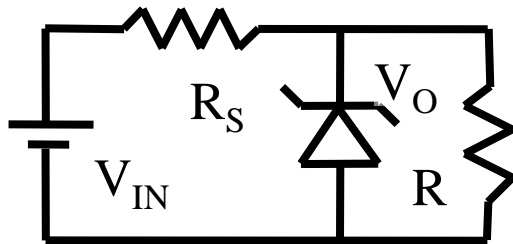

Shunt Controlled Converter

Typical Operating Point



Zener Regulator

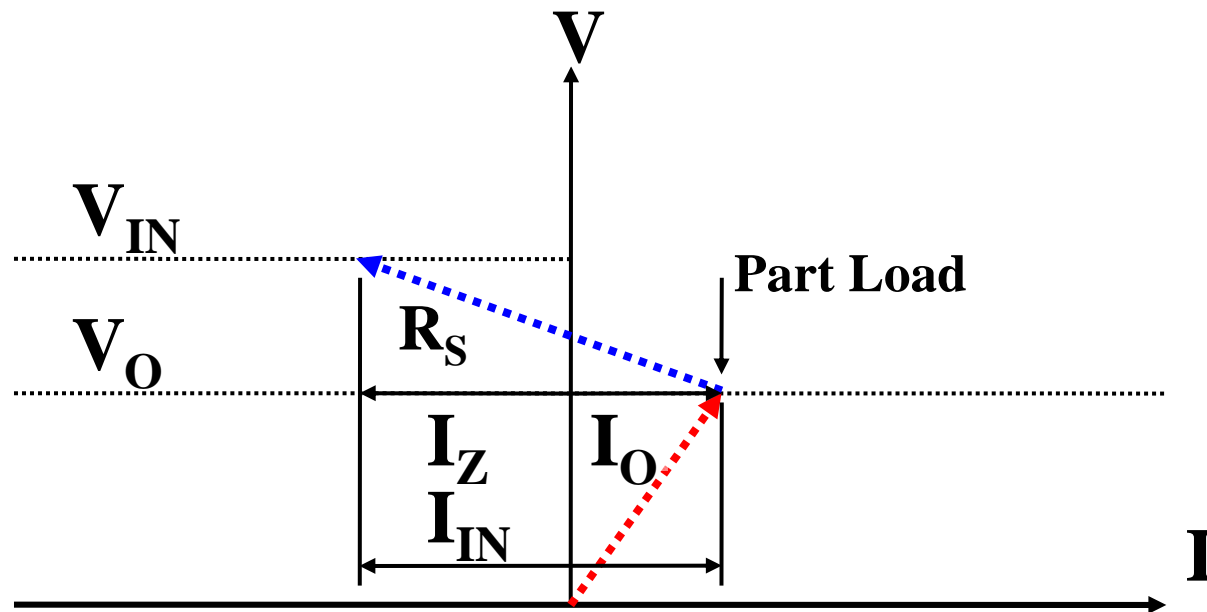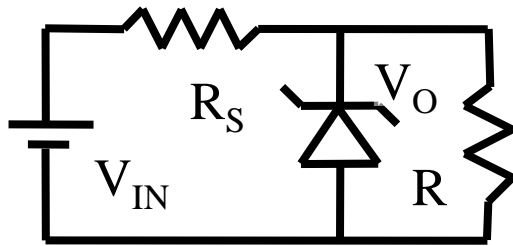

Shunt Controlled Converter

Output Power



Zener Regulator

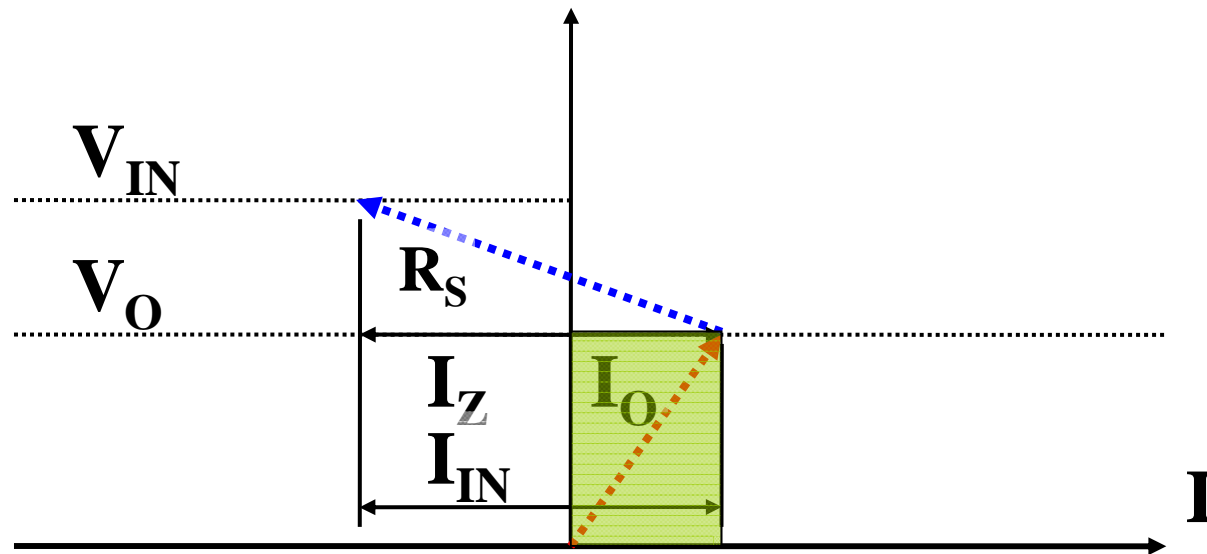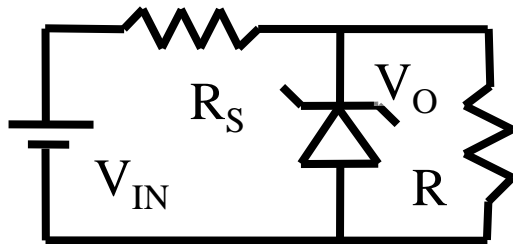

Shunt Controlled Converter

Input Power



Zener Regulator

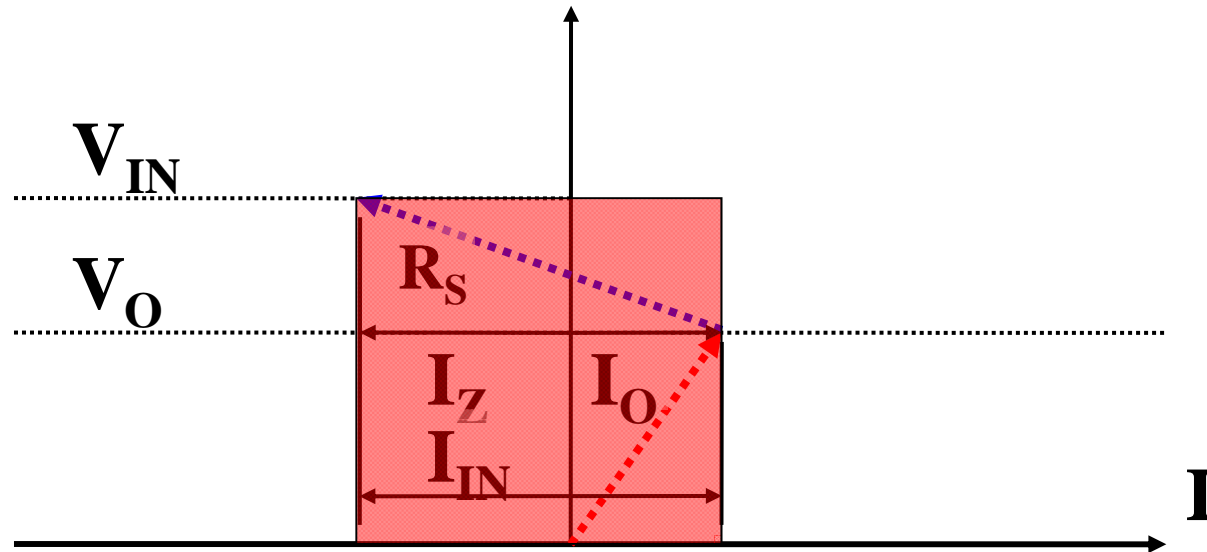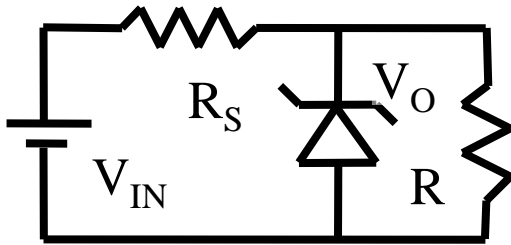

Shunt Controlled Converter

Efficiency



Zener Regulator

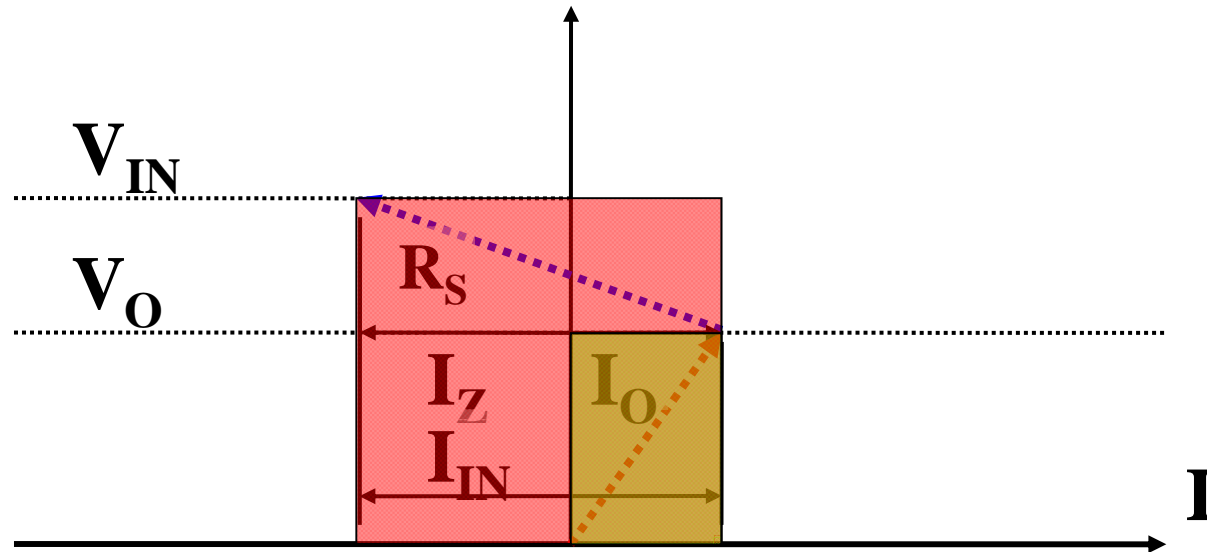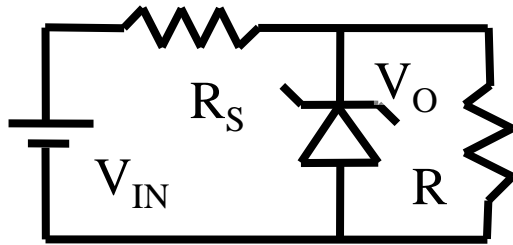

Shunt Controlled Converter

Design Sequence

Zener Regulator

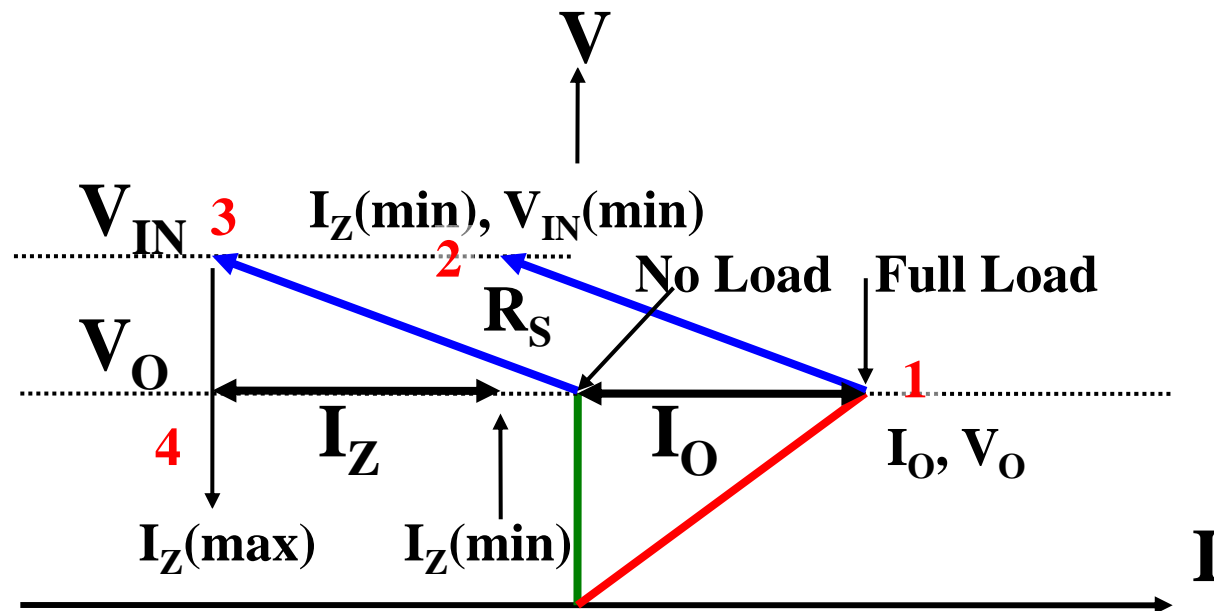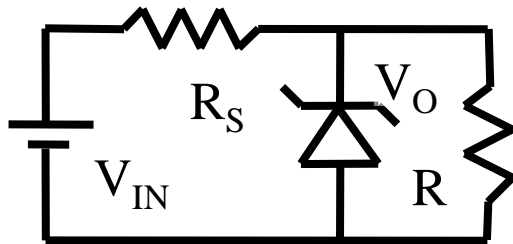


Switched Mode Power Conversion


Prior Art

DC-DC Converters

Series Controlled Converter

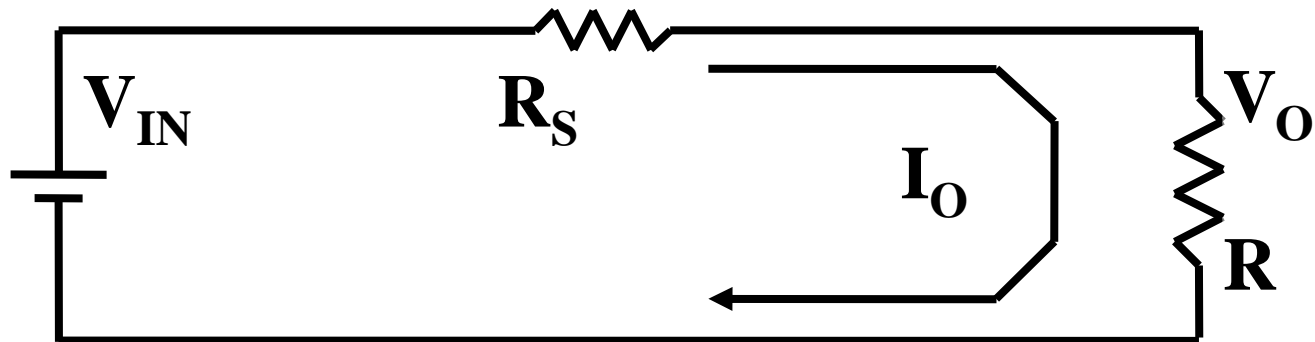


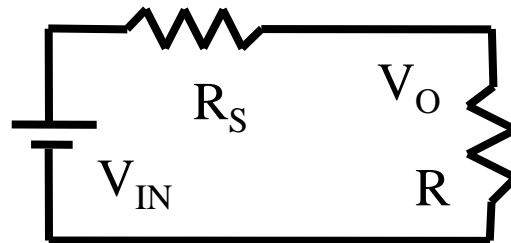
Prior art
Circuit Diagram
Series Controlled Converter





Prior Art

Load Line



Series Controlled Converter

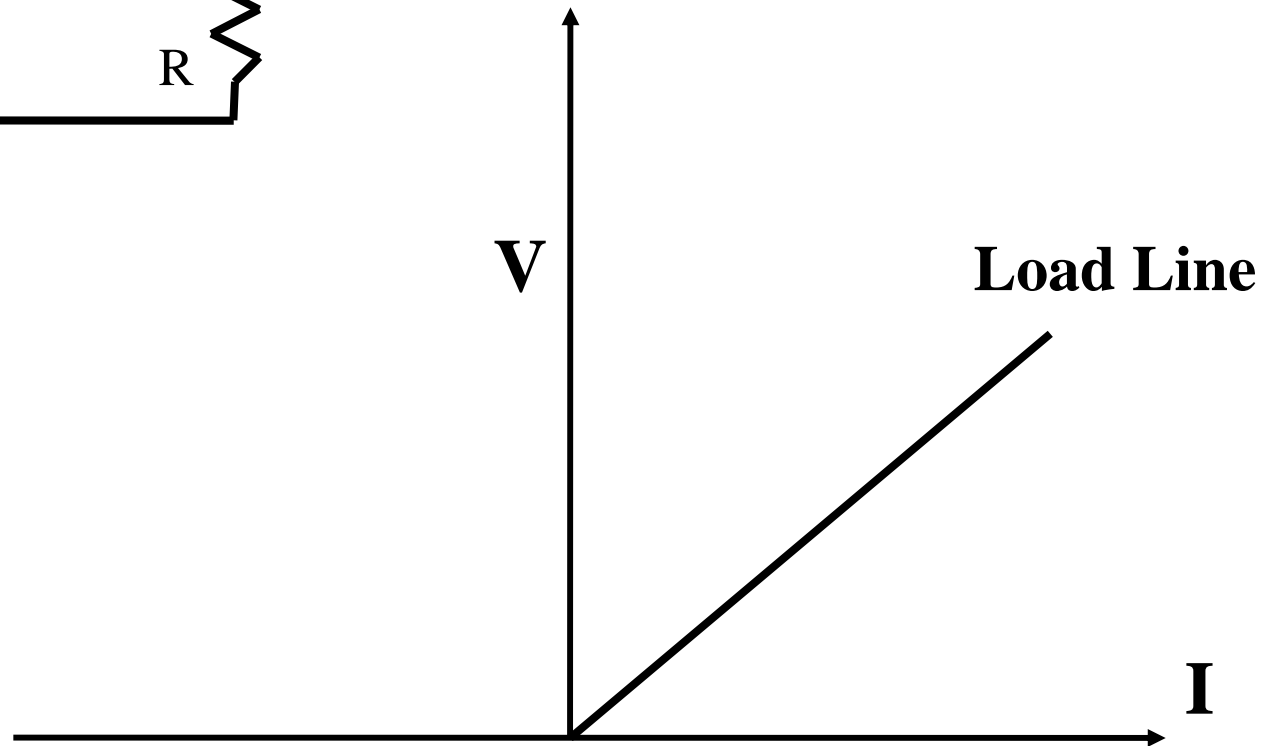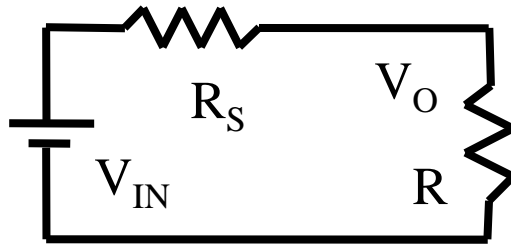

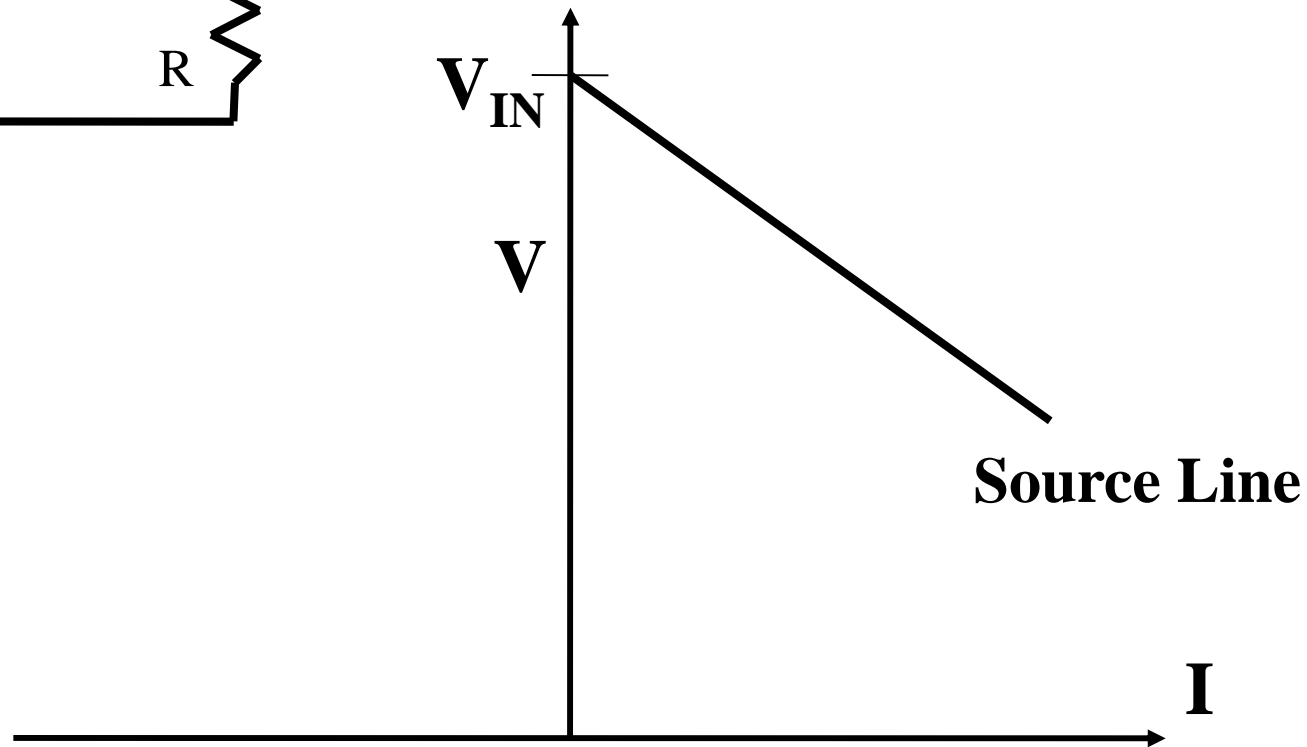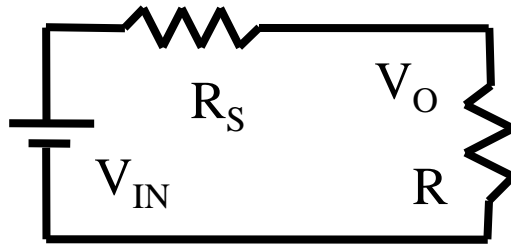Prior Art
Source Line
Series Controlled Converter



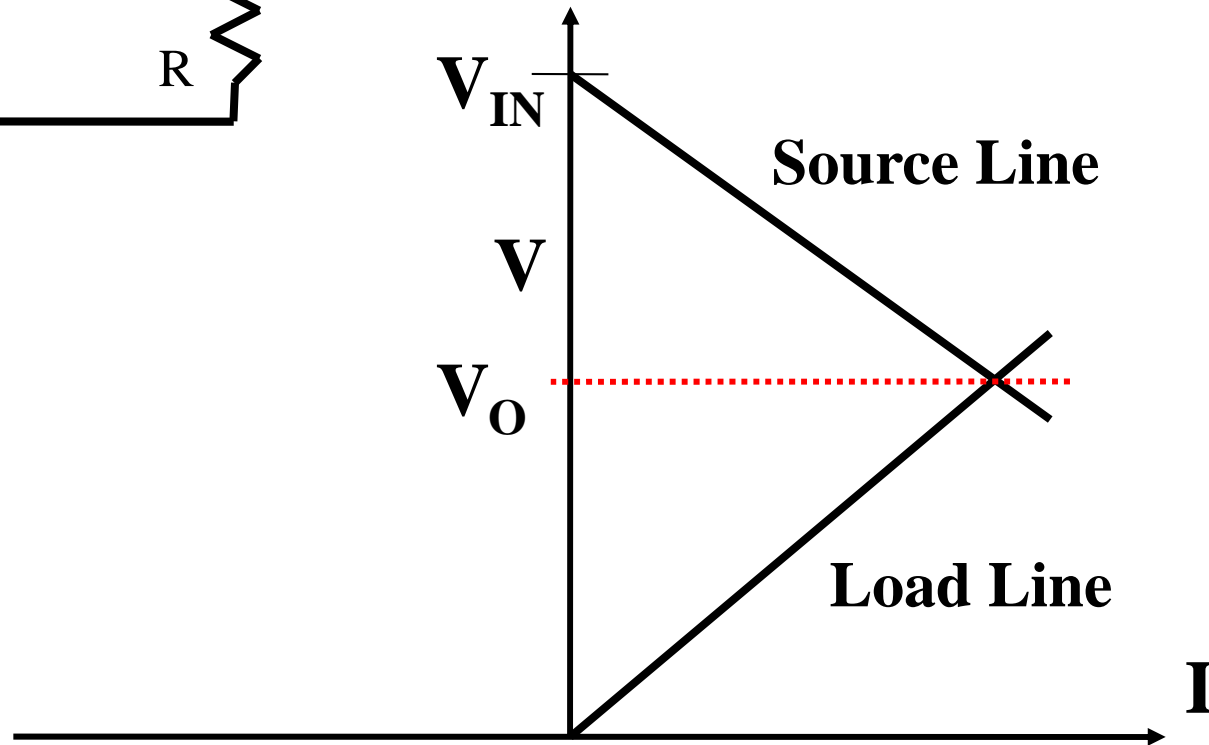
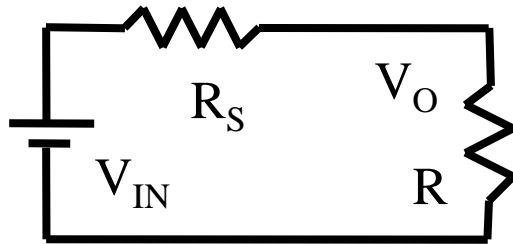
Prior Art
Output Voltage
Series Controlled Converter



Prior Art

Control Strategy



Series Controlled Converter

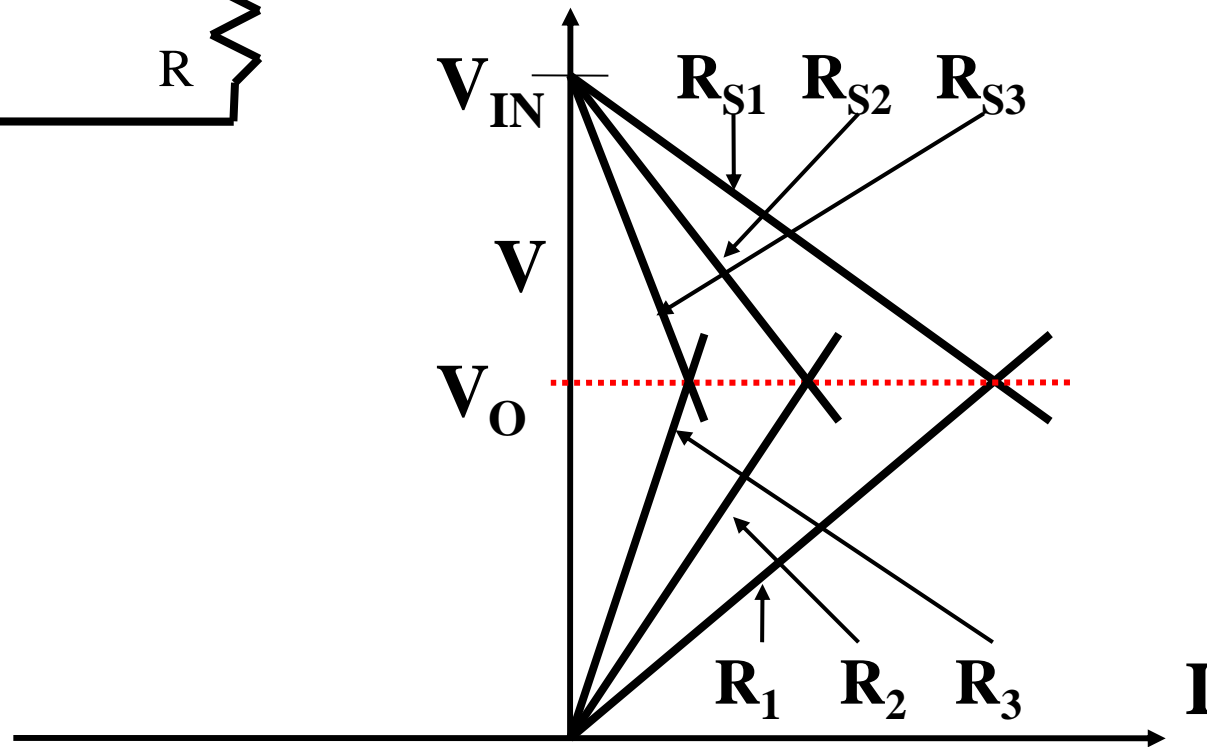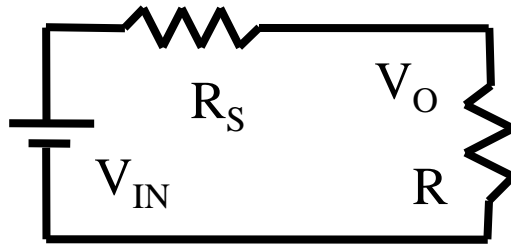

Prior Art

Output Power



Series Controlled Converter

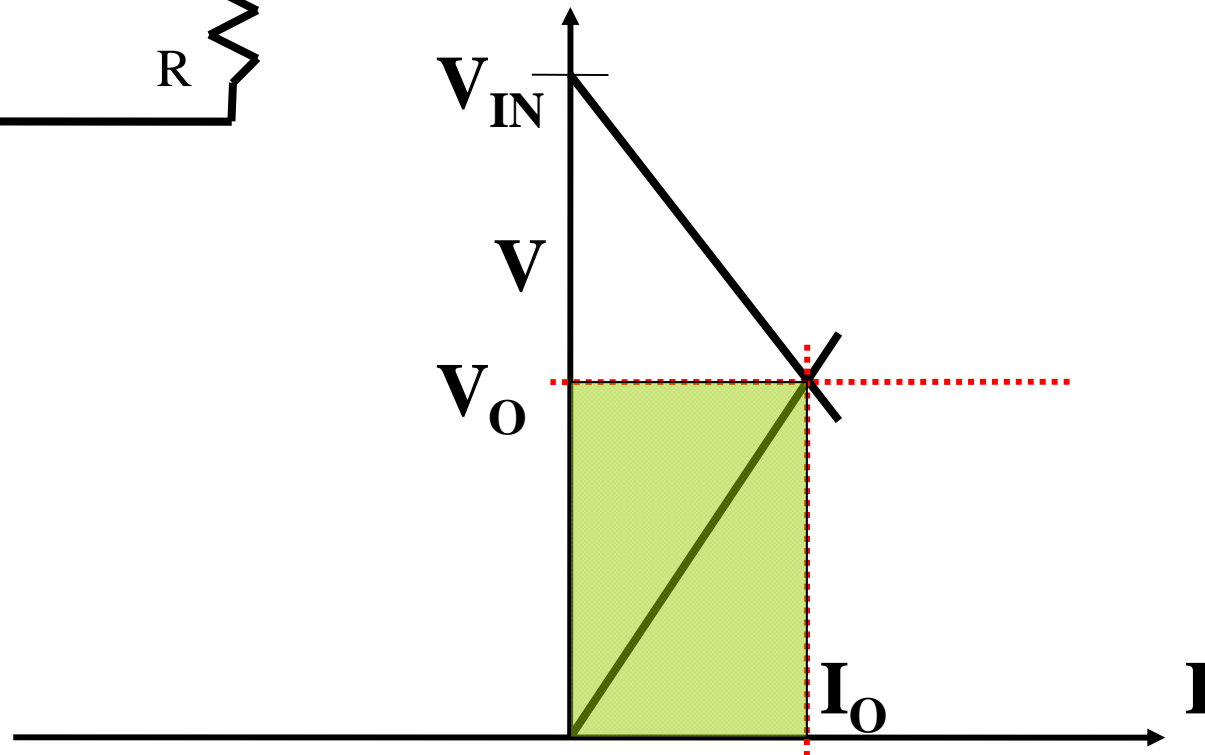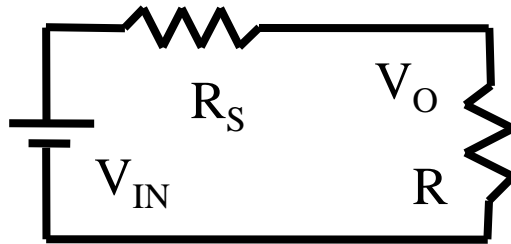

Prior Art

Input Power



Series Controlled Converter

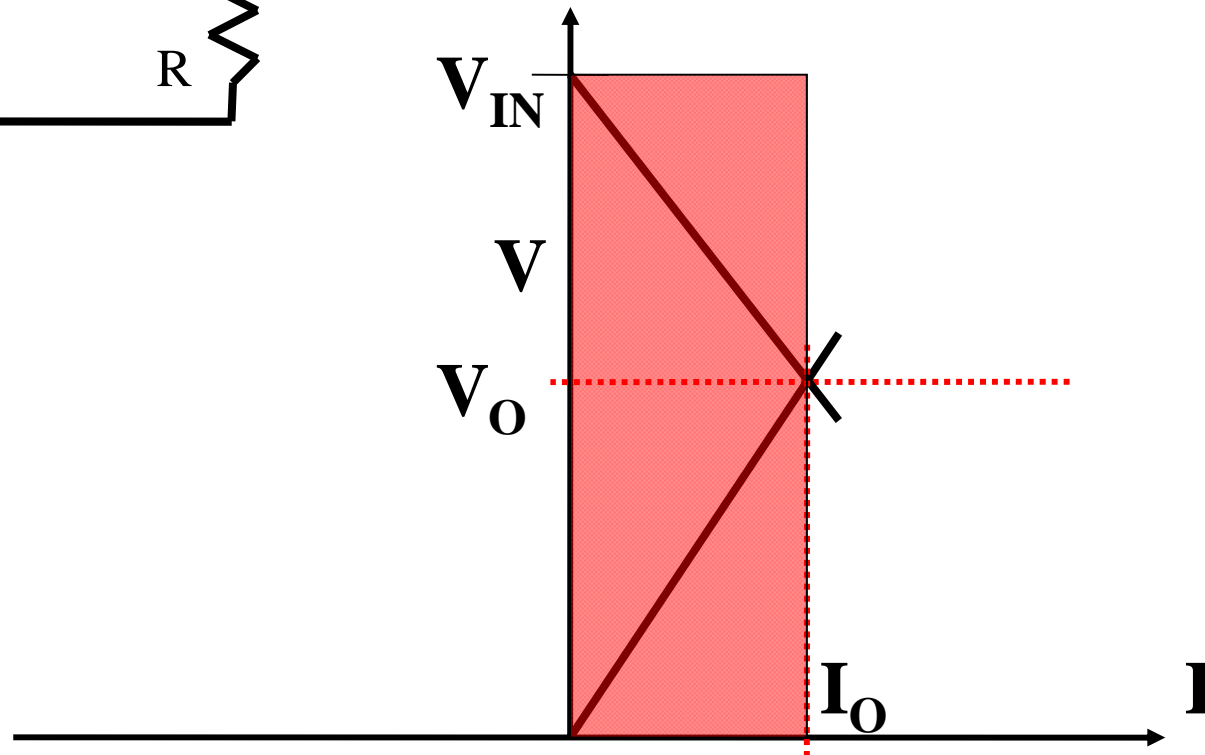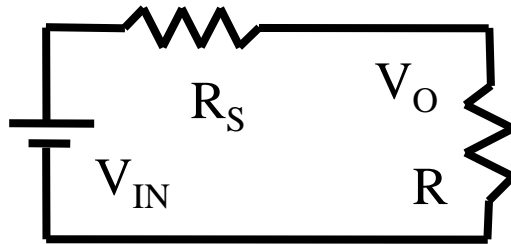

Prior Art

Efficiency



Series Controlled Converter

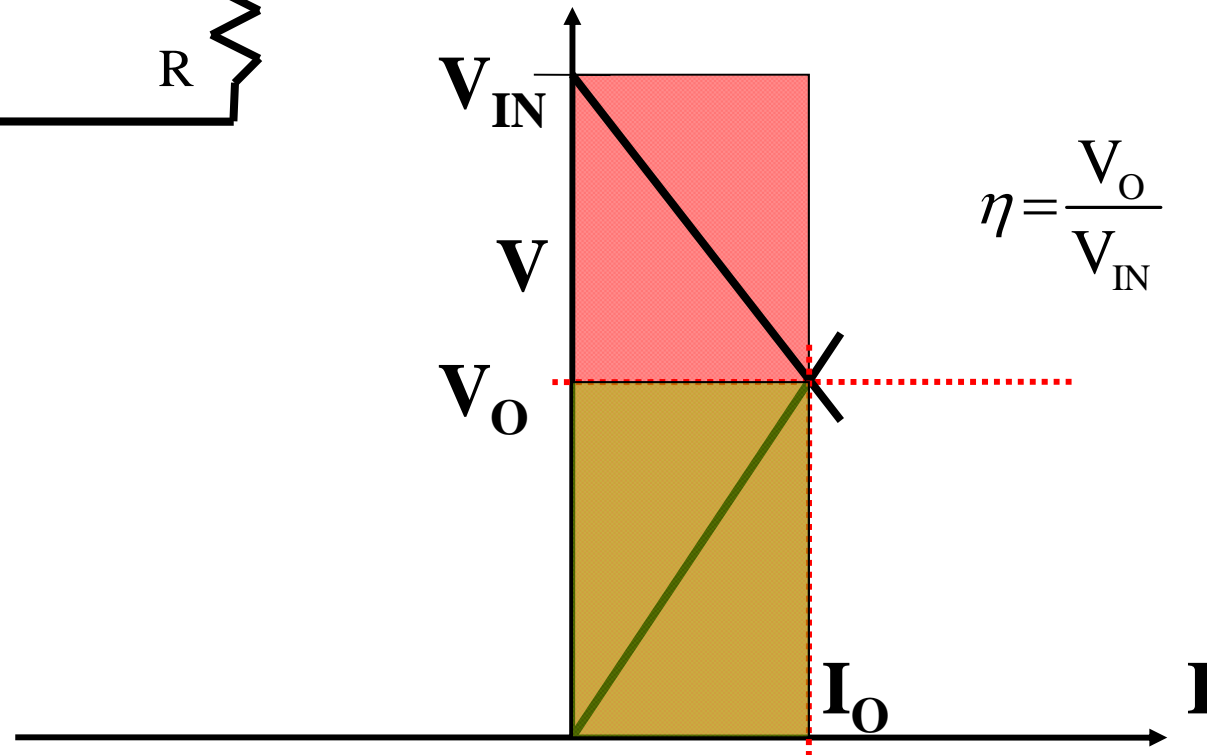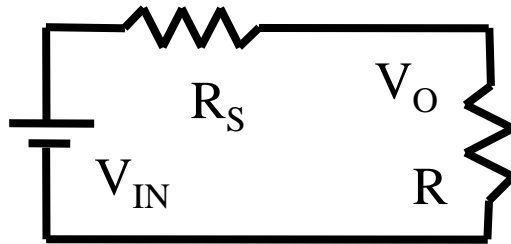

Prior Art

Losses



Series Controlled Converter

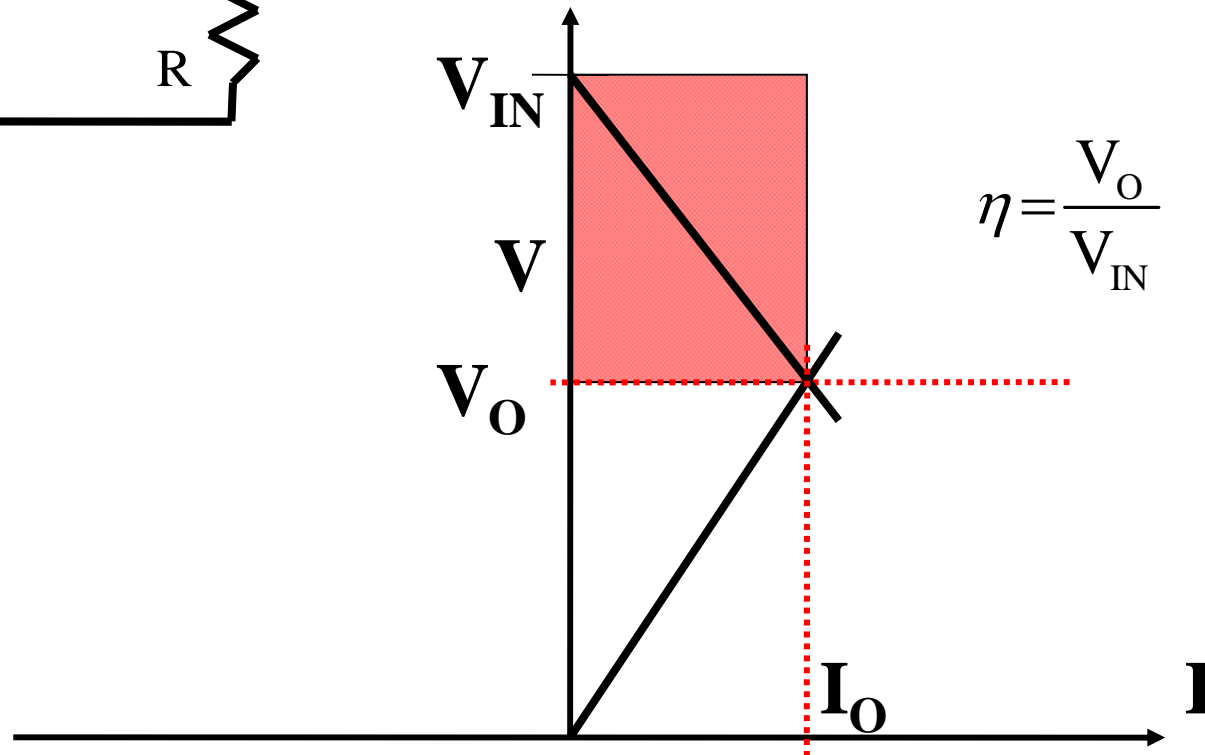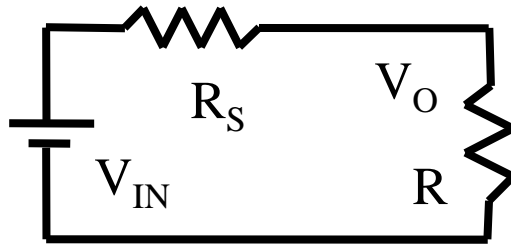

Prior Art

Losses



Series Controlled Converter

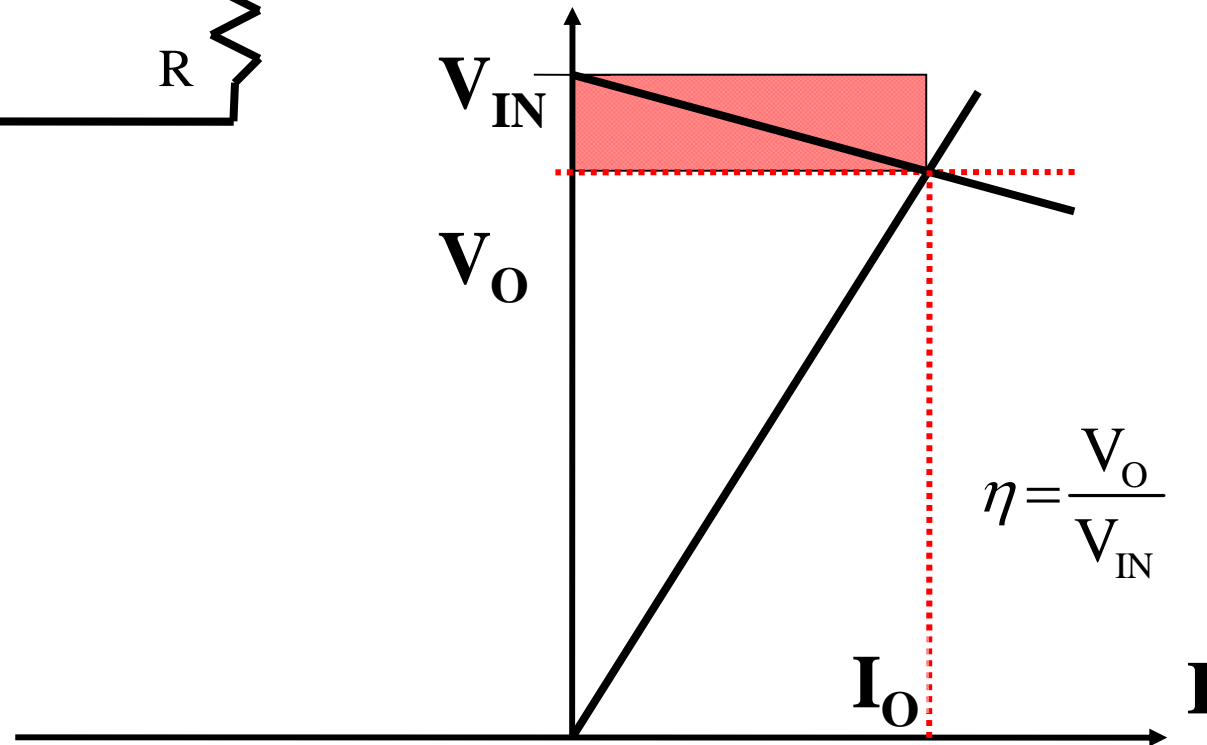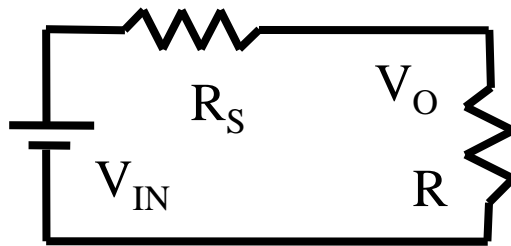

Prior Art



Losses

Series Controlled Converter

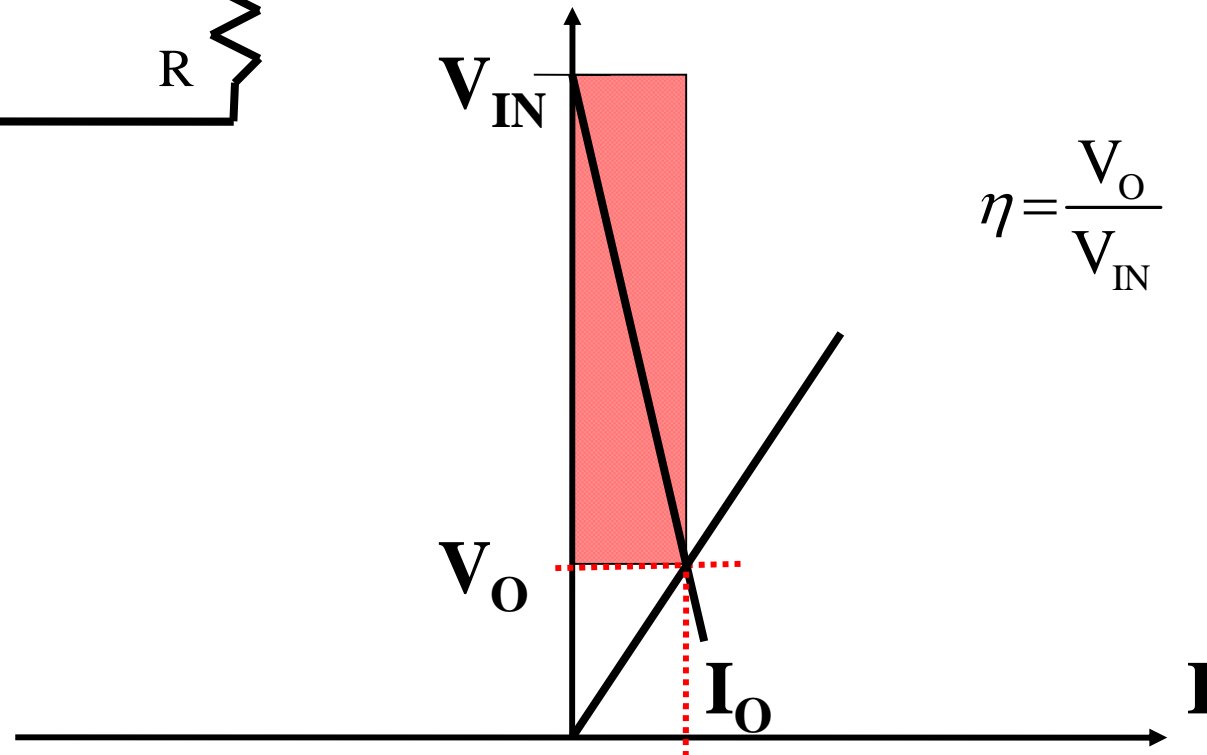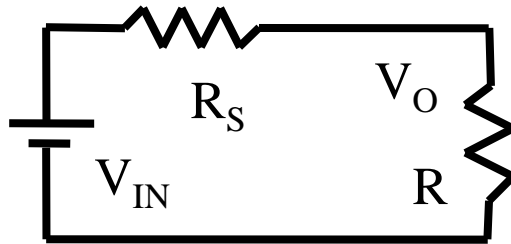




Prior Art

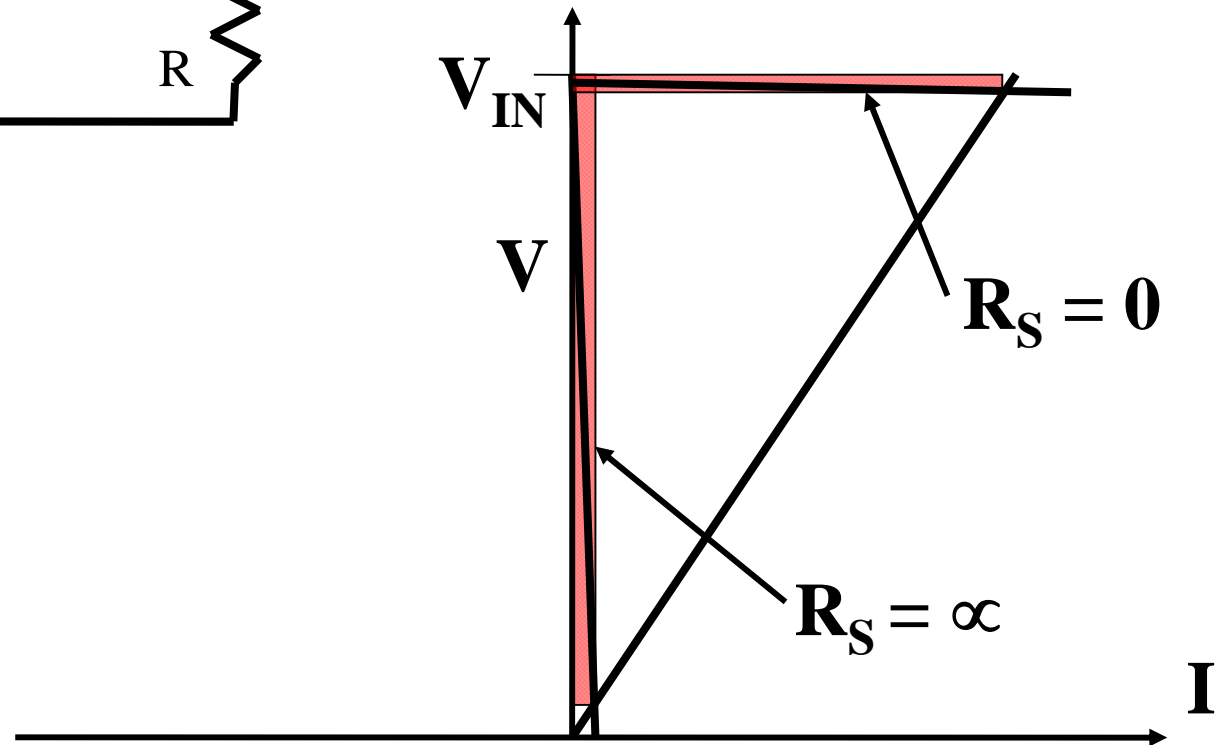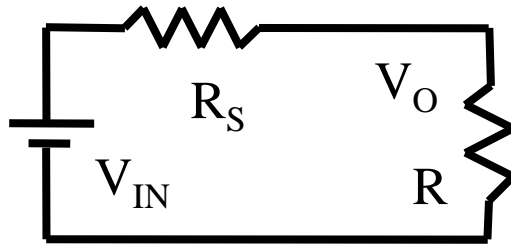Two Low-Loss Conditions Series Controlled Converter



Prior Art

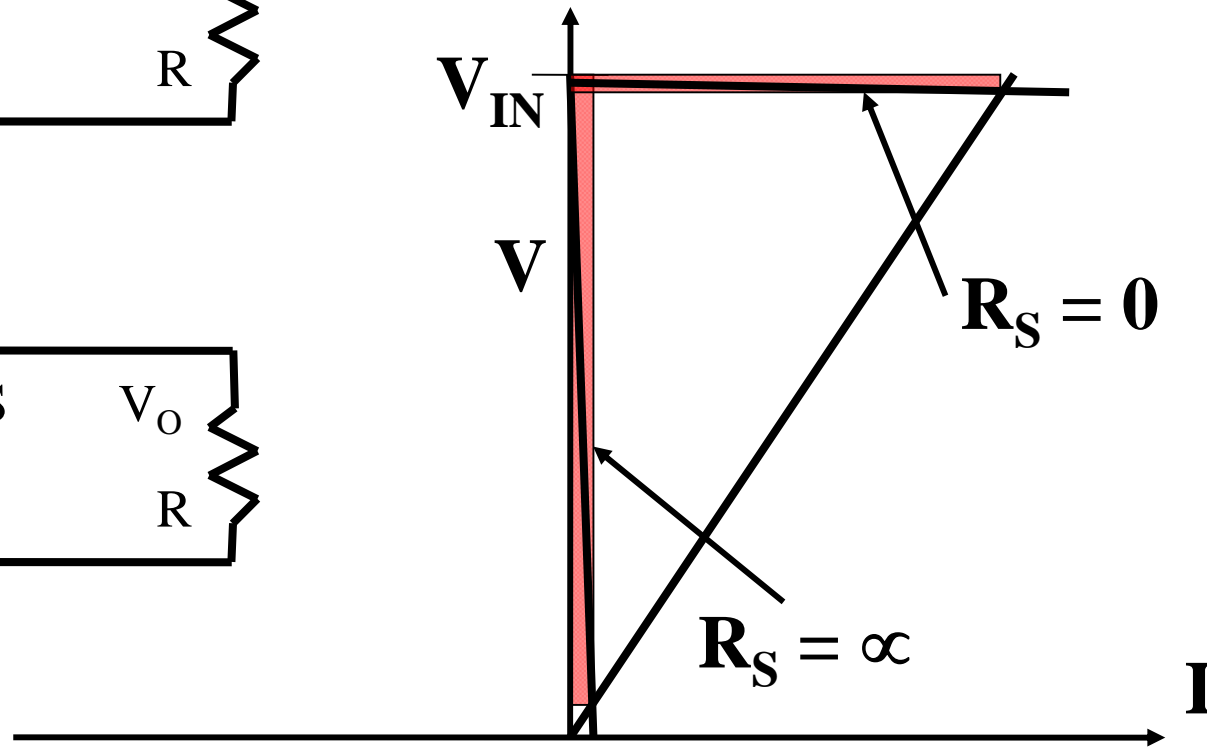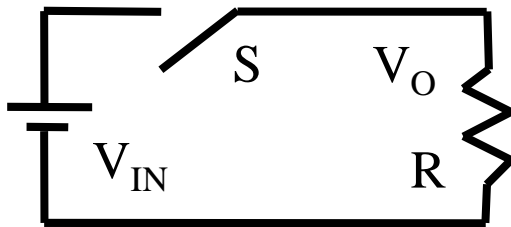
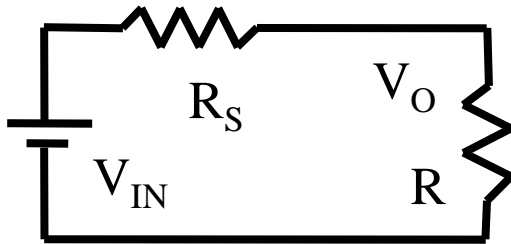
Central Idea of Switch Mode Power Conversion Series Controlled Converter



Prior Art

Another Version



Series Controlled Converter

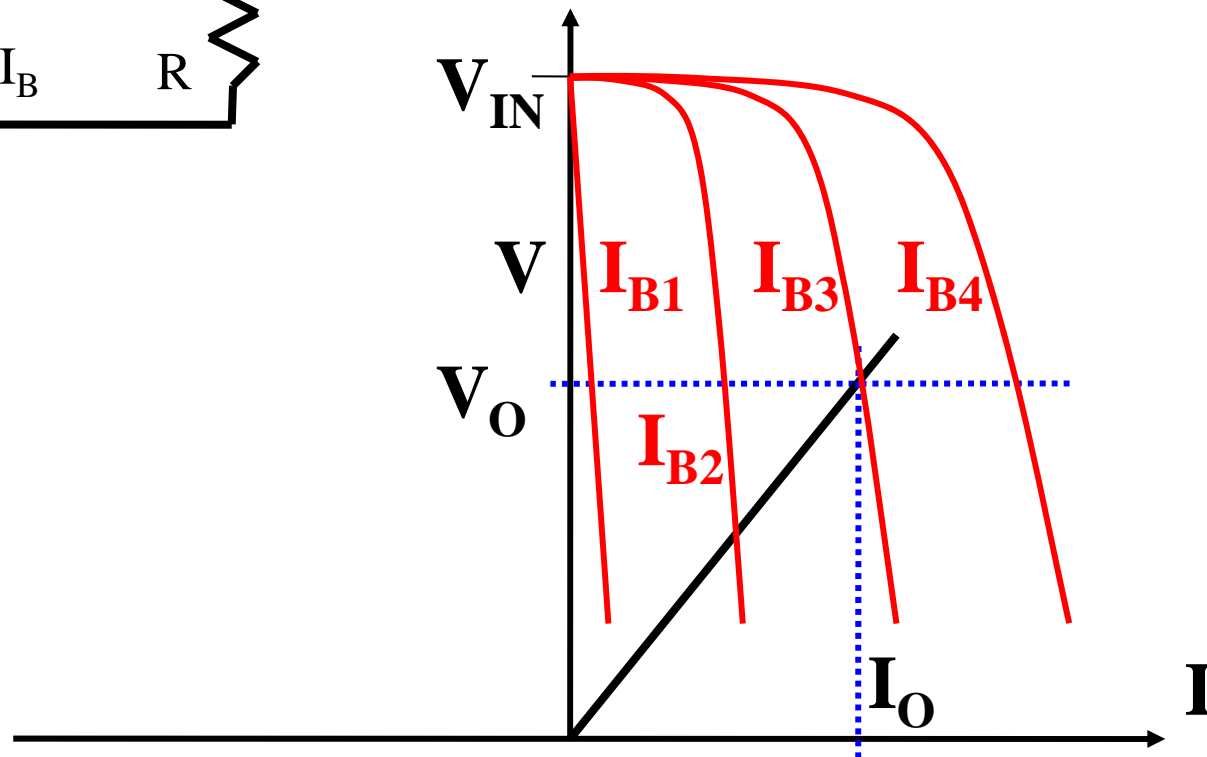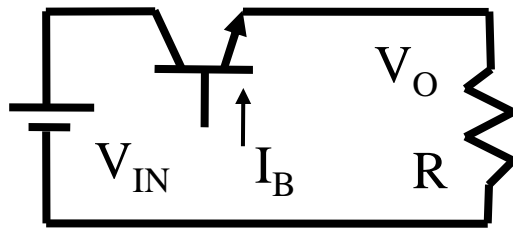

Prior Art

Closed Loop Control


Series Controlled Converter

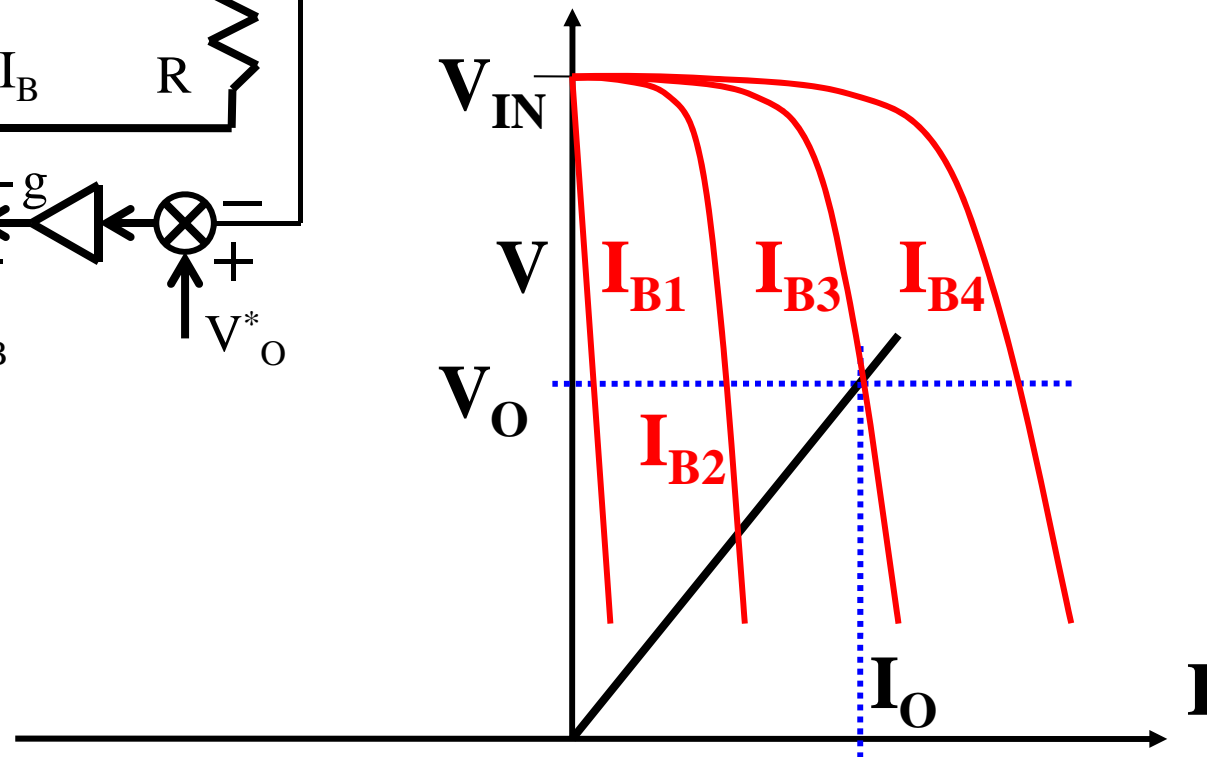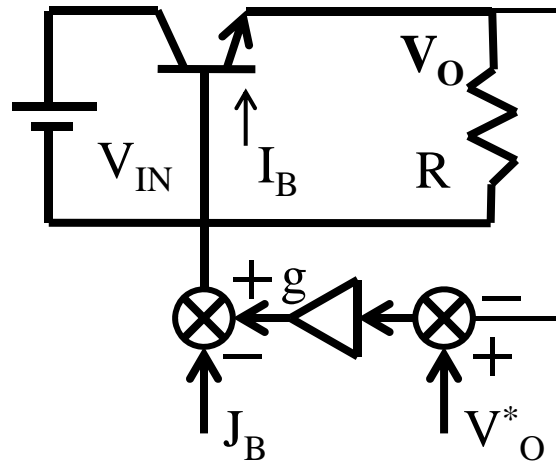

Prior Art

Output Voltage


Series Controlled Converter

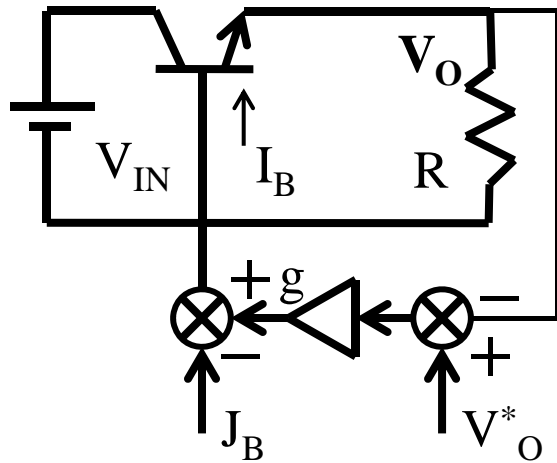

$$(g(V_O^* - V_O) - J_B) \beta R = V_O$$

$$V_O = V_O^* \frac{g\beta R}{1 + g\beta R} + J_B \frac{\beta R}{1 + g\beta R}$$

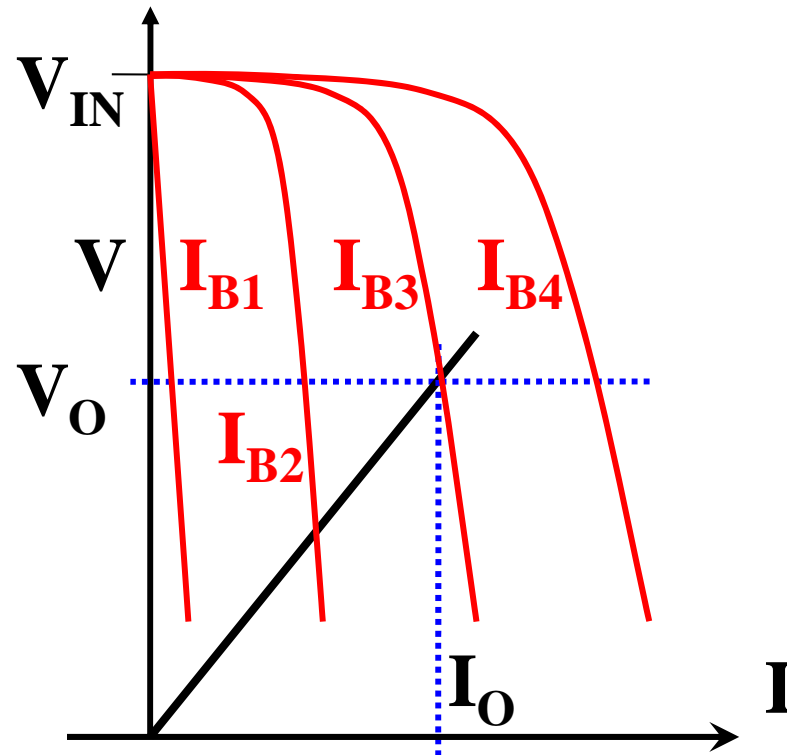
$$V_O \approx V_O^* \text{ for } g \gg \gg 1$$



Shunt Controlled Power Converter


Zener Regulated Power Converter

A Sample Exercise

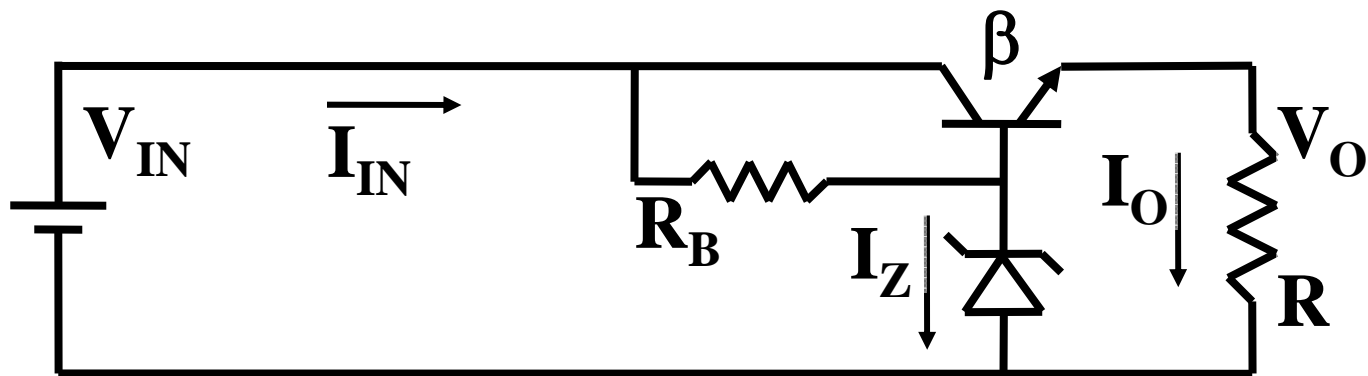

Shunt Controlled Power Converter

A Sample Exercise

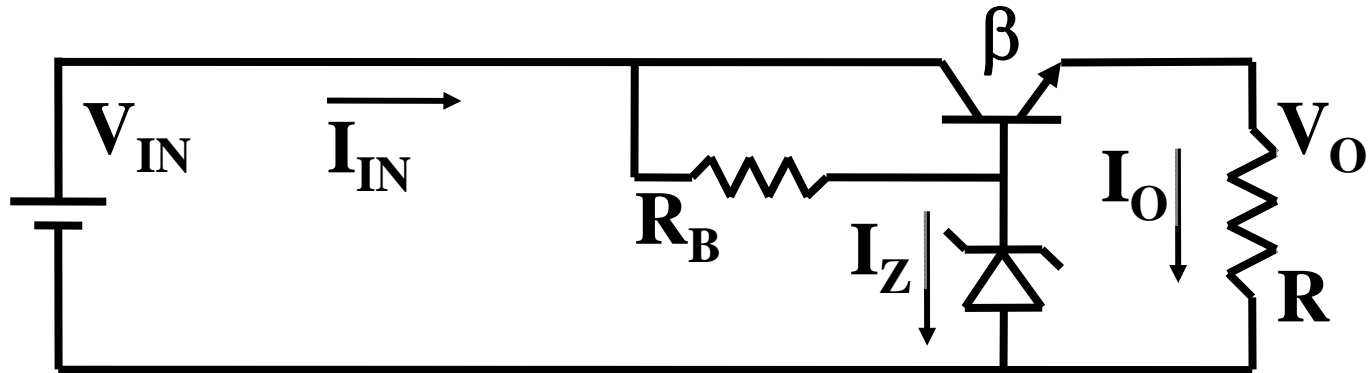

$$V_O = 10 \text{ V} ; P_O = 10 \text{ W} ;$$

$$R = 10 \text{ } \Omega \text{ to } 100 \text{ } \Omega ;$$

$$V_{IN} = 15 \text{ V to } 18 \text{ V} ;$$

$$V_Z = 10 \text{ V}, 7 \text{ } \Omega, 1 \text{ W Zener} ;$$



$$\beta = 20 ;$$

$$R_B = ? ; \eta = ? ;$$

$$\Delta V_O = ? ;$$


Shunt Controlled Power Converter

Load Current

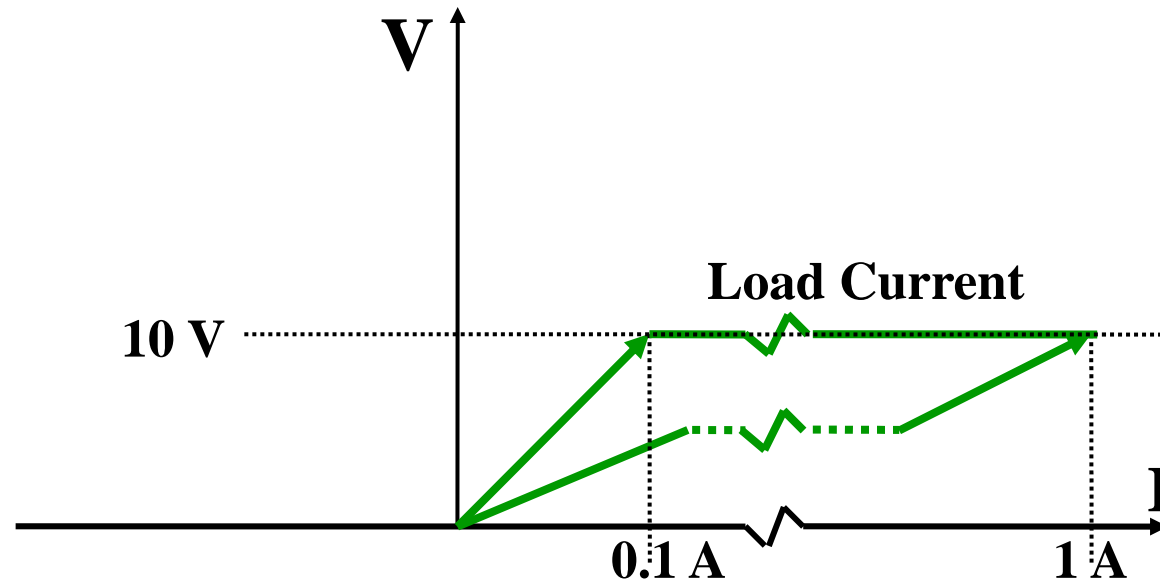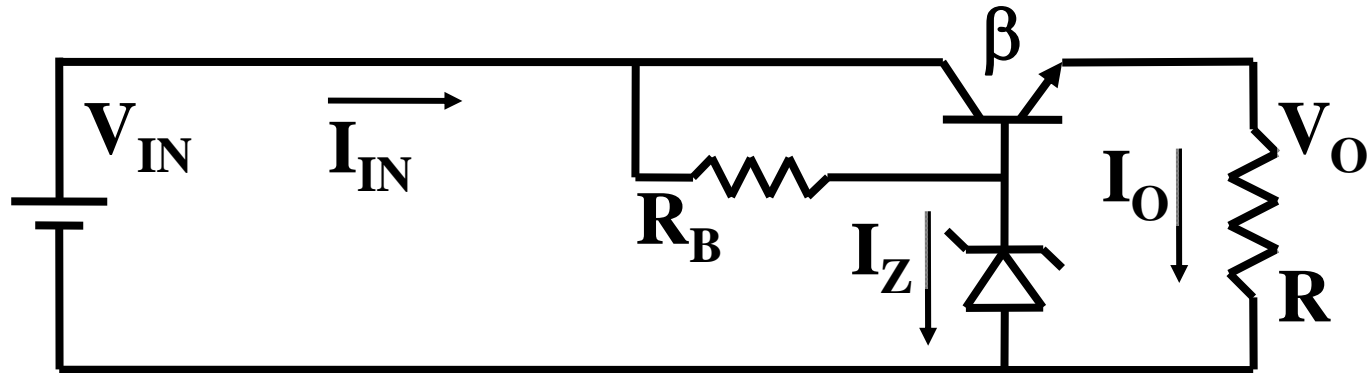



Shunt Controlled Power Converter

Base Current

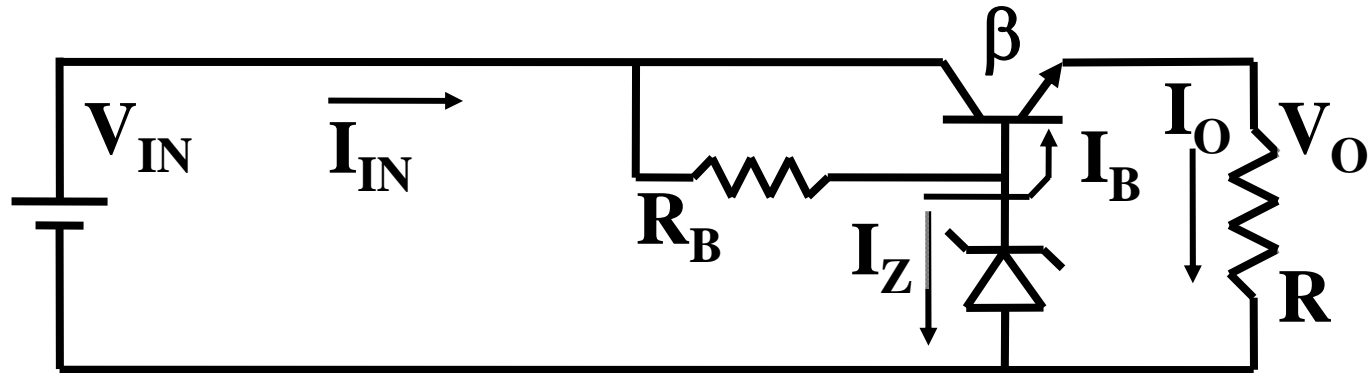


Shunt Controlled Power Converter

Base Current

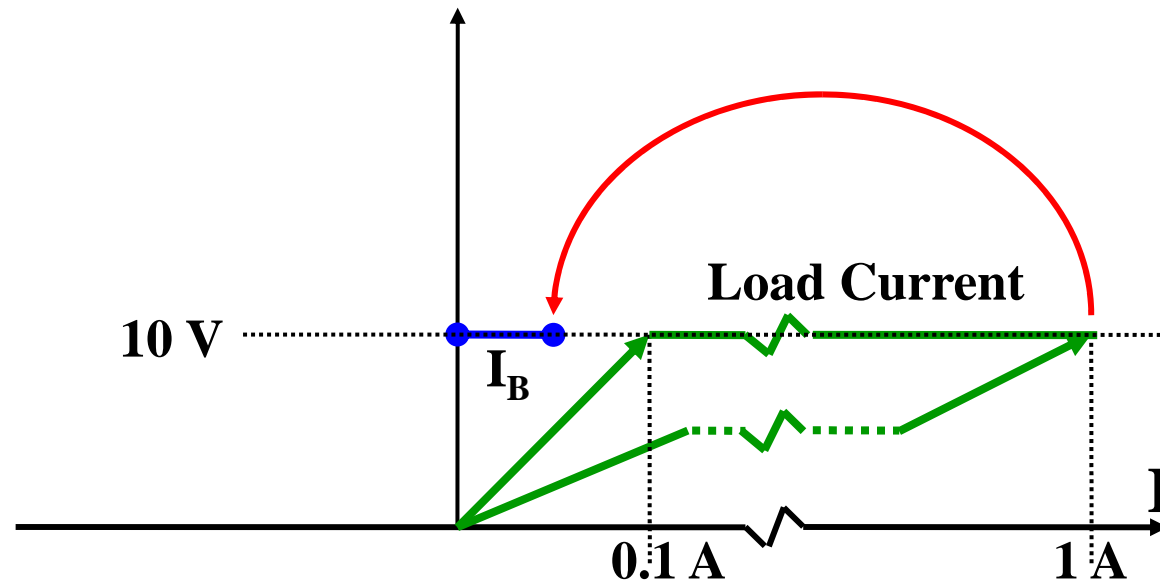
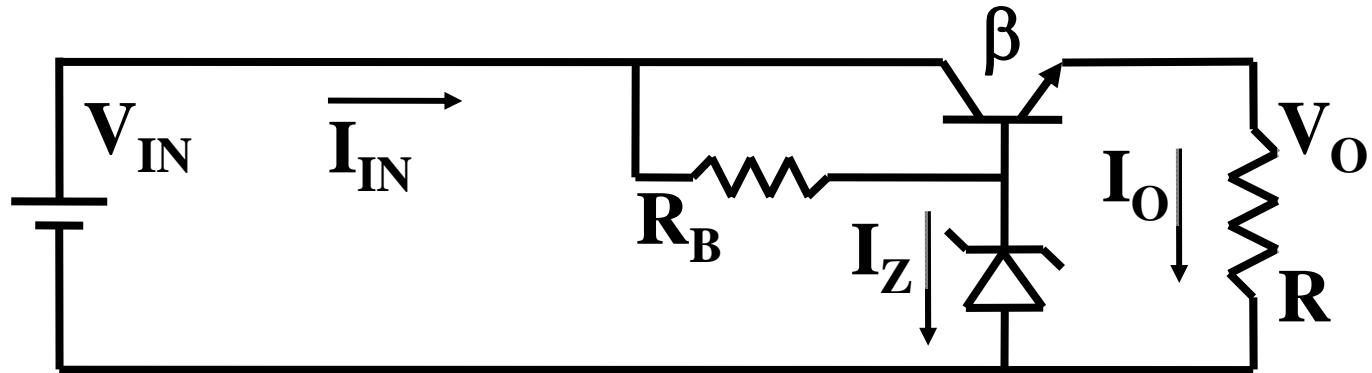


Selection of R_s

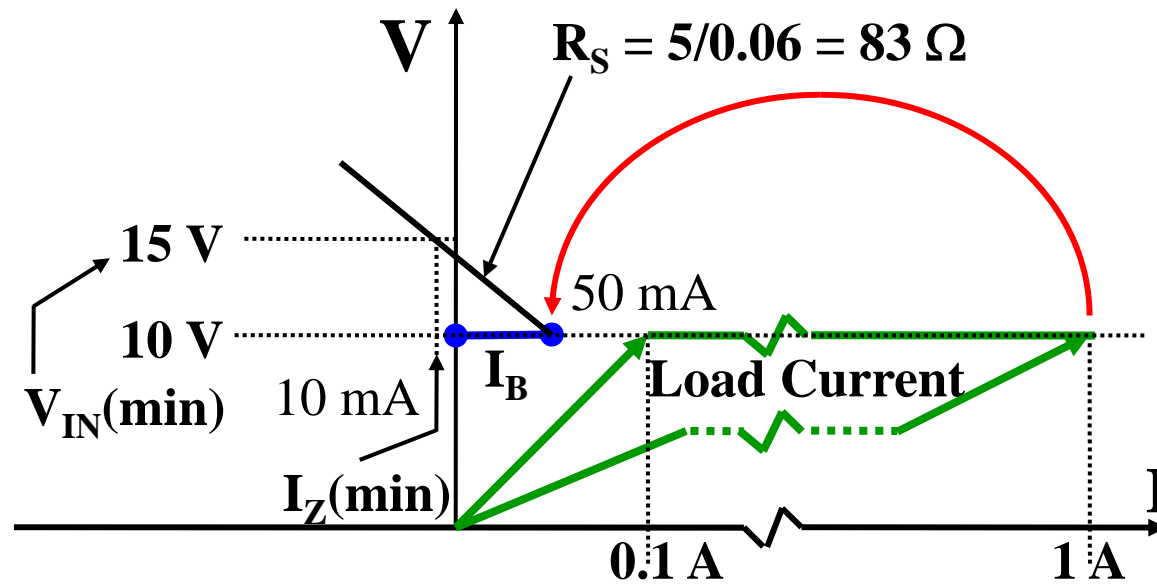



Shunt Controlled Power Converter

Spread of Zener Current

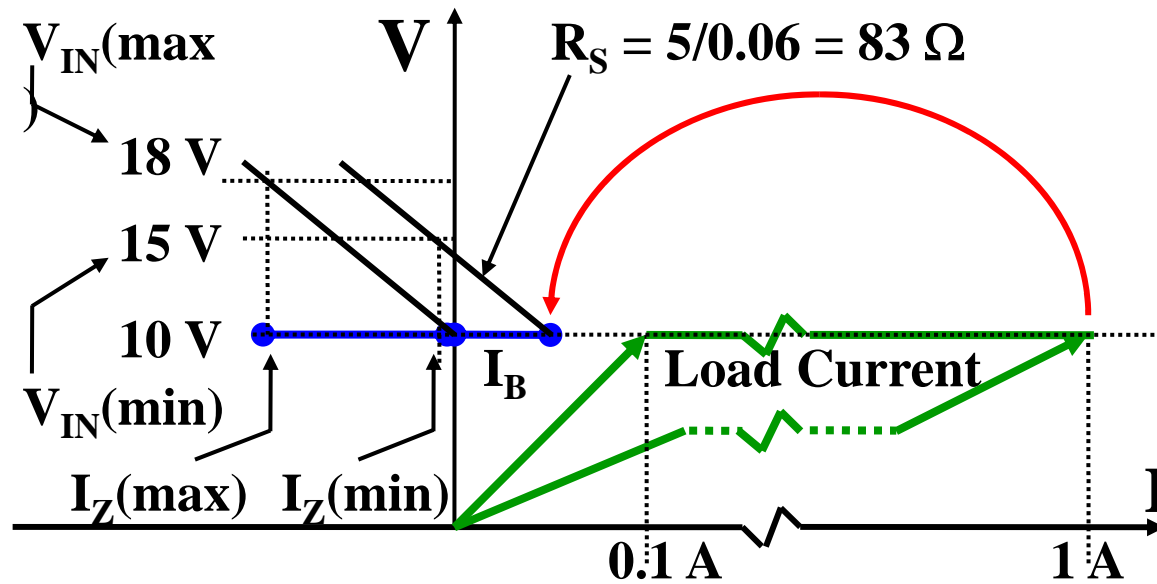
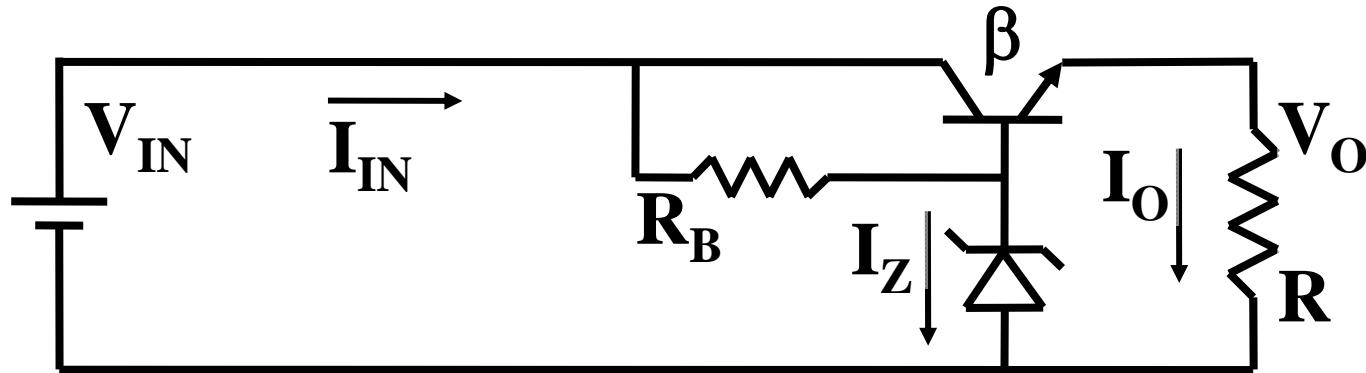


Shunt Controlled Power Converter

Output Power

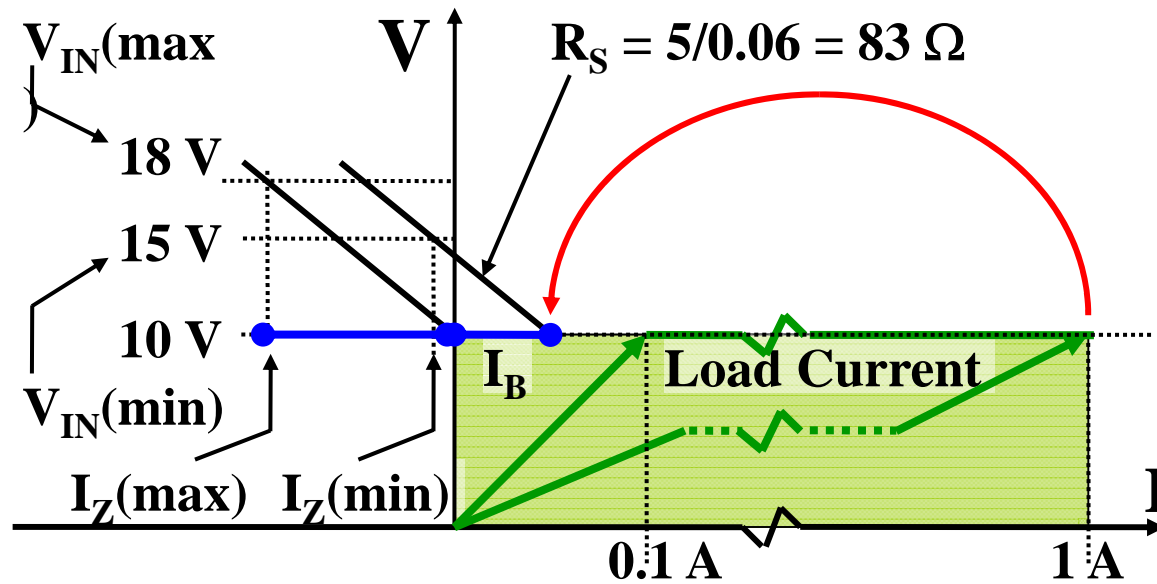
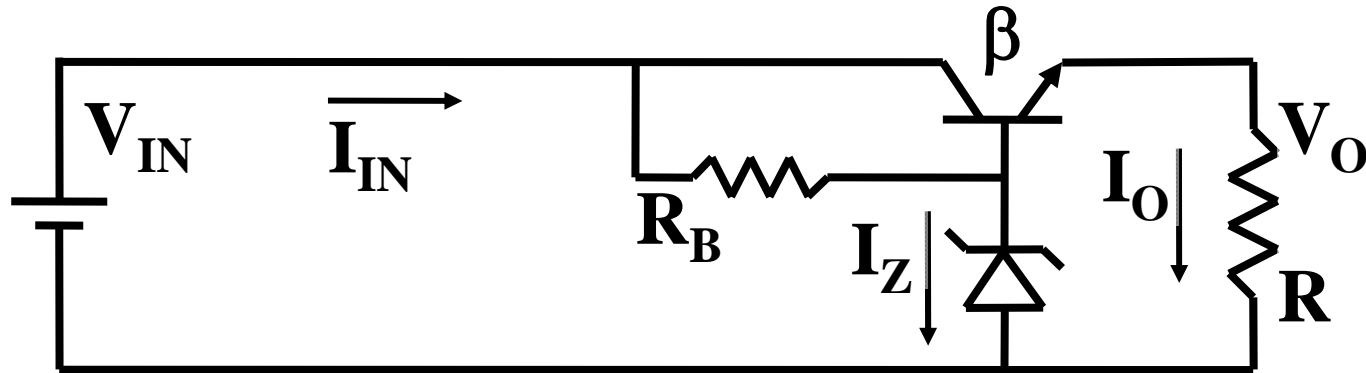


Input Power

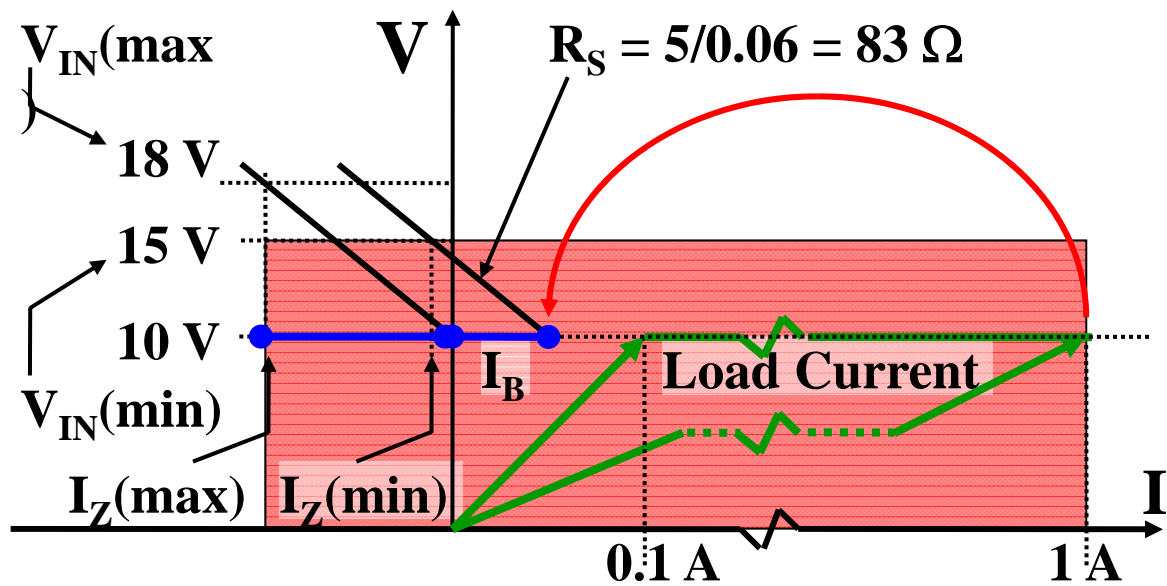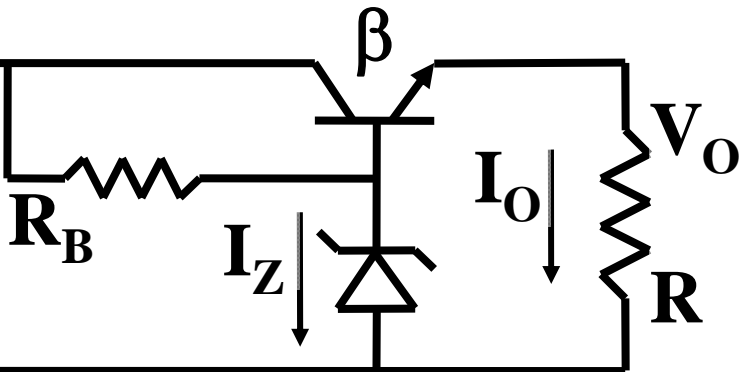



Shunt Controlled Power Converter

Efficiency

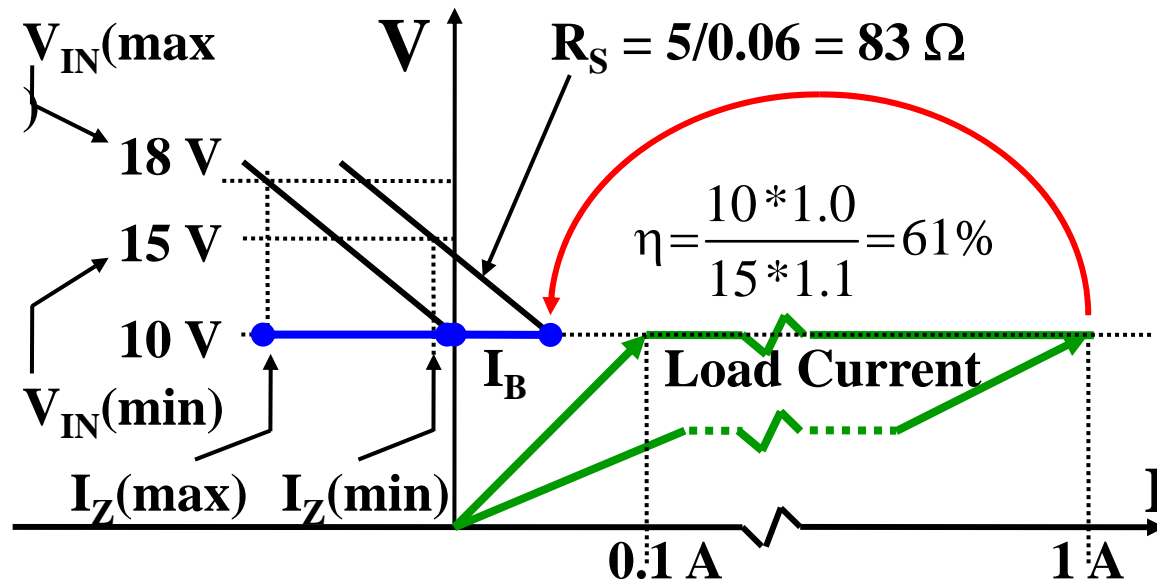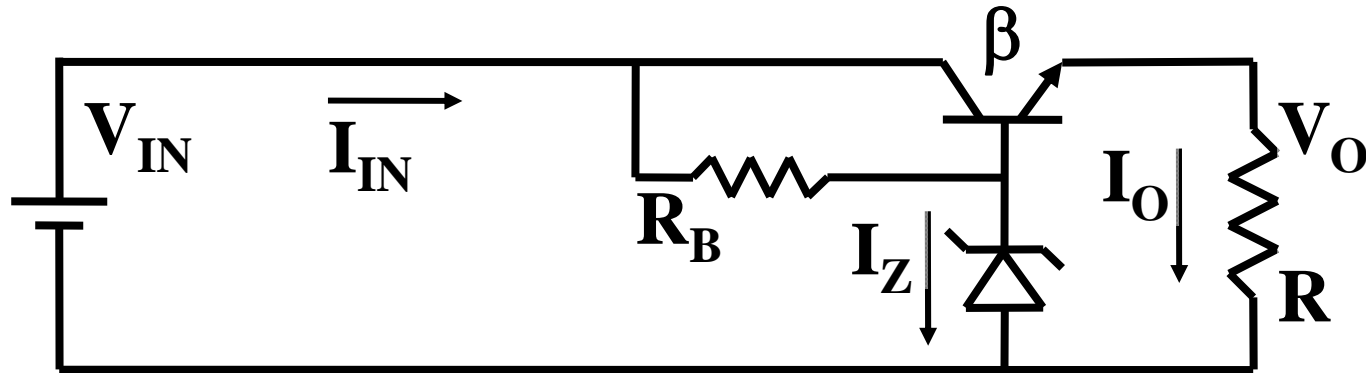



Shunt Controlled Power Converter

Load Regulation

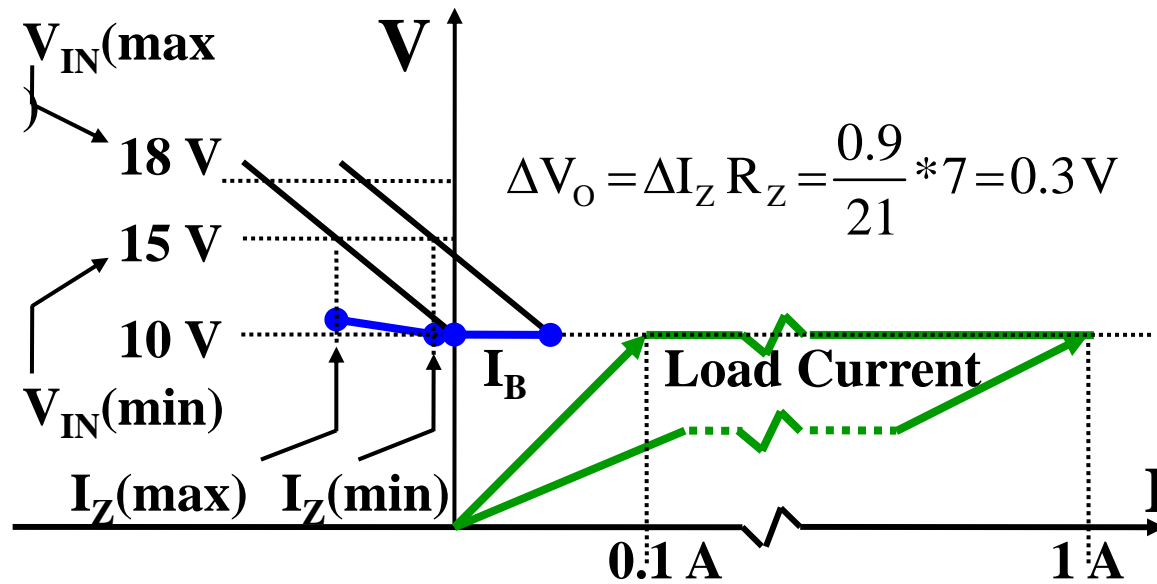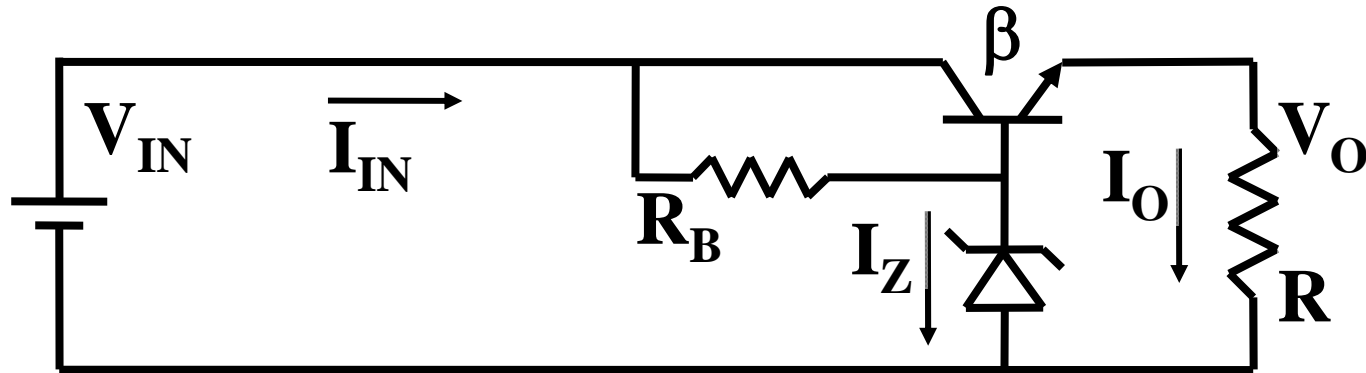



Shunt Controlled Power Converter

Line Regulation

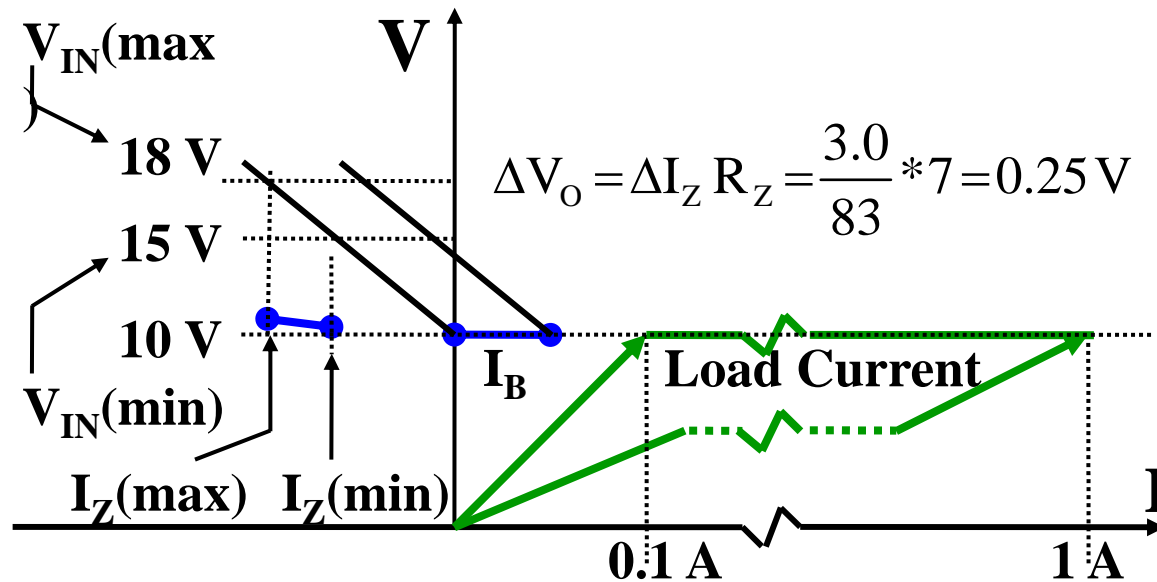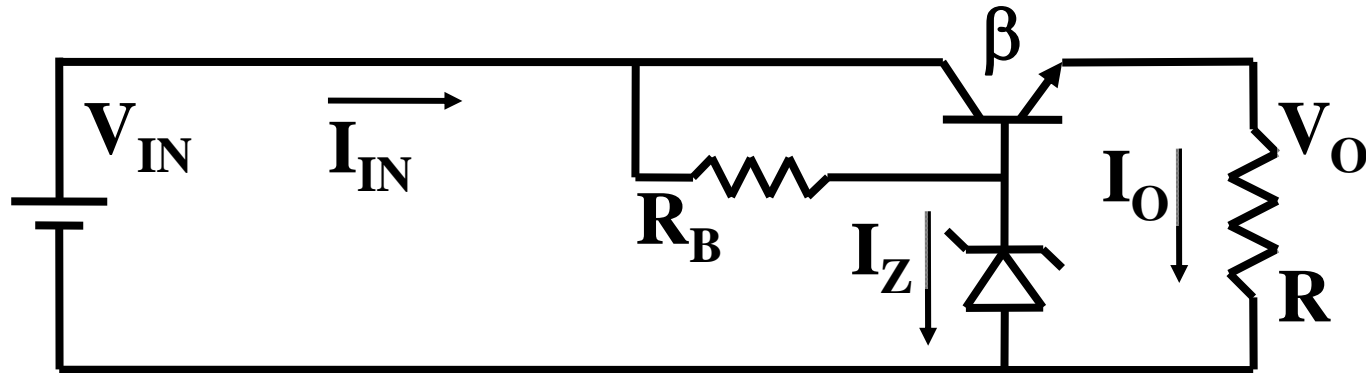



Shunt Controlled Power Converter

Line & Load Regulation

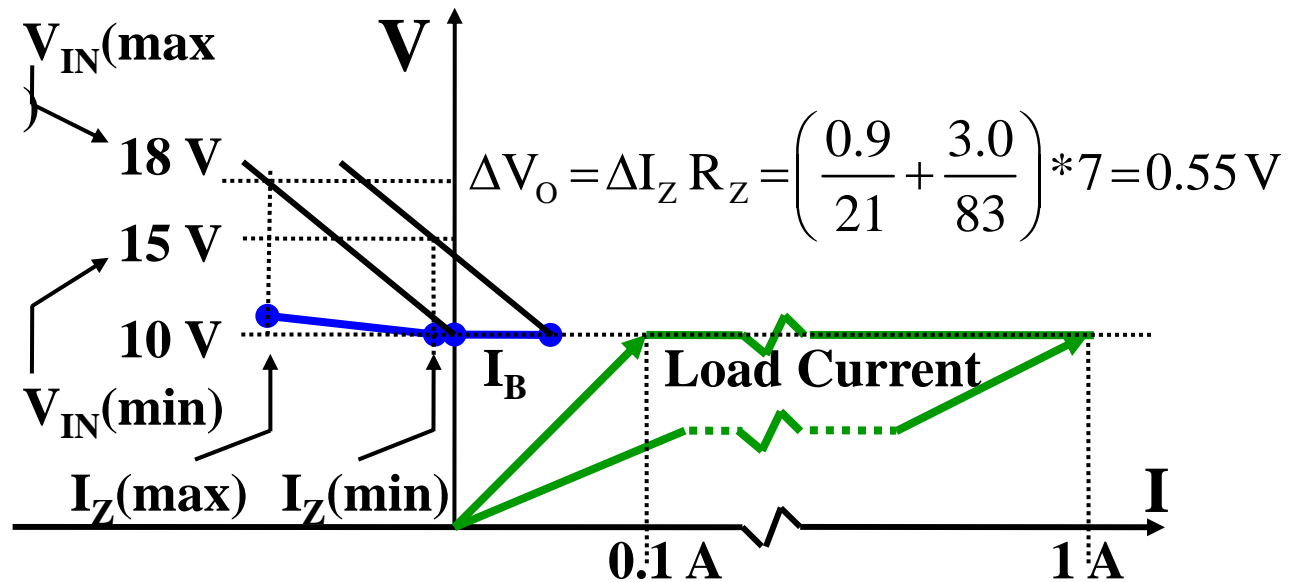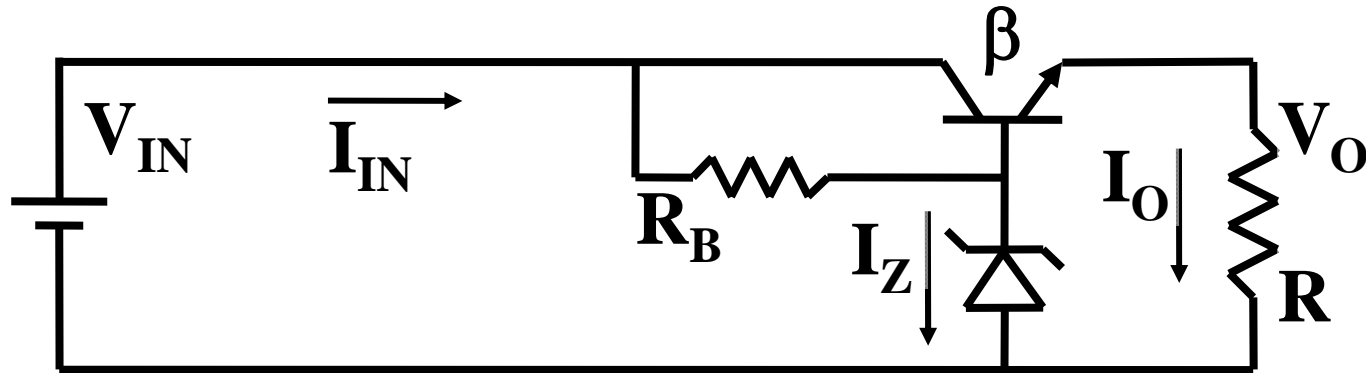

Shunt Controlled Power Converter

Output Voltage Band

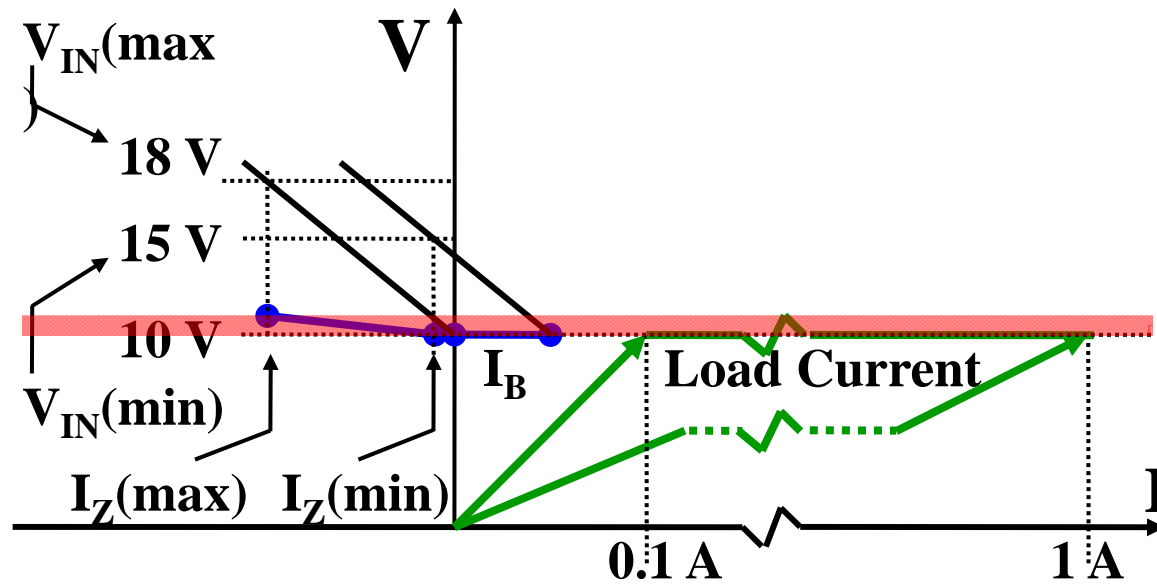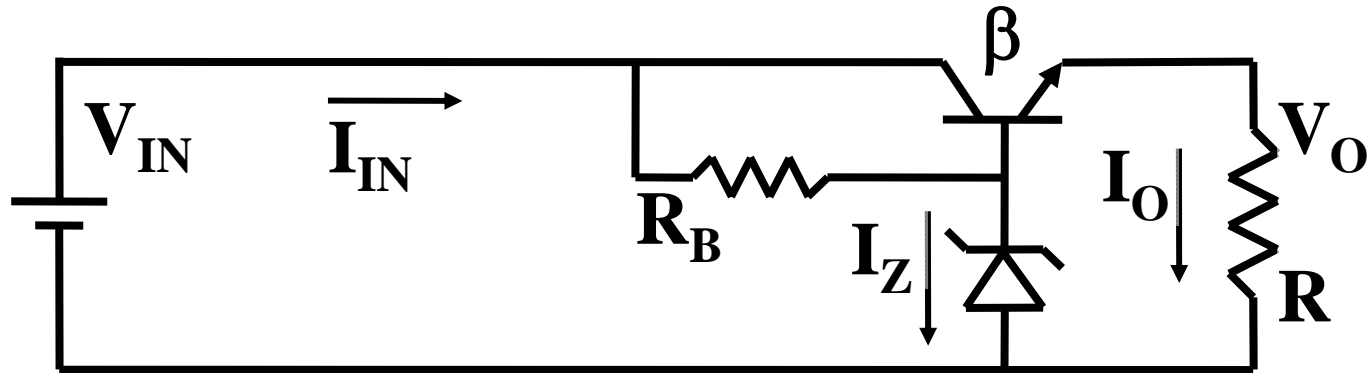


Prior Art

Summary

Series & Shunt Controlled Converters

General Linear Power Converter

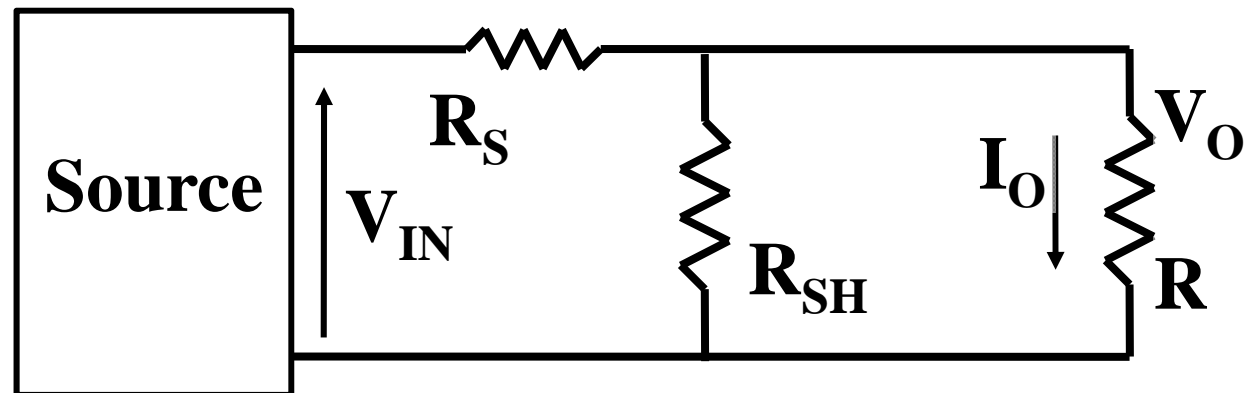


Prior Art

Summary

Series & Shunt Controlled Converters

Simple in Design

Poor Efficiency

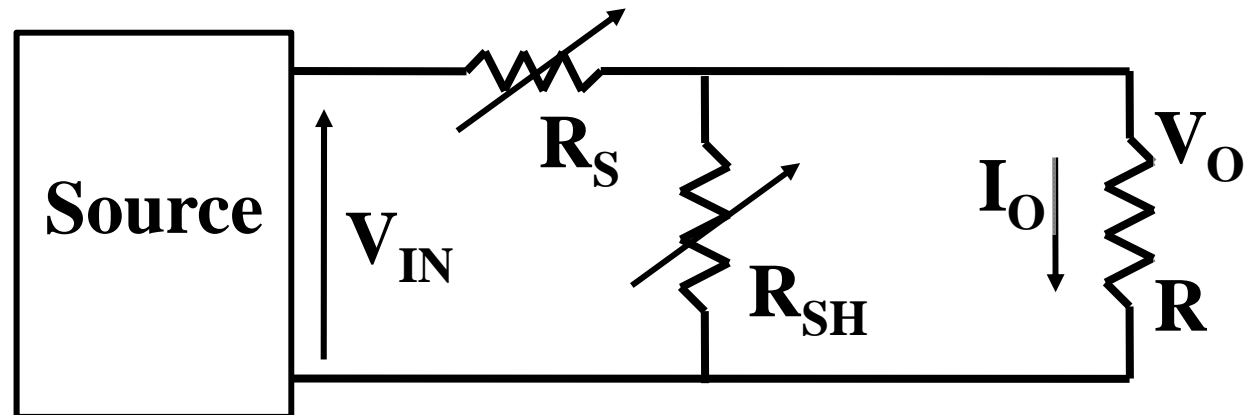


**Loss is Low if R_S and R_{SH} are
Replaced with Switches**

Switched Mode Power Conversion

Central Idea of Loss-less Power Conversion


Switching Converter

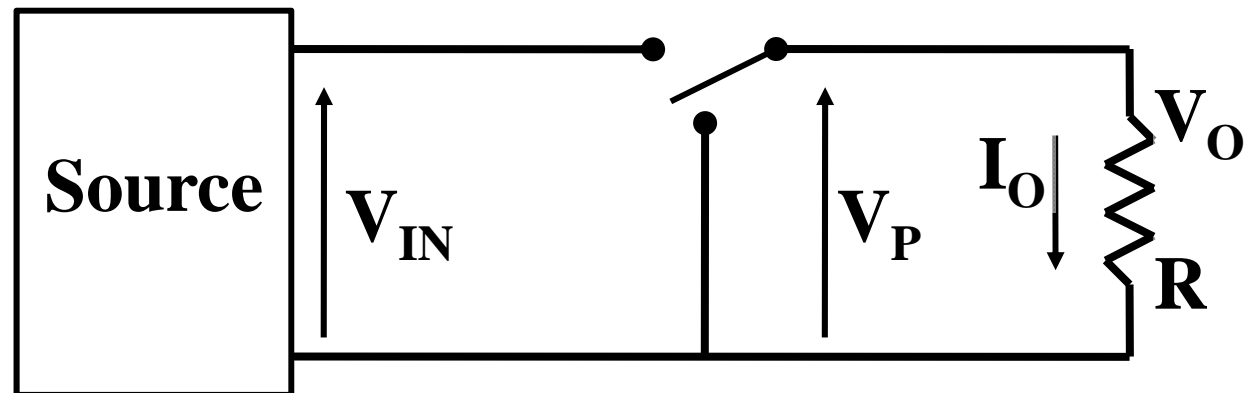

Switched Mode Power Conversion

Central Idea of Loss-less Power Conversion

Switching Converter

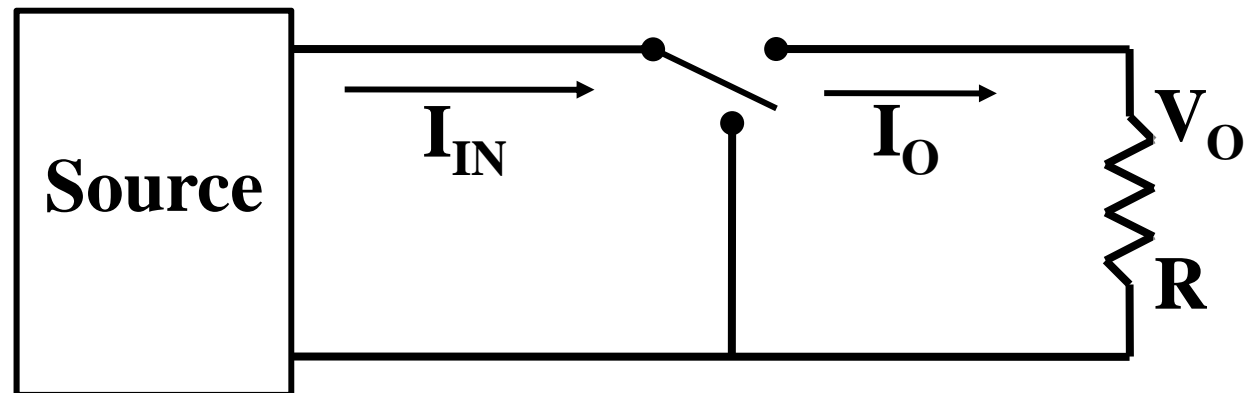

Switched Mode Power Conversion

What Next?

Devices for Efficient Power Conversion

Switches

Inductors

Transformers

Capacitors