

# Switched Mode Power Conversion

## Problem Set 03

### Selected Problems: Power Conversion Circuits

$$\frac{V_o}{V_g} = ?$$

$$\frac{\Delta V_c}{V_c}$$

$$\frac{I_g}{I_o} = ?$$


$$\frac{\Delta I_L}{I_L}$$

7

# Switched Mode Power Conversion

## Problem Set 03


### Problem No. 1

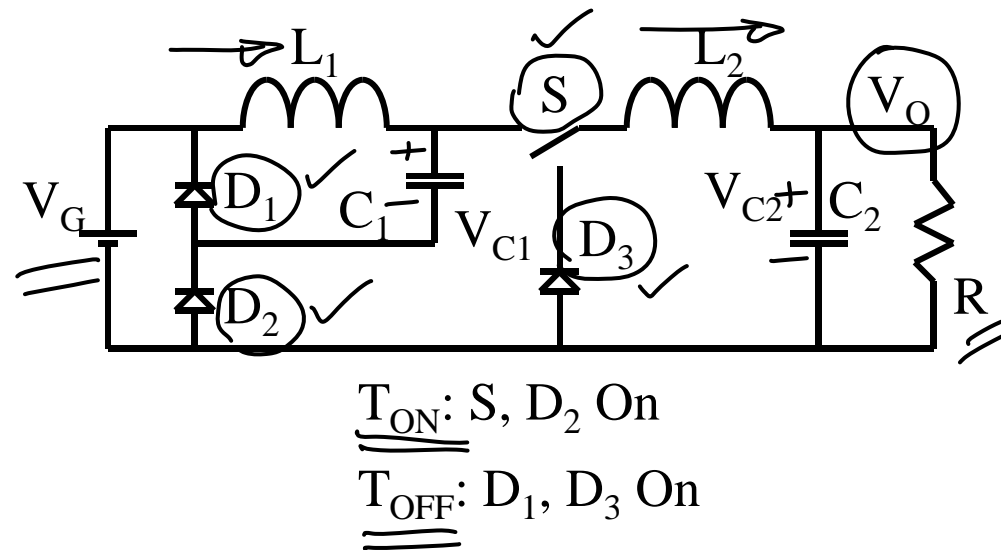

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 1

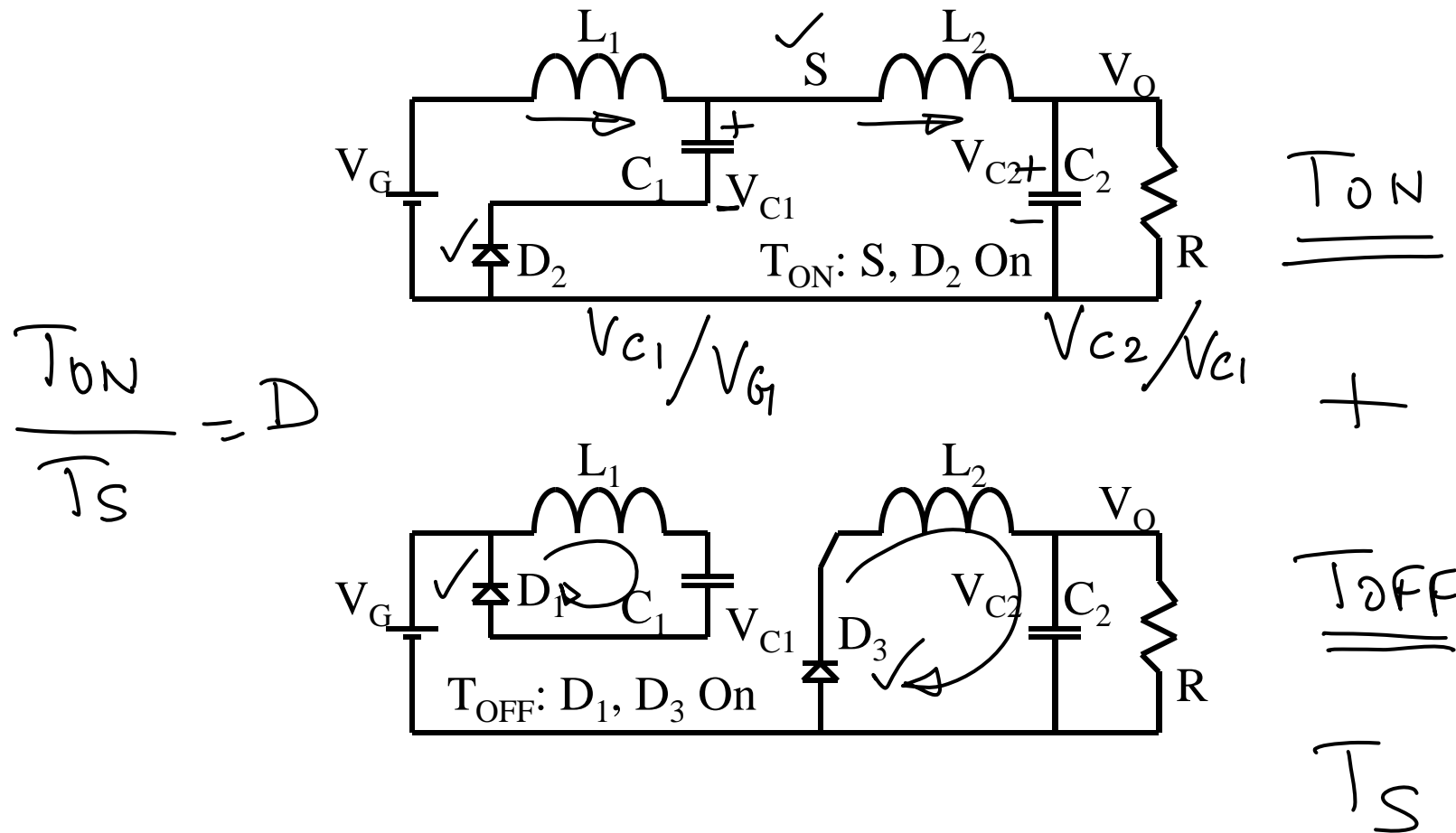

# Problem No. 1


$$V_{ce1} \approx D V_{G1}$$

$$\underline{\underline{V_D = D^2 V_G}}$$

# Switched Mode Power Conversion

## Problem Set 03


### Problem No. 1

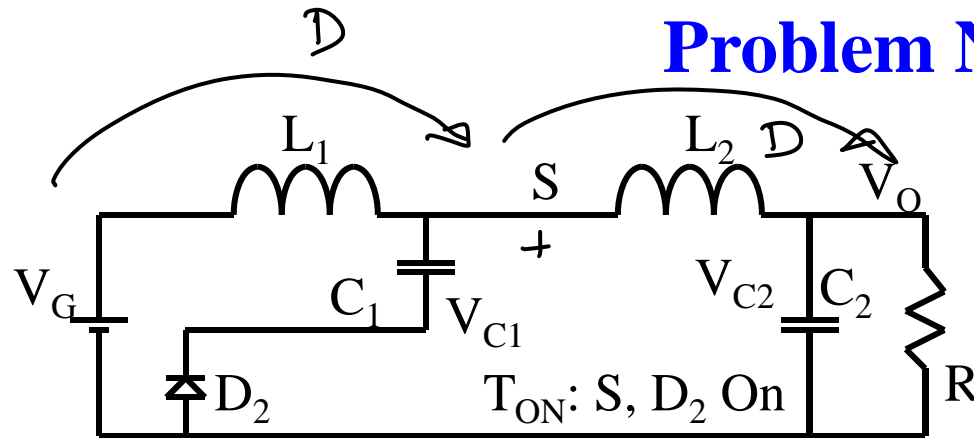

$$\frac{(V_{C1} - V_{C2}) T_{ON} + (-V_{C2}) T_{OFF}}{0}$$

$$V_{C1} T_{ON} = V_{C2} T_S$$

$$V_{C2} = D V_{C1}$$

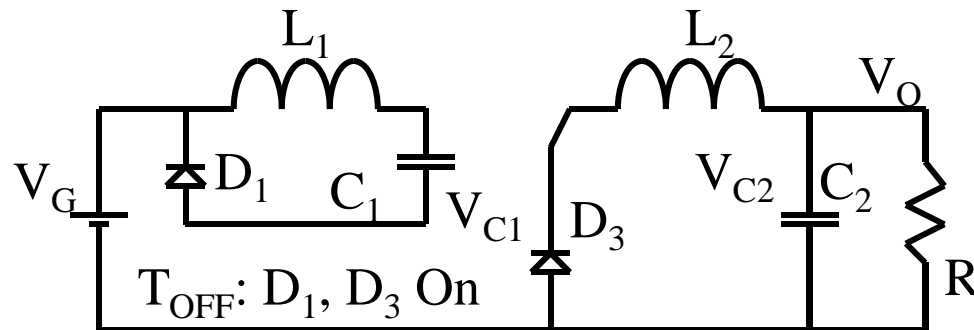


$$\underline{\underline{V_{C2} = V_O = D^2 V_G}}$$

**Volt-sec Balance on  $L_2$**

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 1

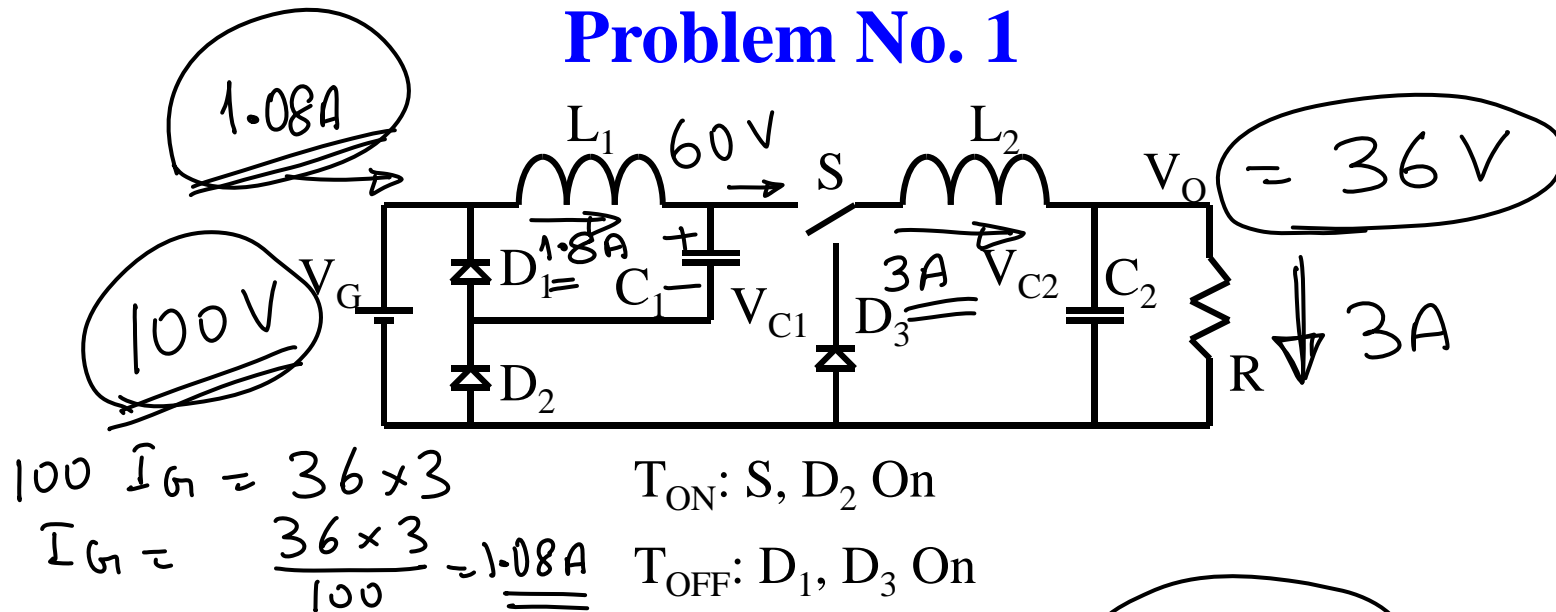

$V_G$ : 100 V;  $D$ : 0.6;  $R$ : 12 ohm;  $T_s$ : 20  $\mu$ s;  
 $L_1, L_2, C_1, C_2$ : ??


$$\frac{I_{L2}}{I_G} = \frac{3 \text{ A}}{1.08 \text{ A}}$$

$$\underline{I_{L1} = 1.8 \text{ A}}$$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 1

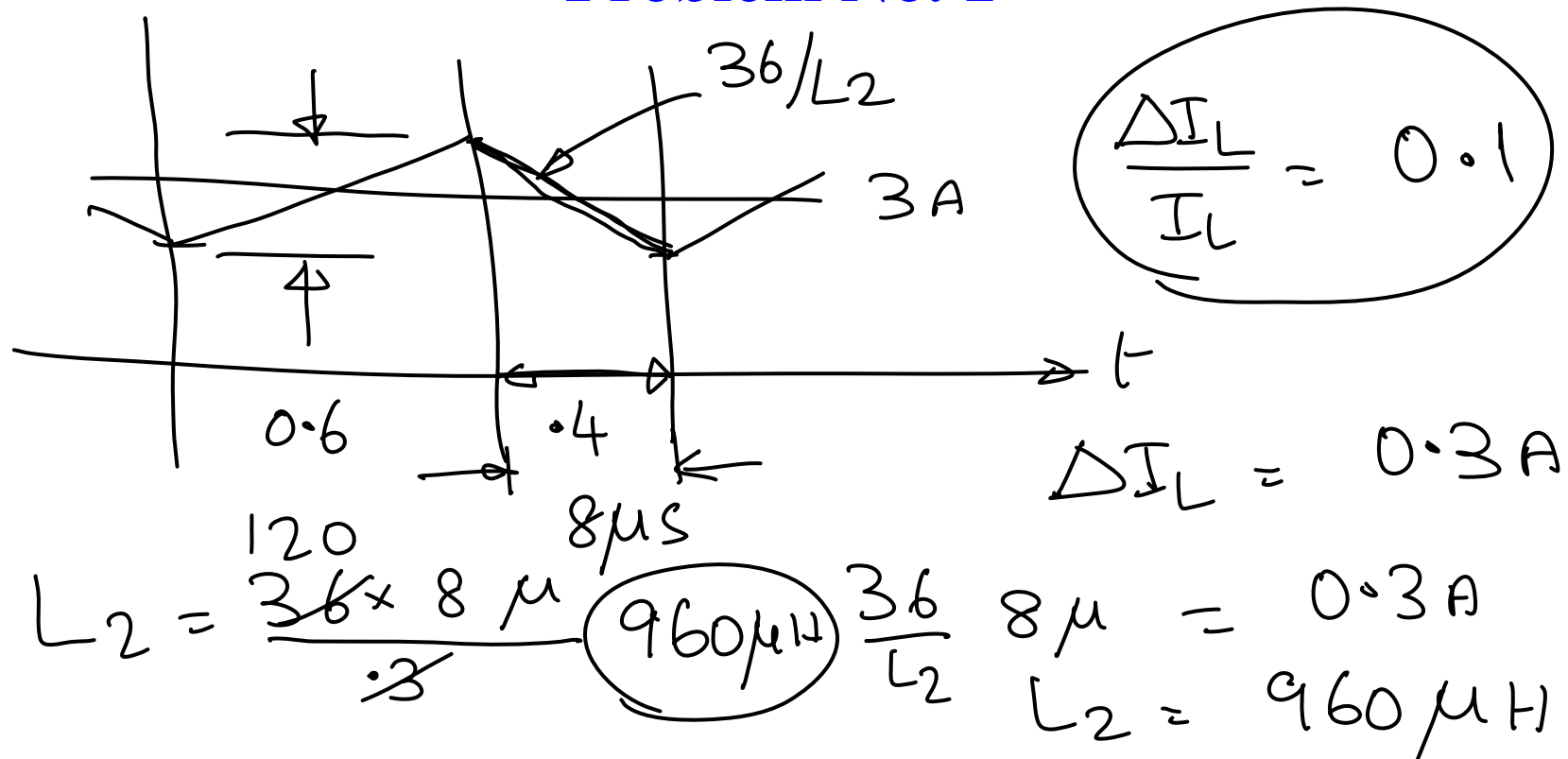


$V_G: 100 \text{ V}; D: 0.6; R: 12 \text{ ohm}; T_s: 20 \mu\text{s};$

$L_2: ??$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 1

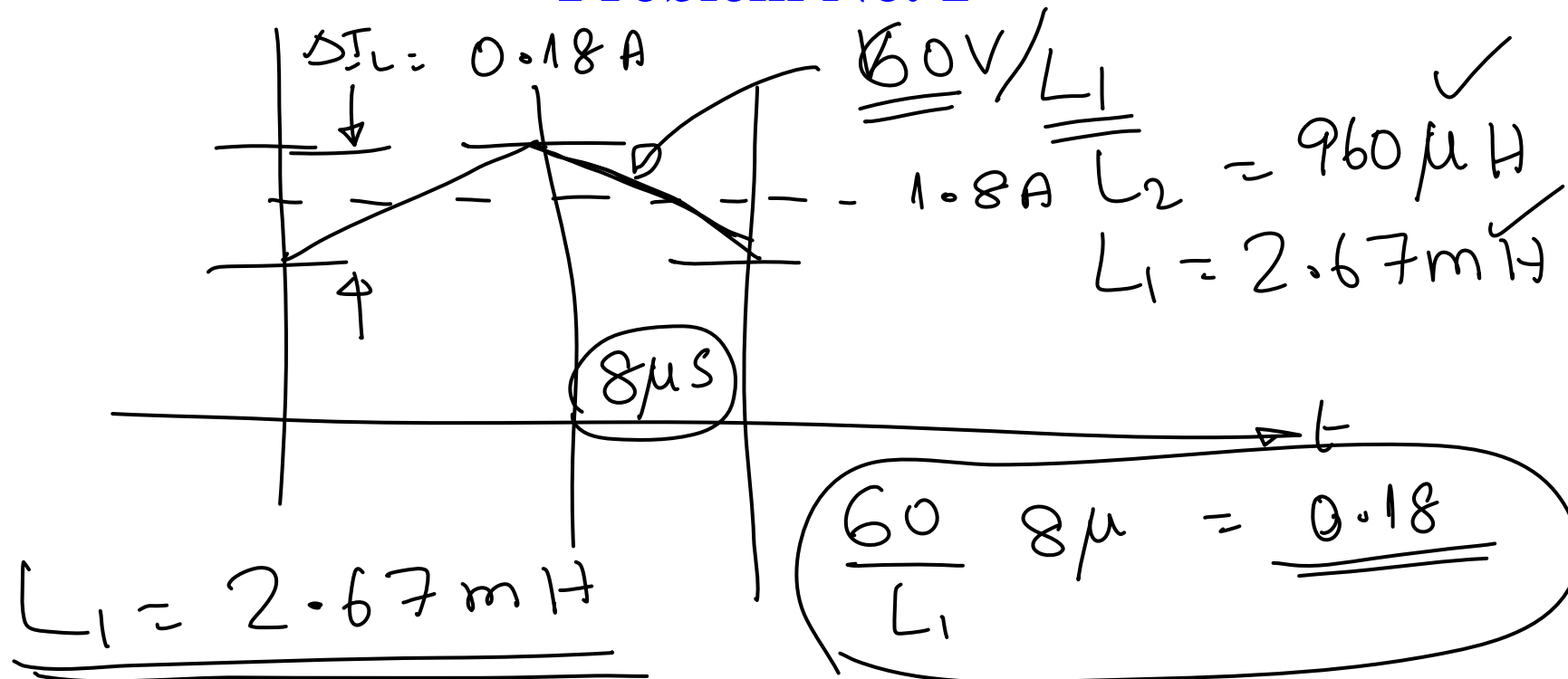

$V_G: 100 \text{ V}; D: 0.6; R: 12 \text{ ohm}; T_s: 20 \mu\text{s};$


$L_1: ??$



# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 1

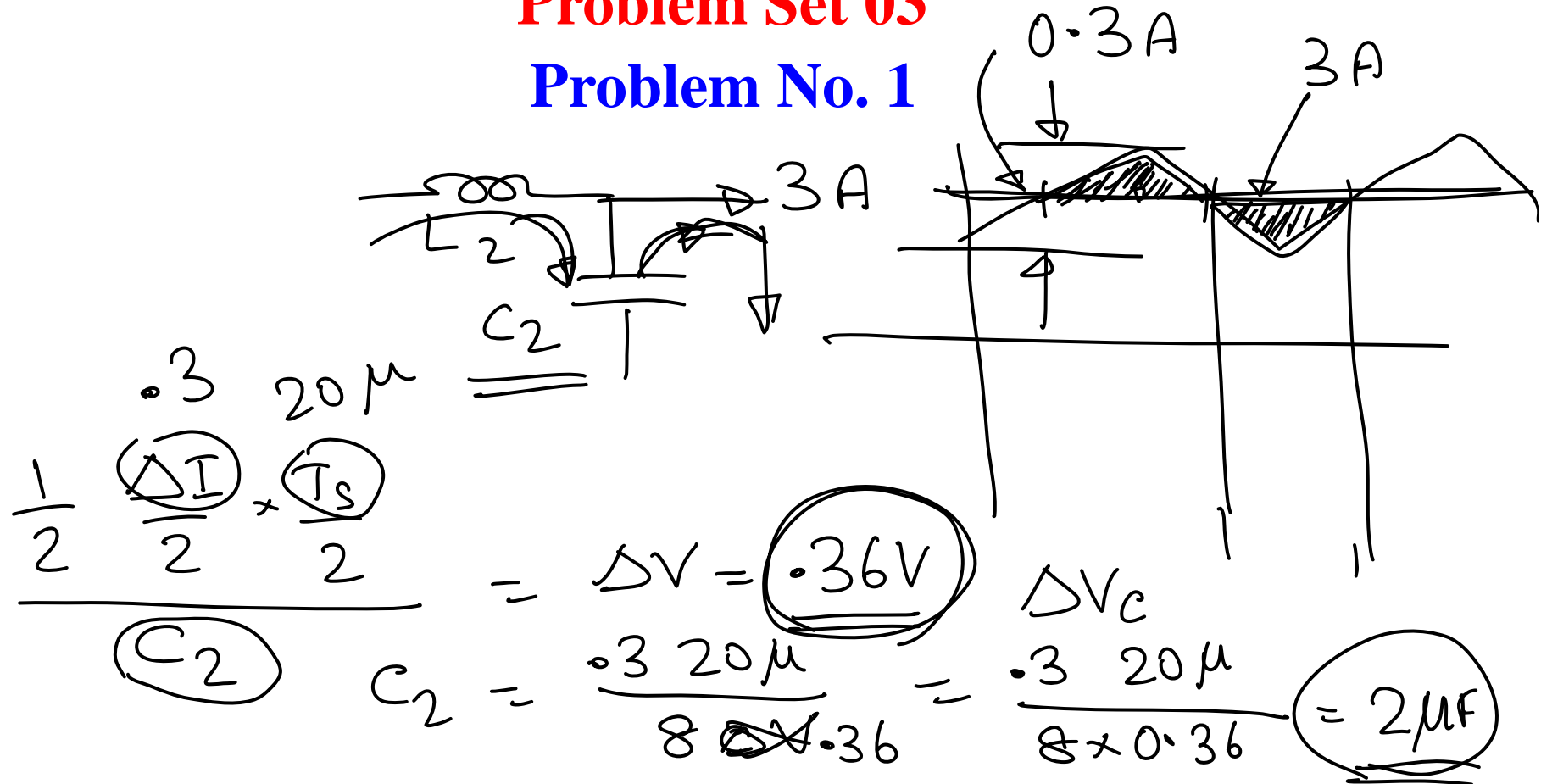

$V_G: 100\text{ V}; D: 0.6; R: 12\text{ ohm}; T_s: 20\text{ }\mu\text{s};$

$C_2: ??$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 1

$$\begin{aligned}V_o &= 36\text{ V} & I_o &= 3\text{ A} \\I_{L2} &= 3\text{ A} & I_{L1} &= 1.8\text{ A} \\V_{C1} &= 60\text{ V} & V_{C2} &= V_o = 36\text{ V} \\L_1 &= 2.67\text{ mH} & L_2 &= 960\text{ }\mu\text{H} \\C_1 &= 24\text{ }\mu\text{F} & C_2 &= 2\text{ }\mu\text{F}\end{aligned}$$

---


**$V_G$ : 100 V;  $D$ : 0.6;  $R$ : 12 ohm;  $T_S$ : 20  $\mu\text{s}$ ;**

**$C_2$ : ??**

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 2

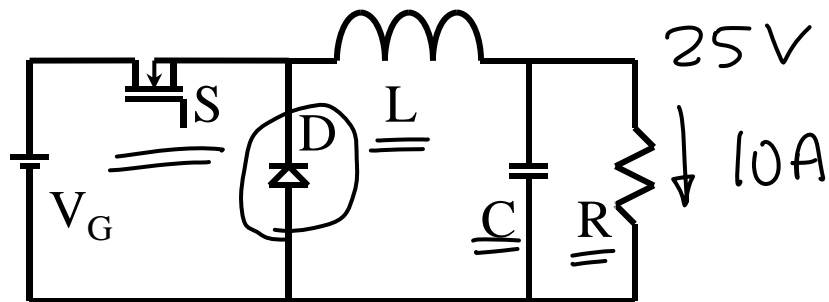

$$D = 0.4$$

$$T_s = 20\mu s$$

$$L = 20\mu H$$

$$\Delta I_L = ?$$

$$E_L = ?$$

$$I_s = ?$$


$$\text{Loss in } S = ?$$

**D: 0.4;  $I_O$ : 10 A;  $T_s$ : 20  $\mu s$ ; L: 20  $\mu H$ ;  $V_O$ : 25 V;**

# Switched Mode Power Conversion


## Problem Set 03

### Problem No. 2

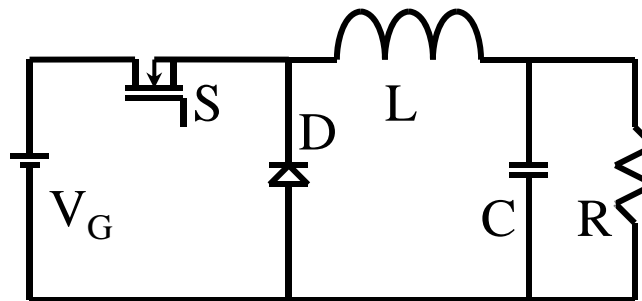

Ripple Current ?

$$\Delta I = 15 \text{ A}$$

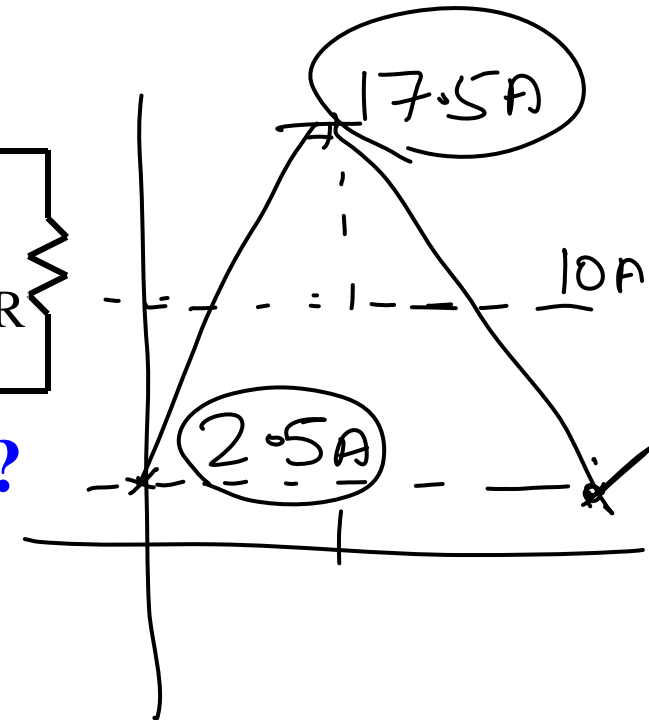

**$D: 0.4; I_O: 10 \text{ A}; T_S: 20 \mu\text{s}; L: 20 \mu\text{H}; V_O: 25 \text{ V};$**

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 2

### Ripple Current ?

$$\Delta I = 15 \text{ A}$$

$$I_{PIZ} = 17.5 \text{ A}$$


$$I_{min} = 2.5 \text{ A}$$

$$D: 0.4; I_O: 10 \text{ A}; T_S: 20 \mu\text{s}; L: 20 \mu\text{H}; V_O: 25 \text{ V};$$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 2

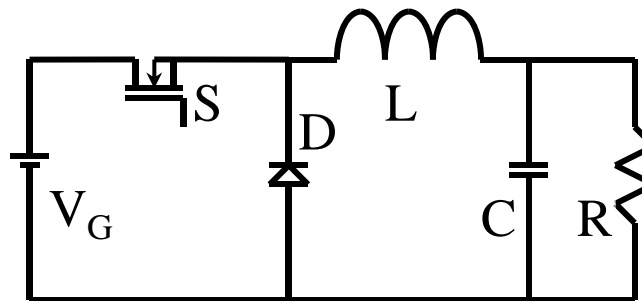

**Peak Stored Energy in L ?**

$$E = 0.5 \cdot 20\mu \cdot 17.5^2$$
$$= 30625\mu\text{J} = \underline{\underline{30.63\text{ mJ}}}$$

$\frac{1}{2} L I^2$

**D: 0.4;  $I_O$ :10 A;  $T_S$ : 20  $\mu\text{s}$ ; L: 20  $\mu\text{H}$ ;  $V_O$ : 25 V;**

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 2

Peak Stored Energy in L ?


$$\text{Peak } E = 30.63 \text{ mJ}$$

**D: 0.4;  $I_O$ : 10 A;  $T_S$ : 20  $\mu\text{s}$ ; L: 20  $\mu\text{H}$ ;  $V_O$ : 25 V;**


# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 2

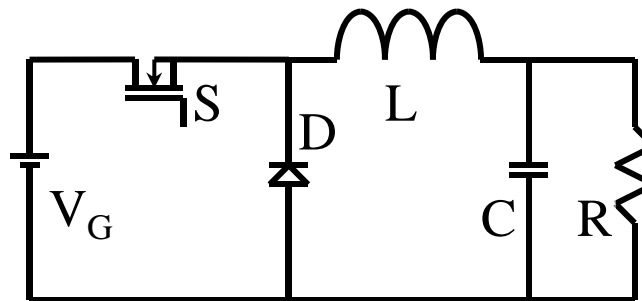

**RMS Current Through Switch ?**

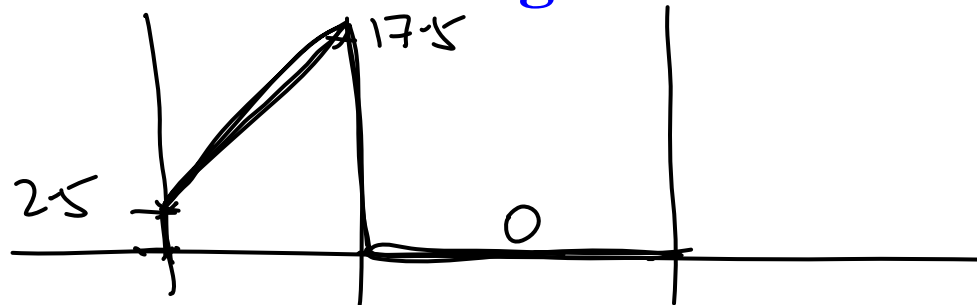

**$D: 0.4; I_O: 10 \text{ A}; T_S: 20 \mu\text{s}; L: 20 \mu\text{H}; V_O: 25 \text{ V};$**




# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 2

Rms Current Through Switch ?  $6.9A$

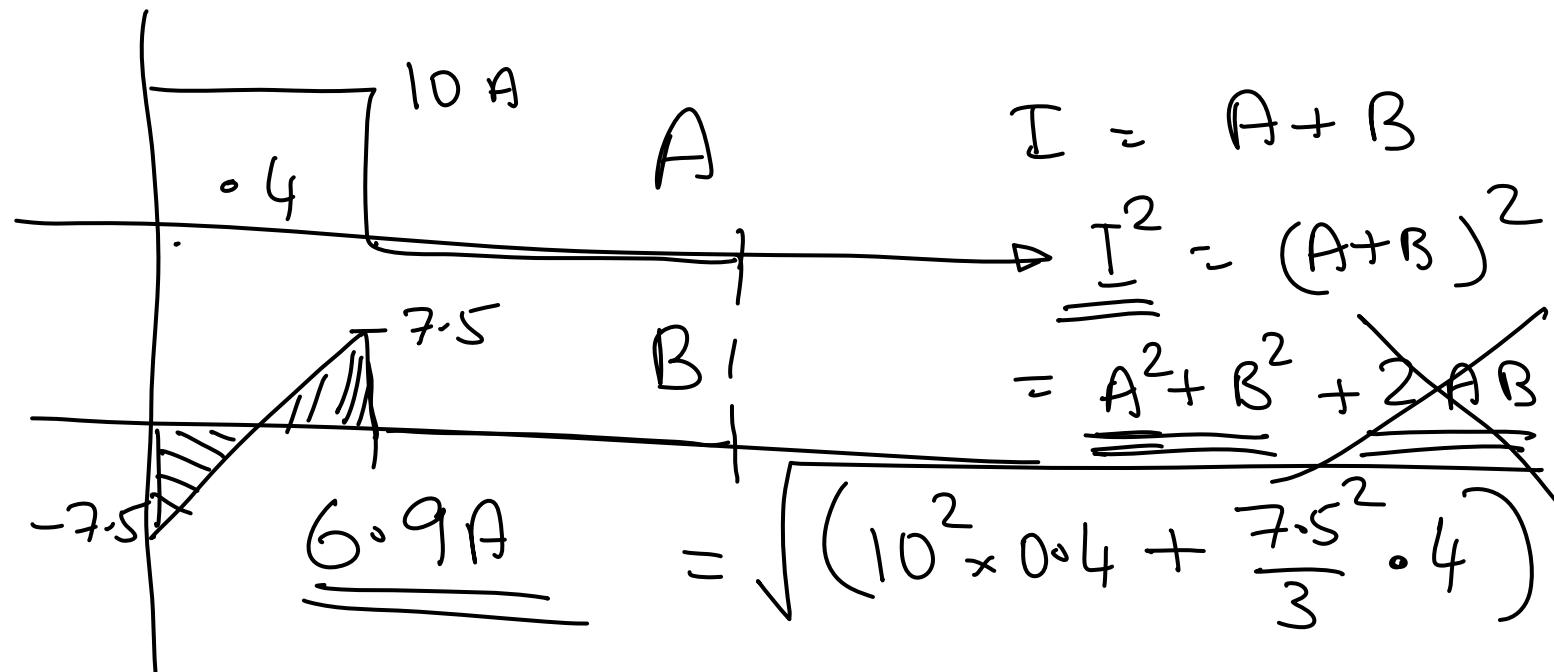


**$D: 0.4; I_0: 10A; T_s: 20\mu s; L: 20\mu H; V_0: 25V;$**

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 2

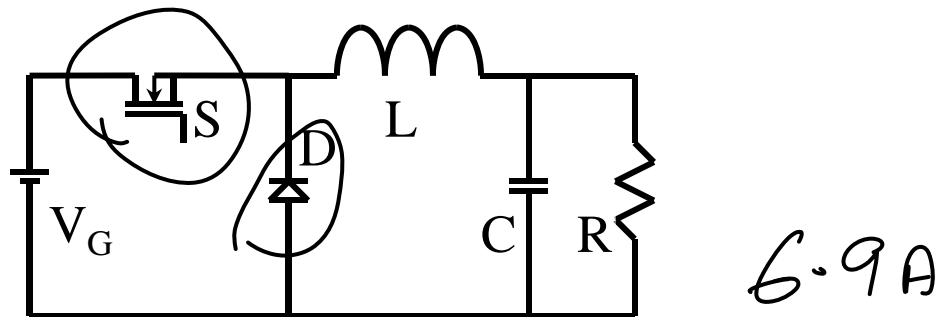

Loss in the Switch ( $R_{ds}(\text{on}) = \underline{\underline{20\text{ m}\Omega}}$ ) ?

$$I_{rms}^2 R_{ds}(\text{on})$$
$$6.9^2 \cdot 20\text{ m}\Omega = \underline{\underline{0.95\text{ W}}}$$


**D: 0.4;  $I_O$ :10 A;  $T_S$ : 20  $\mu\text{s}$ ; L: 20  $\mu\text{H}$ ;  $V_O$ : 25 V;**

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 2

Loss in the Switch ( $R_{ds(on)} = 20 \text{ m}\Omega$ ) ?
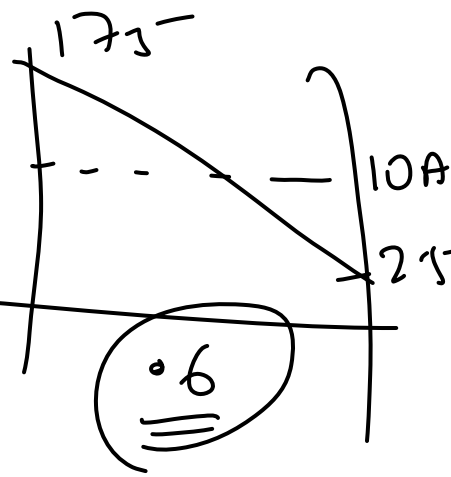
$$P_S = 0.95 \text{ W}$$
$$I_{av} = 10 \times 0.6 = 6 \text{ A}$$
$$V_D = 1 \text{ V}$$
$$P_{loss} = 6 \text{ A} \times 1 \text{ V} = 6 \text{ W}$$
$$17.5 \text{ A} \times 20 \text{ m}\Omega = 0.35 \text{ V}$$


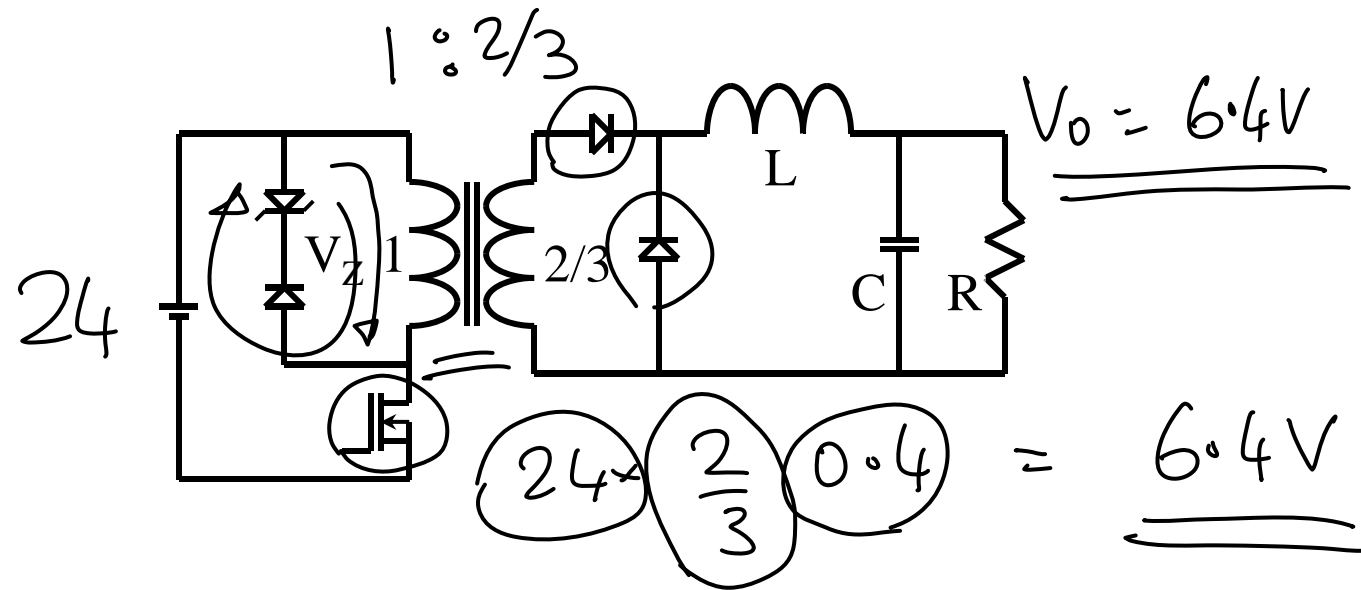
The graph shows a linear ramp down from 17.5 A to 2.5 A. The average current is marked as 6 A. The loss calculation 0.6 is also shown.

**D: 0.4;  $I_O$ : 10 A;  $T_S$ : 20  $\mu\text{s}$ ; L: 20  $\mu\text{H}$ ;  $V_O$ : 25 V;**

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 3




$V_G: 24\text{ V}; D: 0.4; R: 1.0\text{ ohm}; T_s: 20\text{ }\mu\text{s};$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 3

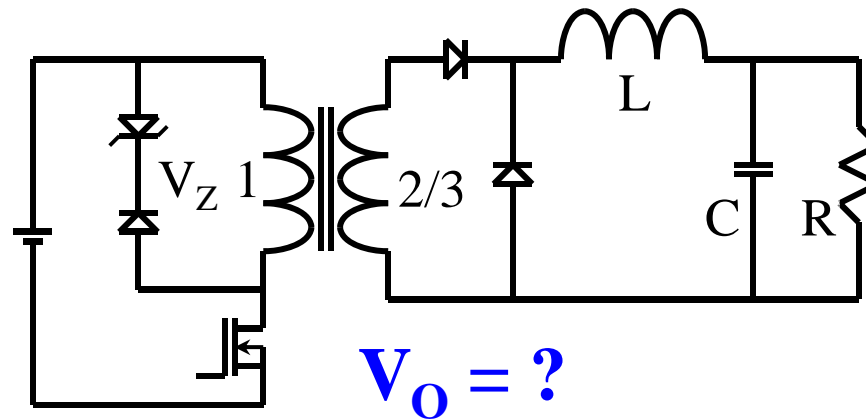


$V_G$ : 24 V; D: 0.4; R:1.0 ohm;  $T_S$ : 20  $\mu$ s;

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 3

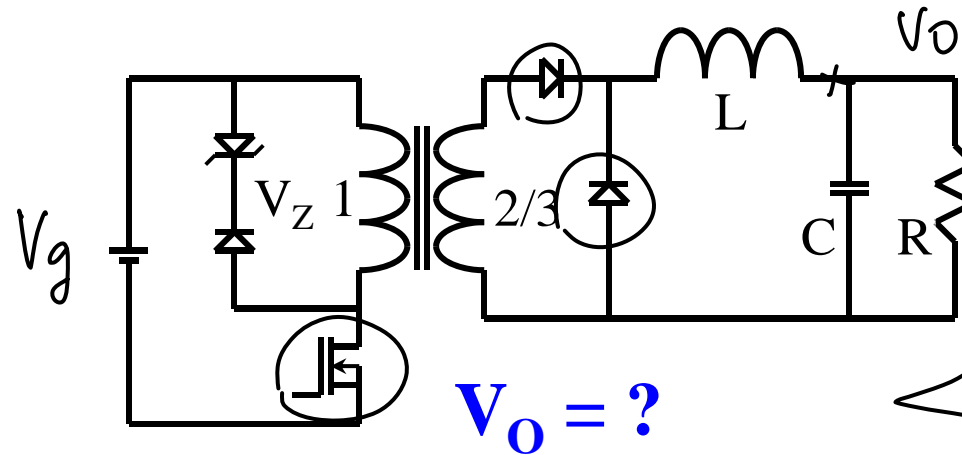

$V_o = ?$

$< \underline{\underline{6.4 \text{ V}}}$

$$\left[ \left( V_g - V_T - I_p R_p \right) \frac{2}{3} - V_d - I_L R_L - I_L R_S - \underline{\underline{V_o}} \right] T_{on} + \left( -V_d - I_L R_L - V_o \right) T_{off}$$

$V_t: 0.4 \text{ V}$ ;  $V_d: 0.8 \text{ V}$ ;  $R_p: 30 \text{ m}\Omega$ ;  $R_s: 60 \text{ m}\Omega$ ;  $R_l: 15 \text{ m}\Omega$ ;

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 3

$$V_O = ?$$

$V_t: 0.4 \text{ V}; V_d: 0.8 \text{ V}; R_p: 30 \text{ m}\Omega; R_s: 60 \text{ m}\Omega; R_l: 15 \text{ m}\Omega;$

$V_G: 24 \text{ V}; D: 0.4; R: 1.0 \text{ ohm}; T_S: 20 \text{ }\mu\text{s};$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 3

$$V_O = ?$$

$V_t: 0.4 \text{ V}; V_d: 0.8 \text{ V}; R_p: 30 \text{ m}\Omega; R_s: 60 \text{ m}\Omega; R_l: 15 \text{ m}\Omega;$


$V_G: 24 \text{ V}; D: 0.4; R: 1.0 \text{ ohm}; T_S: 20 \text{ }\mu\text{s};$



# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 3

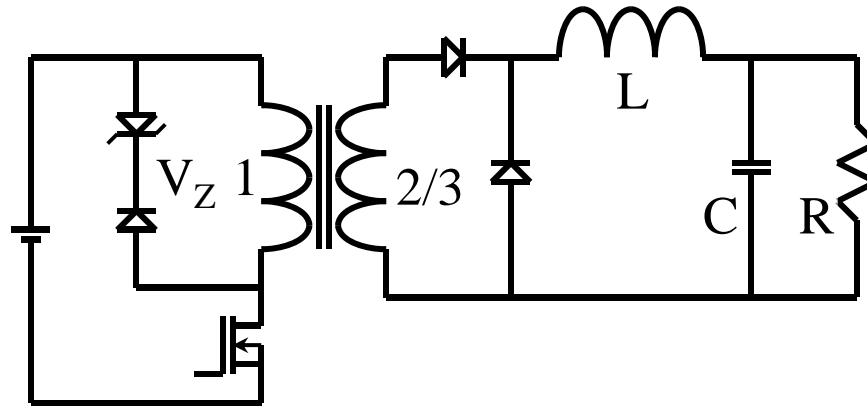


Magnetisation Loss: ?

$L_m: 500 \mu\text{H}$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 3

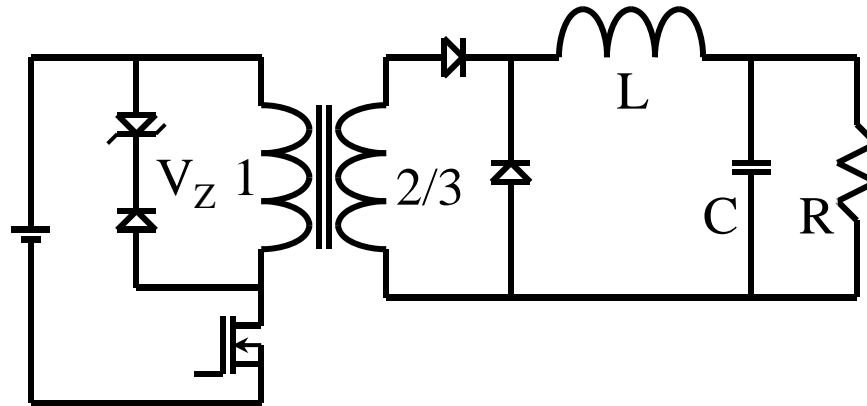

Magnetisation Loss: ?

$L_m: 500 \mu\text{H}$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 3

#### Magnetisation Loss:

$L_m: 500 \mu\text{H}$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 3

Efficiency: ?

$L_m: 500 \mu\text{H}$

# **Switched Mode Power Conversion**


## **Problem Set 03**

### **Problem No. 3**

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 4

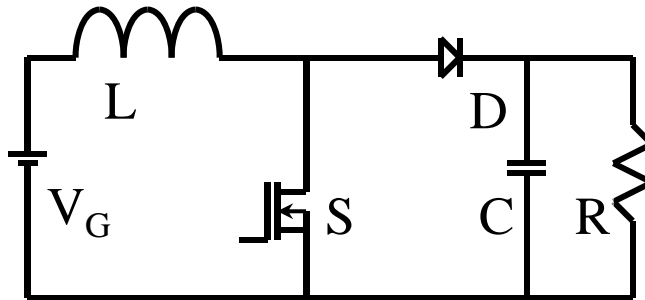


$V_G$ : 20 V;  $D$ : 0.5;  $R$ : 50 ohm;  $V_O$ : 50 V;  $L = 20 \mu\text{H}$ ;

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 4

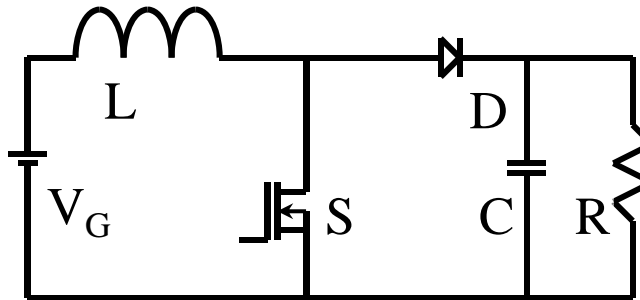


**What is the Conduction Mode?**

$V_G$ : 20 V;  $D$ : 0.5;  $R$ : 50 ohm;  $V_O$ : 50 V;  $L = 20 \mu\text{H}$ ;

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 4

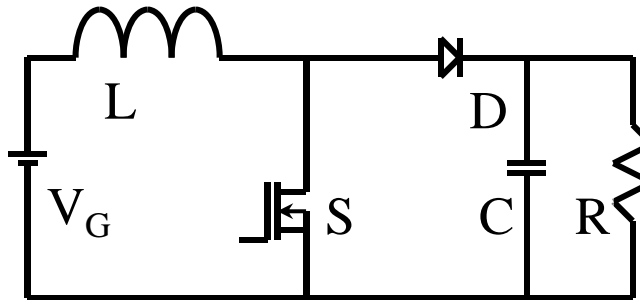

**What is the Average Input Current?**

$V_G$ : 20 V;  $D$ : 0.5;  $R$ : 50 ohm;  $V_O$ : 50 V;  $L = 20 \mu\text{H}$ ;



# **Switched Mode Power Conversion**

## **Problem Set 03**

### **Problem No. 4**

**Periodic Input Current Waveshape**

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 4

**Periodic Input Current Waveshape**

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 4

Switching Frequency?

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 4

Conduction Parameter?

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 4


$V_G$ : 20 V;  $D$ : 0.5;  $R$ : 50 ohm;  $V_O$ : 50 V;  $L = 20 \mu\text{H}$ ;

.

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 5

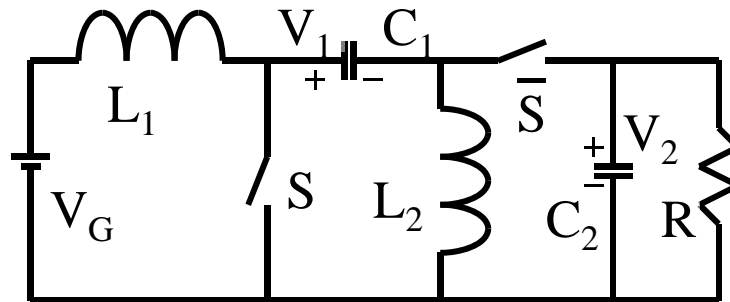


$V_G$ : 40 V;  $D$ : 0.35;  $R$ : 20 ohm;

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 5

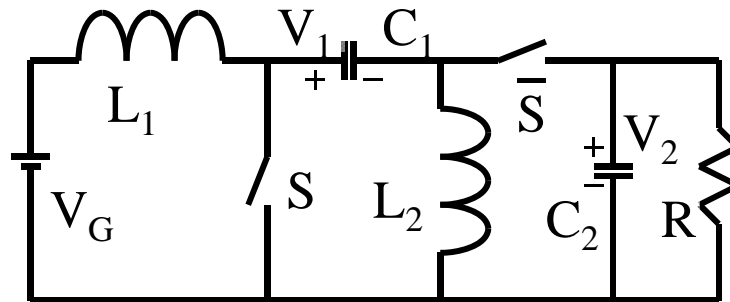

Volt-Sec Balance &  $V_1$  and  $V_2$

Volt-Sec Balance on  $L_2$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 5

Volt-Sec Balance &  $V_1$  and  $V_2$


Volt-Sec Balance on  $L_2$



# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 5

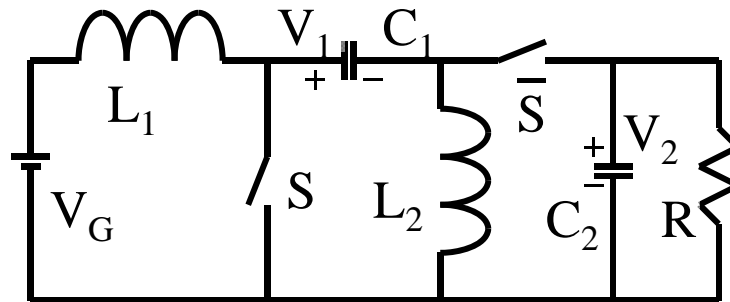

Volt-Sec Balance &  $V_G$  and  $V_1$

Volt-Sec Balance on  $L_1$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 5


Volt-Sec Balance &  $V_G$  and  $V_1$

Volt-Sec Balance on  $L_1$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 5

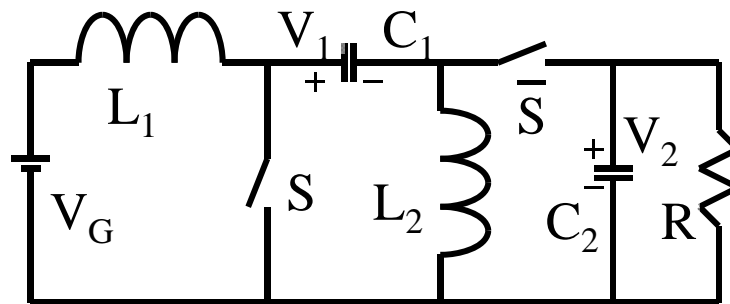

Periodic Current in  $L_2$

Voltage Across  $L_2$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 5


Periodic Current in  $L_2$

Voltage Across  $L_2$

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 5

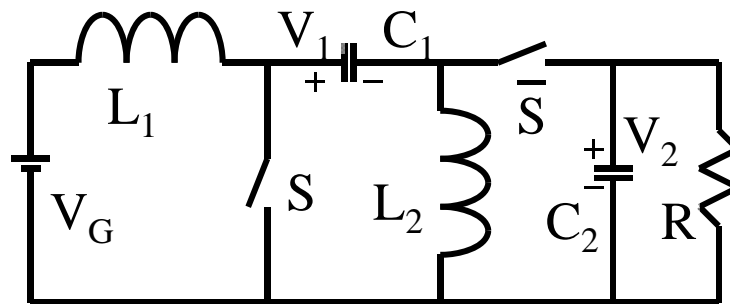

Periodic Current in  $L_2$

Border Between CCM and DCM

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 5


Condition on  $K = 2L_2/RT_s$

Border Between CCM and DCM

# Switched Mode Power Conversion

## Problem Set 03

### Problem No. 5

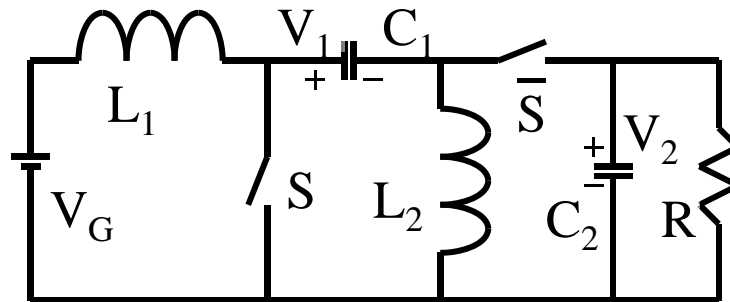

$V_G$ : 40 V;  $D$ : 0.35;  $R$ : 20 ohm;