

# **Switched Mode Power Conversion**


## **Primitive Converters**

### **Interconnection of Switches & Energy Storage Elements**

# Switched Mode Power Conversion

## Primitive Converters

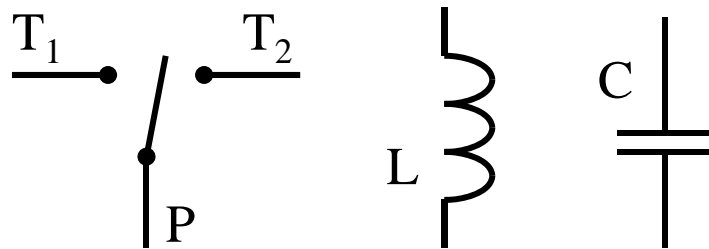
### Interconnection of Switches & Energy Storage Elements



# Switched Mode Power Conversion
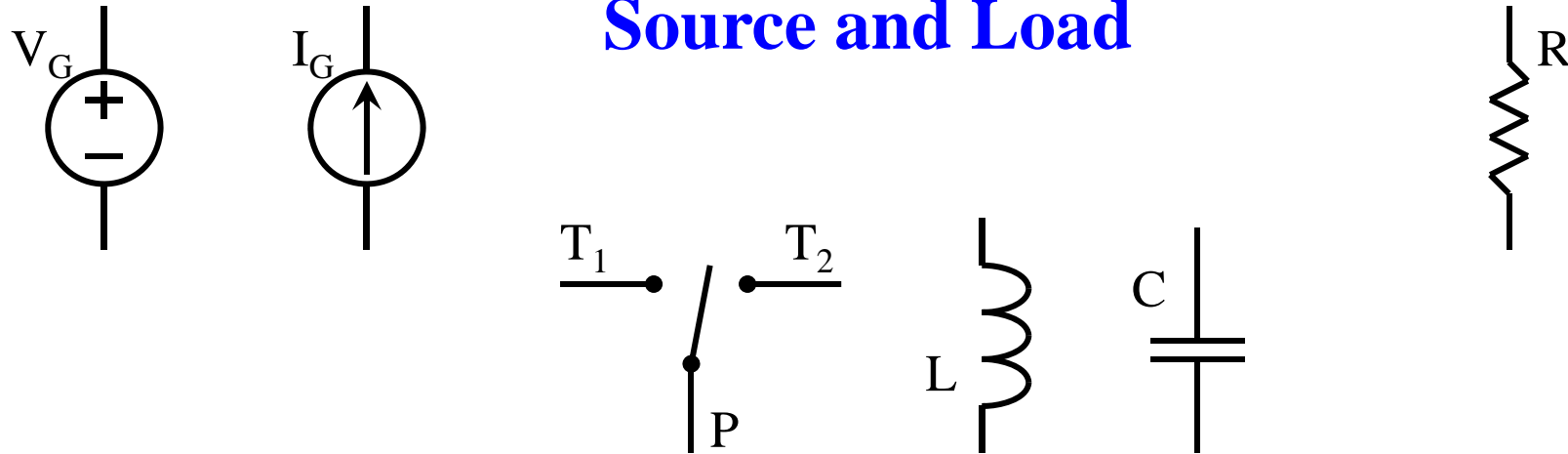
## Primitive Converters

Interconnection  
of  
Switches & Energy Storage Elements  
to  
Source and Load



# **Switched Mode Power Conversion**

## **Primitive Converters**

### **Interconnection Rules**

**Sources may not be Overloaded**

**Voltage Sources are not to be Shorted**

**Current Sources are not to be Opened**

### **Conservation of Energy**


**Inductor Currents are not to be Interrupted**

**Capacitor Voltages are not to be Shorted**

# Switched Mode Power Conversion

## Primitive Converters

### Interconnection Rules

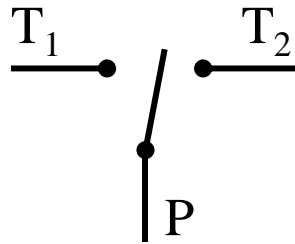

**Voltage sources may not be connected  
across  $PT_1$  or  $PT_2$**

**No Short Circuit of Voltage Sources**


**Capacitors may not be connected across  
 $PT_1$  or  $PT_2$**

**No Disruption of Energy on the Capacitor**

# Switched Mode Power Conversion

## Primitive Converters

### Interconnection Rules

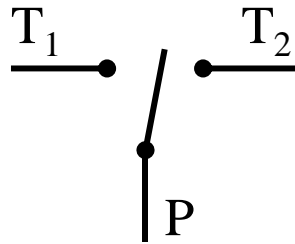

Current sources may not be connected  
in series with  $T_1$  or  $T_2$

**No Open Circuit of Current Sources**


Inductor may not be connected  
in series with  $T_1$  or  $T_2$

**No Disruption of Energy on the Inductor**

# Switched Mode Power Conversion

## Primitive Converters

### Acceptable Switch-Storage Cells

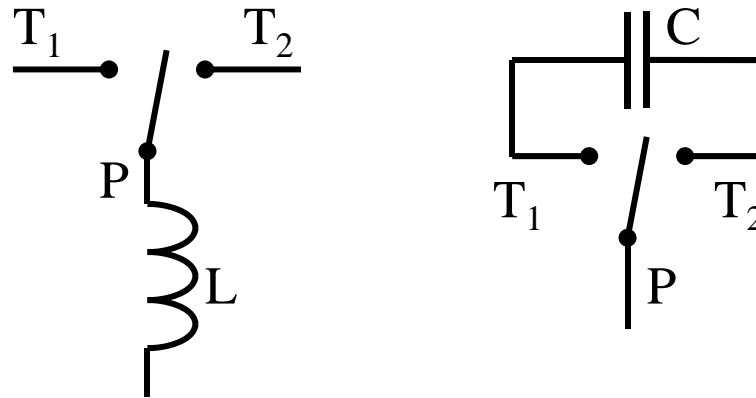


Two possible switch+storage cells

These are dual of each other

# Switched Mode Power Conversion

## Primitive Converters
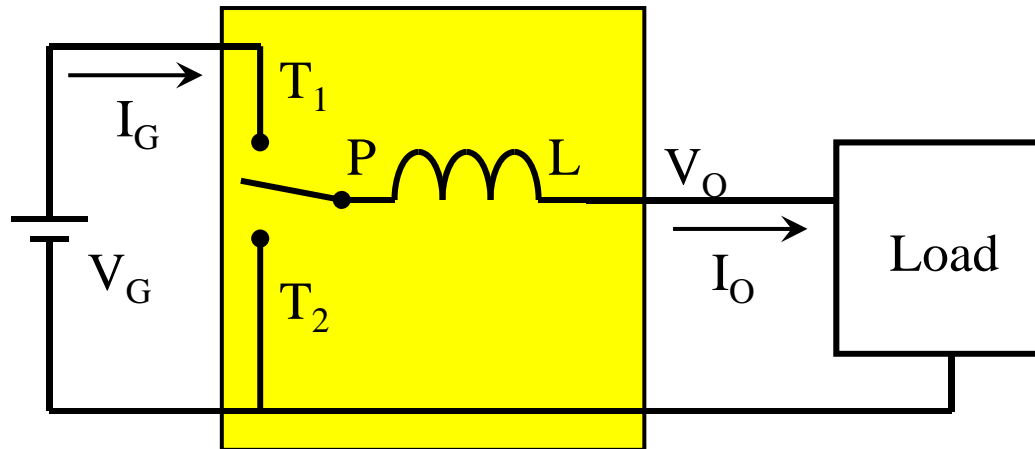
### Primitive Voltage to Current Converter




Input average quantities:  $V_G$  and  $I_G$   
Output average quantities:  $I_O$  and  $V_O$



# Switched Mode Power Conversion

## Primitive Converters

### Strategy of Operation & Control

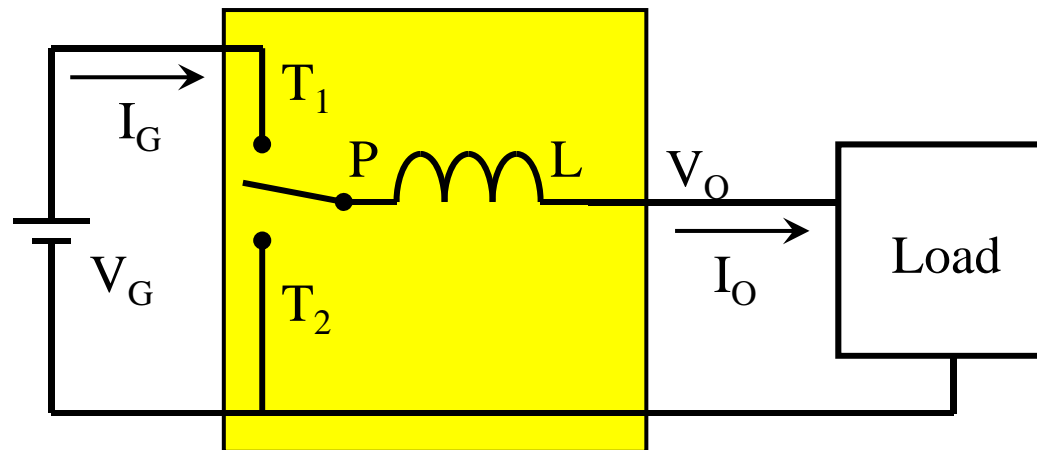

### Constant Switching Period


$T_1$  ON Time  $T_{ON}$  ;  $T_2$  OFF Time  $T_{OFF}$

$$T_{ON} + T_{OFF} = T_S$$

# Switched Mode Power Conversion

## Primitive Converters
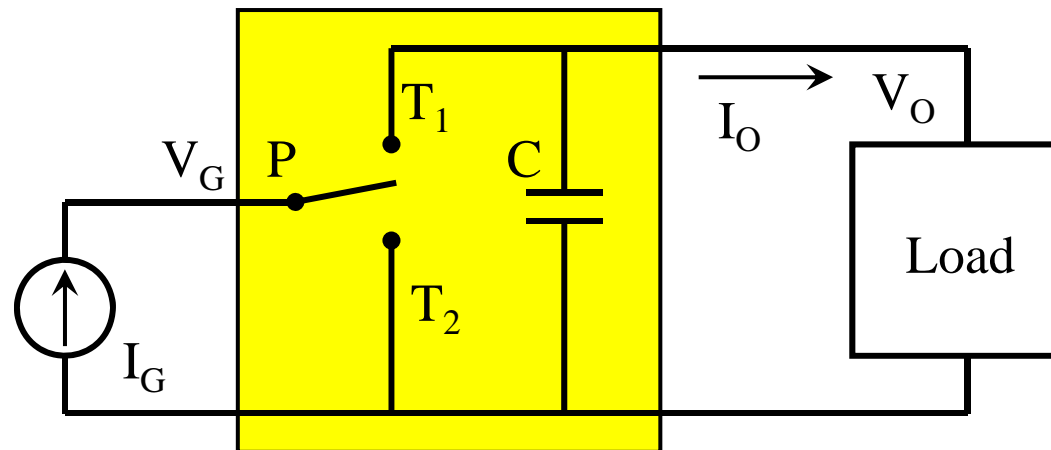
### Primitive Current to Voltage Converter




Input average quantities:  $I_G$  and  $V_G$   
Output average quantities:  $V_O$  and  $I_O$

# Switched Mode Power Conversion

## Primitive Converters
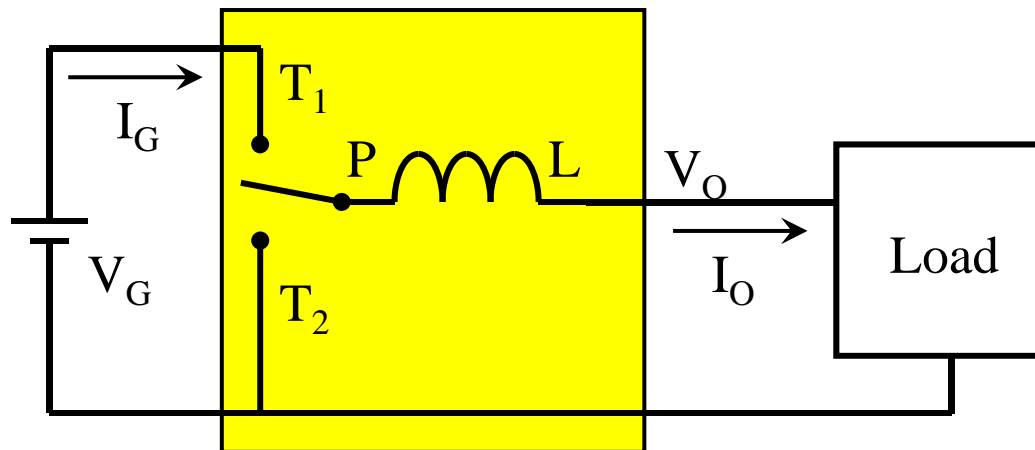
### Primitive Voltage to Current Converter




### Ideal Performance Measures

# Switched Mode Power Conversion

## Primitive Converters
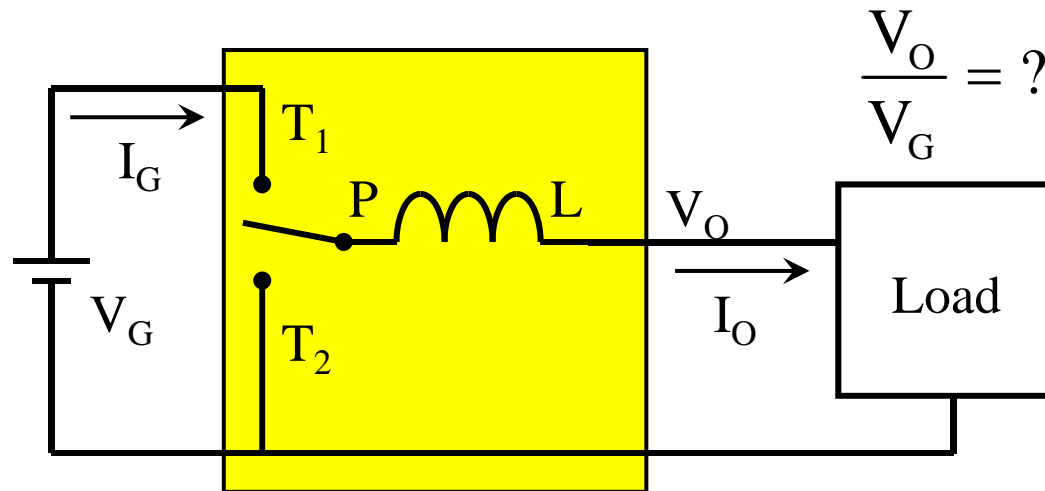
### Primitive Voltage to Current Converter




### First Performance Measure

## Forward Voltage Conversion Ratio

# Switched Mode Power Conversion

## Primitive Converters
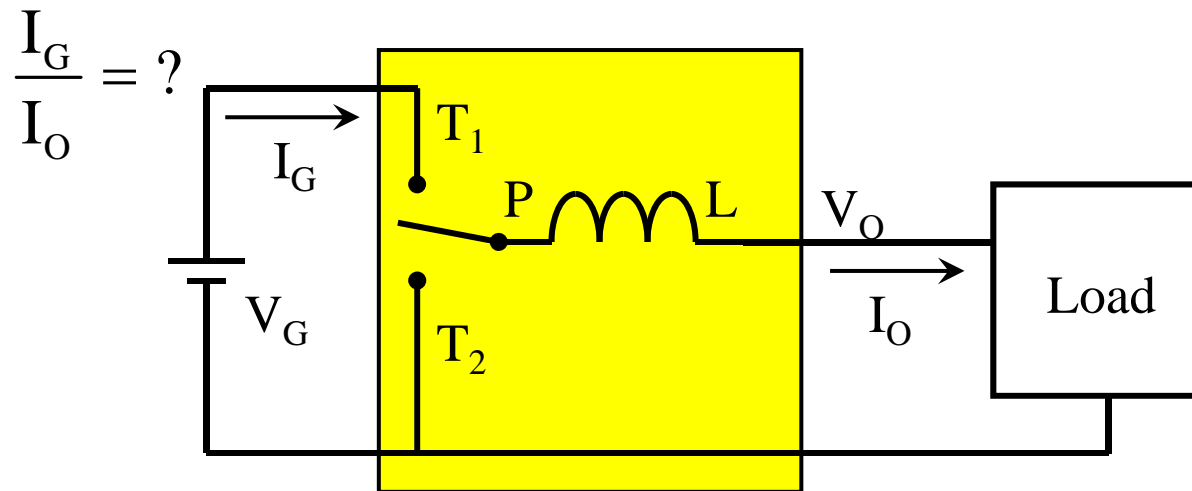
### Primitive Voltage to Current Converter



### Performance Measures


Forward Voltage Conversion Ratio

Reverse Current Conversion Ratio

# Switched Mode Power Conversion

## Primitive Converters

### Forward Voltage Conversion Ratio

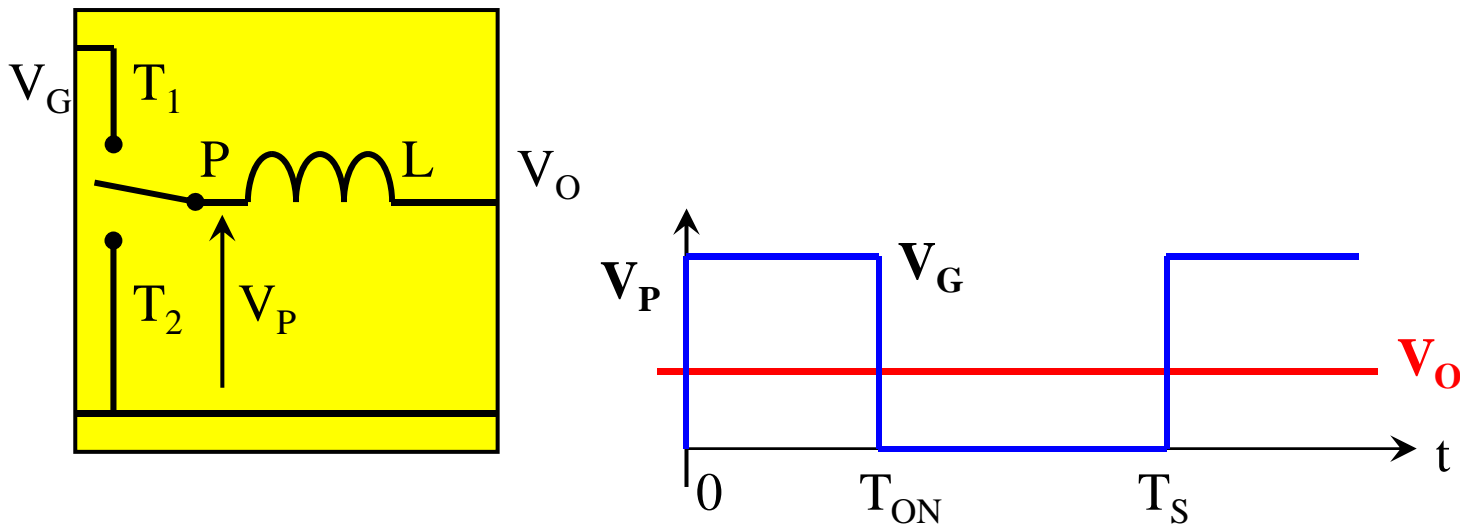


**Average voltage across inductor in one cycle is zero**


# Switched Mode Power Conversion

## Primitive Converters

### Forward Voltage Conversion Ratio

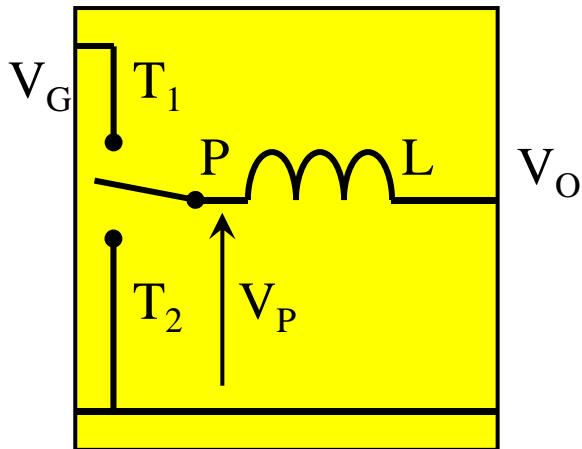
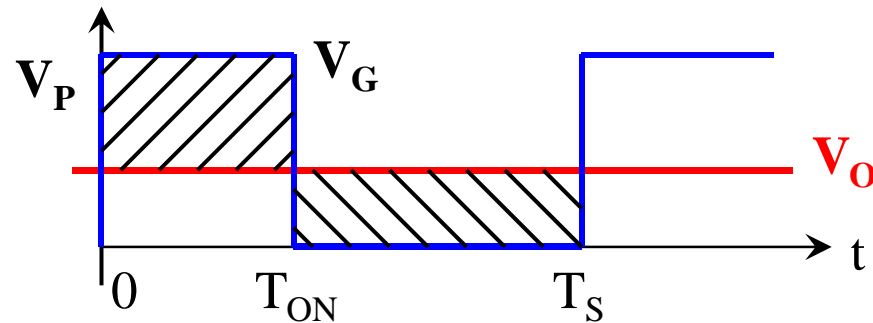
$$(V_G - V_O)T_{ON} - V_O(T_S - T_{ON}) = 0$$




$$\frac{V_O}{V_G} = \frac{T_{ON}}{T_S} = D$$

# Switched Mode Power Conversion

## Primitive Converters

### Reverse Current Transfer Ratio

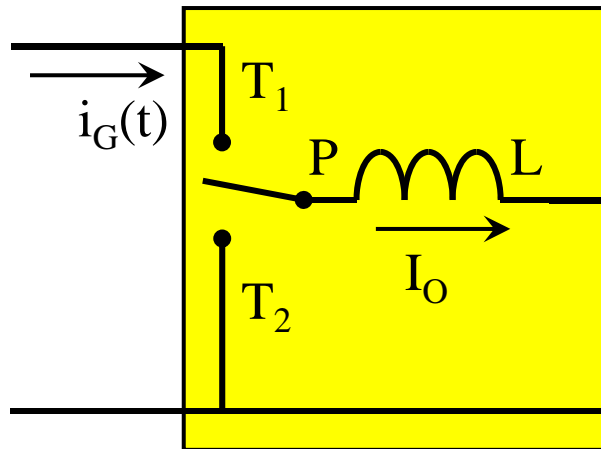

$$\frac{I_G}{I_O} = ?$$


### Reverse Current Conversion Ratio



# Switched Mode Power Conversion

## Primitive Converters

### Reverse Current Transfer Ratio

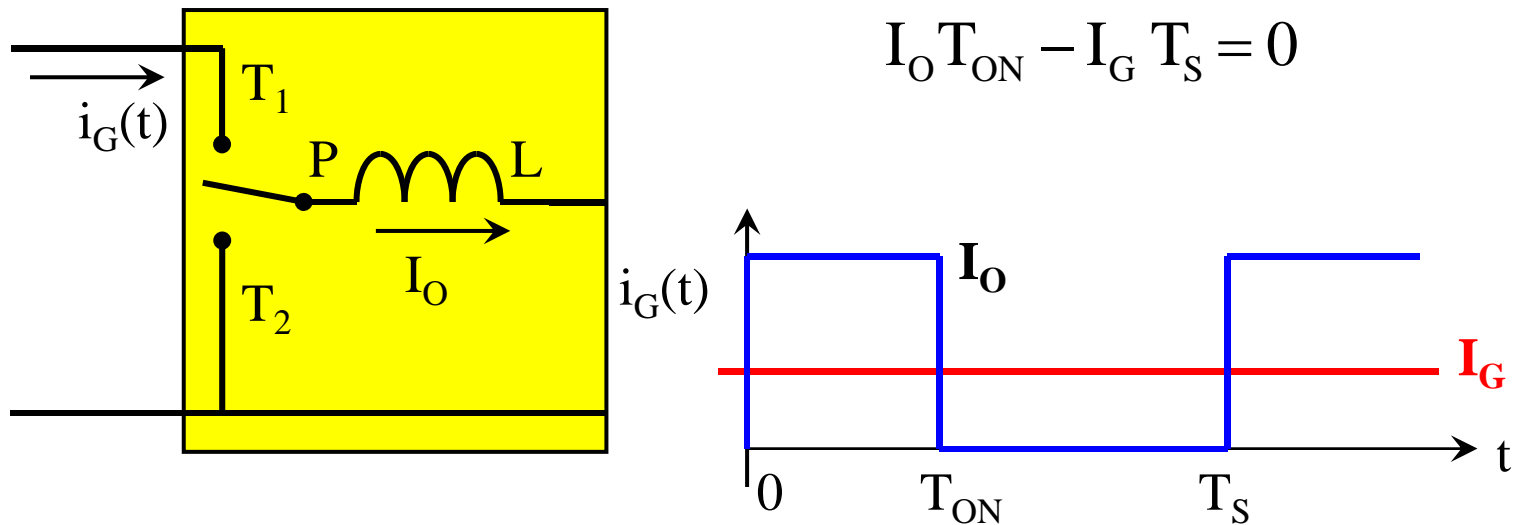


$$\frac{I_G}{I_O} = \frac{T_{ON}}{T_S} = D$$

$$\frac{V_O}{V_G} = \frac{I_G}{I_O} = \frac{T_{ON}}{T_S} = D$$

# Switched Mode Power Conversion

## Primitive Converters
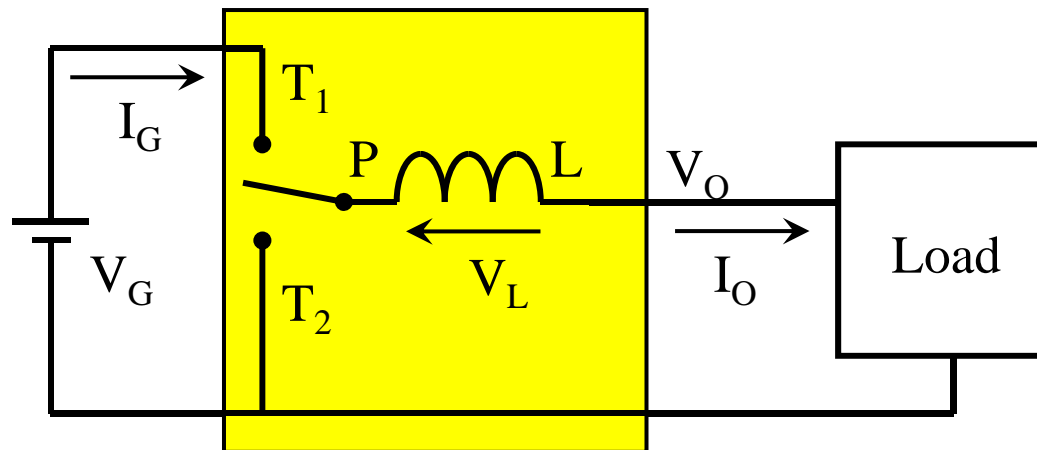
### Primitive Voltage to Current Converter




### Non-Ideality in the Converter Current $I_O$

# Switched Mode Power Conversion

## Primitive Converters

### Ripple Current in the Inductor

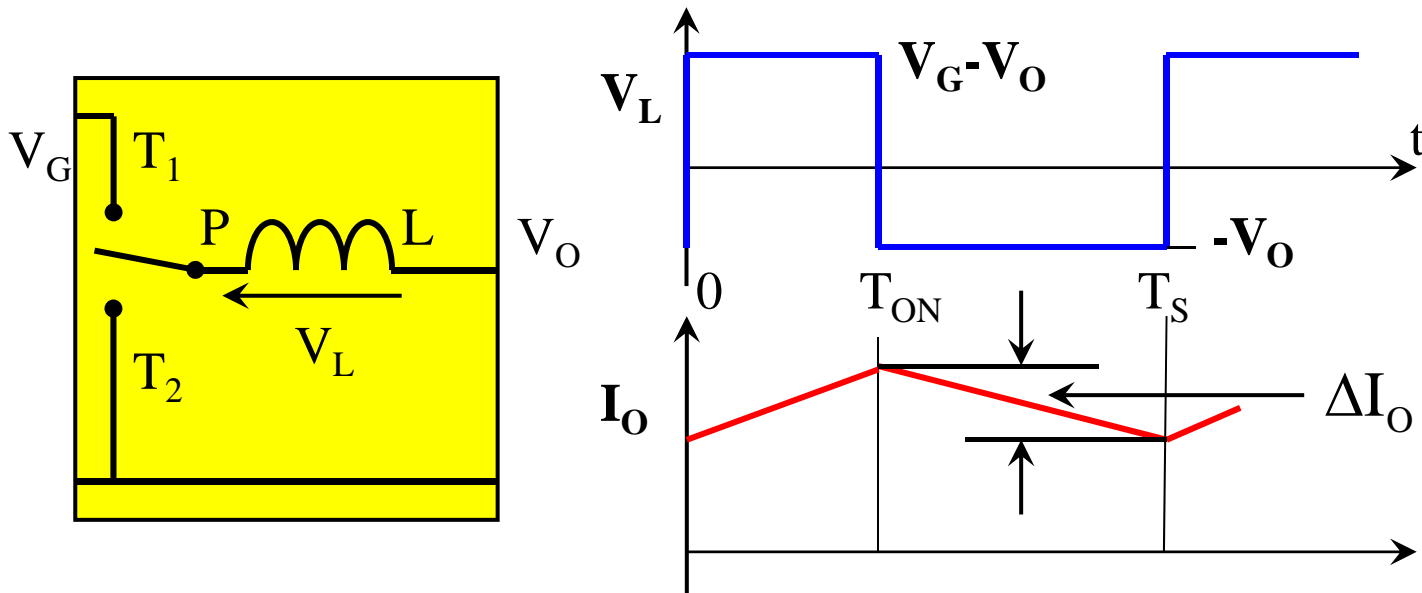


$$\Delta I_O = \frac{V_O}{L} (T_S - T_{ON}) = \frac{V_O}{L} (1 - D) T_S$$

# Switched Mode Power Conversion

## Primitive Converters

### Normalised Ripple Current

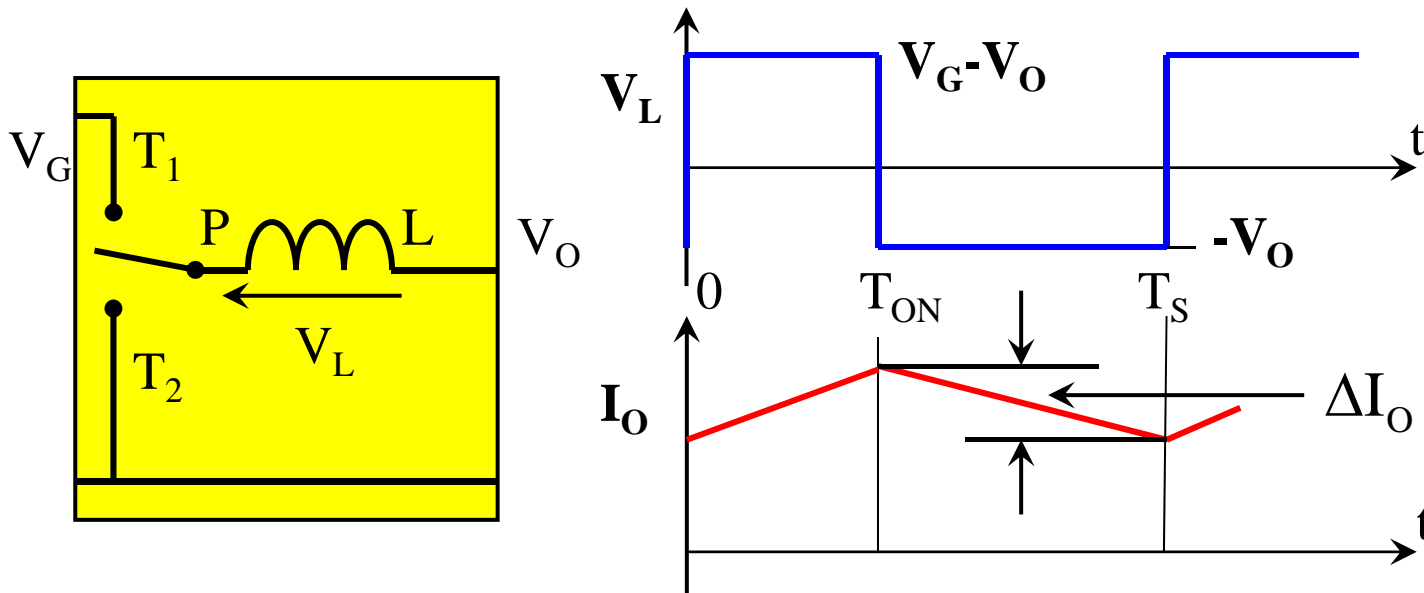


$$\frac{\Delta I_O}{I_O} = \frac{V_O}{I_O L} (1-D) T_s = \frac{(1-D) T_s}{(L/R)}$$

# Switched Mode Power Conversion

## Primitive Converters
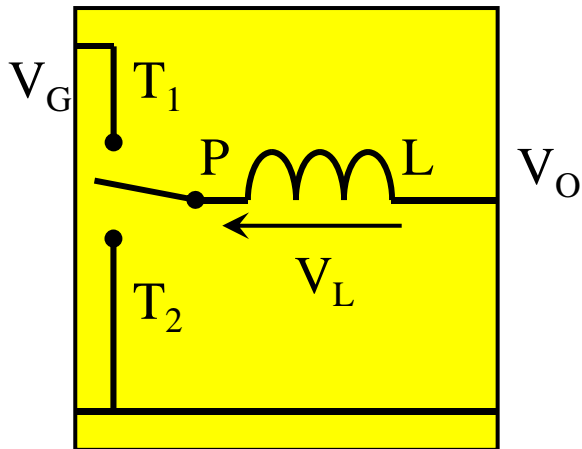
### Condition for Ripple Current to be Low



$$\frac{\Delta I_O}{I_O} = \frac{(1-D)T_s}{(L/R)} \ll 1$$


$$T_s \ll \frac{L}{R}$$

Switching Period  $\ll$  Circuit Time Constant

# Switched Mode Power Conversion

## Primitive Converters
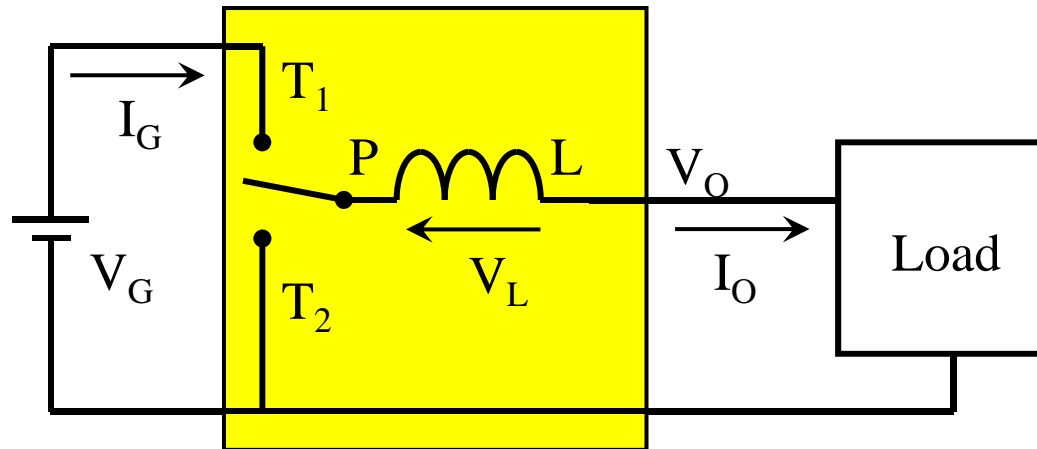
### Primitive Voltage to Current Converter





**Non-Ideality in the Switches – Conduction Drop**

# Switched Mode Power Conversion

## Primitive Converters

Switches are Realised by Real Devices

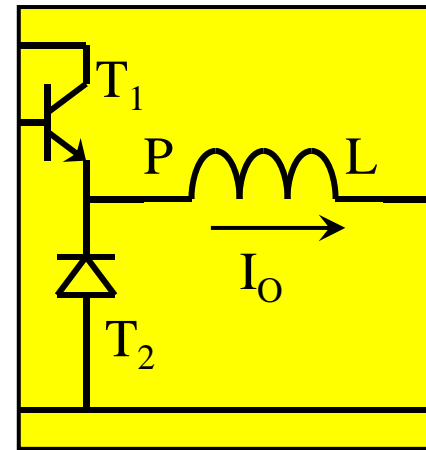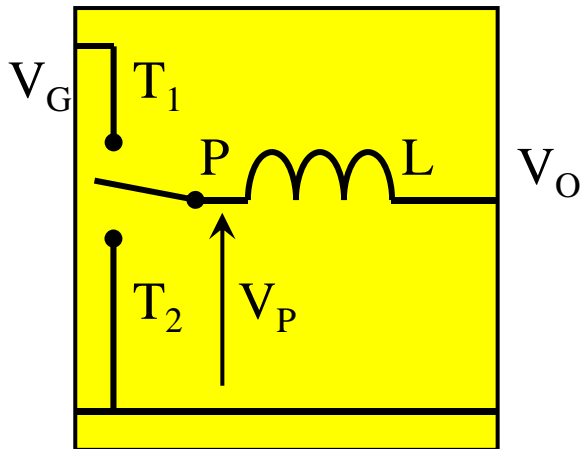



$T_{1P}$  Drop is  $V_T$ ;  $T_{2P}$  Drop is  $V_D$



# Switched Mode Power Conversion
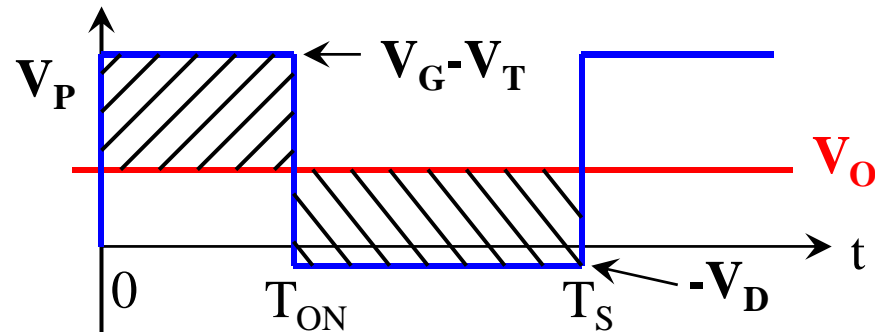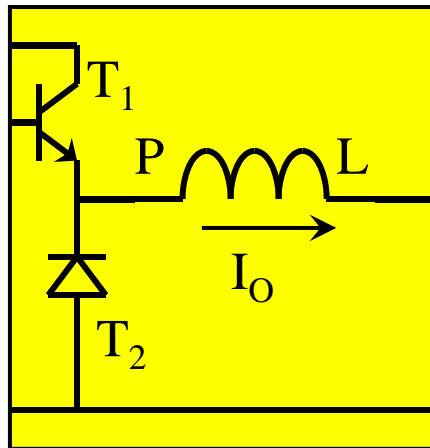
## Primitive Converters

$T_{1P}$  Drop is  $V_T$ ;  $T_{2P}$  Drop is  $V_D$





Inductor ON State Voltage is  $V_G - V_T - V_O$

Inductor OFF State Voltage is  $-V_D - V_O$

# Switched Mode Power Conversion

## Primitive Converters

### Volt-Sec Balance on the Inductor

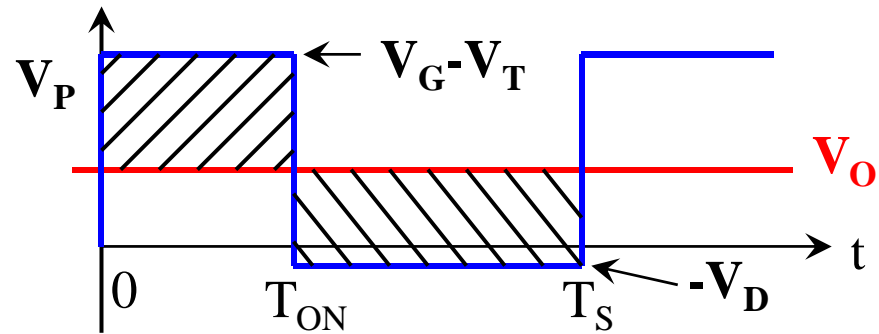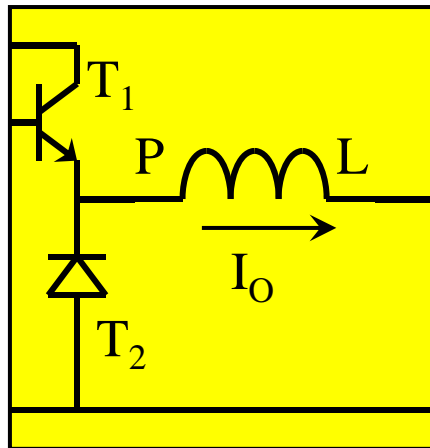


$$(V_G - V_T - V_O)T_{ON} - (V_D + V_O)(T_S - T_{ON}) = 0$$

# Switched Mode Power Conversion

## Primitive Converters

### Forward Voltage Transfer Ratio

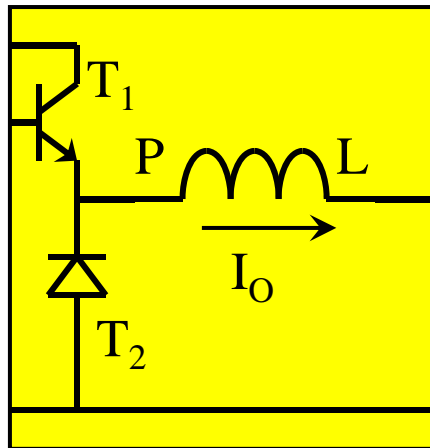


$$(V_G - V_T)T_{\text{ON}} - V_D T_{\text{OFF}} = V_O T_S$$

$$V_O = DV_G \left( 1 - \frac{V_T}{V_G} - \frac{(1-D)V_D}{DV_G} \right)$$


# Switched Mode Power Conversion

## Primitive Converters

### Reverse Current Transfer Ratio

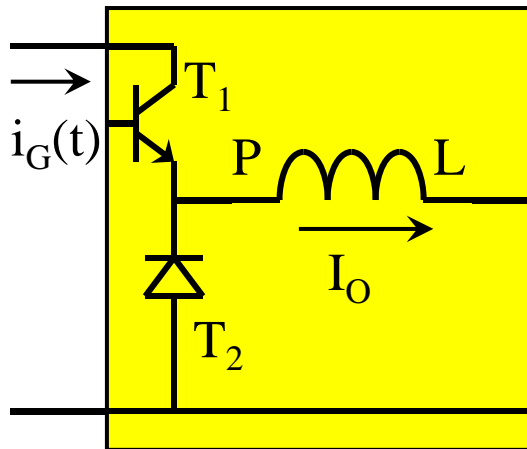

$$I_O T_{ON} - I_G T_S = 0$$

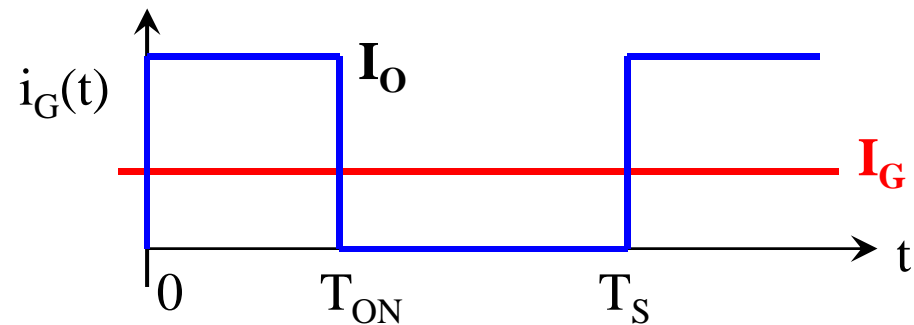


$$\frac{I_G}{I_O} = \frac{T_{ON}}{T_S} = D$$


# Switched Mode Power Conversion
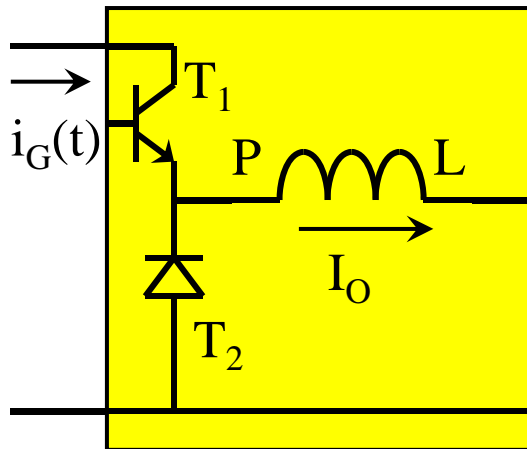
## Primitive Converters

Switch Non-ideality is Series Non-ideality


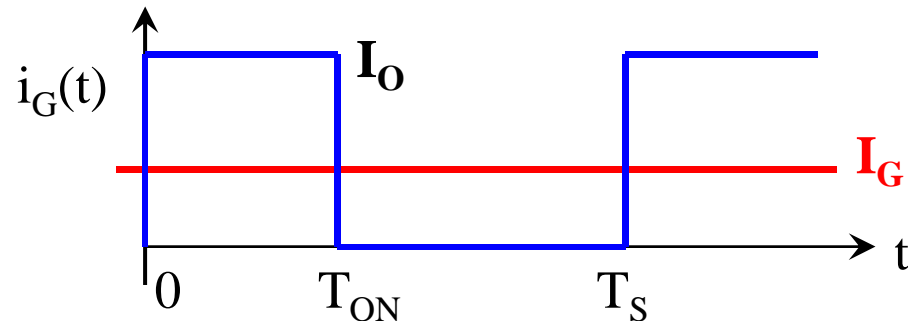
$$\frac{I_G}{I_O} = \frac{T_{ON}}{T_S} = D$$




Switch Non-idealities have no Effect  
on Current Ratio

# Switched Mode Power Conversion

## Primitive Converters

### Efficiency

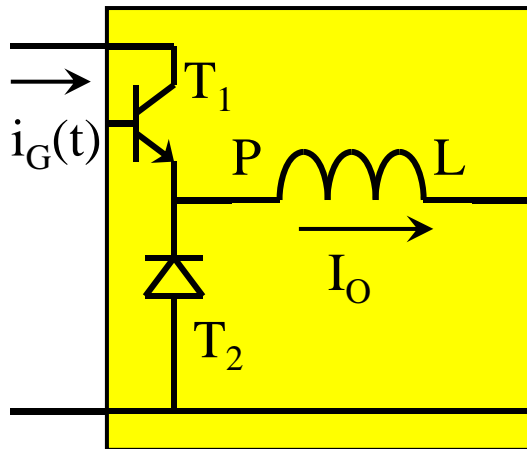

$$\frac{I_G}{I_O} = \frac{T_{ON}}{T_S} = D$$


$$\frac{V_O}{V_G} = D \left( 1 - \frac{V_T}{V_G} - \frac{(1-D)V_D}{DV_G} \right)$$

$$\eta = \frac{V_O I_O}{V_G I_G} = \left( 1 - \frac{V_T}{V_G} - \frac{(1-D)V_D}{DV_G} \right)$$

# Switched Mode Power Conversion

## Primitive Converters
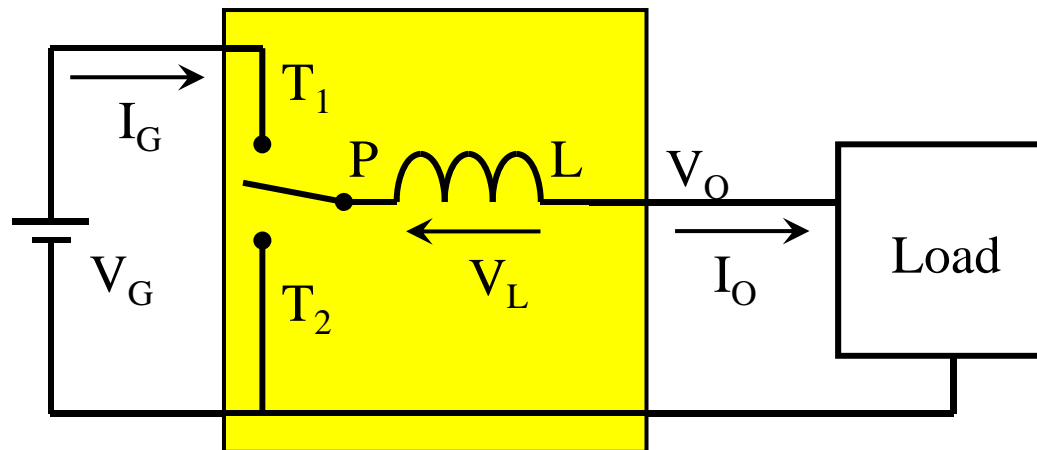
### Primitive Voltage to Current Converter





### Non-Ideality in the Source & Inductor

# Switched Mode Power Conversion

## Primitive Converters
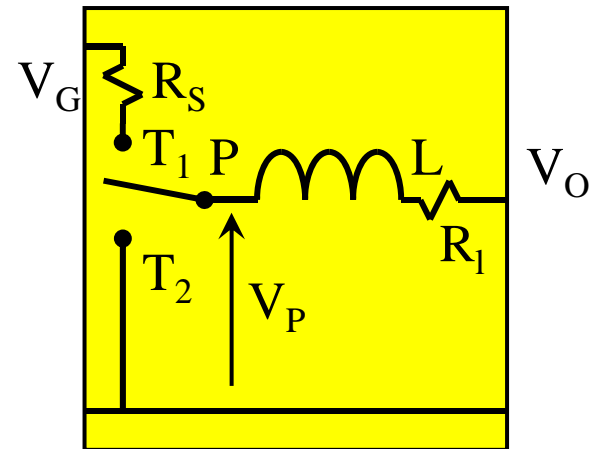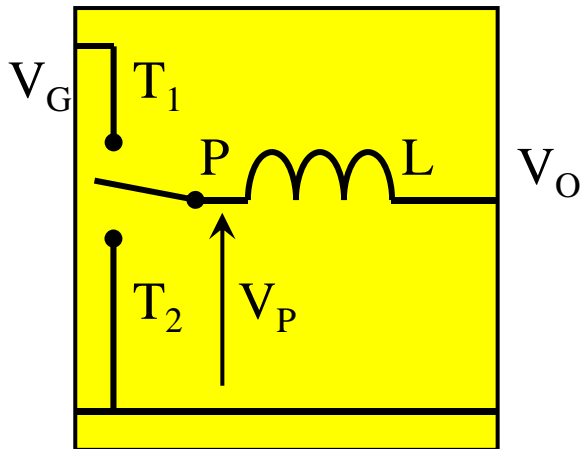
### Source & Inductor Have Internal Resistances




Source Resistance is  $R_S$   
Inductor Resistance is  $R_L$



# Switched Mode Power Conversion

## Primitive Converters

### Volt-Sec Balance on the Inductor

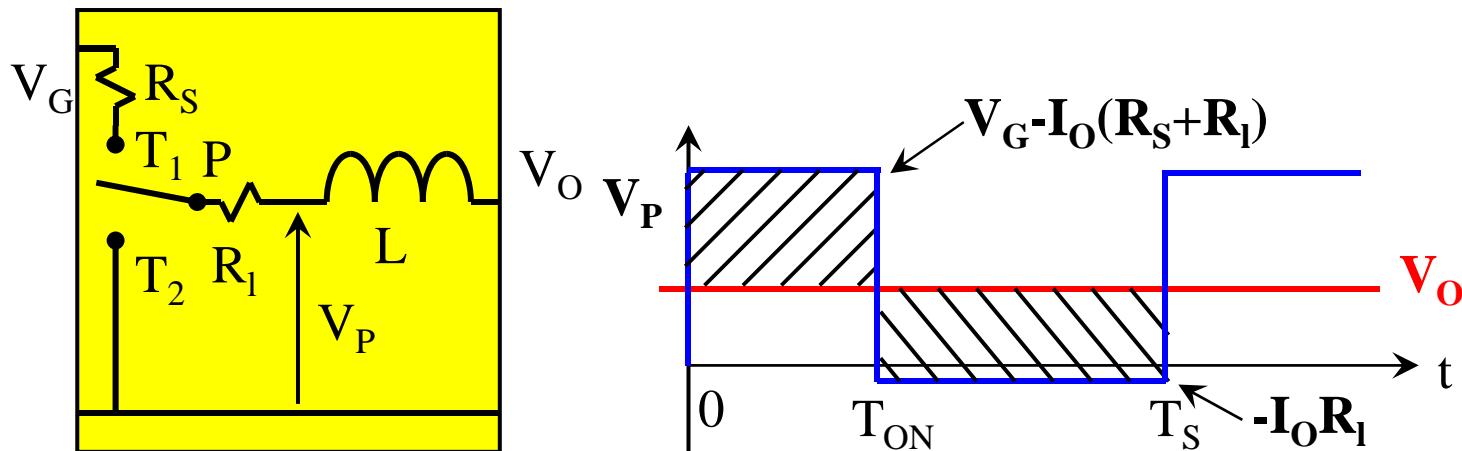


$$(V_G - I_O(R_S + R_1) - V_O)T_{ON} - (I_O R_1 + V_O)(T_S - T_{ON}) = 0$$

# Switched Mode Power Conversion

## Primitive Converters

### Forward Voltage Transfer Ratio

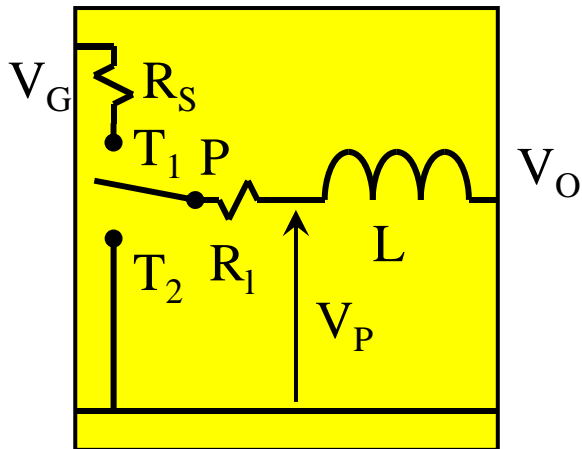

$$\frac{V_O}{V_G} = D \left( \frac{R}{R + DR_S + R_1} \right)$$


$$\frac{V_O}{V_G} = D \left( \frac{1}{1 + \frac{DR_S}{R} + \frac{R_1}{R}} \right)$$

$$(V_G - I_O(R_S + R_1) - V_O)T_{ON} - (I_O R_1 + V_O)(T_S - T_{ON}) = 0$$


# Switched Mode Power Conversion

## Primitive Converters

### Reverse Current Transfer Ratio

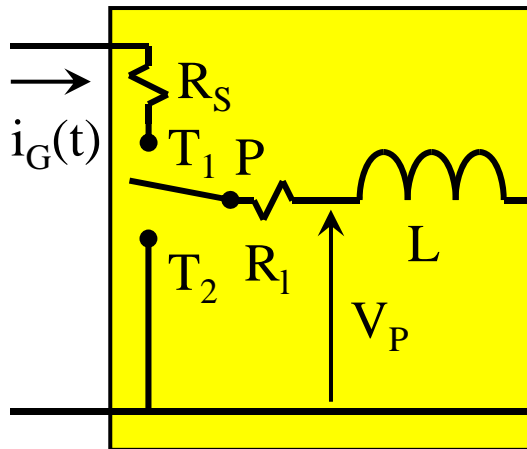

$$I_O T_{ON} - I_G T_S = 0$$

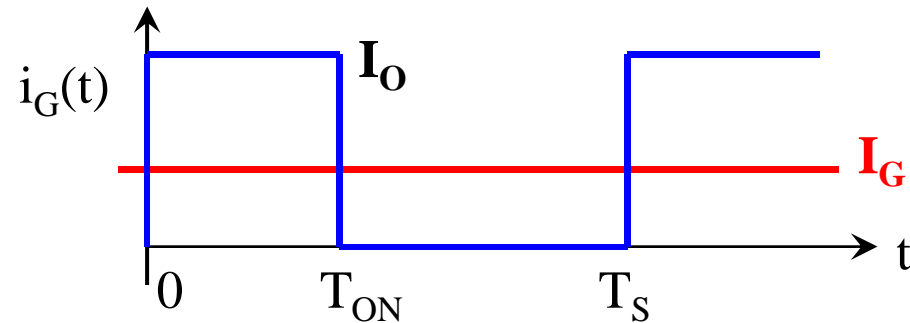


$$\frac{I_G}{I_O} = \frac{T_{ON}}{T_S} = D$$

# Switched Mode Power Conversion

## Primitive Converters

### Efficiency

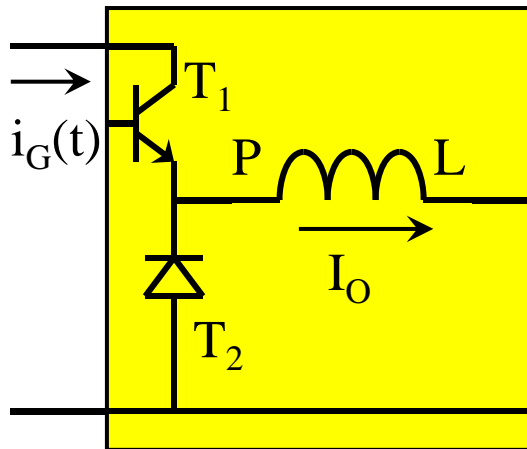

$$\frac{I_G}{I_O} = \frac{T_{ON}}{T_S} = D$$

$$\frac{V_O}{V_G} = D \left( \frac{R}{R + DR_S + R_1} \right)$$

$$\eta = \frac{V_O I_O}{V_G I_G} = \left( \frac{1}{1 + \frac{DR_S}{R} + \frac{R_1}{R}} \right)$$

# Switched Mode Power Conversion

## Primitive Converters

### Efficiency with Switch/Source/Inductor Drops

$$\eta = \frac{V_O I_O}{V_G I_G} = \left( \frac{1 - \frac{V_T}{V_G} - \frac{(1-D)V_D}{DV_G}}{1 + \frac{DR_s}{R} + \frac{R_l}{R}} \right)$$

# Switched Mode Power Conversion

## Primitive Converters

### Guidelines for Good Efficiency

$$\eta = \frac{V_O I_O}{V_G I_G} = \left( \frac{1 - \frac{V_T}{V_G} - \frac{(1-D)V_D}{DV_G}}{1 + \frac{DR_s}{R} + \frac{R_1}{R}} \right)$$


$$V_T \ll V_G ; V_D \ll V_O$$

$$R_s \ll R ; R_1 \ll R$$

# Switched Mode Power Conversion

## Primitive Converters
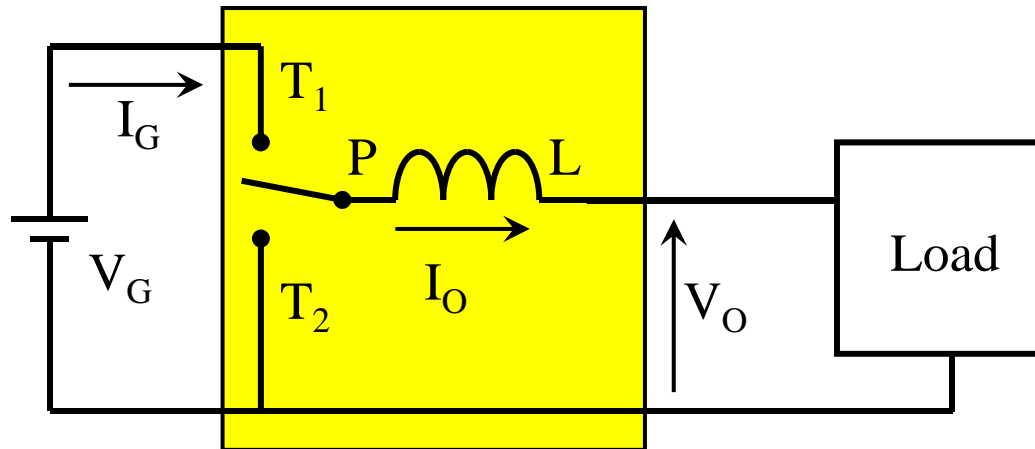
### Non-ideality Related to Output Voltage




**Output Voltage Ripple is a Function of the Load**

# Switched Mode Power Conversion

## Primitive Converters
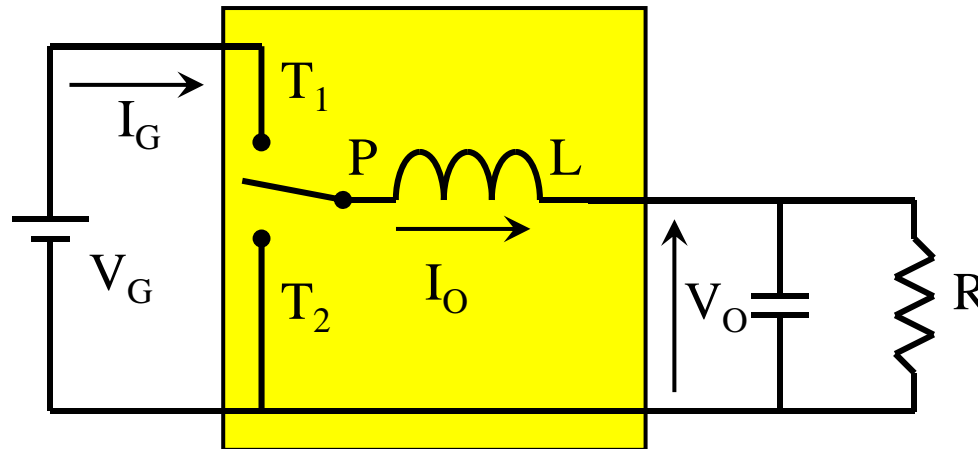
### Evaluation of the Output Voltage Ripple




Capacitor Supported Load is Common



# Switched Mode Power Conversion

## Primitive Converters
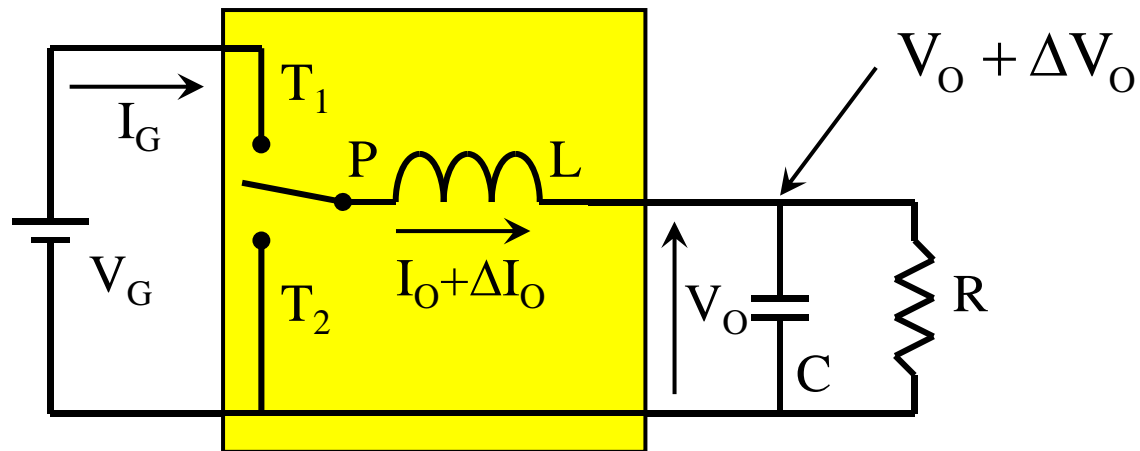
### Inductor Current & Output Voltage Ripple




Output Voltage Ripple is  $\Delta V_O$

# Switched Mode Power Conversion

## Primitive Converters

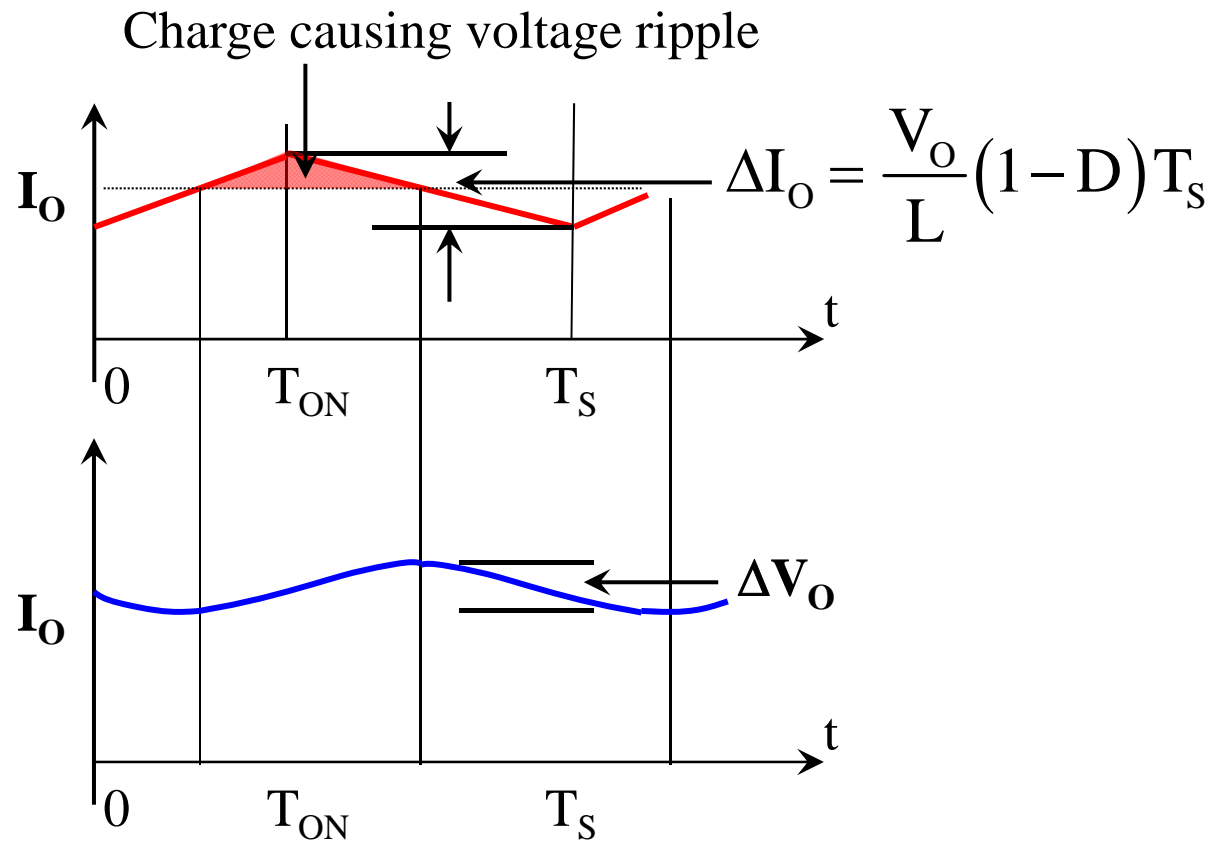
### Inductor Current & Output Voltage Ripple



# Switched Mode Power Conversion

## Primitive Converters
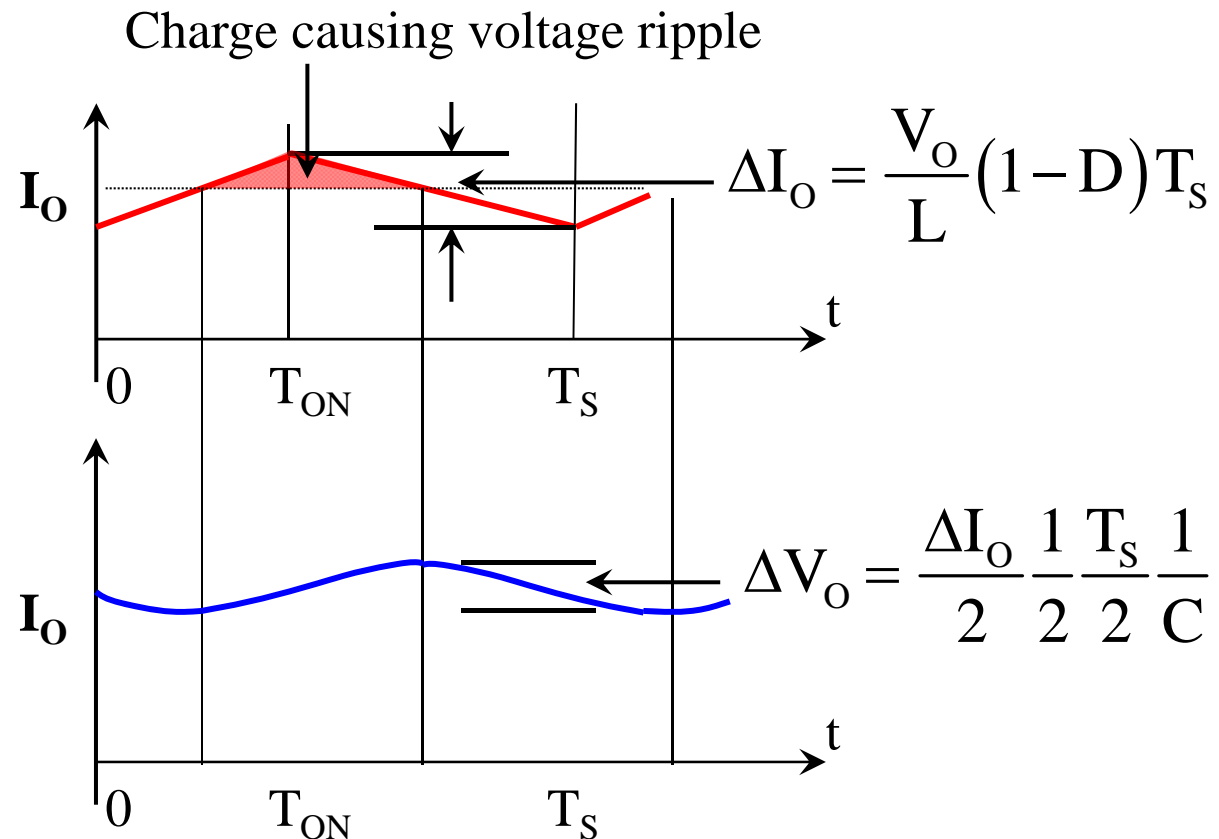
### Inductor Current & Output Voltage Ripple



# Switched Mode Power Conversion

## Primitive Converters

### Inductor Current & Output Voltage Ripple

$$\Delta I_o = \frac{V_o}{L} (1-D) T_s$$

$$\Delta V_o = \frac{V_o (1-D) T_s}{2L} \frac{1}{2} \frac{T_s}{2} \frac{1}{C} = \frac{V_o (1-D) T_s^2}{8LC}$$

$$\frac{\Delta V_o}{V_o} = \frac{(1-D) T_s^2}{8LC}$$

# Switched Mode Power Conversion

## Primitive Converters

### Guidelines for Low Output Ripple

$$\frac{\Delta V_o}{V_o} = \frac{(1-D)T_s^2}{8LC}$$

Switching Period  $\ll$  Natural Frequency

$$T_s \ll \frac{1}{\sqrt{LC}}$$

# Switched Mode Power Conversion

## Primitive Converters

### Summary of Steady State Performance

Voltage Gain  $V_O/V_G$

Current Gain  $I_O/I_G$

Current Ripple  $\Delta I_O/I_O$

Voltage Ripple  $\Delta V_O/V_O$

Switch Non-ideality

Source Non-ideality

Storage Non-ideality

Efficiency

# Switched Mode Power Conversion

## Primitive Converters

### Summary of Steady State Performance

Inductor Volt-sec Balance:  $V_O/V_G$

Current Averaging:  $I_O/I_G$


Inductor Volt-sec in Sub-period:  $\Delta I_O/I_O$

Capacitor Charge in Sub-period:  $\Delta V_O/V_O$

Inductor Volt-sec Balance with Non-ideality:  $\eta$

# Switched Mode Power Conversion

## Transistor Amplifiers



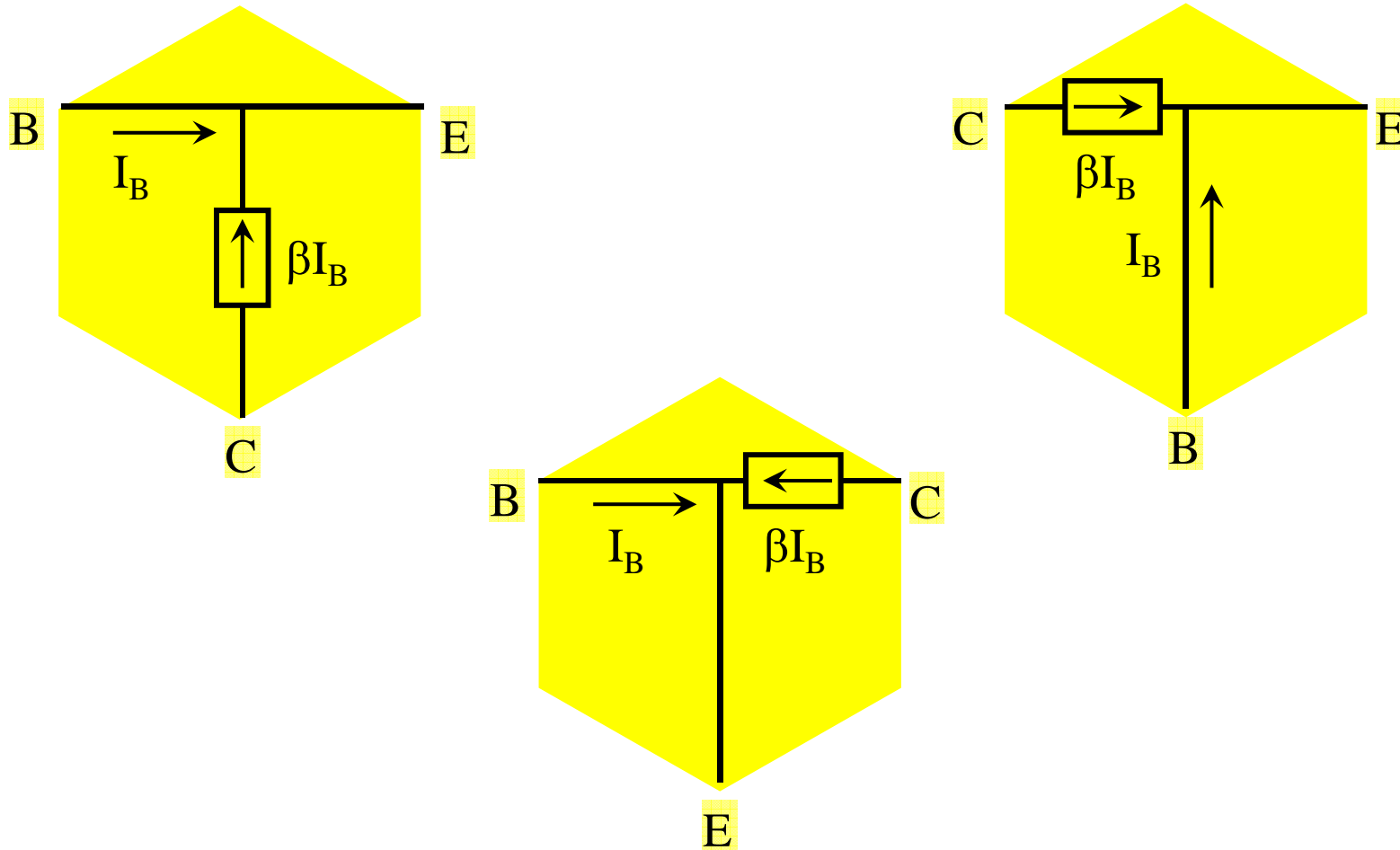


## Transistor Amplifier Variants



# Switched Mode Power Conversion



## Primitive Converters

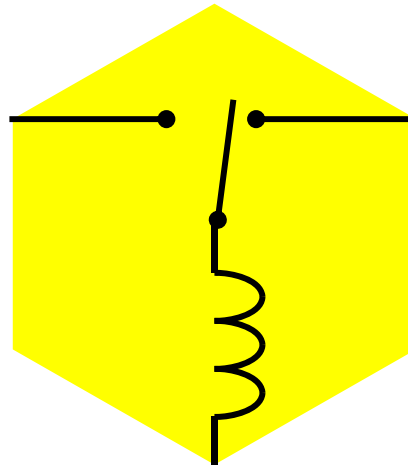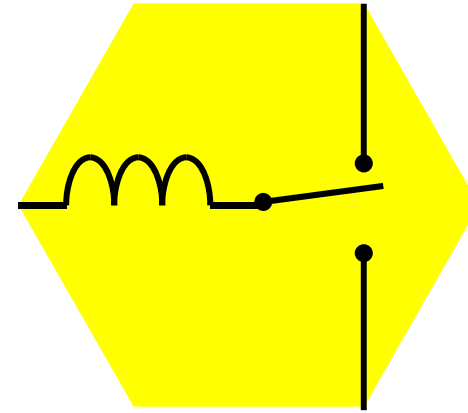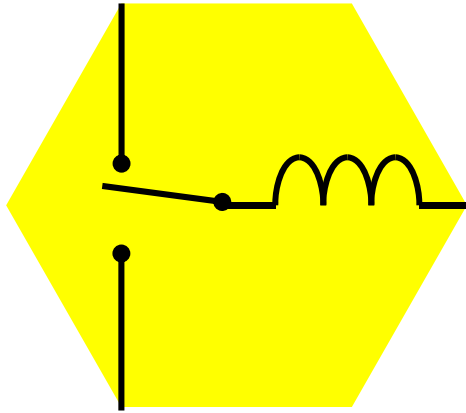

## Buck, Boost & Buck-Boost Variants

# Switched Mode Power Conversion

## Primitive Converters

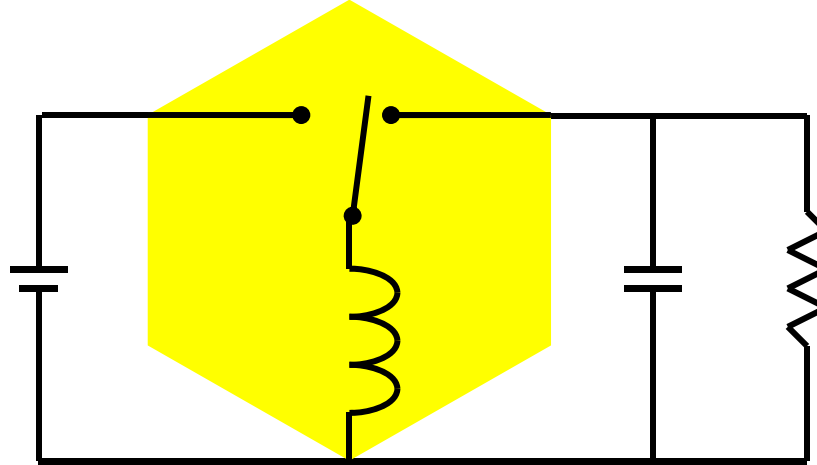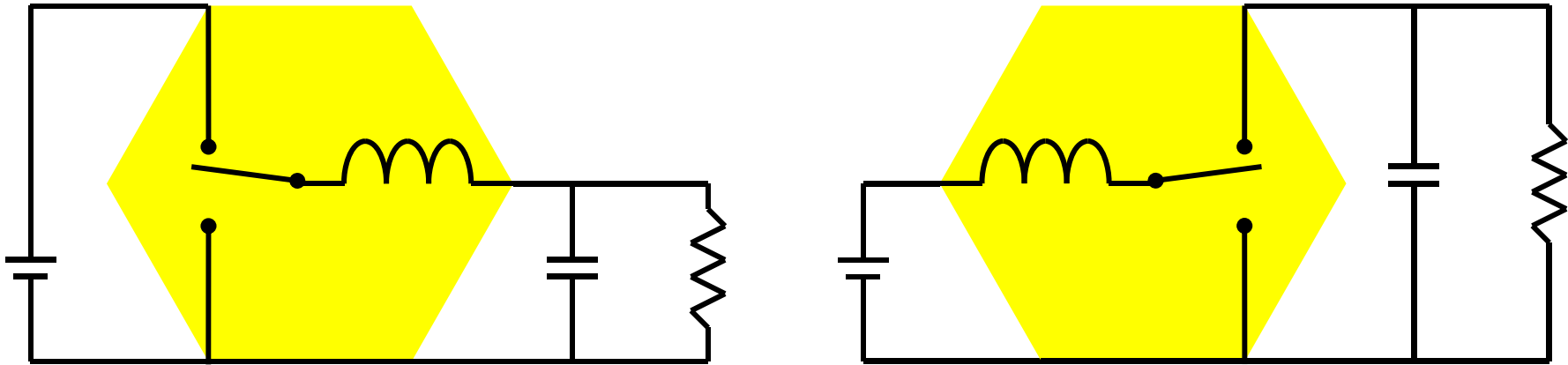

## Buck, Boost & Buck-Boost Variants