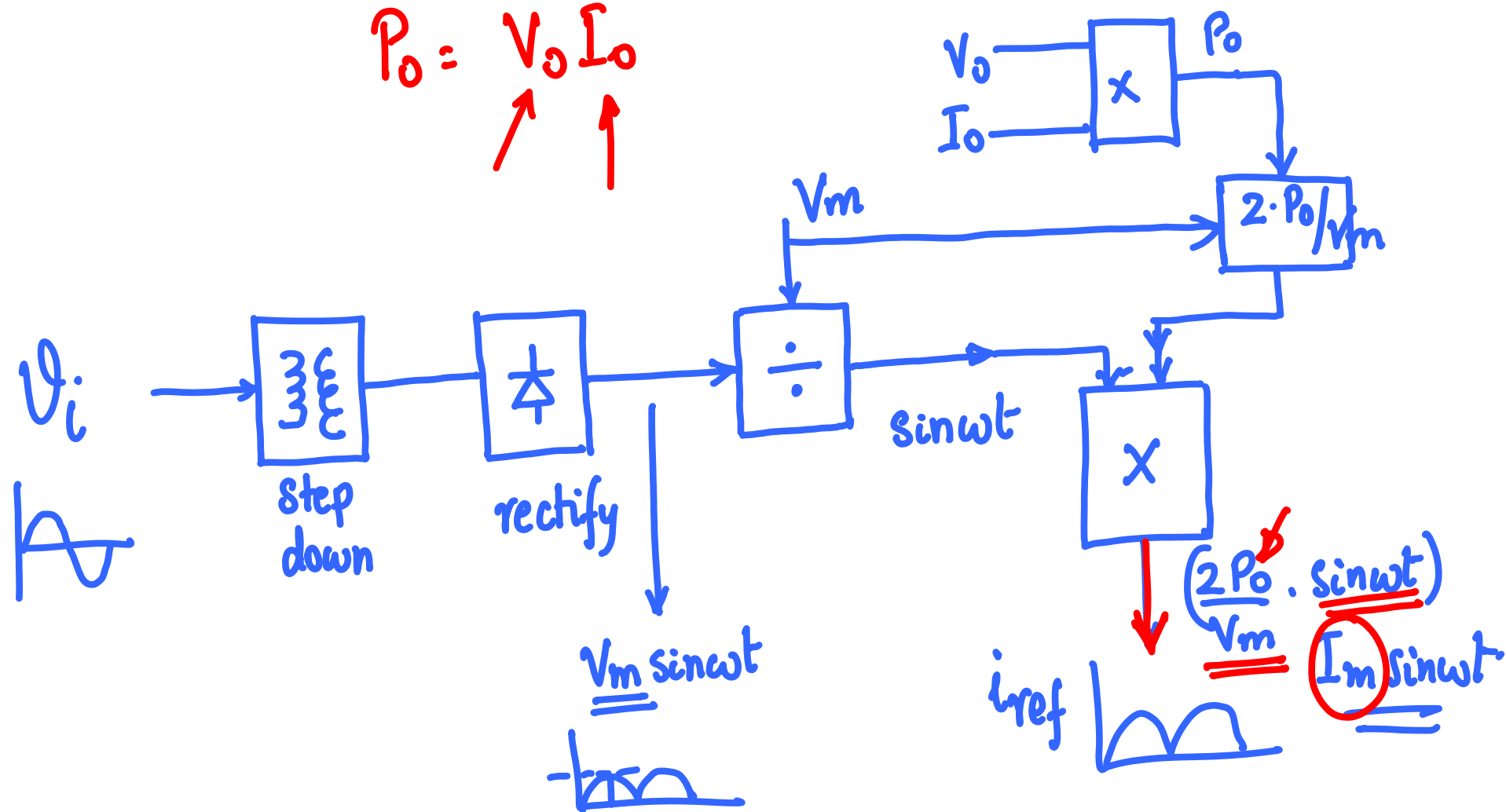



$$I_{rms} = \frac{\sqrt{2} \cdot P_o}{V_m}$$

$$I_m = \sqrt{2} \cdot I_{rms} = \frac{\sqrt{2} \cdot \sqrt{2} \cdot P_o}{V_m} = \frac{2 P_o}{\underline{V_m}}$$

$$i_{ref} : \underbrace{I_m}_{\text{red circle}} \underbrace{\sin \omega t}_{\text{blue circle}} = \underbrace{\left( \frac{2 P_o}{V_m} \right)}_{\text{blue underline}} \cdot \underbrace{\left( \frac{v_i}{V_m} \right)}_{\text{red underline}}$$

$$P_o = V_o I_o$$



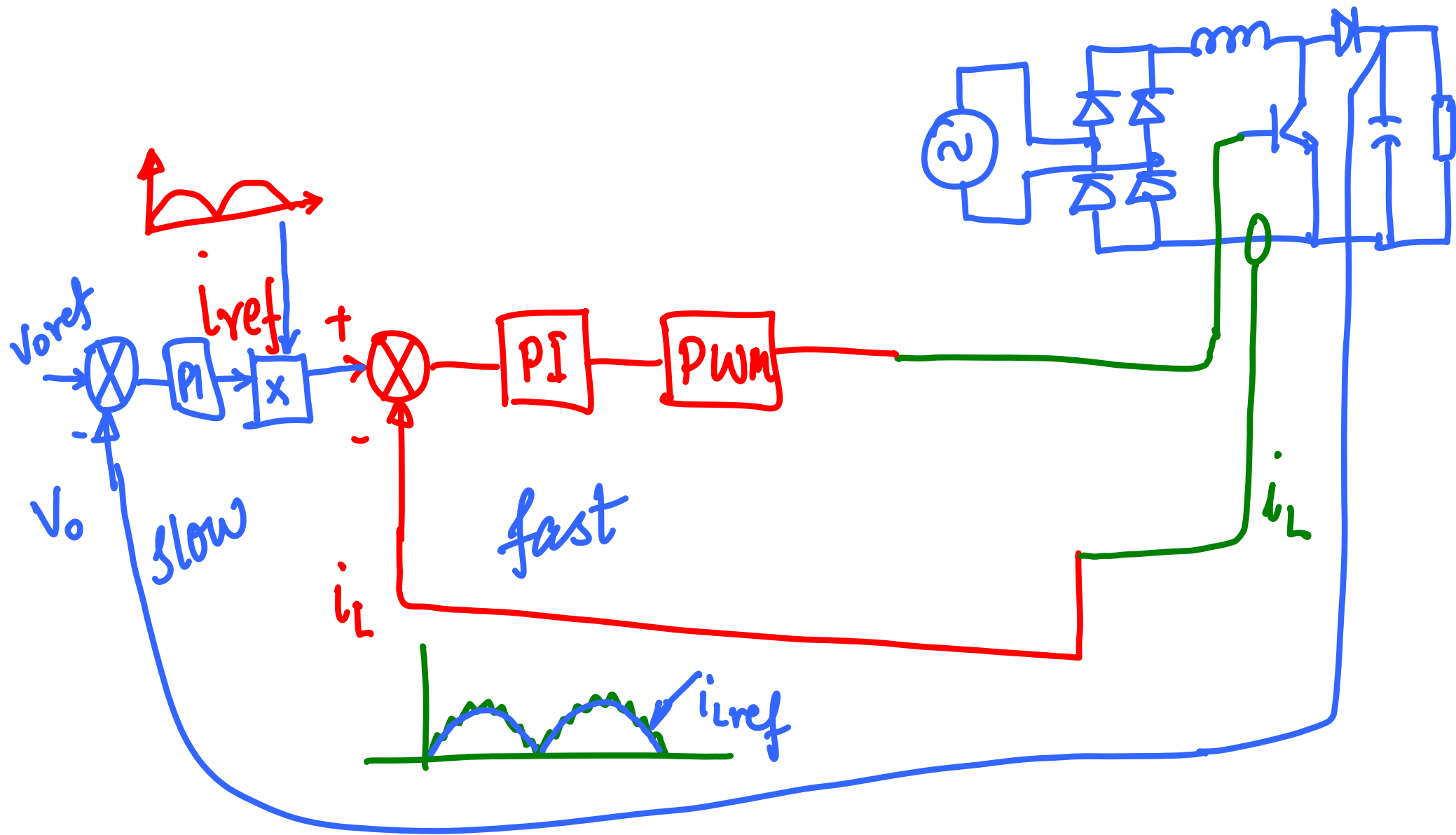


# DESIGN OF DC-DC CONVERTER

- ① Design / Rate the power circuit & components.
2. Design the controller ✓
- ③ Thermal design
4. Reliability Design.

# Functional Design of Power components

1. Power Semiconductor switch  
MOSFET, IGBT, DIODES

2. Capacitor

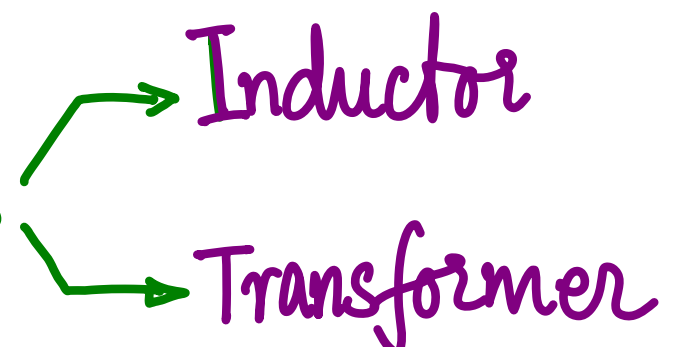3. Magnetic components 

```
graph LR; A[Magnetic components] --> B[Inductor]; A --> C[Transformer]
```

# MAGNETIC COMPONENTS

ELECTRICAL  
PARAMETERS

$L, i, v_L, \mathcal{E}_L$

$I_m,$

MAG / MECHANICAL  
PARAMETERS

$A_c, A_w,$

$\mu, B_{sat},$  material of  
core

