
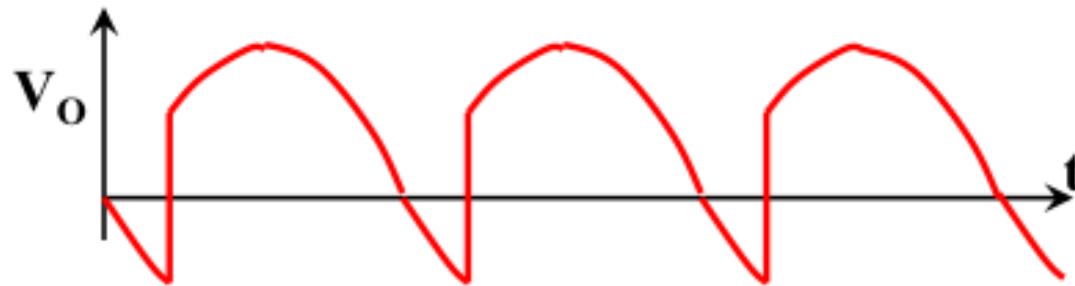


Switched Mode Power Conversion




SCR – A Simple Application

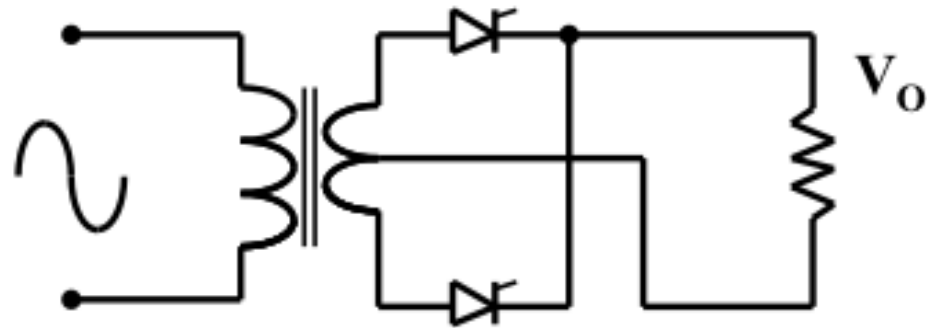

Controlled AC/DC Rectifier


Switched Mode Power Conversion

Ideal Switch – In the VI Plane

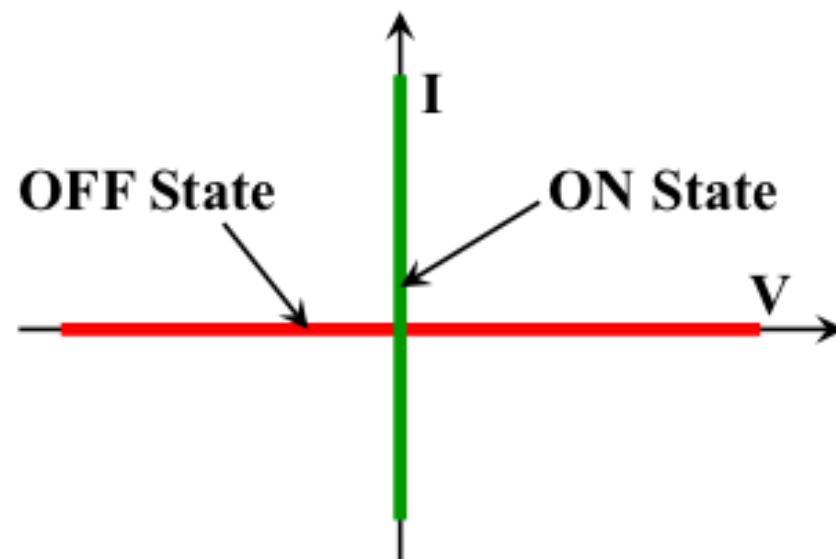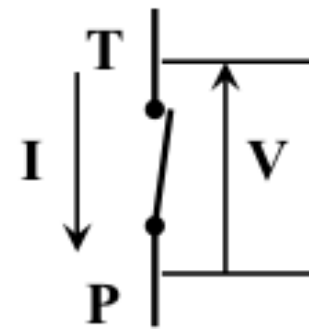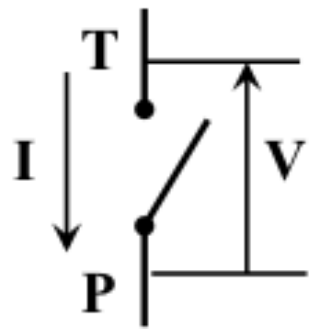

Switched Mode Power Conversion

A Fully Controlled Switch – BJT

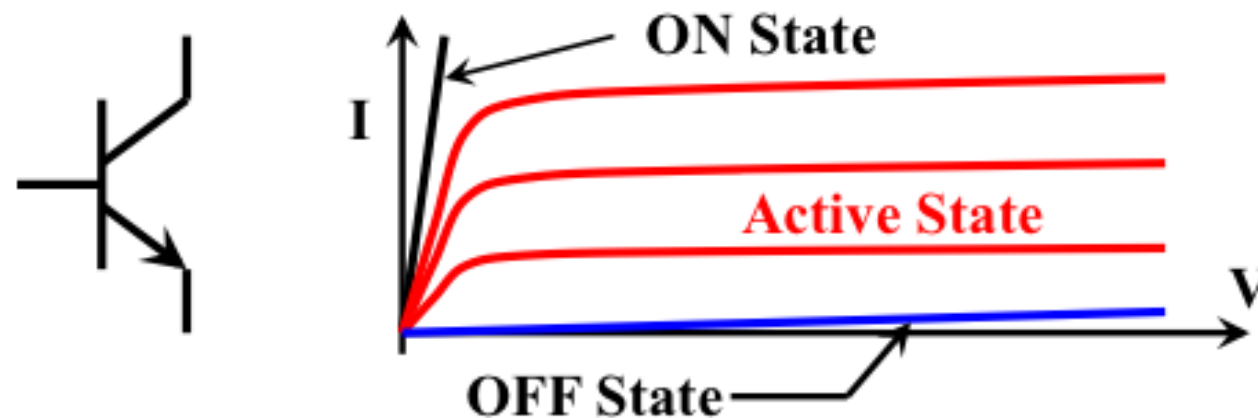



BJT

ON Switch for $I > 0$

OFF Switch for $V > 0$

Switched Mode Power Conversion


Switching Characteristics

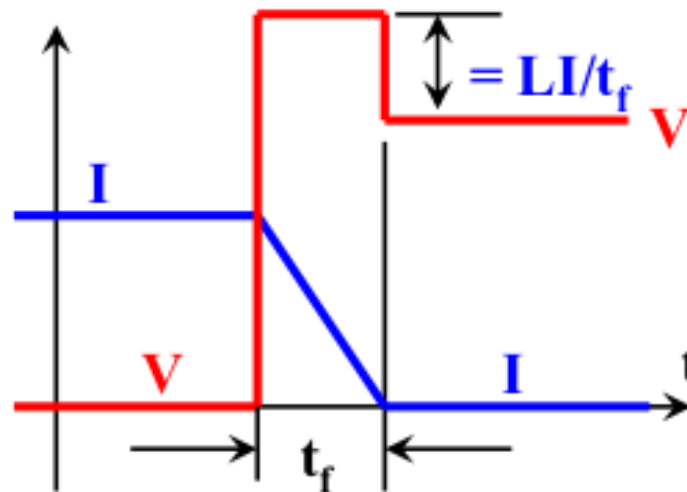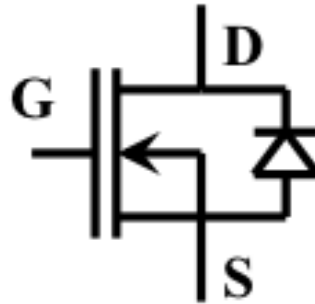

Turn-Off of Inductive Load
Over-voltage in Turn-Off

Switched Mode Power Conversion

Switching Aid Circuit

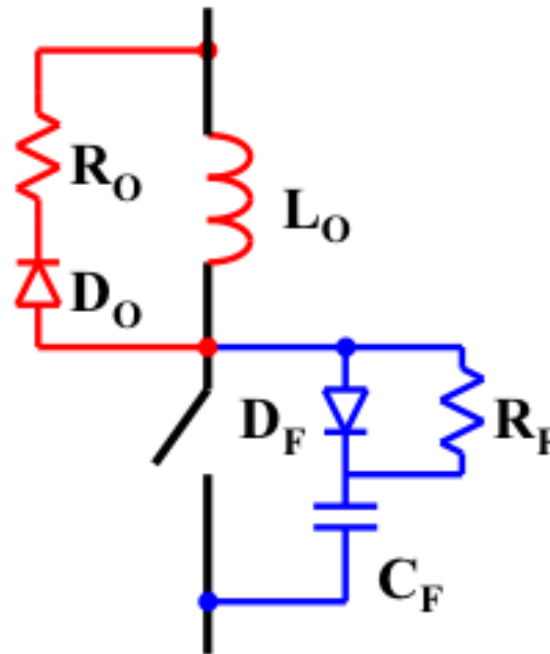

Strategy for Reducing Switching Stress


L_O , R_O , D_O , form Turn-On Aid Circuit

L_F , R_F , D_F , form Turn-Off Aid Circuit

Prior Art

Output Voltage


Series Controlled Converter

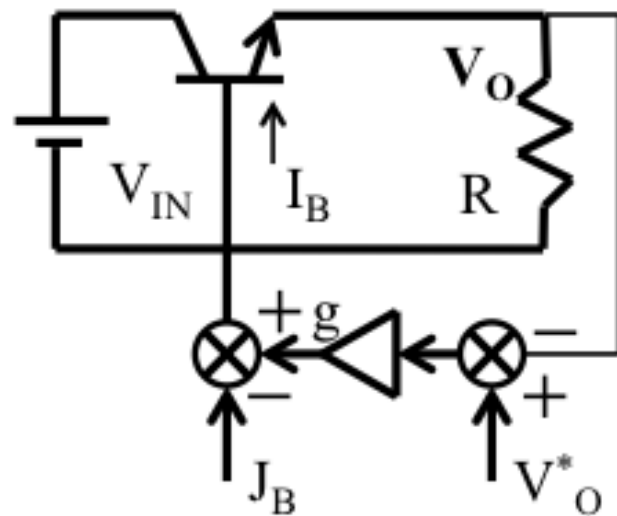

$$(g(V_O^* - V_O) - J_B)\beta R = V_O$$


$$V_O = V_O^* \frac{g\beta R}{1 + g\beta R} + J_B \frac{\beta R}{1 + g\beta R}$$
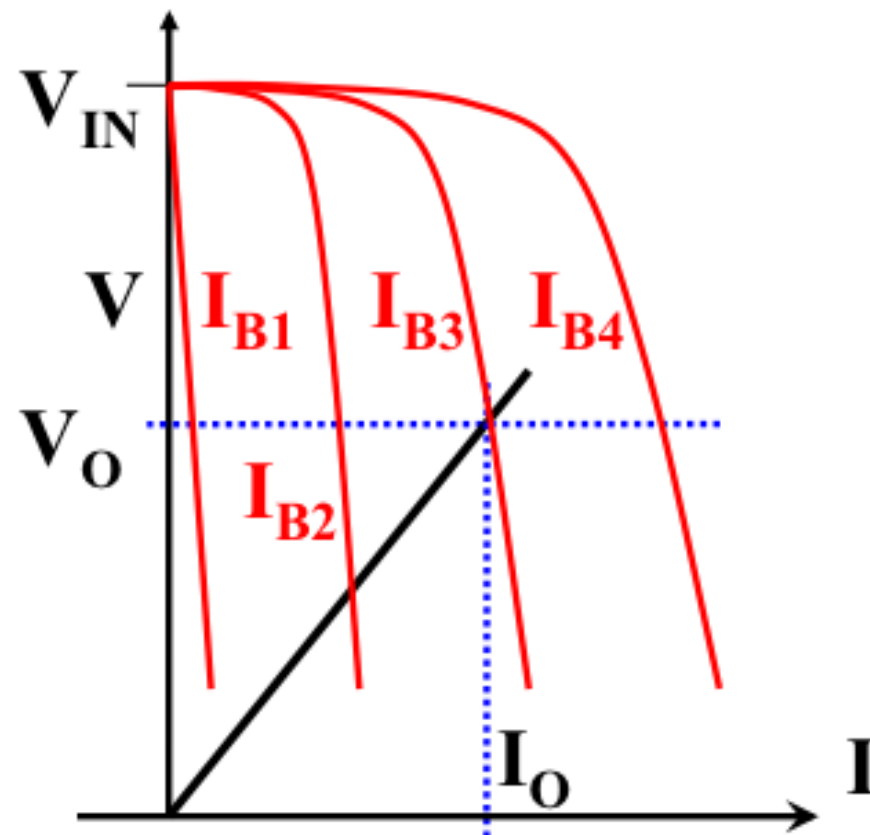
$$V_O \approx V_O^* \text{ for } g \gg \gg 1$$




Switched Mode Power Conversion

Inductors

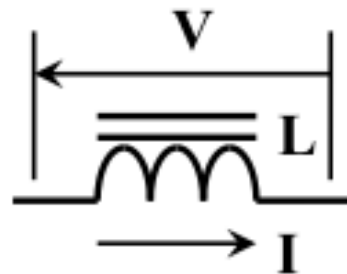

$$V = L \frac{dI}{dt}$$

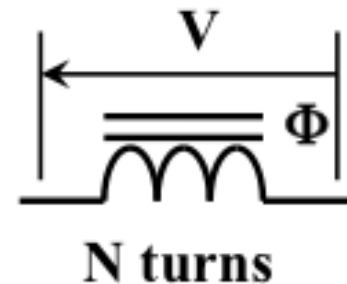


$$LI = N\Phi$$

$$V = N \frac{d\Phi}{dt}$$

**How to Relate the Electrical Circuit V , L , I
and
The Magnetic Circuit of the Inductor N , Φ , I & R**

Switched Mode Power Conversion

Practical Design of an Inductor

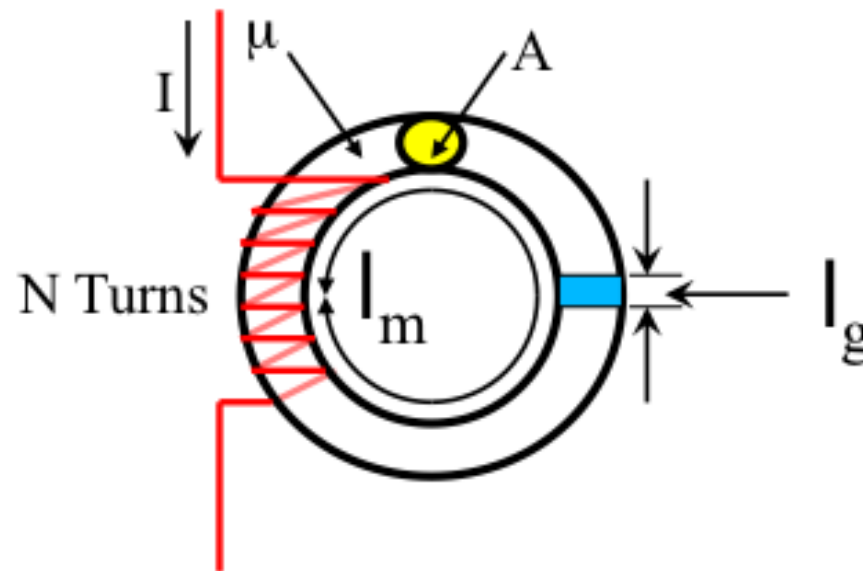

$$L = \frac{N\Phi}{I} = \frac{N^2}{\left(\frac{l_m}{A\mu_o\mu_m} + \frac{l_g}{A\mu_o} \right)} \approx \frac{N^2 A \mu_o}{l_g}$$


Inductance is Independent of Core Material (μ)

Inductance is Independent of Core Shape (l_m)

Switched Mode Power Conversion

Transformers


Voltage Equation

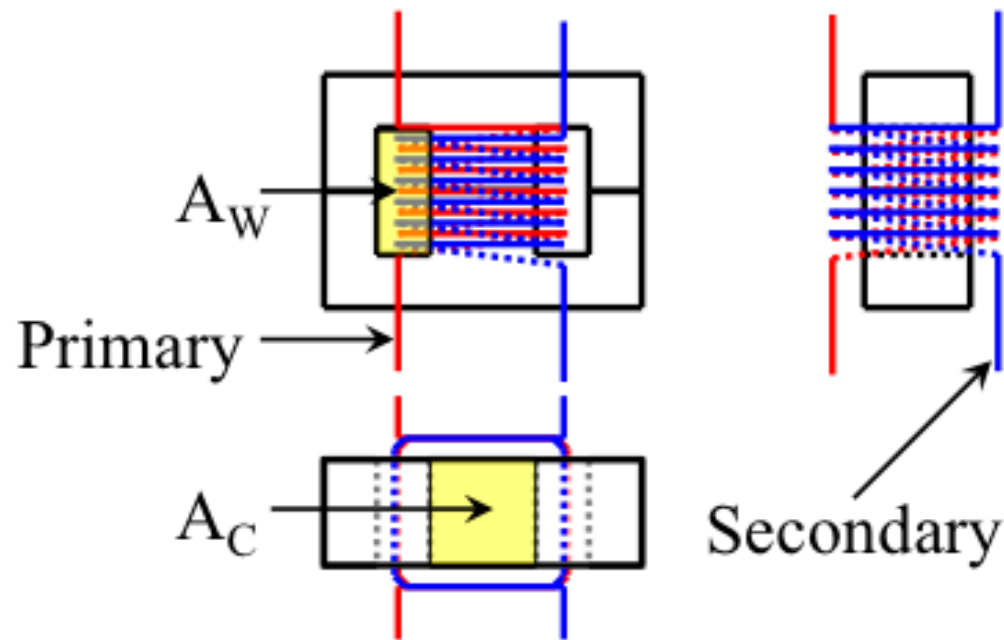

$$V_1 = N_1 \frac{d\Phi}{dt}; V_2 = N_2 \frac{d\Phi}{dt}$$

Switched Mode Power Conversion

Capacitors

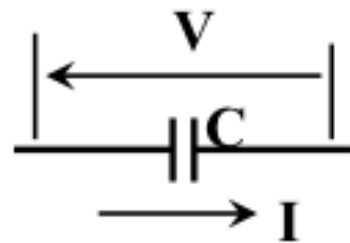


$$I = C \frac{dV}{dt} ; V(t) = V_i + \frac{1}{C} \int_0^t I dt$$

Electrical Circuit Element Equation
V, C, I are Electrical Circuit Quantities

Switched Mode Power Conversion

Capacitors – Stored Energy

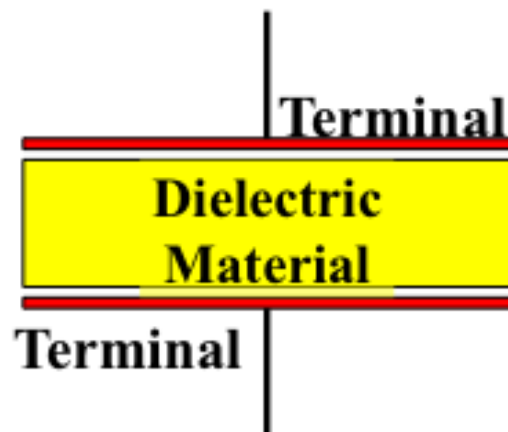


$$E = \int_0^V Q dV = \int_0^V CV dV = \frac{1}{2} CV^2$$

**Energy is Work Done to Separate the Charge
Through a Potential of V**

Switched Mode Power Conversion

Primitive Converters

Primitive Voltage to Current Converter

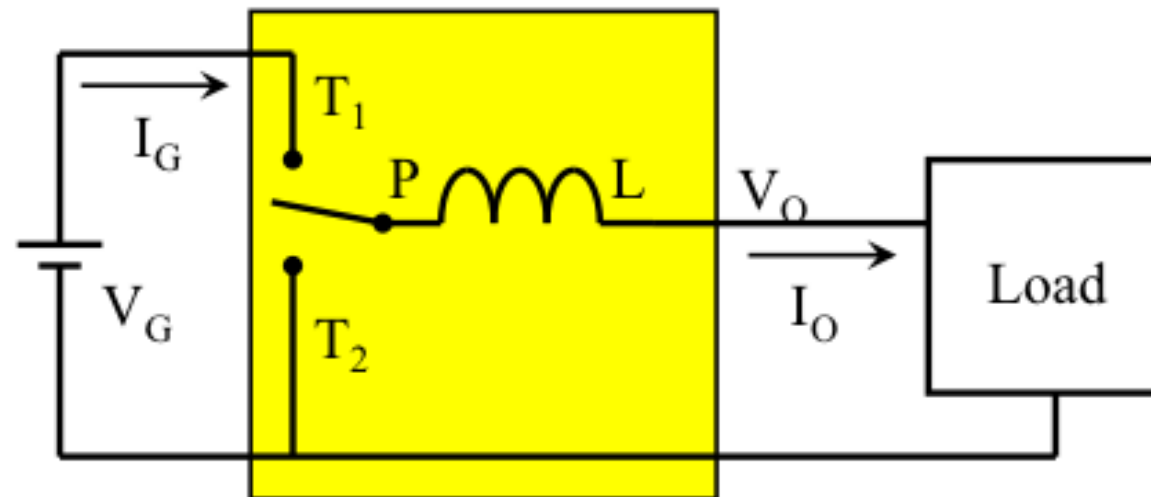


Input average quantities: V_G and I_G

Output average quantities: I_O and V_O

Switched Mode Power Conversion


Basic Power Converters

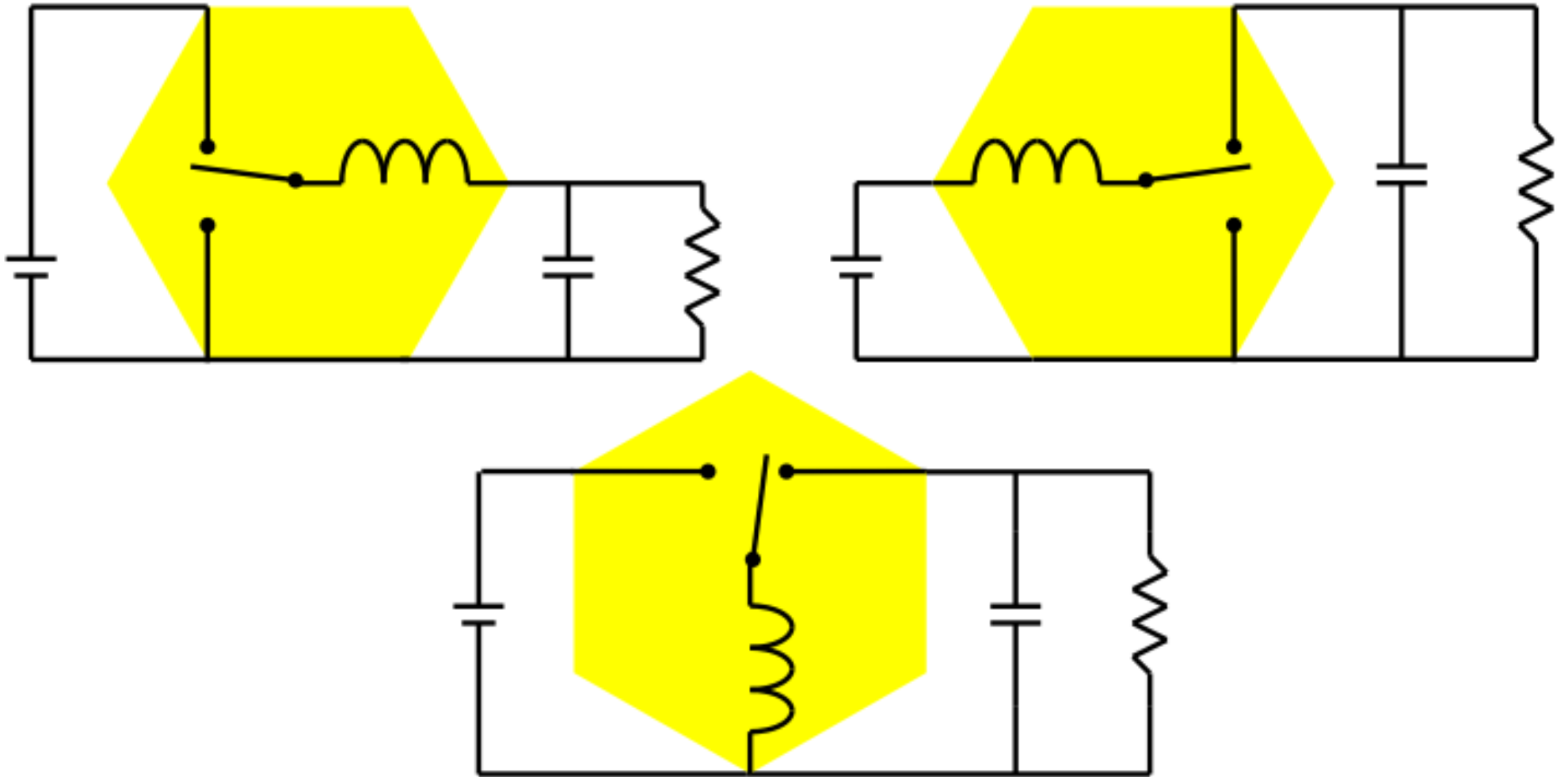

Buck, Boost & Buck-Boost Variants

Switched Mode Power Conversion

Flyback Converter

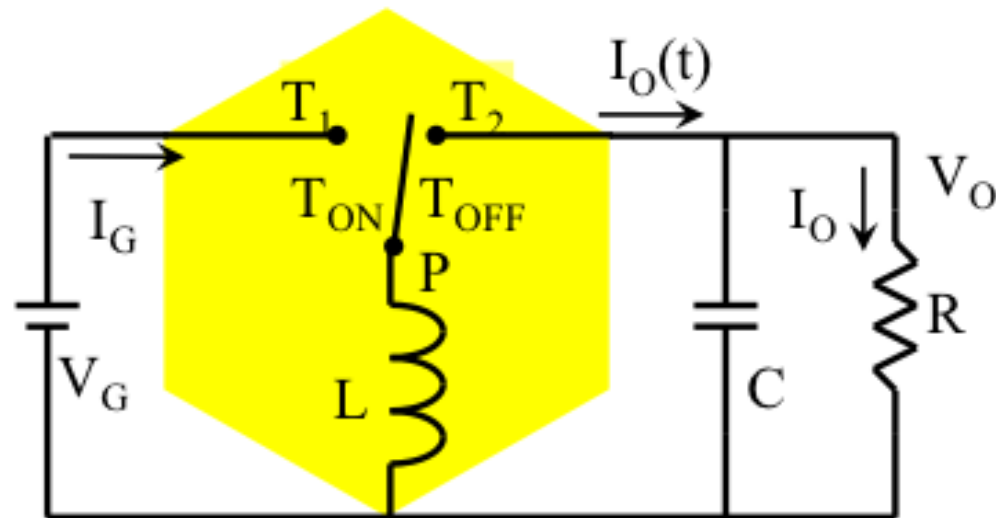


$$\frac{V_O I_O}{V_G I_G} = \frac{D}{1-D} \frac{1-D}{D} = 1$$

Ideal Efficiency is Unity

Switched Mode Power Conversion


Forward Converter

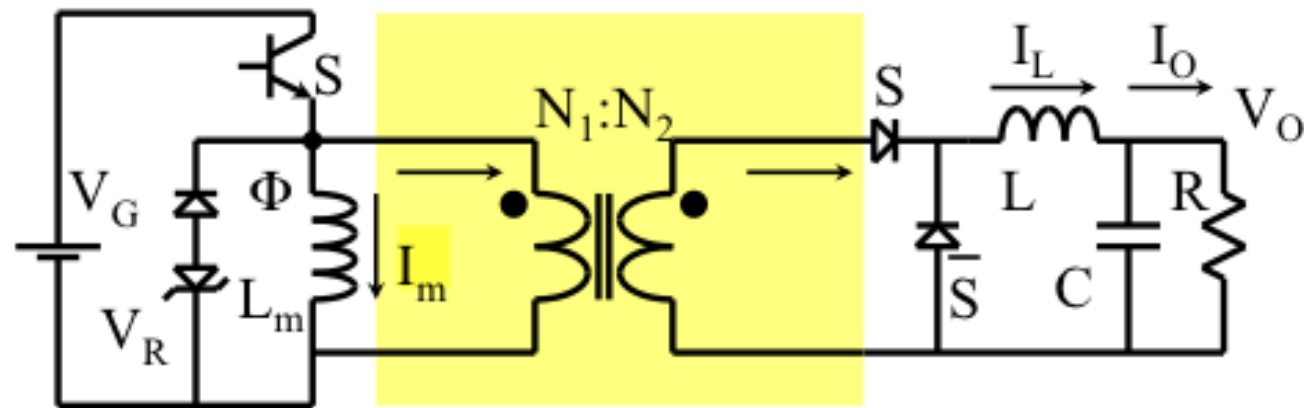

Forward Converter – Circuit Realisation

Switched Mode Power Conversion

Push-Pull Converter

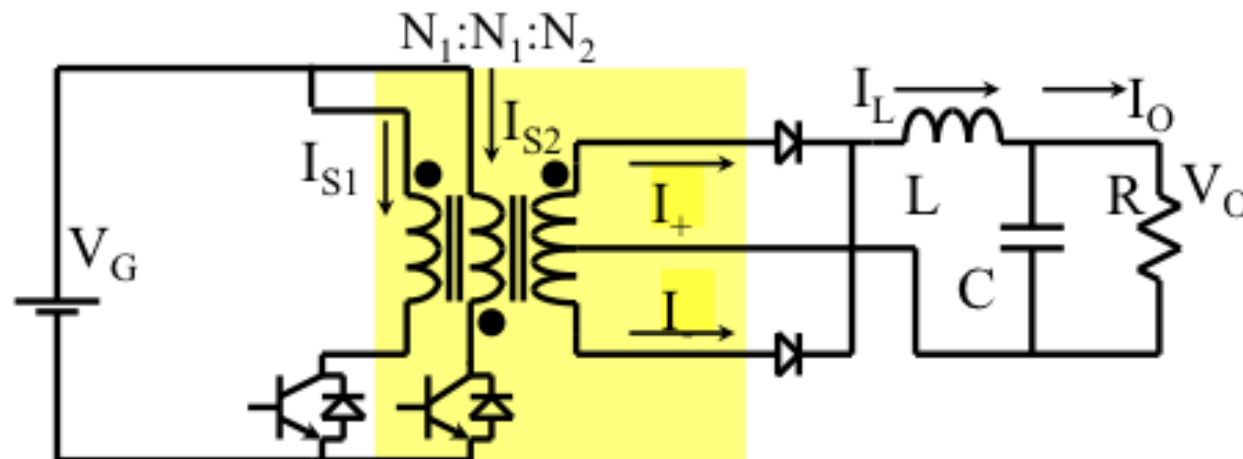

Switches turn-on with PWM in alternate half cycles

Flux resetting is done in Complementary Fashion


Duty ratio of primary switches < 50%

Secondary duty ratio < 100%

Back-to-Back Forward Converters


Switched Mode Power Conversion

Half Bridge Converters

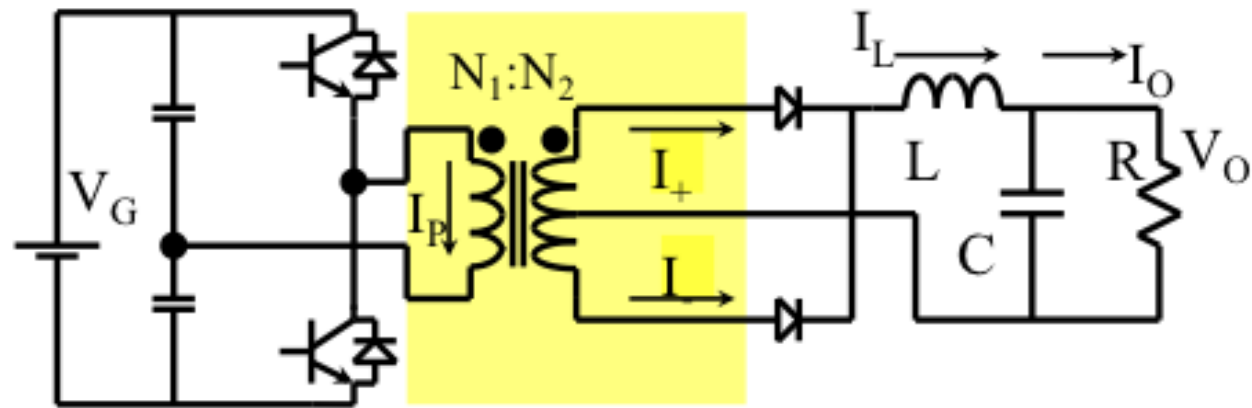



Switched Mode Power Conversion

Full Bridge Converters

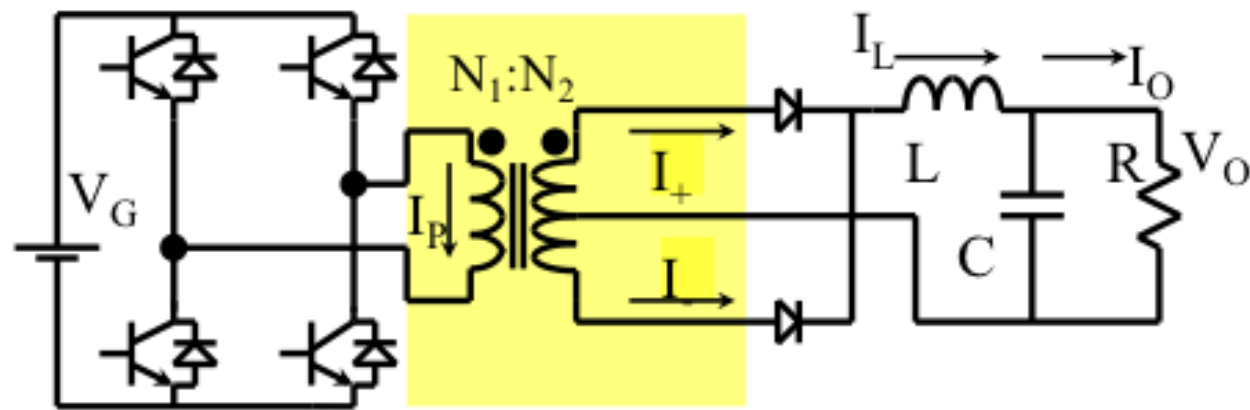


Switched Mode Power Conversion


Buck Converter – DCM

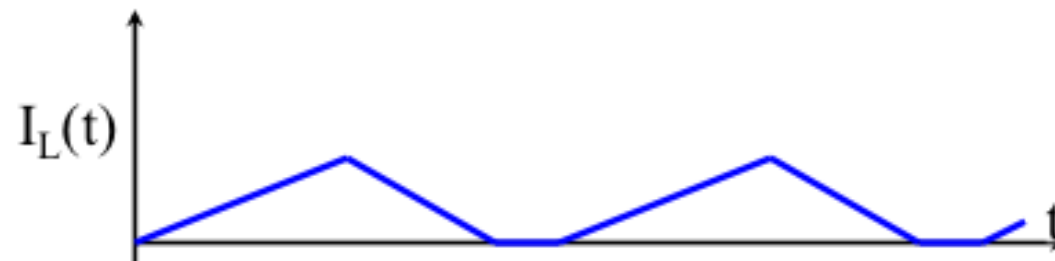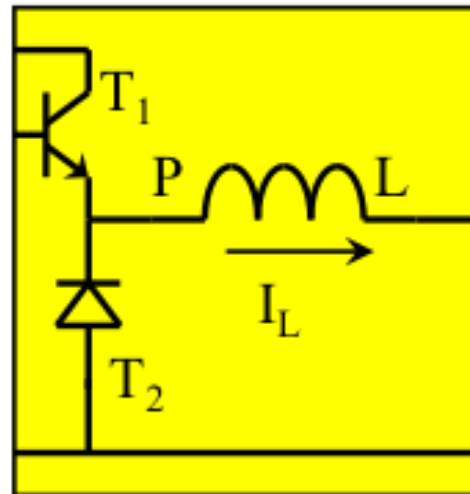


Third State: Transistor & Diode Both are OFF

Modeling Basics

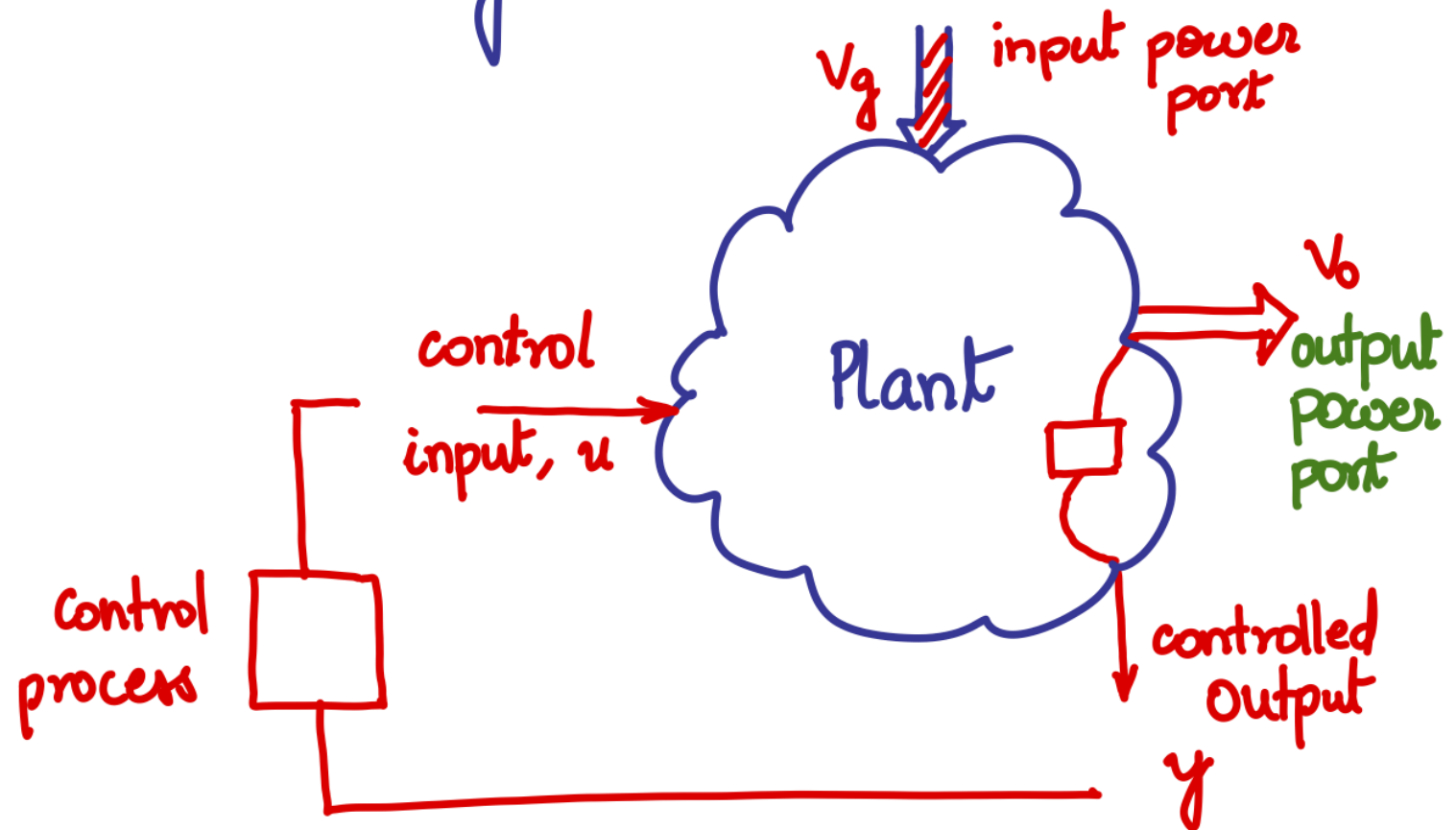

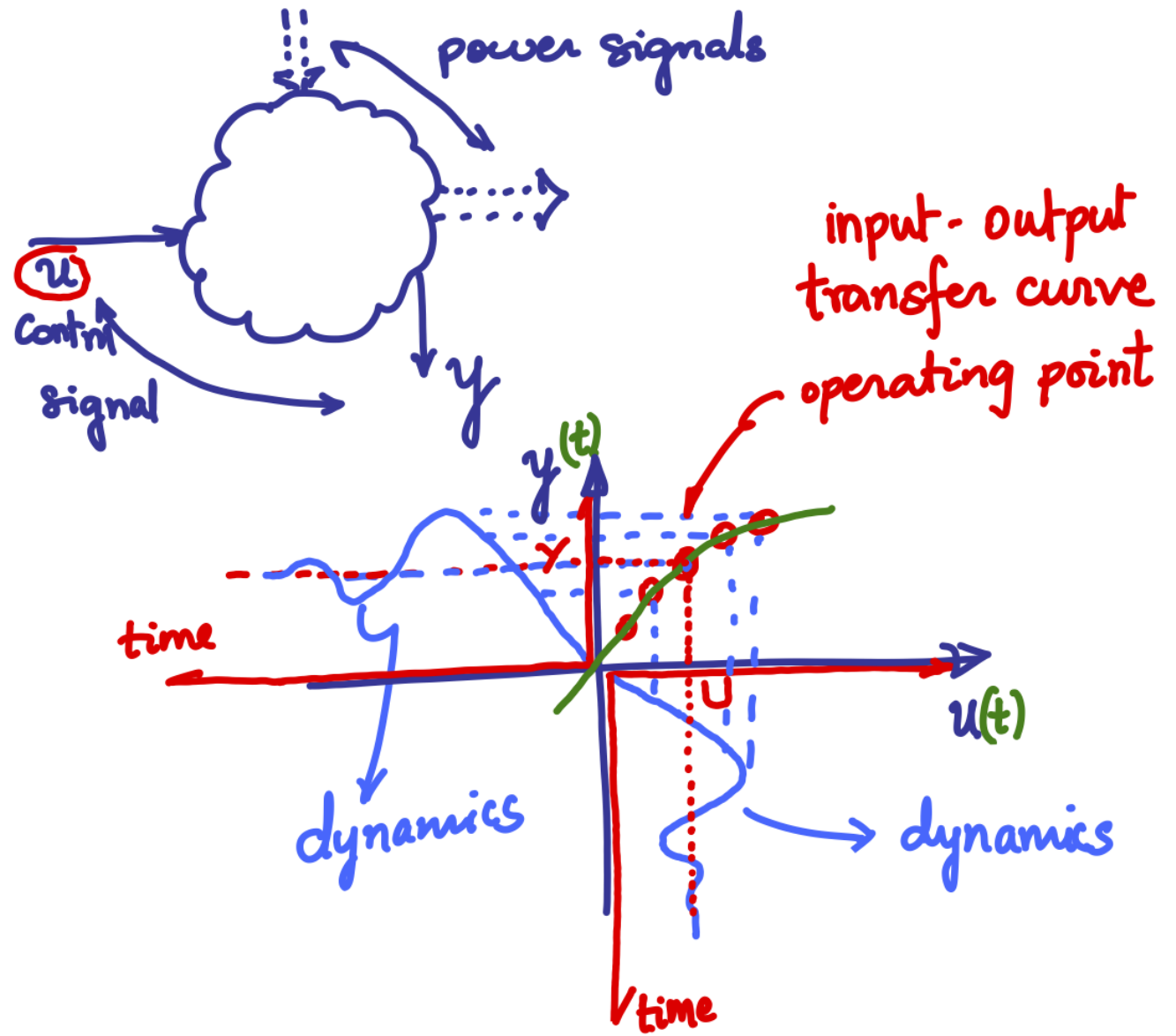

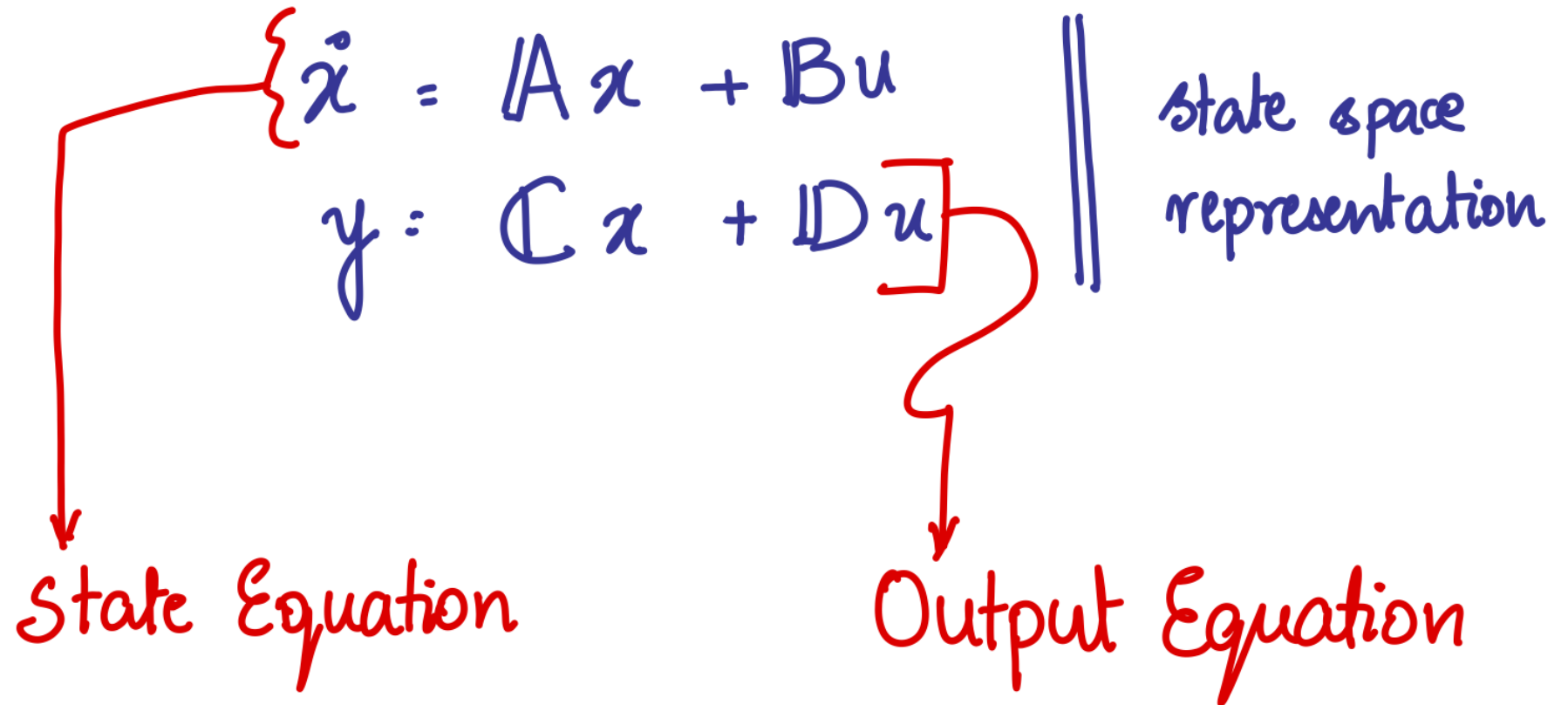

STANDARD

$$\frac{di_L}{dt} = -\left(\frac{R_1}{L}\right) i_L - \left(\frac{1}{L}\right) v_c + \left(\frac{1}{L}\right) v_g$$


$$\frac{dv_c}{dt} = \left(\frac{1}{C}\right) i_L - \left(\frac{1}{R_2 C}\right) v_c + \underline{0} v_g$$

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_c \end{bmatrix} = \underbrace{\begin{bmatrix} -\frac{R_1}{L} & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{R_2 C} \end{bmatrix}}_{\mathbf{A}} \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \underbrace{\begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}}_{\mathbf{B}} [v_g]$$

$\dot{x} = \mathbf{A} \cdot x + \mathbf{B} \cdot u$

STATE EQUATION

Circuit Averaging Method

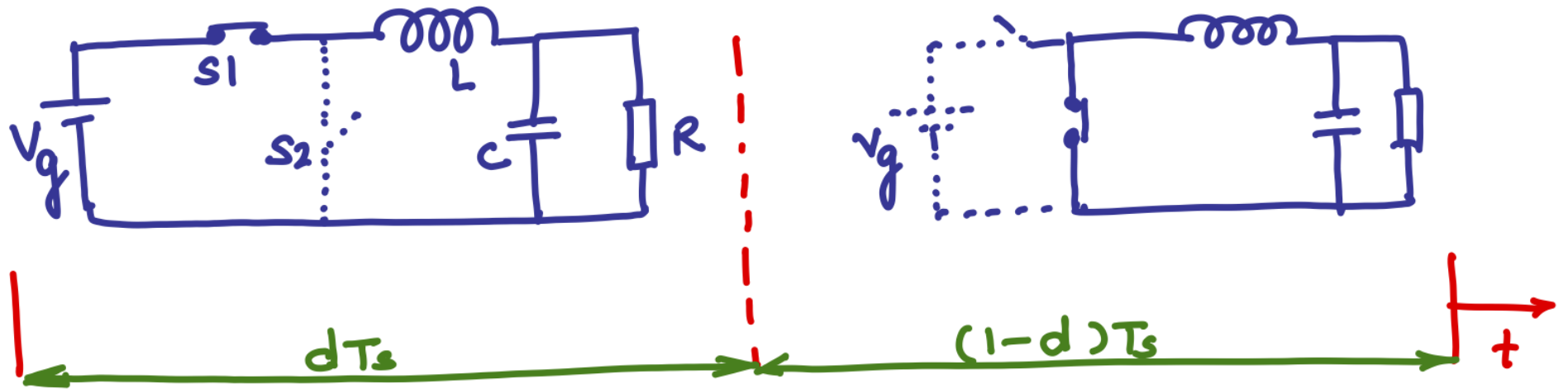

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_C \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} [v_g] \quad T_s$$

$$v_o = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \end{bmatrix} [v_g]$$

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_C \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} [v_g]$$

$$v_o = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \end{bmatrix} v_g$$


Large signal : $\dot{x} = Ax + Bu$ | actual system


Steady State : $\dot{X} = 0 = AX + BU$ | **Equilibrium**
DESIGN
of converter

Small signal : $\hat{\dot{x}} = A\hat{x} + B\hat{u}$ | **CONTROLLER**
DESIGN

linear
model

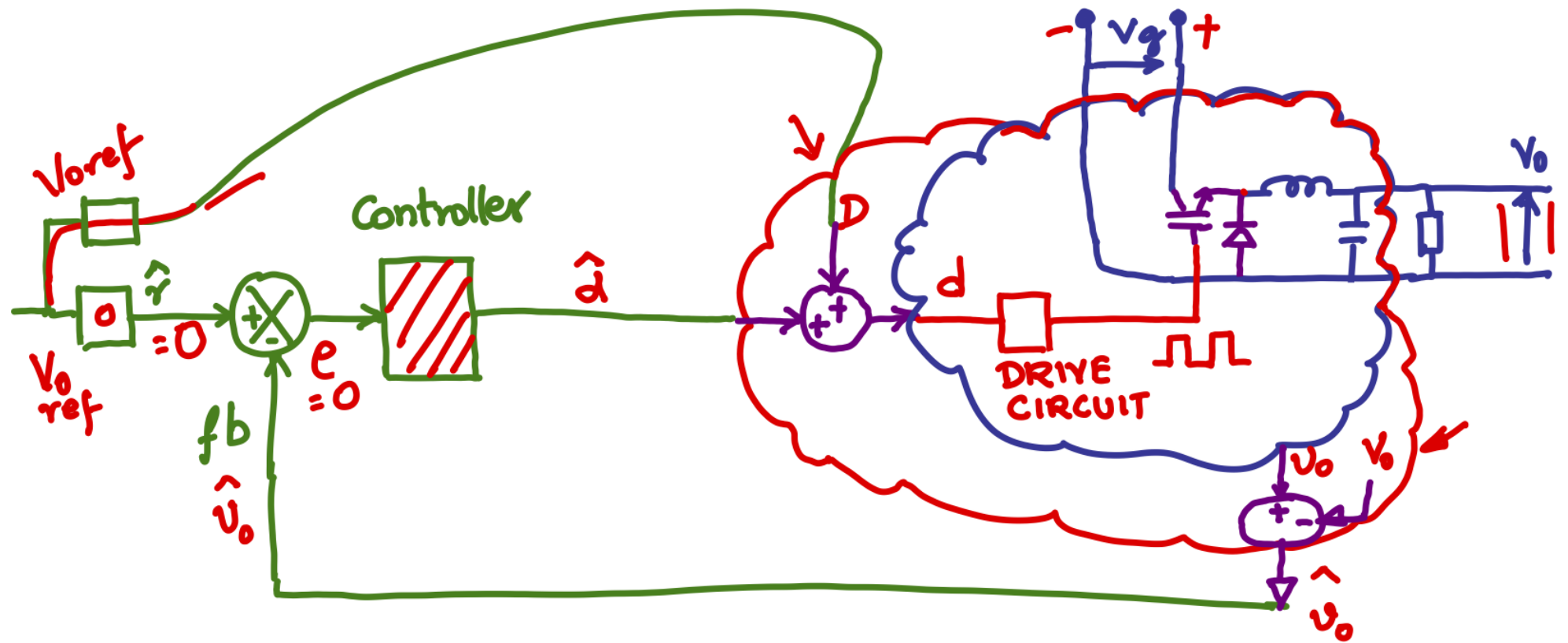dynamics
variations about
OPERATING POINT




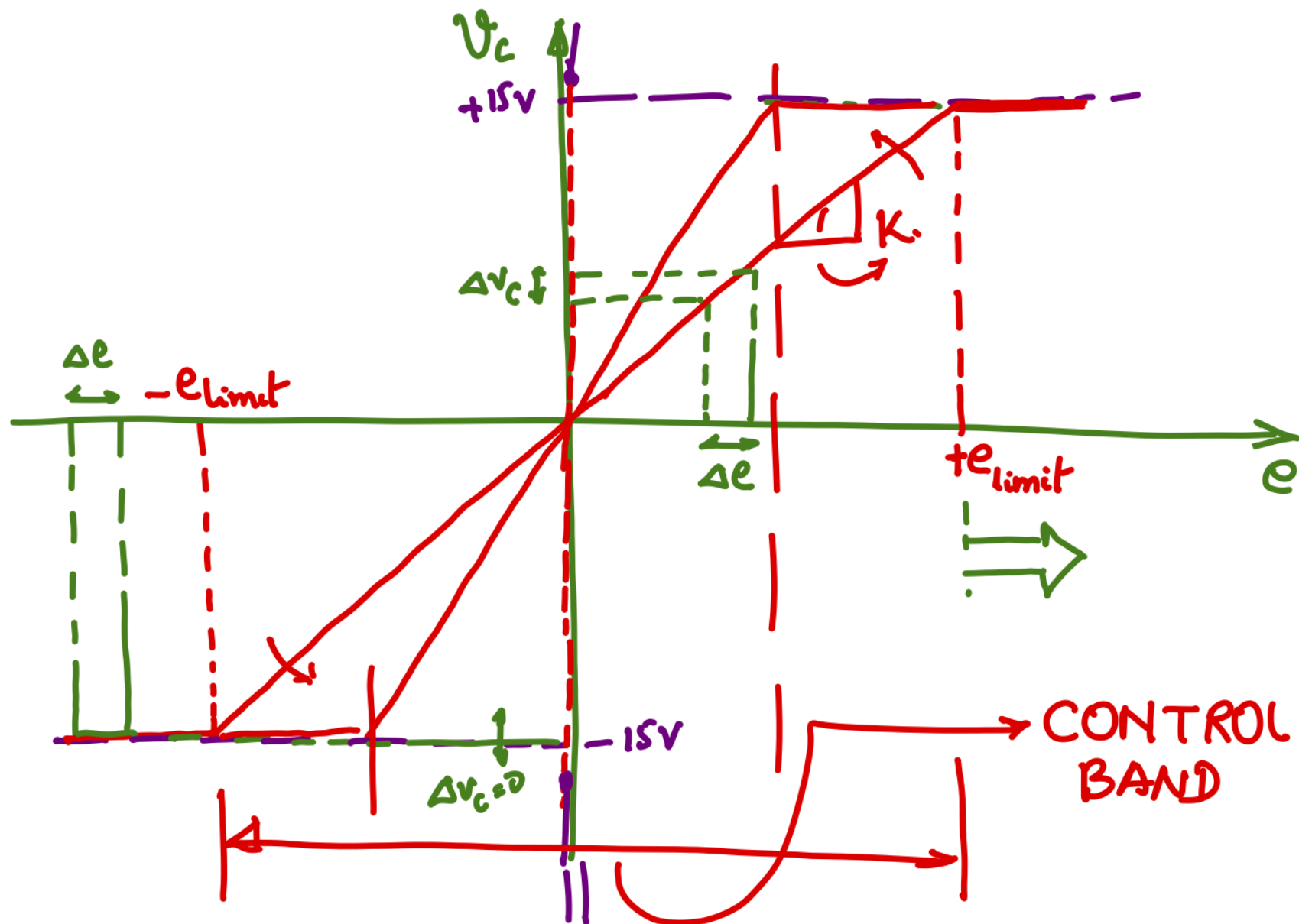

Proportional

$$K_p$$


$$dB = 20 \log_{10} K_p$$

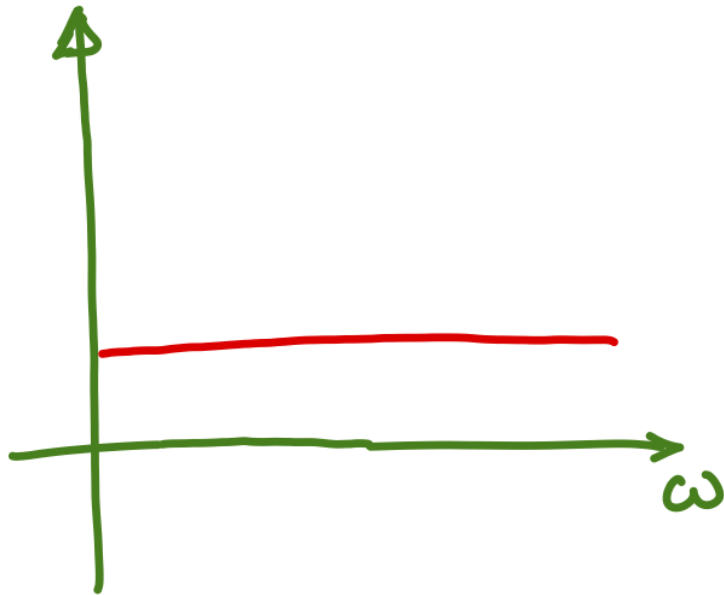

Integrator

$$\frac{K_i}{s}$$

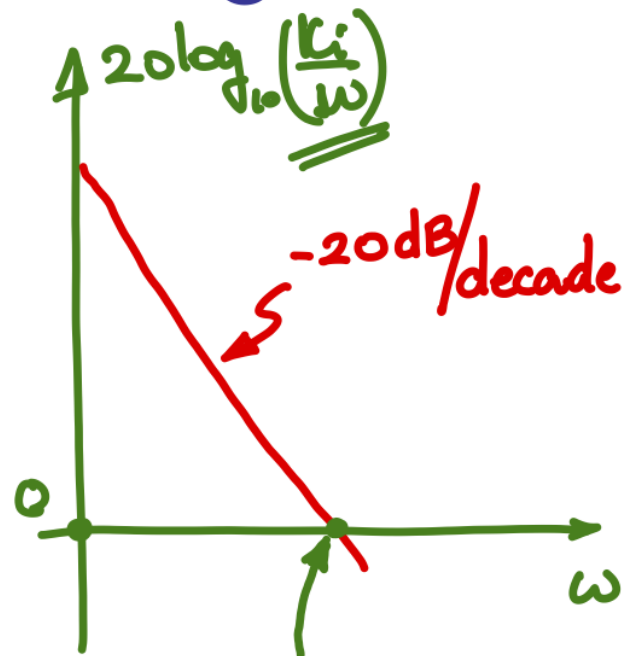
$$20 \log_{10} \left(\frac{K_i}{\omega} \right)$$





Derivative

$$\frac{K_d s}{s+a}$$



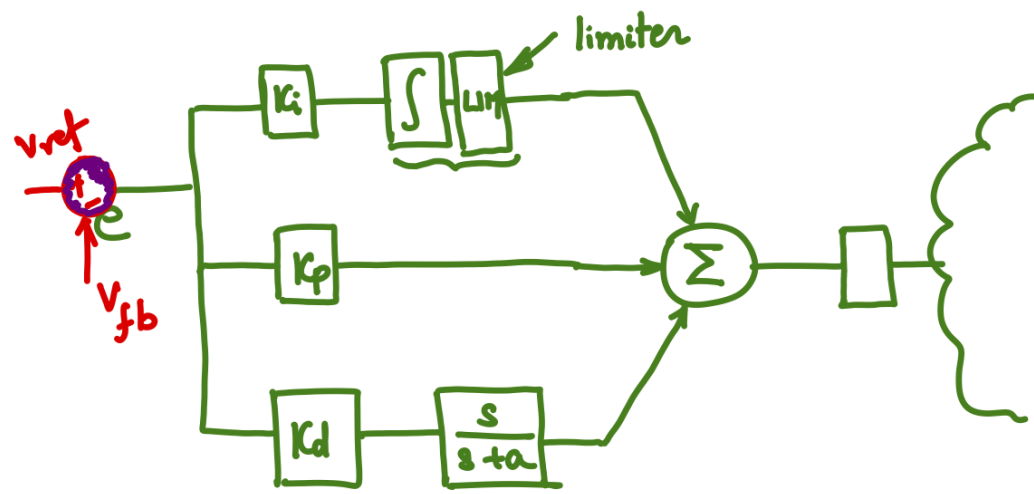

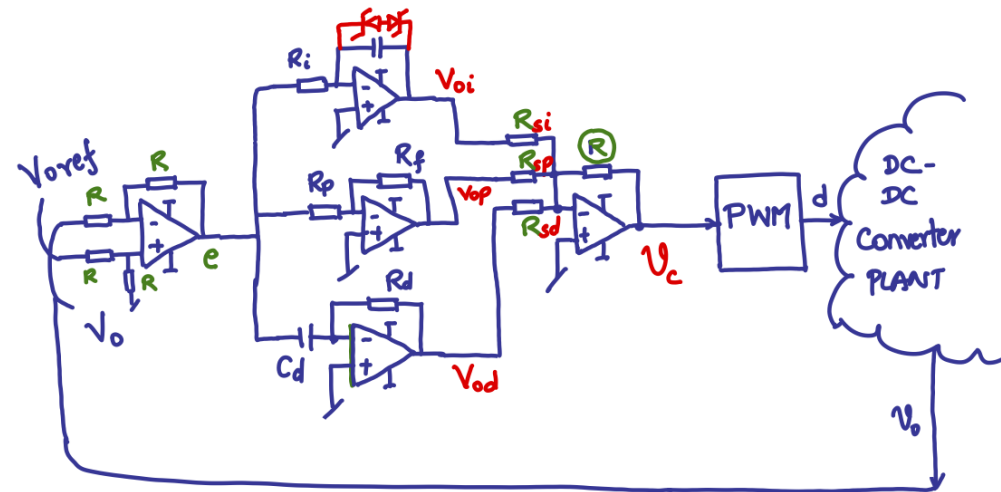

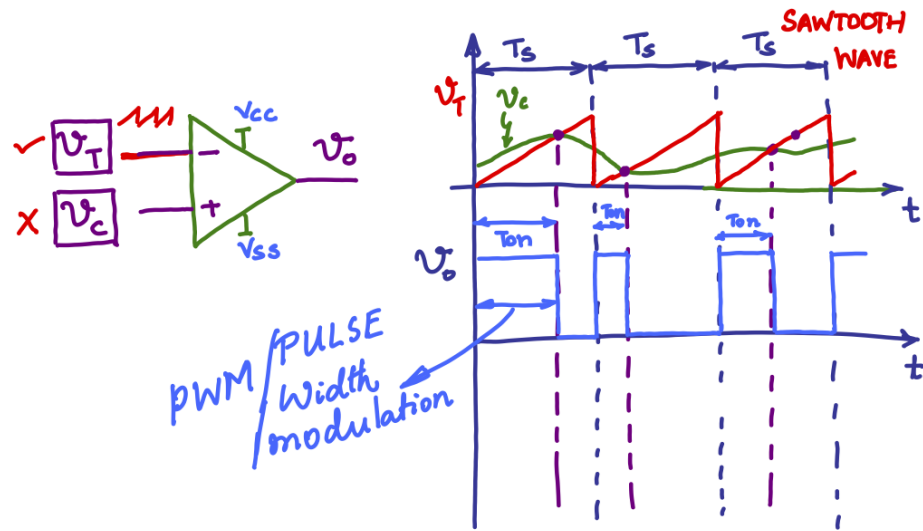

CONTROLLER DESIGN


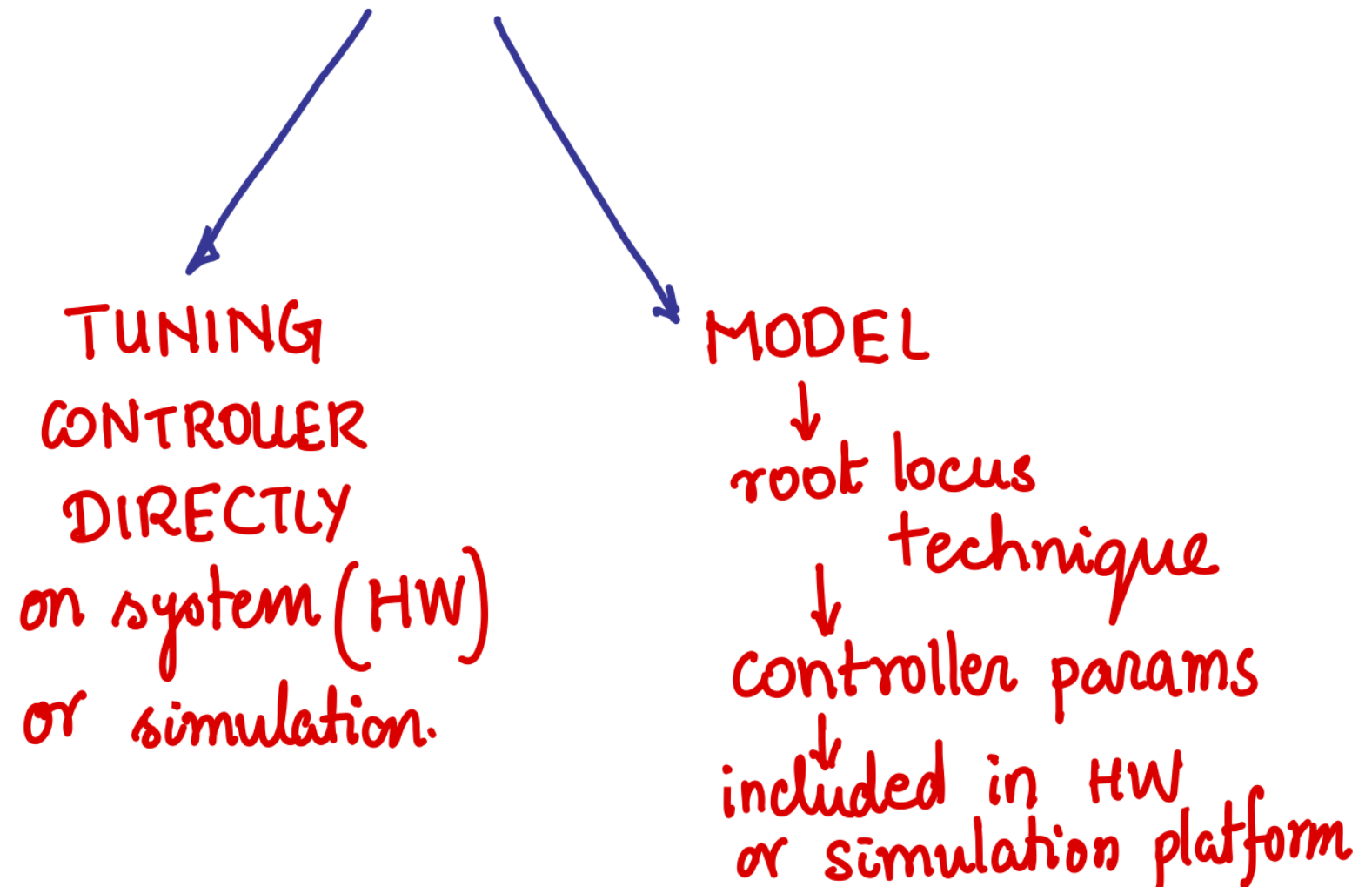


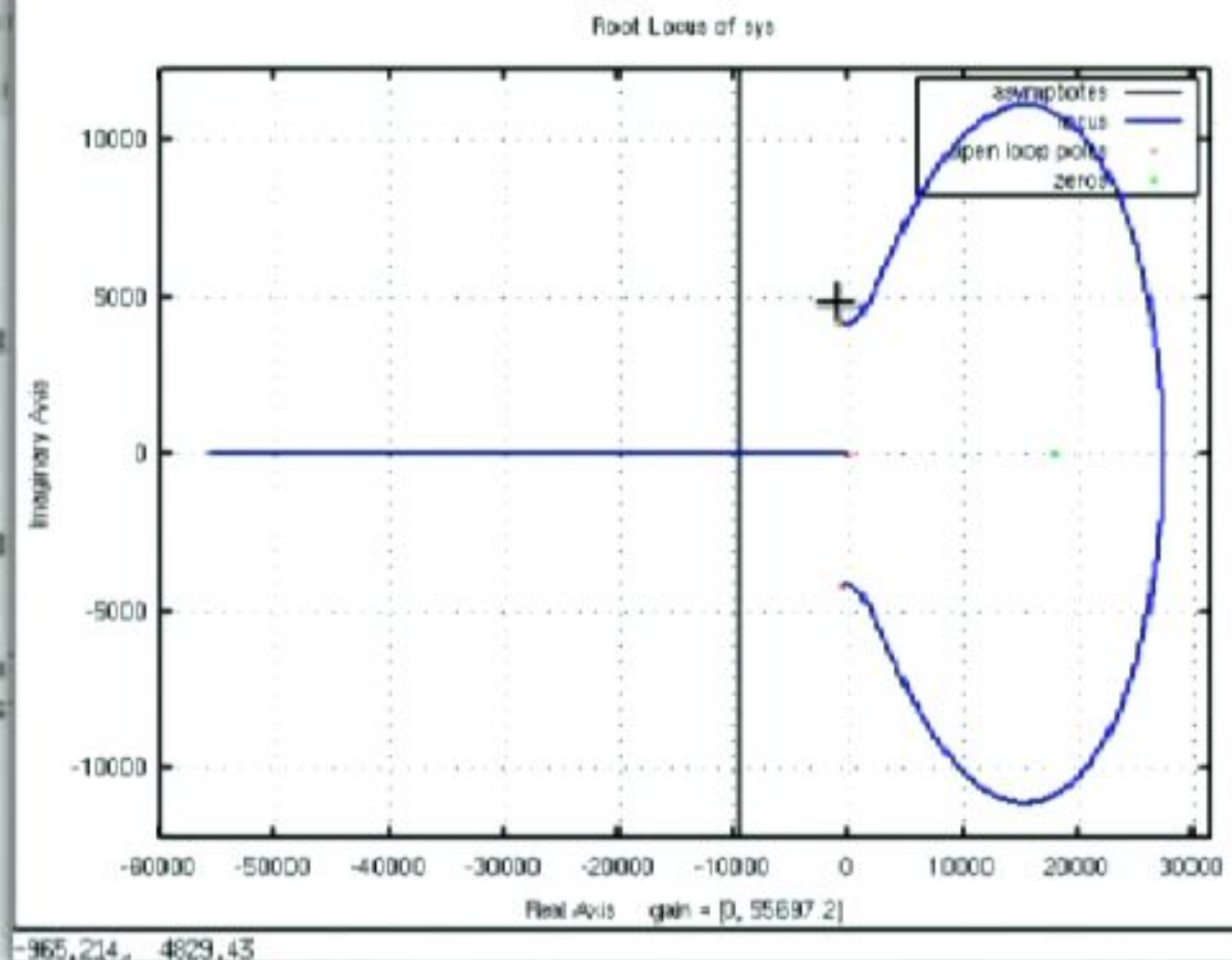

Figure 1



Continuous-time model.

octave:18> ng

ng =

-4.1667e+34 7.5000e+08

octave:19> dg

dg =

1.0000e+30 1.0000e+03

octave:20> rloc_des

warning: polyderiv is obsolete; please use polyder instead

k = 480.15

p =

-7562.3 + 0.01i

3281.1 - 6070.71i


3281.1 + 6070.71i

Enter 0 to quit or 1 to continue [0/1] = 1

1

29 elf;

COUPLED INDUCTOR METHOD

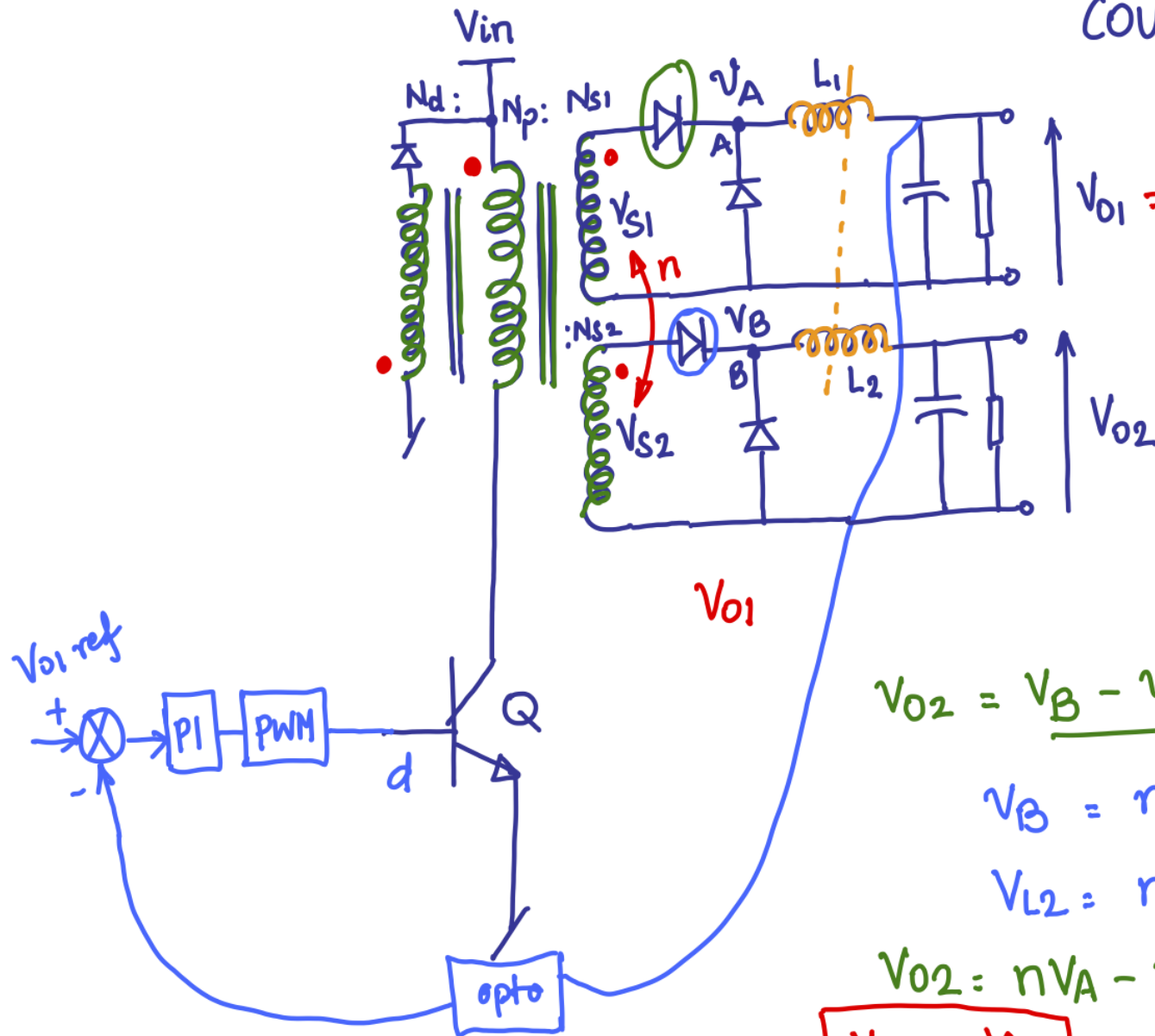

$$V_{o1} = V_A - V_{L1}$$

$$\frac{V_{s2}}{V_{s1}} = n = \frac{N_{s2}}{N_{s1}}$$

$$n = \frac{N_{L2}}{N_{L1}}$$

$$V_{o2} = V_B - V_{L2}$$


$$V_B = n V_A$$

$$V_{L2} = n V_{L1}$$


$$V_{o2} = n V_A - n V_{L1} = n (V_A - V_{L1})$$

$$\underline{V_{o2} = n V_{o1}}$$

$$\therefore V_{s2} = n V_{s1}$$

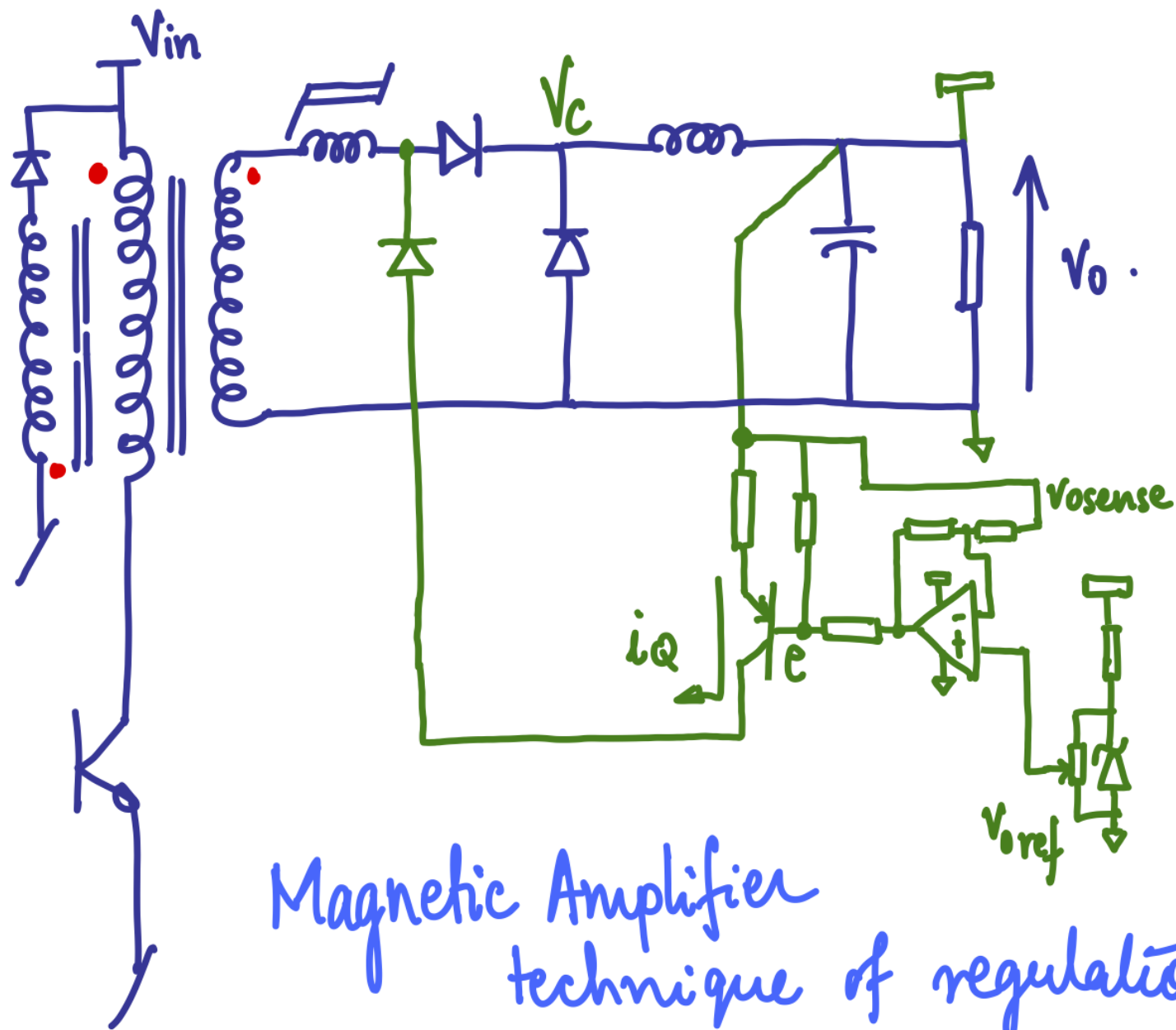

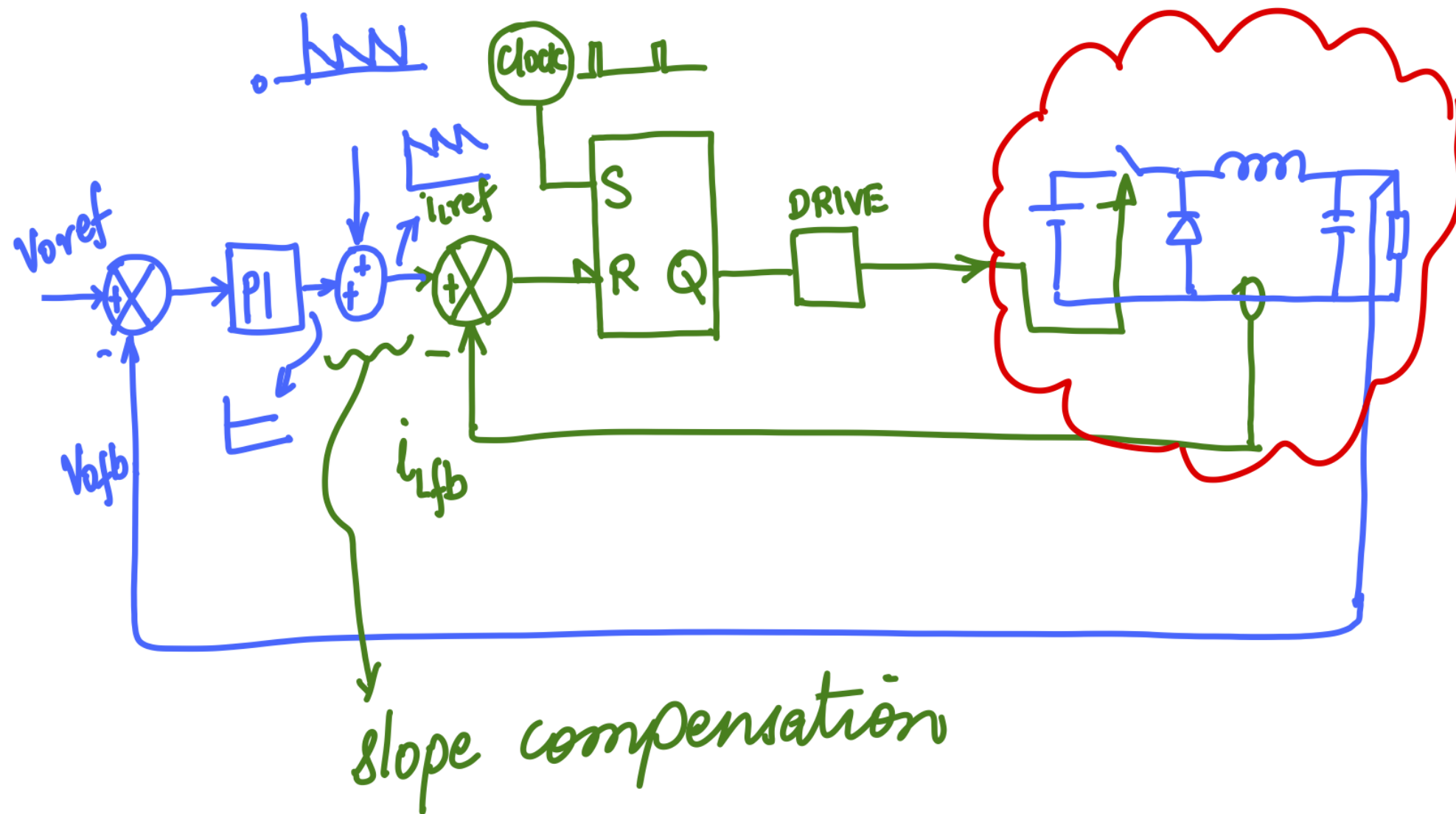Magnetic Amplifier
technique of regulation



FARADAY EQN.

AMPERE'S RULE

Electric

Magnetic.

$\mathcal{V} = N \frac{d\phi}{dt}$

$Ni = \text{mmf}$

mmf

$Ni = \int H \cdot dl$

$Ni = H \cdot l_m$

$H = \frac{Ni}{l_m}$

i

$\frac{d\phi}{dt}$

N

Number
of turns of the winding.

FULL BRIDGE FORWARD CONVERTER.

