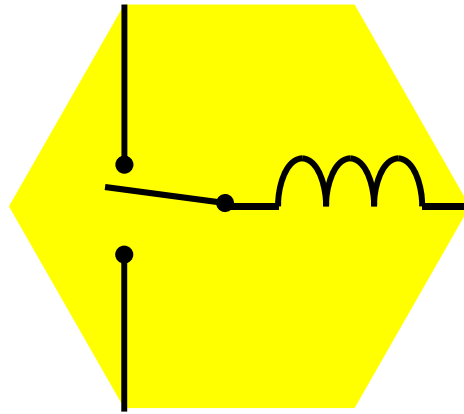


Switched Mode Power Conversion


Non-Isolated Converters



Basic Converter Cell

Switched Mode Power Conversion


Non-Isolated Converters

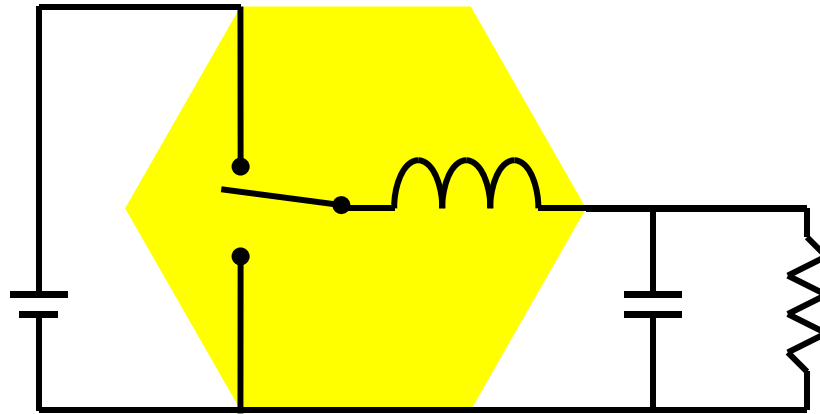

Buck Converter

Switched Mode Power Conversion

Non-Isolated Converters

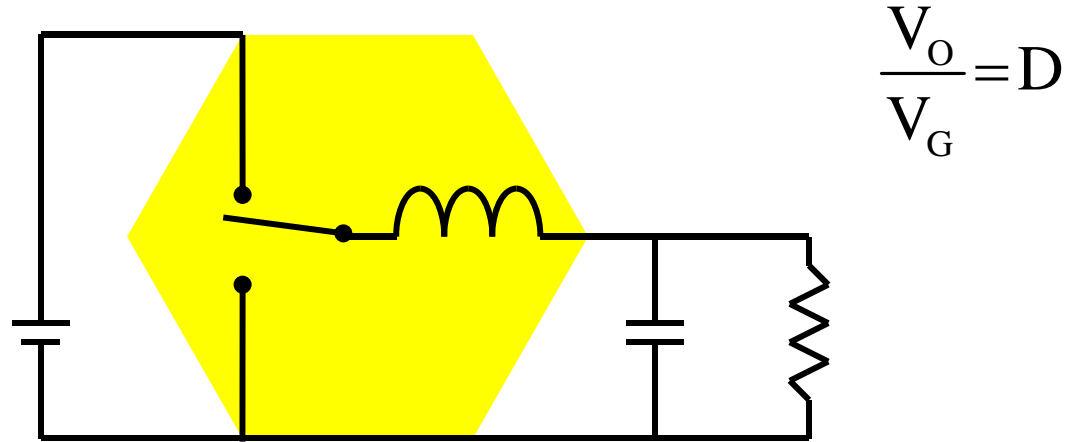


Buck Converter

Switched Mode Power Conversion

Non-Isolated Converters

$$\frac{I_O}{I_G} = \frac{1}{D}$$

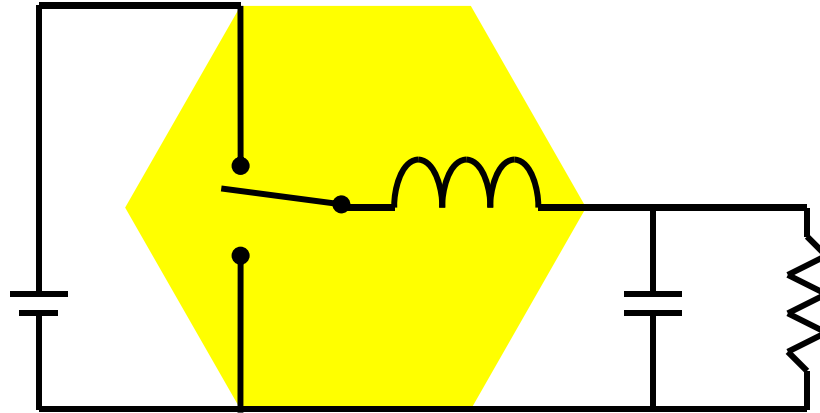


$$\frac{V_O}{V_G} = D$$

Buck Converter

Switched Mode Power Conversion


Non-Isolated Converters

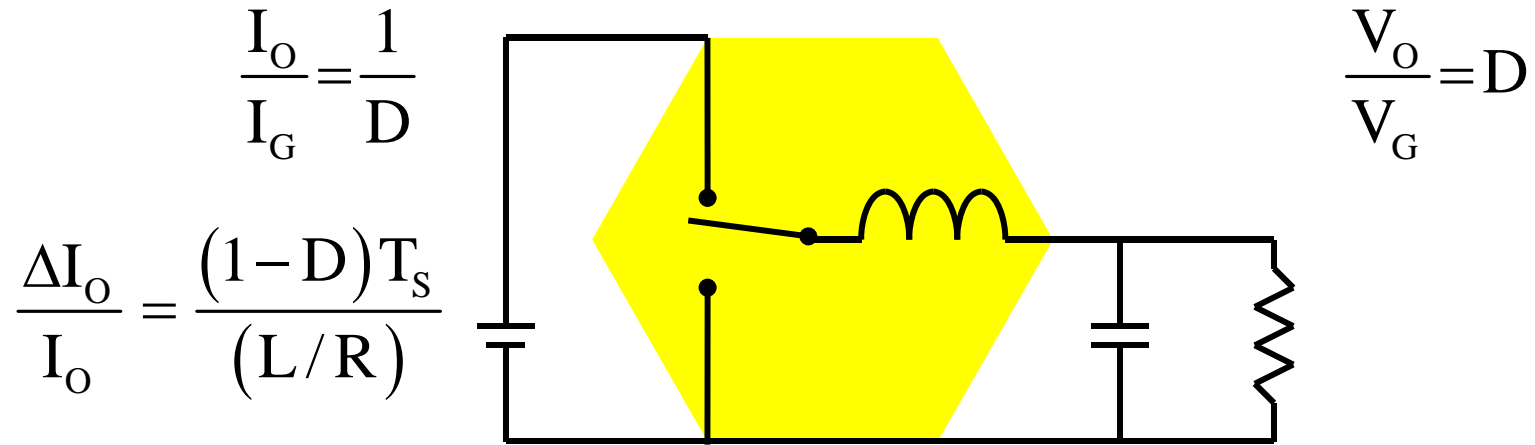

Buck Converter

Switched Mode Power Conversion


Non-Isolated Converters

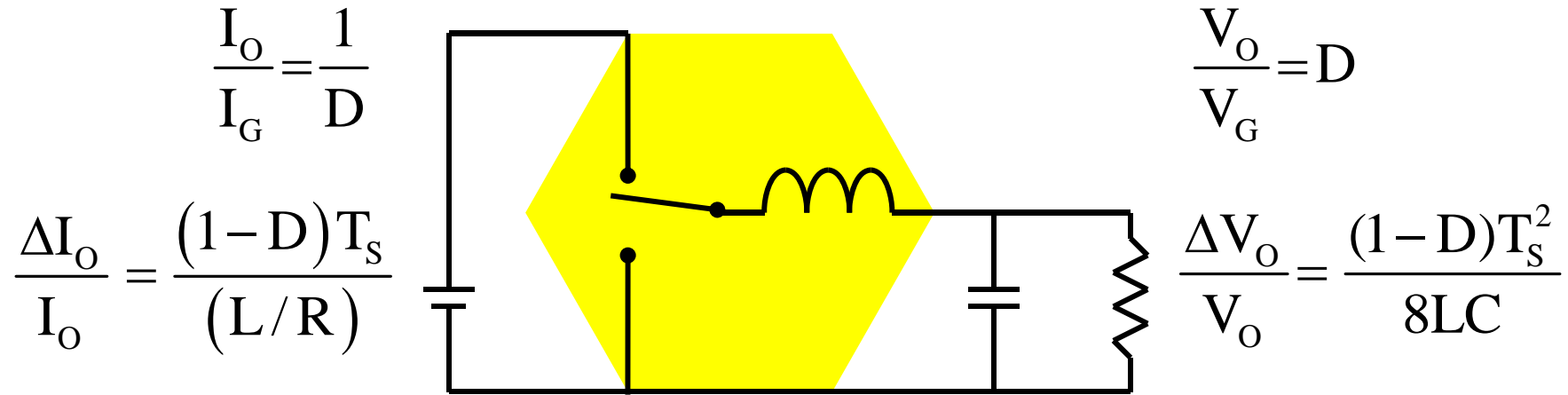

Buck Converter

Switched Mode Power Conversion

Non-Isolated Converters

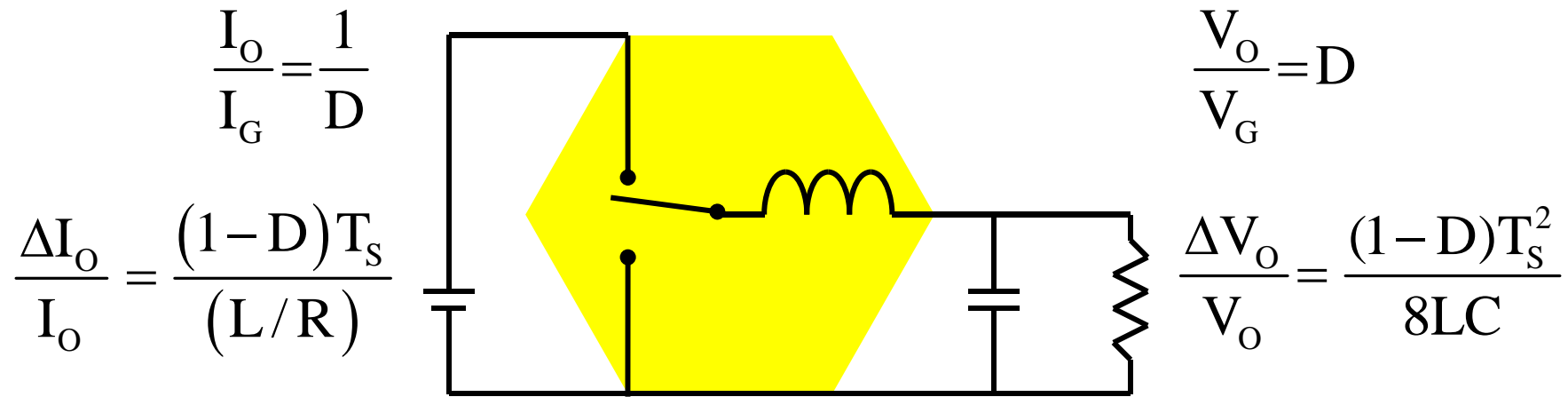


$$\frac{V_O}{V_G} = D \left(\frac{1 - \frac{V_T}{V_G} - \frac{(1-D)V_D}{DV_G}}{1 + \frac{DR_s}{R} + \frac{R_l}{R}} \right)$$

Buck Converter

Switched Mode Power Conversion

Non-Isolated Converters


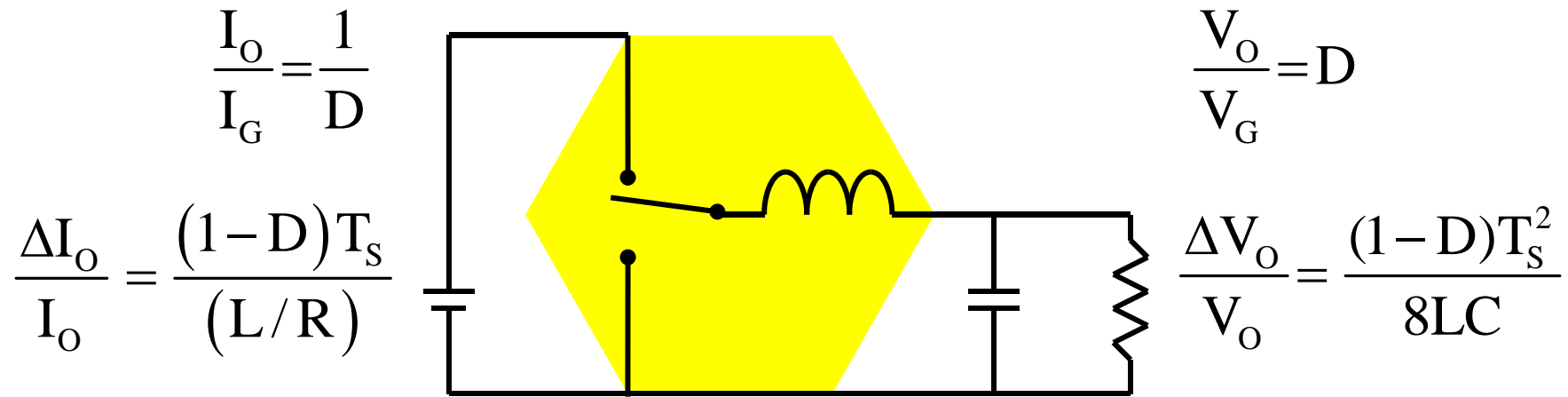


$$\frac{V_O}{V_G} = D \left(\frac{1 - \frac{V_T}{V_G} - \frac{(1-D)V_D}{DV_G}}{1 + \frac{DR_s}{R} + \frac{R_1}{R}} \right) \quad \eta = \frac{V_O I_O}{V_G I_G} = \left(\frac{1 - \frac{V_T}{V_G} - \frac{(1-D)V_D}{DV_G}}{1 + \frac{DR_s}{R} + \frac{R_1}{R}} \right)$$

Buck Converter

Switched Mode Power Conversion




Non-Isolated Converters

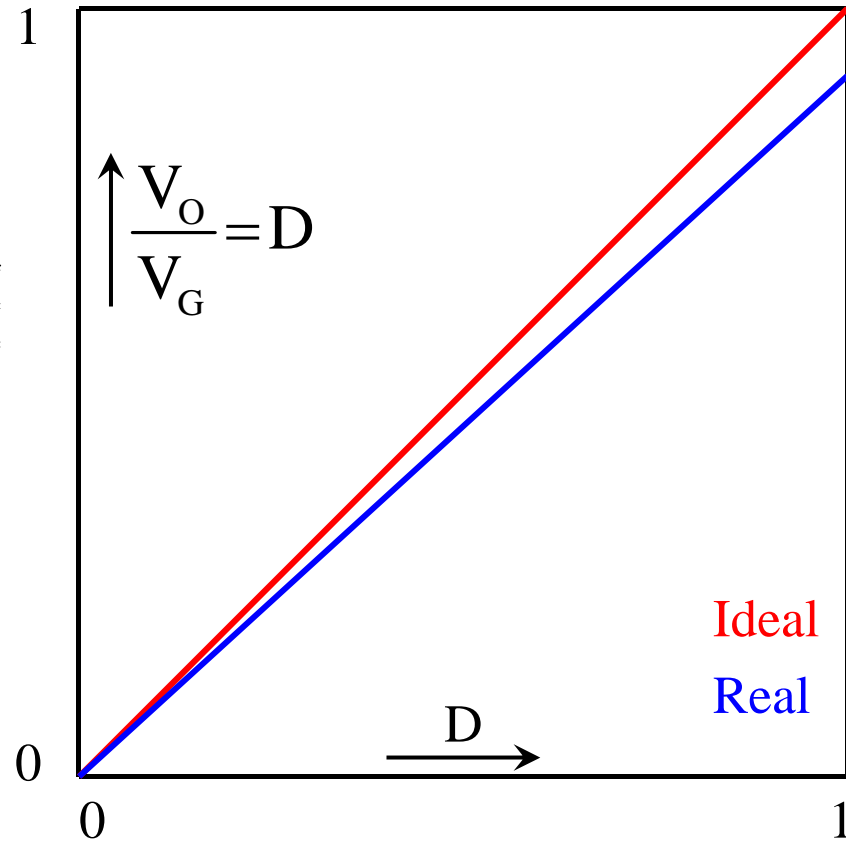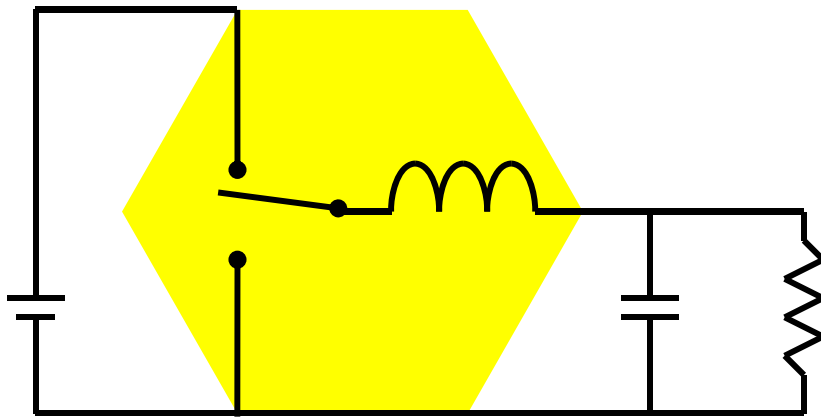

Step-Down Converter

Switched Mode Power Conversion


Basic Converter Cell

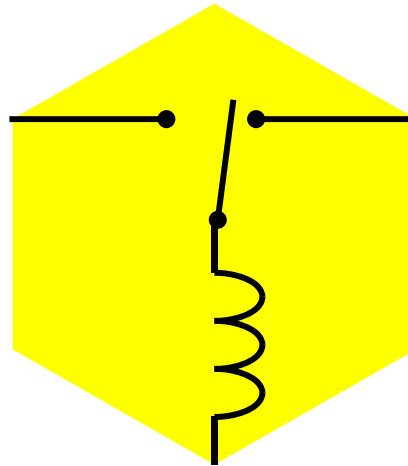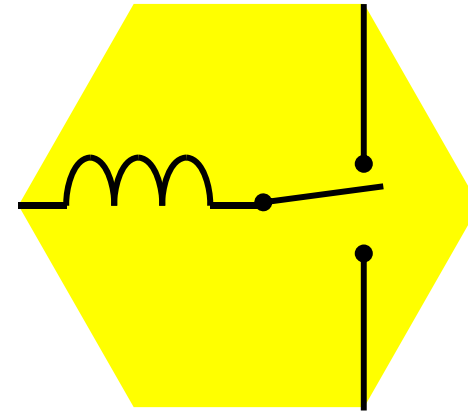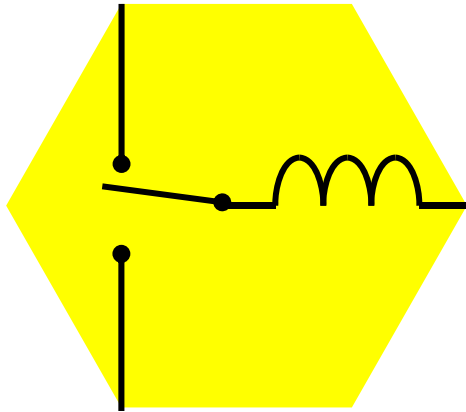

Three Variants of the Switch-Inductor Cell

Switched Mode Power Conversion


Buck Converter

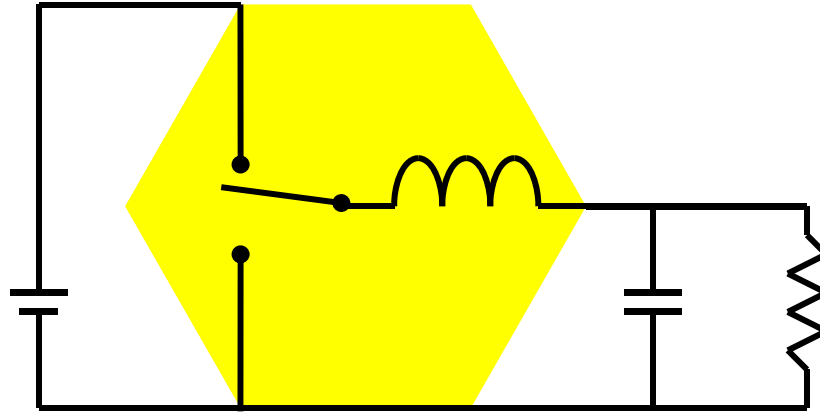

Voltage Input Current Output Converter

Switched Mode Power Conversion



Basic Power Converters

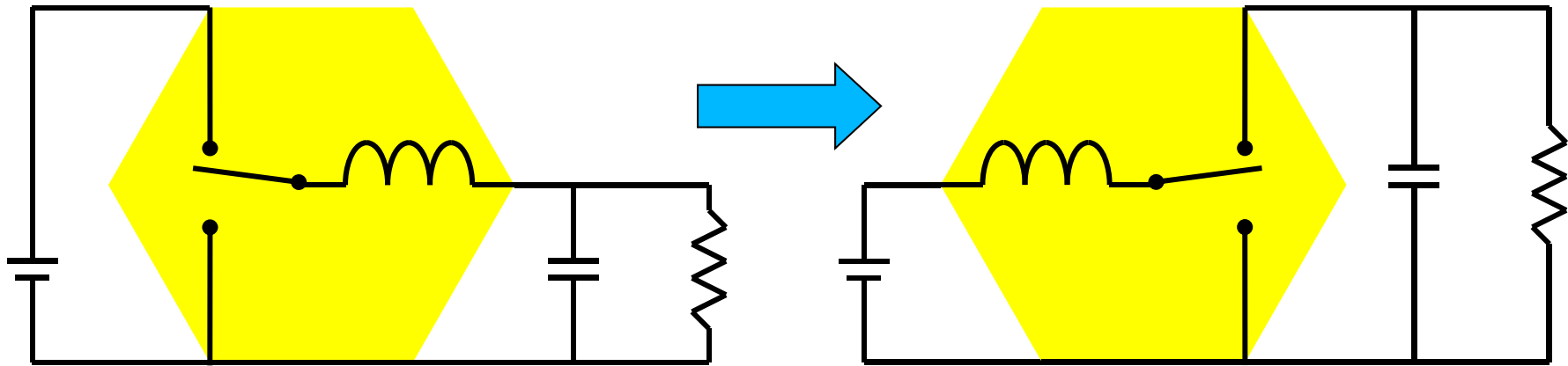

Current Input Voltage Output Variant

Switched Mode Power Conversion


Basic Power Converters

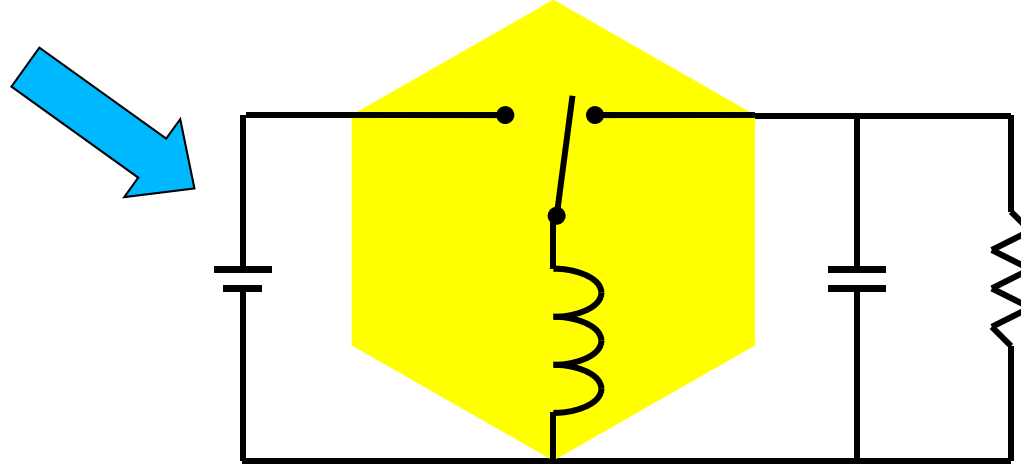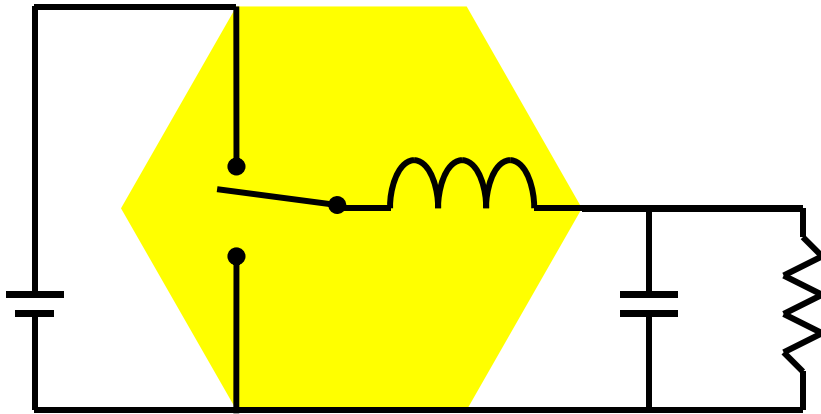

Current Input Current Output Variant

Switched Mode Power Conversion


Basic Power Converters

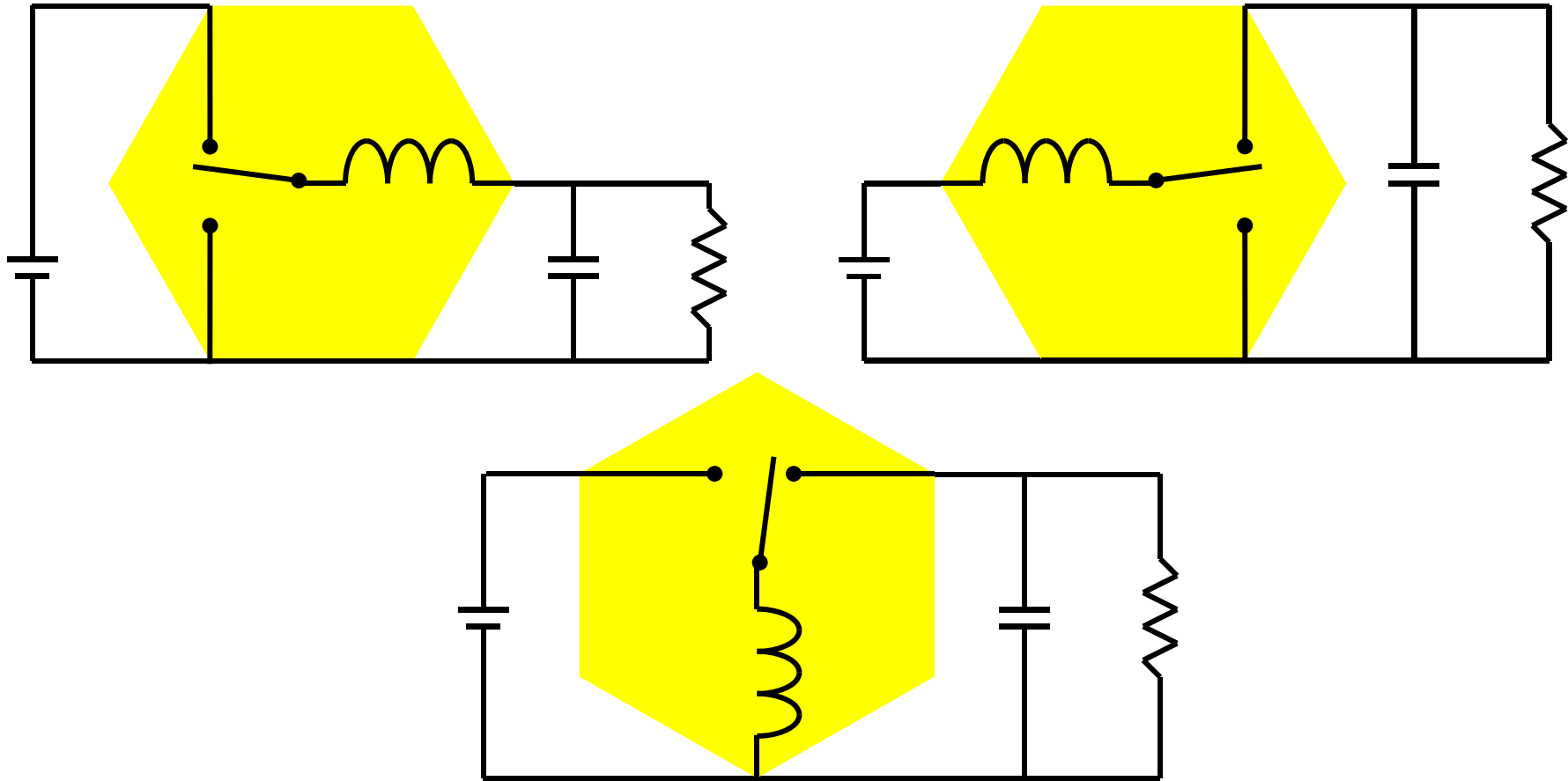

Buck, Boost & Buck-Boost Variants

Switched Mode Power Conversion


Analysis of Boost Converters

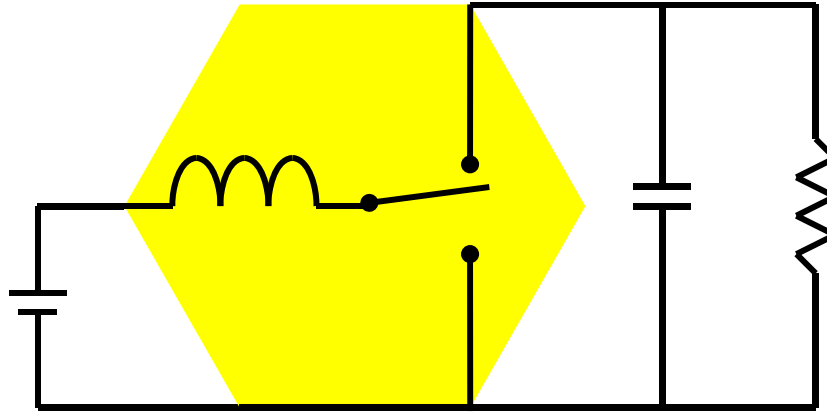

Boost Converter

Switched Mode Power Conversion

Analysis of Boost Converters

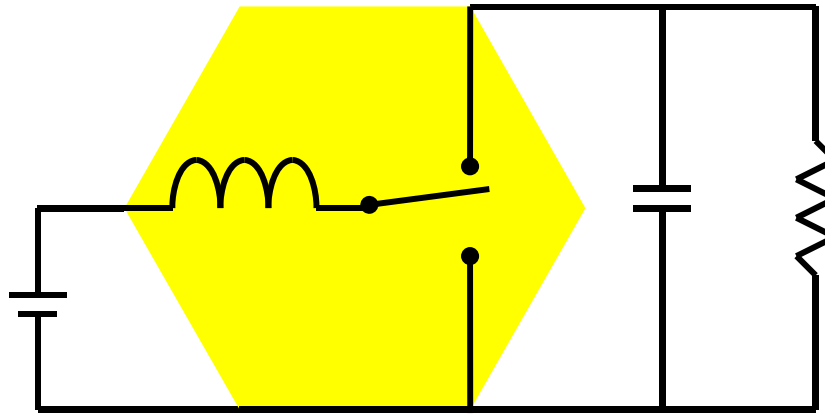

Voltage Gain V_O/V_G

Current Gain I_O/I_G

Current Ripple $\Delta I_O/I_O$


Voltage Ripple $\Delta V_O/V_O$

Switch, Source, Storage Non-ideality

Efficiency

Switched Mode Power Conversion

Boost Converter


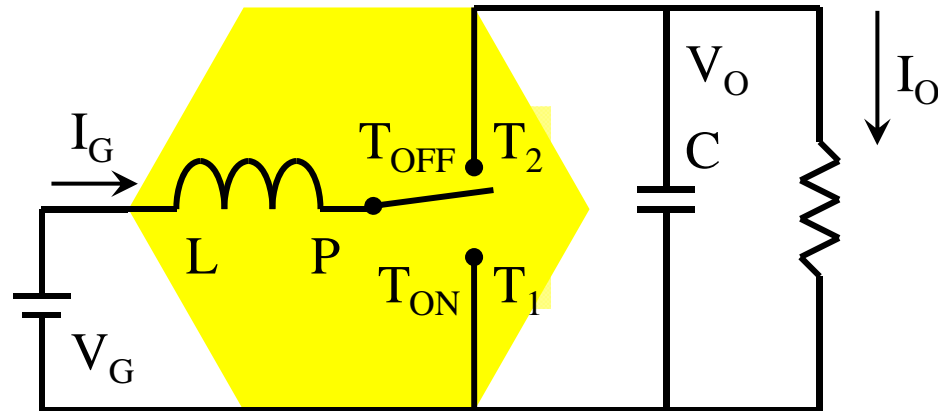


$$\frac{V_O}{V_G} = ?$$

Voltage Conversion Ratio

Switched Mode Power Conversion



Boost Converter

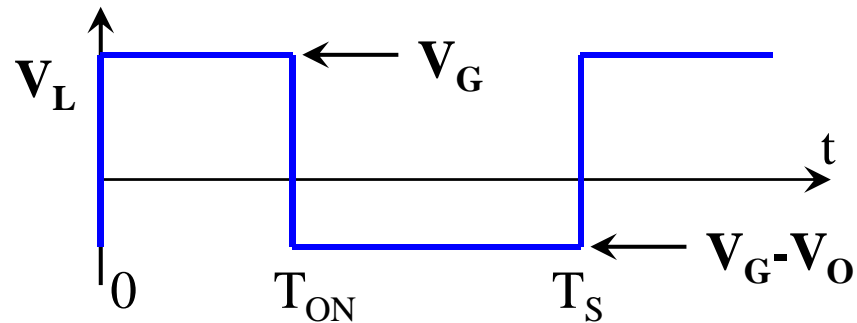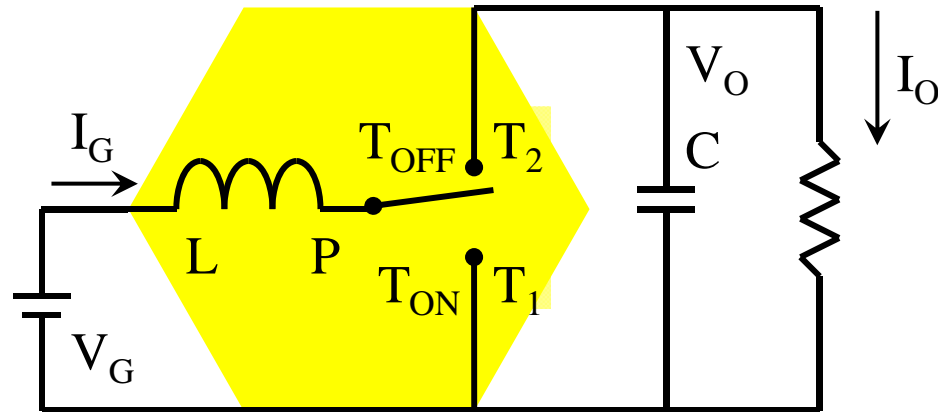

Inductor Volt-Sec Balance

Switched Mode Power Conversion


Boost Converter

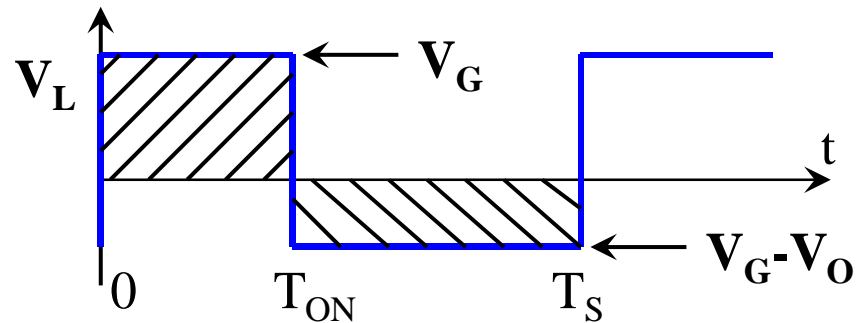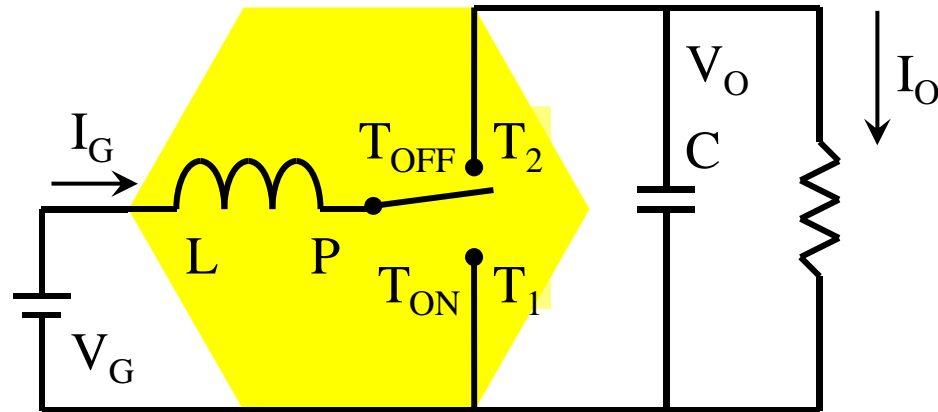

Inductor Volt-Sec Balance

Switched Mode Power Conversion

Boost Converter

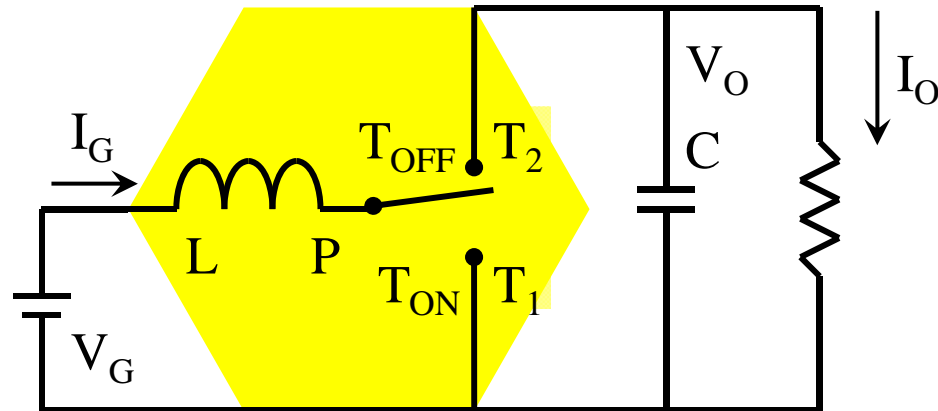


$$(V_G)T_{ON} + (V_G - V_O)T_{OFF} = 0$$

$$\frac{V_O}{V_G} = \frac{T_S}{T_{OFF}} = \frac{1}{1-D}$$


Switched Mode Power Conversion

Boost Converter

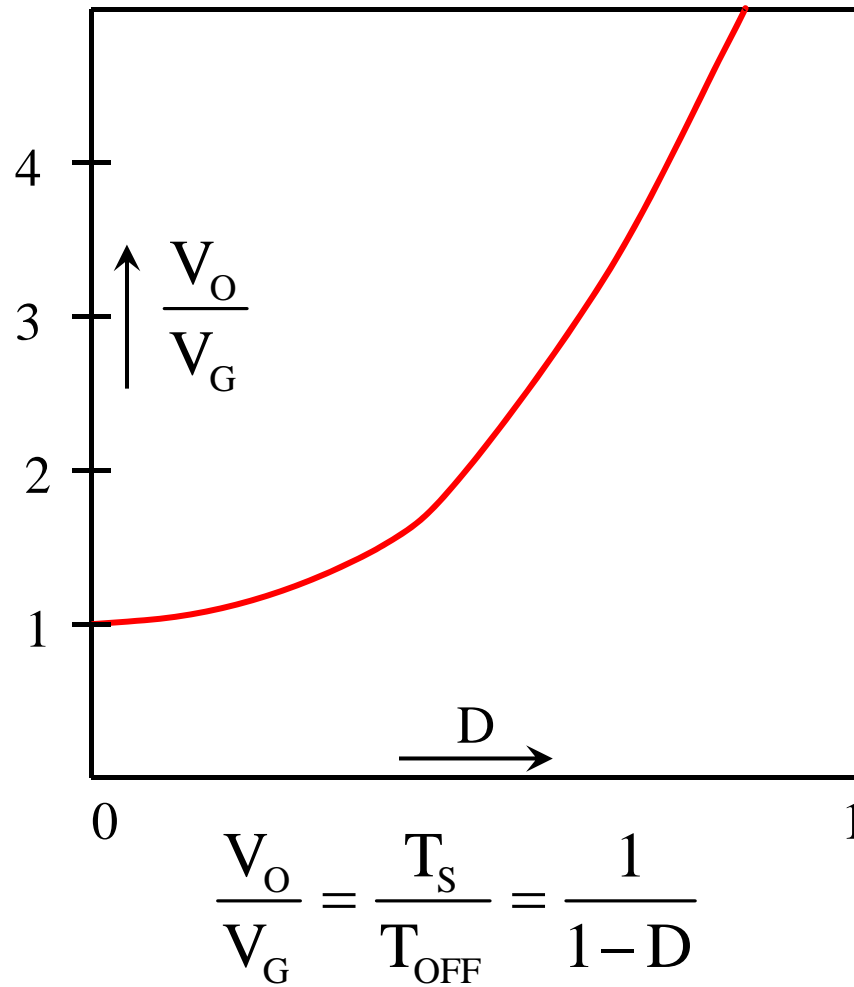

Switched Mode Power Conversion

Boost Converter

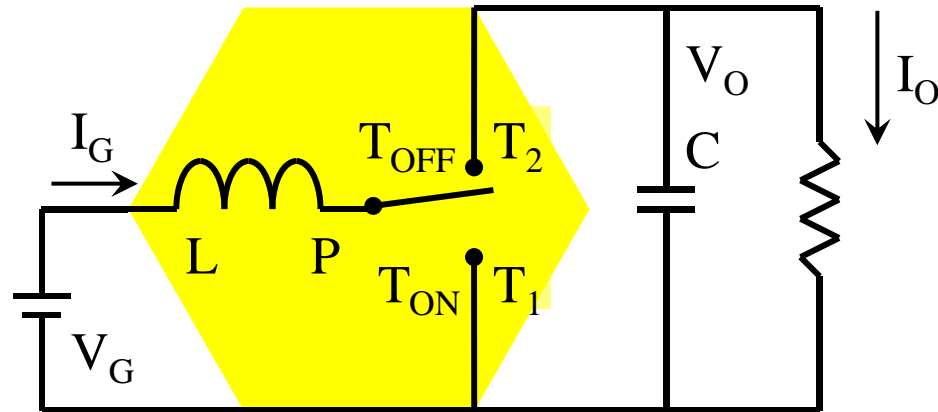


$$\frac{I_G}{I_O} = ?$$

Current Conversion Ratio

Switched Mode Power Conversion

Boost Converter

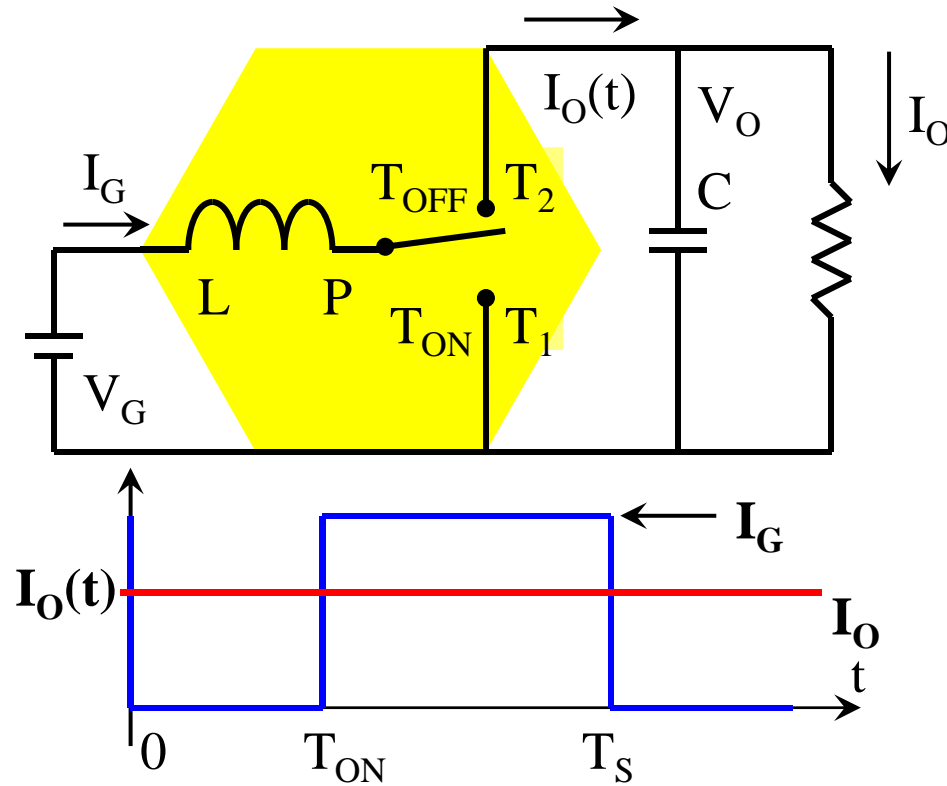


$$I_G T_{OFF} = I_O T_S$$

Average Output Current

Switched Mode Power Conversion

Boost Converter

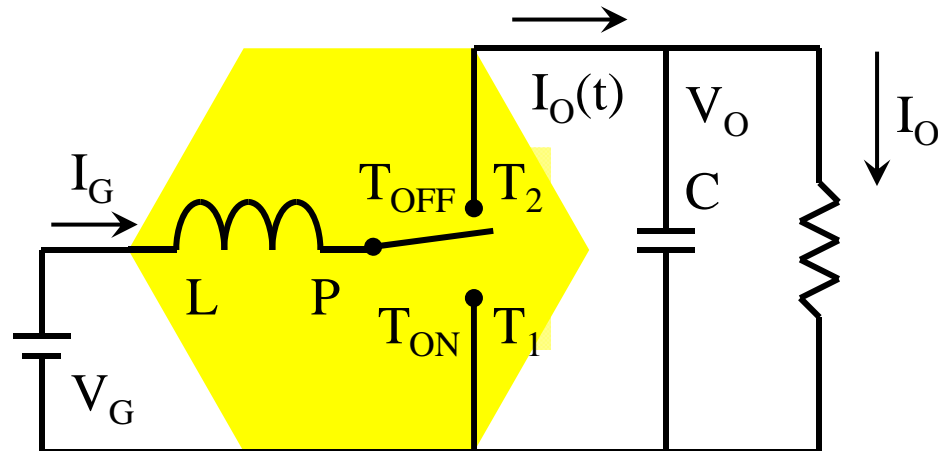


$$I_G T_{OFF} = I_O T_S$$

$$\frac{I_G}{I_O} = \frac{T_S}{T_{OFF}} = \frac{1}{1-D}$$

Current Conversion Ratio

Switched Mode Power Conversion

Boost Converter

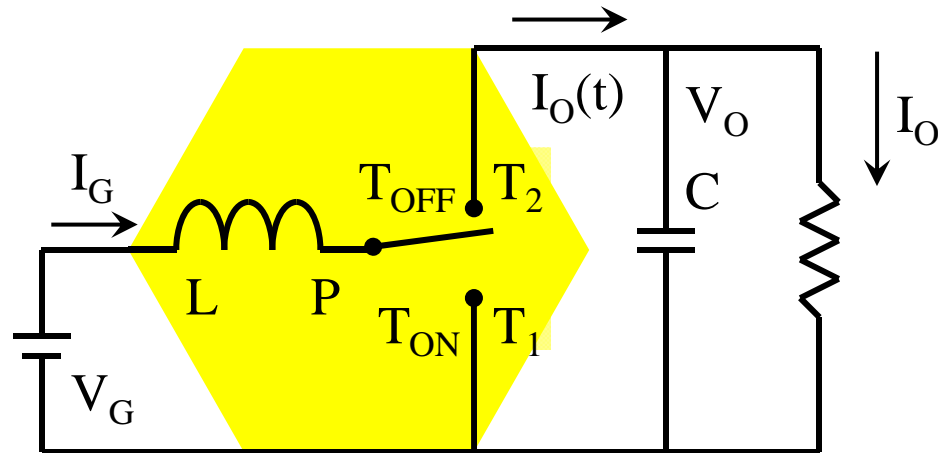


$$\frac{V_O}{V_G} \frac{I_O}{I_G} = \frac{1}{1-D} \frac{1-D}{1} = 1$$

Ideal Efficiency is Unity

Switched Mode Power Conversion



Boost Converter

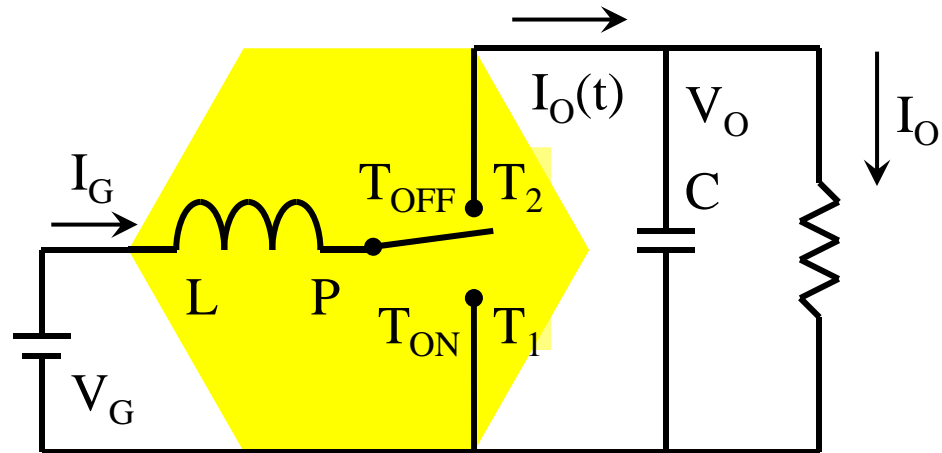

Non-Ideality in the Inductor Current

Switched Mode Power Conversion


Boost Converter

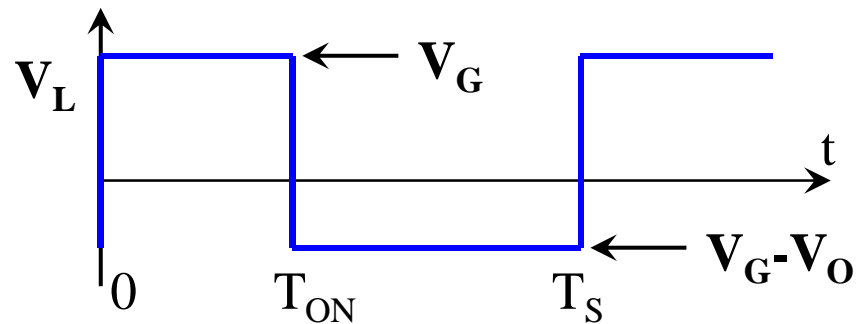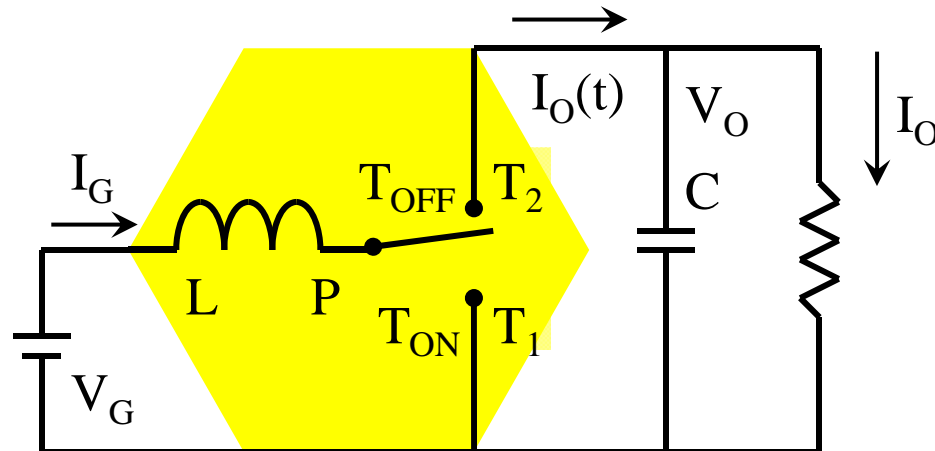

Inductor Current Ripple – Integral of Inductor Voltage

Switched Mode Power Conversion

Boost Converter

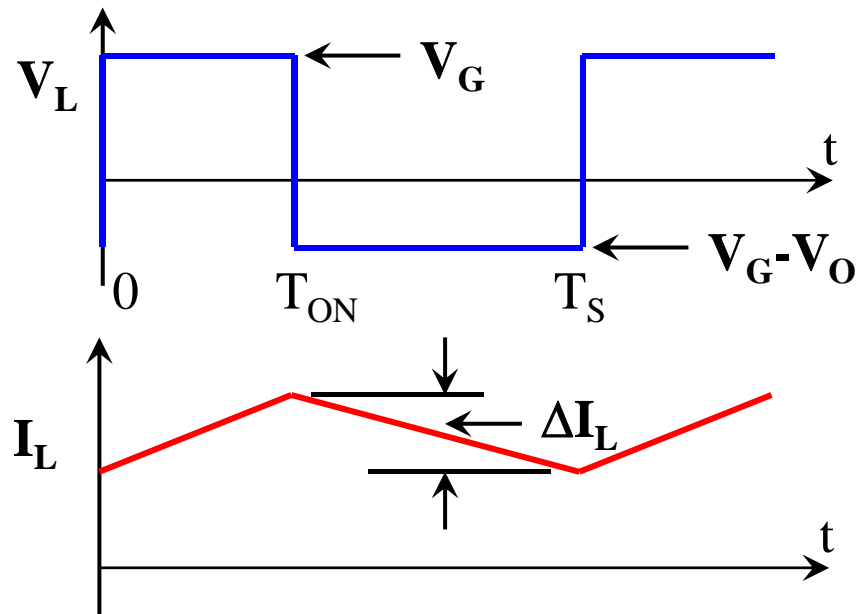


$$\Delta I_L = \frac{V_G}{L} D T_S$$

Inductor Current Ripple – Integral of Inductor Voltage

Switched Mode Power Conversion

Boost Converter

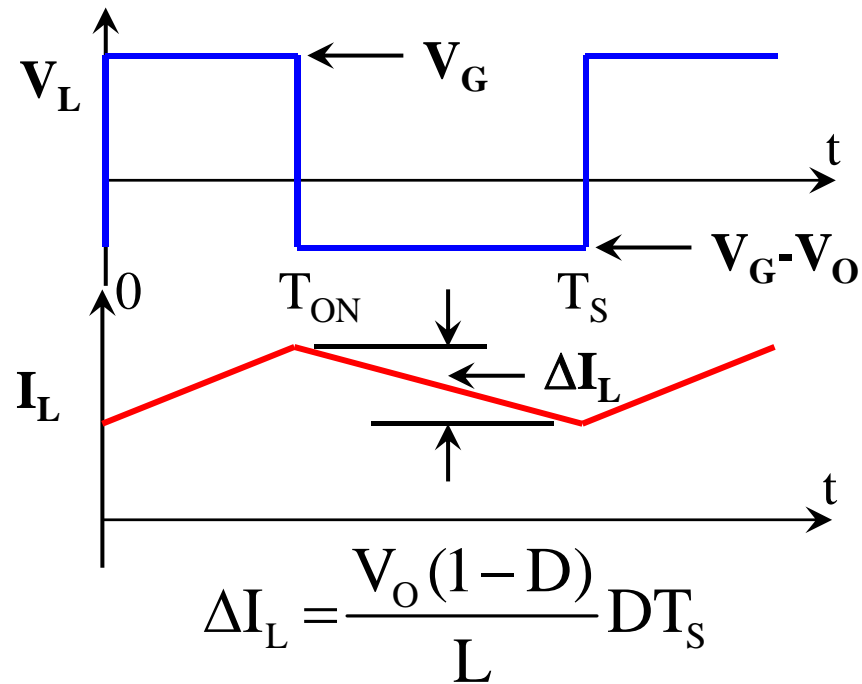


$$I_L = \frac{I_O}{1 - D} = \frac{V_O}{R (1 - D)}$$

Inductor Current Ripple – Integral of Inductor Voltage

Switched Mode Power Conversion

Boost Converter

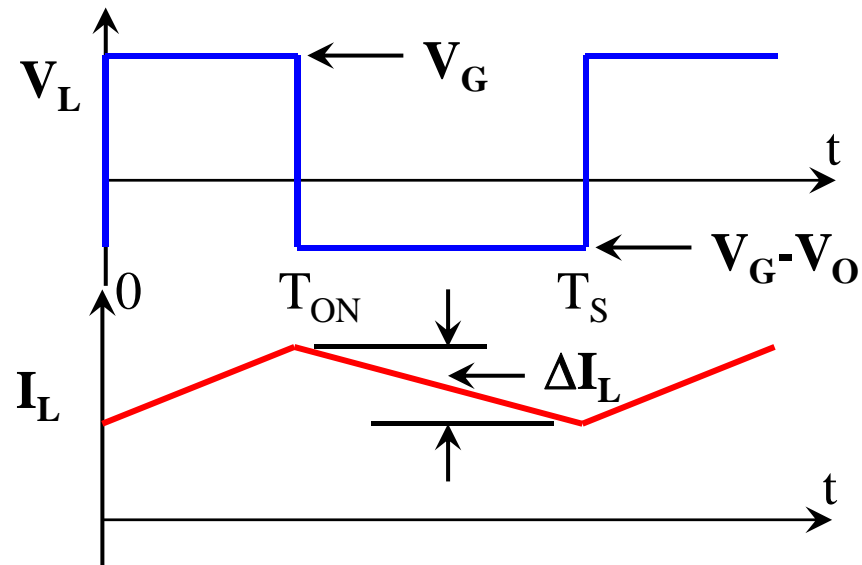


$$\frac{\Delta I_L}{I_L} = \frac{(1-D)^2}{(L/R)} D T_s$$

Inductor Current Ripple – Integral of Inductor Voltage

Switched Mode Power Conversion

Boost Converter

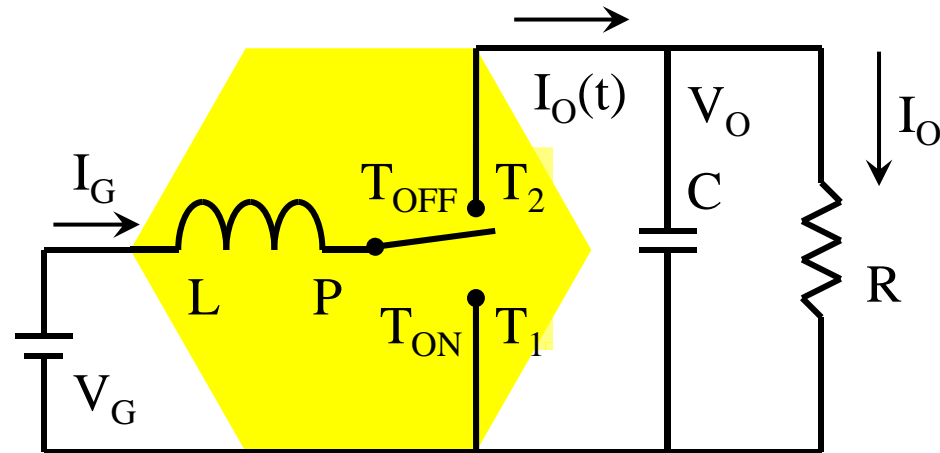


$$\frac{\Delta I_L}{I_L} = \frac{(1-D)^2}{(L/R)} D T_s \quad T_s \ll \frac{L}{R}$$

Condition for Low Ripple Current

Switching Period $T_s \ll$ Circuit Time Constant (L/R)

Switched Mode Power Conversion

Boost Converter


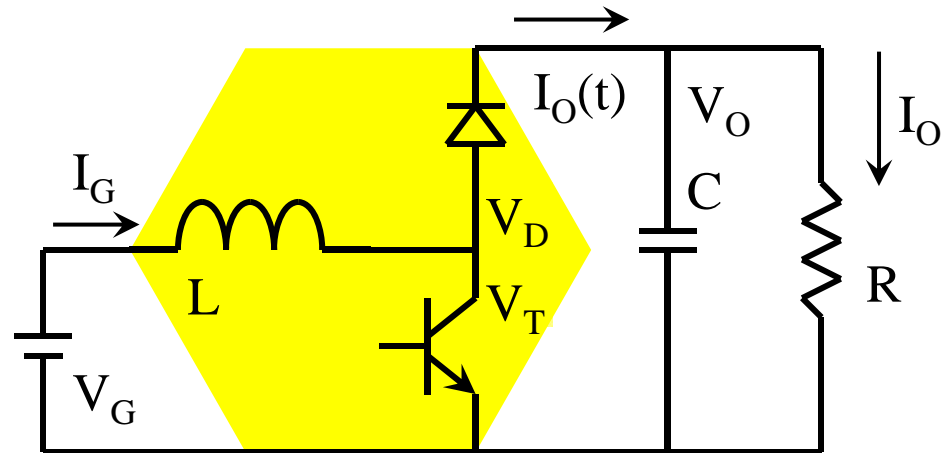


$$\frac{V_O}{V_G} = ?$$

Non-Ideality of the Switches

Switched Mode Power Conversion


Boost Converter

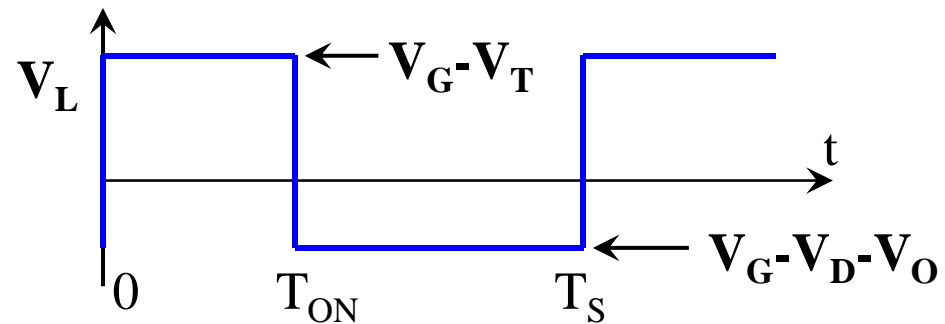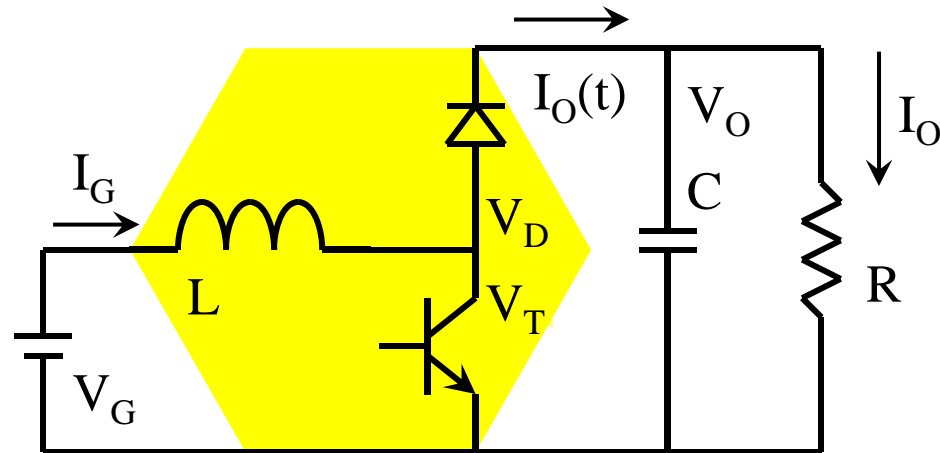

Volt-Sec Balance on Inductor

Switched Mode Power Conversion

Boost Converter

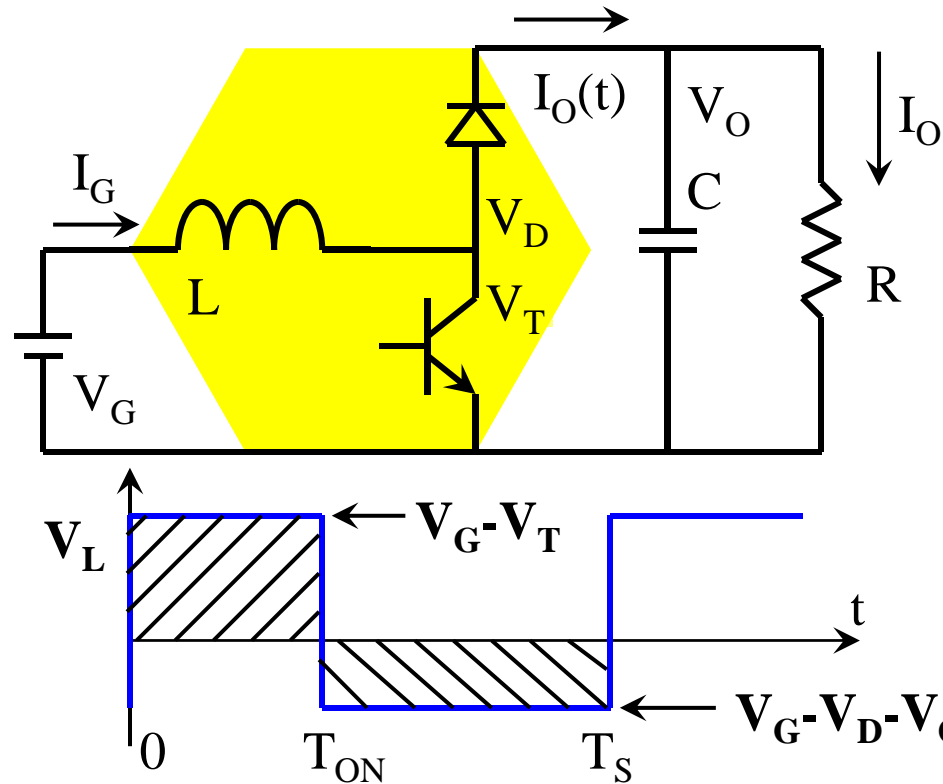


$$(V_G - V_T)T_{ON} + (V_G - V_D - V_O)T_{OFF} = 0$$

Volt-Sec Balance on Inductor

Switched Mode Power Conversion

Boost Converter

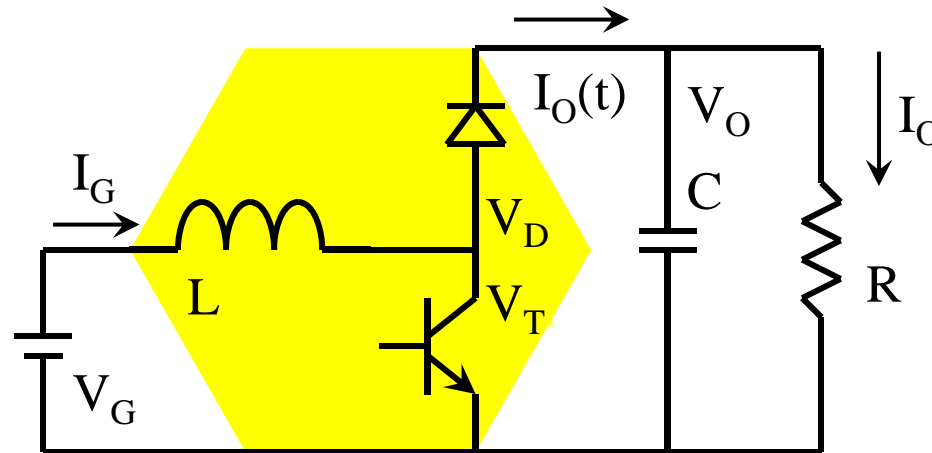


$$\frac{V_O}{V_G} = \frac{1}{1-D} \left(1 - \frac{DV_T}{V_G} - \frac{(1-D)V_D}{V_G} \right)$$

$$\eta = \left(1 - \frac{DV_T}{V_G} - \frac{(1-D)V_D}{V_G} \right)$$

Volt-Sec Balance on Inductor

Switched Mode Power Conversion

Boost Converter

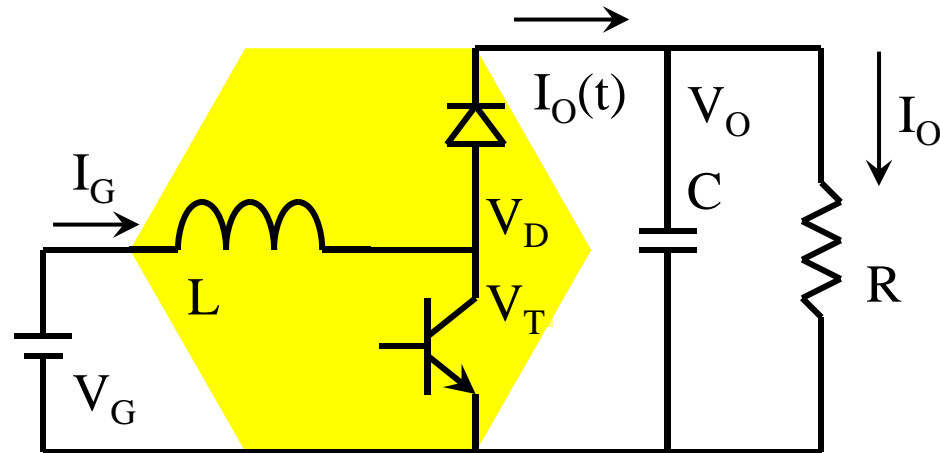


$$\frac{I_G}{I_O} = \frac{1}{1-D}$$

Current Averaging

Switched Mode Power Conversion

Boost Converter

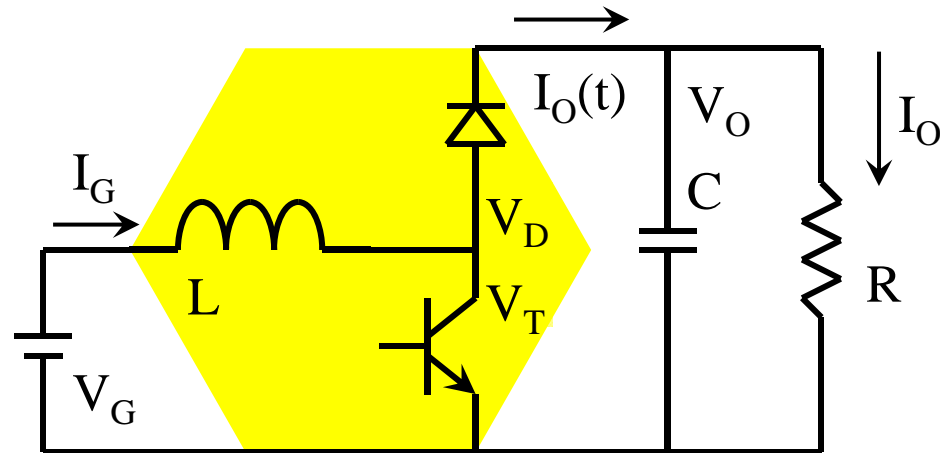



$$\frac{V_O I_O}{V_G I_G} = \frac{1}{1-D} \left(1 - \frac{D V_T}{V_G} - \frac{(1-D) V_D}{V_G} \right) \frac{1-D}{1}$$

$$\eta = \left(1 - \frac{D V_T}{V_G} - \frac{(1-D) V_D}{V_G} \right)$$

Efficiency of Power Conversion

Switched Mode Power Conversion

Boost Converter

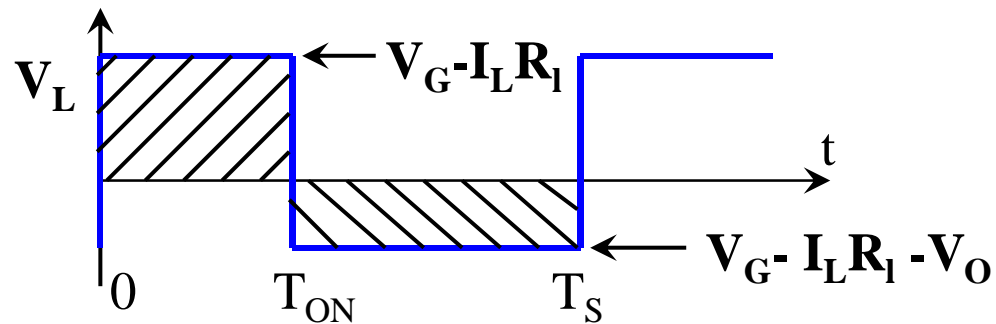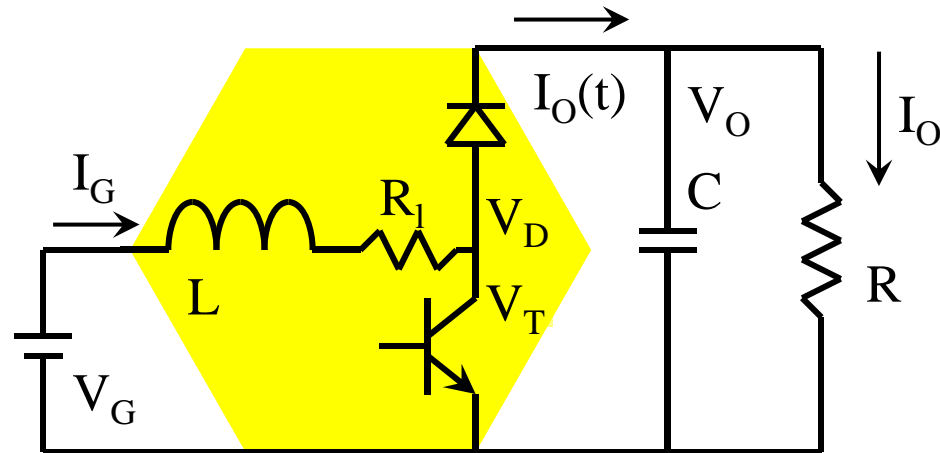

Non-Ideality of the Inductor


Switched Mode Power Conversion

Boost Converter

$$(V_G - I_L R_1) T_{\text{on}} + (V_G - I_L R_1 - V_O) T_{\text{OFF}} = 0$$

$$V_G = V_O (1 - D) + I_L R_1 = V_O (1 - D) + \frac{I_O}{(1 - D)} R_1$$
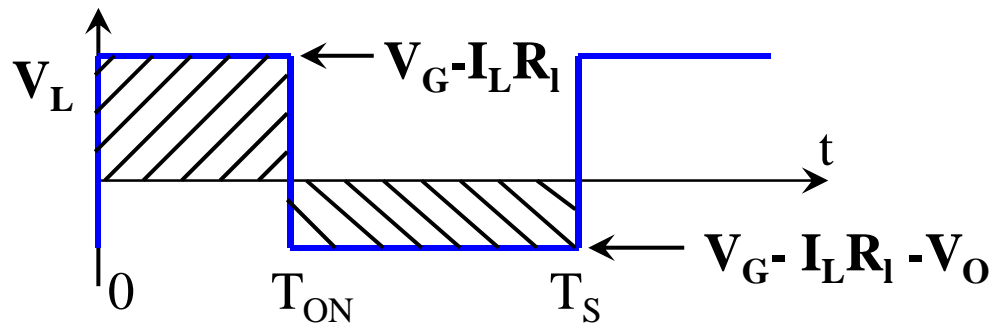
$$V_G = V_O (1 - D) + \frac{V_O}{(1 - D)} \frac{R_1}{R}$$



Volt-Second Balance

Switched Mode Power Conversion

Boost Converter

$$V_G = V_O(1-D) + \frac{V_O}{(1-D)} \frac{R_1}{R}$$

Define : $\alpha = \frac{R_1}{R}$

$$\frac{V_O}{V_G} = \frac{1}{(1-D)} \frac{1}{\left(1 + \frac{\alpha}{(1-D)^2}\right)}$$

Voltage Conversion Ratio

Switched Mode Power Conversion

Boost Converter

$$\frac{V_O}{V_G} = \frac{1}{(1-D)} \frac{1}{\left(1 + \frac{\alpha}{(1-D)^2}\right)}$$

$$\frac{I_G}{I_O} = \frac{1}{(1-D)}$$


$$\eta = \frac{V_O I_O}{V_G I_G} = \frac{1}{\left(1 + \frac{\alpha}{(1-D)^2}\right)}$$

Efficiency of Power Conversion

Switched Mode Power Conversion

Boost Converter
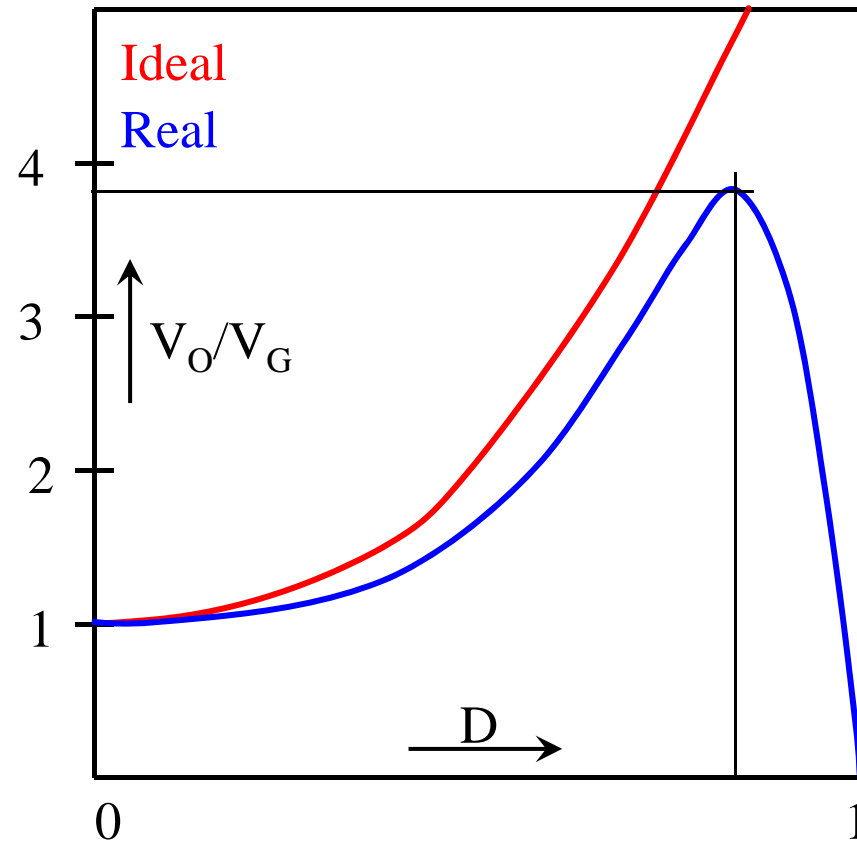
$$\frac{V_O}{V_G} = \frac{1}{(1-D)} \frac{1}{\left(1 + \frac{\alpha}{(1-D)^2}\right)}$$




Real Forward Voltage Gain

Switched Mode Power Conversion

Boost Converter
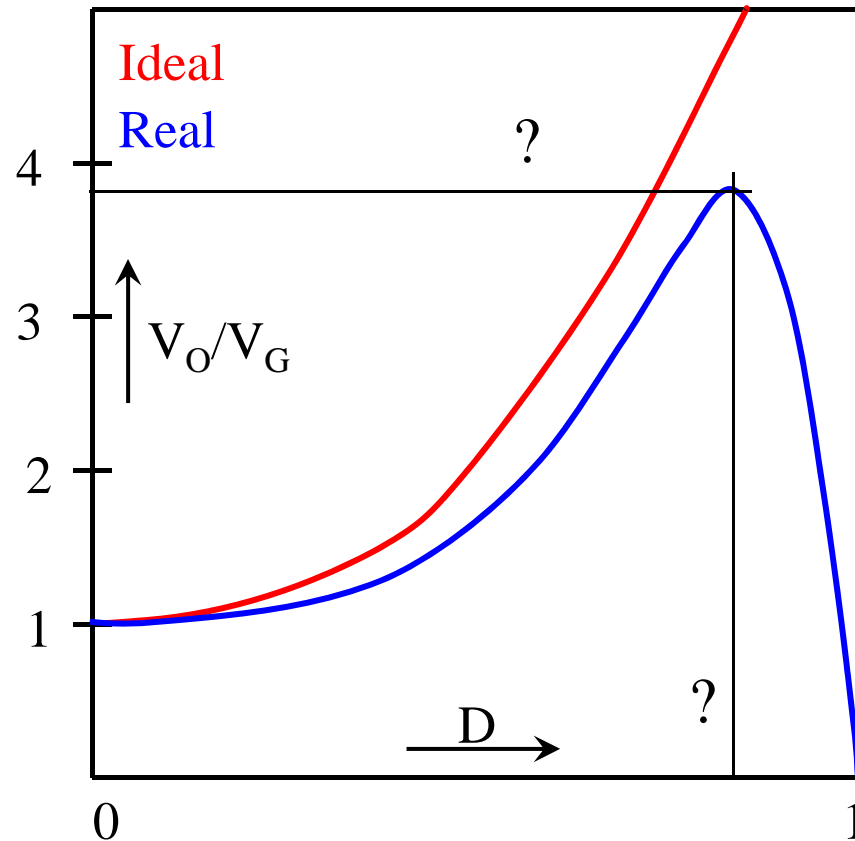
$$\frac{V_O}{V_G} = \frac{1}{(1-D)} \frac{1}{\left(1 + \frac{\alpha}{(1-D)^2}\right)}$$



Real Forward Voltage Gain


Switched Mode Power Conversion

Boost Converter

$$\frac{V_O}{V_G} = \frac{1}{(1-D)} \frac{1}{\left(1 + \frac{\alpha}{(1-D)^2}\right)}$$

$$\frac{V_O}{V_G} = \frac{(1-D)}{\left((1-D)^2 + \alpha\right)}$$
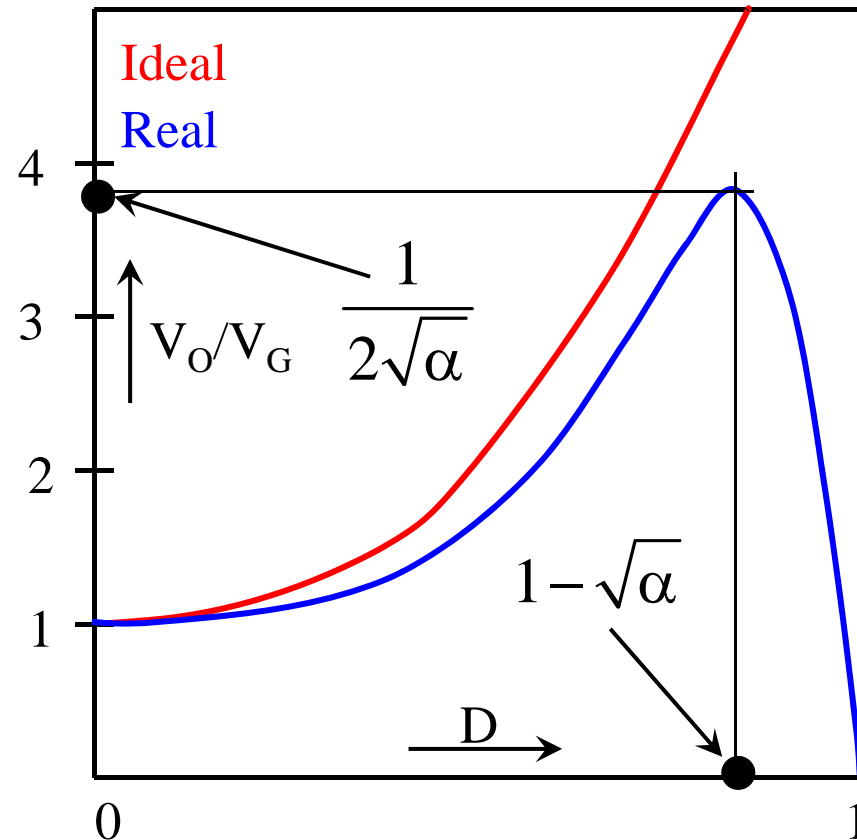
$$\frac{d\left(\frac{V_O}{V_G}\right)}{dD} = 0 \Rightarrow \alpha = (1-D)^2$$




Real Forward Voltage Gain

Switched Mode Power Conversion

Boost Converter

$$\eta = \frac{1}{\left(1 + \frac{\alpha}{(1-D)^2}\right)}$$
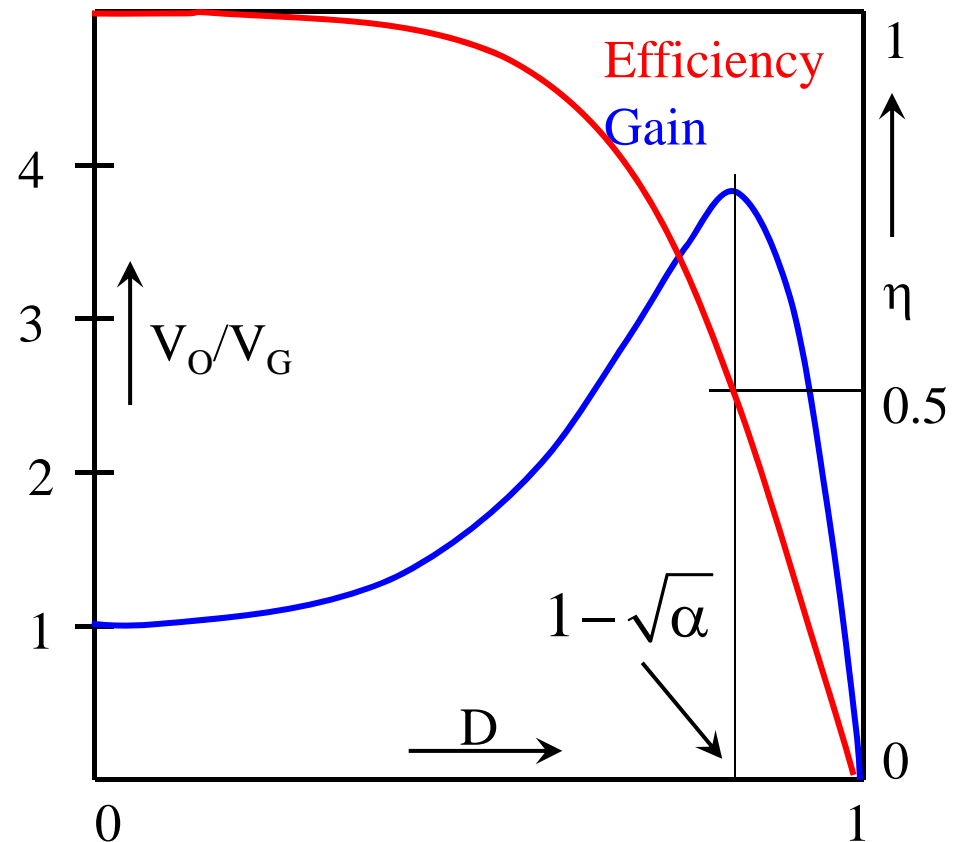
$$\eta = \frac{(1-D)^2}{\left((1-D)^2 + \alpha\right)}$$



Efficiency of a Real Converter


Switched Mode Power Conversion

Boost Converter

$$\eta = \frac{1}{\left(1 + \frac{\alpha}{(1-D)^2}\right)}$$

$$\eta = \frac{(1-D)^2}{((1-D)^2 + \alpha)}$$



Preferred
Operating Region

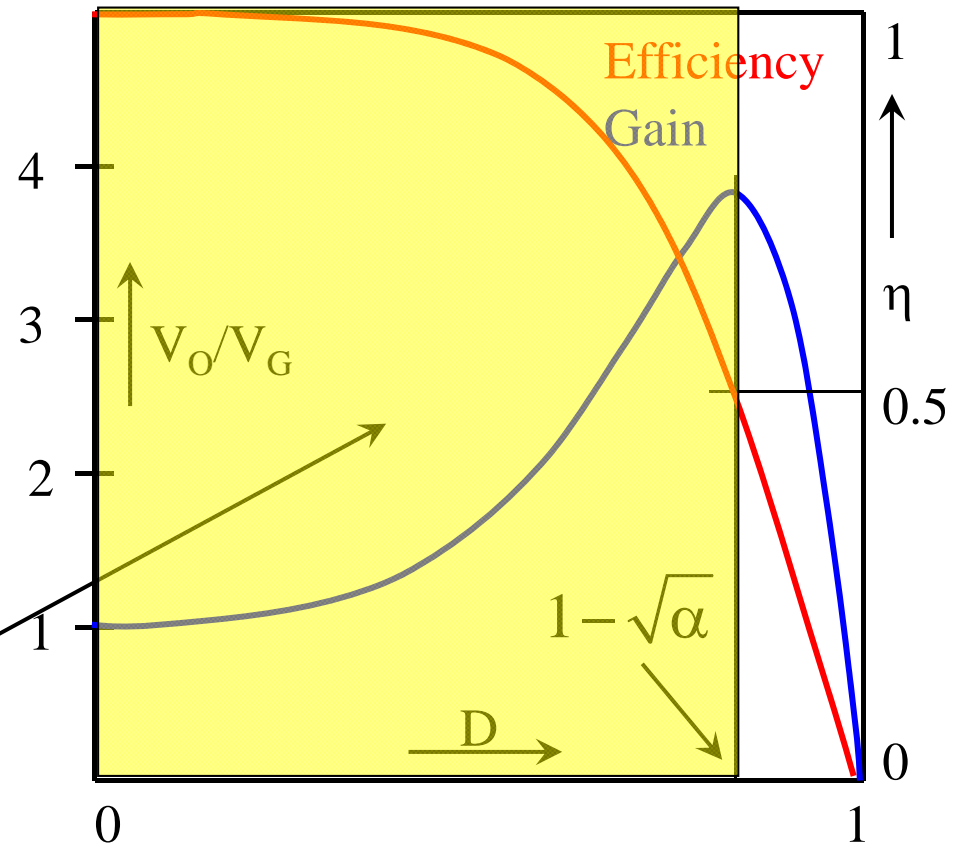

Preferred Range of Duty Ratio

Switched Mode Power Conversion



Boost Converter

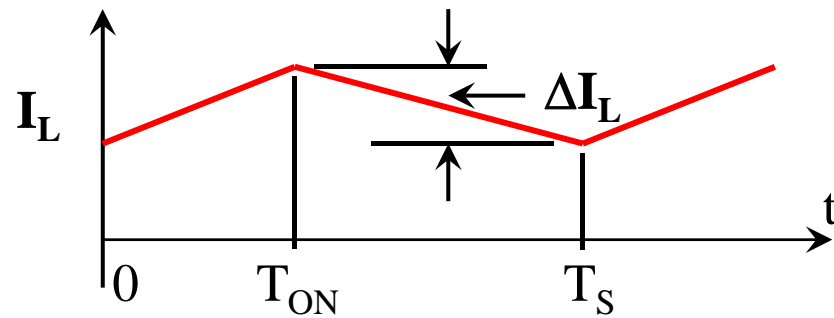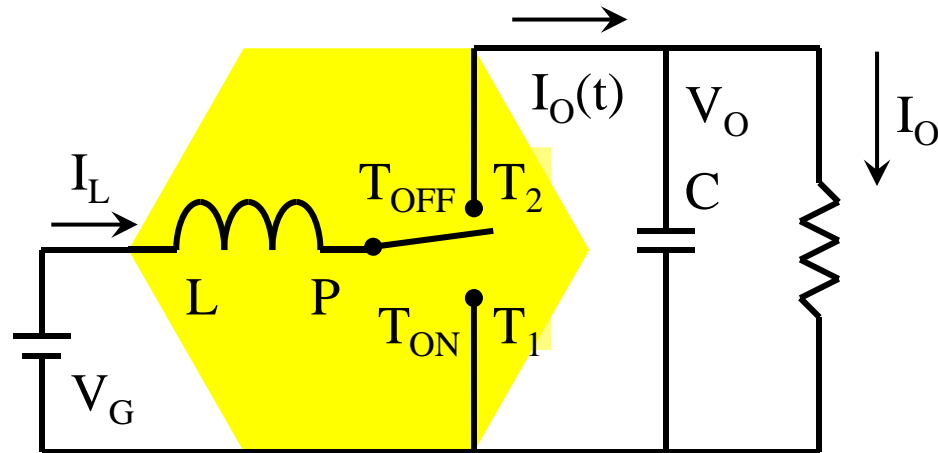

Output Voltage Ripple

Switched Mode Power Conversion



Boost Converter

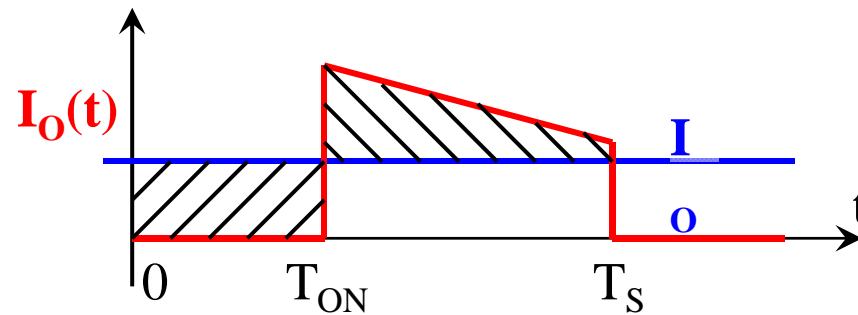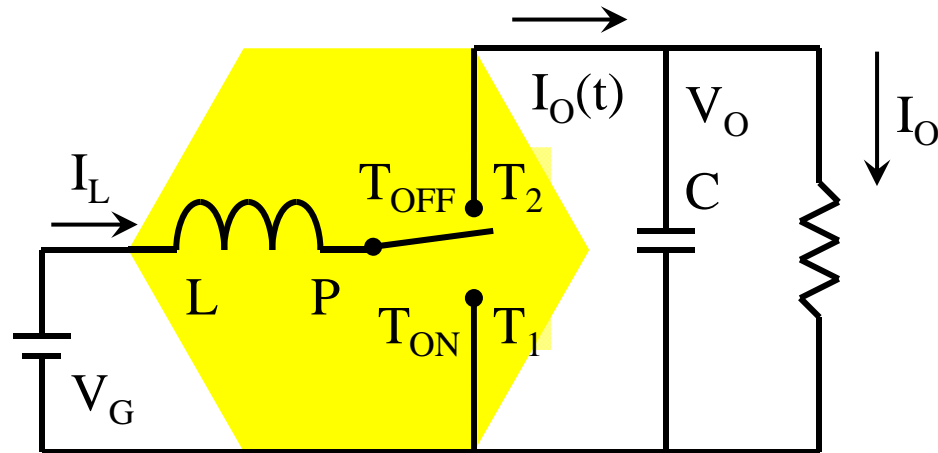

Capacitor Charge Balance

Switched Mode Power Conversion


Boost Converter

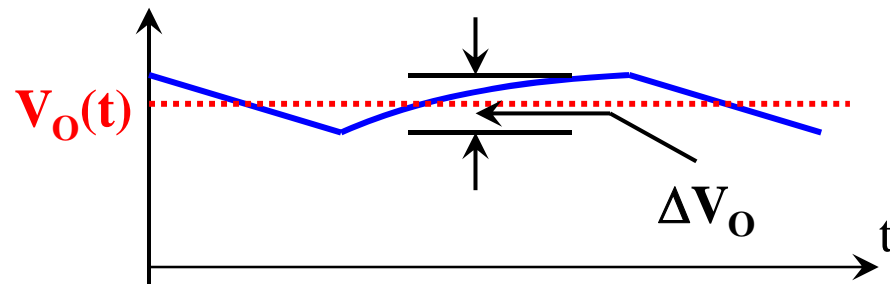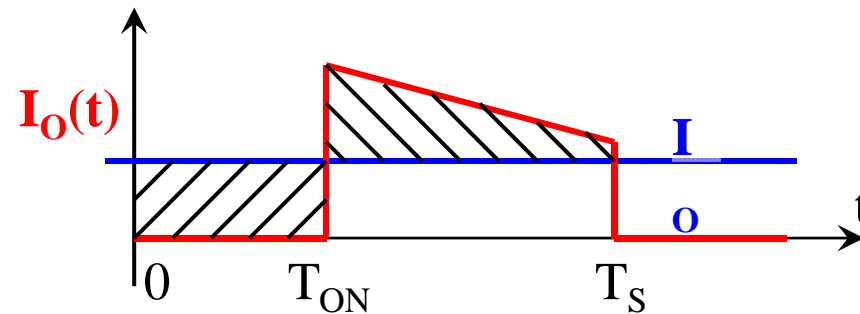

Capacitor Charge Balance

Switched Mode Power Conversion

Boost Converter

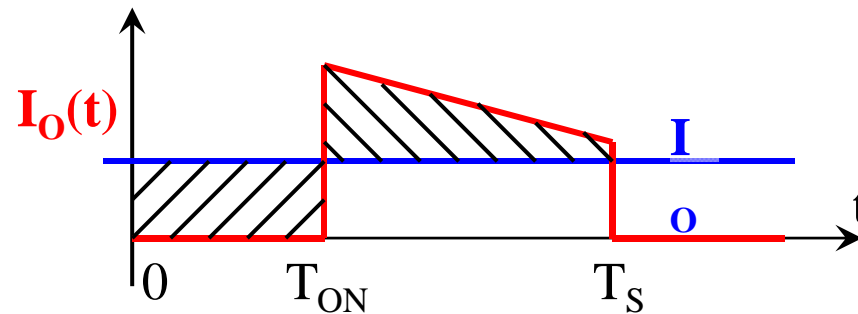


$$\Delta V_o = \frac{I_o D T_s}{C} = \frac{V_o D T_s}{R C}$$

Capacitor Charge Balance

Switched Mode Power Conversion

Boost Converter

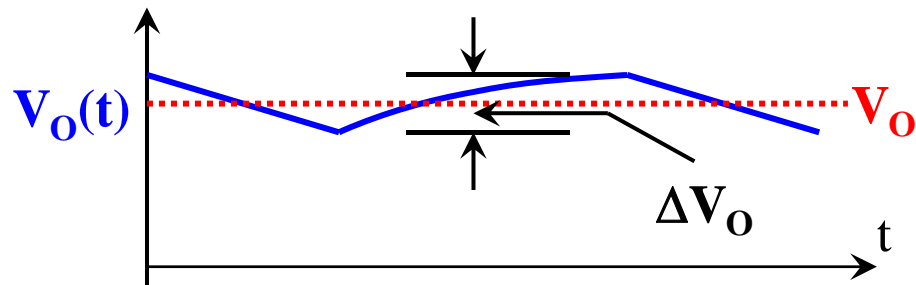

$$\frac{\Delta V_o}{V_o} = \frac{DT_s}{RC}$$

Design Guideline: $T_s \ll RC$

Capacitor Charge Balance

Switched Mode Power Conversion

Boost Converter

Ideal Voltage Gain

$$\frac{V_O}{V_G} = \frac{T_s}{T_{OFF}} = \frac{1}{1-D}$$

Switched Mode Power Conversion

Boost Converter

Ideal Voltage Gain

Ideal Current Gain

$$\frac{I_G}{I_O} = \frac{T_S}{T_{OFF}} = \frac{1}{1-D}$$

Switched Mode Power Conversion

Boost Converter

Ideal Voltage Gain

Ideal Current Gain

Current Ripple

$$\frac{\Delta I_L}{I_L} = \frac{(1-D)^2}{(L/R)} DT_s$$

Switched Mode Power Conversion

Boost Converter

Ideal Voltage Gain

Ideal Current Gain

Current Ripple

Voltage Ripple

$$\frac{\Delta V_o}{V_o} = \frac{D T_s}{R C}$$

Switched Mode Power Conversion

Boost Converter

Ideal Voltage Gain

Ideal Current Gain

Current Ripple

Voltage Ripple

Real Voltage Gain

$$\frac{V_O}{V_G} = \frac{1}{(1-D)} \frac{1}{\left(1 + \frac{\alpha}{(1-D)^2}\right)}$$

$$\frac{V_O}{V_G} = \frac{1}{1-D} \left(1 - \frac{DV_T}{V_G} - \frac{(1-D)V_D}{V_G}\right)$$

Switched Mode Power Conversion

Boost Converter

Ideal Voltage Gain

Ideal Current Gain

Current Ripple

Voltage Ripple

Real Voltage Gain

Real Current Gain

$$\frac{I_G}{I_O} = \frac{T_S}{T_{OFF}} = \frac{1}{1-D}$$

Switched Mode Power Conversion

Boost Converter

Ideal Voltage Gain

Ideal Current Gain

Current Ripple

Voltage Ripple

Real Voltage Gain

Real Current Gain

Efficiency

$$\eta = \frac{(1-D)^2}{((1-D)^2 + \alpha)}$$

$$\eta = \left(1 - \frac{DV_T}{V_G} - \frac{(1-D)V_D}{V_G} \right)$$

Switched Mode Power Conversion

Boost Converter

Ideal Voltage Gain

Ideal Current Gain

Current Ripple

Voltage Ripple

Real Voltage Gain

Real Current Gain

Efficiency

Preferred Operating Range

$$0 \leq D \leq (1 - \sqrt{\alpha}); \quad \alpha = R_1 / R$$

Switched Mode Power Conversion

Buck-Boost Converter

